

ECE 205 “Electrical and Electronics Circuits”

Spring 2024 – LECTURE 10

MWF – 12:00pm

Prof. Umberto Ravaioli

2062 ECE Building

Lecture 10 – Summary

Learning Objectives

1. More practice with equivalent circuits
2. The maximum power transfer theorem

Quiz #1 on February, 12 to 14

To-date: 30 students do not have CBTF reservation!

No Class on Monday 2/12/2024

Practice Problems videos (links on Canvas Modules):

Resistor Circuits Review (Week 2 – Lecture 3)


Guided Solution Worksheet 2 (Week 3 – Lecture 6)

Practice Problems on Node method (Week 3 – Lecture 8)

Practice Problems on Equivalent Circuits + WS#3 (Week 4 – Lecture 9)

Practice Problem 3 – Find Thevenin equivalent

$$V_T = V_A - V_B$$

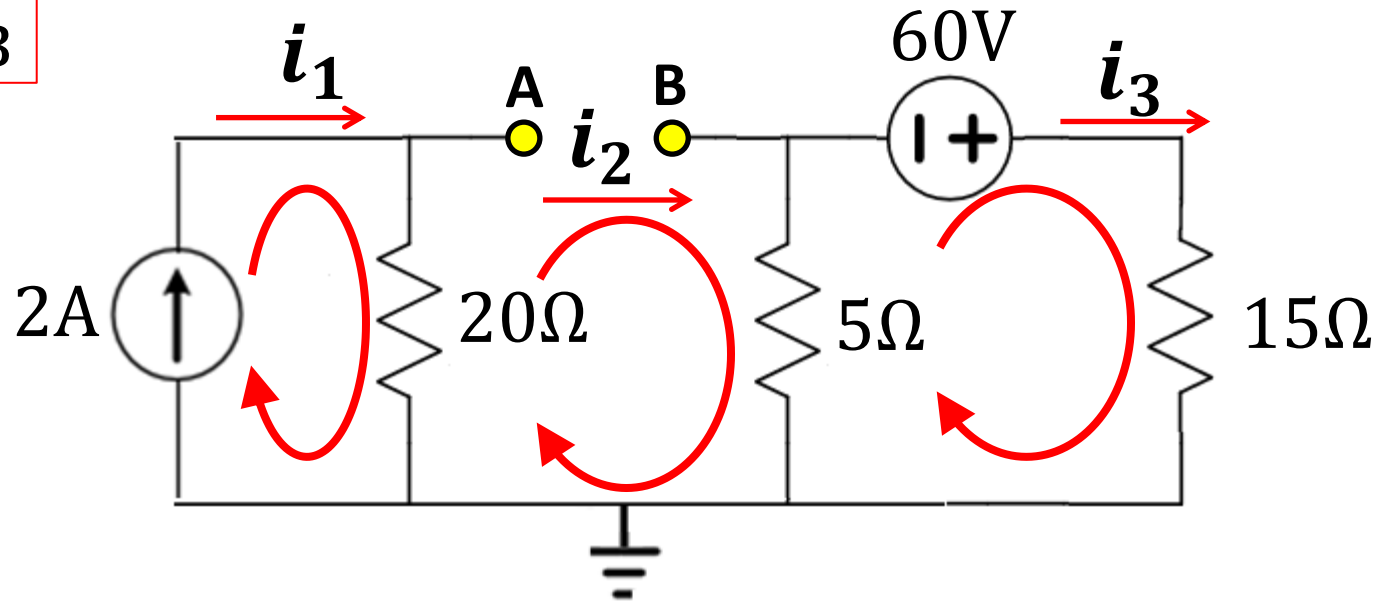


Loop 2

$$i_2 = 0$$

Loop 1

$$i_1 = 2A$$

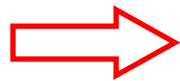

$$V_A = 20\Omega \times 2A = 40V$$


Loop 3

$$60V = 15\Omega i_3 + 5\Omega i_3 \Rightarrow i_3 = 3A$$

$$V_B = -60 + 15\Omega \times 3A = -15V \quad \text{or} \quad V_B = -5\Omega \times 3A = -15V$$


$$V_T = V_A - V_B = 40 - (-15) = 55V$$

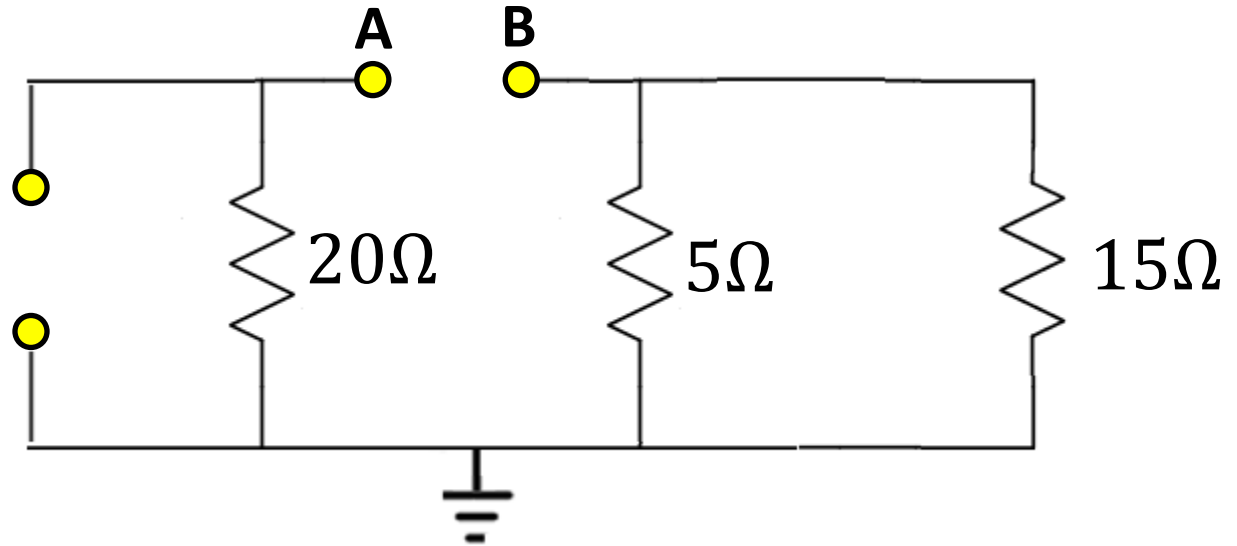Practice Problem 3 – Find Thevenin equivalent




$$R_{eq} = R_T = 20\Omega + 15\Omega // 5\Omega = 20\Omega + 3.75\Omega$$

$$R_T = 23.75\Omega$$

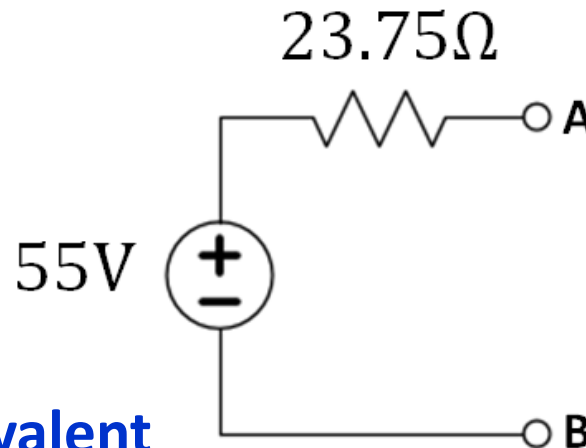

Thevenin equivalent

Practice Problem 4 – Repeat #2 for Norton equivalent

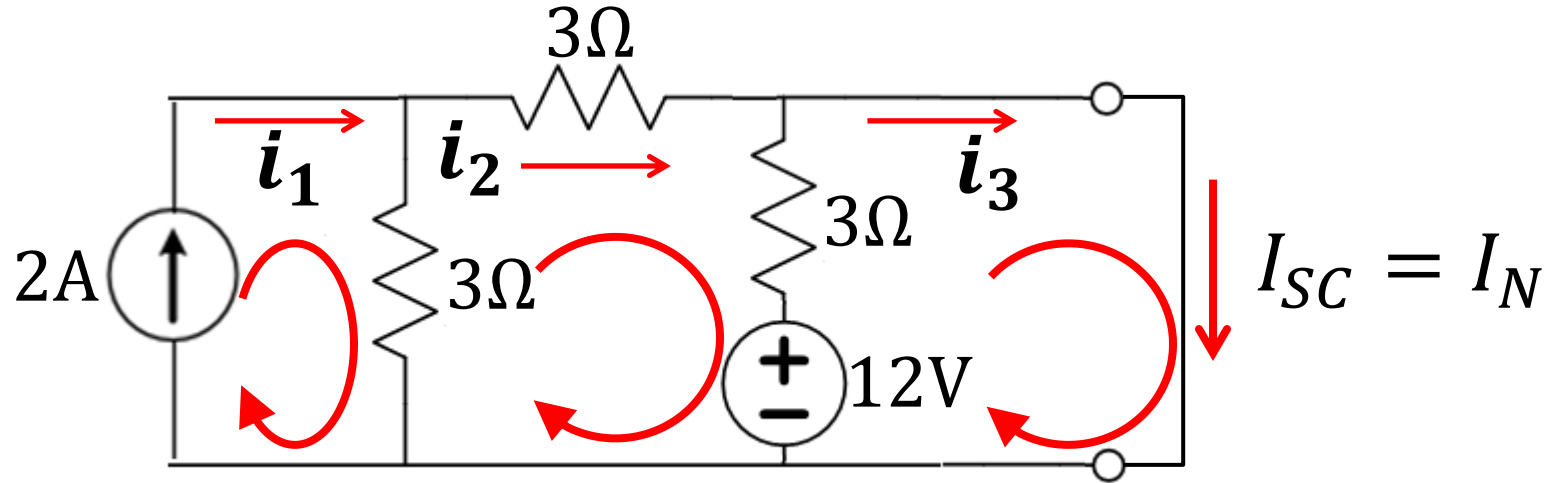

Loop 1

$$i_1 = 2A$$

Loop 2

$$3\Omega i_2 + 3\Omega(i_2 - i_3) + 12V + 3\Omega(i_2 - 2A) = 0$$


$$\Rightarrow 9\Omega i_2 - 3\Omega i_3 = -6V \quad \textcircled{1}$$

Loop 3

$$-12V + 3\Omega(i_3 - i_2) = 0$$

$$\Rightarrow -3\Omega i_2 + 3\Omega i_3 = 12V \quad \textcircled{2}$$

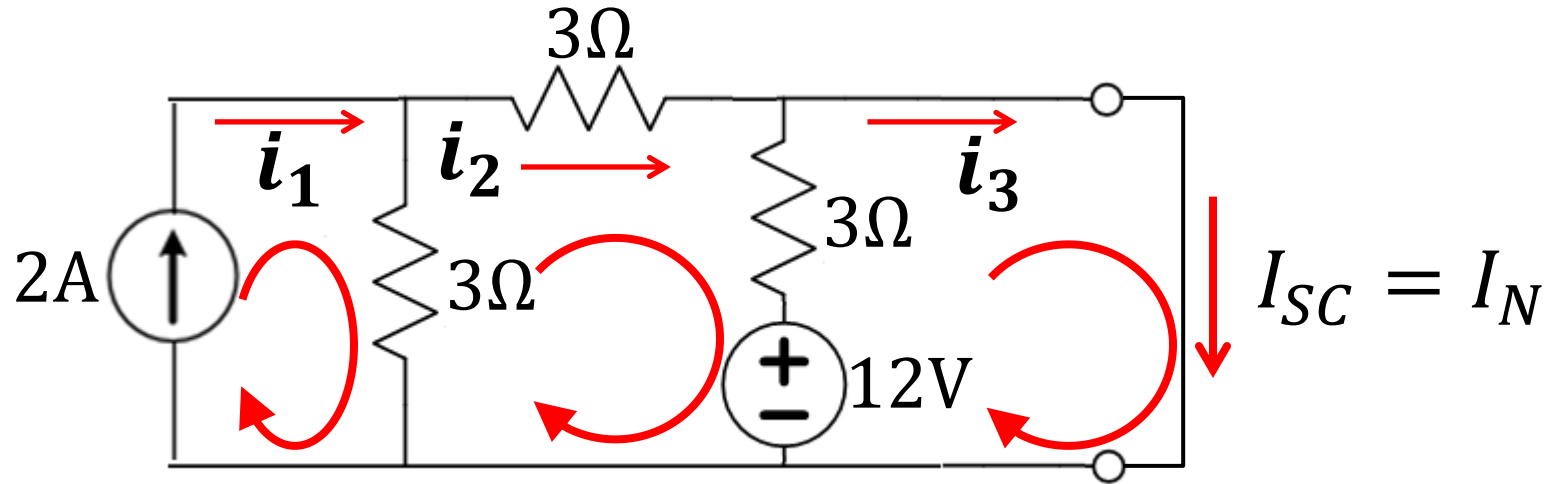
Practice Problem 4 – Repeat #2 for Norton equivalent



$$9\Omega i_2 - 3\Omega i_3 = -6V \quad \textcircled{1}$$


$$-3\Omega i_2 + 3\Omega i_3 = 12V \quad \textcircled{2}$$

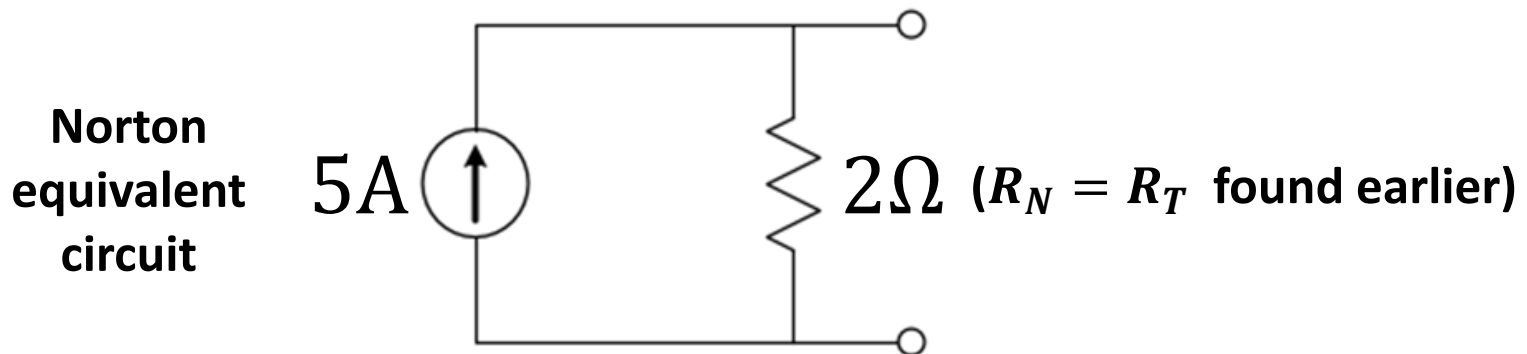Solving $\textcircled{1}$ & $\textcircled{2}$ \Rightarrow $i_2 = 1A$ $i_3 = I_N = 5A$




Practice Problem 4 – Only using source transformations


Transform to Thevenin source

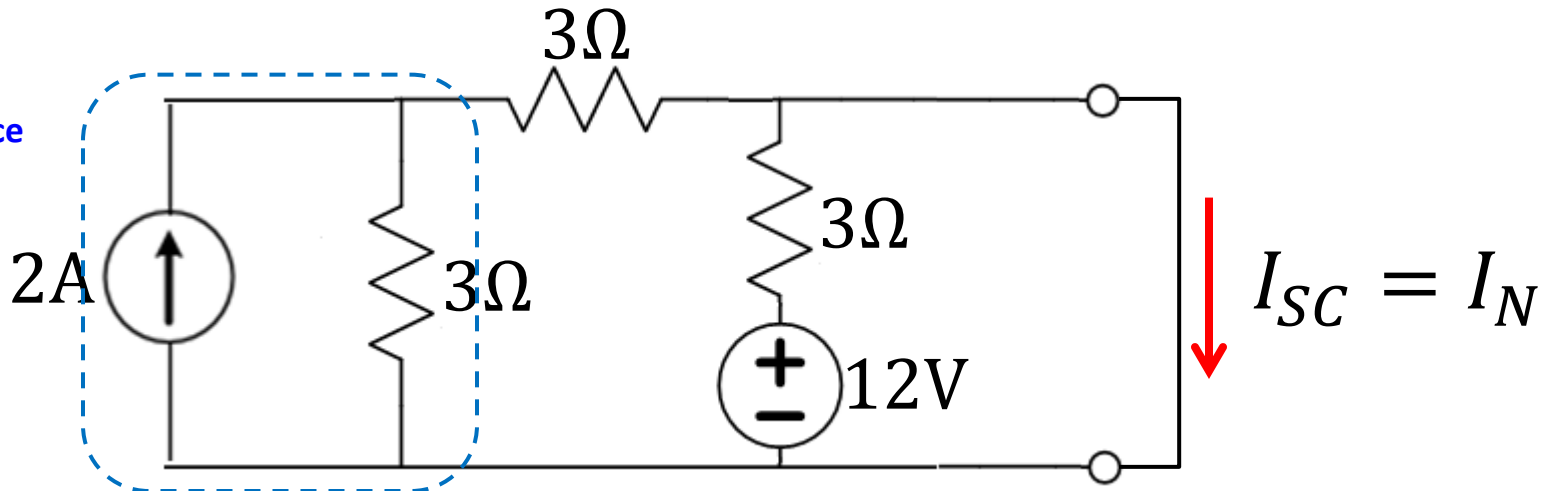


Add series resistors

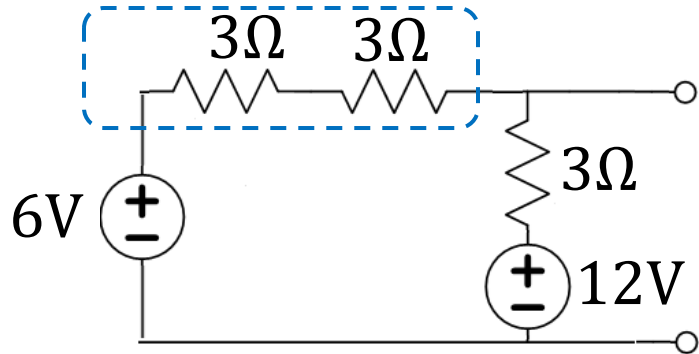


Transform to Norton source

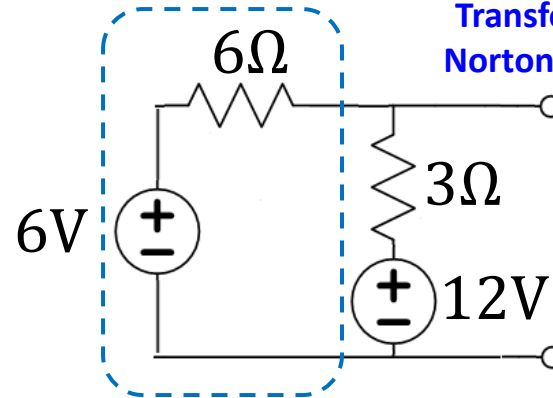


Transform to Norton source

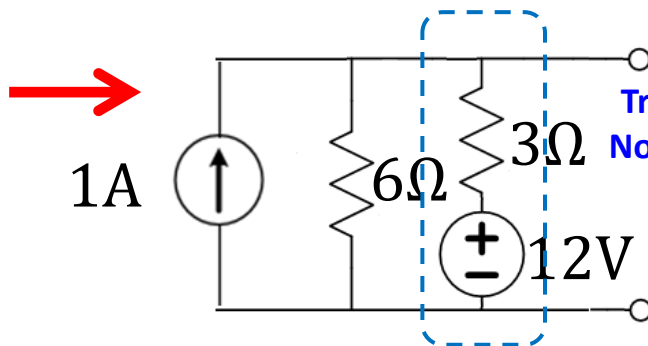

→

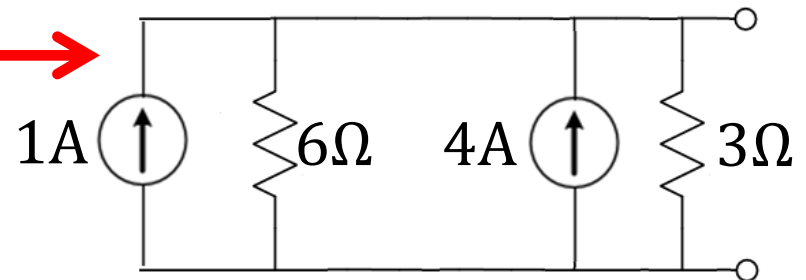


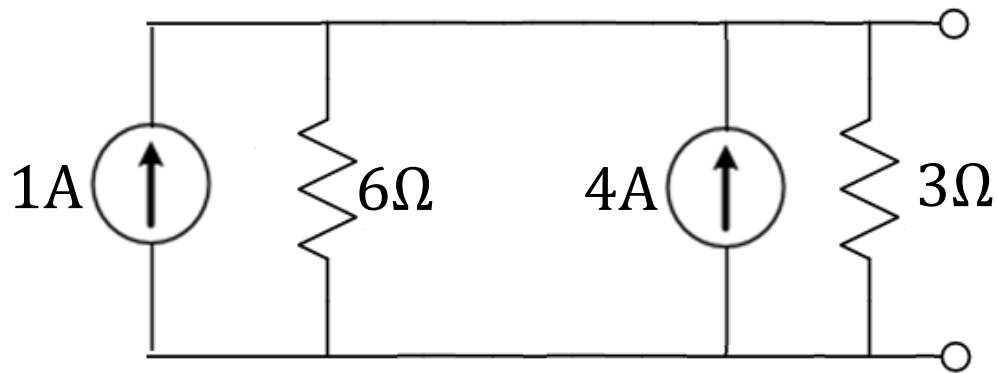

Rearrange order of elements





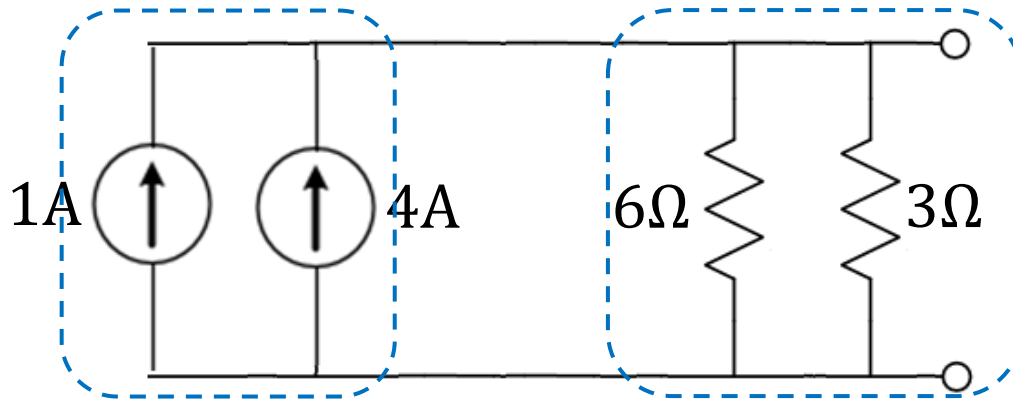Add current sources injecting into the same nodes




Combine parallel resistors

Norton equivalent circuit

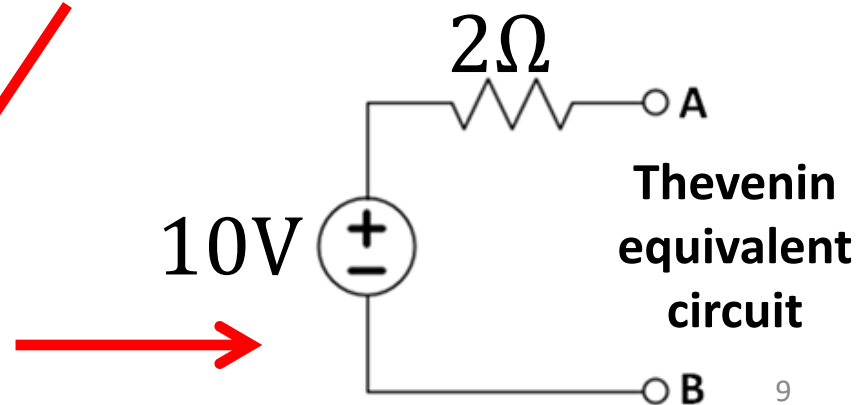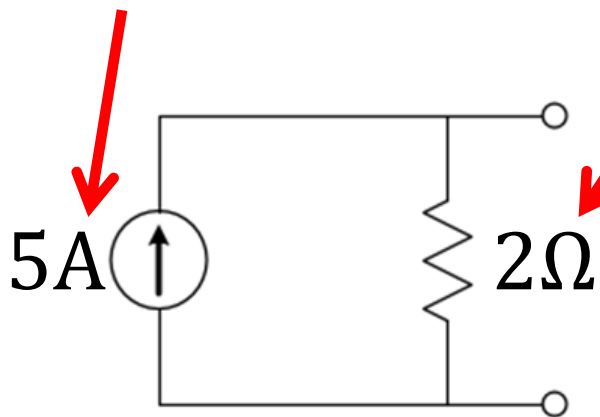


Maximum Power Transfer Theorem

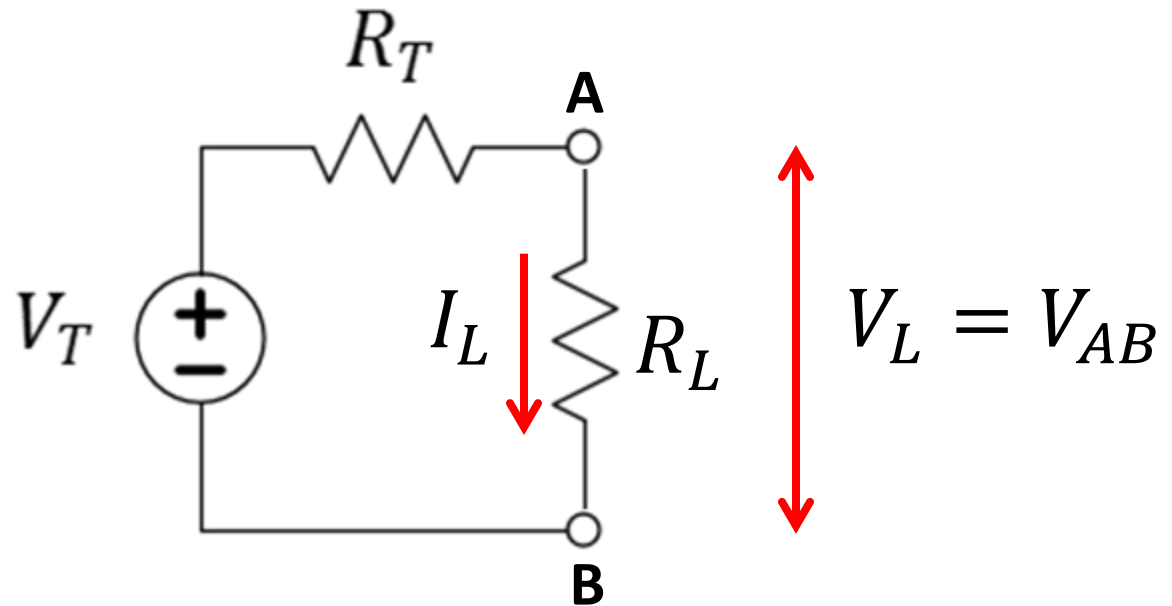

We would like to find for what load resistance R_L the power P_L transferred to R_L is maximum.


Remember: Power is

$$P_L = V_L I_L$$

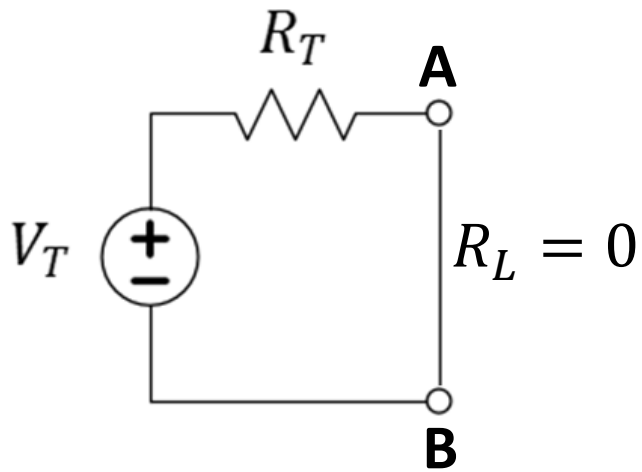


$$V_L = 0$$

$$P_L = 0$$

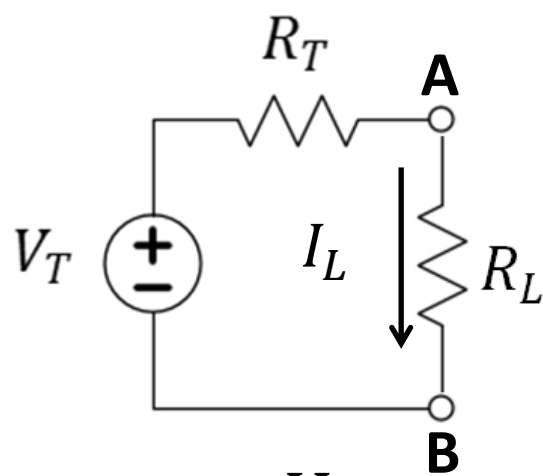

$$I_L = \frac{V_T}{R_T + R_L}$$


$$P_L = V_L I_L = R_L I_L^2$$

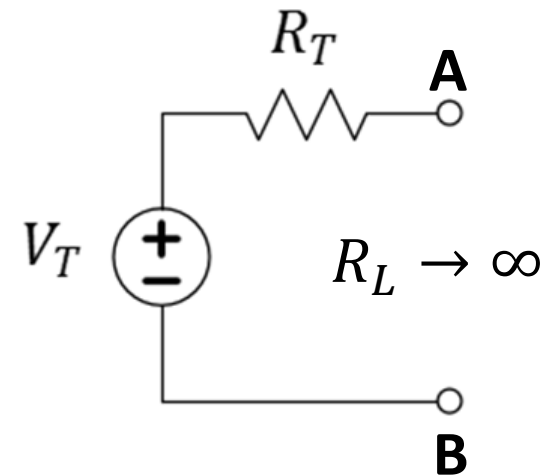

$$I_L = 0$$

$$P_L = 0$$



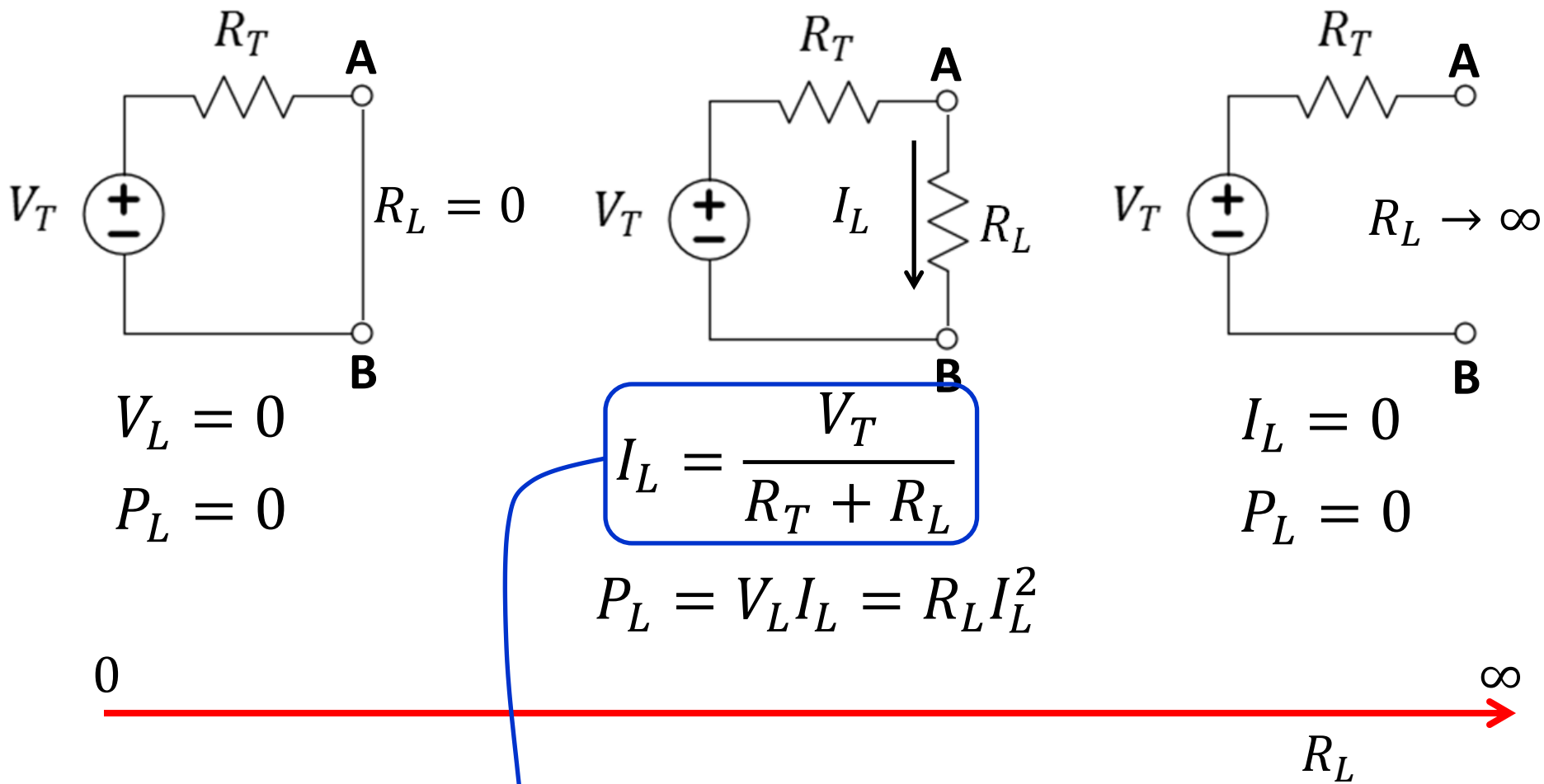

Maximum Power transfer when $R_L = R_T$ as required by

$$\frac{dP_L}{dR_L} = \frac{d}{dR_L} R_L I_L^2 = V_T^2 \frac{d}{dR_L} \left[\frac{R_L}{(R_T + R_L)^2} \right] = 0$$

Proof

$$\frac{d}{dR_L} \left[\frac{R_L}{(R_T + R_L)^2} \right] = 0$$

$$f(R_L) = R_L$$

$$g(R_L) = (R_T + R_L)^2$$

$$\frac{d}{dR_L} \left(\frac{f(R_L)}{g(R_L)} \right) = \frac{f'(R_L)g(R_L) - f(R_L)g'(R_L)}{g(R_L)^2}$$

$$\frac{d}{dR_L} \left[\frac{R_L}{(R_T + R_L)^2} \right] = \frac{(R_T + R_L)^2 - 2R_L(R_T + R_L)}{(R_T + R_L)^4} = 0$$


$$(R_T + R_L)^2 - 2R_L(R_T + R_L) = 0$$

$$(R_T + R_L) - 2R_L = 0$$



$$R_L = R_T$$

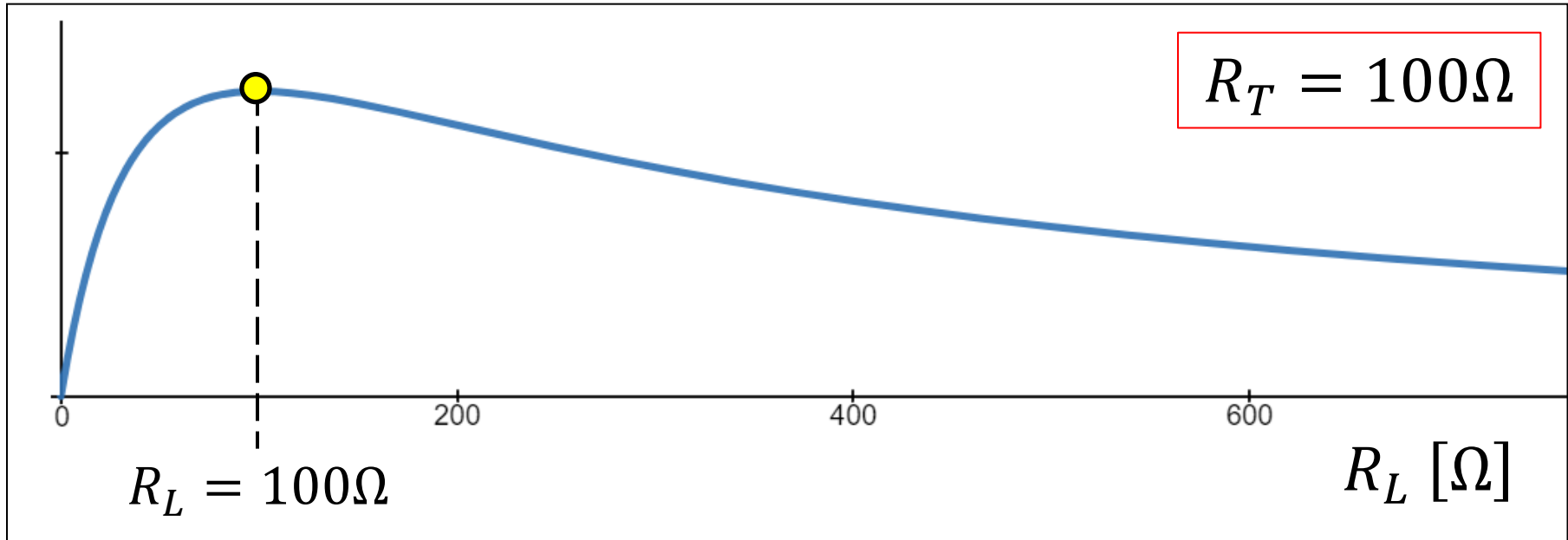Power transferred to load as a function of load resistance



In conditions of maximum power transfer, 50% of the power generated by the source is dissipated by the source resistance R_T and 50% by the load resistance R_L .