

ECE 205 “Electrical and Electronics Circuits”

Spring 2024 – LECTURE 11

MWF – 12:00pm

Prof. Umberto Ravaioli

2062 ECE Building


Lecture 11 – Summary

Learning Objectives

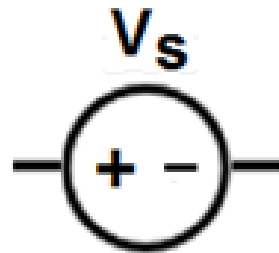
1. Introduction to “dependent” sources
2. Solution strategies with “loop” and “node” analysis

Independent Sources

These are sources whose behavior does not depend on the circuit they are connected to.




Voltage source

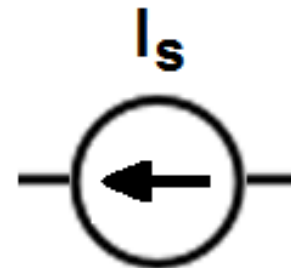


Current source


I-V Curves of ideal voltage sources

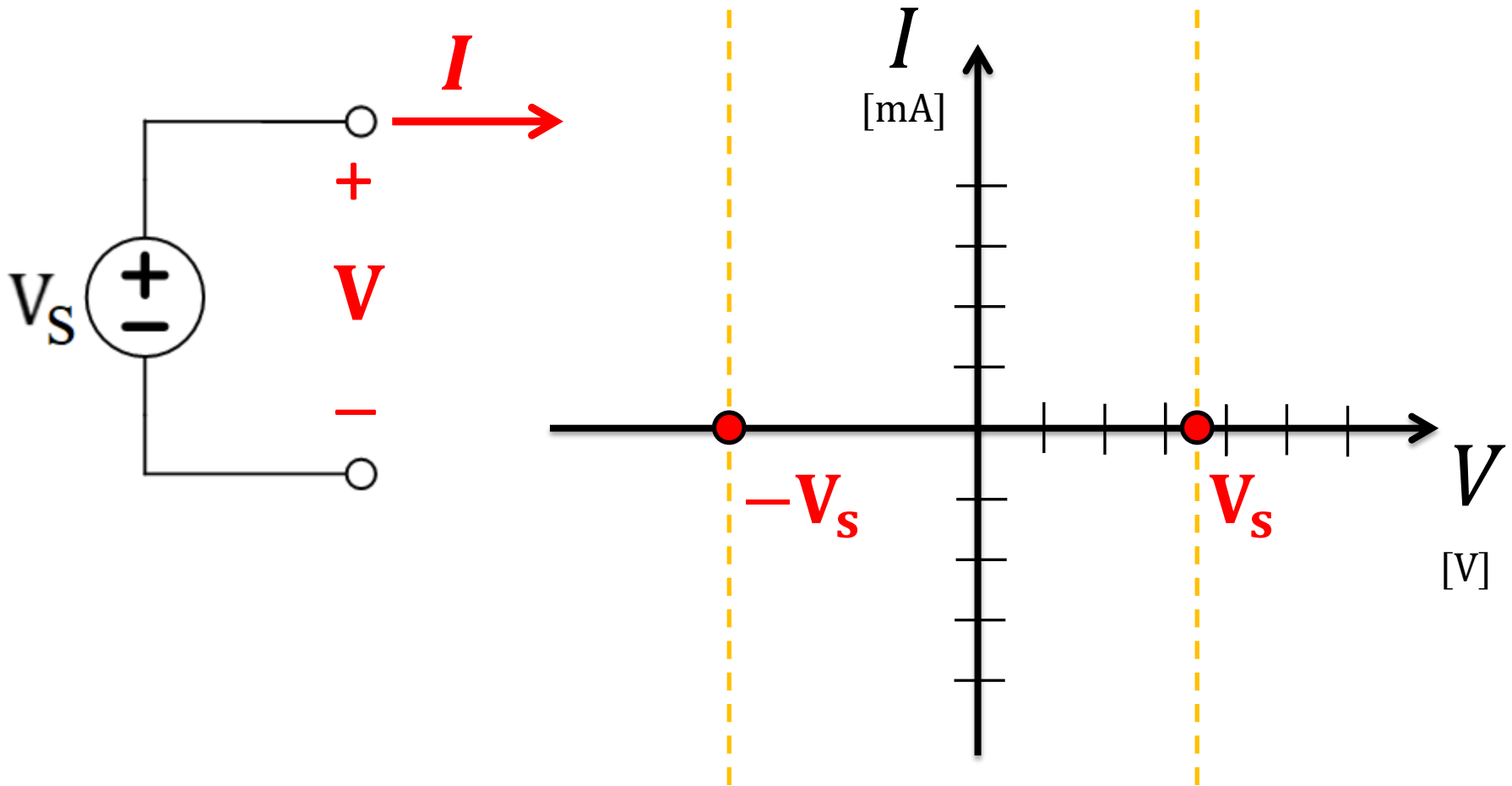


I-V Curve of a short circuit

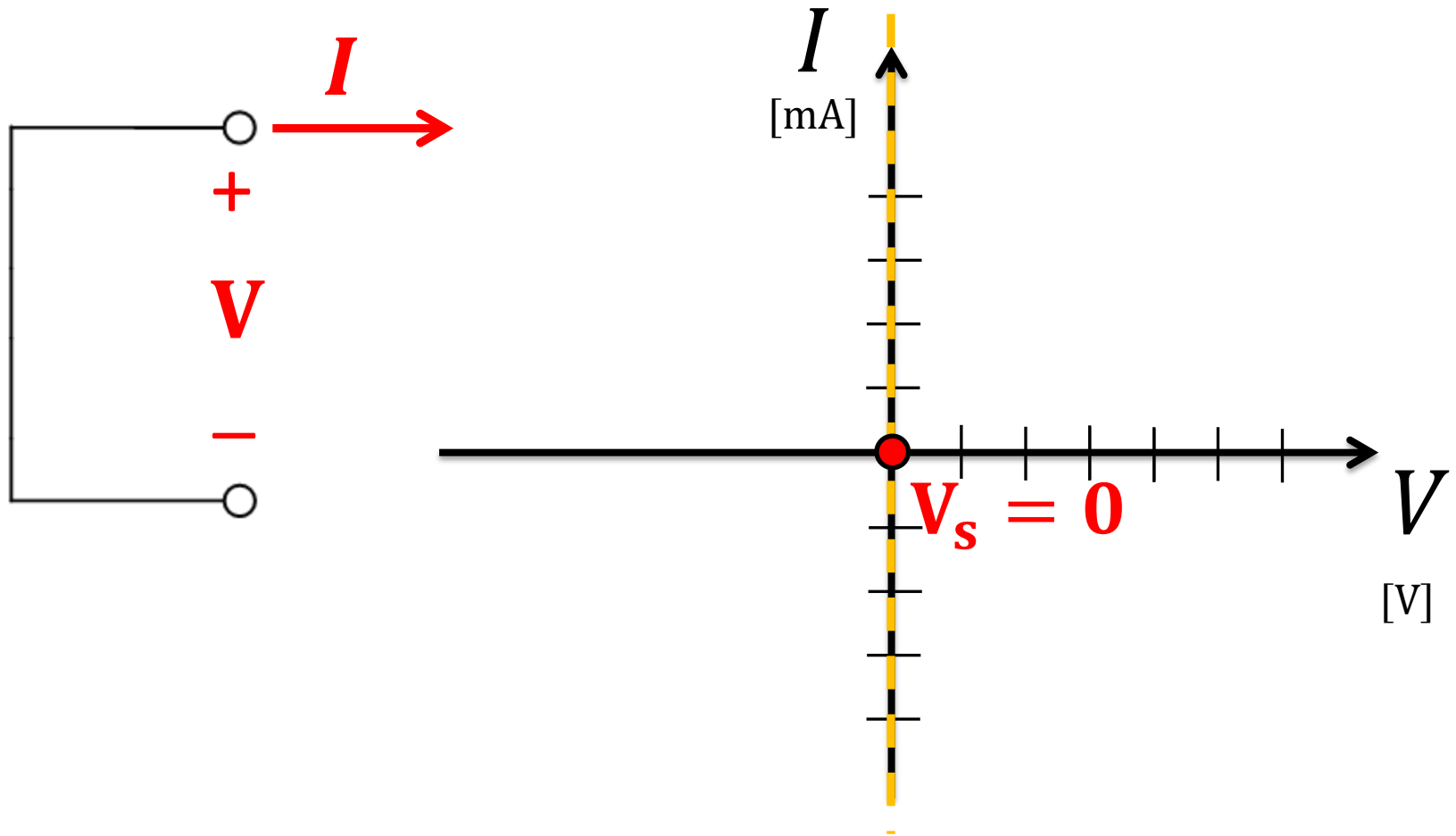

I-V Curves of ideal current sources


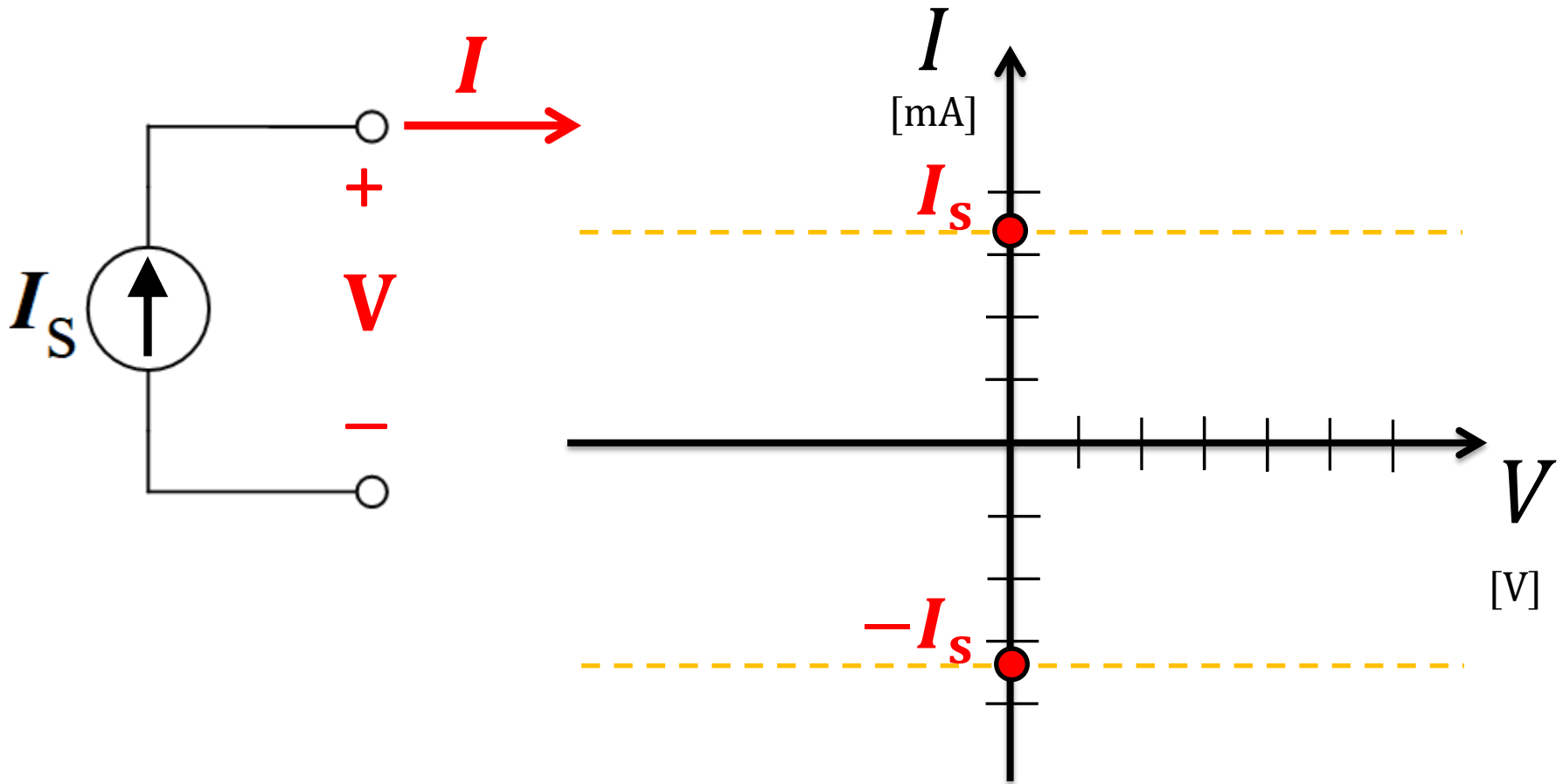


I-V Curve of an open circuit

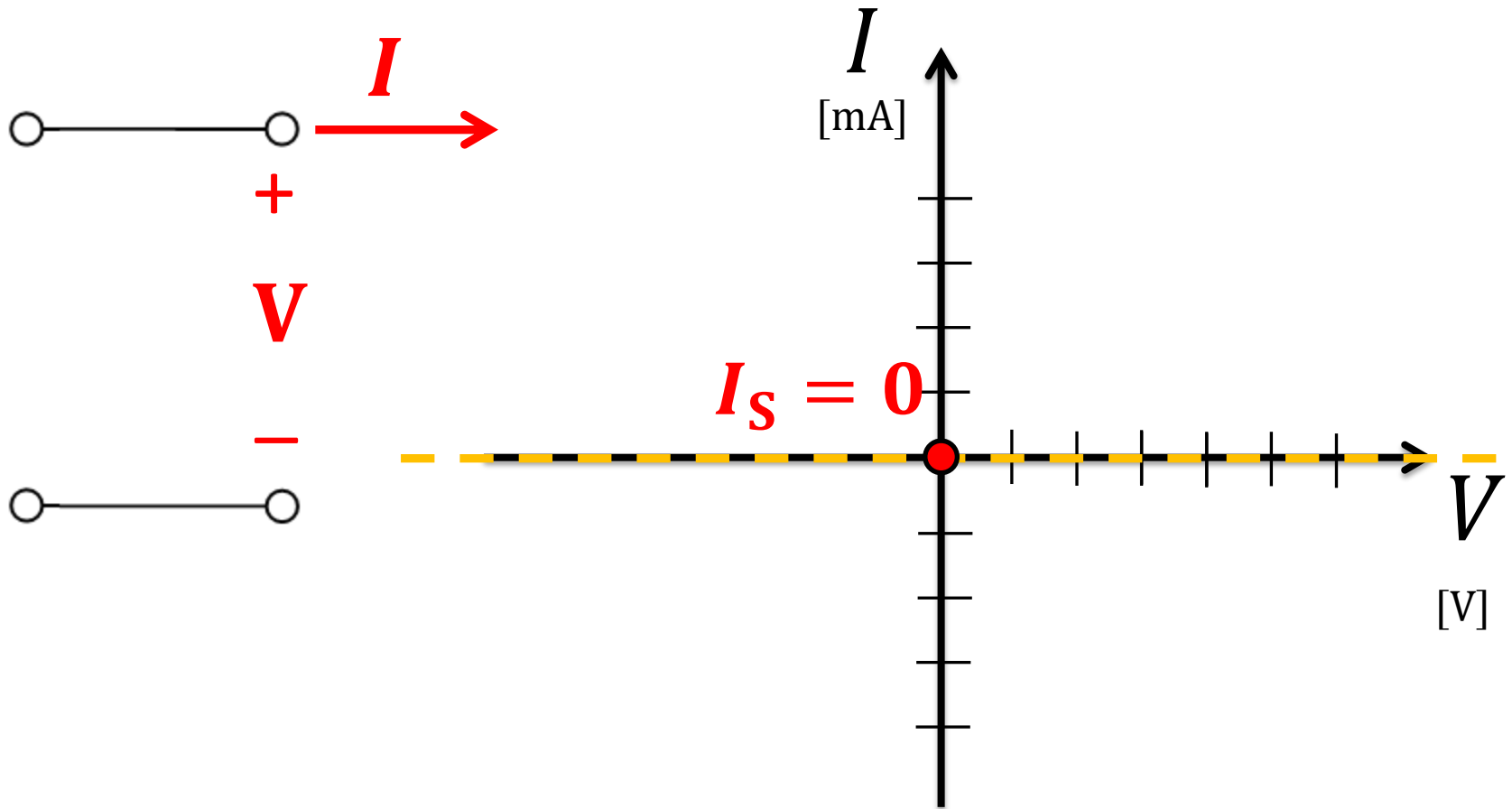

Dependent Sources

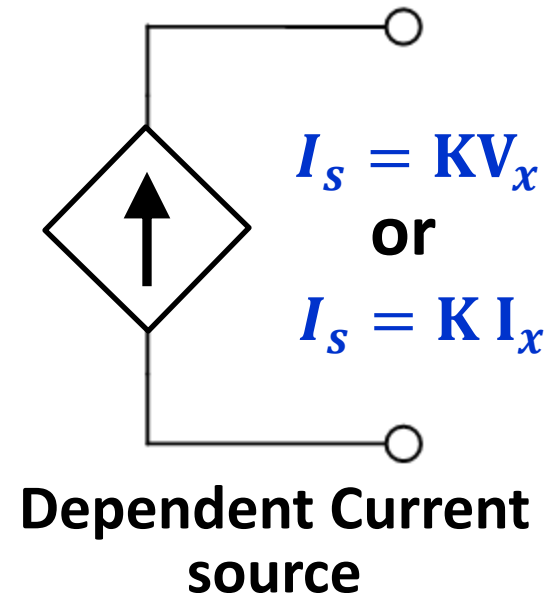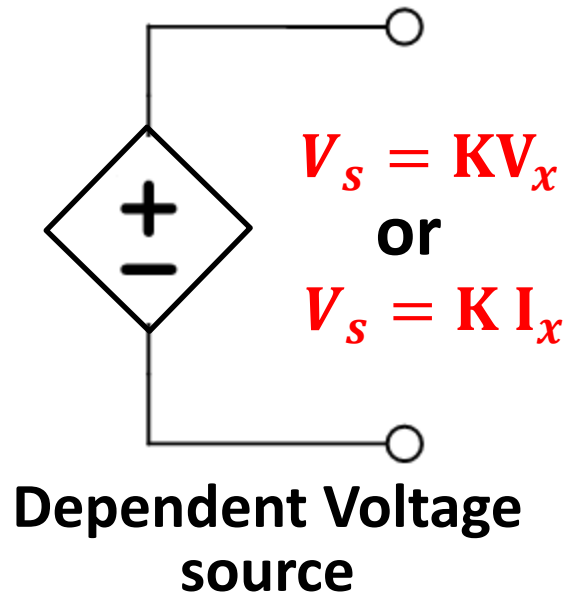These are sources which are “controlled” by a current or a voltage in another part of the circuit.



Common representations of dependent sources.
Other symbols may be used by practitioners.



Possible Configurations

We have the following types of dependent sources

- 1. Voltage Controlled Voltage Source (VCVS)**
- 2. Current Controlled Voltage Source (CCVS)**
- 3. Voltage Controlled Current Source (VCCS)**
- 4. Current Controlled Current Source (CCCS)**

Where do we find dependent sources?

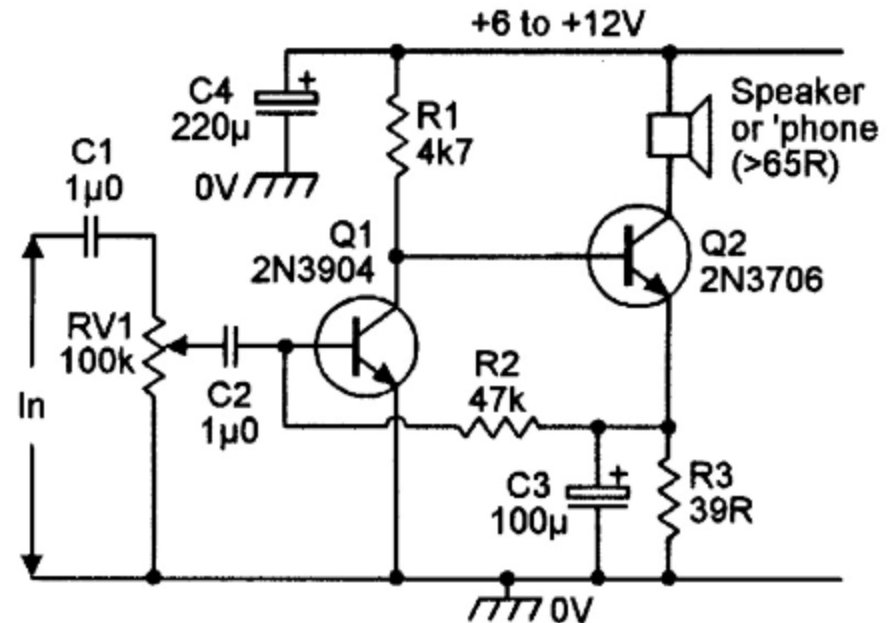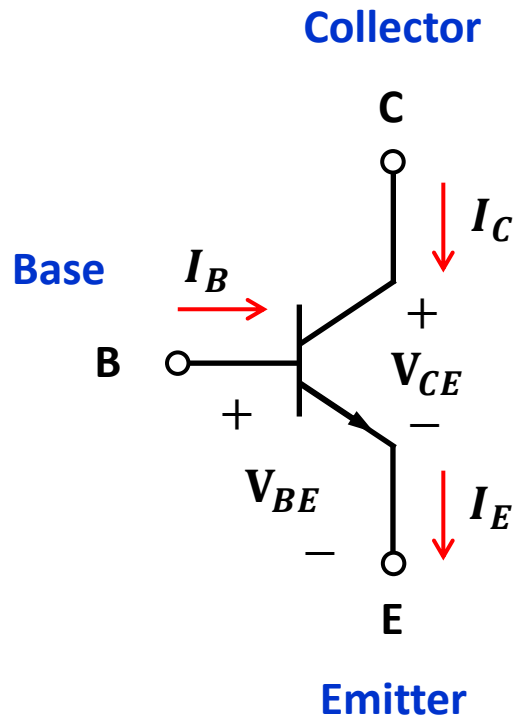Example: bipolar junction transistor (BJT)




n-p-n BJT transistor symbol


Basic low-power transistor audio amplifier circuit

Where do we find dependent sources?

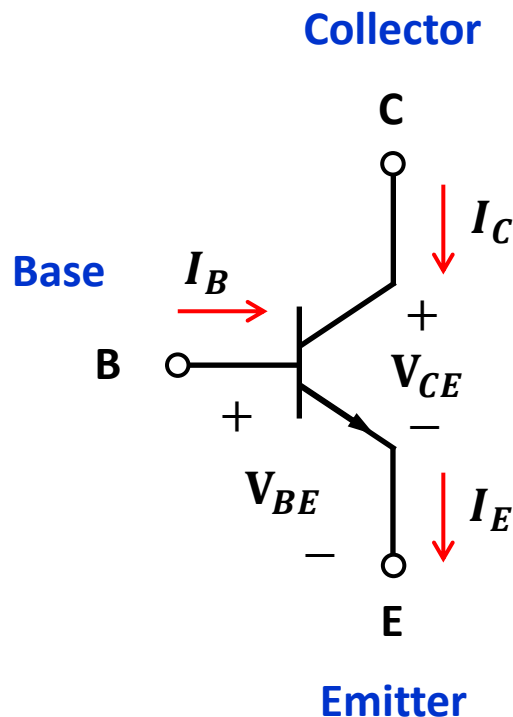Example: Simple DC equivalent circuit model of a bipolar transistor





n-p-n BJT transistor symbol

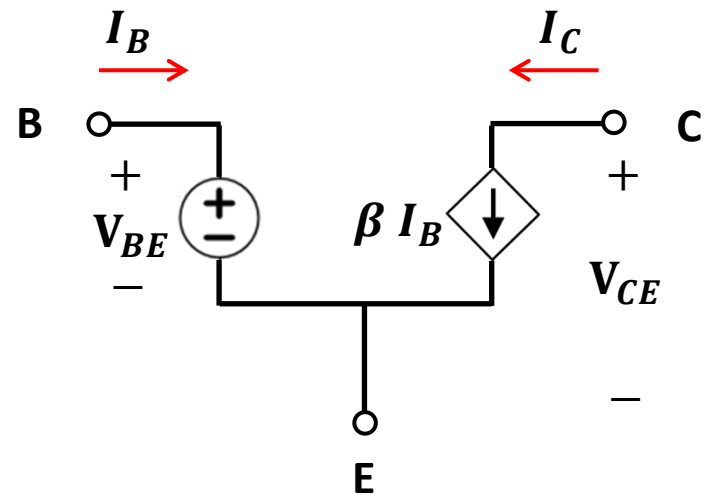


equivalent DC electrical circuit

Homework 4 PL – Problem 4

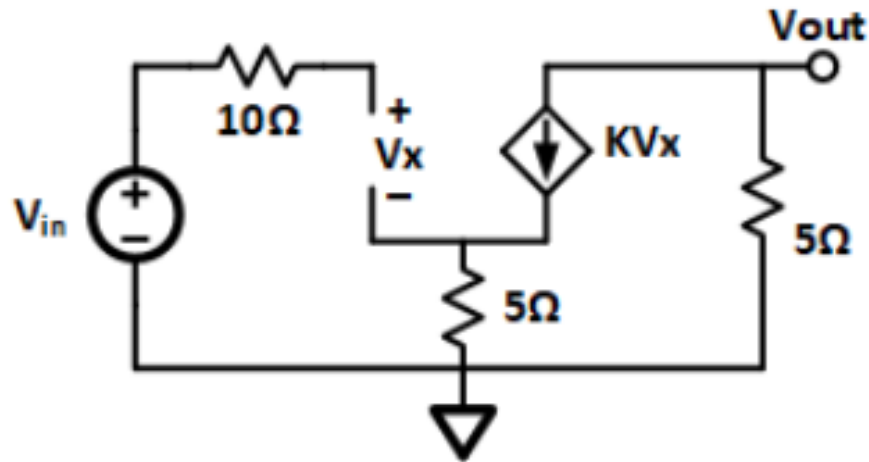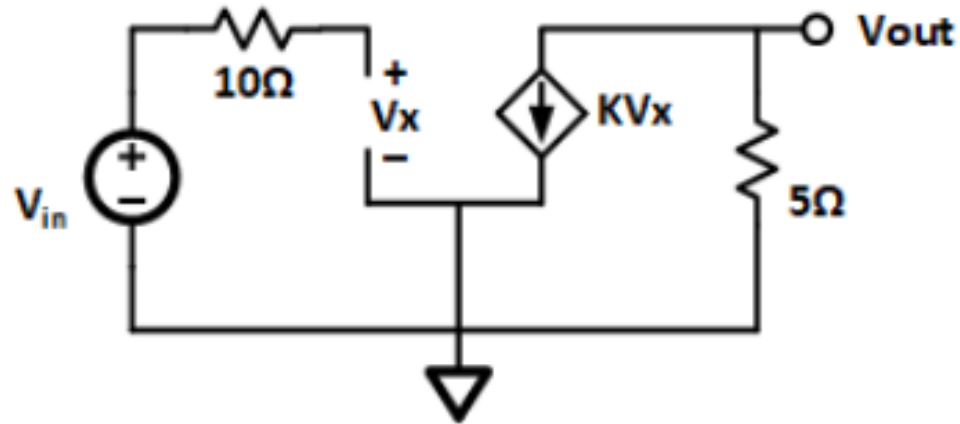


Homework 4 PL – Problem 4


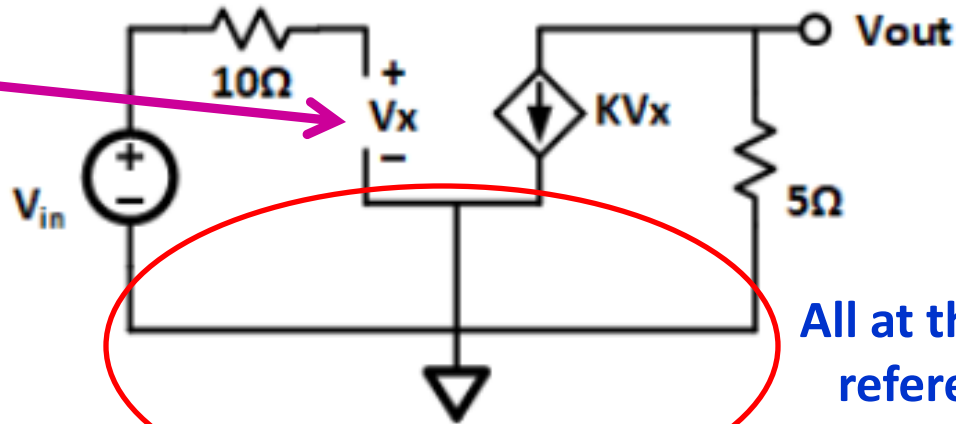
Open circuit,
no current
flows
(capacitive
structure)



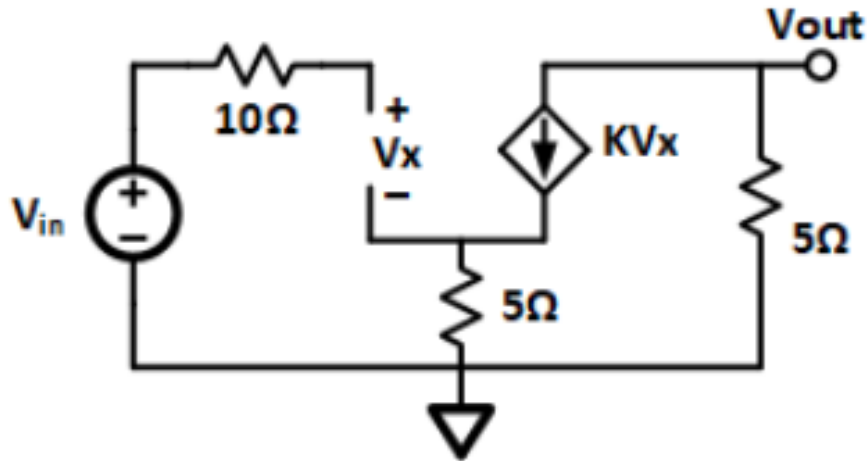All at the same ground
reference potential




Homework 4 PL – Problem 4

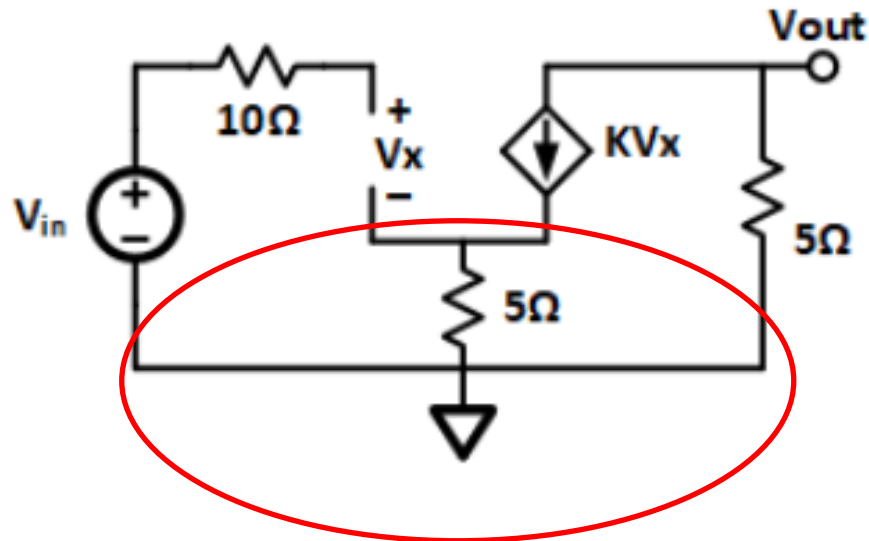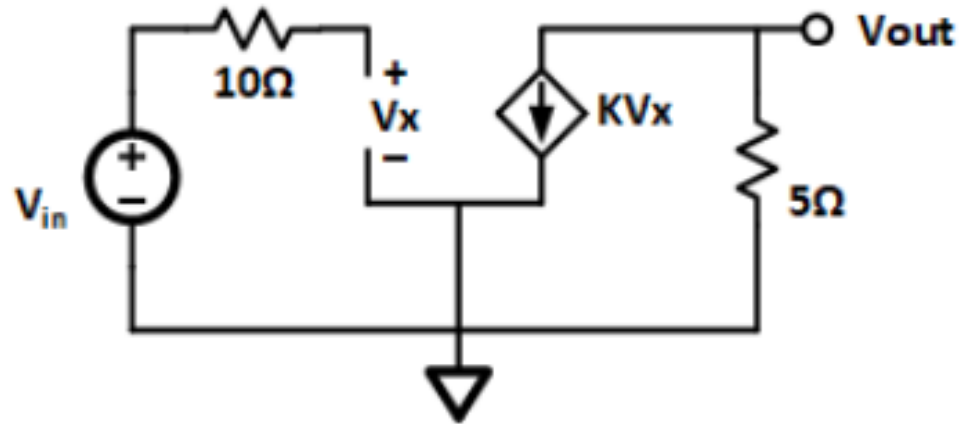

Additional resistor increases coupling between right and left sides of circuit


Example 1

Find the Voltage V_1

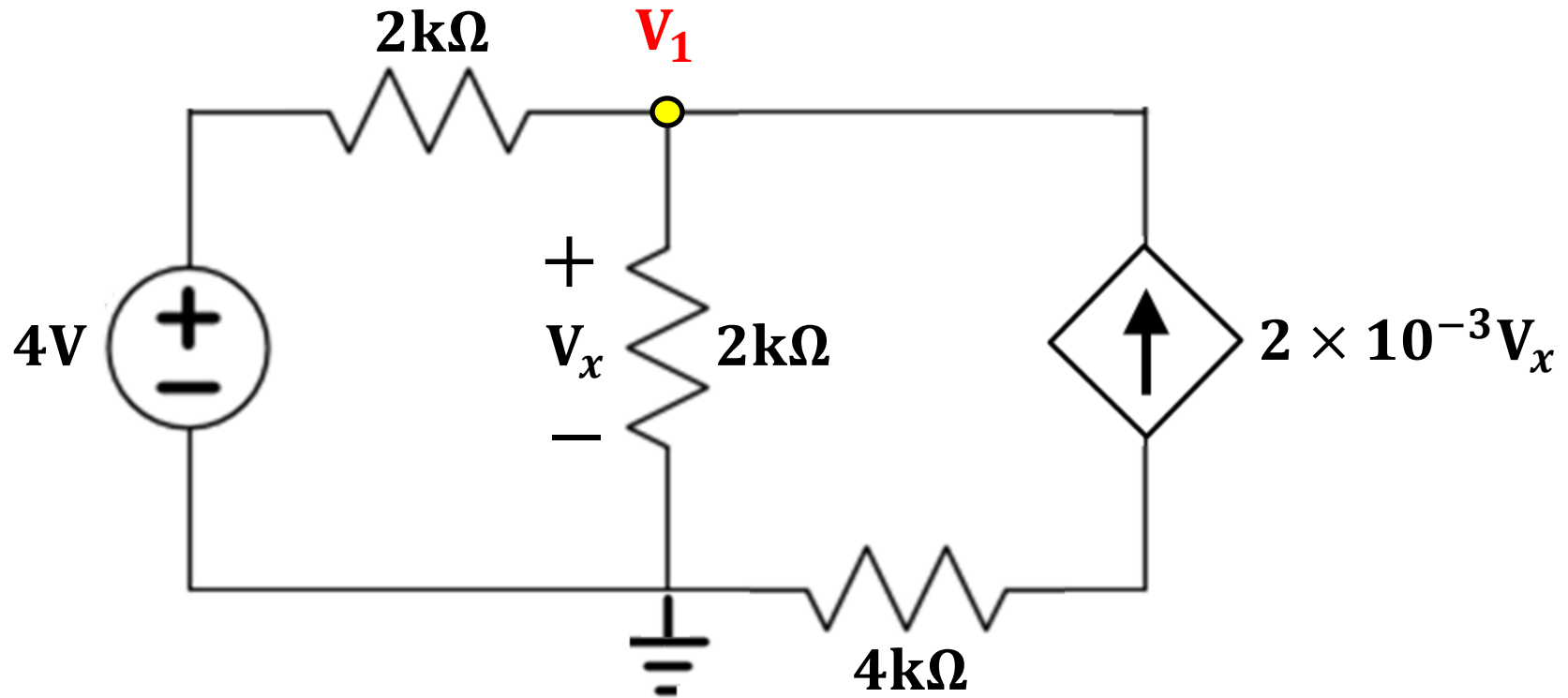


Example 1

Find the Voltage V_1

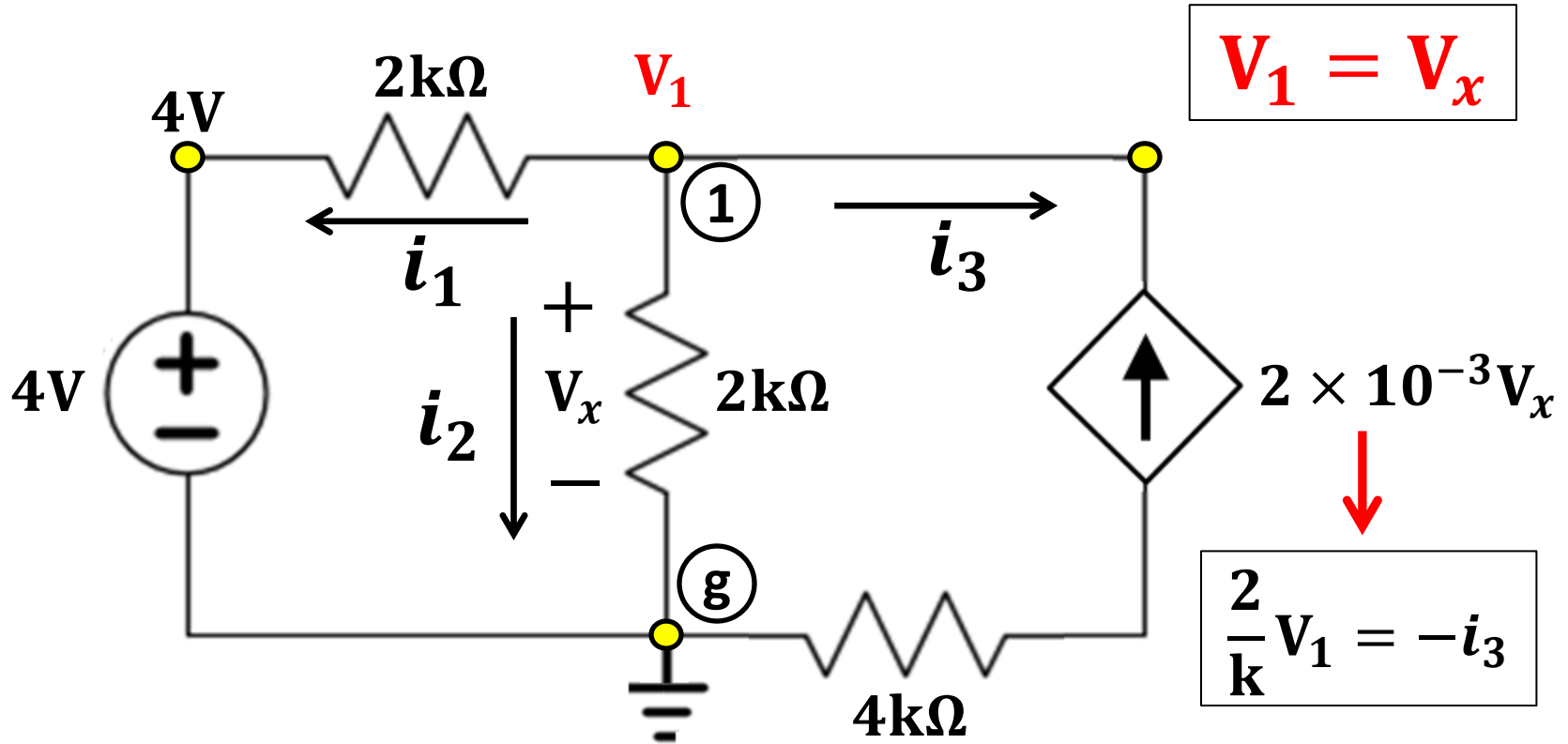

Example 1

Find the Voltage V_1

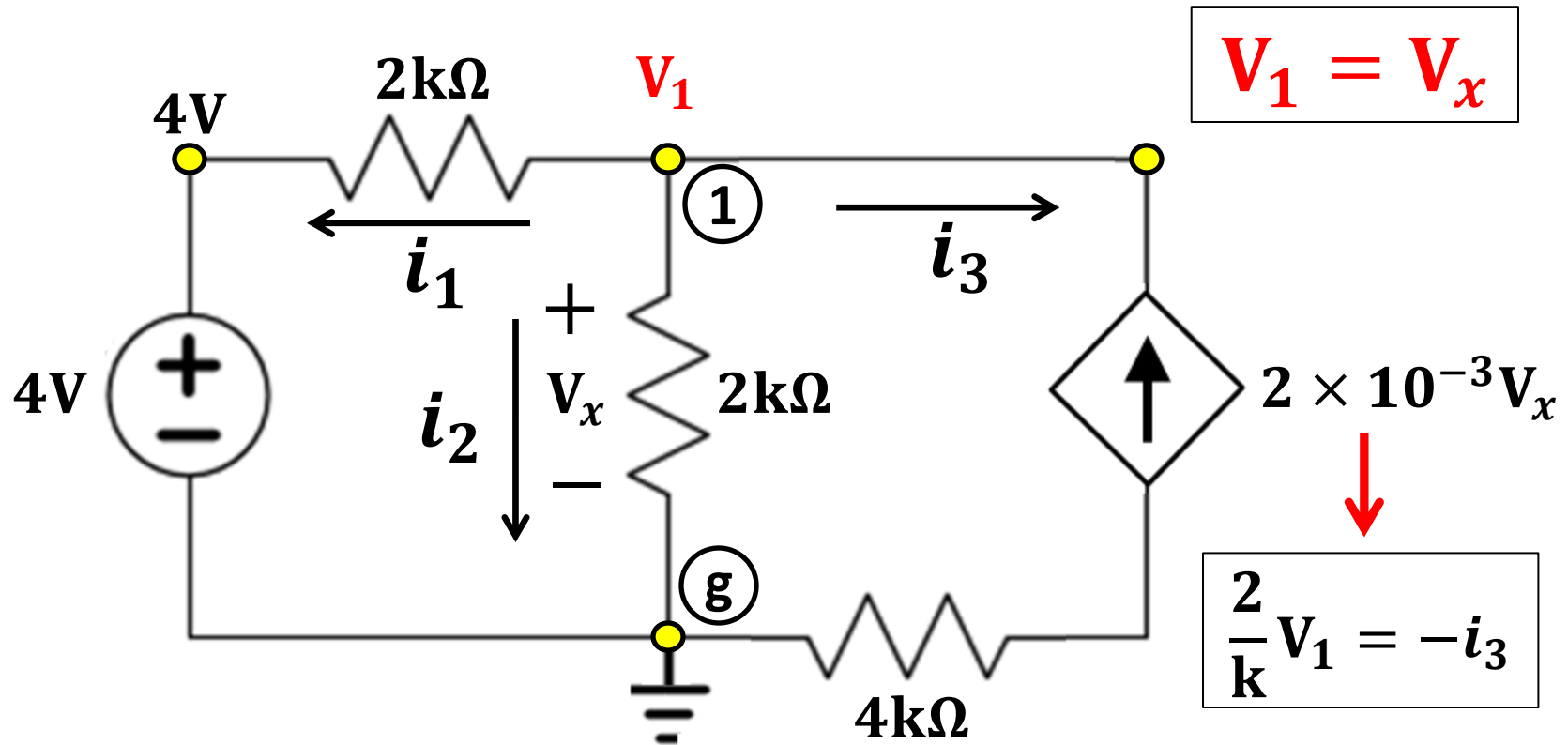


Node ① $\frac{V_1 - 4}{2k} + \frac{V_1}{2k} - \frac{2}{k} V_1 = 0 \rightarrow V_1 - 2V_1 = 2$

$i_1 + i_2 + i_3 = 0$

$V_1 = -2V$

Example 1

Find the Voltage V_1

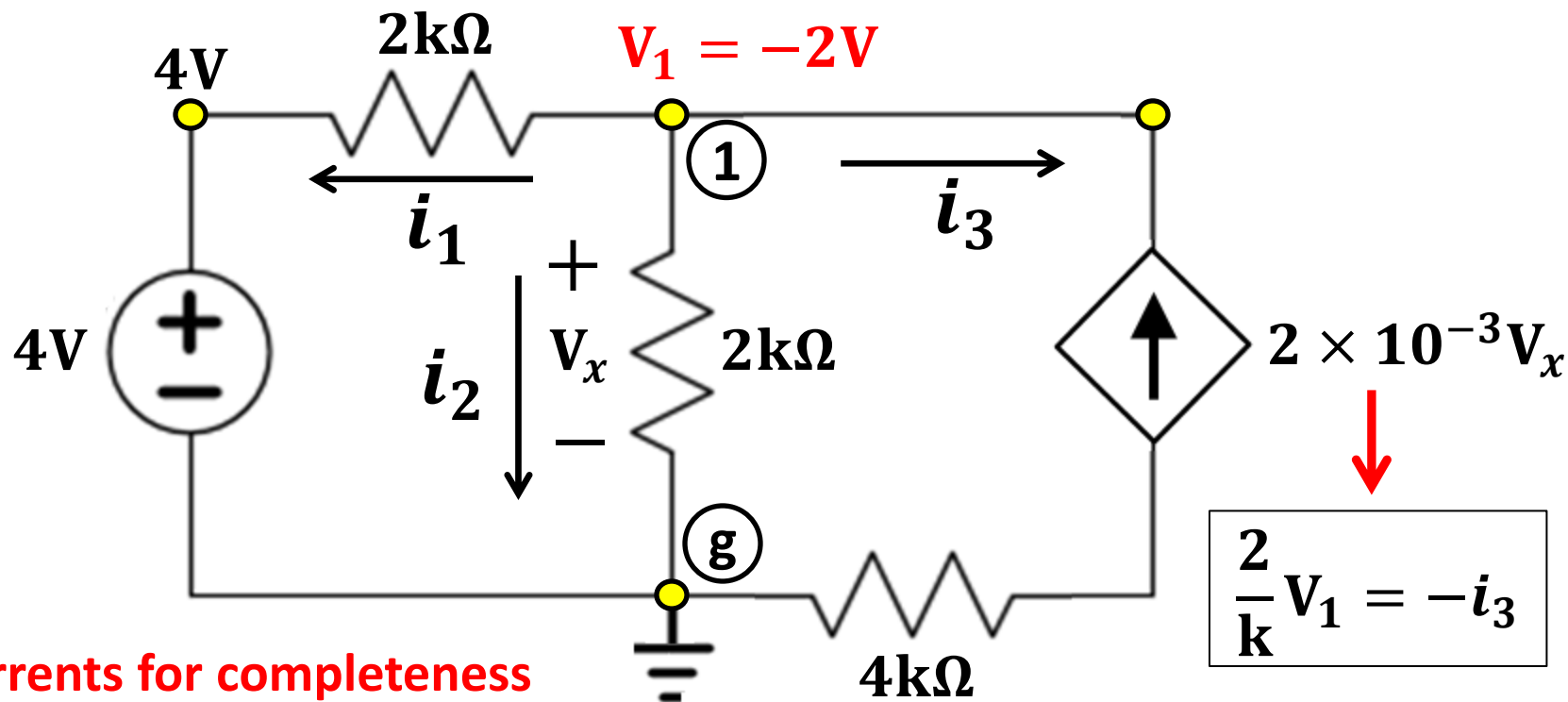

Find currents for completeness


$$i_1 = \frac{V_1 - 4}{2\text{k}} = \frac{-2 - 4}{2\text{k}} = -3\text{mA}$$

$$i_2 = \frac{V_1}{2\text{k}} = \frac{-2}{2\text{k}} = -1\text{mA}$$

$$i_3 = -i_1 - i_2 = 4\text{mA}$$

Example 1

Find the Voltage V_1

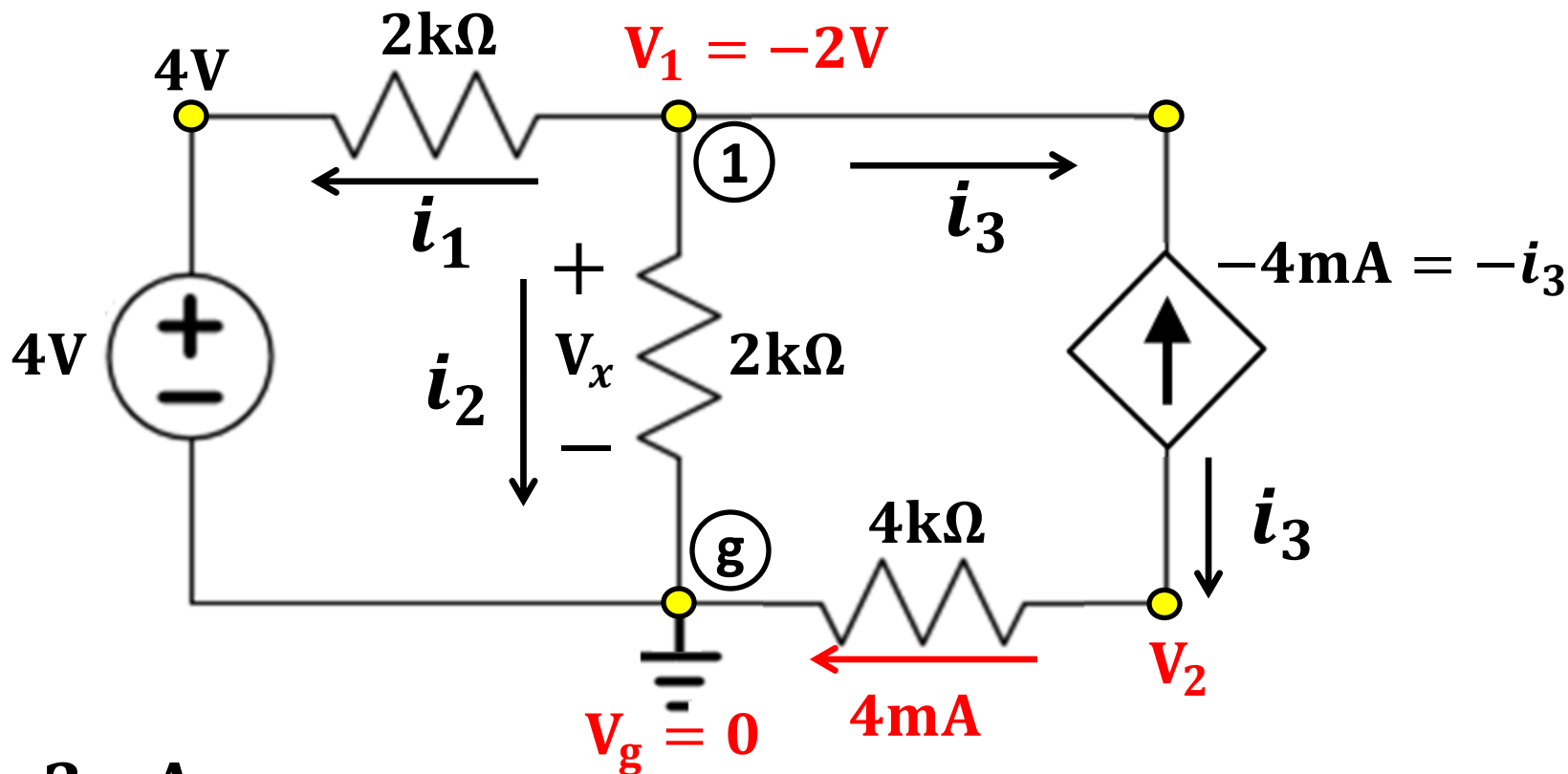

$$i_1 = -3\text{mA}$$

$$i_2 = -1\text{mA}$$

$$i_3 = 4\text{mA}$$

Across the 4kΩ resistor


$$V_2 - V_g = 4\text{k}\Omega \times 4\text{mA} = 16\text{V}$$

Across the current source

$$V_2 - V_1 = 16 - (-2) = 18\text{V}$$

Example 2


Find the currents i_x and i_y

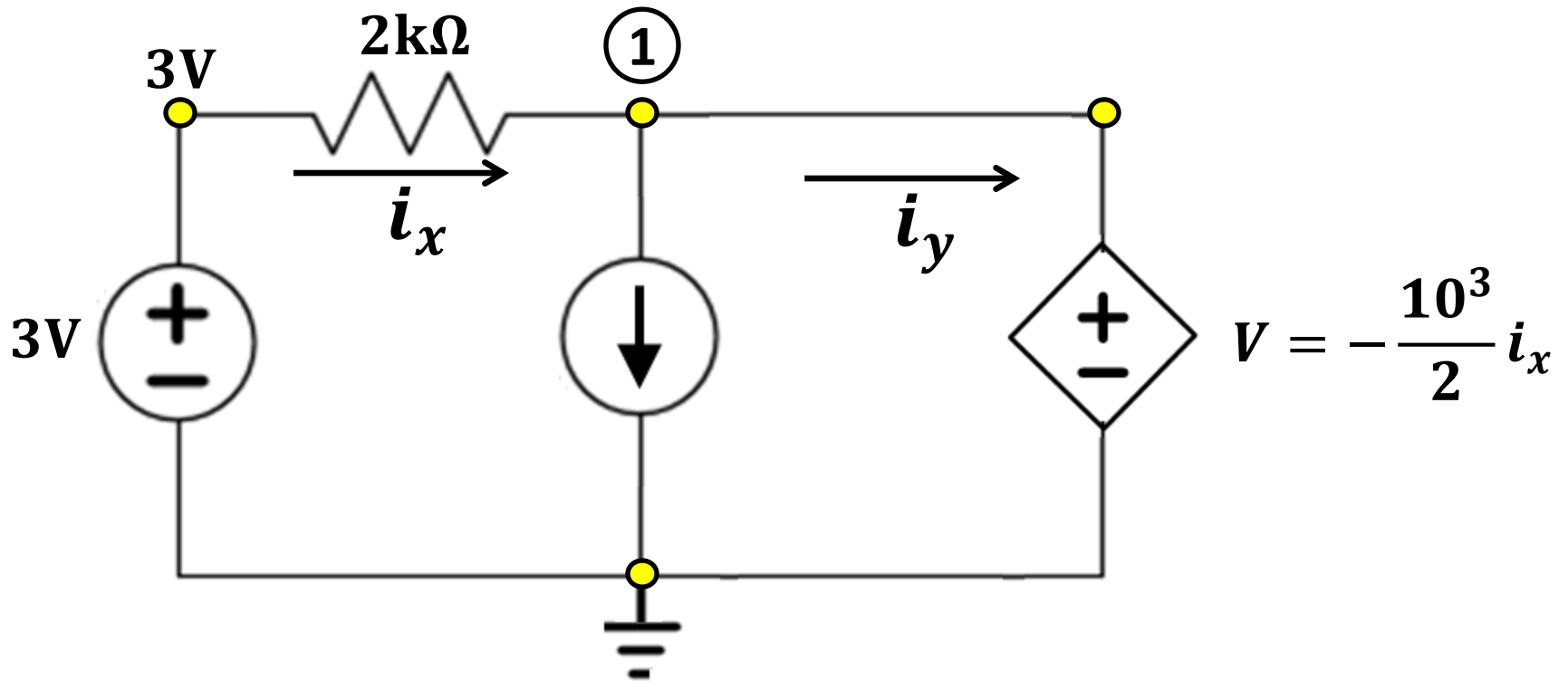

$$V = -\frac{10^3}{2} i_x$$

Example 2

Find the currents i_x and i_y

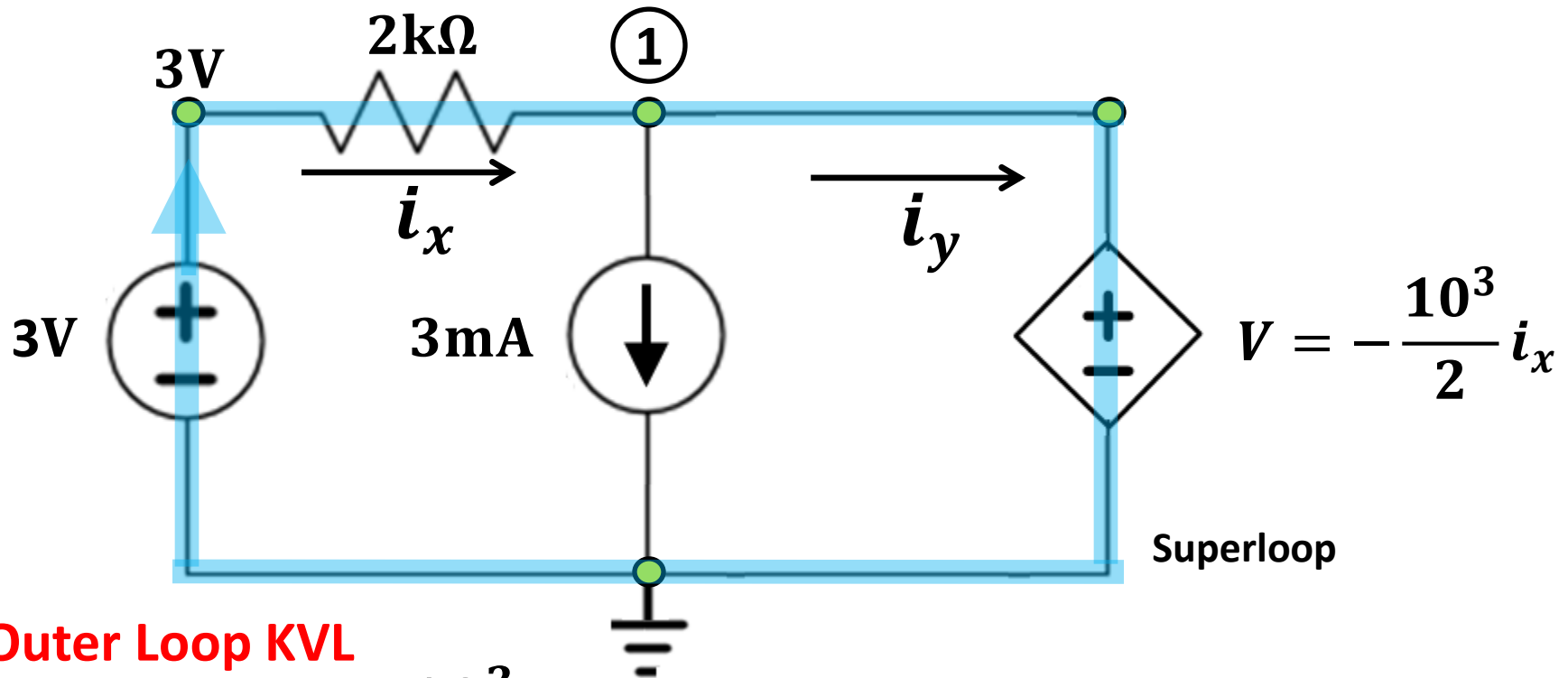

Outer Loop KVL

$$-3 + 2k i_x - \frac{10^3}{2} i_x = 0$$

$$1.5 i_x = 3m$$

Node ① KCL


$$-i_x + i_y + 3mA = 0$$

$$i_x = 2mA$$

$$i_y = -1mA$$


Example 3

Find V_y

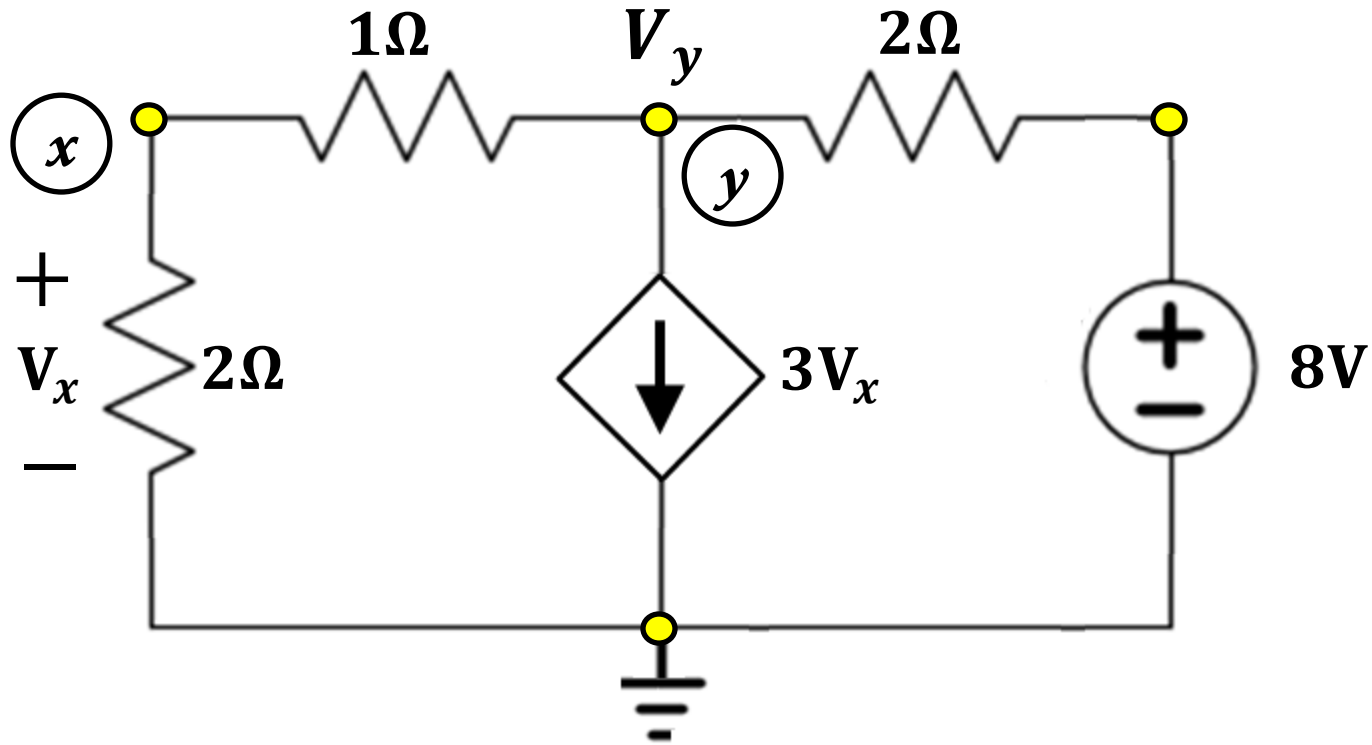

Example 3


Find V_y

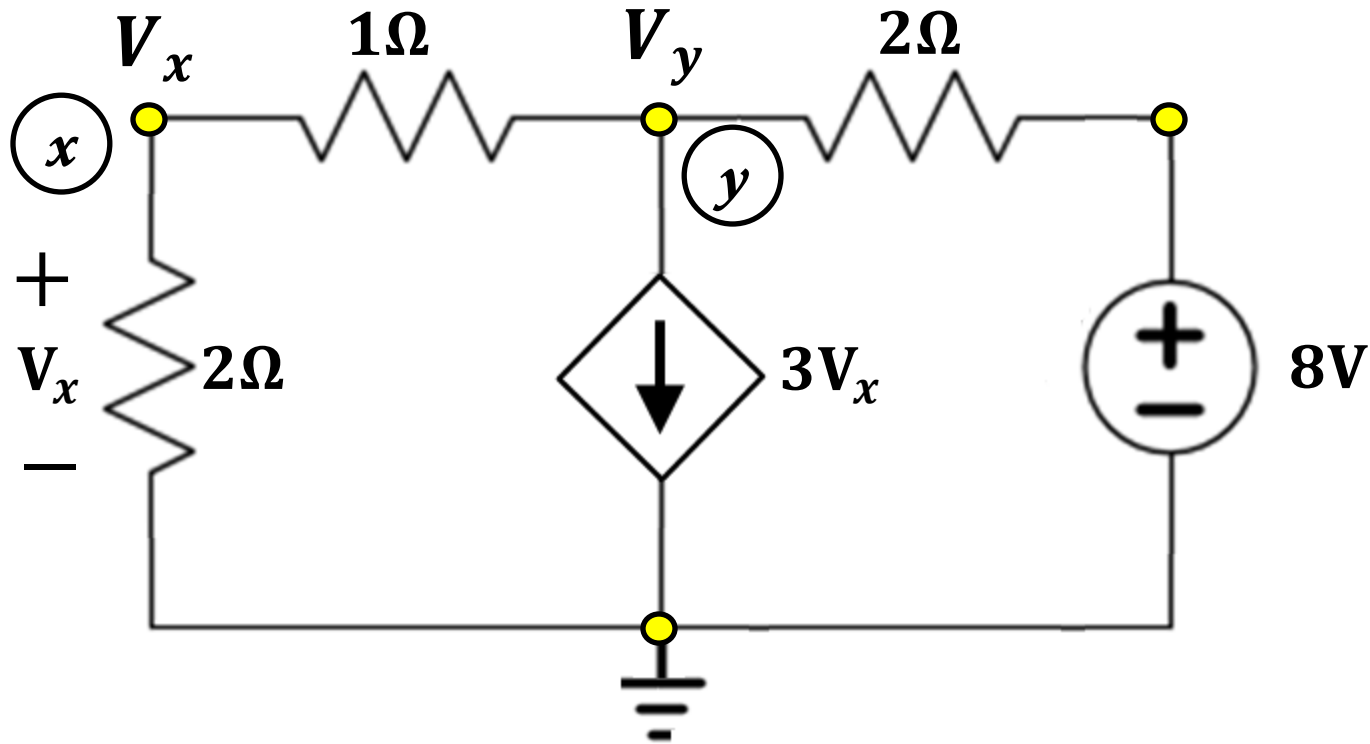

Node x
$$\frac{V_x - 0}{2} + \frac{V_x - V_y}{1} = 0$$

Example 3

Find V_y

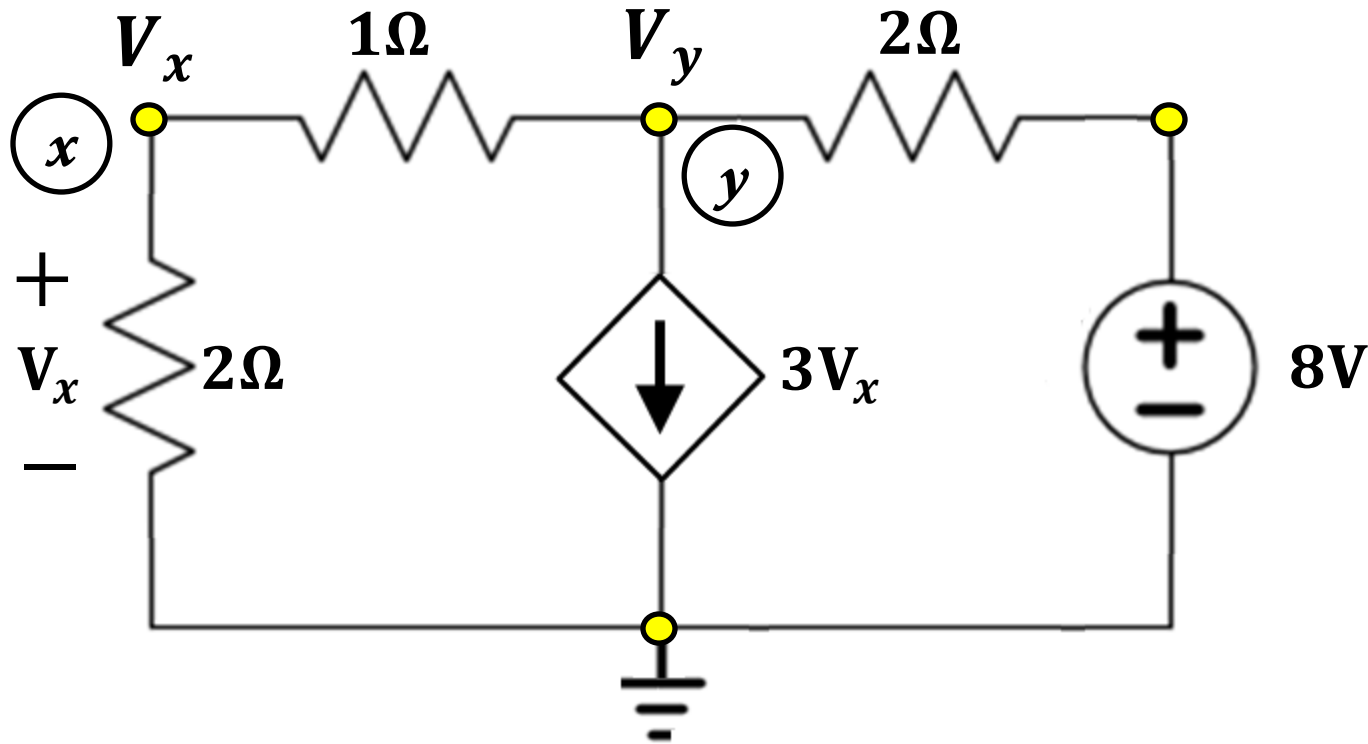


Node x
$$\frac{V_x - 0}{2} + \frac{V_x - V_y}{1} = 0$$

Node y
$$\frac{V_y - V_x}{1} + 3V_x + \frac{V_y - 8}{2} = 0$$

Example 3

Find V_y

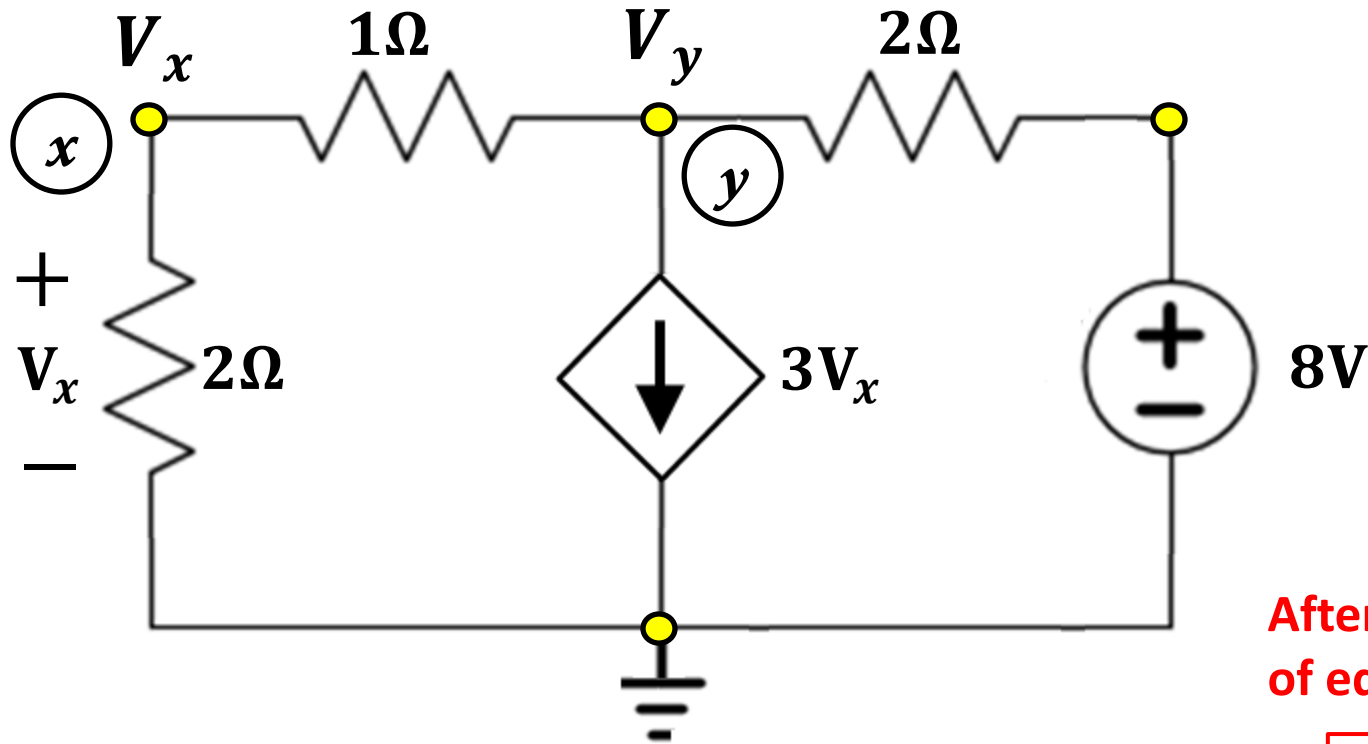

After solving system of equations

Node x
$$\frac{V_x - 0}{2} + \frac{V_x - V_y}{1} = 0$$


Node y
$$\frac{V_y - V_x}{1} + 3V_x + \frac{V_y - 8}{2} = 0$$

$$V_x = \frac{16}{17} \text{ V}$$

$$V_y = \frac{24}{17} \text{ V}$$

Example 3

Verification

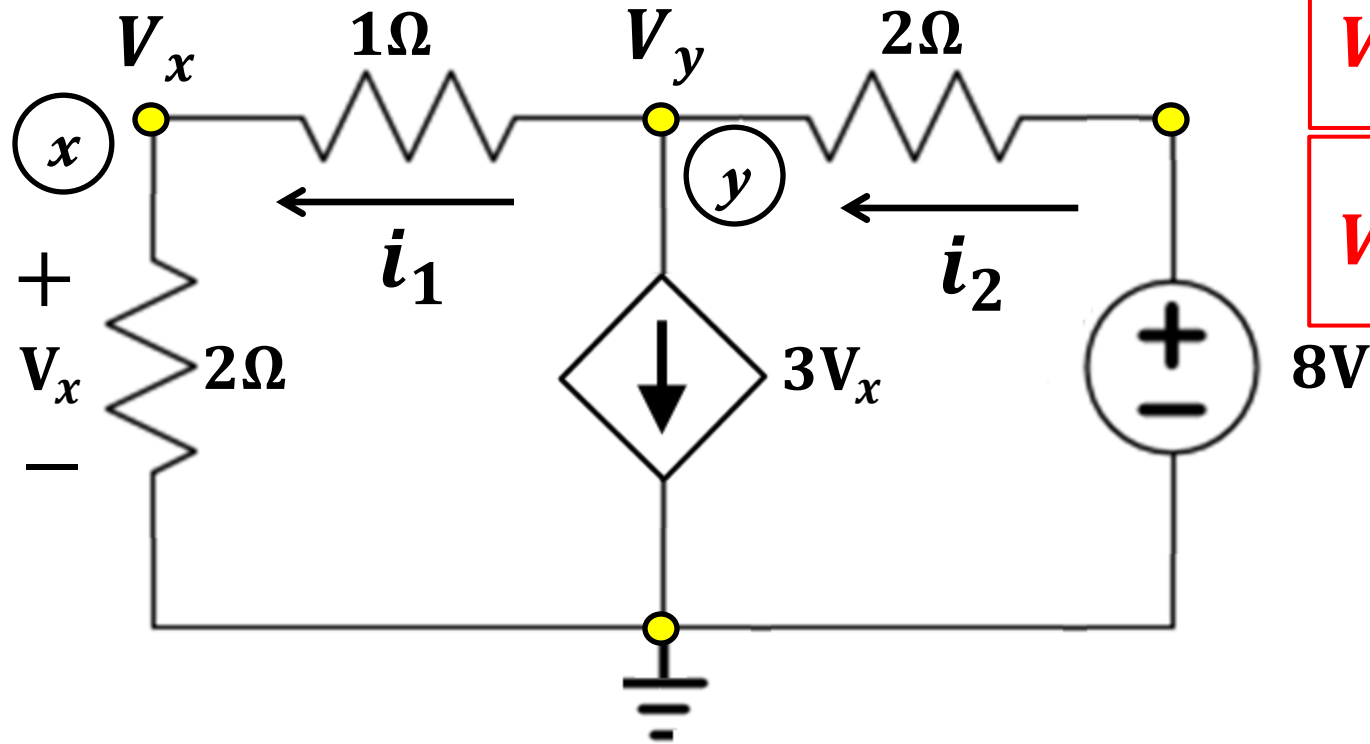

$$V_x = \frac{16}{17} \text{ V}$$

$$V_y = \frac{24}{17} \text{ V}$$

$$i_1 = \frac{V_x}{2} = \frac{1}{2} \times \frac{16}{17} = \frac{8}{17} \text{ A}$$


$$i_1 = \frac{V_y - V_x}{1\Omega} = \frac{24}{17} - \frac{16}{17} = \frac{8}{17} \text{ A}$$

$$i_2 = \frac{8 - V_y}{2} = 4 - \frac{12}{17} = \frac{56}{17} \text{ A}$$

$$i_2 = i_1 + 3V_x = \frac{8}{17} + 3 \frac{16}{17} = \frac{56}{17} \text{ A}$$


Example 4

Find V_x , V_y

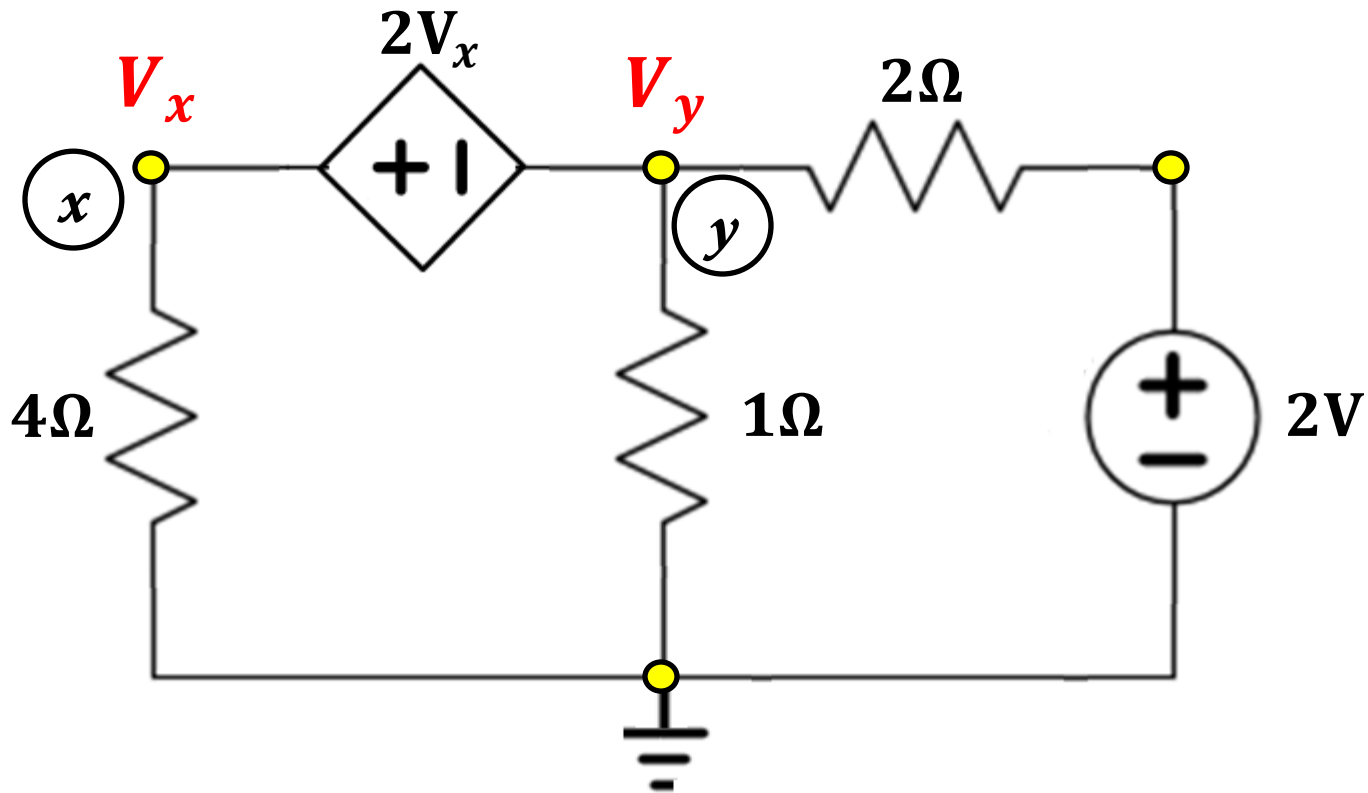

Example 4


Find V_x , V_y

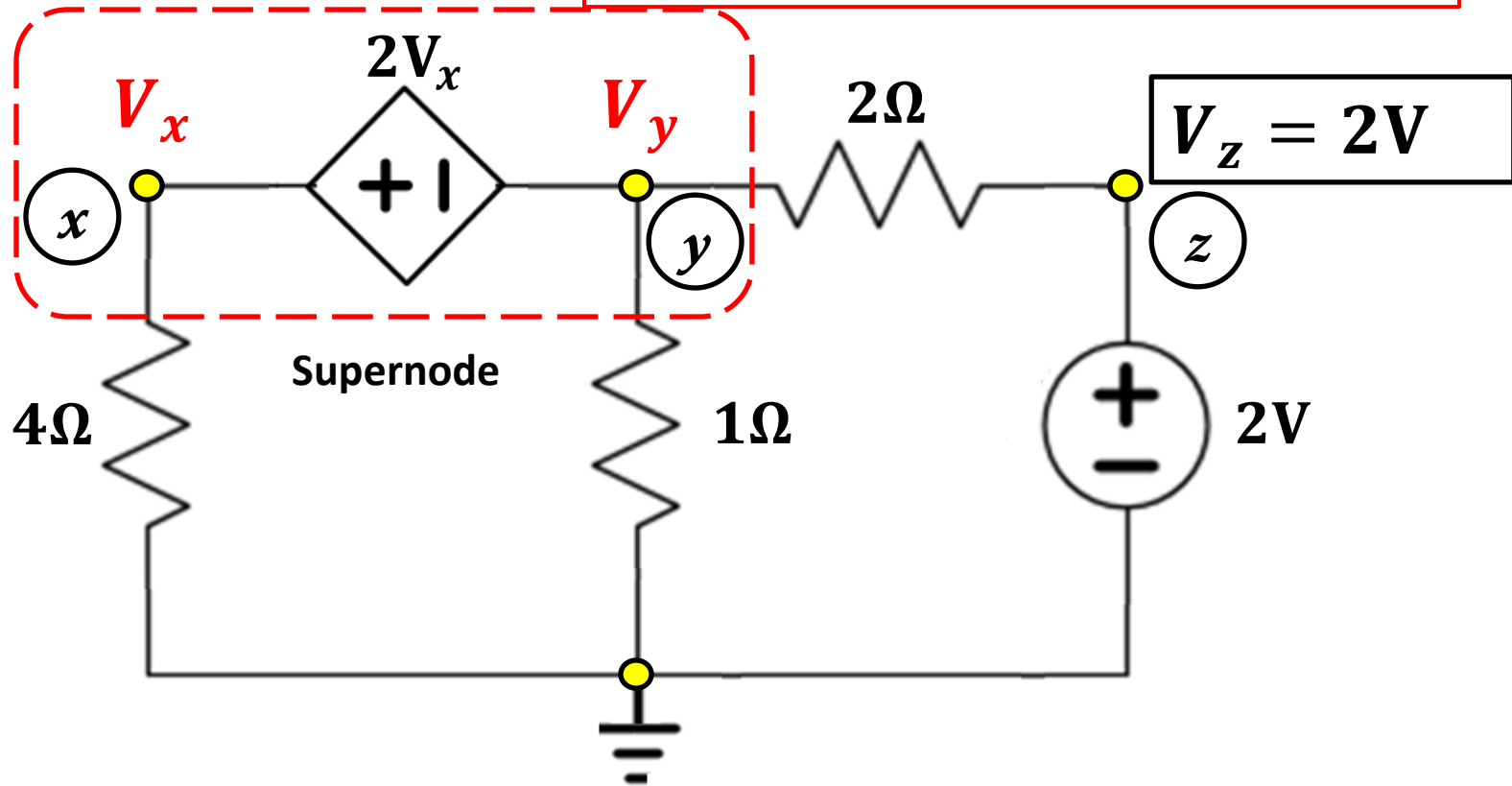

Node x $V_x = V_y + 2V_x \rightarrow V_x = -V_y$

Example 4

Find V_x, V_y

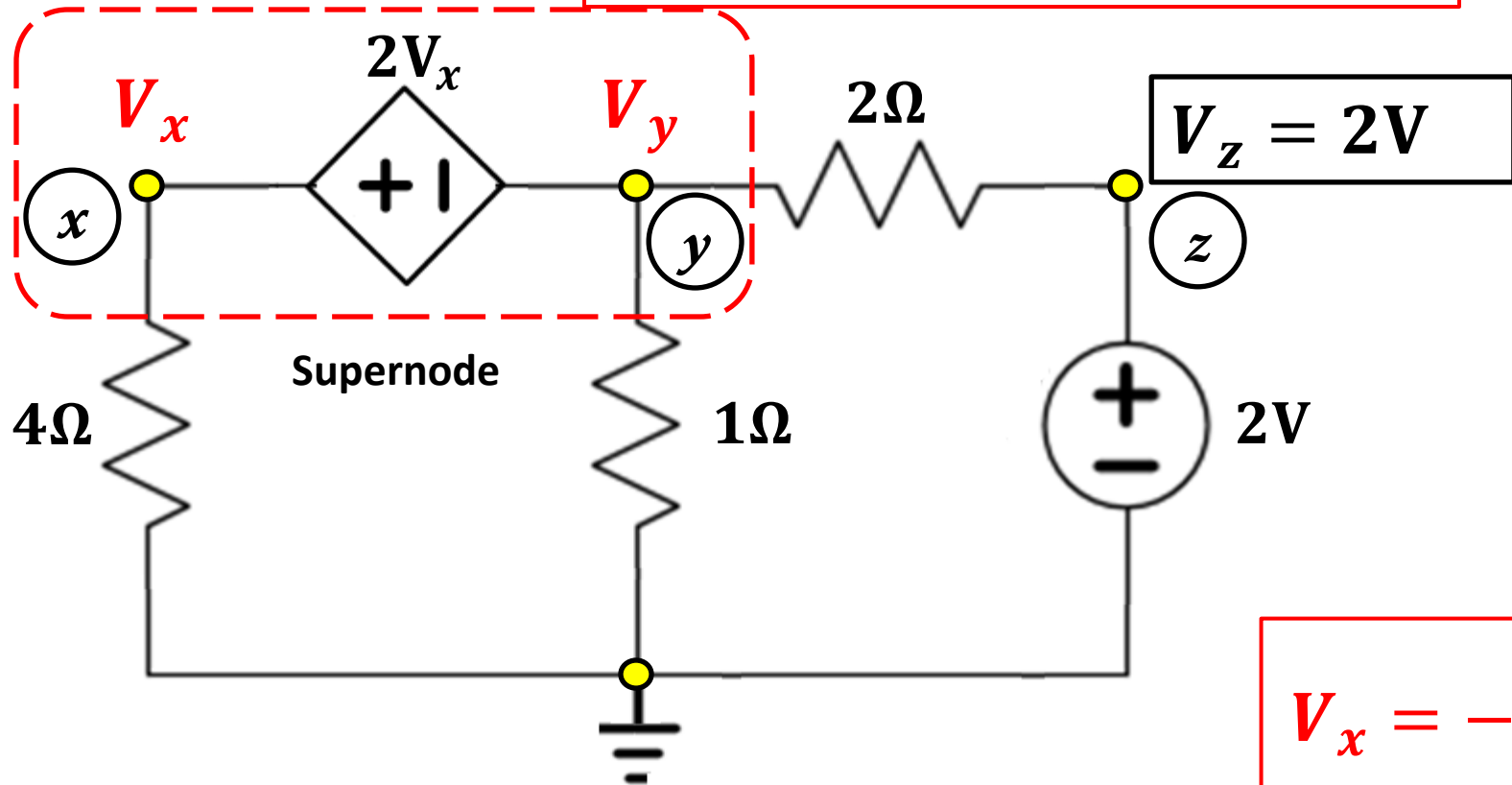

Node x $V_x = V_y + 2V_x \rightarrow V_x = -V_y$


Supernode KCL $\frac{V_y - 2}{2} + \frac{V_y}{1} + \frac{V_x}{4} = 0$

$$V_x = -\frac{4}{5}V$$

$$V_y = \frac{4}{5}V$$


Example 5

Find I_x, I_y

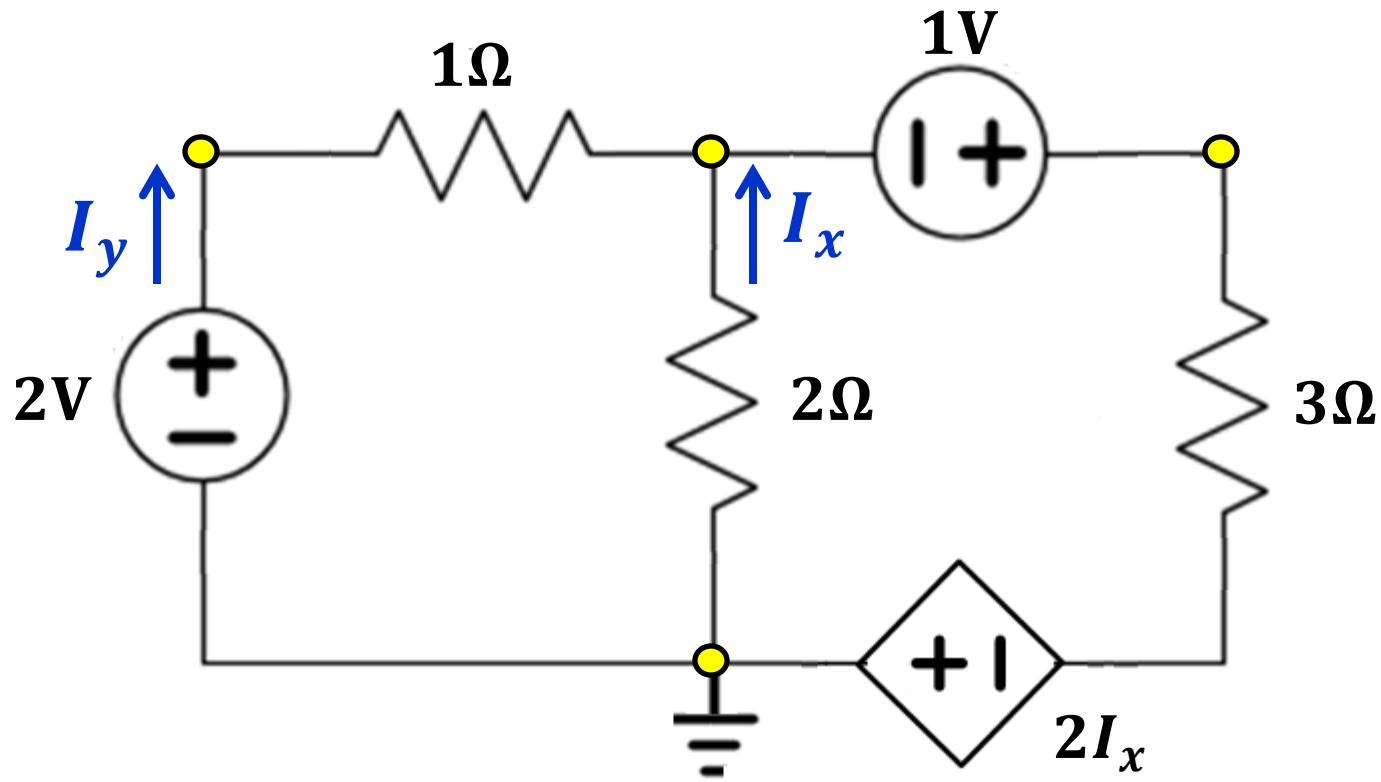

Example 5

Find I_x, I_y

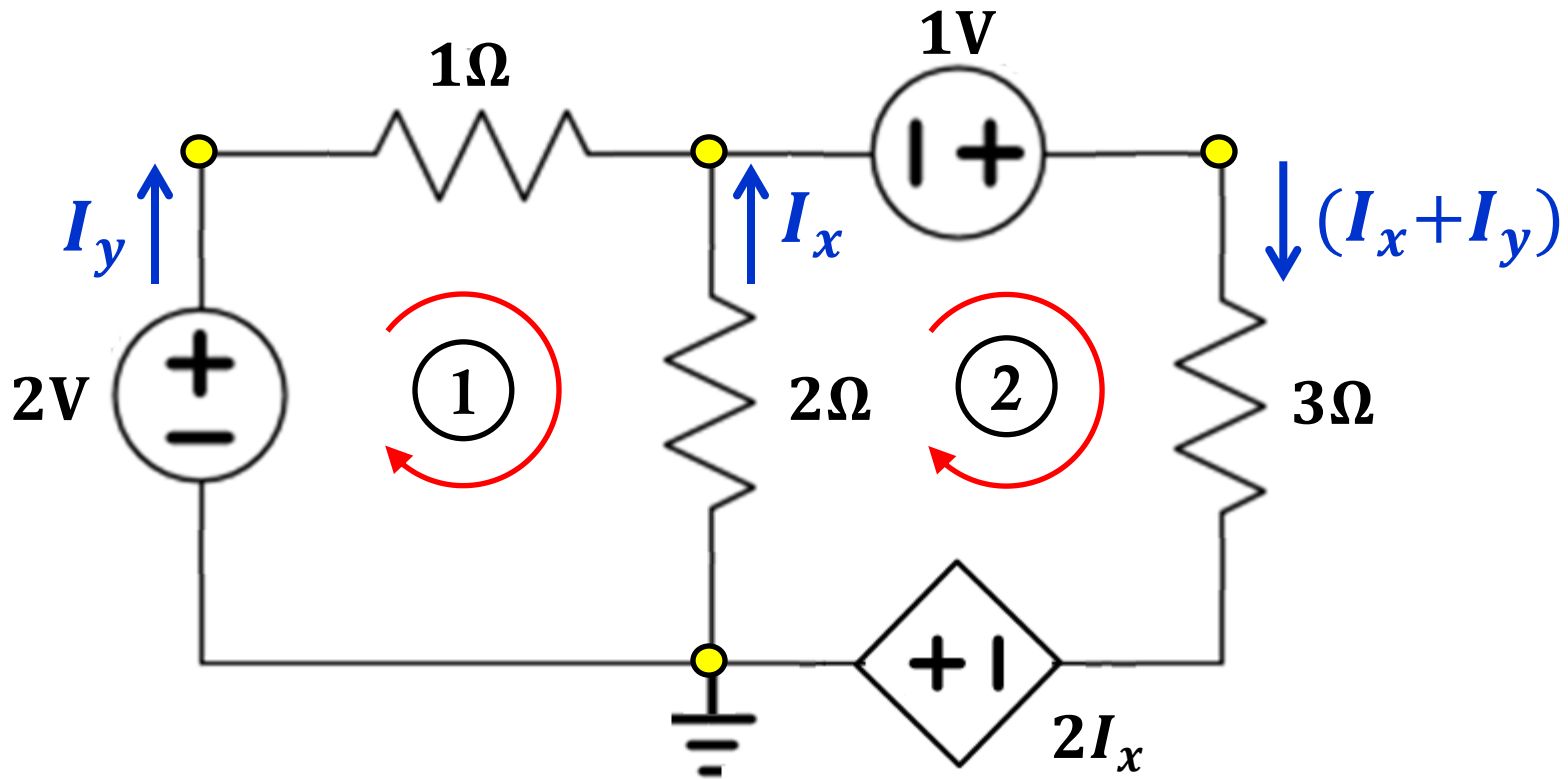


Loop ① $-2V + 1\Omega I_y - 2\Omega I_x = 0$

Loop ② $-1V + 3\Omega(I_x + I_y) - 2I_x + 2\Omega I_x = 0$

Example 5

Find I_x, I_y

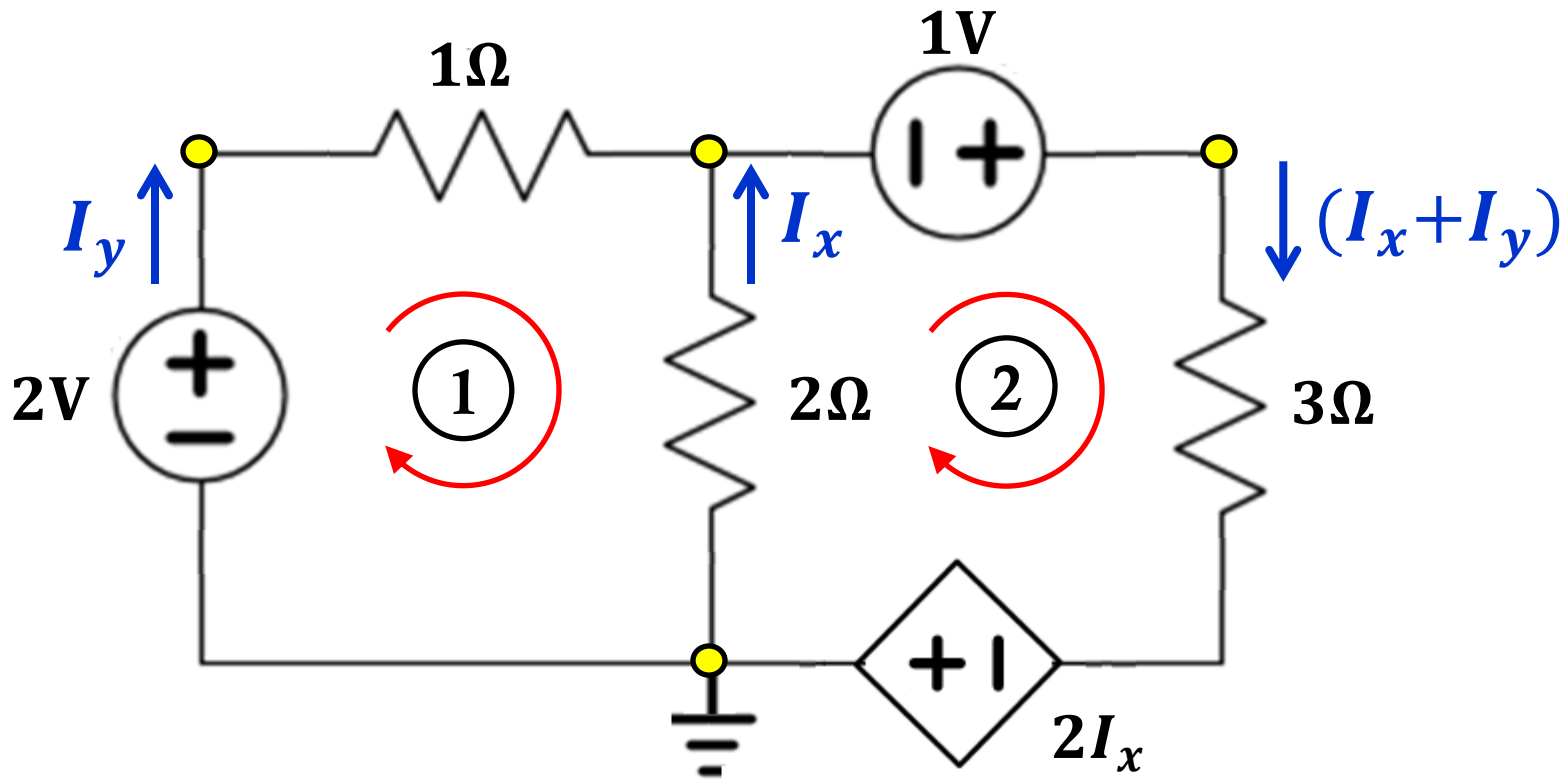

Loop ① $-2I_x + I_y = 2$

Loop ② $I_x + I_y = 1/3$

Example 5

Find I_x, I_y

Loop ① $-2I_x + I_y = 2$

Loop ② $I_x + I_y = \frac{1}{3}$

① $I_y = 2 + 2I_x$

② $I_x + 2 + 2I_x = \frac{1}{3}$

$$3I_x = -2 + \frac{1}{3} = -\frac{5}{3}$$

\Rightarrow $I_x = -\frac{5}{9}$


① $-2 \times \left(-\frac{5}{9}\right) + I_y = 2$

$$I_y = 2 - \frac{10}{9}$$

\Rightarrow $I_y = \frac{8}{9}$

Example 5

Verification

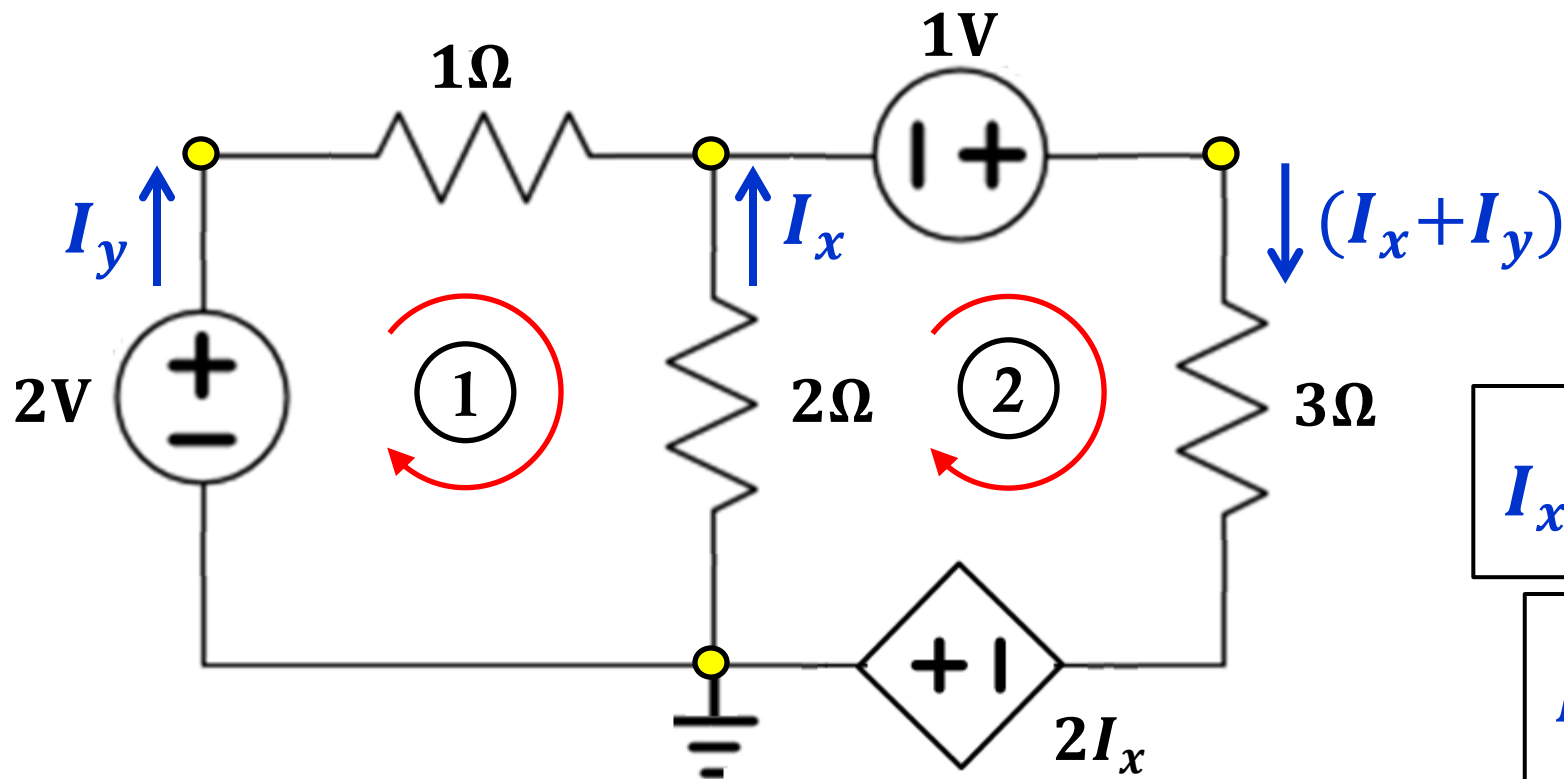

$$I_x = -\frac{5}{9}$$

$$I_y = \frac{8}{9}$$


Loop ① $-2 + I_y - 2I_x = 0$

$$-2 + \frac{8}{9} - 2\left(-\frac{5}{9}\right) = 0$$

$$-2 + 2 = 0$$

Example 5

Verification

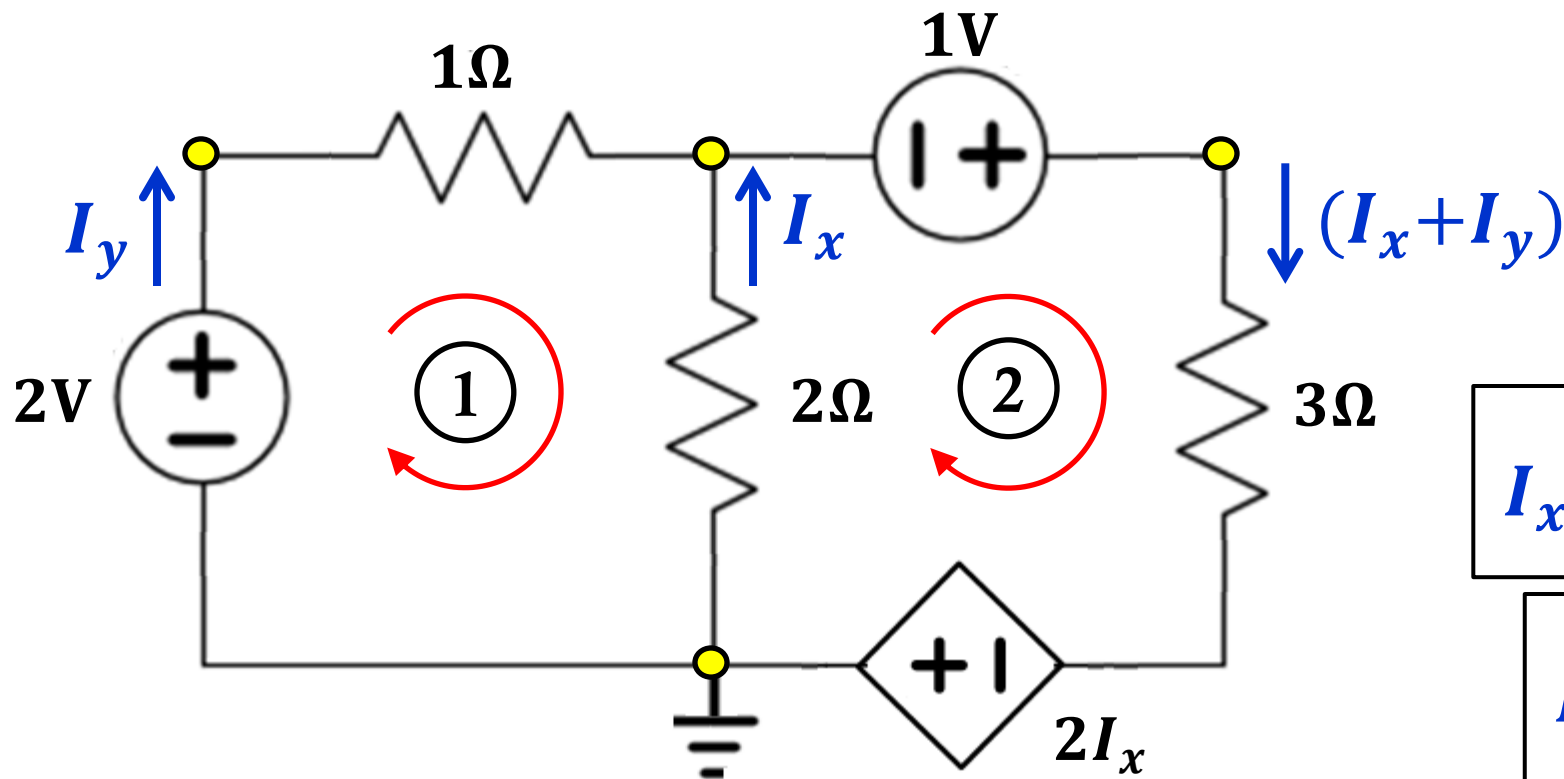

$$I_x = -\frac{5}{9}$$

$$I_y = \frac{8}{9}$$


Loop ② $-1 + 3(I_x + I_y) - 2I_x + 2I_x = 0$

$$-1 + 3\left(-\frac{5}{9} + \frac{8}{9}\right) = 0$$

$$-1 + 1 = 0$$

Example 5

Verification

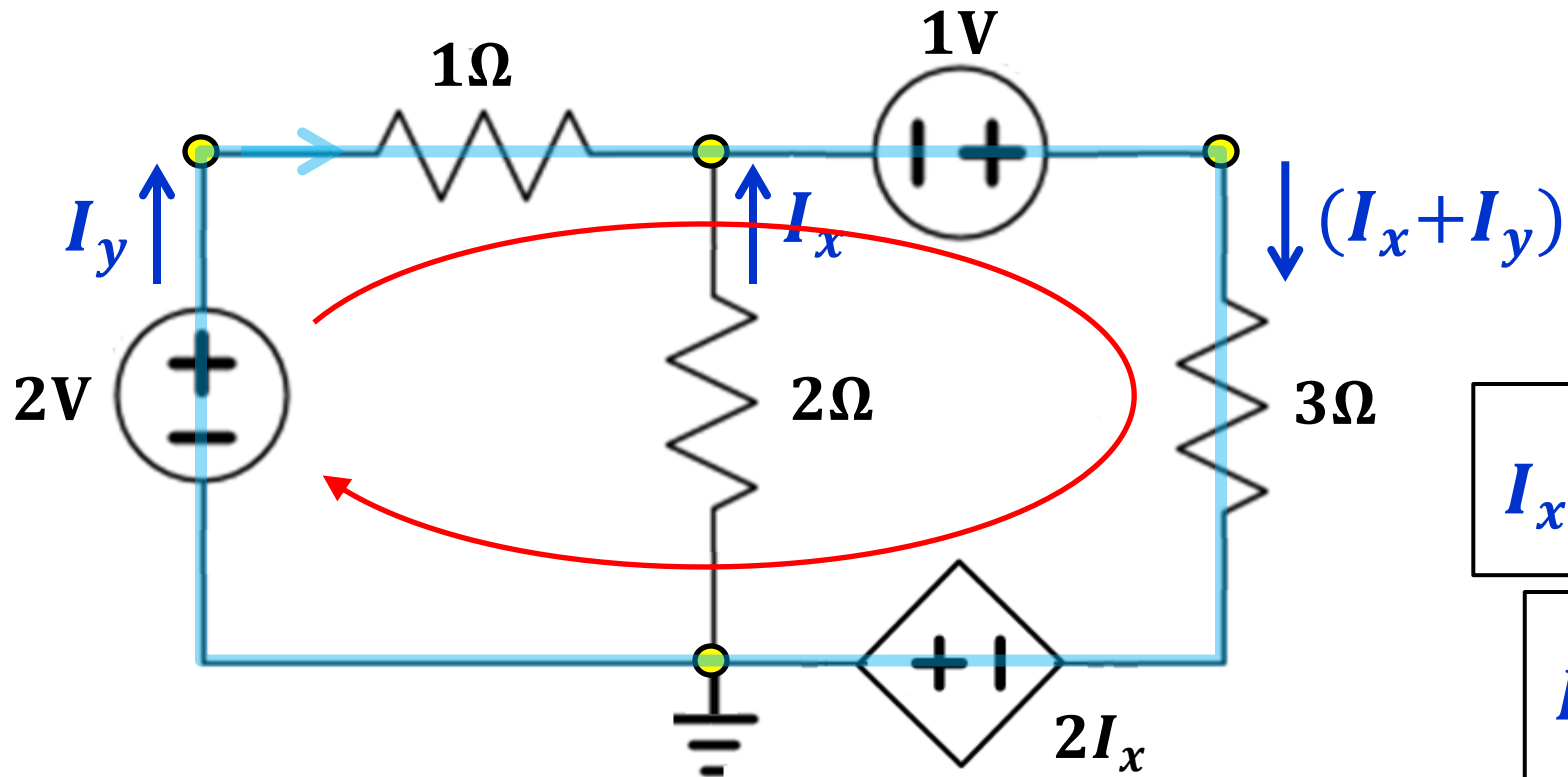

$$I_x = -\frac{5}{9}$$

$$I_y = \frac{8}{9}$$

Superloop

$$-2 + I_y - 1 + 3(I_x + I_y) - 2I_x = 0$$

$$-2 + \frac{8}{9} - 1 + 3\left(-\frac{5}{9} + \frac{8}{9}\right) - 2\left(-\frac{5}{9}\right) = 0$$

$$-3 + 27/9 = -3 + 3 = 0$$