

ECE 205 “Electrical and Electronics Circuits”

Spring 2024 – LECTURE 16

MWF – 12:00pm

Prof. Umberto Ravaioli

2062 ECE Building

Lecture 16 – Summary


Learning Objectives

1. Power considerations
2. Detailed analysis of RC and RL circuits with time-dependent sources
3. Solution of circuit differential equations

Power Considerations

1. Energy stored by a capacitor
2. Energy stored by an inductor

Capacitor

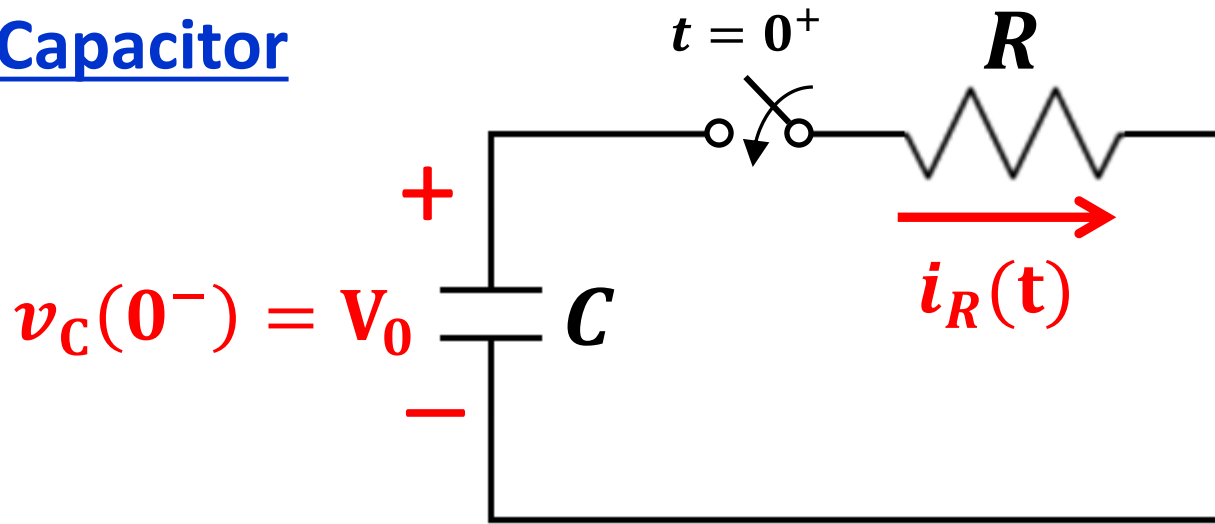


$$\alpha = \frac{1}{\tau} = \frac{1}{RC}$$

$$C = \frac{\tau}{R}$$

At $t \rightarrow \infty$ the resistor has dissipated all the energy stored in the capacitor

Power
$$p_R(t) = v_C(t) \cdot i_R(t) = \frac{v_C^2(t)}{R} = \frac{V_0^2 e^{-2\alpha t}}{R}$$

Energy absorbed
$$w_R(t) = \int_0^t p_R(t') dt' = \int_0^t \frac{V_0^2 e^{-2\alpha t'}}{R} dt'$$
$$= -\frac{\tau V_0^2}{2R} e^{-2\alpha t} \Big|_0^t = \frac{1}{2} C V_0^2 [1 - e^{-2\alpha t}]$$

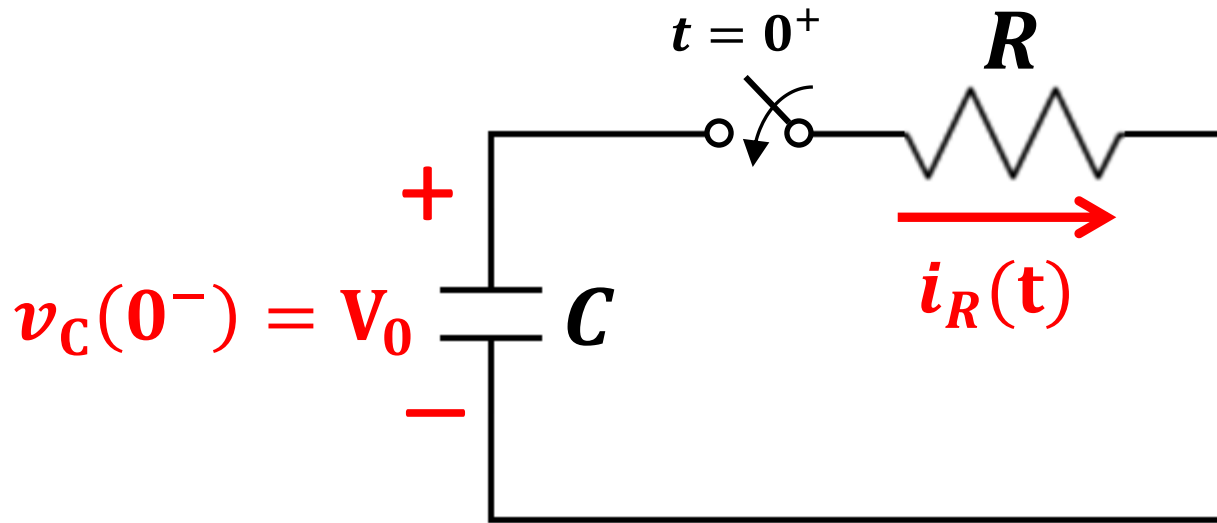

$$\alpha = \frac{1}{\tau} = \frac{1}{RC}$$

$$C = \frac{\tau}{R}$$

Energy
absorbed


$$w_R(t) = \frac{1}{2} C V_0^2 [1 - e^{-2\alpha t}]$$

$t \rightarrow \infty$

$$w_R(t \rightarrow \infty) = \frac{1}{2} C V_0^2$$

Energy dissipated by R = Energy stored by C

Inductor

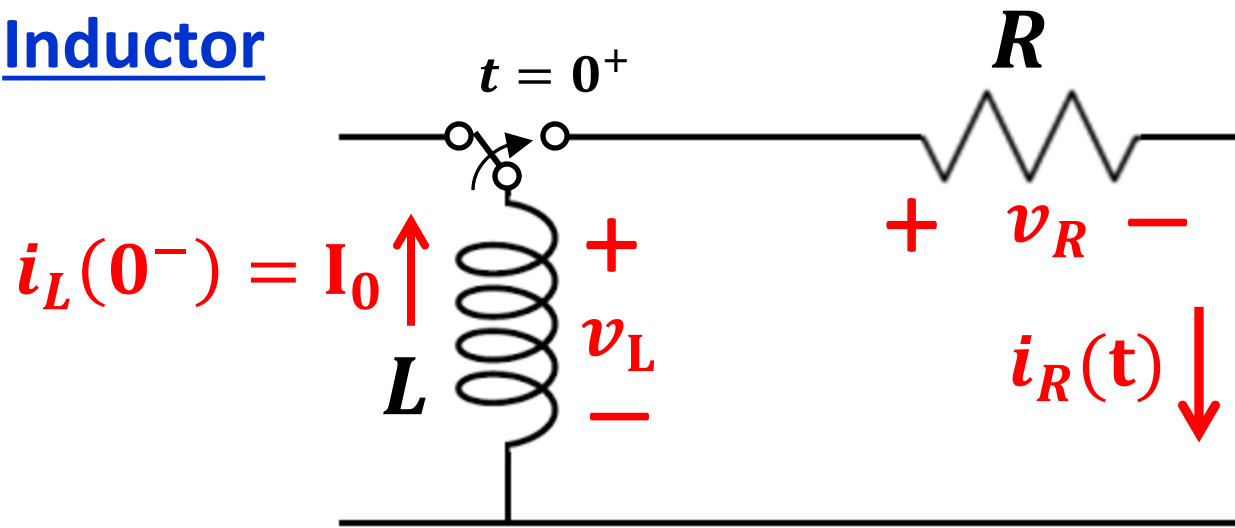

$$\alpha = \frac{1}{\tau} = \frac{R}{L}$$


$$L = \tau R$$

At $t \rightarrow \infty$ the resistor has dissipated all the energy stored in the inductor

Power $p_R(t) = v_R(t) \cdot i_R(t) = i_L^2(t)R = RI_0^2 e^{-2\alpha t}$

Energy absorbed

$$\begin{aligned} w_R(t) &= \int_0^t p_R(t') dt' = \int_0^t RI_0^2 e^{-2\alpha t'} dt' \\ &= -\frac{\tau RI_0^2}{2} e^{-2\alpha t} \Big|_0^t = \frac{1}{2} L I_0^2 [1 - e^{-2\alpha t}] \end{aligned}$$

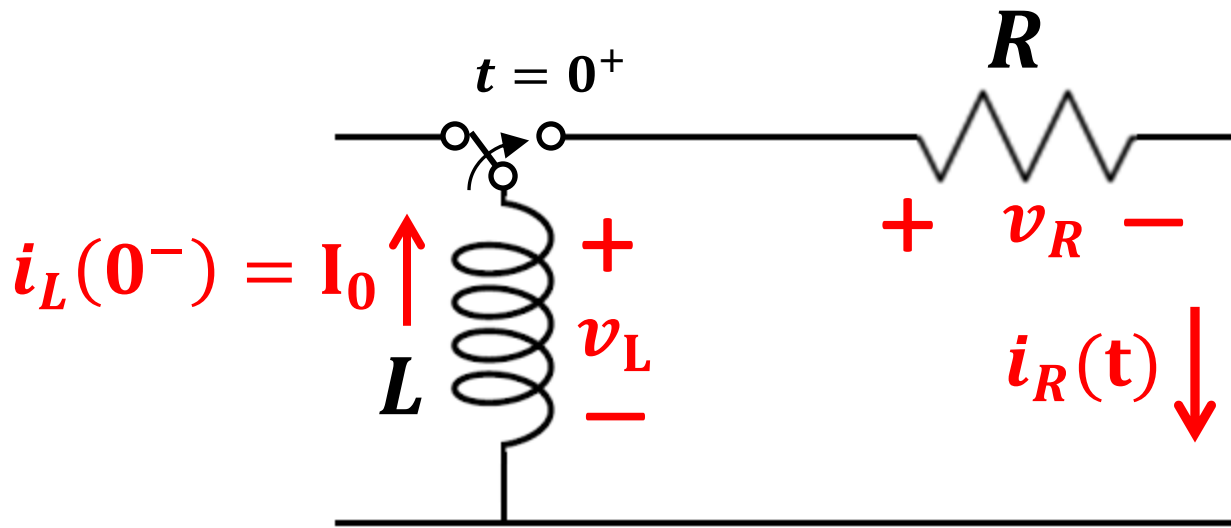

$$\alpha = \frac{1}{\tau} = \frac{R}{L}$$

$$L = \tau R$$

Energy absorbed

$$w_R(t) = \frac{1}{2} L I_0^2 [1 - e^{-2\alpha t}]$$

$t \rightarrow \infty$


$$w_R(t \rightarrow \infty) = \frac{1}{2} L I_0^2$$

Energy dissipated by R = Energy stored by L

RC and RL circuits with time-dependent input

RC circuit

Time-dependent

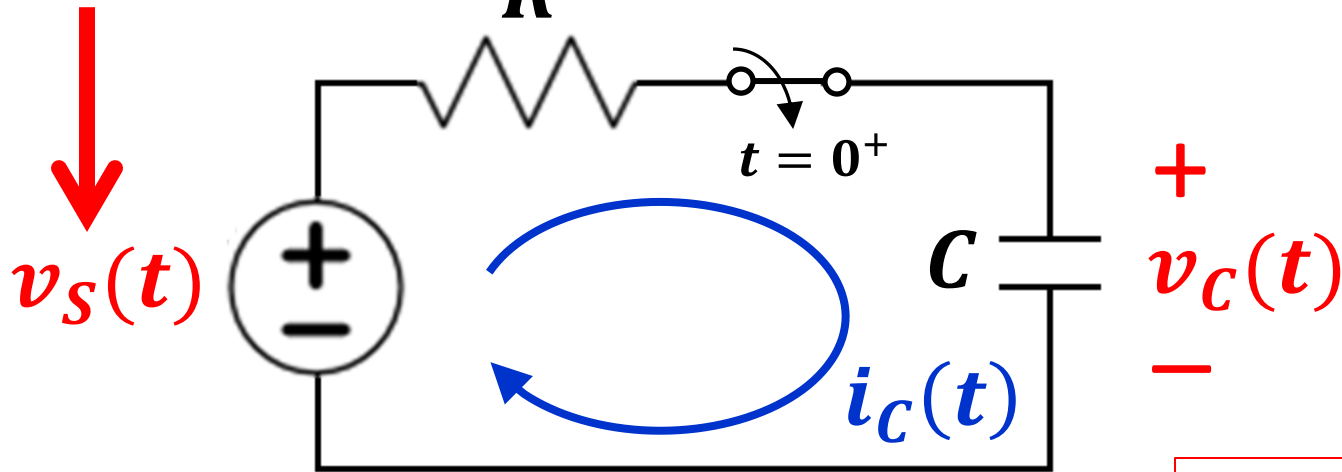


$$i_C(t) = C \frac{dv_C(t)}{dt}$$

KVL for the RC circuit

$$-v_S(t) + Ri_C(t) + v_C(t) = 0$$

$$RC \frac{d}{dt} v_C(t) + v_C(t) = v_S(t)$$

RC circuit

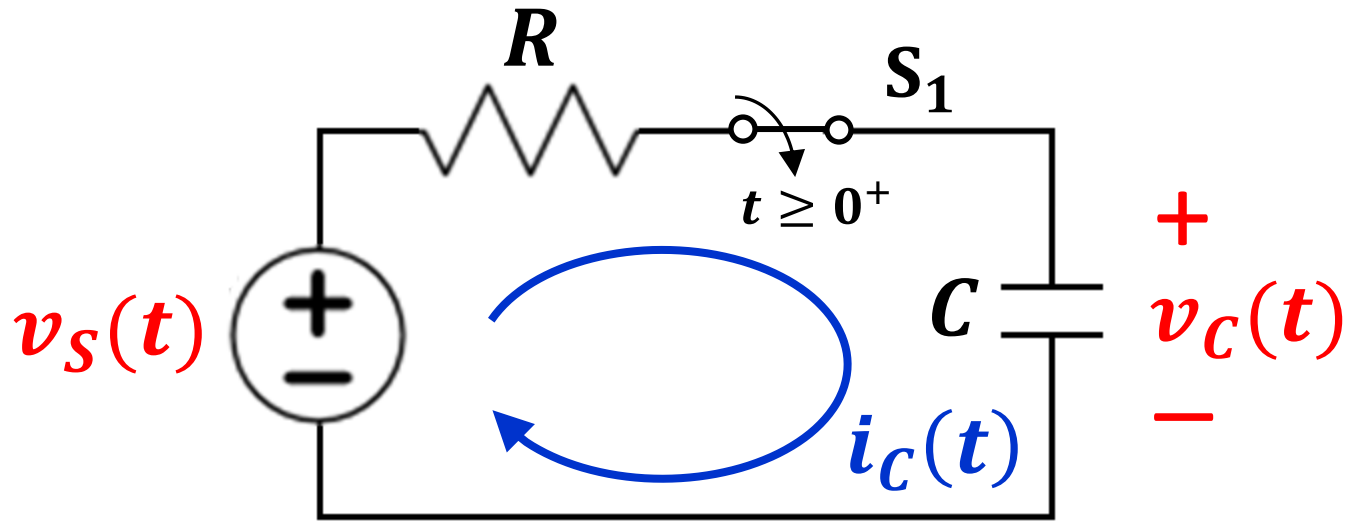


The RC circuit is described by the differential equation

$$\frac{d}{dt} v_C(t) + \frac{1}{RC} v_C(t) = \frac{1}{RC} v_S(t)$$

RL circuit

Time-dependent

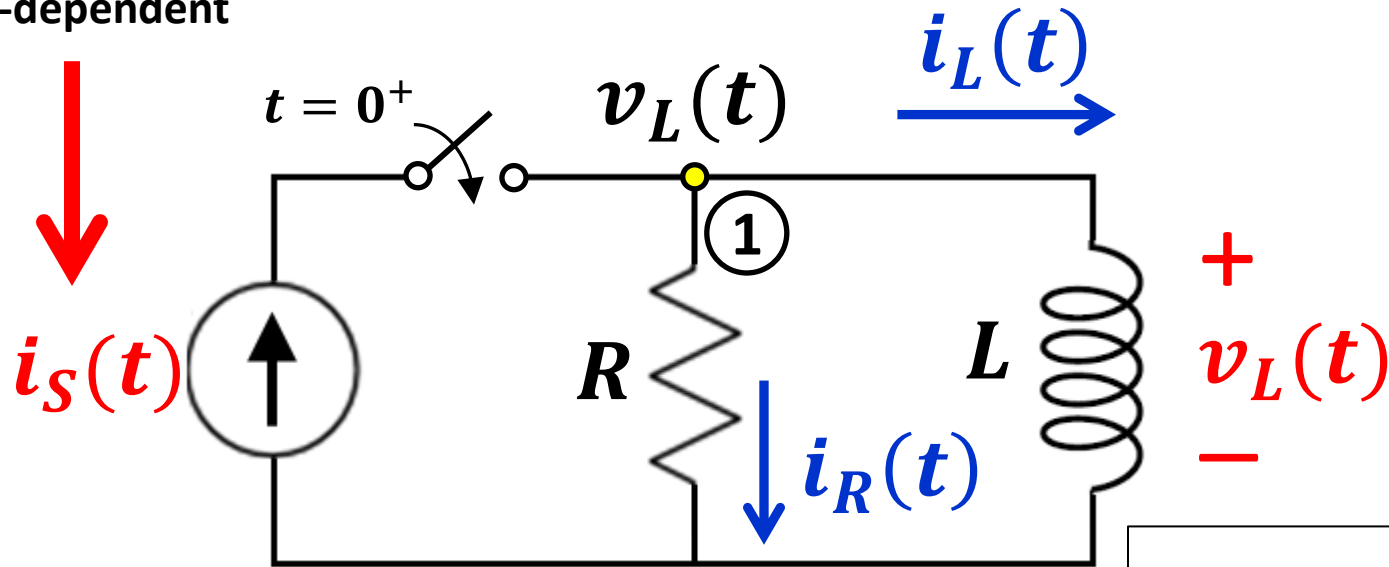


$$v_L(t) = L \frac{d}{dt} i_L(t)$$

KVL for the RL loop

$$v_L(t) - R[i_S(t) - i_L(t)] = 0$$

$$L \frac{d}{dt} i_L(t) + R i_L(t) = R i_S(t)$$

RL circuit

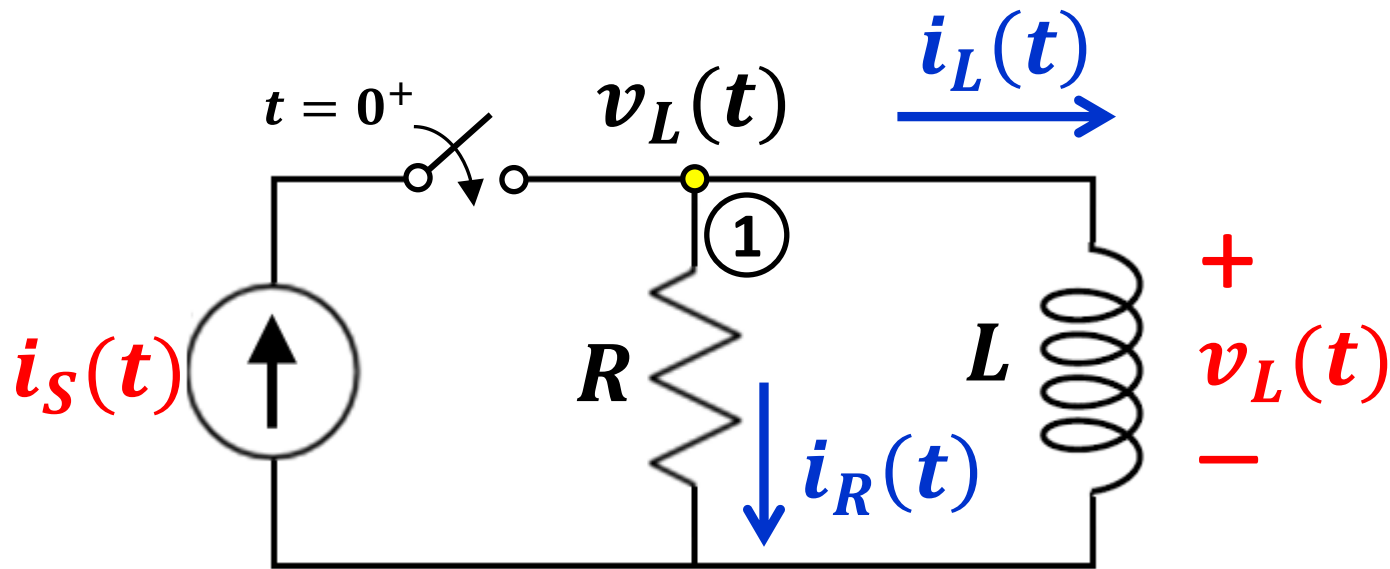

The RL circuit is described by the differential equation

$$\frac{d}{dt} i_L(t) + \frac{R}{L} i_L(t) = \frac{R}{L} i_S(t)$$

The transient behavior for RC and RL circuits is described by the first order ordinary differential equation


$$\frac{d}{dt}y(t) + a y(t) = b f(t)$$

Forcing term

A solution satisfies the initial condition

$$y(0^-) = y(0^+)$$

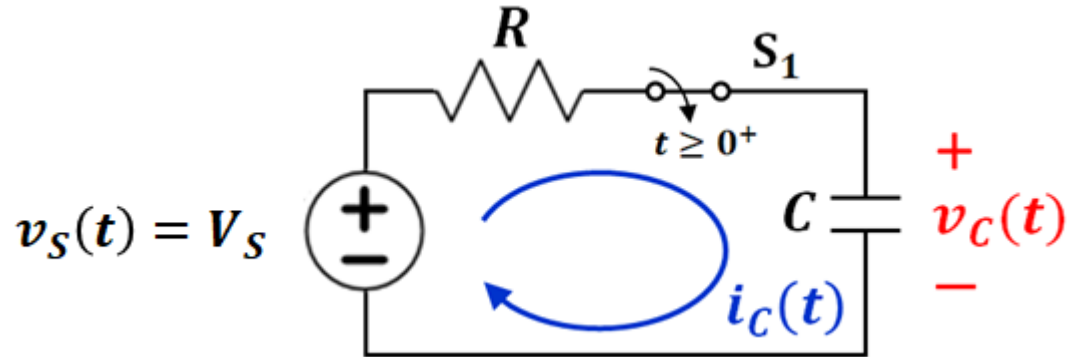CASE 1 – RC circuit with constant $v_S(t) = V_S$



$$\frac{d}{dt} V_C(t) + \frac{1}{RC} V_C(t) = \frac{1}{RC} V_S \quad \boxed{1}$$

Initial
condition

$$V_C(0^-) = V_C(0^+)$$

The solution can be written in the form

$$V_C(t) = u_h(t) + \underbrace{K_2}_{\text{constant}}$$

In our case, we have:

$$V_C(t) = V_h(t) + V_S$$



$$\frac{d}{dt} [V_h + V_S] + \frac{1}{RC} [V_h + \cancel{V_S}] = \frac{1}{RC} \cancel{V_S}$$



$$\frac{d}{dt} V_h(t) + \frac{1}{RC} V_h(t) = 0 \quad \boxed{2}$$

Equation **2** is homogeneous and can be integrated as

$$V_h(t) = K_1 e^{-t/RC}$$

Complete solution

$$V_c(t) = V_h(t) + K_2 = K_1 e^{-t/RC} + K_2$$

Equation **2** is homogeneous and can be integrated as

$$V_h(t) = K_1 e^{-t/RC}$$

Complete solution

$$V_C(t) = V_h(t) + K_2 = K_1 e^{-t/RC} + K_2$$

$$V_C(0^-) = V_C(0^+) \rightarrow V_C(0^-) = K_1 + K_2$$



$$K_1 = V_C(0^-) - K_2$$

Also,

$$V_C(t \rightarrow \infty) = K_2 = V_S$$

Equation 2 is homogeneous and can be integrated as

$$V_h(t) = K_1 e^{-t/RC}$$

Complete solution

$$V_C(t) = V_h(t) + K_2 = K_1 e^{-t/RC} + K_2$$

$$V_C(0^-) = V_C(0^+) \rightarrow V_C(0^-) = K_1 + K_2$$




$$K_1 = V_C(0^-) - K_2$$

Also,

$$V_C(t \rightarrow \infty) = K_2 = V_S$$

$$V_C(t) = [V_C(0^-) - V_S] e^{-t/RC} + V_S$$

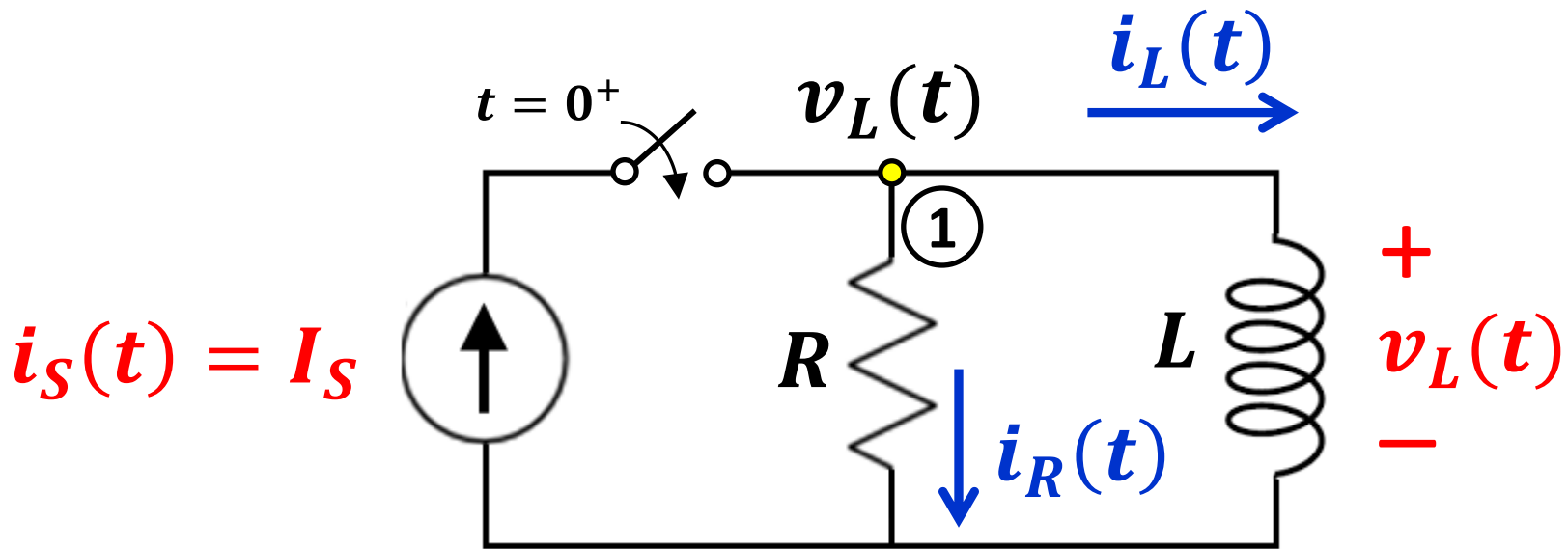CASE 2 – RL circuit with constant $i_S(t) = I_S$



Following the same solution steps

$$i_L(t) = [I_L(0^-) - I_S] e^{-(L/R)t} + I_S$$

CASE 3 – RC or RL circuit with arbitrary input

Differential equation of the type

$$\frac{d}{dt}y(t) + a y(t) = b f(t)$$

General solution

$$y(t) = y_h(t) + y_p(t) \quad t \geq 0$$

Solution of the
homogeneous equation



Particular solution

$$\frac{d}{dt}y(t) + a y(t) = 0$$

Solution to the homogeneous equation has the form

$$y_h(t) = K_1 e^{-\alpha t}$$

so, the general solution is

$$y_h(t) = K_1 e^{-\alpha t} + y_p(t)$$



**Homogeneous
solution**



**Particular
solution**

The particular solution depends on the form of the forcing term $f(t)$ (the source).


Examples of particular solutions to

$$\frac{d}{dt}y(t) + a y(t) = b f(t)$$

	function $f(t)$	Particular solution $y_p(t)$
1	constant D	constant K
2	$D \times t$	$Kt + L$ for some K and L
3	$D \times e^{mt}$	$K e^{mt}$ if $m \neq -a$ $K t e^{mt}$ if $m = -a$
4	$\cos(\omega t)$	$A \cos(\omega t + \theta) *$
5	$\sin(\omega t)$	$A \sin(\omega t + \theta) *$

* A and θ depend on ω , a , and b

Example

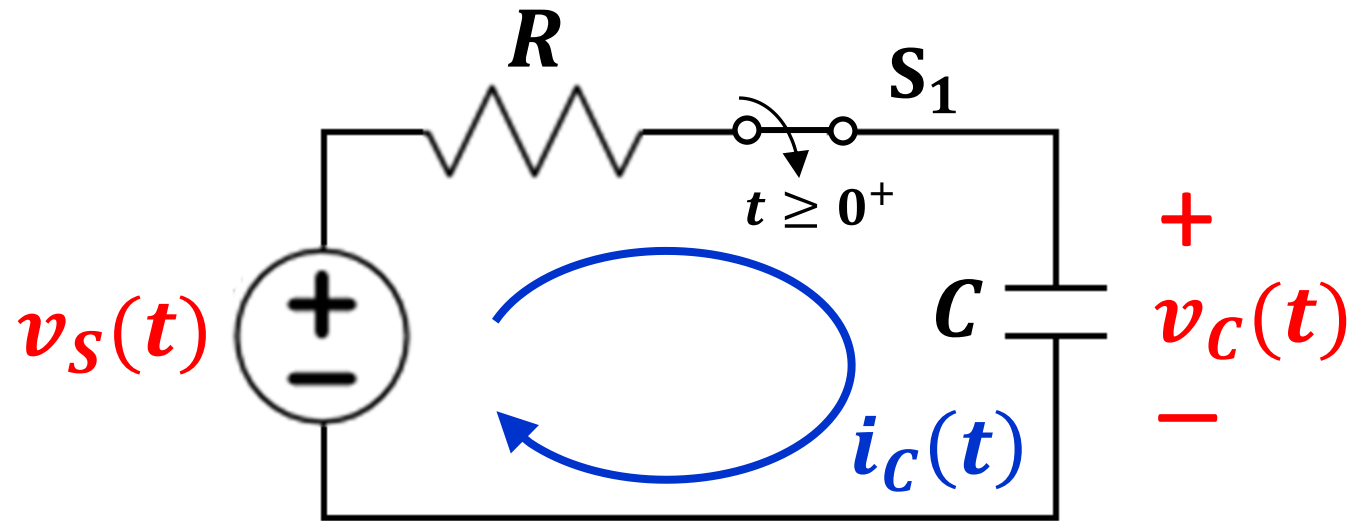

For simplicity

$$RC = 1\text{s}$$


$$v_s(t) = \cos(t)$$

$$v_c(t = 0^-) = 0\text{V}$$

zero initial condition

(the capacitor is not charged at time $t = 0^-$)

Example

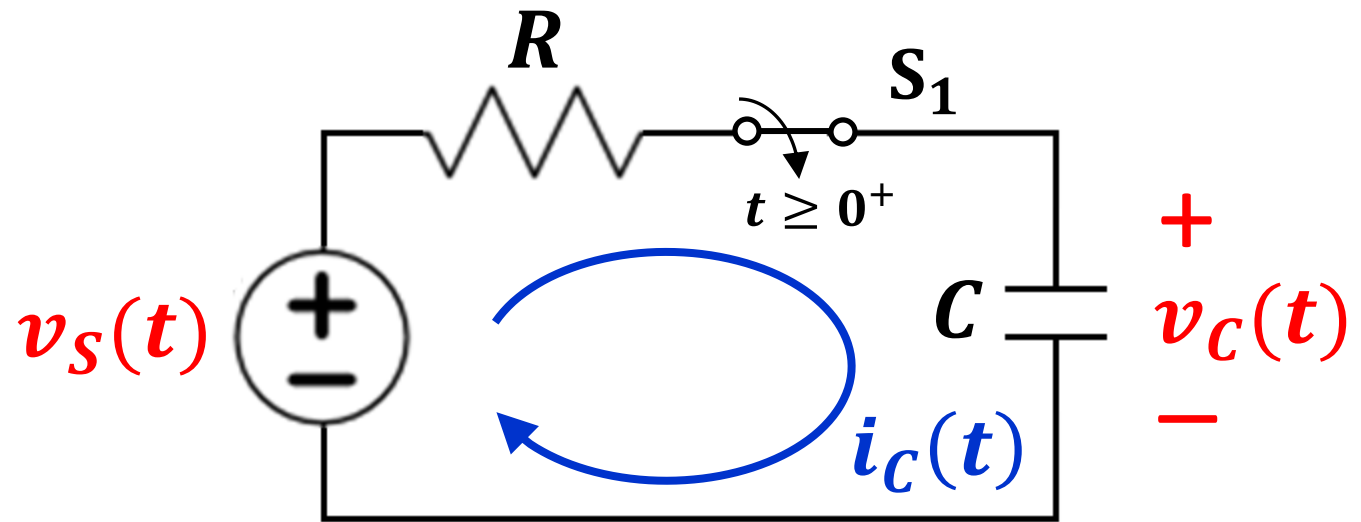

For simplicity

$$RC = 1\text{s}$$


$$v_S(t) = \cos(t)$$

$$v_C(t = 0^-) = 0\text{V}$$

Differential equation:

$$\frac{d}{dt} v_C(t) + v_C(t) = \cos(t)$$

Example

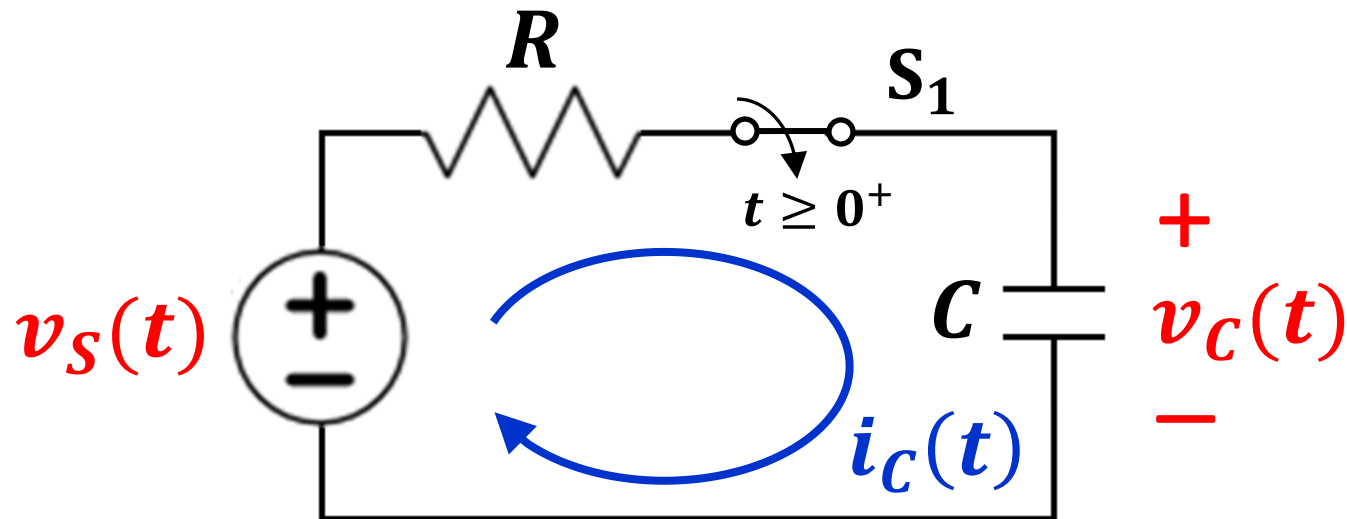

For simplicity

$$RC = 1\text{s}$$

$$v_s(t) = \cos(t)$$

$$v_c(t = 0^-) = 0\text{V}$$

Differential equation:

$$\frac{1}{RC} = 1 [\text{s}^{-1}]$$

$$\frac{d}{dt} v_c(t) + v_c(t) = \cos(t)$$

$$\omega = 2\pi f = 1$$

$$\frac{d}{dt}v_C(t) + v_C(t) = \cos(t)$$

From the table of particular solutions

$$V_p(t) = A \cos(t + \theta)$$

$$= \underbrace{A \cos(\theta)}_B \cos(t) - \underbrace{A \sin(\theta)}_C \sin(t)$$

$$\frac{d}{dt}v_C(t) + v_C(t) = \cos(t)$$

From the table of particular solutions

$$V_p(t) = A \cos(t + \theta)$$

$$= \underbrace{A \cos(\theta)}_B \cos(t) - \underbrace{A \sin(\theta)}_C \sin(t)$$

$$V_p(t) = B \cos(t) - C \sin(t)$$

$$\frac{d}{dt}V_p(t) = -B \sin(t) - C \cos(t)$$

Substituting the particular solution and its derivative

$$V_p(t) = B \cos(t) - C \sin(t)$$

$$\frac{d}{dt} V_p(t) = -B \sin(t) - C \cos(t)$$

in the original differential equation

$$\frac{d}{dt} v_C(t) + v_C(t) = \cos(t)$$

Substituting the particular solution and its derivative

$$V_p(t) = B \cos(t) - C \sin(t)$$

$$\frac{d}{dt} V_p(t) = -B \sin(t) - C \cos(t)$$

in the original differential equation

$$\Rightarrow \frac{d}{dt} V_p(t) + V_p(t) = \cos(t)$$


Substituting the particular solution and its derivative

$$V_p(t) = B \cos(t) - C \sin(t)$$

$$\frac{d}{dt} V_p(t) = -B \sin(t) - C \cos(t)$$

in the original differential equation

$$\frac{d}{dt} V_p(t) + V_p(t) = \cos(t)$$


$$\begin{aligned} & -B \sin(t) - C \cos(t) \\ & + B \cos(t) - C \sin(t) = \cos(t) \end{aligned}$$


Substituting the particular solution and its derivative

$$V_p(t) = B \cos(t) - C \sin(t)$$

$$\frac{d}{dt} V_p(t) = -B \sin(t) - C \cos(t)$$

in the original differential equation

$$\frac{d}{dt} V_p(t) + V_p(t) = \cos(t)$$

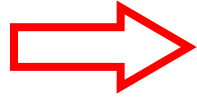

$$\begin{aligned} & -B \sin(t) - C \cos(t) \\ & + B \cos(t) - C \sin(t) = \cos(t) \end{aligned}$$

$$(B - C) \cos(t) - (B + C) \sin(t) = \cos(t)$$

$$(B - C) = 1 \quad (B + C) = 0$$

$$(B - C) = 1$$

$$(B + C) = 0$$




$$B = \frac{1}{2} = A \cos \theta$$

$$C = -\frac{1}{2} = A \sin(\theta)$$

definitions of B and C

$$(B - C) = 1$$

$$(B + C) = 0$$

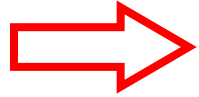

$$B = \frac{1}{2} = A \cos \theta$$


$$C = -\frac{1}{2} = A \sin(\theta)$$

definitions of B and C

From the ratio C/B


$$\frac{C}{B} = \frac{A \sin(\theta)}{A \cos(\theta)} = \tan(\theta) = -1$$

we obtain readily that

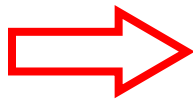

$$\theta = -\frac{\pi}{4}$$

$$\theta = -\frac{\pi}{4}$$

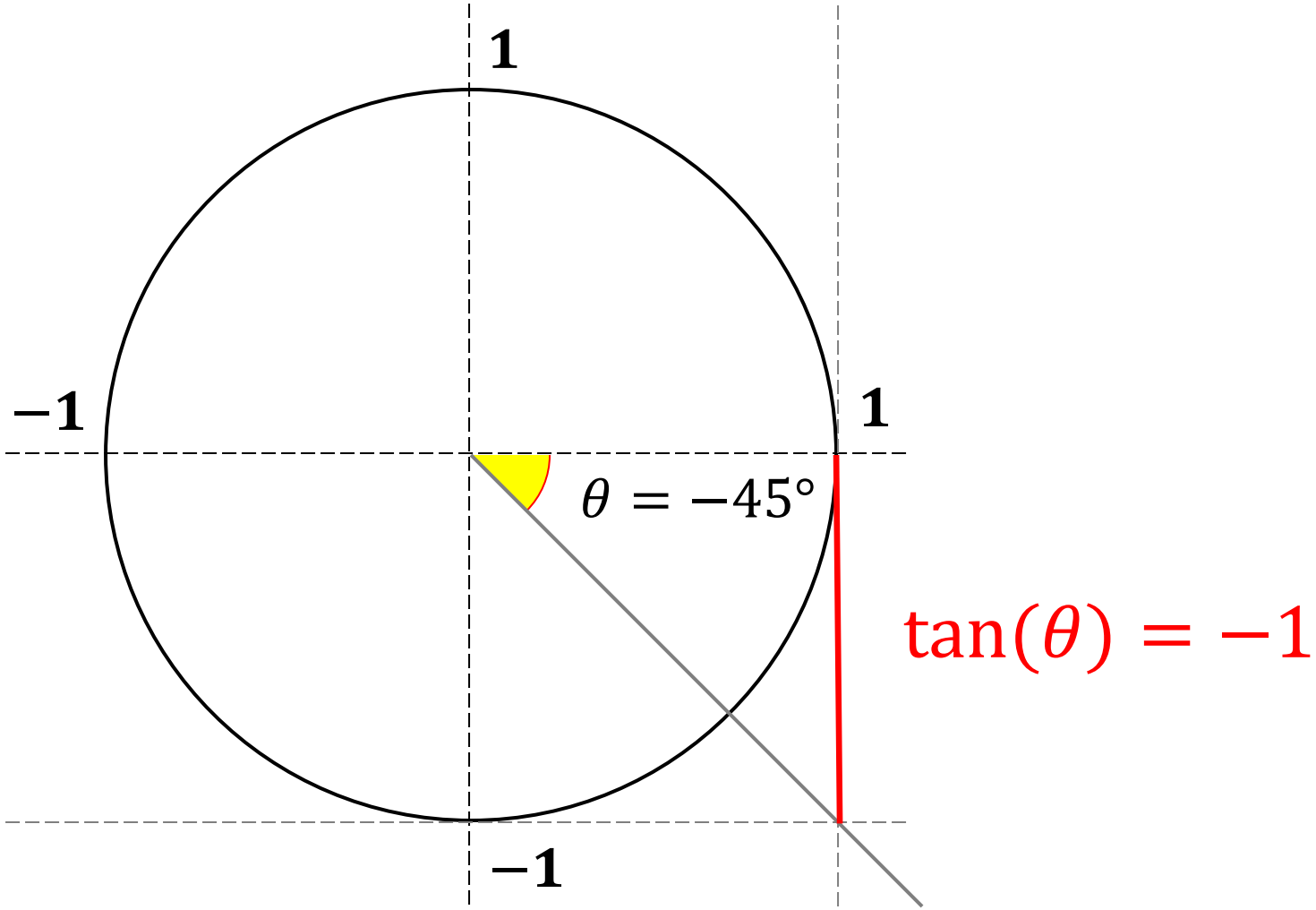


$$B = A \cos \theta = \frac{1}{2}$$

$$C = A \sin(\theta) = -\frac{1}{2}$$

$$B = A \cos \theta = \frac{1}{2}$$

$$C = A \sin(\theta) = -\frac{1}{2}$$


$$A = \frac{1}{2 \cos \theta} = \frac{1}{2 \cos\left(-\frac{\pi}{4}\right)} = \frac{1}{2 \frac{\sqrt{2}}{2}} = \frac{1}{\sqrt{2}}$$

$$B = A \cos \theta = \frac{1}{2}$$

$$C = A \sin(\theta) = -\frac{1}{2}$$

$$A = \frac{1}{2 \cos \theta} = \frac{1}{2 \cos\left(-\frac{\pi}{4}\right)} = \frac{1}{2 \frac{\sqrt{2}}{2}} = \frac{1}{\sqrt{2}}$$

$$A = \frac{-1}{2 \sin \theta} = \frac{-1}{2 \sin\left(-\frac{\pi}{4}\right)} = \frac{-1}{2 \frac{-\sqrt{2}}{2}} = \frac{1}{\sqrt{2}}$$

$$B = A \cos \theta = \frac{1}{2}$$

$$C = A \sin(\theta) = -\frac{1}{2}$$

$$A = \frac{1}{2 \cos \theta} = \frac{1}{2 \cos\left(-\frac{\pi}{4}\right)} = \frac{1}{2 \frac{\sqrt{2}}{2}} = \frac{1}{\sqrt{2}}$$

$$A = \frac{-1}{2 \sin \theta} = \frac{-1}{2 \sin\left(-\frac{\pi}{4}\right)} = \frac{-1}{2 \frac{-\sqrt{2}}{2}} = \frac{1}{\sqrt{2}}$$

$$A = \frac{1}{\sqrt{2}}$$

From these results, the particular solution is

$$V_p(t) = A \cos(t + \theta) = \frac{1}{\sqrt{2}} \cos\left(t - \frac{\pi}{4}\right)$$

and the complete solution is

$$V_C(t) = K_1 e^{-t} + \frac{1}{\sqrt{2}} \cos\left(t - \frac{\pi}{4}\right)$$

From these results, the particular solution is

$$V_p(t) = A \cos(t + \theta) = \frac{1}{\sqrt{2}} \cos\left(t - \frac{\pi}{4}\right)$$

and the complete solution is



$$V_C(t) = K_1 e^{-t} + \frac{1}{\sqrt{2}} \cos\left(t - \frac{\pi}{4}\right)$$


At $t = 0^+$

$$0 = K_1 + \frac{1}{\sqrt{2}} \cos\left(-\frac{\pi}{4}\right) = K_1 + \frac{1}{2} \Rightarrow K_1 = -\frac{1}{2}$$

Finally:
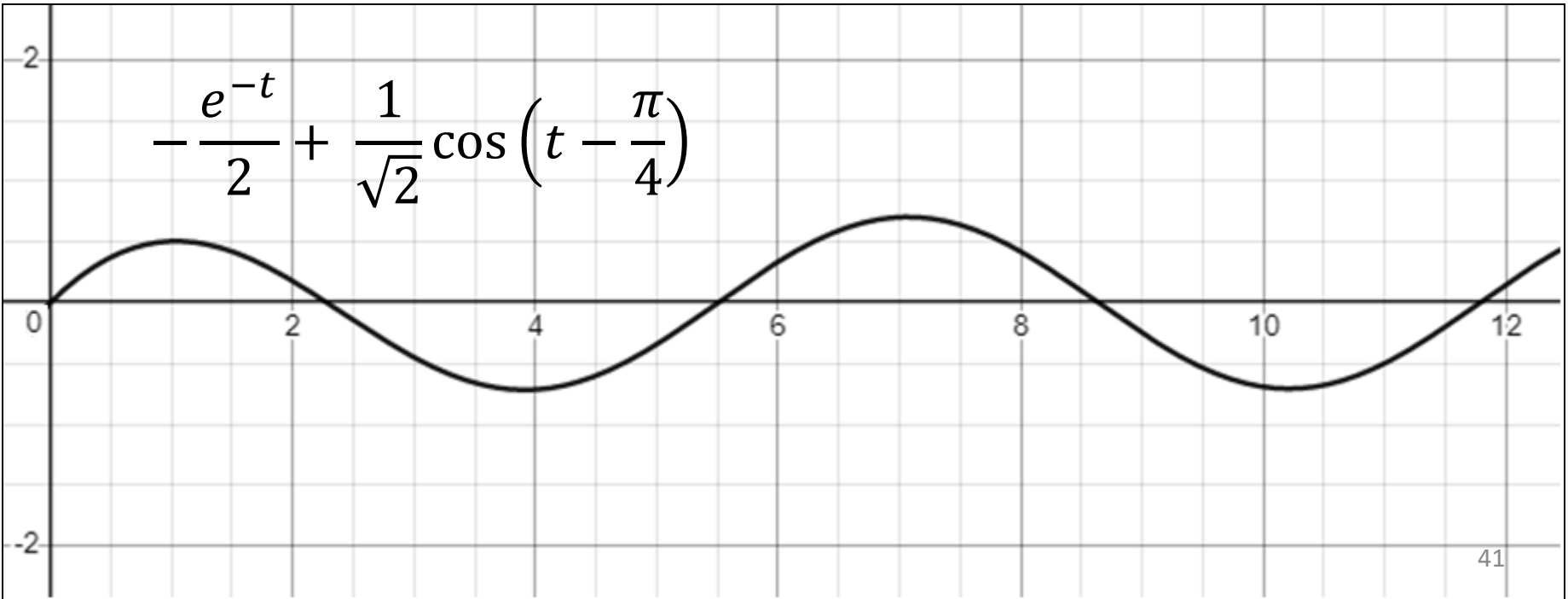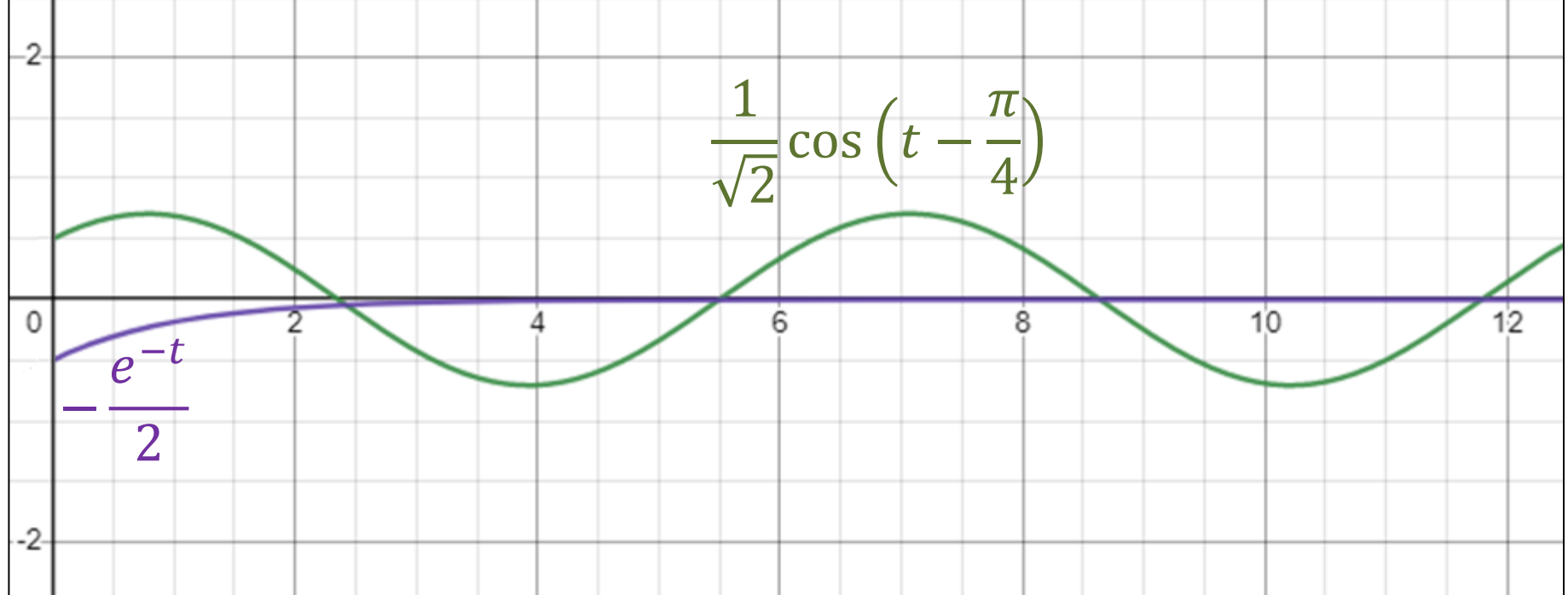
$$V_C(t) = -\frac{e^{-t}}{2} + \frac{1}{\sqrt{2}} \cos\left(t - \frac{\pi}{4}\right)$$



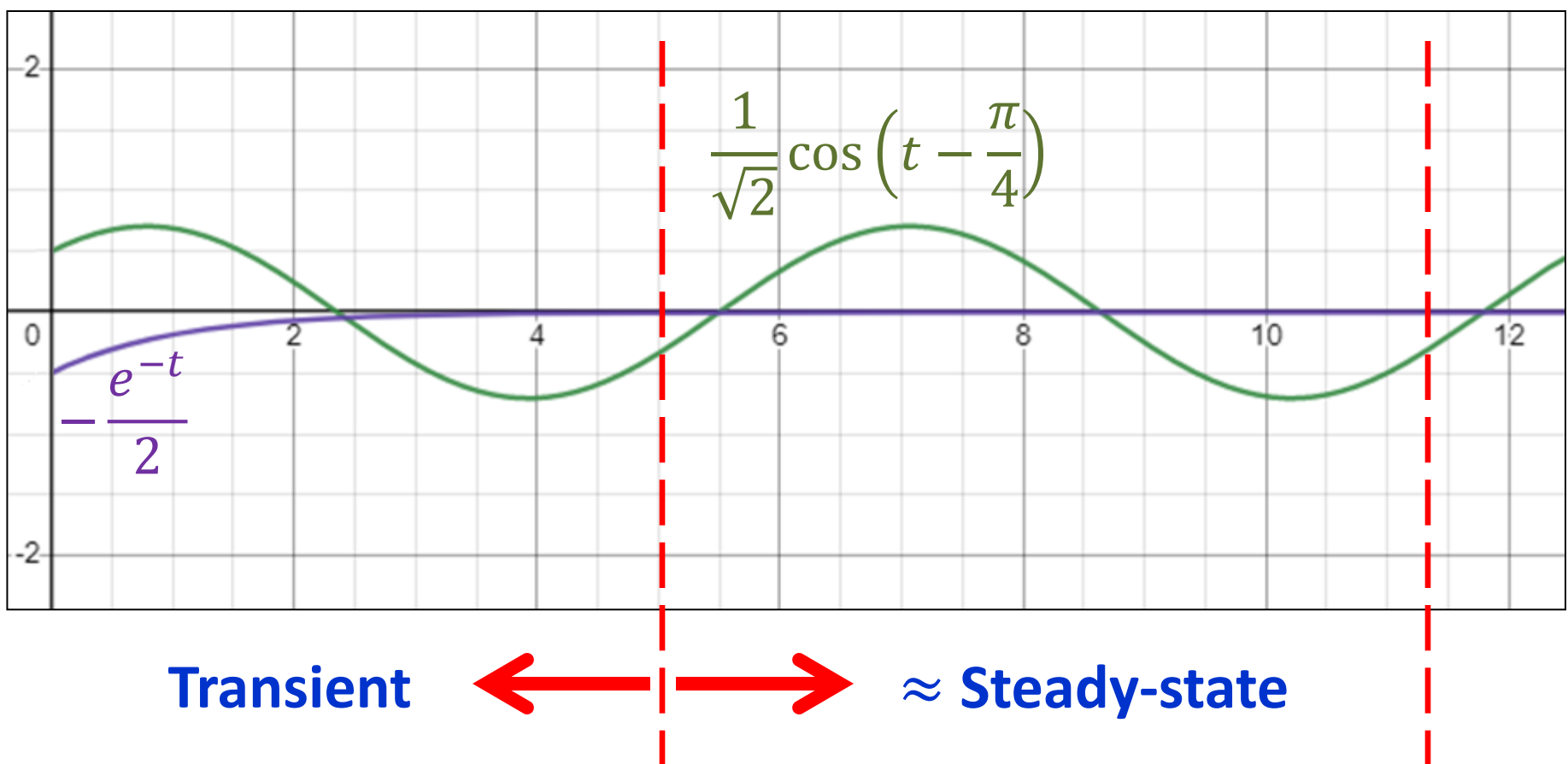

In many practical situations the transients are very short. We are interested in describing steady-state system response with a more immediate mathematical approach for a **specified frequency of operation**. This will be accomplished next by introducing the **phasor** formalism.


ECE 205 - HW 7
Written

Name:

UIN:

- Using KCL and the v - i relations for resistors and capacitors, show that the voltage $v(t)$ in the following circuit satisfies the following ODE if $R = 5\Omega$ and $C = 2F$. Also find the capacitor voltage $v(t)$ if $i_s(t) = \cos(t)$. Assume zero initial conditions.
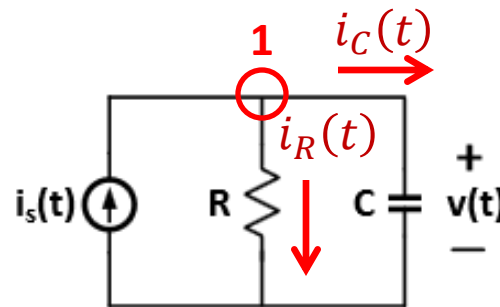
$$2\frac{dv}{dt} + \frac{1}{5}v(t) = i_s(t) \text{ for } t > 0.$$



Hints: Write the KCL at node 1 to verify the given differential equation

Rewrite the equation in the form $\frac{d}{dt}v(t) + a v(t) = b f(t)$

and follow the procedure we outlined today to find $v(t)$