

ECE 205 “Electrical and Electronics Circuits”

Spring 2024 – LECTURE 23

MWF – 12:00pm

Prof. Umberto Ravaioli


2062 ECE Building

Lecture 23 – Summary


Learning Objectives

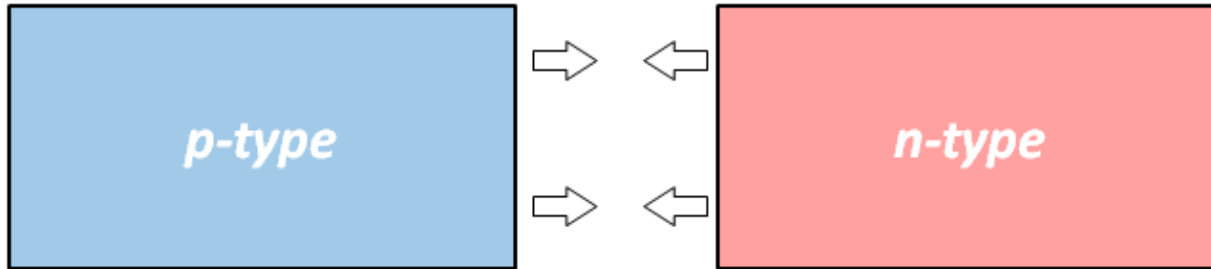1. Solution of circuits with p - n junction diodes


A p - n junction is obtained when two regions of semiconductor with different type of dopants are in contact



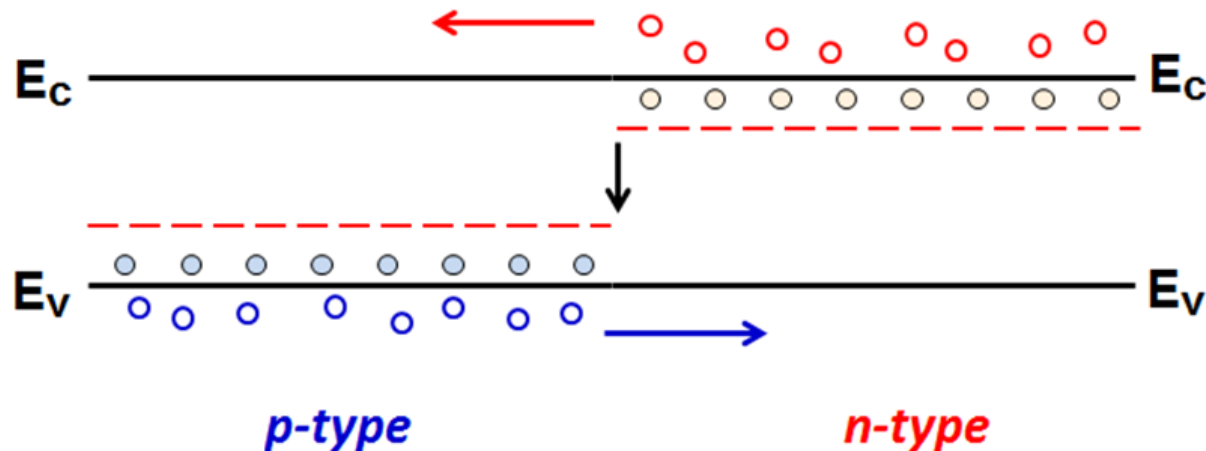
The two sides have different **electrochemical potential** due to the different doping and equilibrium is reached when a certain region about the junction is depleted of holes on the p-side and of electrons on the n-side.



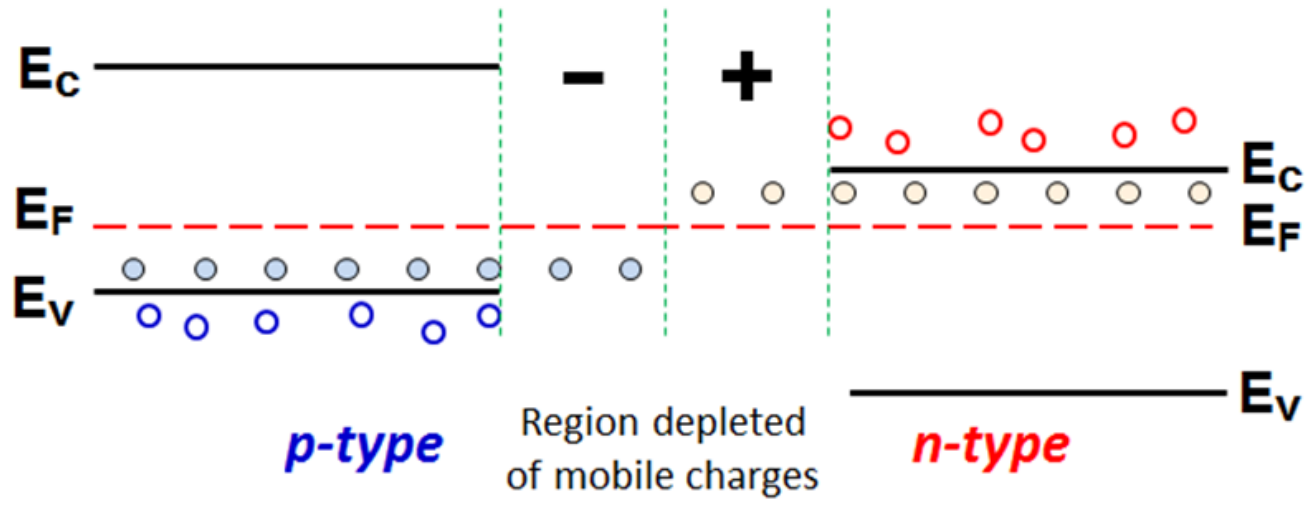
The fixed charge dipole creates a potential barrier preventing further movement of electrons and holes across the junction



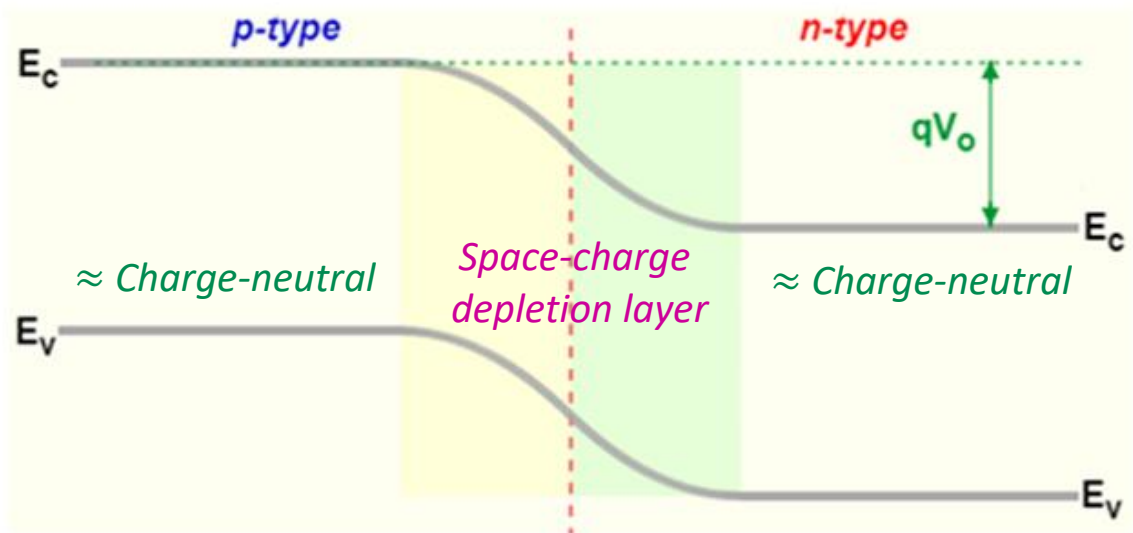Equilibrium potential barrier – No current flows




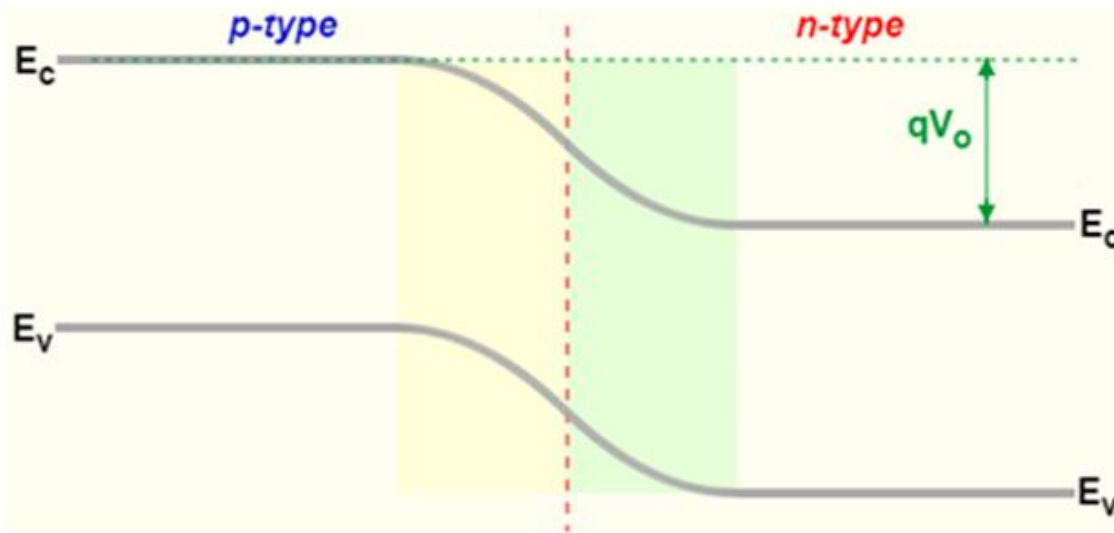Equilibrium potential barrier – No current flows




No potential applied

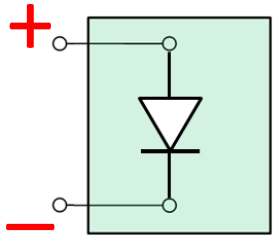Barrier is lowered – electrons and hole can diffuse across junction




Forward potential applied

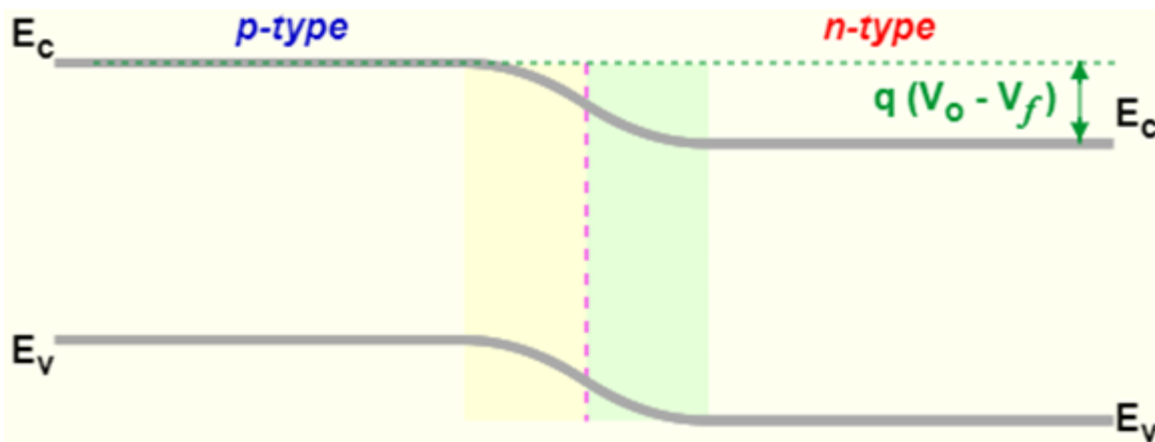


The depletion layer shrinks

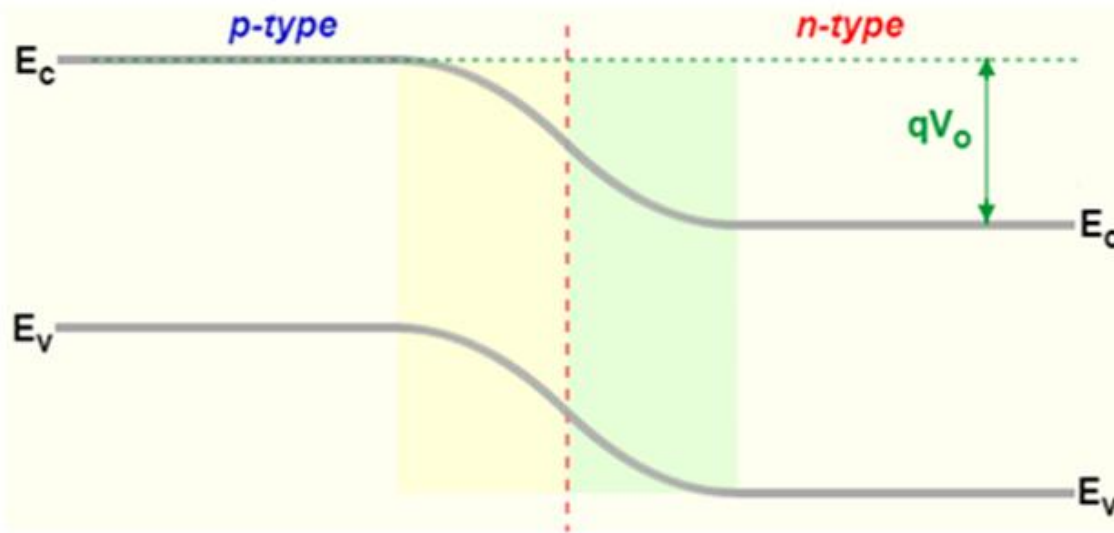Equilibrium potential barrier – No current flow




No potential applied

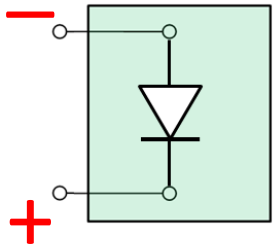Barrier is higher – Electrons and holes cannot diffuse across junction



Reverse potential applied

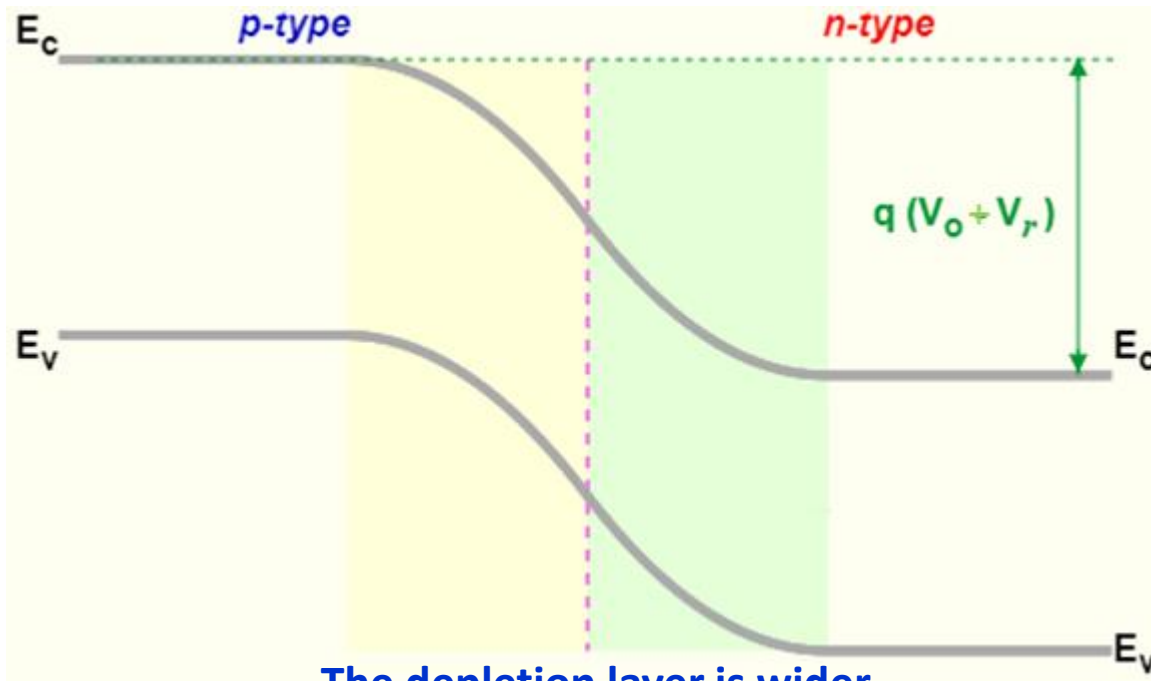


The depletion layer is wider

Equilibrium

\approx Charge-neutral


Space-charge depletion layer

\approx Charge-neutral

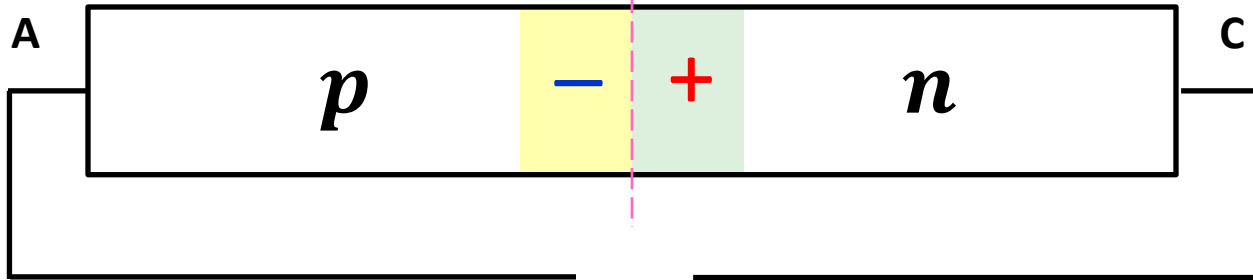


No potential applied


Forward bias

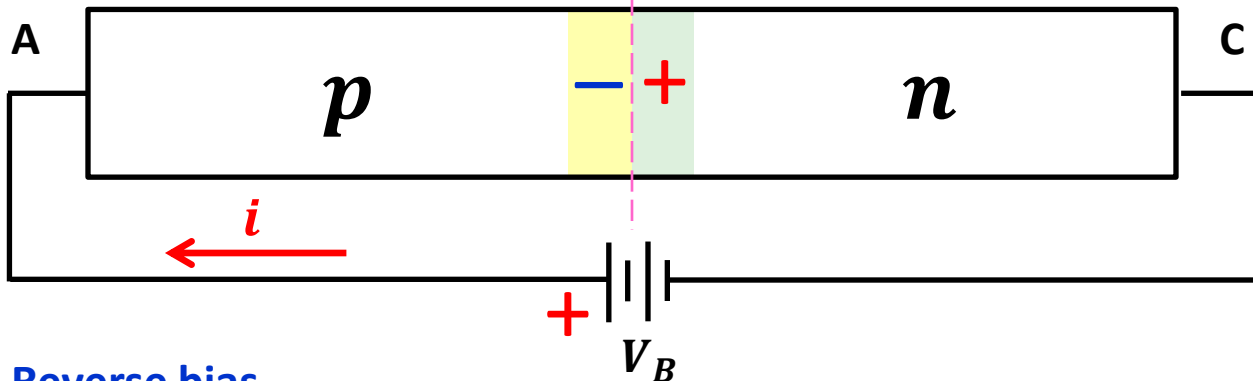


$$V_A > V_C$$

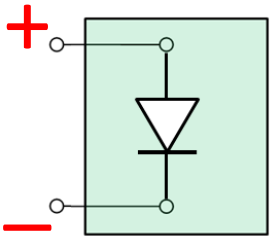


Reverse bias

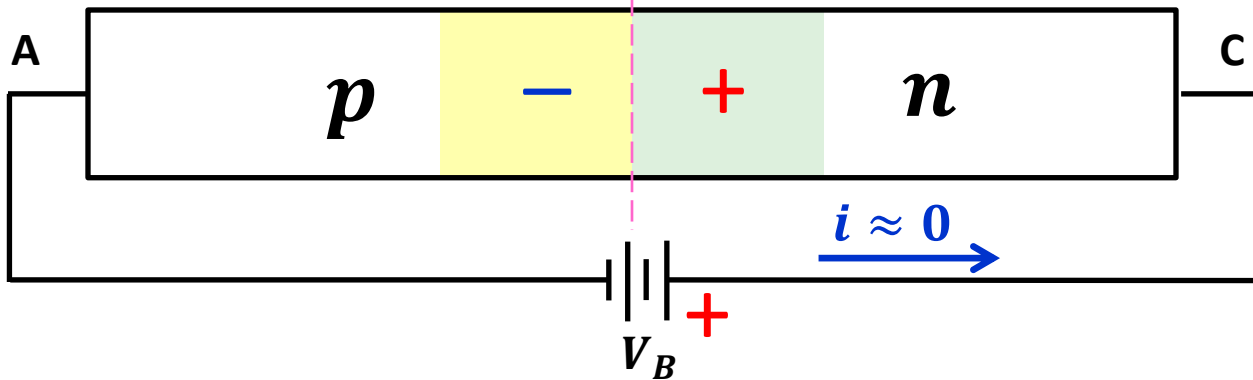


$$V_A < V_C$$

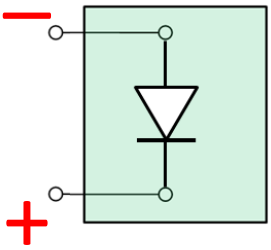

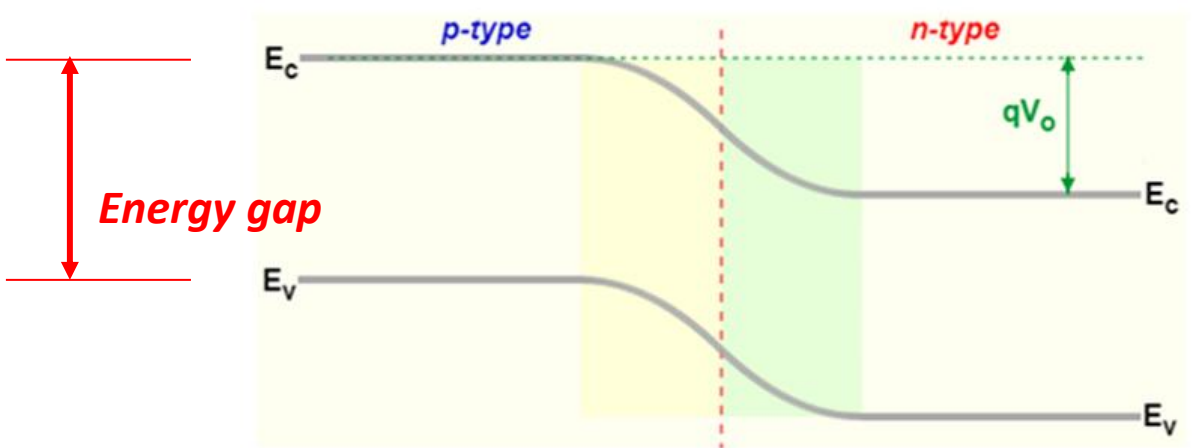
The voltage threshold (in Volts) of the diode is a bit smaller than the energy gap (in electron Volts) of the material used. Silicon has energy gap $E_g \approx 1.2\text{eV}$ and $V_F \approx 0.6$ to 0.8V .




surface

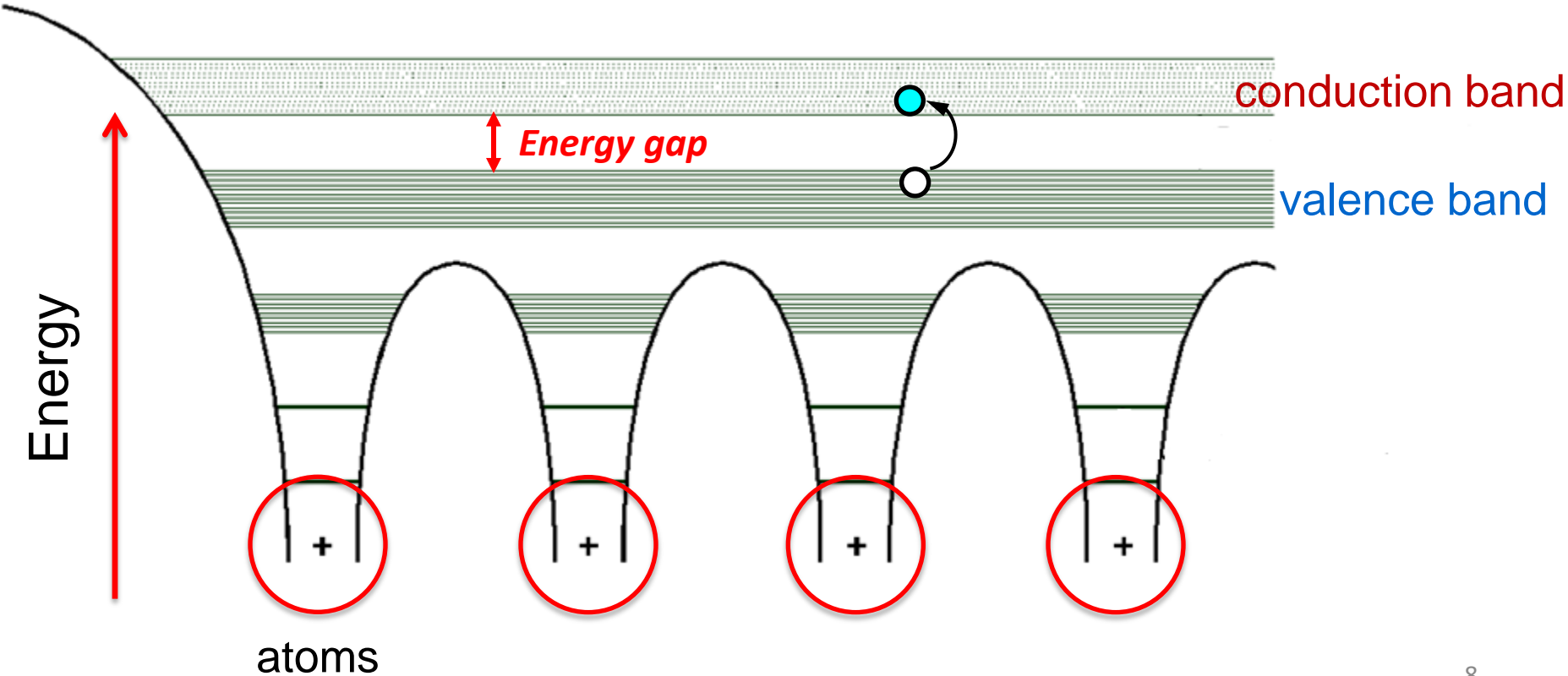

Ideal diode model for circuit analysis

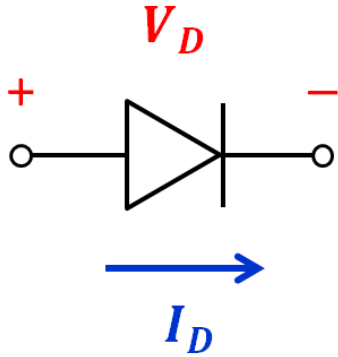

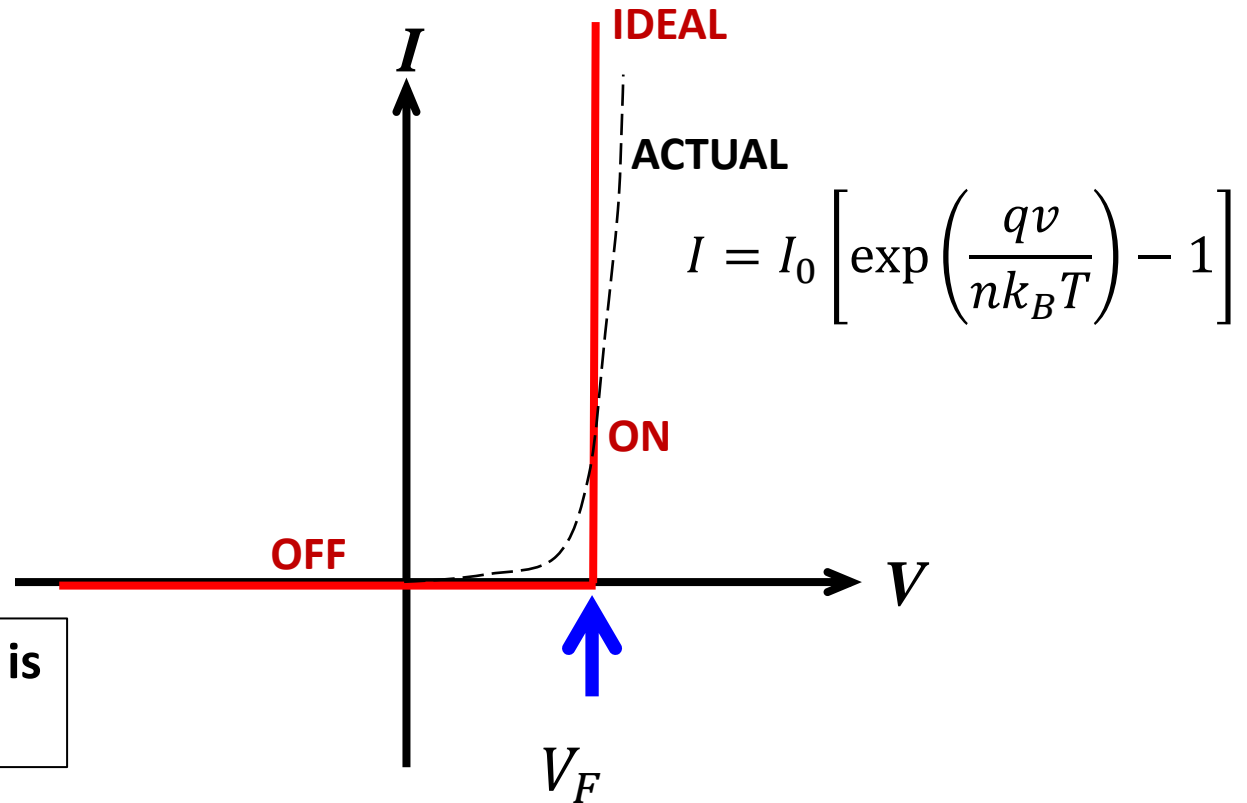Typical value for Si diodes is
 $V_F = 0.7 \text{ V}$



$$V_D < V_F$$

Diode is OFF

$$V_D = V_F$$

Diode is ON

Diode circuit analysis

Diodes are non-linear devices, and we cannot state *a priori* whether a diode is ON or OFF. Therefore, we can start a problem by making an assumption.

Diode circuit analysis

Diodes are non-linear devices, and we cannot state *a priori* whether a diode is ON or OFF. Therefore, we can start a problem by making an assumption.

If we assume that a diode is conducting (ON), the voltage from anode to cathode is “pinned” to the threshold voltage V_F and we solve the circuit with KVL and KCL linear equations, by imposing that voltage. If the result is *physical*, we accept it.


Diode circuit analysis

Diodes are non-linear devices, and we cannot state *a priori* whether a diode is ON or OFF. Therefore, we can start a problem by making an assumption.

If we assume that a diode is conducting (ON), the voltage from anode to cathode is “pinned” to the threshold voltage V_F and we solve the circuit with KVL and KCL linear equations, by imposing that voltage. If the result is *physical*, we accept it.

If instead the assumption has generated *unphysical* results, there is a contradiction and we solve the problem again, imposing that the diode is equivalent to an open circuit (OFF).

Example 1A – Solve for I_D

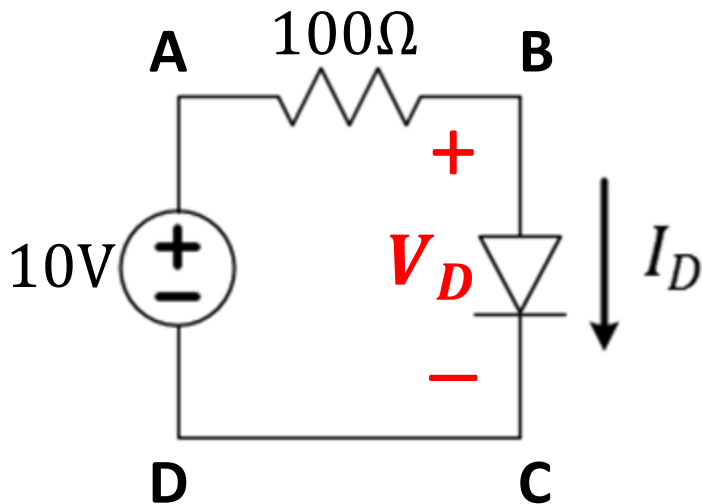

Assume $V_F = 0.7 \text{ V}$

Assume that the diode is conducting (there must be 0.7V across the diode)

KVL $V_{AB} + V_{BC} + V_{CD} + V_{DA} = 0$


$$100I_D + 0.7 - 10 = 0$$

$$I_D = 9.3\text{V}/100\ \Omega = 93\text{mA}$$

CHECK: $I_D > 0$ and it flows from Anode to Cathode

Results follow expected physics and there is no contradiction. OK

Example 1B – Solve for I_D

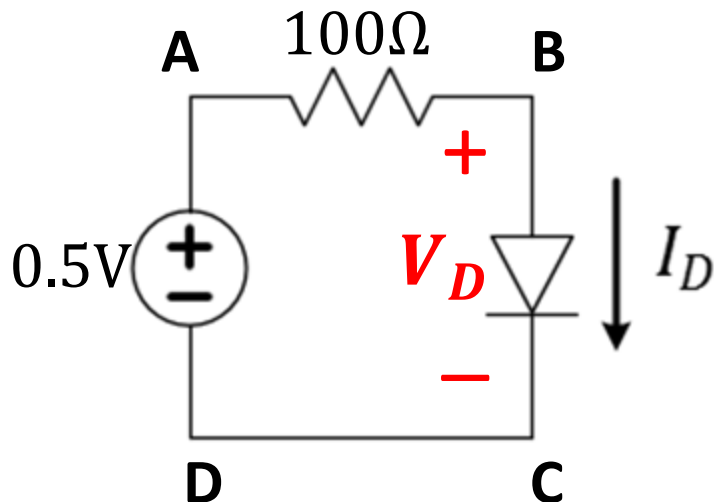

Assume $V_F = 0.7 \text{ V}$

Assume that the diode is conducting (there must be 0.7V across the diode)

KVL $V_{AB} + V_{BC} + V_{CD} + V_{DA} = 0$

$$100I_D + 0.7 - 0.5 = 0$$


$$I_D = (0.5\text{V} - 0.7\text{V})/100 \Omega = -2\text{mA}$$

CHECK: $I_D < 0$ and it flows from Cathode to Anode

Physics is incorrect. Also, DIODE cannot provide power. There is contradiction.


Conclusion: Diode is OFF and $I_D = 0\text{V}$

Example 2: Solve for I_D

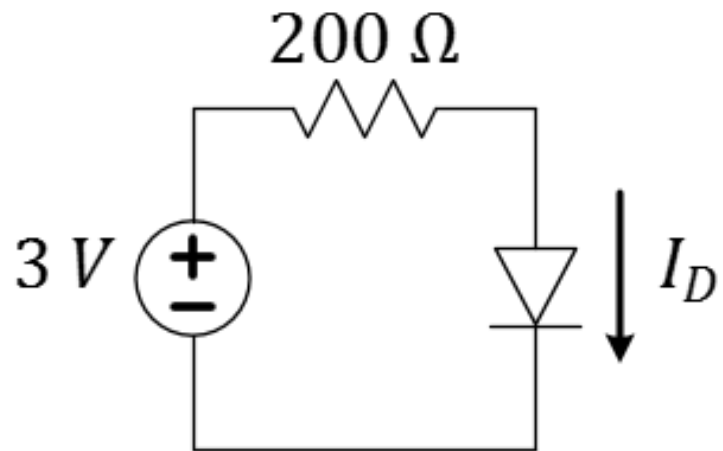

Assume $V_F = 0.7 \text{ V}$


Example 2: Solve for I_D

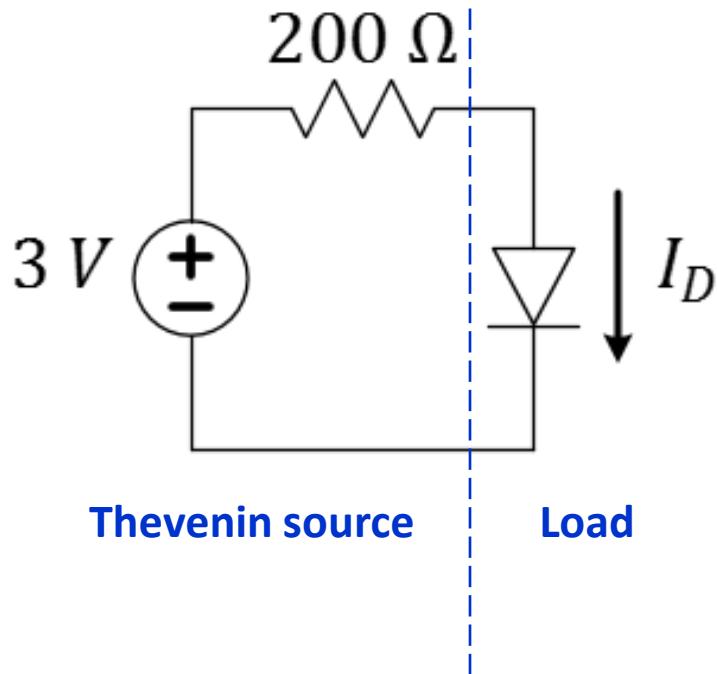

Assume $V_F = 0.7 \text{ V}$

Let's solve with the I-V curve.
First, characterize the source.

Example 2: Solve for I_D

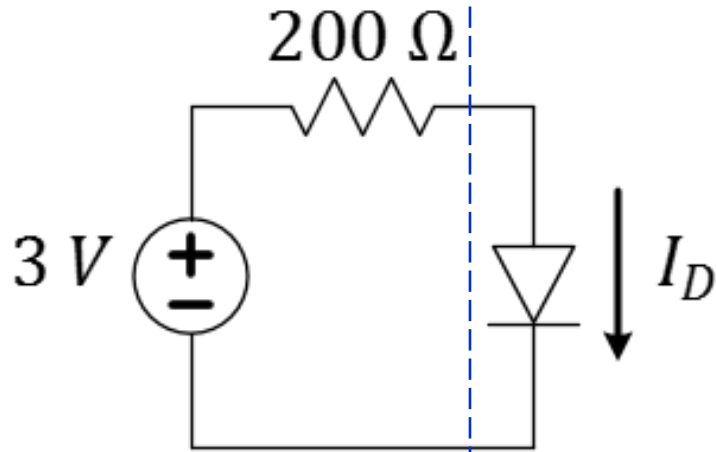

Thevenin source


Load

$$I_{sc} = \frac{3}{200} = 15\text{mA}$$

$$I_{sc} = 15\text{mA}$$


Assume $V_F = 0.7\text{ V}$

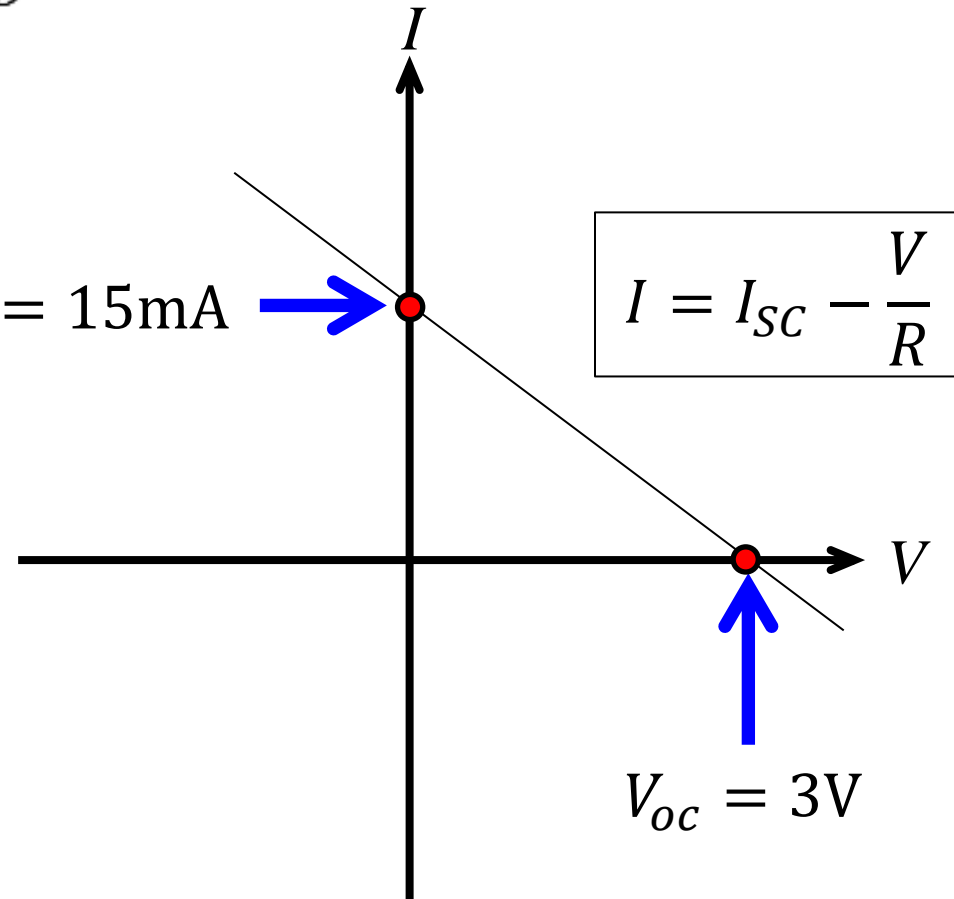Let's solve with the I-V curve.
First, characterize the source.



Assume $V_F = 0.7\text{ V}$

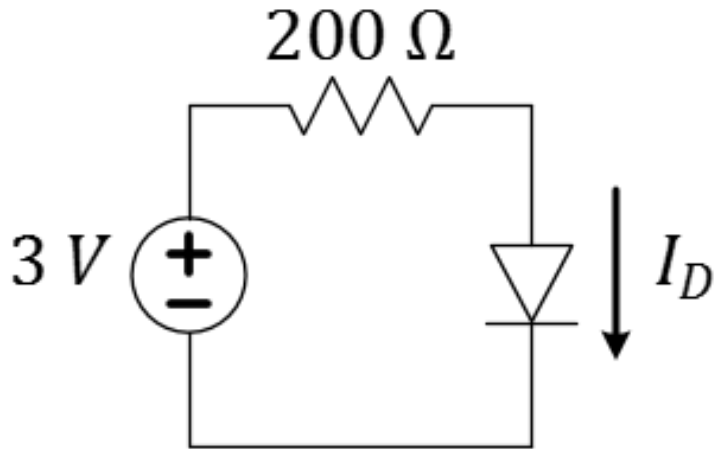Assume that the diode is conducting
The diode is included in the KVL as a virtual voltage source of 0.7 V .




$$I_{sc} = \frac{3}{200} = 15\text{mA}$$

$$-3 + 200I_D + 0.7 = 0 \quad \text{KVL}$$

$$I_D = \frac{2.3}{200} = 11.5\text{ mA}$$


$$I_{sc} = 15\text{mA}$$

$$I_D = 11.5\text{mA}$$

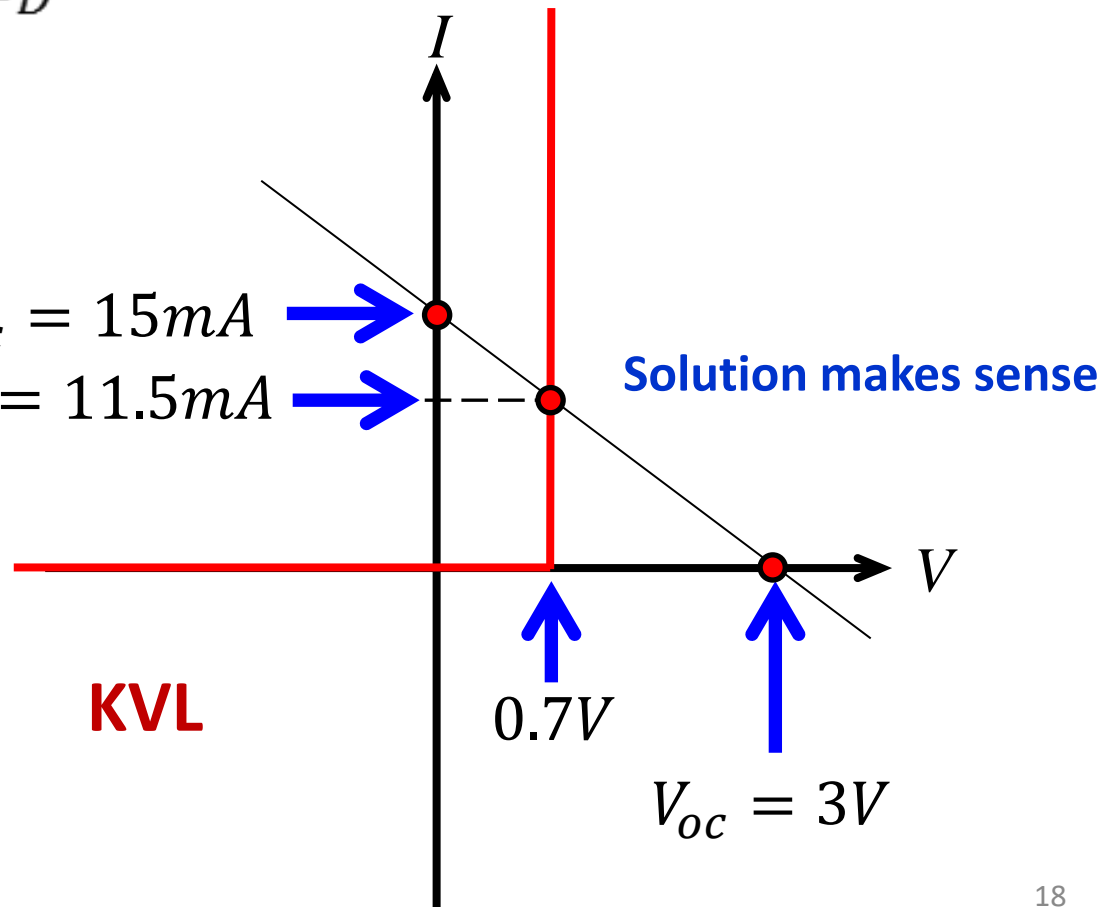

Now reverse the bias

Assume $V_F = 0.7 \text{ V}$

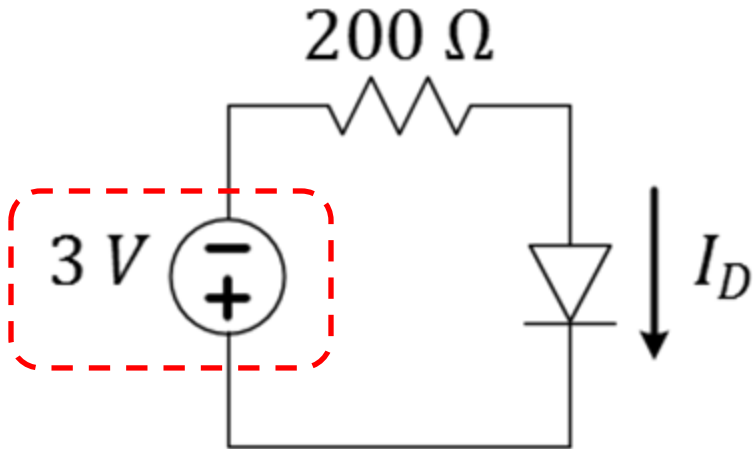


The current is $I_D = -I_0 \approx 0$
(reverse bias current)


In practice, the diode behaves like an open circuit

$$I = I_{SC} - \frac{V}{R}$$

$$I_{SC} = -\frac{3}{200} = -15\text{mA}$$

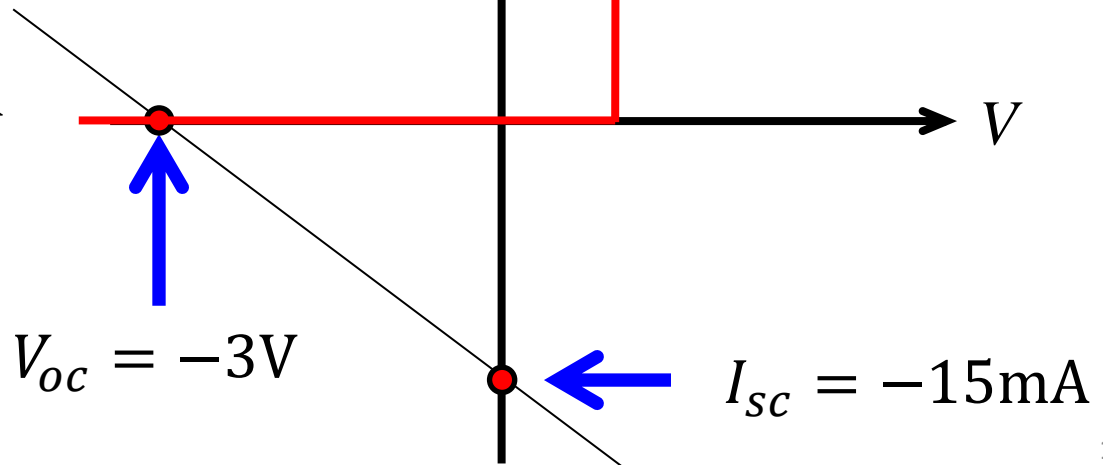

Example 3: Solve for I_D

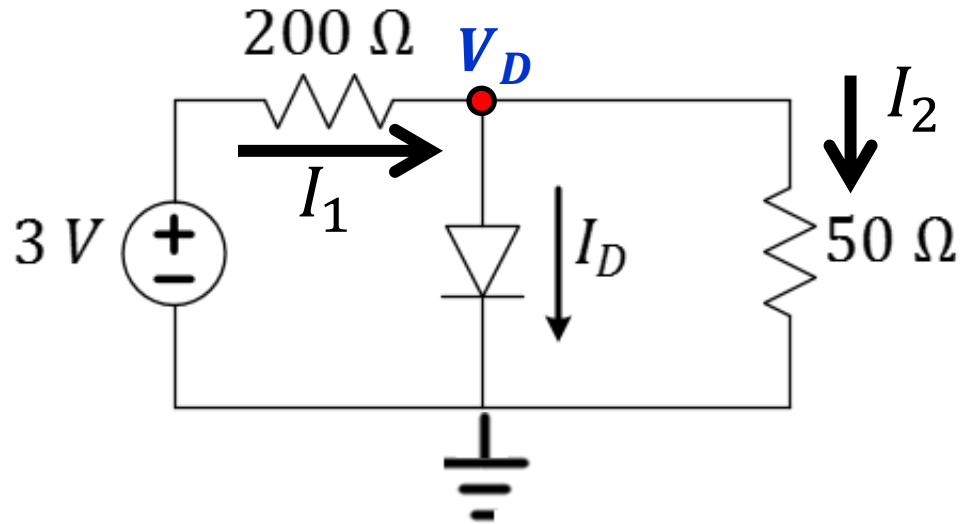


Assume $V_F = 0.7\text{ V}$

Assume that the diode is conducting (there must be 0.7V across the diode)

$$I_1 = \frac{3 - 0.7}{200} = \frac{2.3}{200} = 11.5\text{mA}$$

$$I_2 = \frac{0.7}{50} = 14\text{mA}$$

Example 3: Solve for I_D

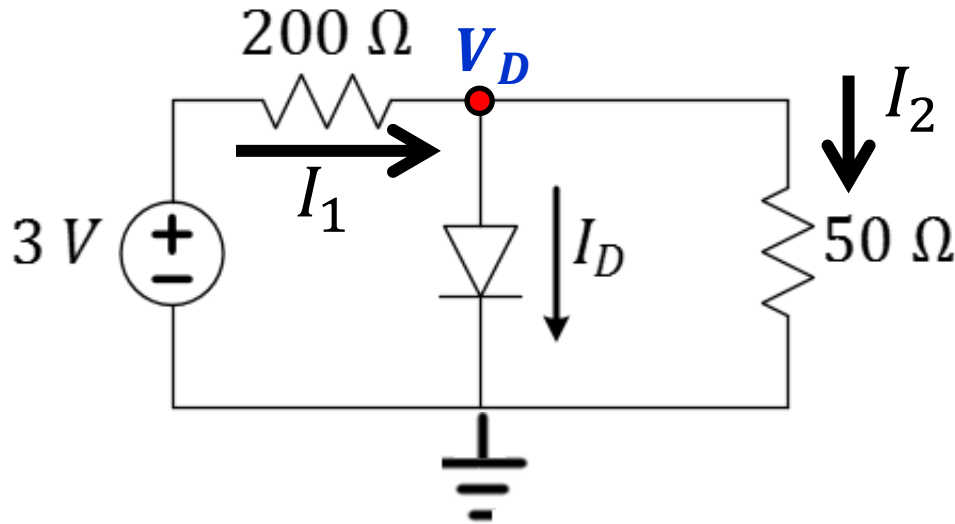

Assume $V_F = 0.7 \text{ V}$

Assume that the diode is conducting (there must be 0.7V across the diode)


$$I_1 = \frac{3 - 0.7}{200} = \frac{2.3}{200} = 11.5 \text{ mA}$$

$$I_2 = \frac{0.7}{50} = 14 \text{ mA}$$

From KCL:

$I_D = I_1 - I_2 = -2.5 \text{ mA} \rightarrow$ NOT PHYSICAL: diode not conducting

Example 3: Solve for I_D

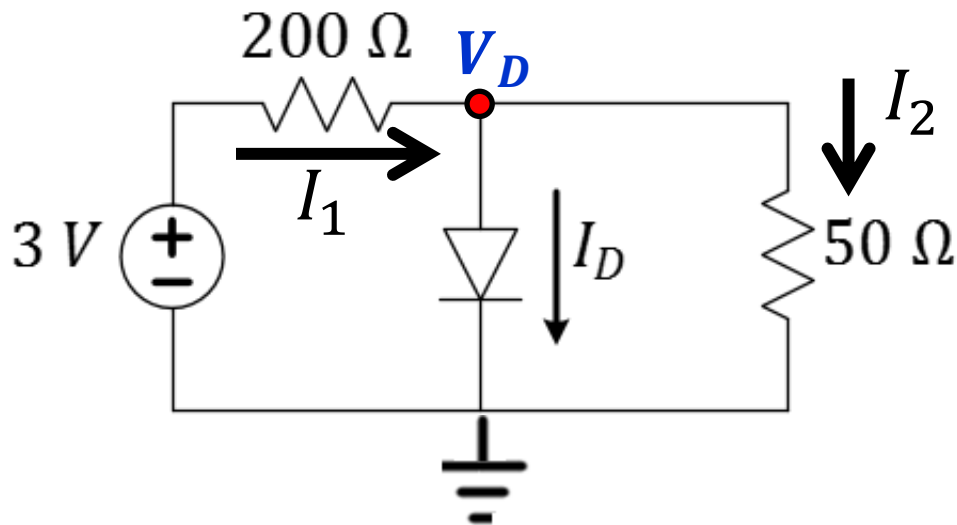

Assume $V_F = 0.7\text{ V}$

Assume that the diode is conducting (there must be 0.7V across the diode)

$$I_1 = \frac{3 - 0.7}{200} = \frac{2.3}{200} = 11.5\text{mA}$$

$$I_2 = \frac{0.7}{50} = 14\text{mA}$$

From KCL:

$$I_D = I_1 - I_2 = -2.5\text{mA} \rightarrow \text{NOT PHYSICAL: diode not conducting}$$

Therefore:

$$I_D = 0$$

$$I_1 = I_2 = \frac{3}{250} = 12\text{mA}$$

$$V_D = I_2 \times 50 = 0.6\text{V}$$



below threshold


or:

$$V_D = 3 \times \frac{50}{250} = 0.6\text{V}$$


from voltage divider

Analysis with IV curve

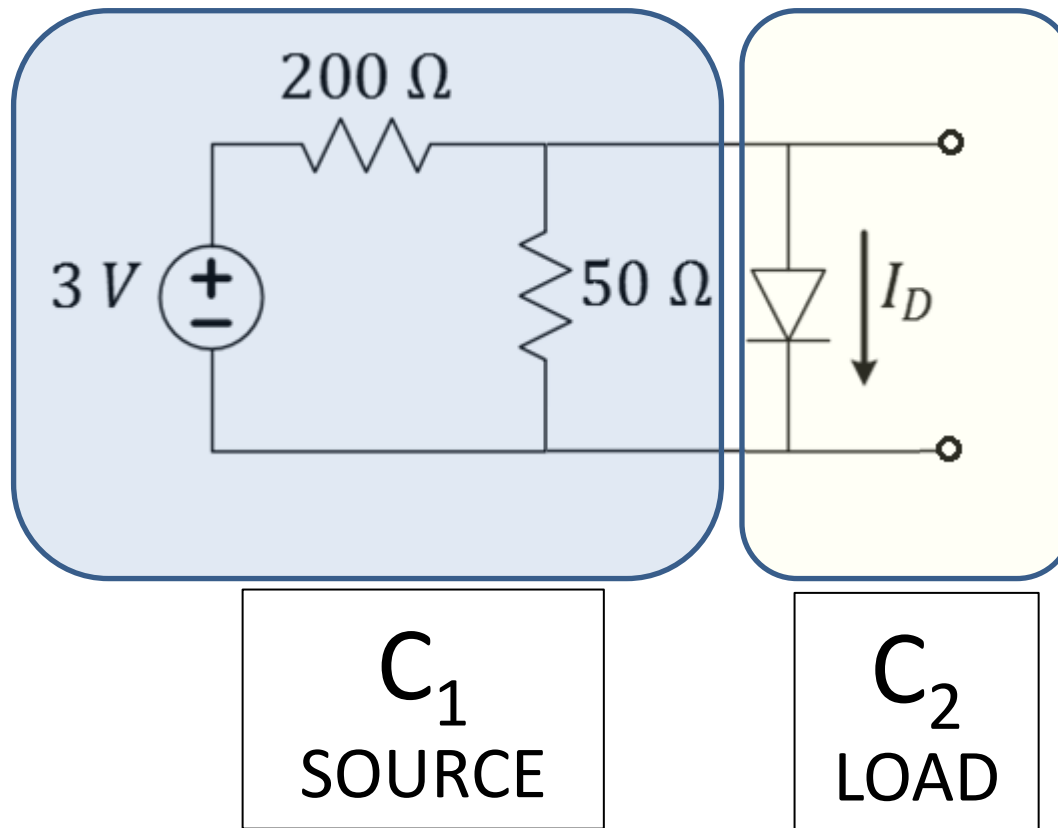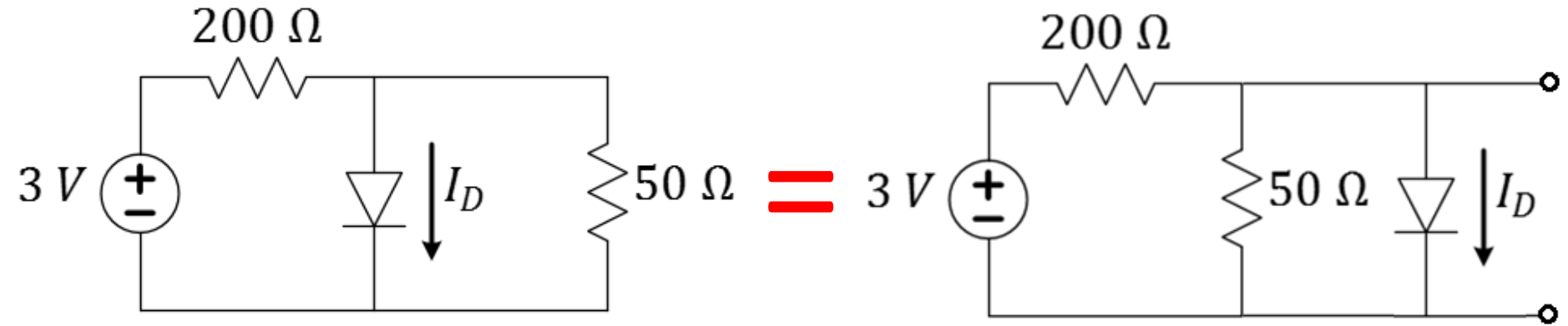

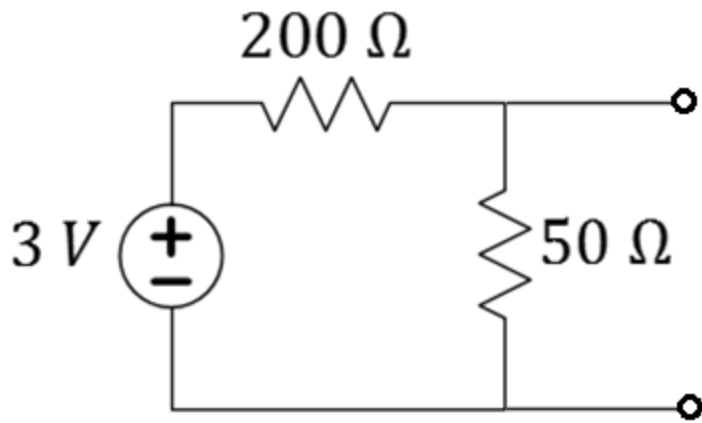

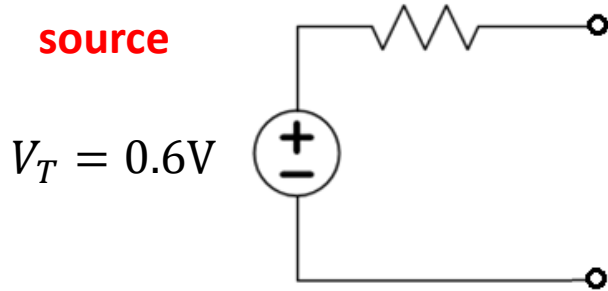Thevenin source
 $R_T = 40\Omega = 200\Omega // 50\Omega$




$V_T = 0.6V$


$$V_{OC} = V_T = 3 \frac{50}{200 + 50} = 0.6V$$

$$I_{SC} = \frac{3}{200} = \frac{V_T}{R_T} = \frac{0.6}{40} = 0.015A = 15mA$$


$I_{SC} = 15mA$

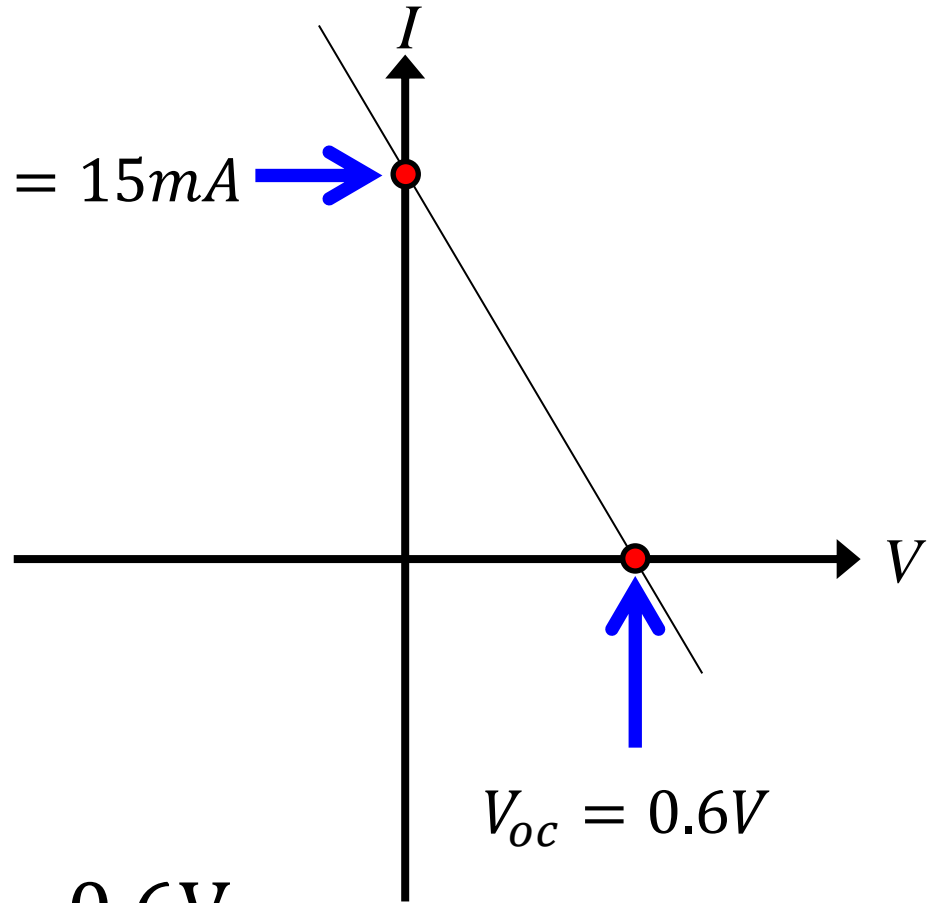


$V_{oc} = 0.6V$

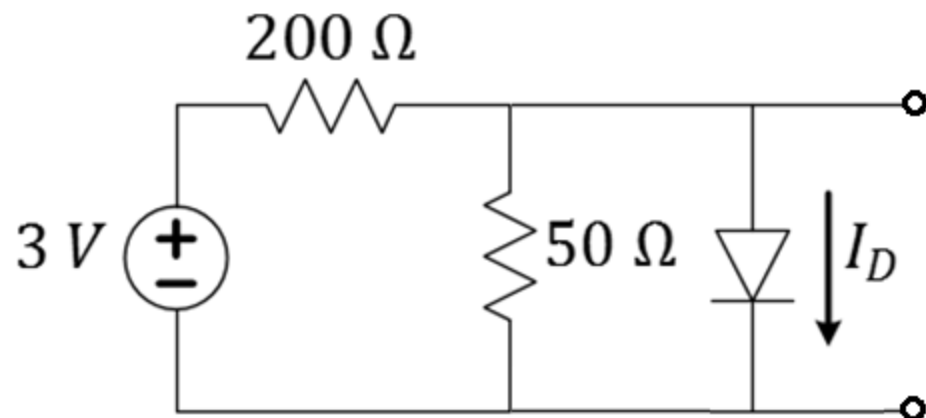

$$I_{sc} = 15mA$$

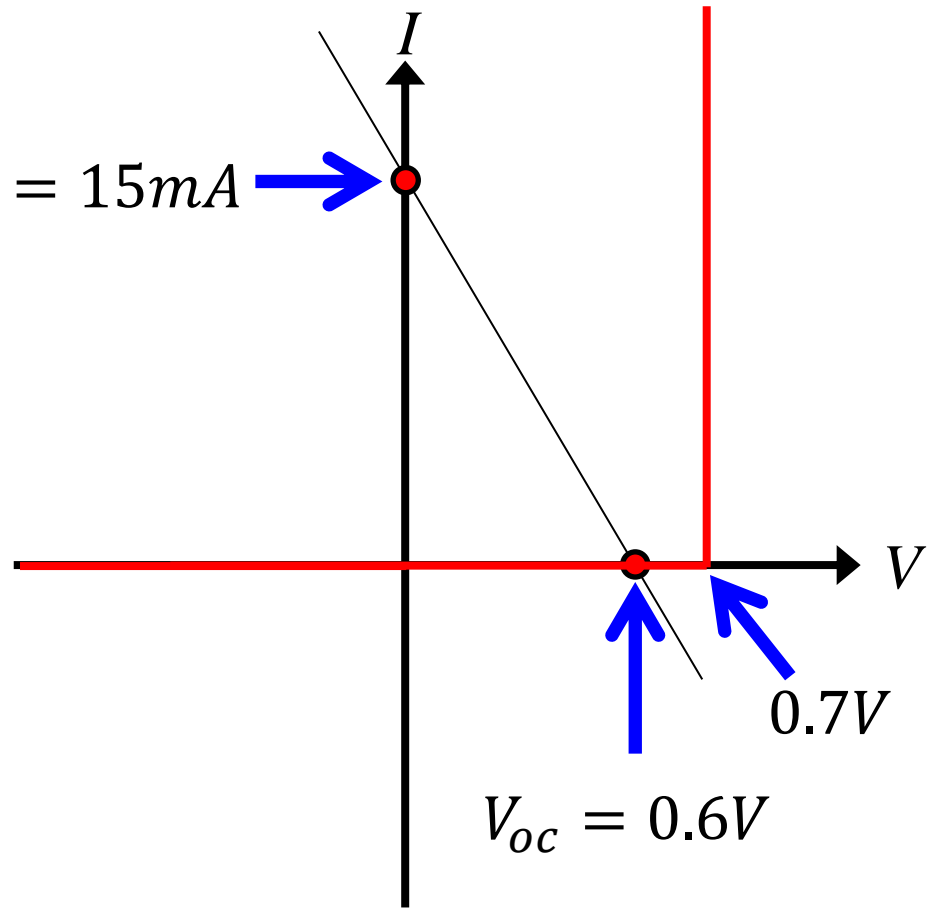


Diode is OFF

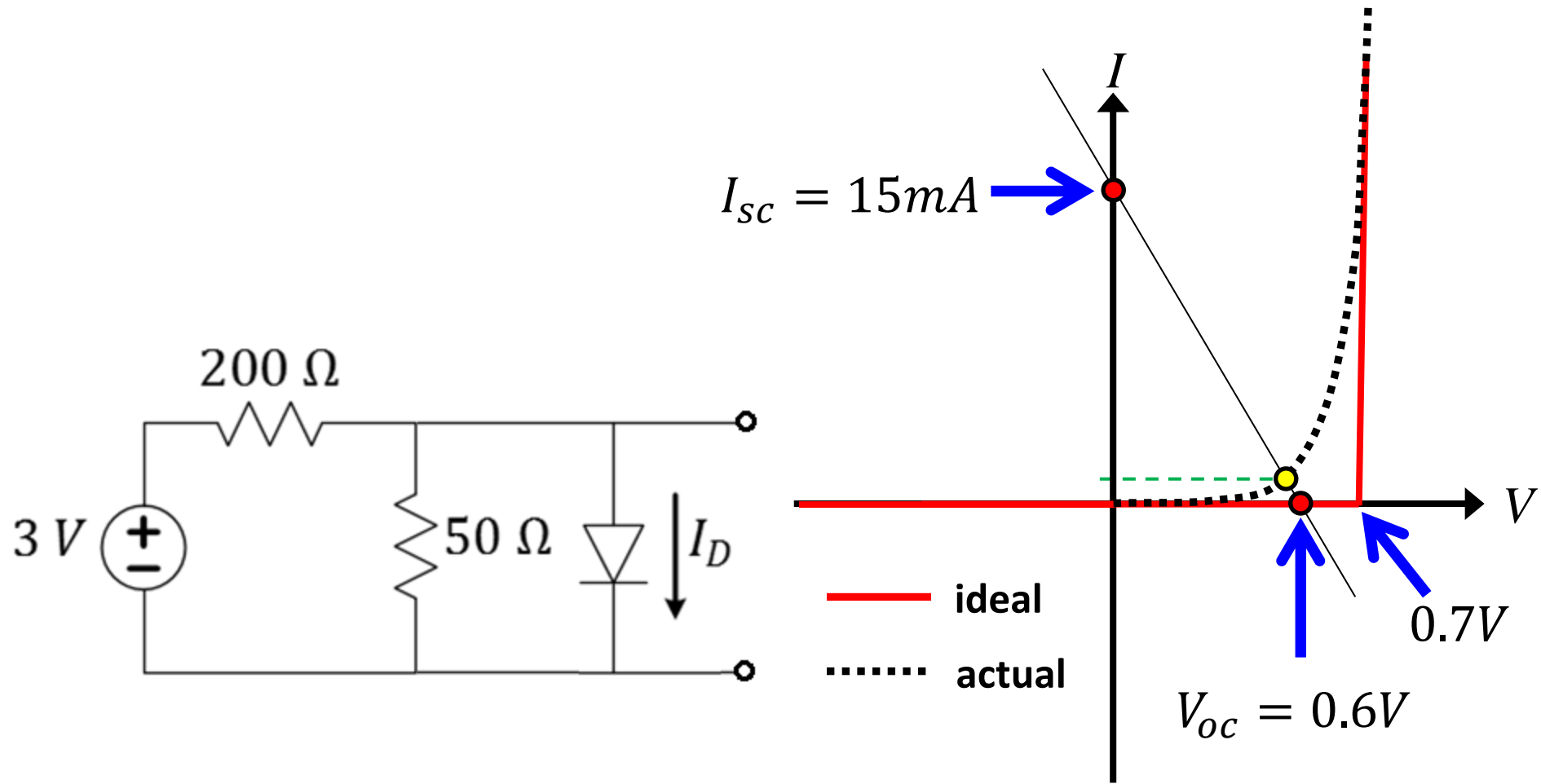

Considering an actual I-V characteristic curve, there is a small current flowing, but it is practically negligible.


Example 4A: Solve for I

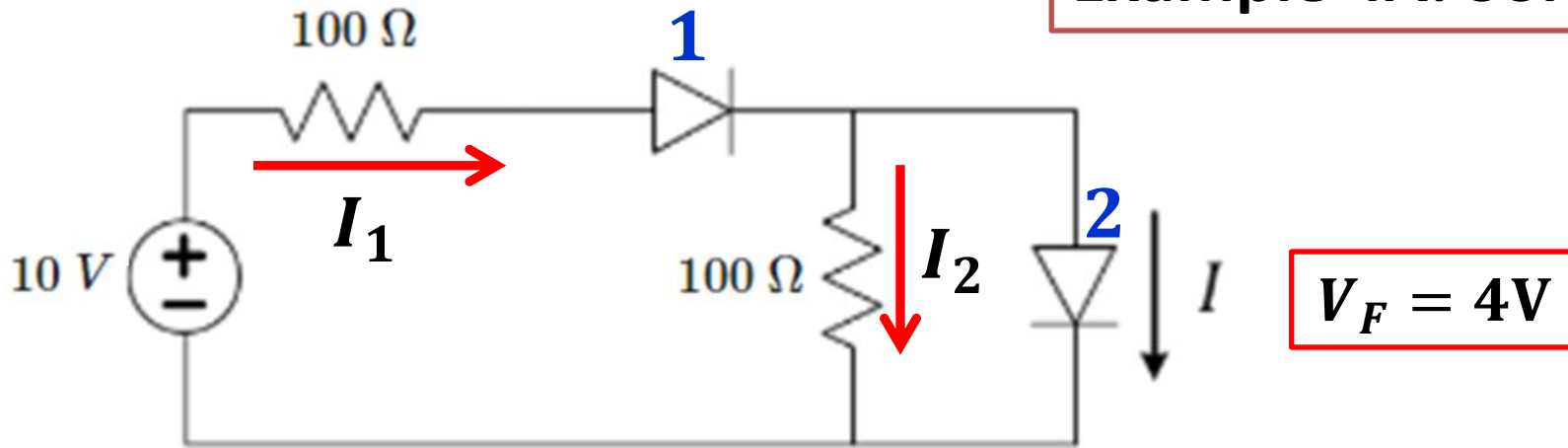

Assume both diodes conduct

$$I_1 = I_2 + I$$

Example 4A: Solve for I

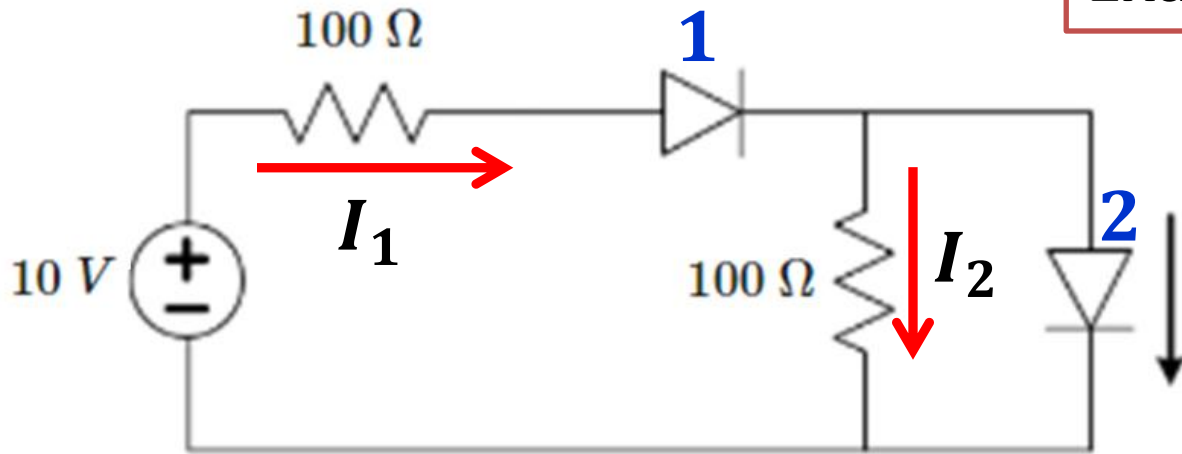

Assume both diodes conduct

$$I_1 = I_2 + I$$

KVL

$$-10 + 100I_1 + 4 + 4 = 0$$


$$I_1 = \frac{2}{100} = 20\text{mA}$$

$$I_2 = \frac{4}{100} = 40\text{mA}$$

But $I_2 > I_1 \rightarrow$ diode **2** cannot conduct

$$I = 0$$

Example 4A: Solve for I

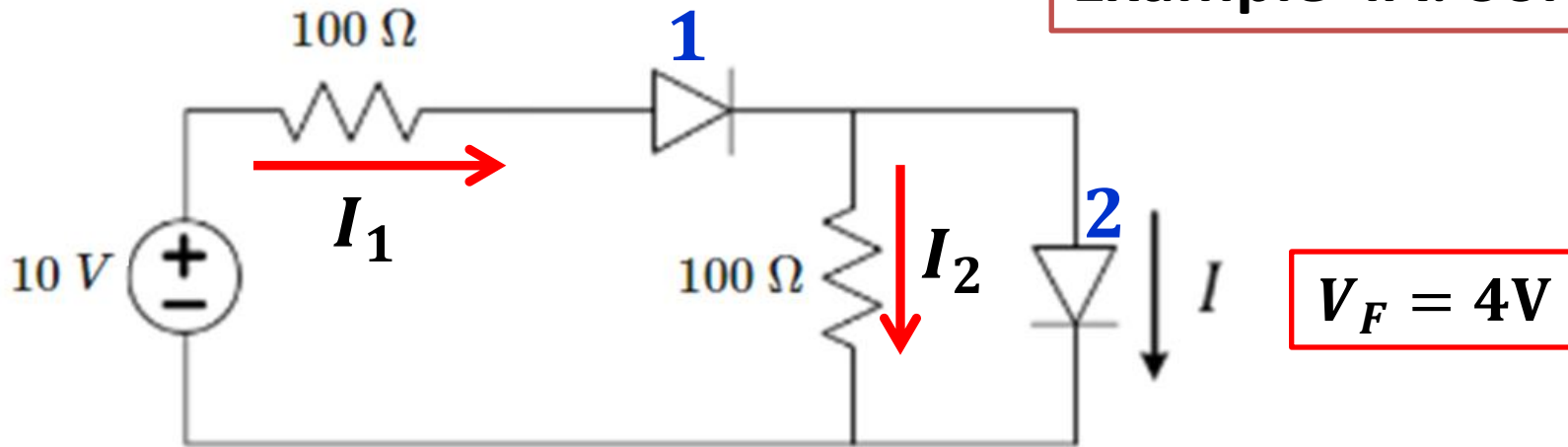

Assume both diodes conduct

$$I_1 = I_2 + I$$

KVL

$$-10 + 100I_1 + 4 + 4 = 0$$

$$I_1 = \frac{2}{100} = 20\text{mA}$$

$$I_2 = \frac{4}{100} = 40\text{mA}$$


But $I_2 > I_1 \rightarrow$ diode 2 cannot conduct

$$I = 0$$

new KVL with diode 2 open circuit

$$-10 + 100I_1 + 4 + 100I_1 = 0$$

$$I_1 = \frac{6}{200} = 30\text{mA}$$


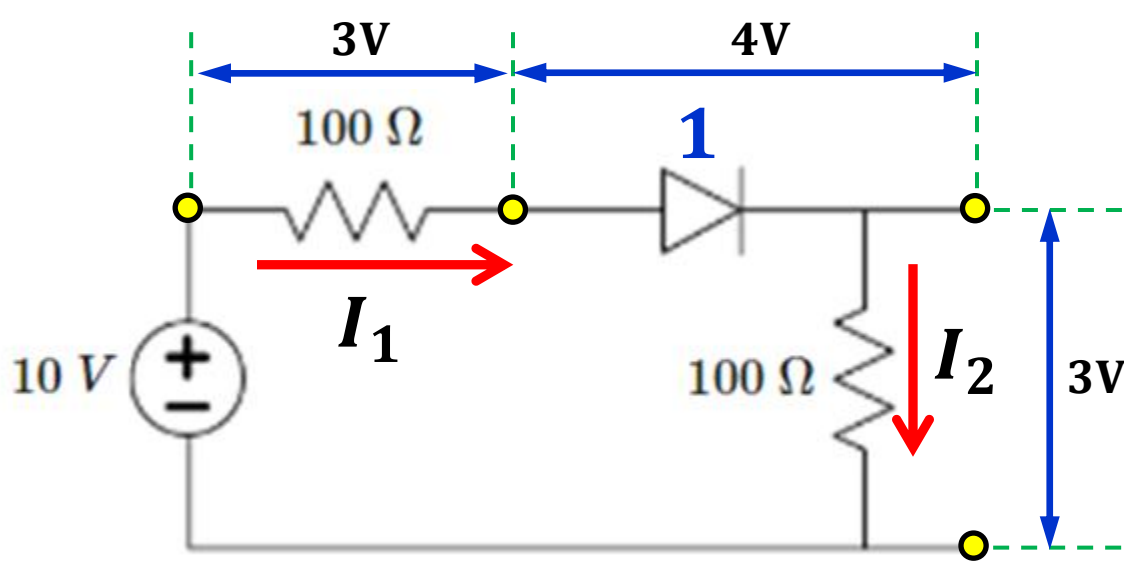


$$I = 0$$


$$V_F = 4\text{ V}$$

$$I_1 = I_2 = 30\text{ mA}$$


Only diode 1 conducts. The two resistors drop 3V each.

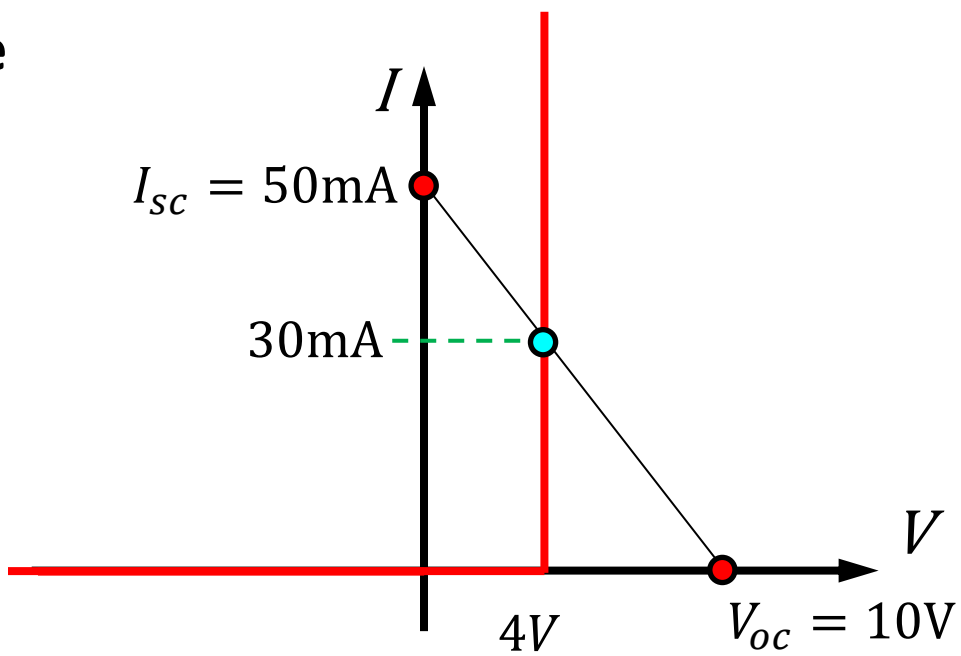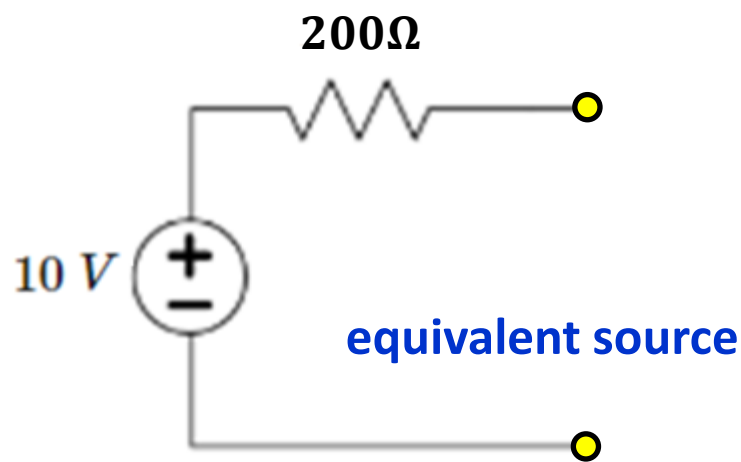

Example 4B: Solve for I

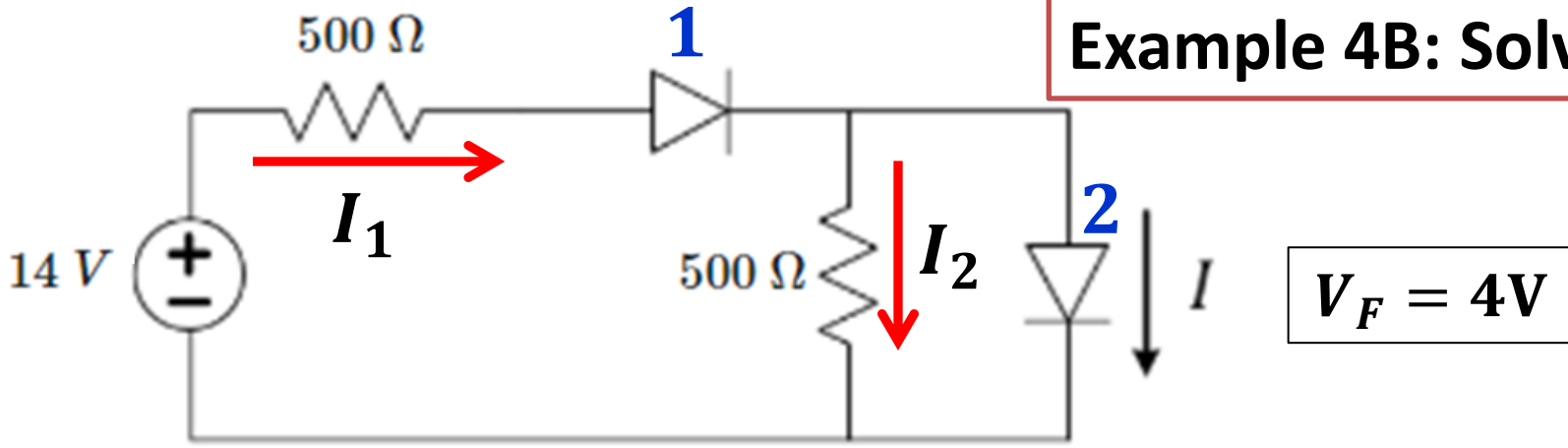

The source voltage has been increased

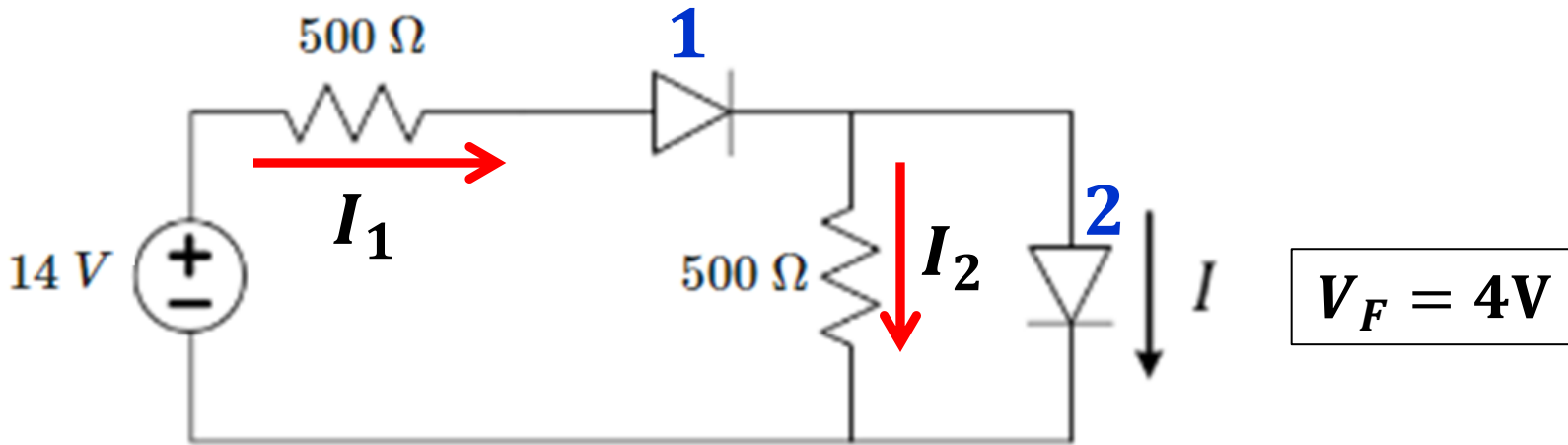

Assume both diodes conduct

$$I_1 = I_2 + I$$


KVL

$$-14 + 500I_1 + 4 + 4 = 0$$

$$I_1 = \frac{6}{500} = 12\text{mA}$$

$$I_2 = \frac{4}{500} = 8\text{mA} < I_1$$

$$I = I_1 - I_2 = 4\text{mA}$$

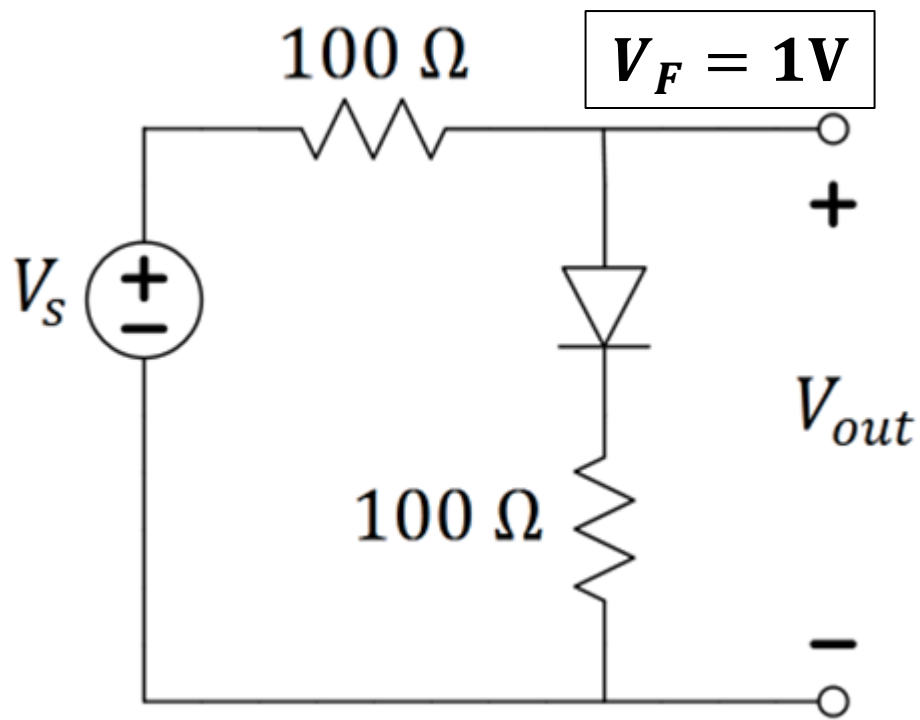


Example 5: Solve for V_{out}

Find V_{out} when

a) $V_S = 5V$

b) $V_S = -12V$

Example 5: Solve for V_{out}

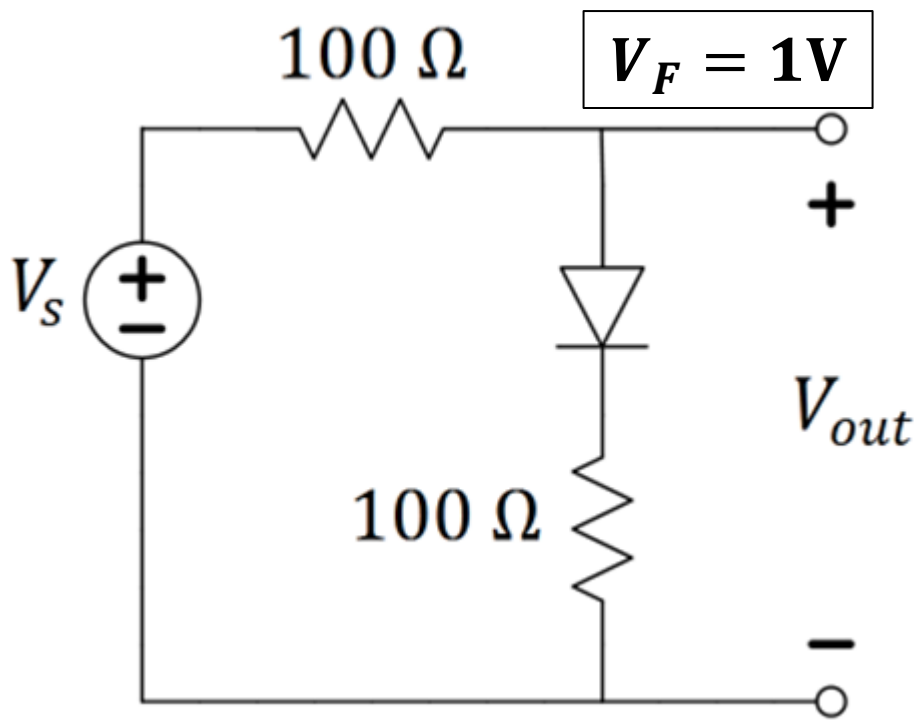

Find V_{out} when

a) $V_S = 5V$

b) $V_S = -12V$


a)

$$-5 + 100I_1 + 1 + 100I = 0$$

$$200I_1 = 4 \quad \rightarrow \quad I = 20\text{mA}$$

$$V_{out} = 100 \times 20\text{m} + 1 = 3V$$

Example 5: Solve for V_{out}

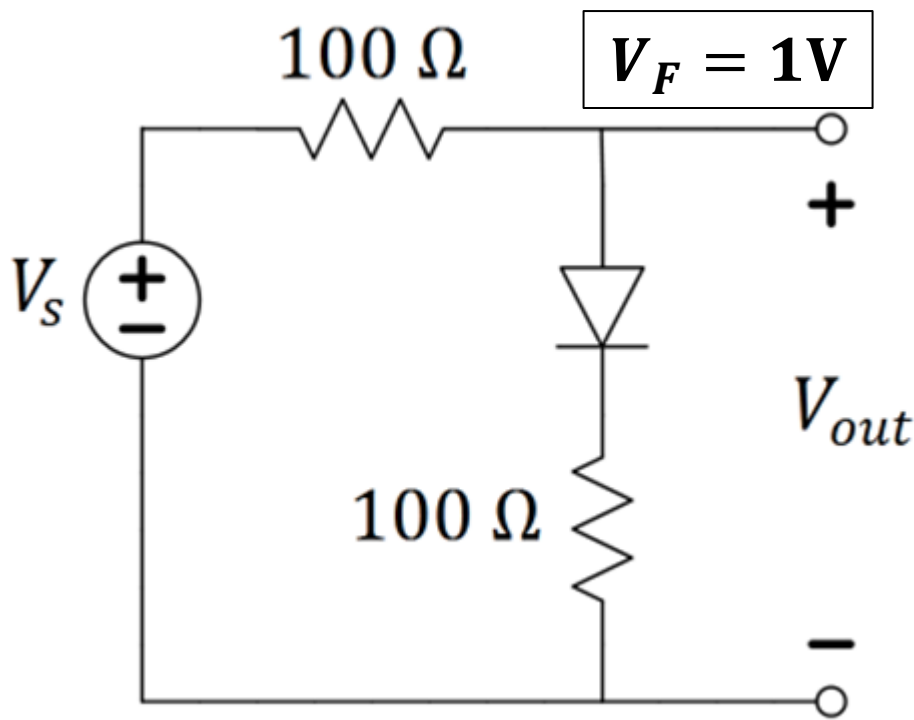

Find V_{out} when

a) $V_S = 5V$

b) $V_S = -12V$


a)
$$-5 + 100I_1 + 1 + 100I = 0$$
$$200I_1 = 4 \rightarrow I = 20\text{mA}$$
$$V_{out} = 100 \times 20\text{m} + 1 = 3V$$

b) $I = 0\ \text{A}$ **Diode does not conduct (reverse bias)**

$$V_{out} = -12V$$


Example 6: Solve for I_{D1} and I_{D2}

$V_{D1} = V_{D2} = 0.7V$

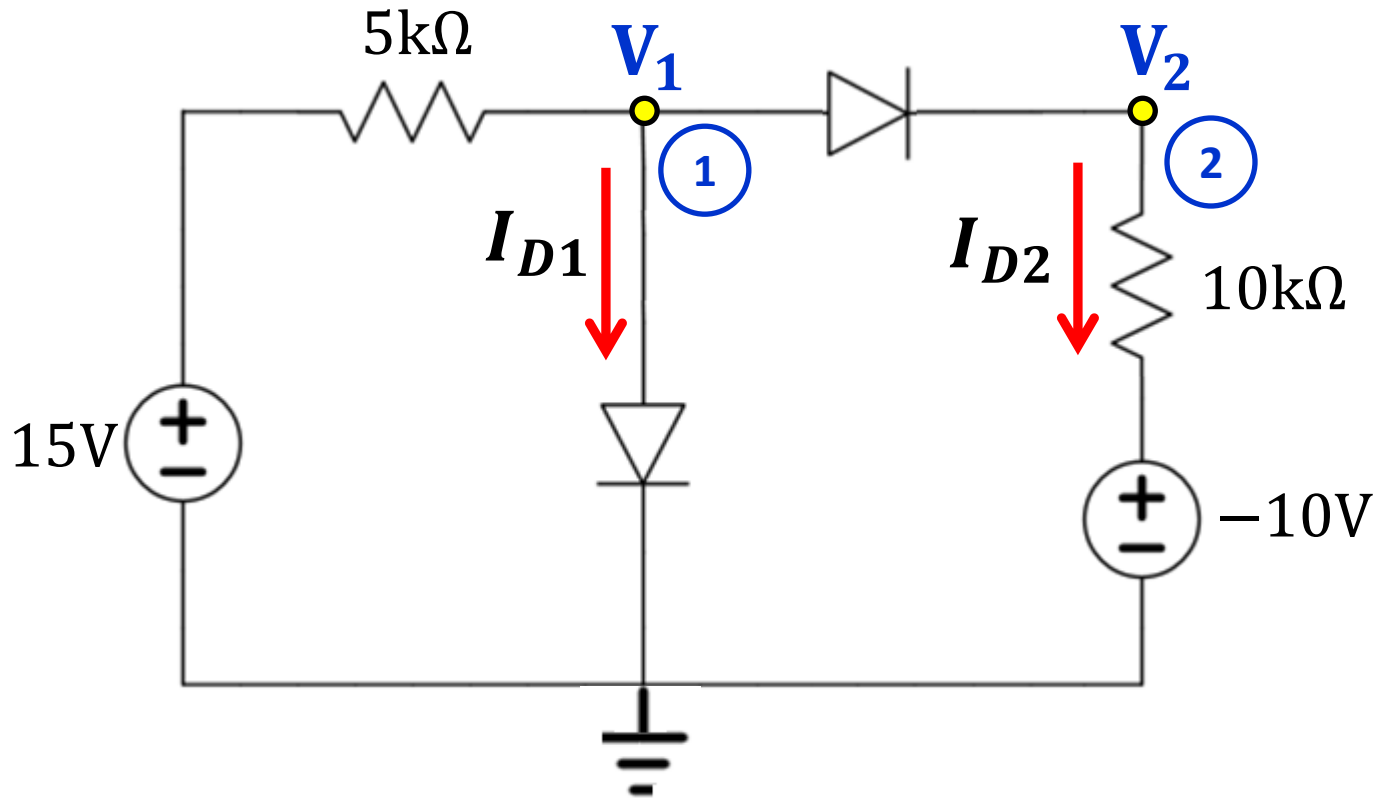

Example 6: Solve for I_{D1} and I_{D2}

$$V_{D1} = V_{D2} = 0.7V$$

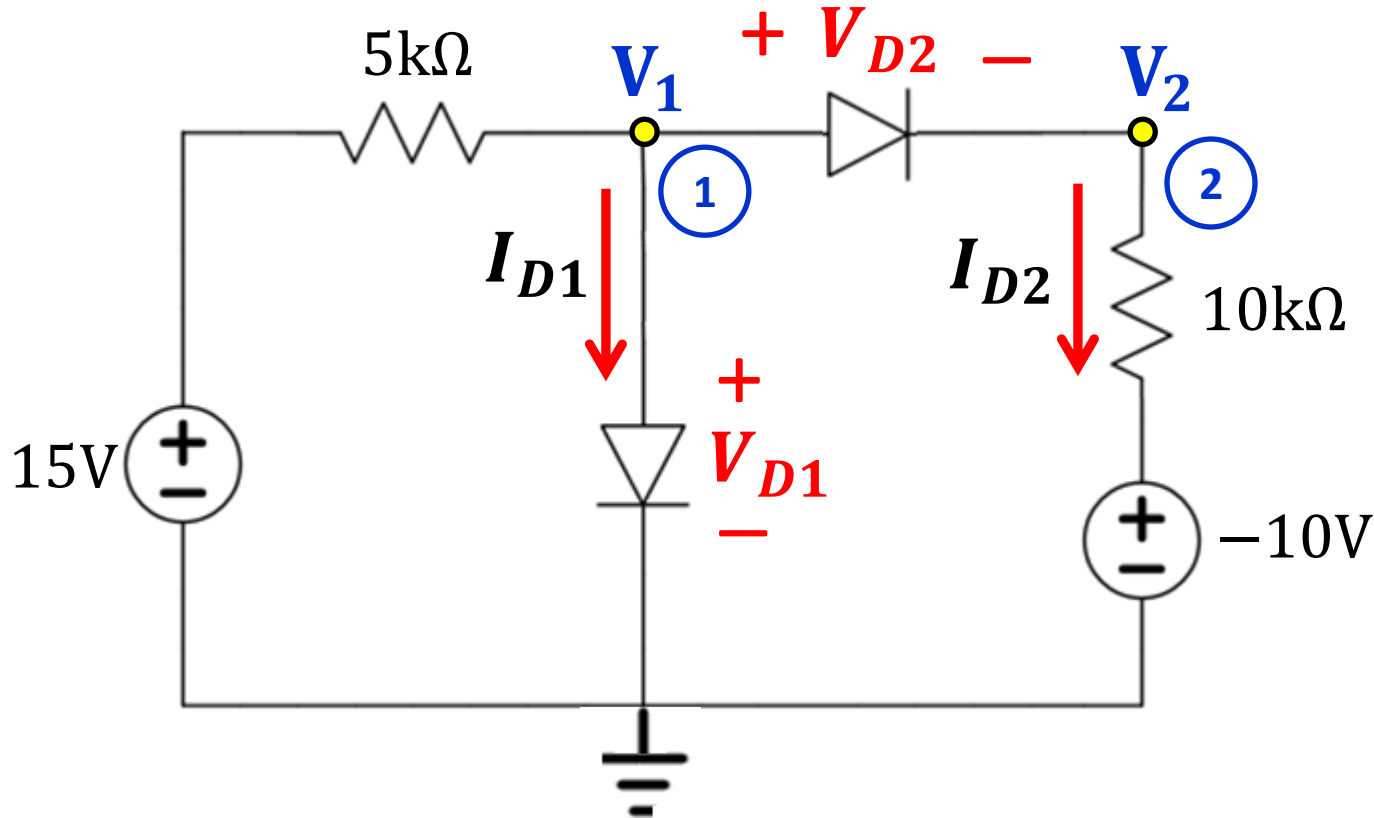


- Assume both diodes are ON

- By inspection:

$$V_1 = V_{D1} = 0.7V$$

$$V_1 - V_2 = 0.7V$$

$$V_2 = V_1 - V_{D2} = 0.7 - 0.7 = 0V$$

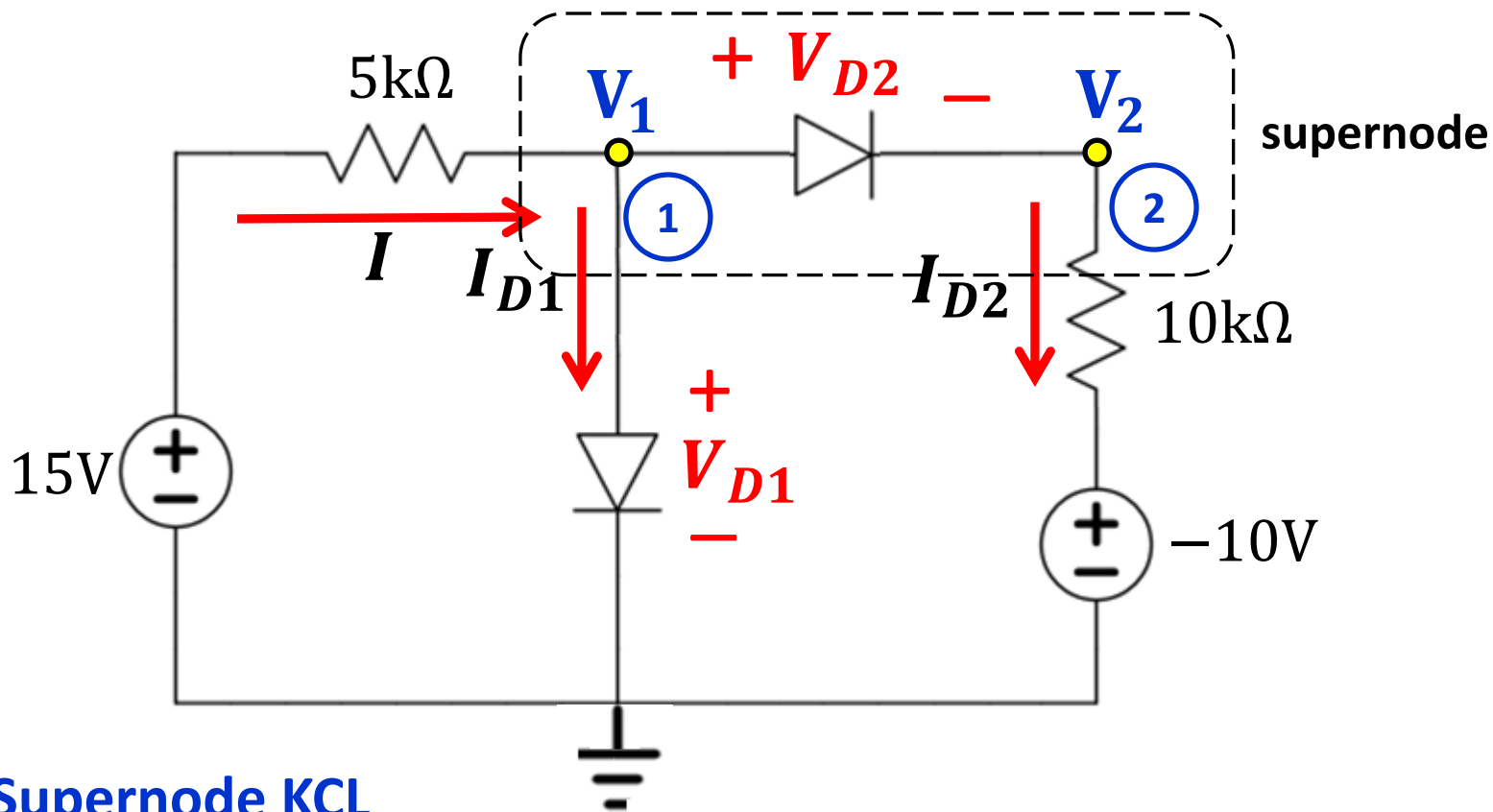


Supernode KCL

$$\frac{V_1 - 15}{5k} + I_{D1} + \frac{V_2 - (-10)}{10k} = 0$$

$$\frac{0.7 - 15}{5k} + I_{D1} + \frac{0 + 10}{10k} = 0$$
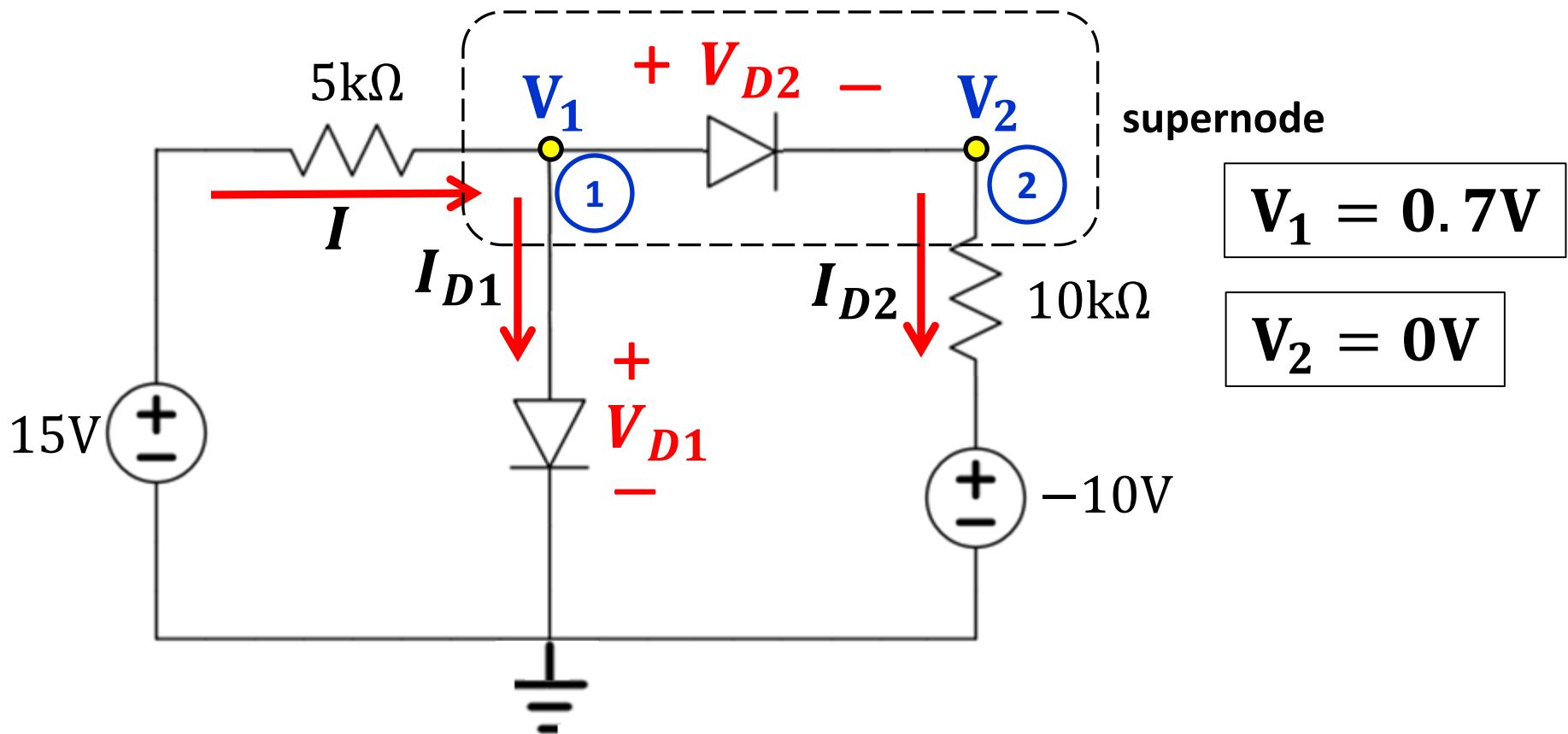
$$I_{D1} = \frac{9.3}{5k} = 1.86\text{mA}$$




$$I_{D1} = \frac{9.3}{5k} = 1.86\text{mA}$$

$$I_{D2} = \frac{V_2 + 10}{10k} = 1\text{mA}$$


$$I = \frac{15 - 0.7}{5k} = 2.86\text{mA} = I_{D1} + I_{D2}$$

Results present no contradiction, both diodes are ON

Right side of the circuit

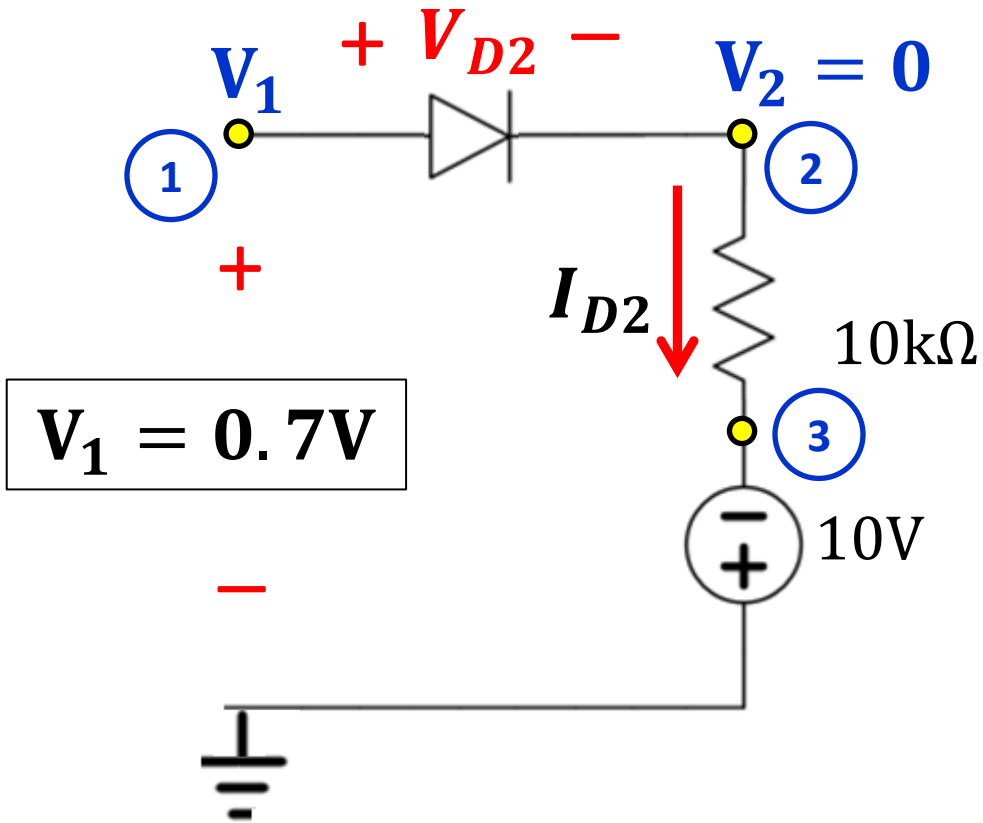


Right side of the circuit

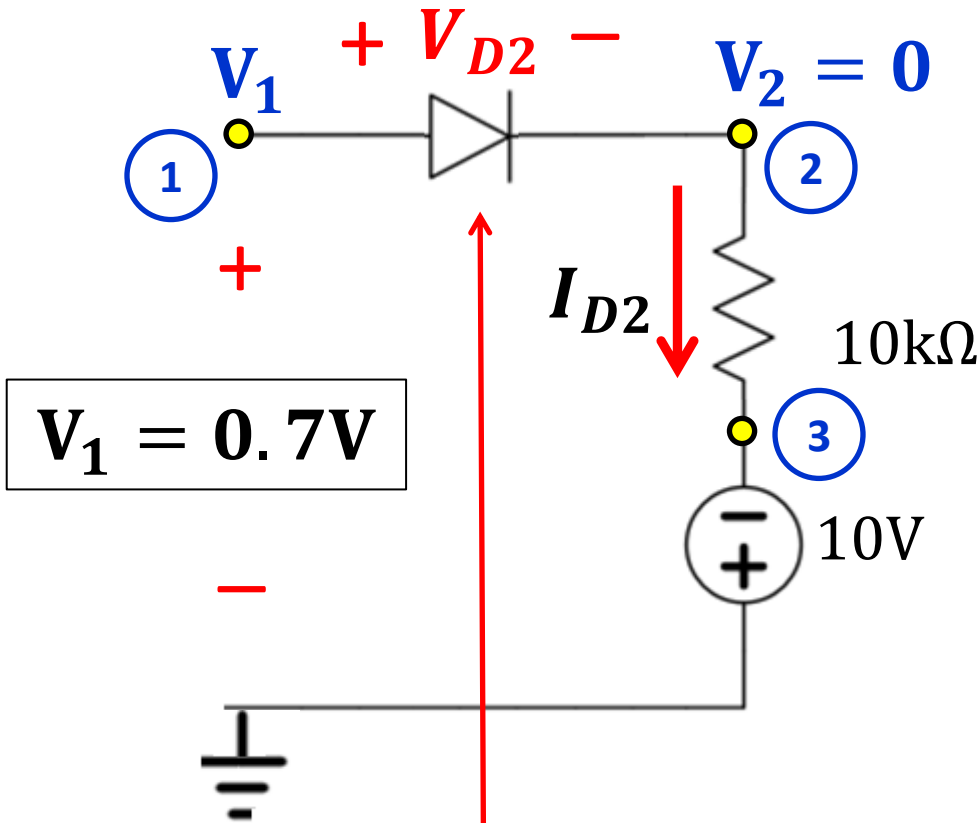

$$V_1 = 0.7V$$

$$V_{23} = 10k\Omega \times 1mA = 10V$$

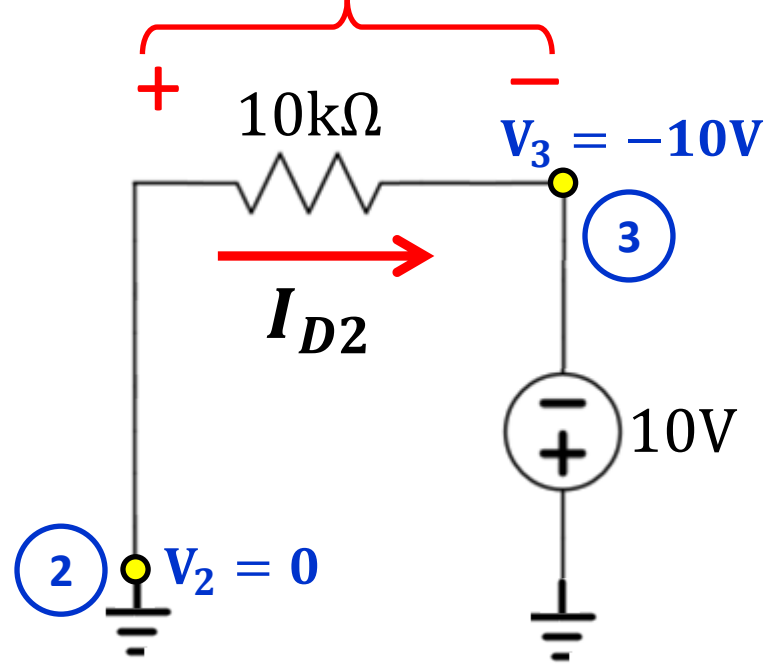

This is the effective circuit seen by the 10V source

$$-V_2 + 10k I_{D2} - 10 = 0$$

$$= 0$$

Because of continuity (KCL) at node 2, this is the current which flows also through the diode

$$I_{D2} = \frac{10}{10k} = 1mA$$