

# **ECE 205 “Electrical and Electronics Circuits”**

**Spring 2024 – LECTURE 24**

MWF – 12:00pm

**Prof. Umberto Ravaioli**

2062 ECE Building


# Lecture 24 – Summary

## Learning Objectives

1. More problems on diodes
2. Introduction to the bipolar junction transistor (BJT)
3. Modes of operations of a BJT
4. Amplification
5. Solution approaches for BJT circuits

We solved this problem last time

**Example 4A: Solve for  $I$**

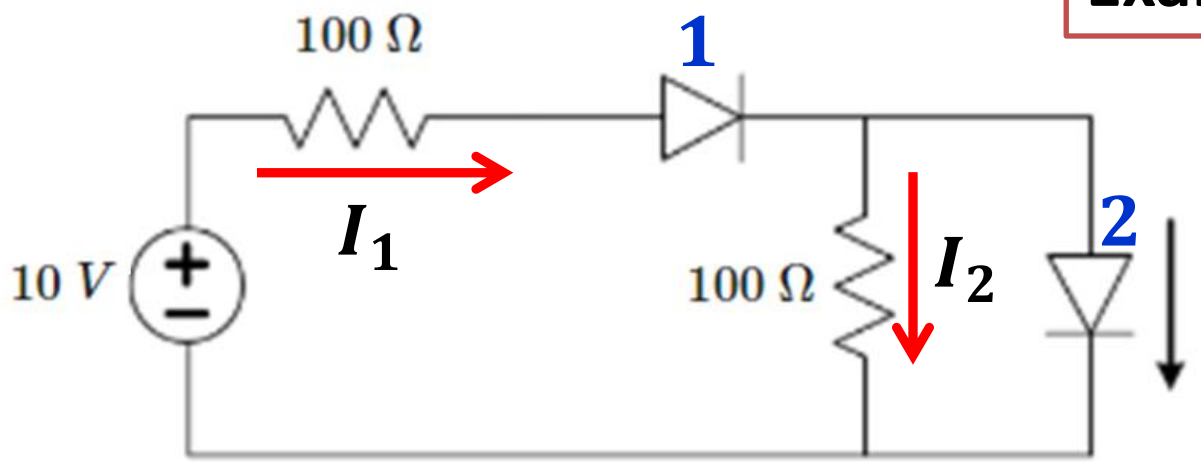

$V_F = 4V$

Assume both diodes conduct

$I_1 = I_2 + I$

**KVL**

$-10 + 100I_1 + 4 + 4 = 0$

$I_1 = \frac{2}{100} = 20mA$

$I_2 = \frac{4}{100} = 40mA$


But  $I_2 > I_1 \rightarrow$  diode **2** cannot conduct

$I = 0$

**new KVL with diode 2 open circuit**

$I_1 = \frac{6}{200} = 30mA$

$-10 + 100I_1 + 4 + 100I_1 = 0$


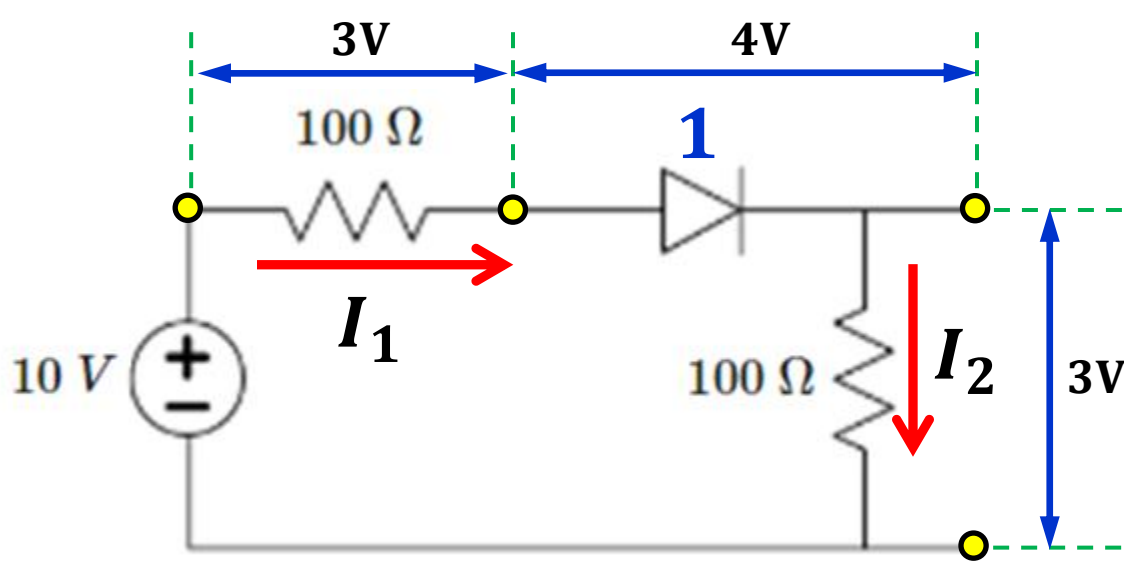


$$I = 0$$


$$V_F = 4\text{ V}$$

$$I_1 = I_2 = 30\text{ mA}$$

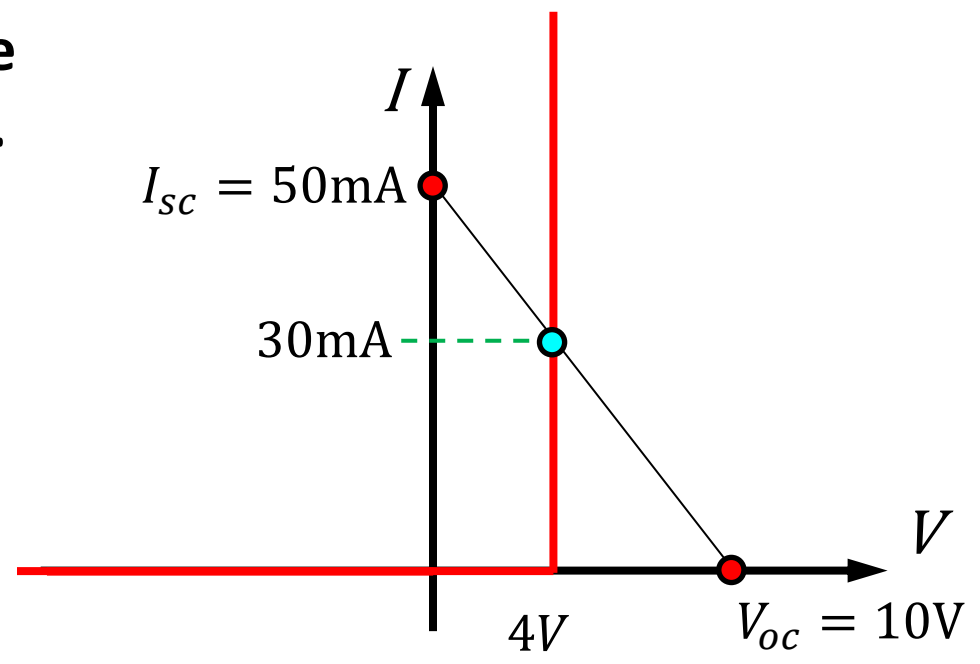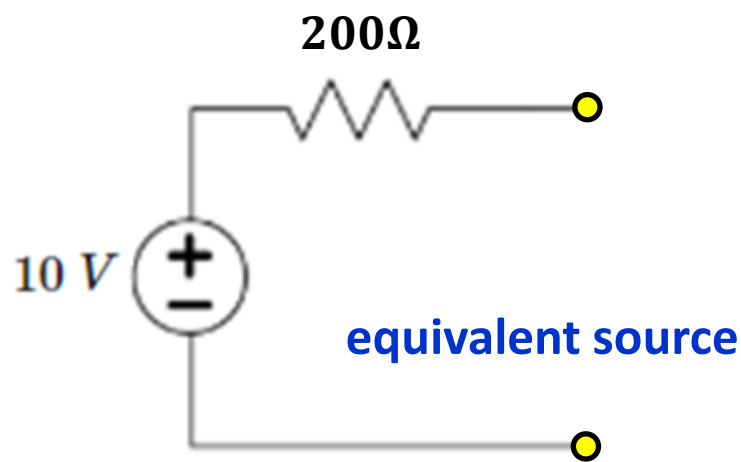Only diode 1 conducts. The two resistors drop 3V each.




## Example 4B: Solve for $I$

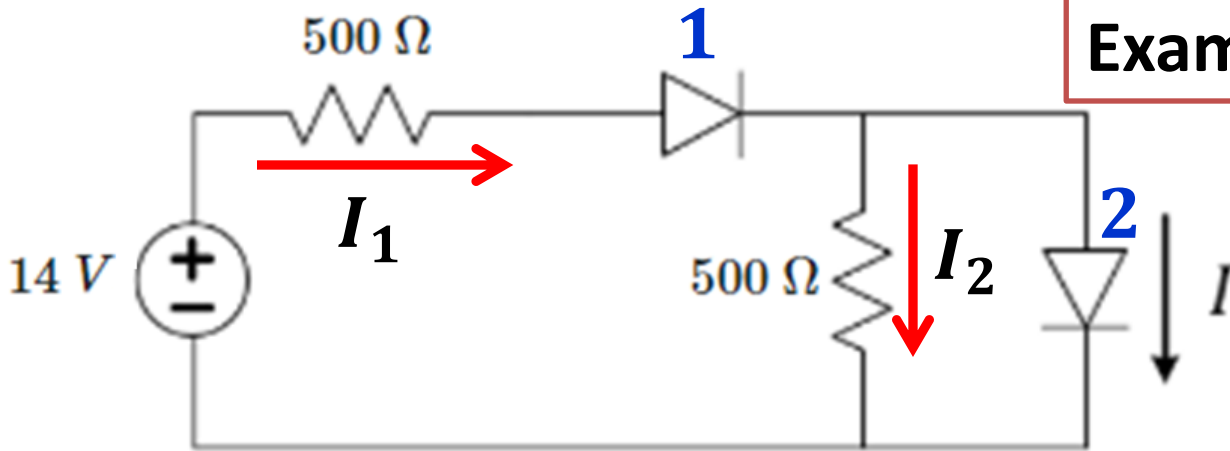

$$V_F = 4V$$

The source voltage has been increased

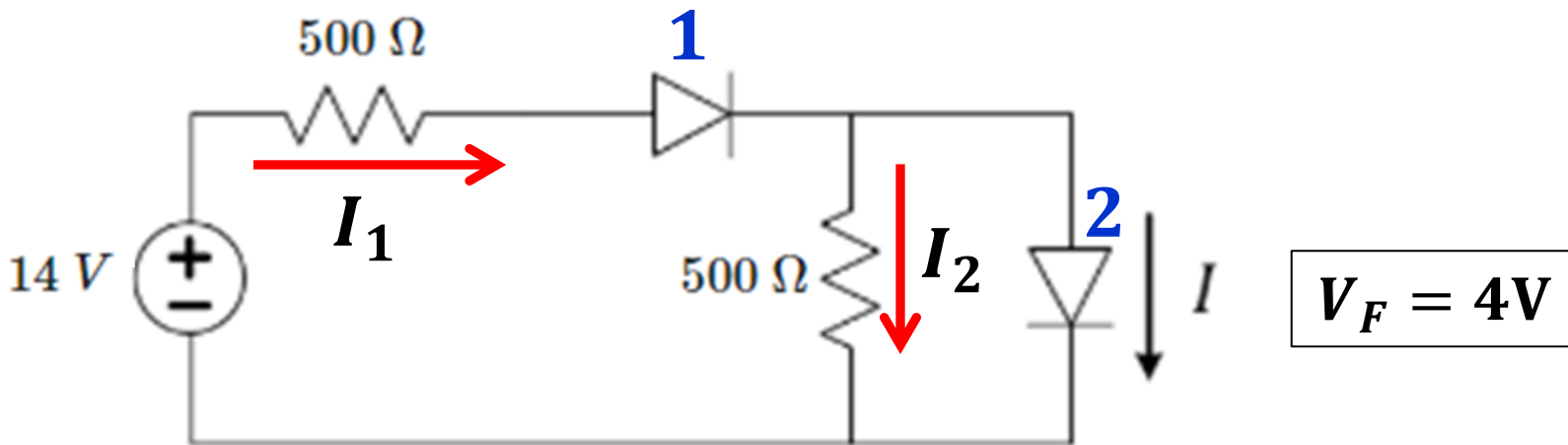

Assume both diodes conduct

$$I_1 = I_2 + I$$

KVL


$$-14 + 500I_1 + 4 + 4 = 0$$

$$I_1 = \frac{6}{500} = 12\text{mA}$$

$$I_2 = \frac{4}{500} = 8\text{mA} < I_1$$

$$I = I_1 - I_2 = 4\text{mA}$$

Assumption is valid – No contradiction

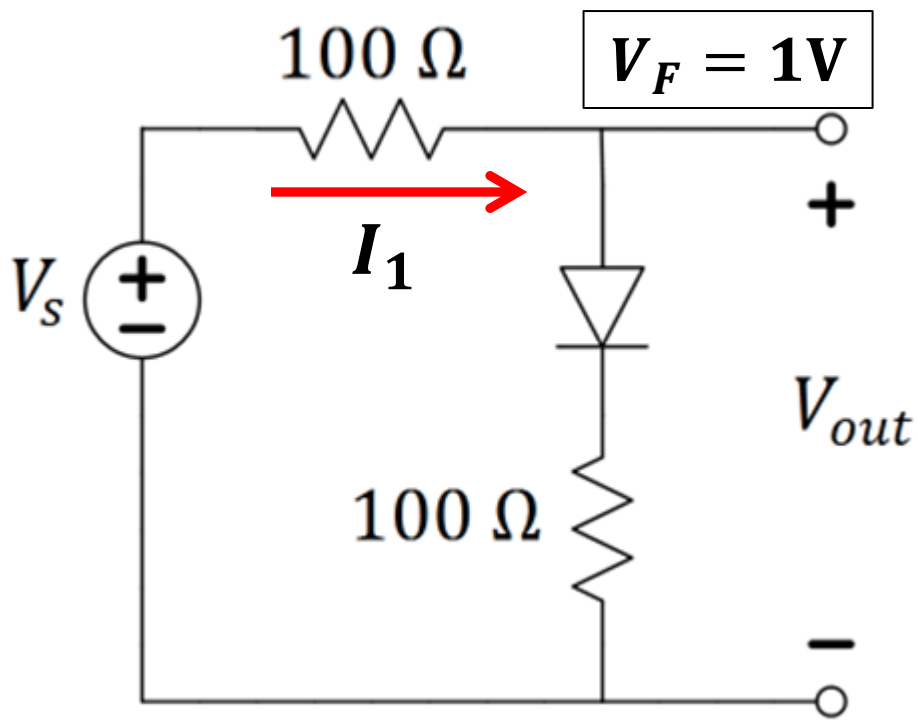


## Example 5: Solve for $V_{out}$

Find  $V_{out}$  when

a)  $V_S = 5\text{V}$

b)  $V_S = -12\text{V}$

## Example 5: Solve for $V_{out}$

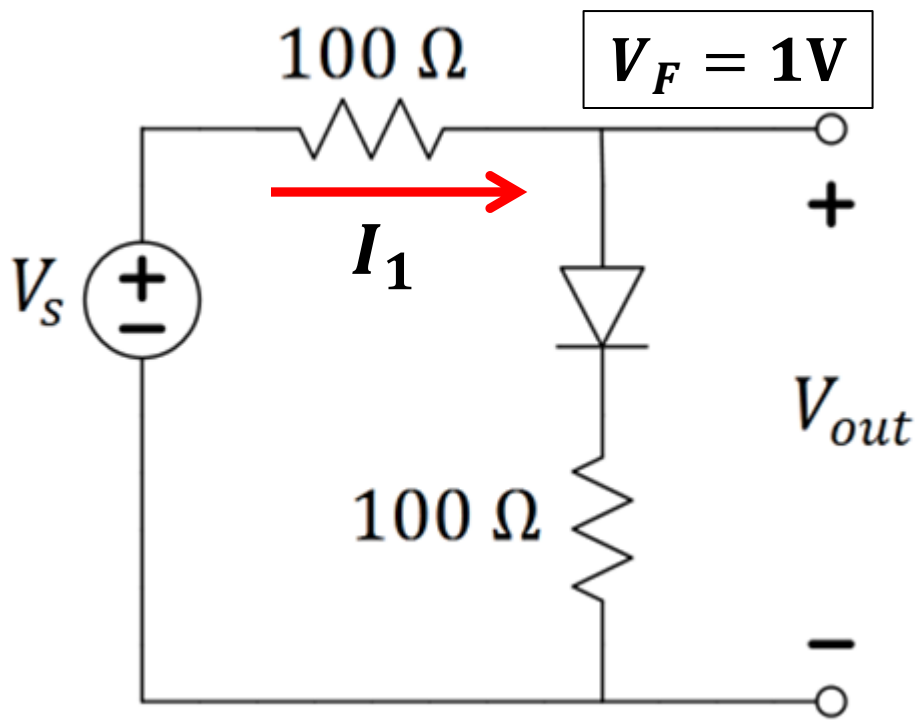

Find  $V_{out}$  when

a)  $V_S = 5\text{V}$

b)  $V_S = -12\text{V}$


a)  $-5 + 100I_1 + 1 + 100I_1 = 0$

$$200I_1 = 4 \quad \rightarrow \quad I_1 = 20\text{mA}$$

$$V_{out} = 100 \times 20\text{m} + 1 = 3\text{V}$$



## Example 5: Solve for $V_{out}$

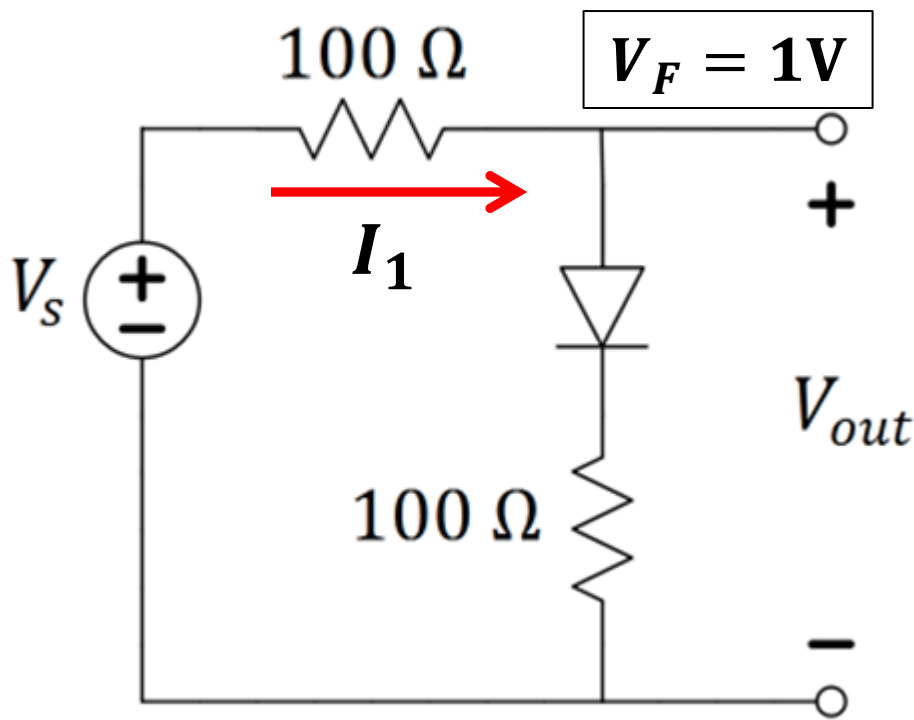

Find  $V_{out}$  when

a)  $V_S = 5\text{V}$

b)  $V_S = -12\text{V}$

a)  $-5 + 100I_1 + 1 + 100I_1 = 0$

$$200I_1 = 4 \rightarrow I_1 = 20\text{mA}$$


$$V_{out} = 100 \times 20\text{m} + 1 = 3\text{V}$$

b)  $I_1 = 0\text{A}$  **Diode does not conduct (reverse bias)**

$$V_{out} = -12\text{V}$$


**Example 6: Solve for  $I_{D1}$  and  $I_{D2}$**

$V_{D1} = V_{D2} = 0.7V$

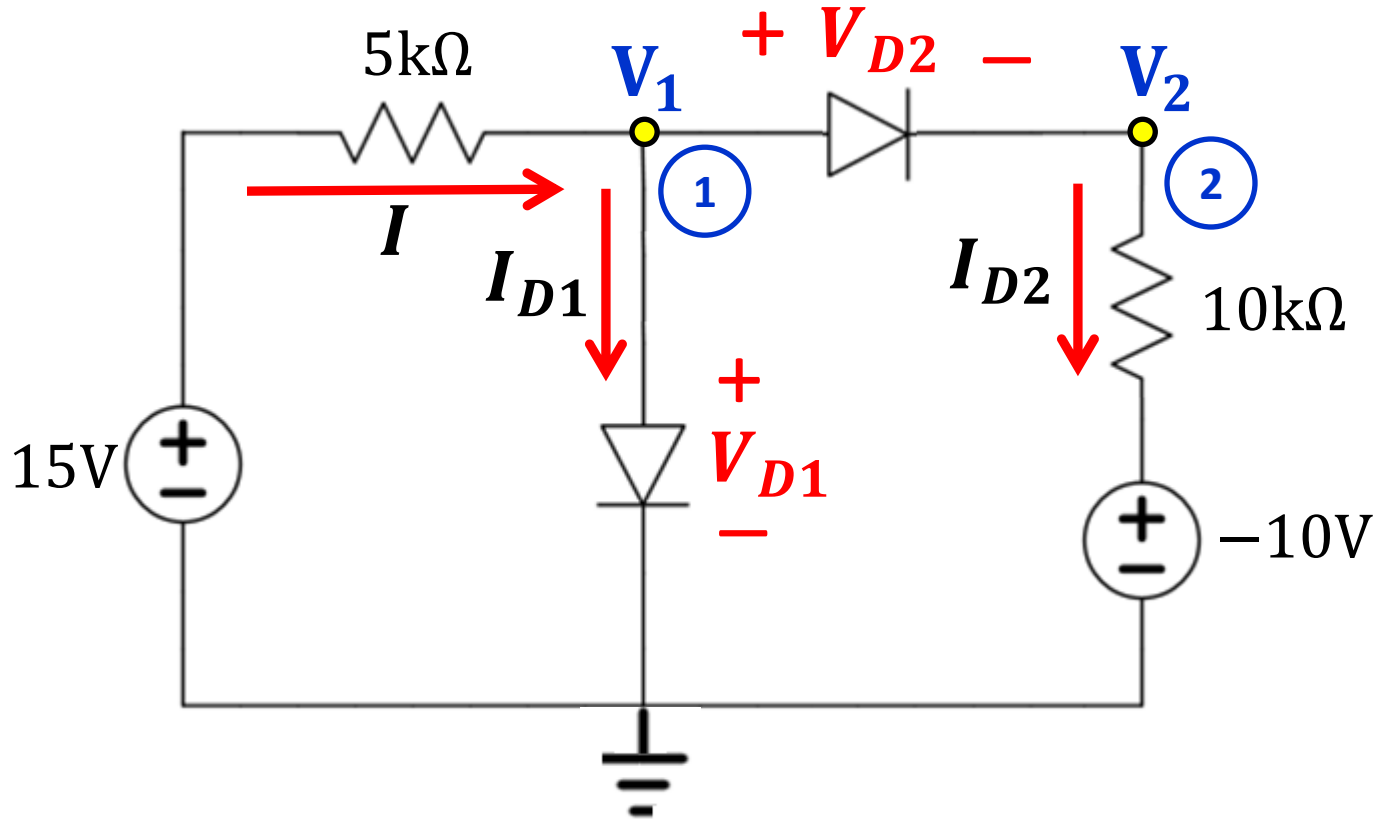

## Example 6: Solve for $I_{D1}$ and $I_{D2}$


$$V_{D1} = V_{D2} = 0.7V$$

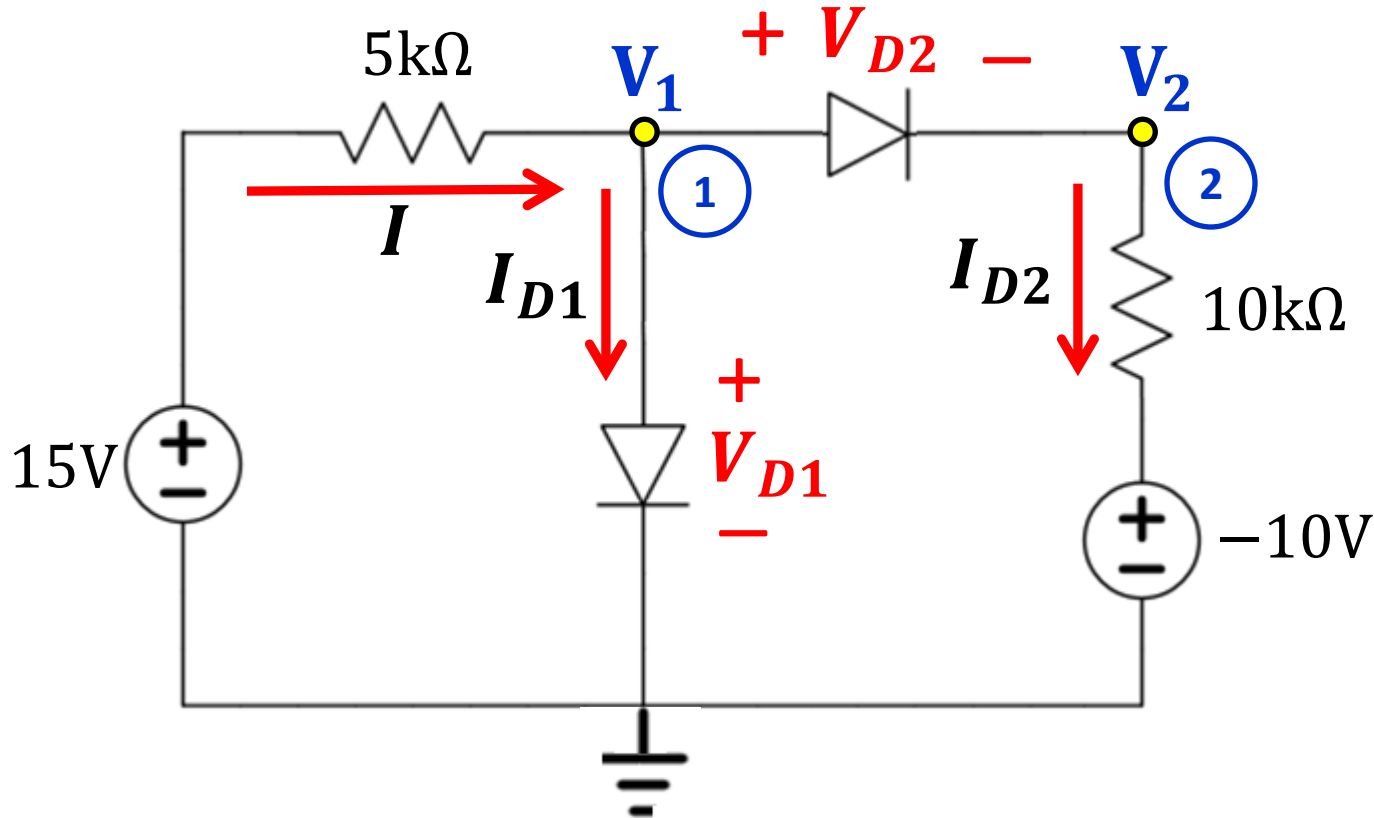

- Assume both diodes are ON

• By inspection:  $V_1 = V_{D1} = 0.7V$        $V_1 - V_2 = 0.7V$

$$V_2 = V_1 - V_{D2} = 0.7 - 0.7 = 0V$$

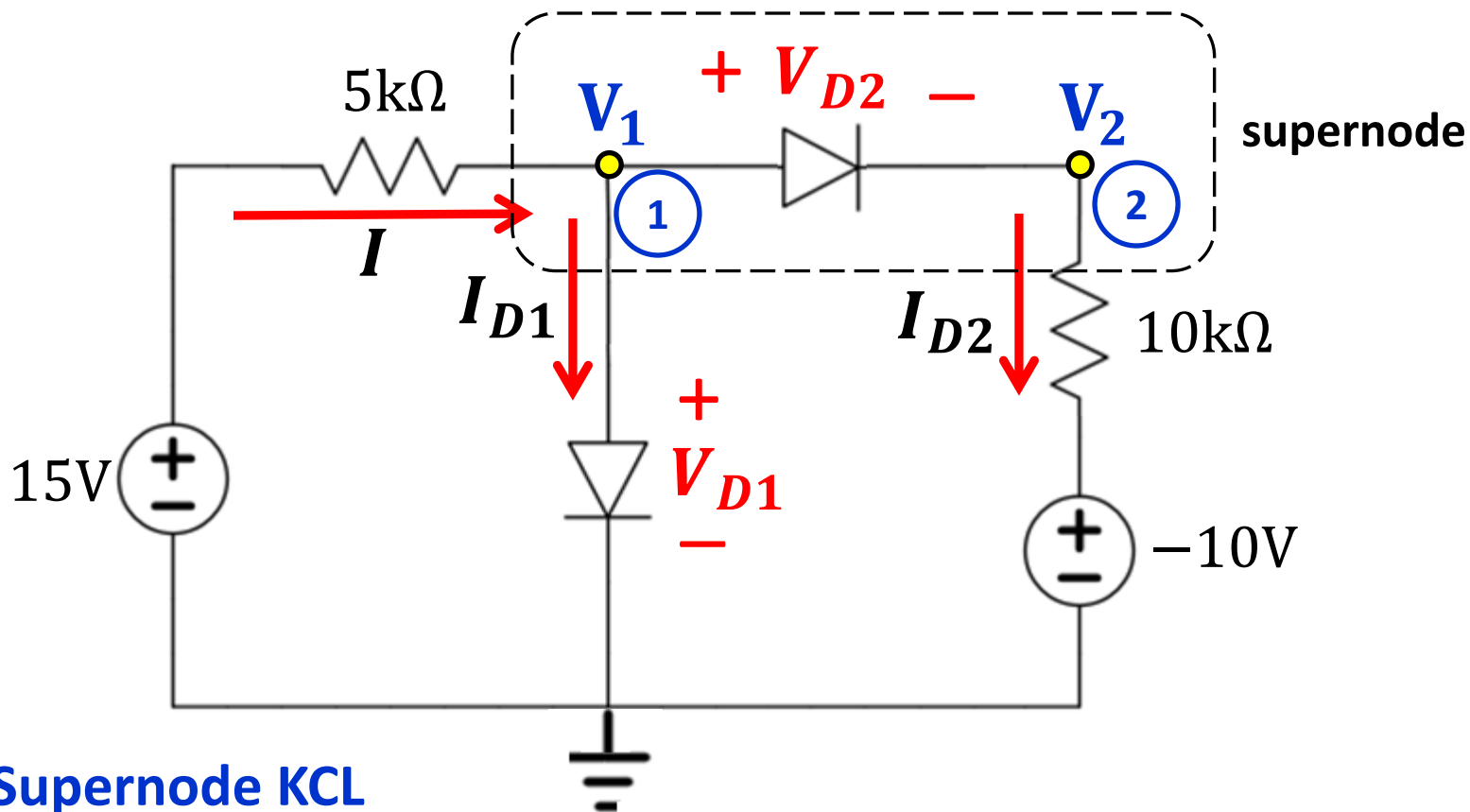


**Supernode KCL**

$$\frac{V_1 - 15}{5k} + I_{D1} + \frac{V_2 - (-10)}{10k} = 0$$

$$\frac{0.7 - 15}{5k} + I_{D1} + \frac{0 + 10}{10k} = 0$$
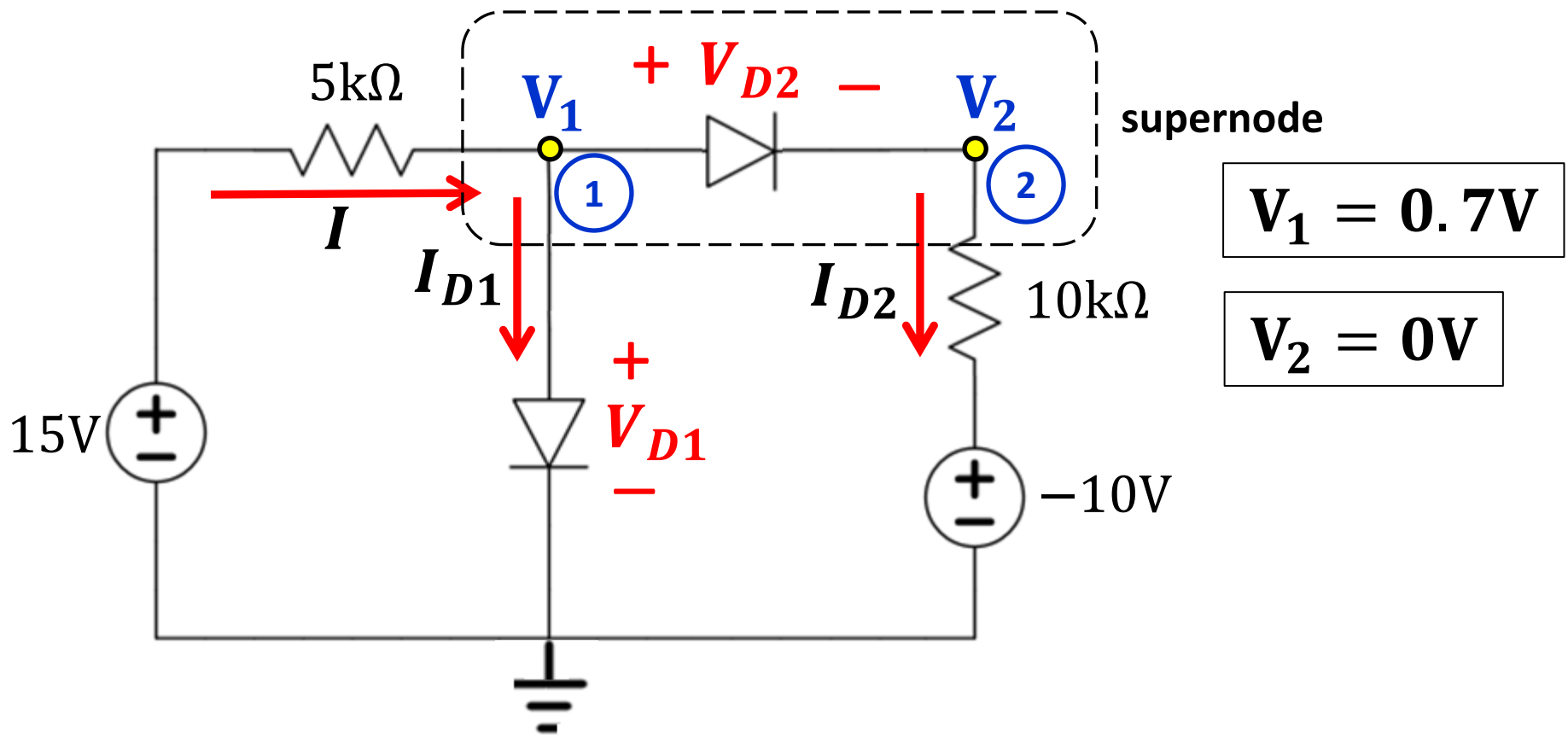
$$I_{D1} = \frac{9.3}{5k} = 1.86\text{mA}$$




$$I_{D1} = \frac{9.3}{5k} = 1.86mA$$

$$I_{D2} = \frac{V_2 + 10}{10k} = 1mA$$


$$I = \frac{15 - 0.7}{5k} = 2.86mA = I_{D1} + I_{D2}$$

**Results present no contradiction, both diodes are ON**


# Right side of the circuit

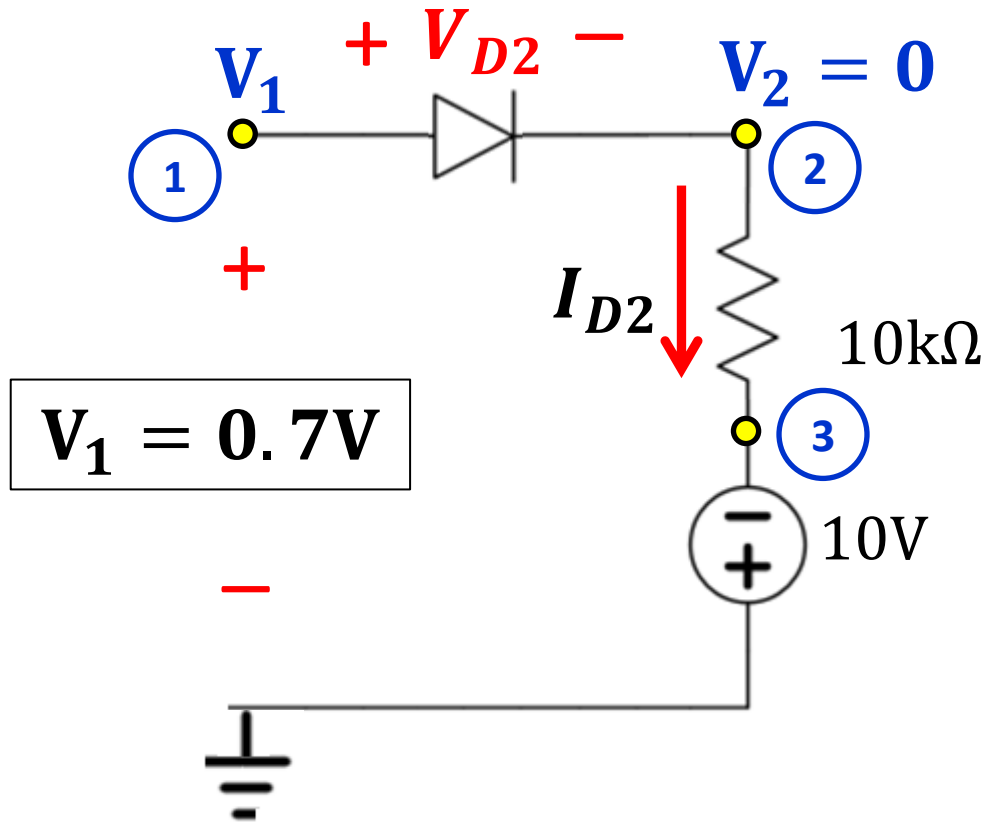

Right side of the circuit

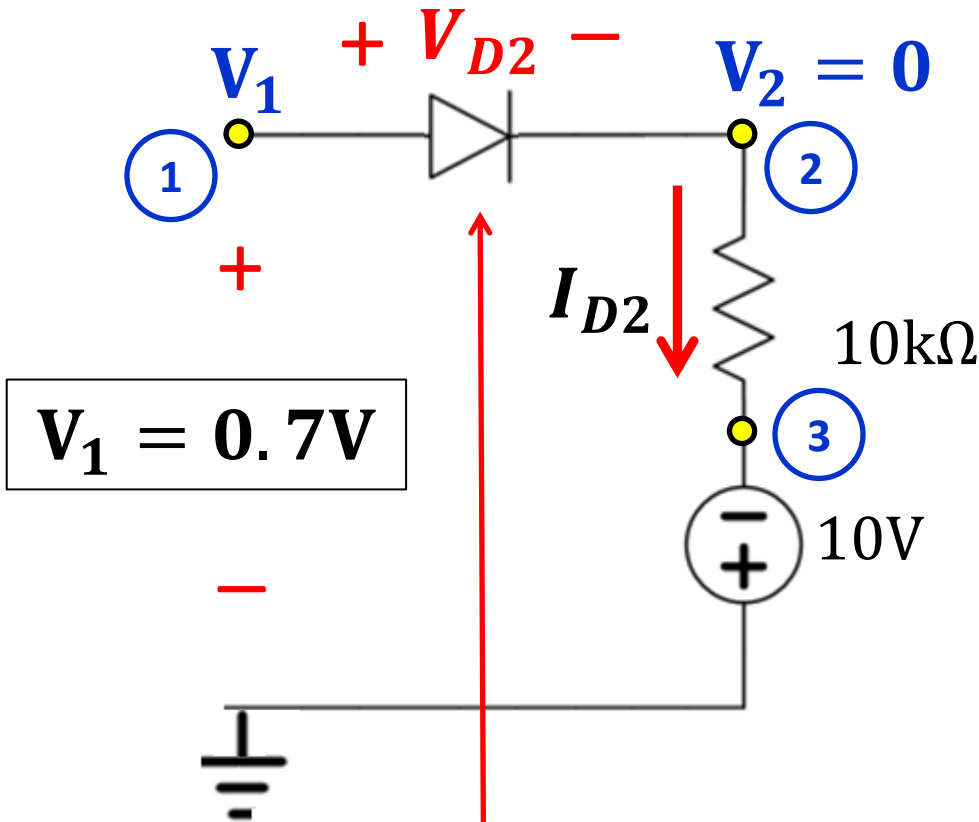

$$V_{23} = 10k\Omega \times 1mA = 10V$$

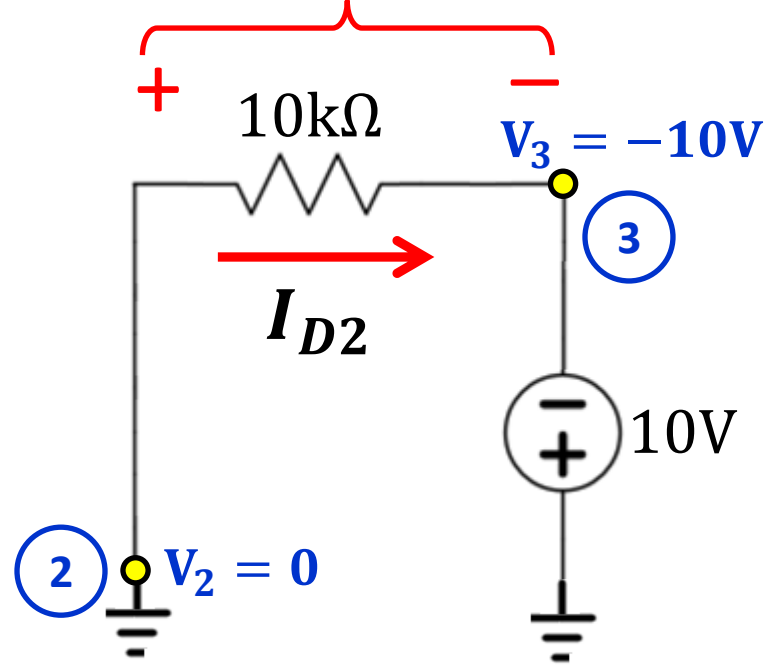

This is the effective circuit seen by the 10V source

$$-V_2 + 10k I_{D2} - 10 = 0$$

$$= 0$$

Because of continuity (KCL) at node 2, this is the current which flows also through the diode

$$I_{D2} = \frac{10}{10k} = 1mA$$

# More diode problems

in the extra video posted on Canvas at

Module Week 10

Mon 3/25

(it includes solution of Worksheet 8)



# Bipolar Junction Transistor

- We start from the  $p-n$  junction
- What happens if we create a structure with two  $p-n$  junctions?


### Equilibrium

$\approx$  Charge-neutral


Space-charge depletion layer

$\approx$  Charge-neutral


No potential applied

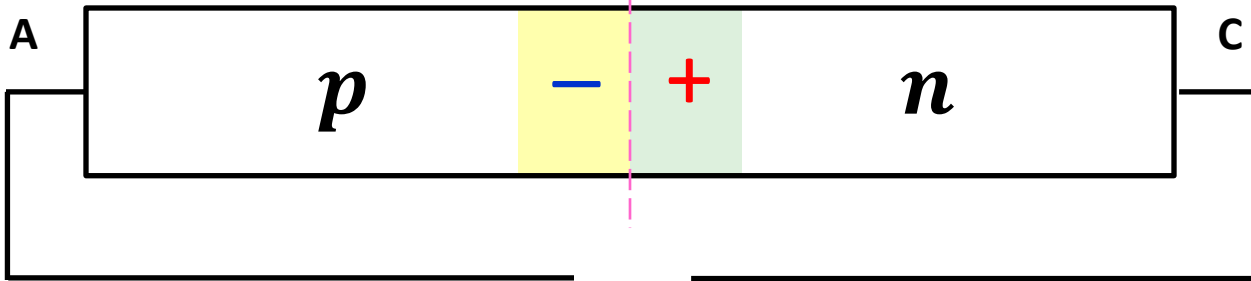


### Forward bias

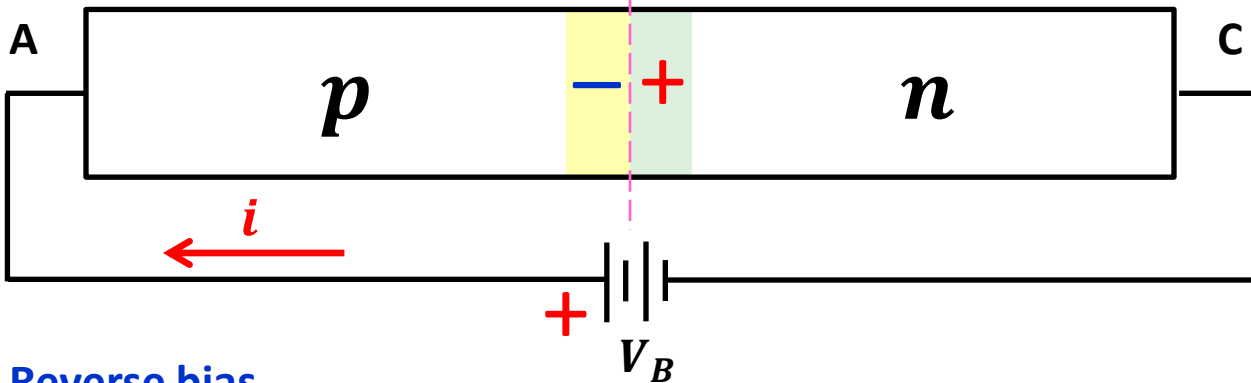


### Reverse bias

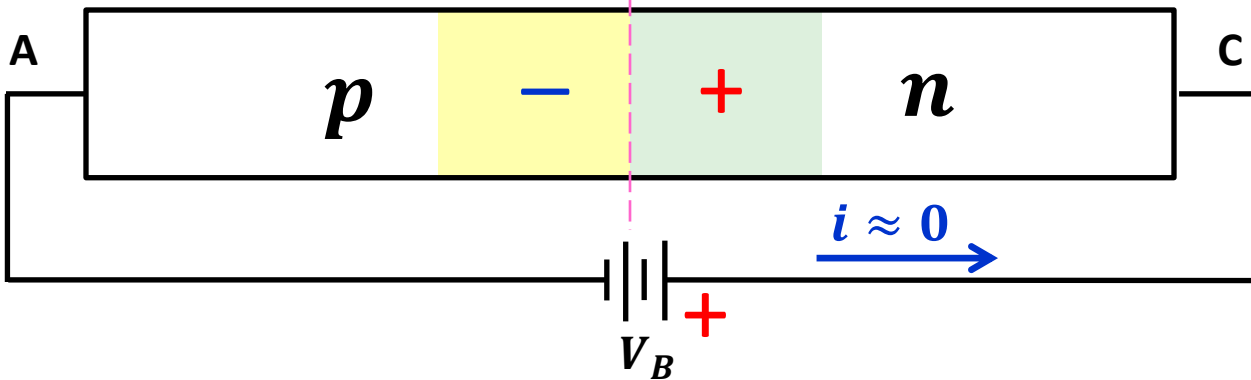

$$V_A > V_C$$


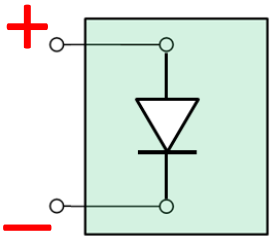


$$V_A < V_C$$

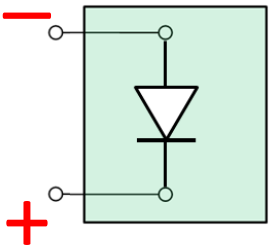

# Bipolar Junction Transistor (BJT)

*n-p-n*

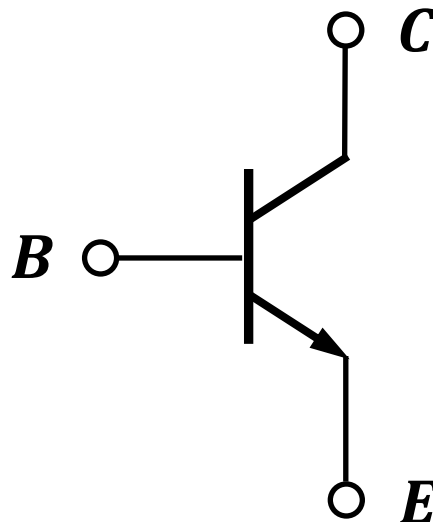
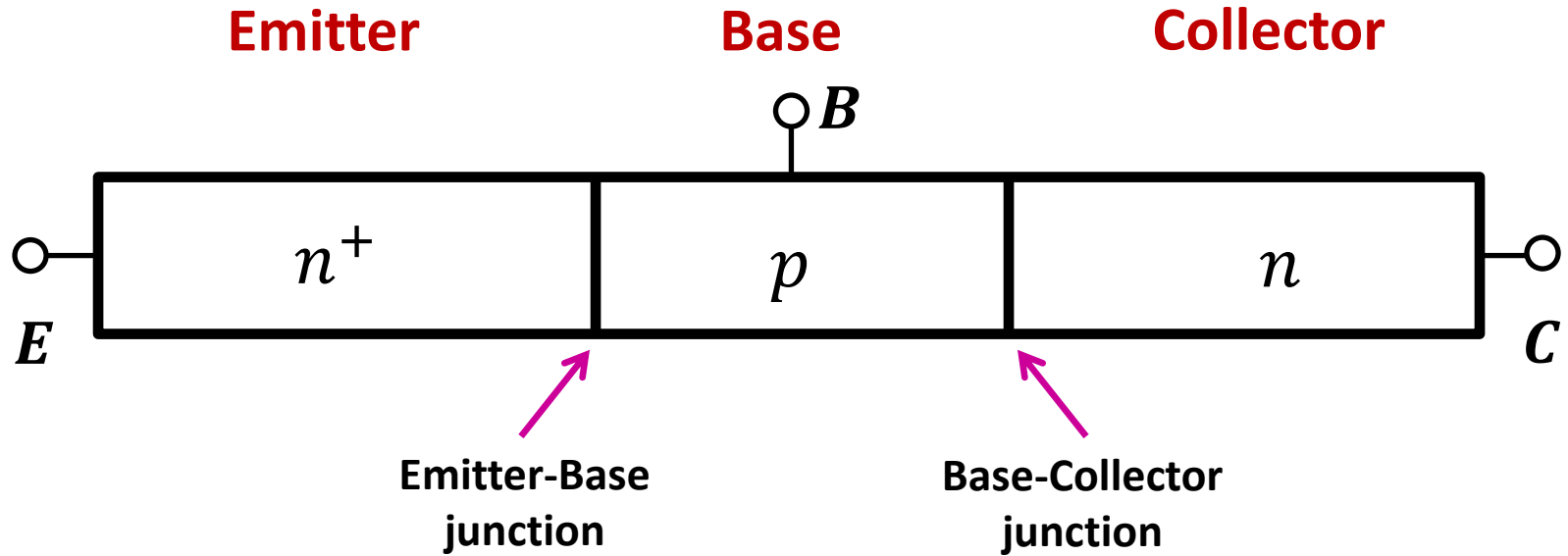


Circuit Symbol

*n-p-n* BJT

# Bipolar Junction Transistor (BJT)

*p-n-p*

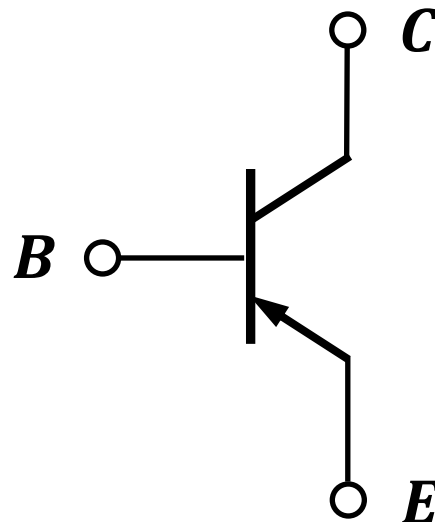
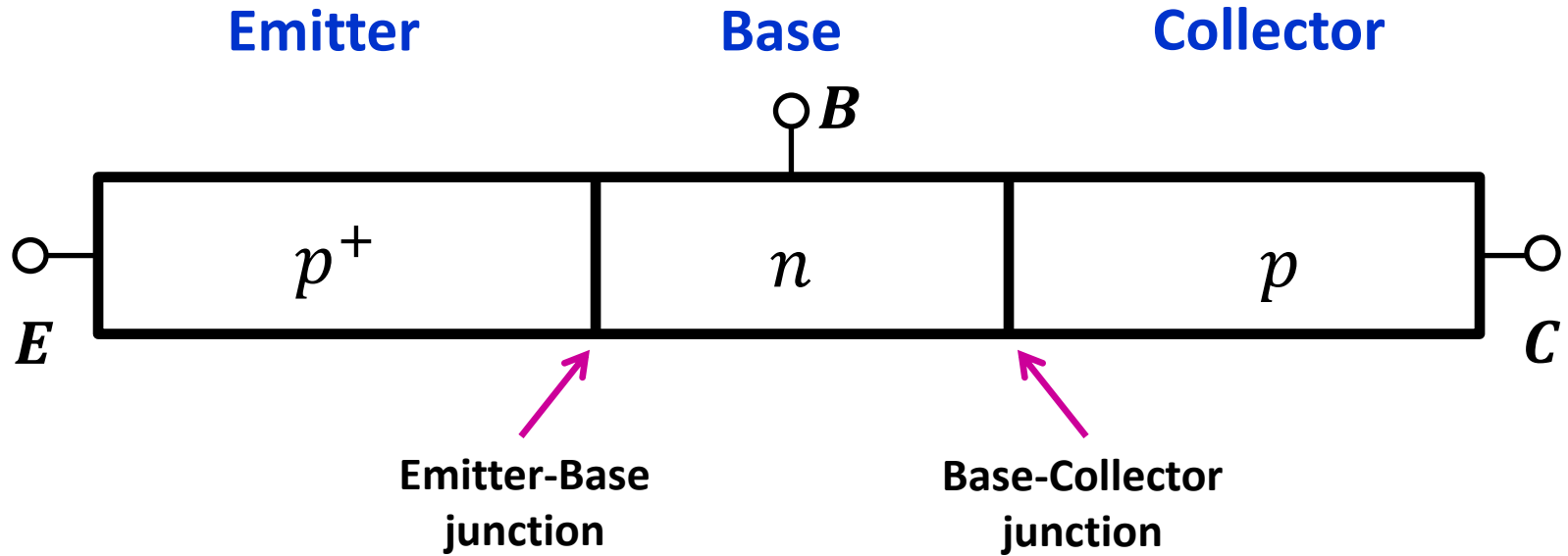


Circuit Symbol

*p-n-p* BJT


# Bipolar Junction Transistor (BJT)

*n-p-n*

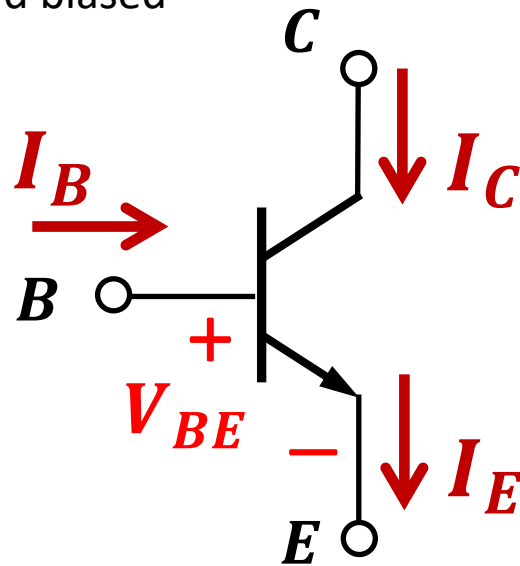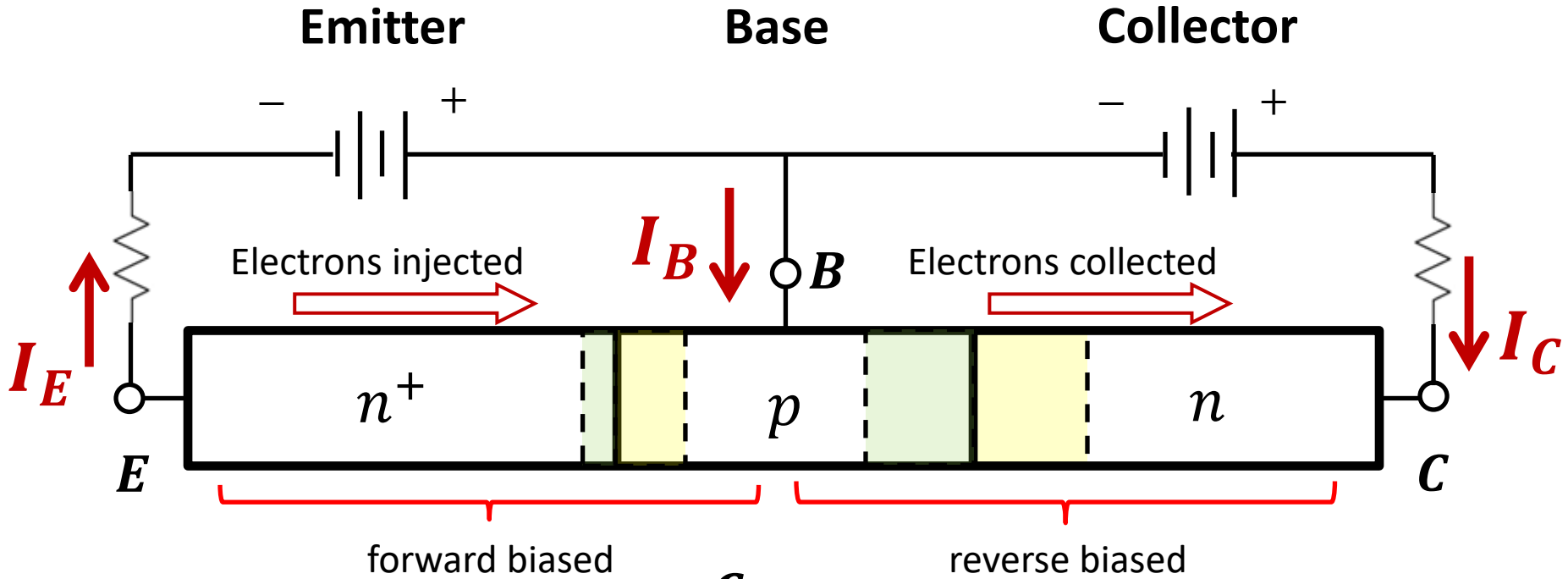


# Bipolar Junction Transistor (BJT)

*p-n-p*

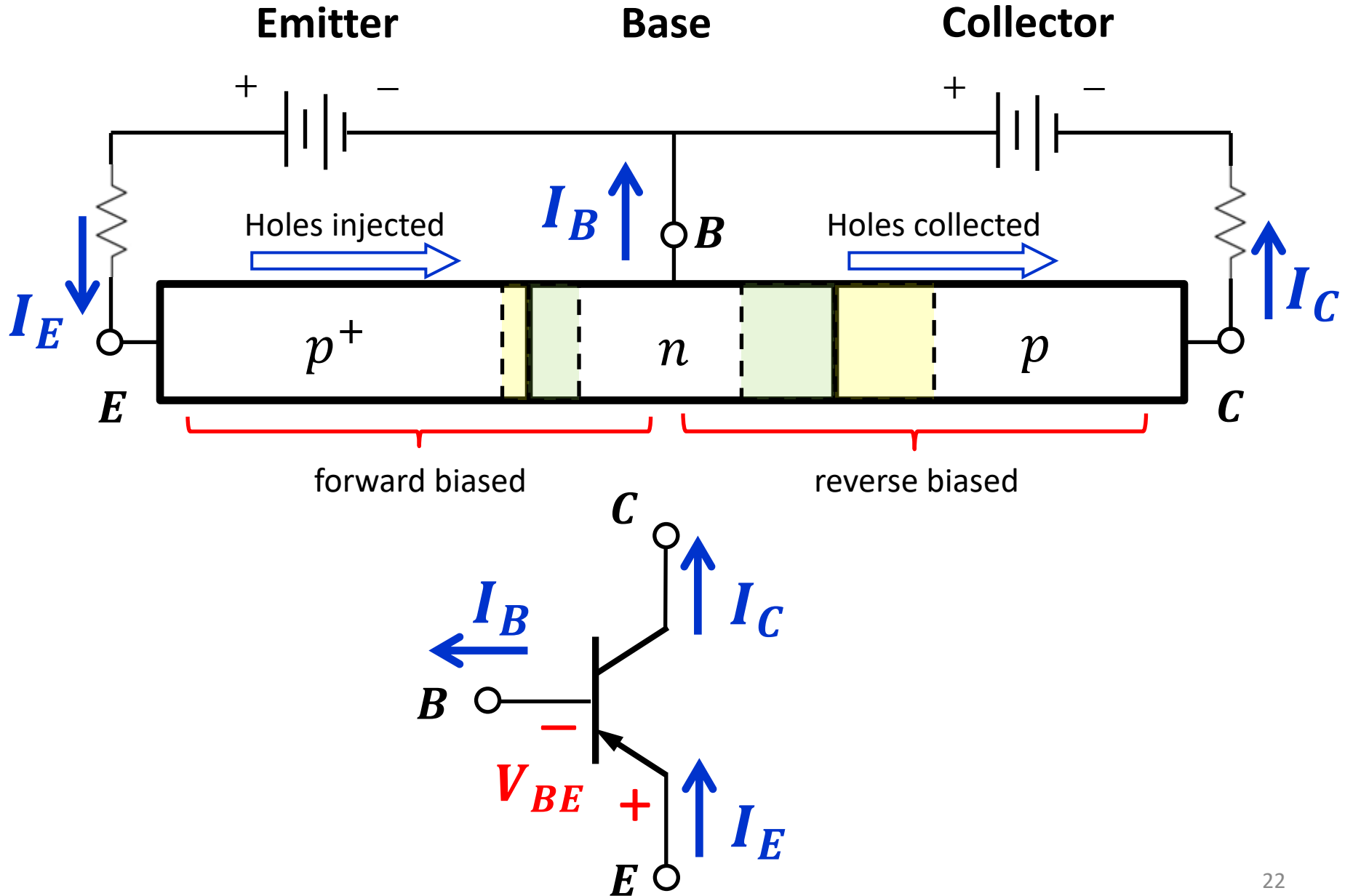
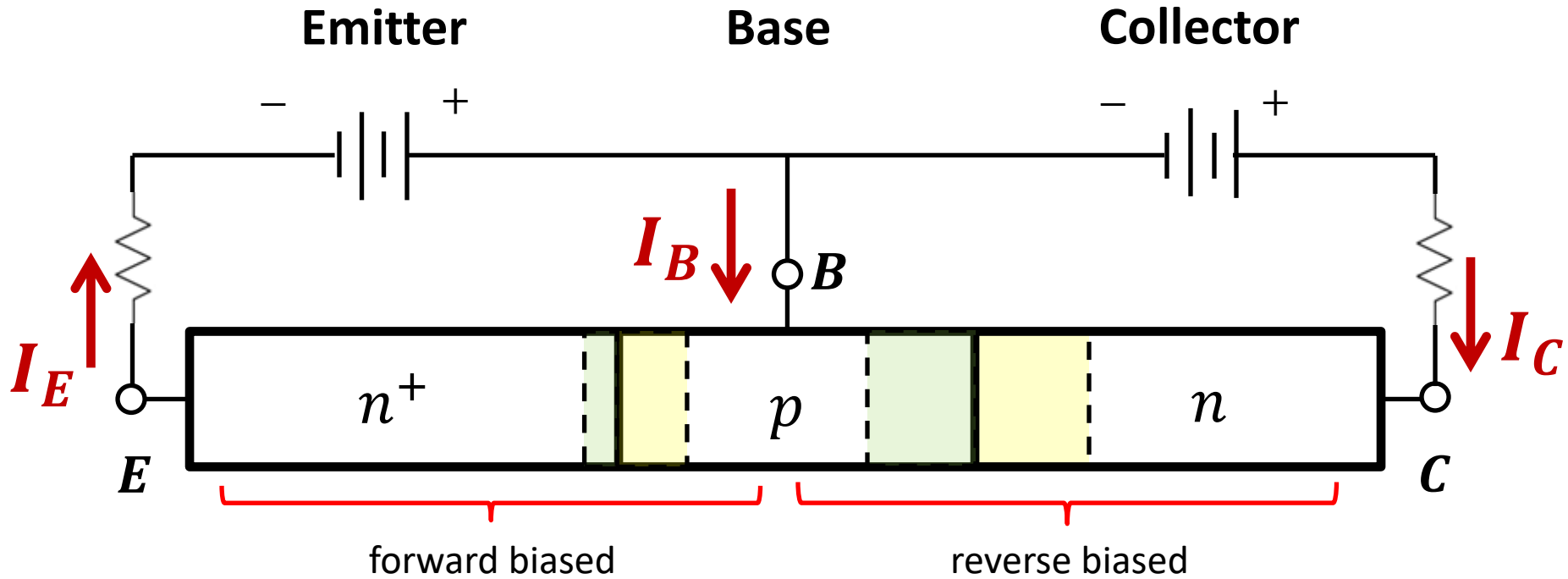
# Simple physics explanation – Forward active mode



Electrons are injected from the emitter into the base through a forward biased emitter-base diode




Most electrons traverse the base. The base current injects holes which recombine with some electrons, controlling the current flow from emitter to collector.




Electrons reaching the reverse biased junction are swept into the collector by high electron field in the depletion region.

# Transistor circuit configurations

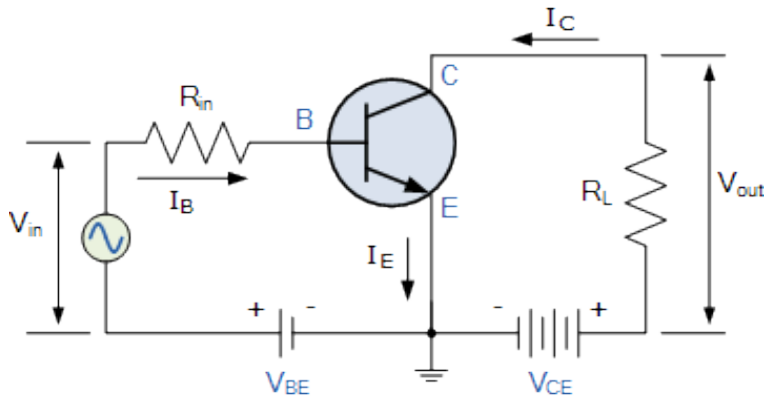


## Common Emitter

- Current gain
- Voltage gain

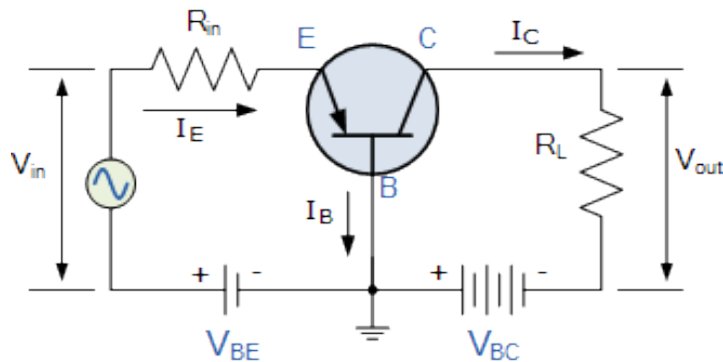

## Common Base

- Voltage gain

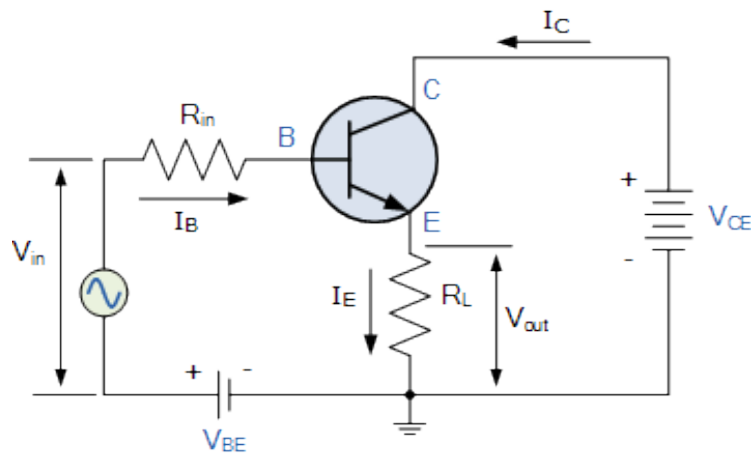


## Common Collector


- Current gain



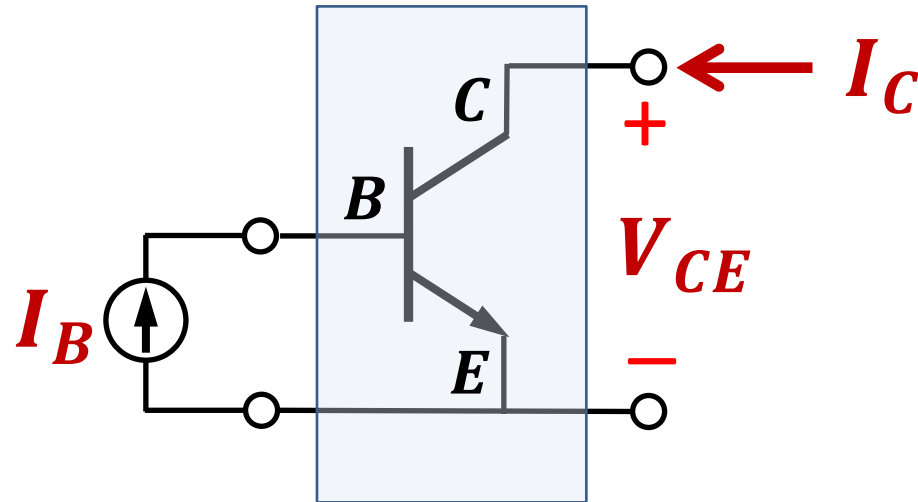
# Common Emitter is the most important configuration




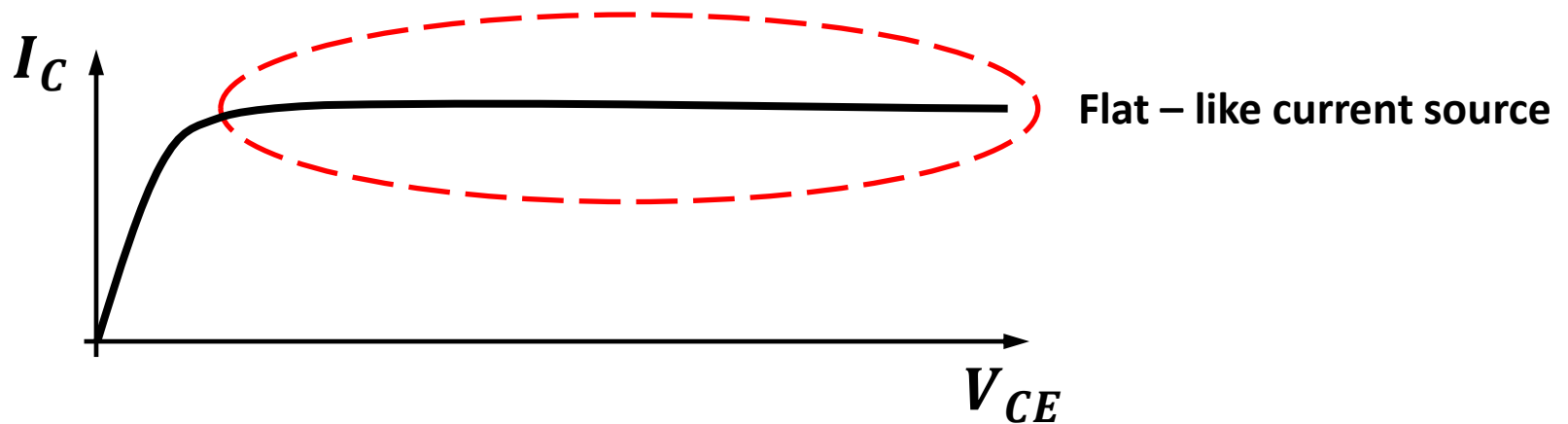
For a given  $I_B$  (input) we can measure the resulting  $I_C$  and  $V_{CE}$  (output)



# Example of complete $I$ - $V$ curves

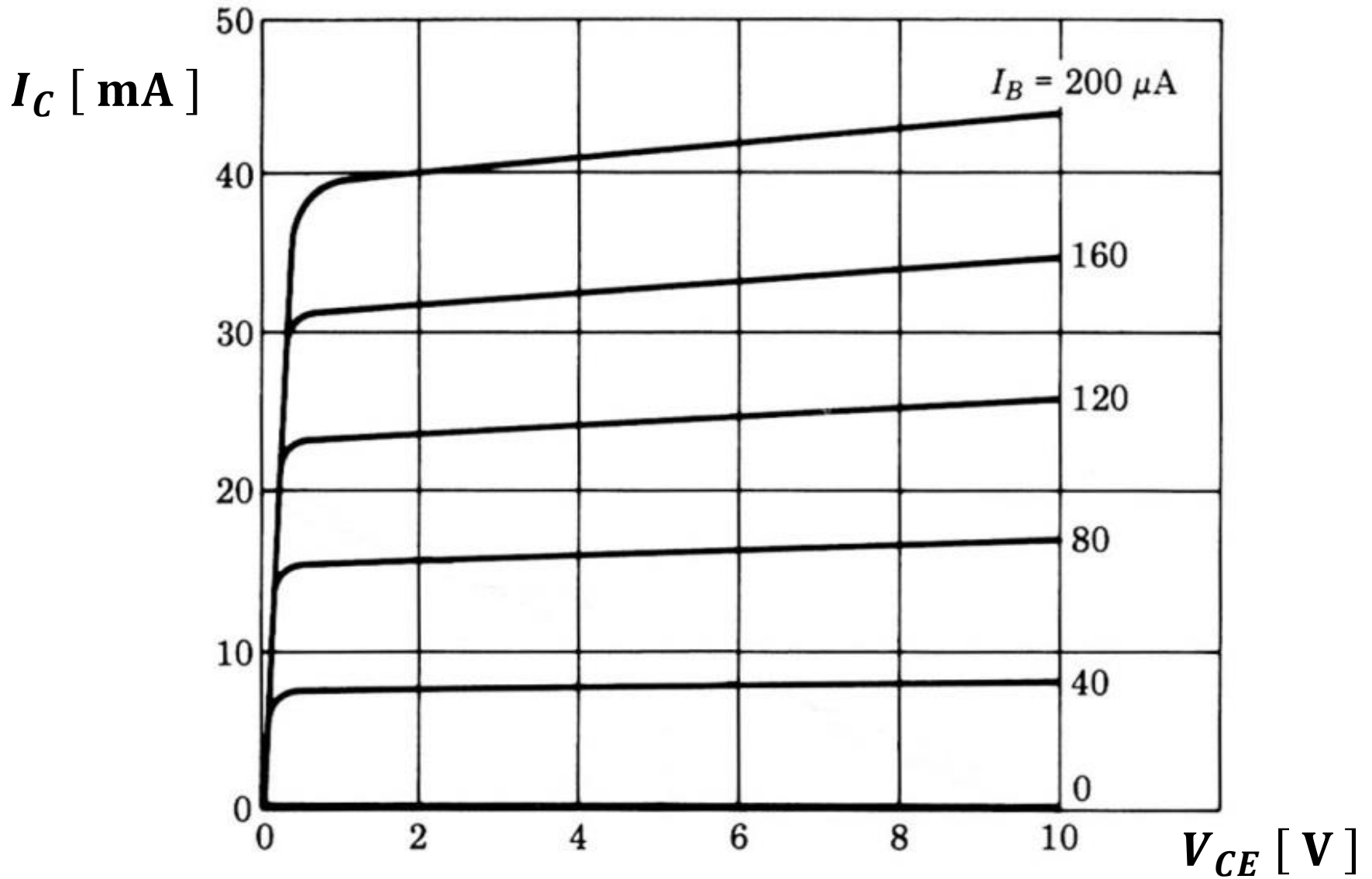
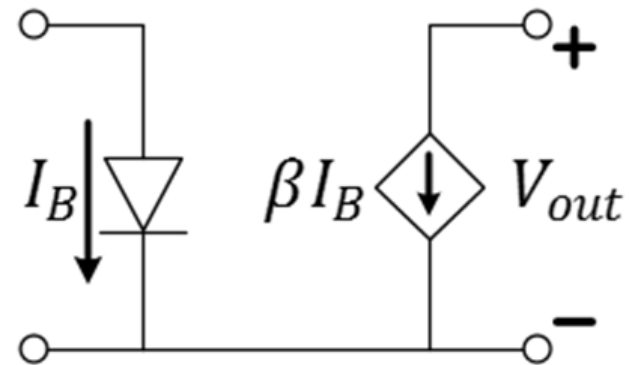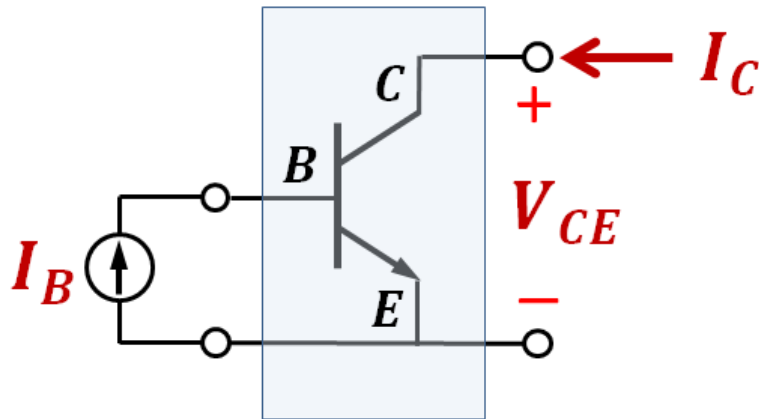
## BJT common emitter n-p-n circuit model





$\beta$  is the common emitter current gain factor  
(typically, between 5 and 100)

**NOTE:** The transistor has a small DC current in input and a much larger DC current in output.

However, it **DOES NOT** produce power. The power is provided by the DC sources which bias the device.

An AC input signal is amplified and a much larger AC signal is obtained at the output (at the cost of DC power).
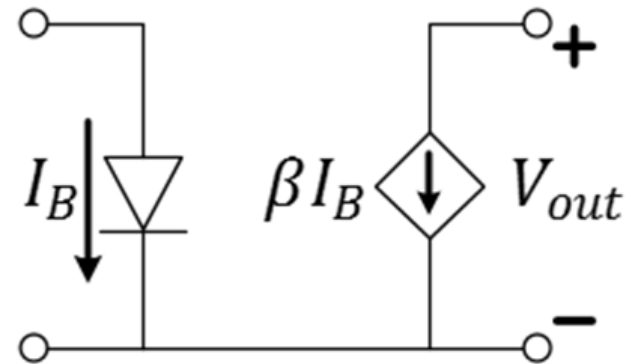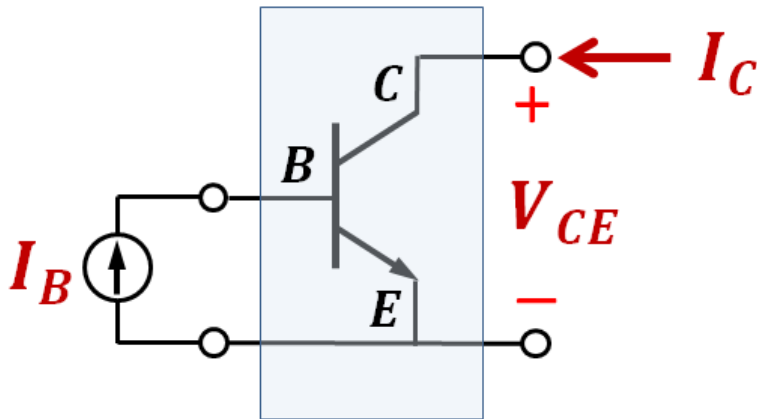
## States of BJT operation: 1) Cut-off mode





**OFF:  $V_{BE} < V_{BE}(\text{ON})$**

The base-emitter junction is like a *p-n* diode junction. If it is biased below threshold, the base current is negligible and there is no collector current in output. The output voltage  $V_{CE}$  is maximum (equal to the DC voltage applied to the collector).

For silicon transistors, typically  $V_{BE}(\text{ON}) \approx 0.6\text{V}$  to  $0.7\text{V}$
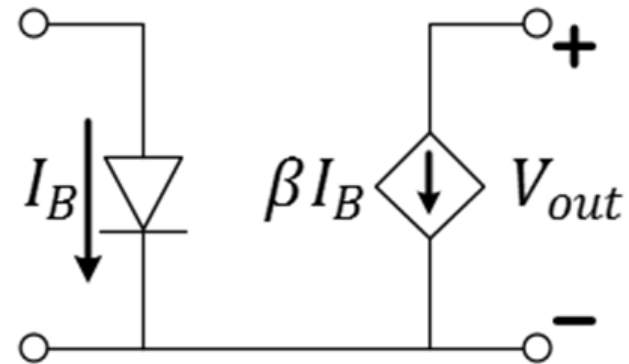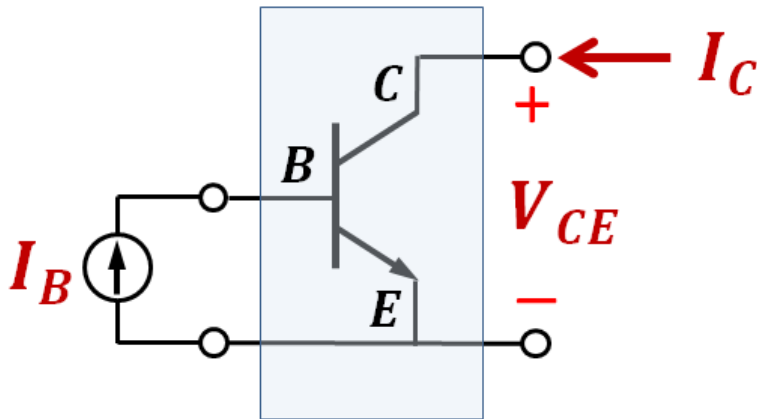
## States of BJT operation: 2) Forward Active mode





**ON:**  $V_{BE} = V_{BE}(\text{ON})$  &  $V_{CE} > V_{CE}(\text{sat})$

The base-emitter junction conducts, with input current  $I_B$ . The output voltage  $V_{CE}$  is less than the DC bias voltage on the collector.

As long as  $V_{CE}$  is larger than a minimum "saturation" value  $V_{CE}(\text{sat})$ , the transistor is in forward active mode, with collector current  $\beta I_B$  proportional to the base current.

For silicon transistors, typically  $V_{CE}(\text{sat}) \approx 0.2\text{V}$
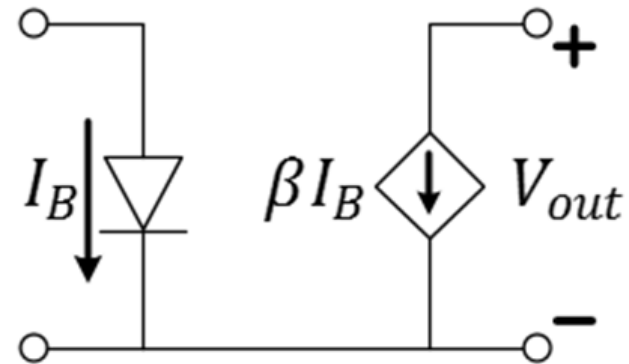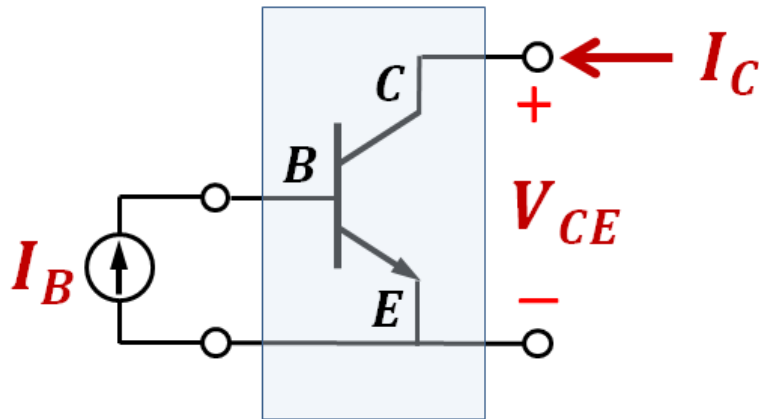
## States of BJT operation: 3) Saturation mode




**ON:**  $V_{BE} = V_{BE}(\text{ON})$  &  $V_{CE} = V_{CE}(\text{sat})$

**When the base current  $I_B$  exceeds a certain value, the voltage  $V_{CE}$  reaches the minimum saturation value  $V_{CE}(\text{sat})$ .**

**The collector current saturates and can no longer follow the base current.**

## When the transistor is ON

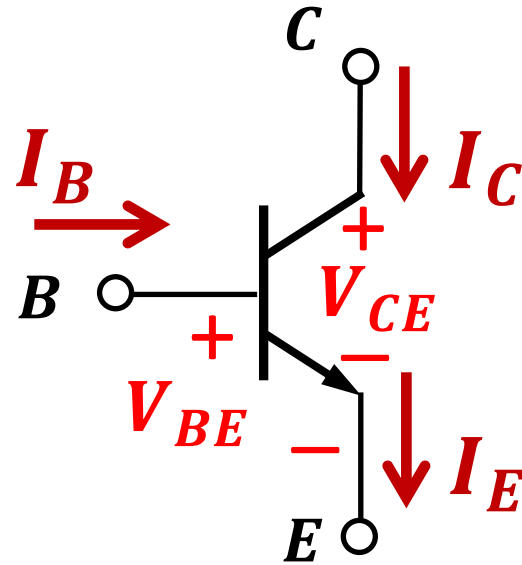

$$V_{BE} = V_{BE}(\text{ON}) \approx 0.6 \text{ to } 0.7\text{V}$$

$$I_B > 0 \quad I_C > 0 \quad I_E > 0$$

$$I_E = I_B + I_C$$

$$I_C = \beta I_B \quad \text{Forward active mode}$$

$$I_C = I_C(\text{sat}) \quad \text{Saturation mode} \quad [V_{CE} = V_{CE}(\text{sat}) \approx 0.2\text{V}]$$

# When the transistor is ON


## In Forward Active mode

$$I_C = \beta I_B$$

KCL  $I_E = I_B + I_C$

$$I_E = (\beta + 1)I_B$$
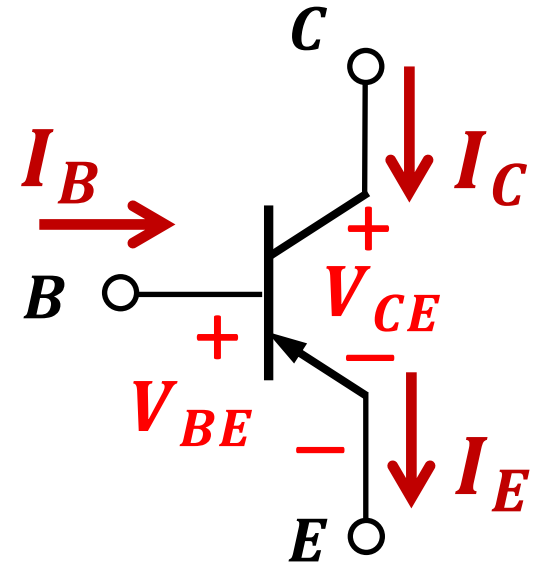
$$I_E = \frac{I_C}{\beta} + I_C = \frac{\beta + 1}{\beta} I_C = \frac{1}{\alpha} I_C$$



$$\alpha = \frac{\beta}{\beta + 1}$$

$$I_C = \alpha I_E$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

## Current transfer ratio

Quantifies the % of electrons originating from the emitter which are able to reach the collector



# BJT solution strategy (Summary)

## STEP 1 – Check if the BJT is ON

The voltage applied in input must turn on the  $p$ - $n$  junction (diode) between base and emitter so that

$$V_{BE} = V_{BE}(\text{on})$$

$$I_B \neq 0$$

If BJT is OFF → STOP here. If BJT is ON → PROCEED to STEP 2

## STEP 2 – Assume that the BJT is in Forward Active state

$$V_{BE} = V_{BE}(\text{on})$$

$$I_C = \beta I_B$$

If circuit analysis shows that  $V_{CE} > V_{CE}(\text{sat})$  the assumption is verified.

If assumption is verified → STOP here. If not → PROCEED to STEP 3

## STEP 3 – Select Saturation state

If the result from circuit analysis at STEP 2 is that  $V_{CE} < V_{CE}(\text{sat})$  then the calculated collector current is excessive.

Set  $V_{CE} = V_{CE}(\text{sat})$  and calculate the corresponding  $I_C = I_C(\text{sat})$

# BJT solution strategy

## STEP 1 – Check if the BJT is ON

The voltage applied in input must turn on the  $p$ - $n$  junction (diode) between base and emitter so that

$$V_{BE} = V_{BE}(\text{on})$$

$$I_B \neq 0$$

If BJT is OFF → STOP here. If BJT is ON → PROCEED to STEP 2

# BJT solution strategy

## STEP 2 – Assume BJT is in Forward Active state

$$V_{BE} = V_{BE}(\text{on})$$

$$I_C = \beta I_B$$

If circuit analysis shows that assumption is verified.

$$V_{CE} > V_{CE}(\text{sat}) \quad \text{the}$$

**If assumption is verified → STOP here. If not → PROCEED to STEP 3**

# BJT solution strategy

## STEP 3 – Select Saturation state

If the result from circuit analysis at STEP 2 is that

$$V_{CE} < V_{CE}(\text{sat})$$

then the calculated collector current is excessive.

Set  $V_{CE} = V_{CE}(\text{sat})$

and calculate the corresponding  $I_C = I_C(\text{sat})$

$V_{BE} \geq V_{BE}(\text{ON})?$

NO

YES

BJT *OFF*

$V_{CE} > V_{CE}(\text{sat}) ?$

YES

NO

Forward Active

$$I_C = \beta I_B$$

Saturation

$$V_{CE} = V_{CE}(\text{sat})$$

$$I_C = I_C(\text{sat})$$