

ECE 205 “Electrical and Electronics Circuits”

Spring 2024 – LECTURE 25

MWF – 12:00pm

Prof. Umberto Ravaioli


2062 ECE Building

Lecture 25 – Summary


Learning Objectives

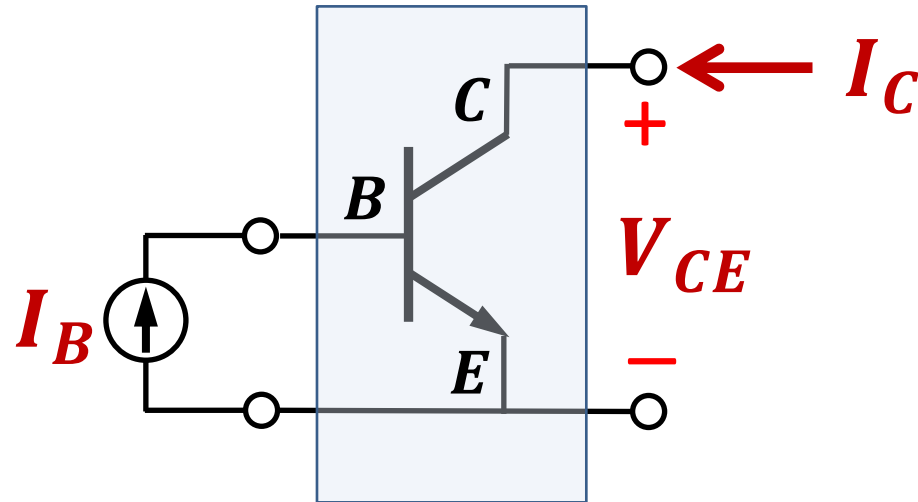1. Solution approaches for BJT circuits


Common Emitter is the most important configuration




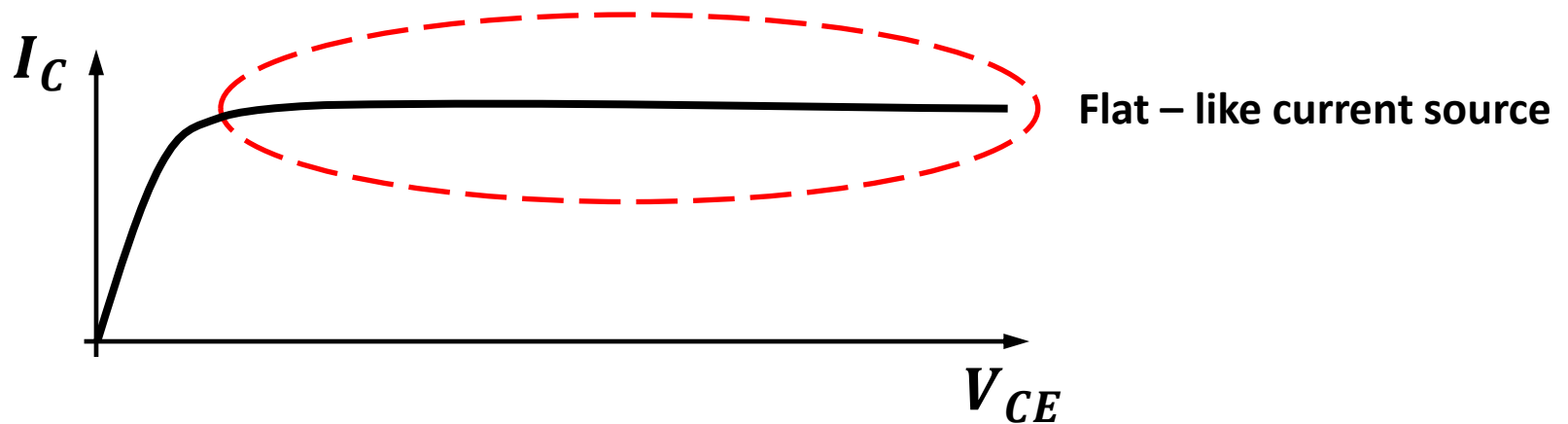
For a given I_B (input) we can measure the resulting I_C and V_{CE} (output)



Example of complete I - V curves

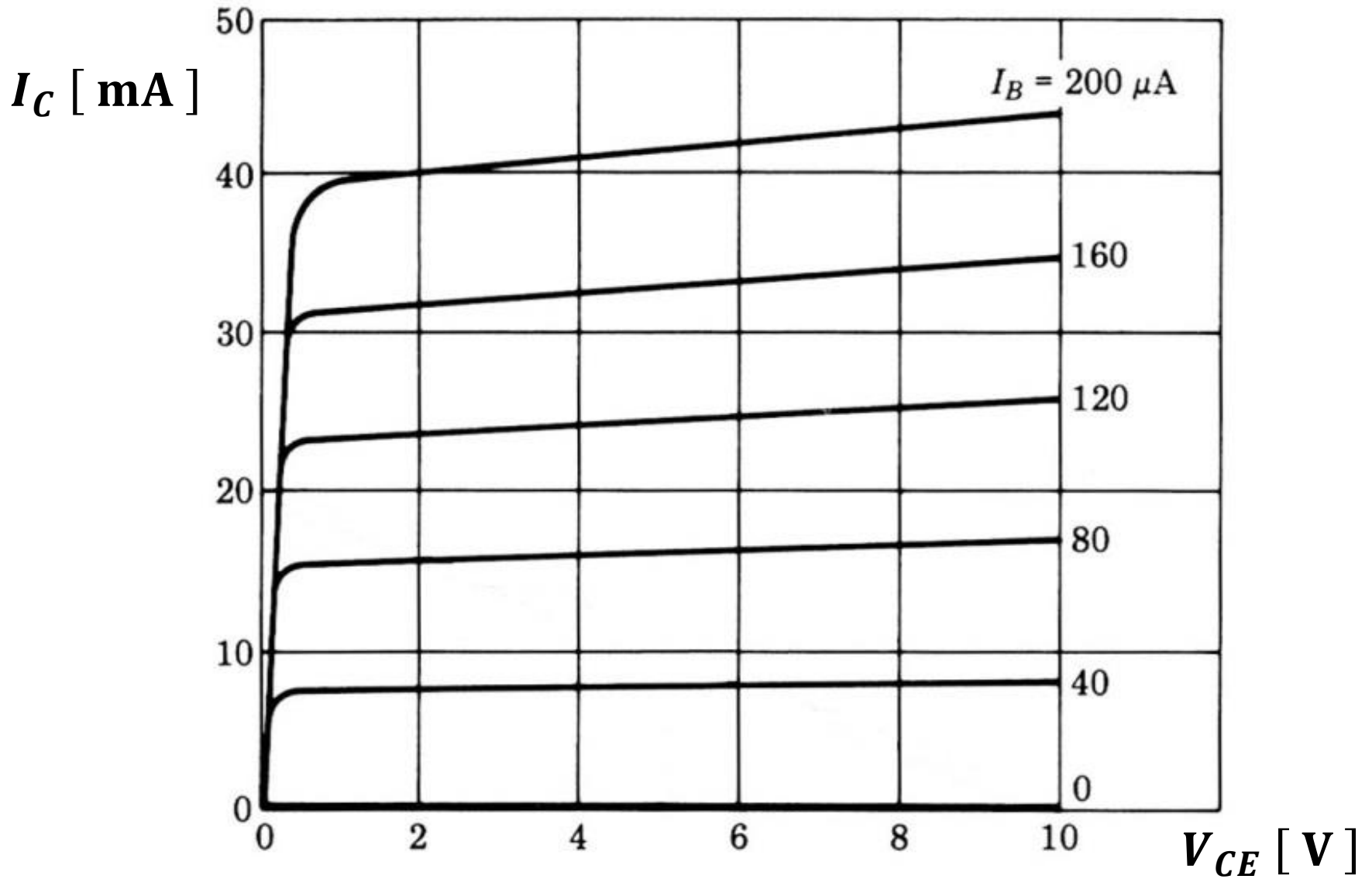

BJT common emitter n-p-n circuit model

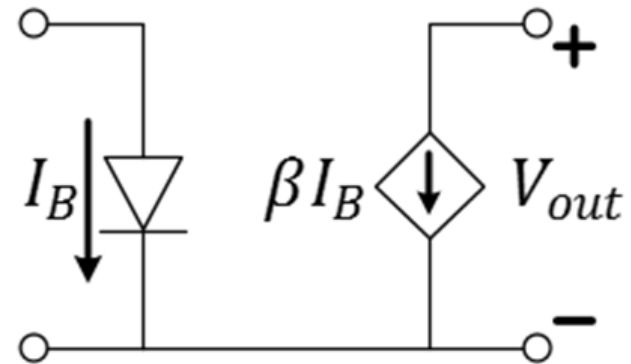
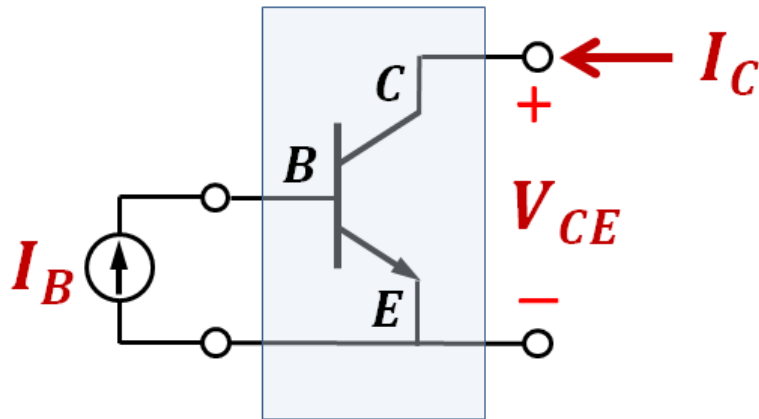


This equivalent circuit model describes the BJT when it behaves as an amplifier (Forward-Active mode)

β is the common emitter current gain factor
(typically, between 5 and 100)

Another name used by manufacturers is: h_{FE}

BJT common emitter n-p-n circuit model

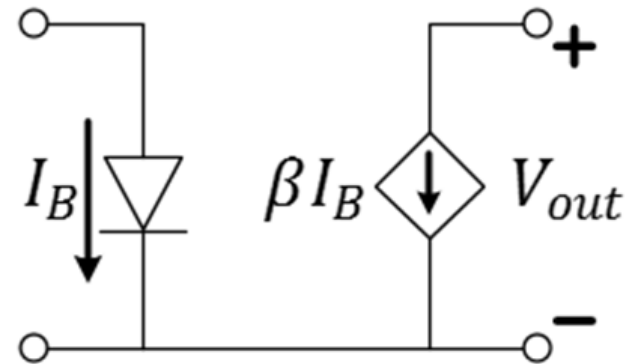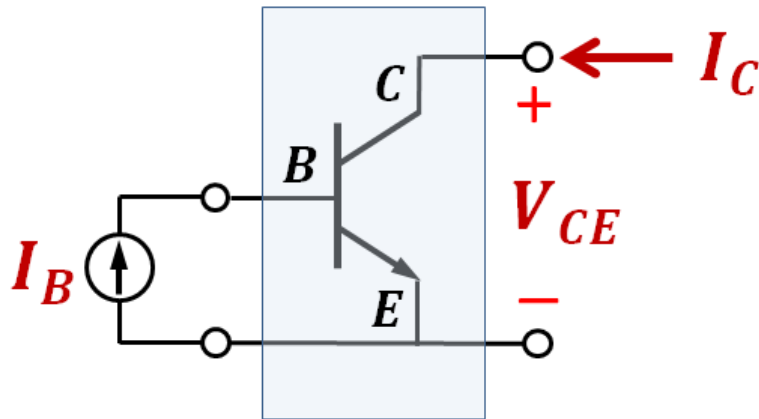

NOTE: The transistor has a small DC base current in input and a much larger DC collector current in output.



However, it DOES NOT produce power. The power is provided by the DC generators which bias the device.

An AC input signal can be amplified and a much larger AC signal is obtained at the output (at the cost of DC power).

There are 3 regimes of operation

- 1) CUT-OFF MODE**
- 2) FORWARD-ACTIVE MODE**
- 3) SATURATION MODE**

States of BJT operation: 1) Cut-off mode

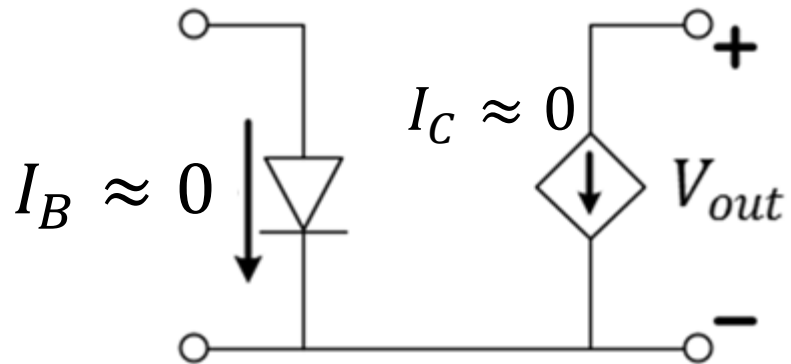
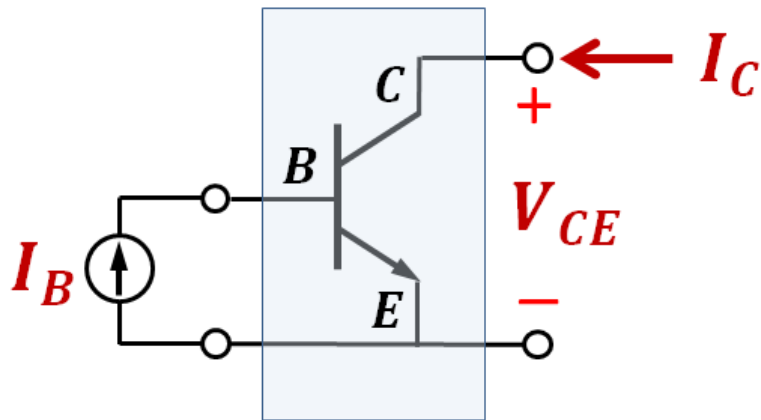


OFF: $V_{BE} < V_{BE}(\text{ON})$

The base-emitter junction is like a $p-n$ diode junction. If it is biased below threshold, the base current is negligible and there is no collector current in output. The output voltage V_{CE} is maximum (equal to the DC voltage applied to the collector).

For silicon transistors, typically $V_{BE}(\text{ON}) \approx 0.6\text{V}$ to 0.7V

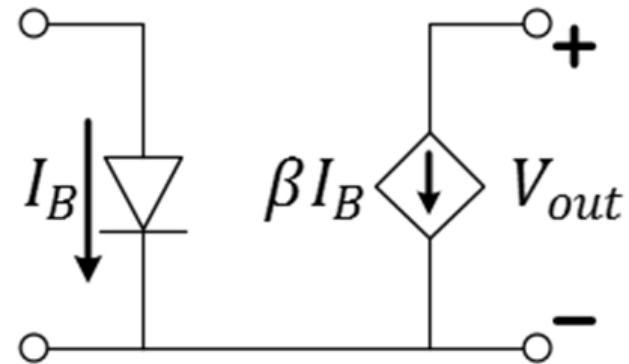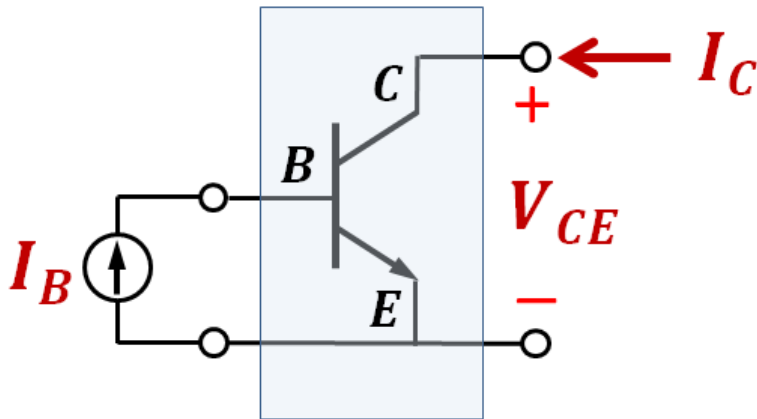States of BJT operation: 2) Forward Active mode





ON: $V_{BE} = V_{BE}(\text{ON})$ & $V_{CE} > V_{CE}(\text{sat})$

The base-emitter junction conducts, with input current I_B . The output voltage V_{CE} is less than the DC bias voltage on the collector.

As long as V_{CE} is larger than a minimum "saturation" value $V_{CE}(\text{sat})$, the transistor is in forward active mode, with collector current βI_B proportional to the base current.

For silicon transistors, typically $V_{CE}(\text{sat}) \approx 0.2\text{V}$

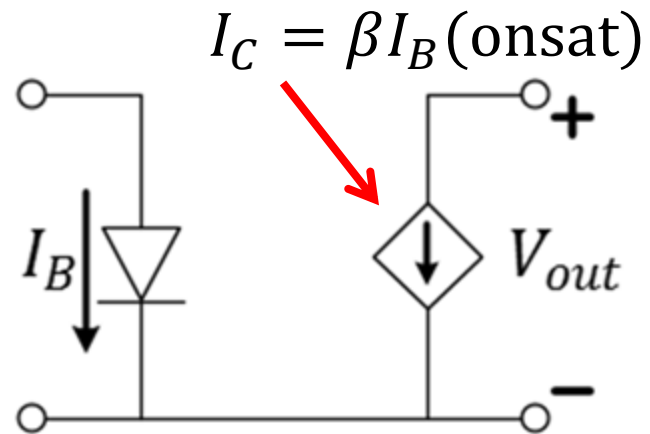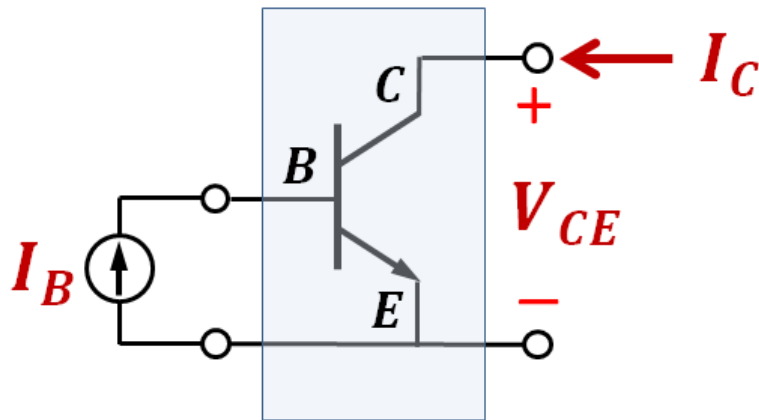States of BJT operation: 3) Saturation mode



ON: $V_{BE} = V_{BE}(\text{ON})$ & $V_{CE} = V_{CE}(\text{sat})$

When the base current I_B reaches a sufficiently high value, the voltage V_{CE} reaches the minimum saturation value $V_{CE}(\text{sat})$. **The collector current saturates and can no longer follow the base current.** This starts happening at the "onset of saturation" $I_B = I_B(\text{onsat})$, corresponding to the condition under which $V_{CE} = V_{CE}(\text{sat})$ is first reached, when base current is increased.

$$I_C = I_C(\text{sat}) = \text{constant for } I_B \geq I_B(\text{onsat})$$

THIS IS VALID WHEN THE EMITTER TERMINAL IS GROUNDED.

IMPORTANT FOR PROBLEM SOLUTION


At the onset of saturation point, the **Forward-Active** and the **Saturation** conditions coincide.

So, as the base current increases, this is the last point at which the amplification relation

$$I_C = \beta I_B = \beta I_B(\text{onsat})$$

is still formally valid, after which amplification control is lost by the BJT and the collector current stops growing.

When the transistor is ON

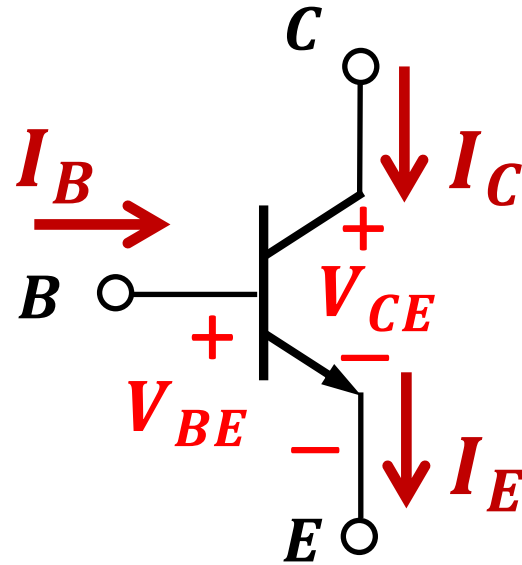

$$V_{BE} = V_{BE}(\text{ON}) \approx 0.6 \text{ to } 0.7\text{V}$$

$$I_B > 0 \quad I_C > 0 \quad I_E > 0$$

$$I_E = I_B + I_C$$

$$\left\{ \begin{array}{ll} I_C = \beta I_B & \text{Forward active mode} \\ I_C = I_C(\text{sat}) & \text{Saturation mode } [V_{CE} = V_{CE}(\text{sat}) \approx 0.2\text{V}] \end{array} \right.$$

Typically

When the transistor is ON


In Forward Active mode

$$I_C = \beta I_B$$

KCL $I_E = I_B + I_C$

$$I_E = (\beta + 1)I_B$$
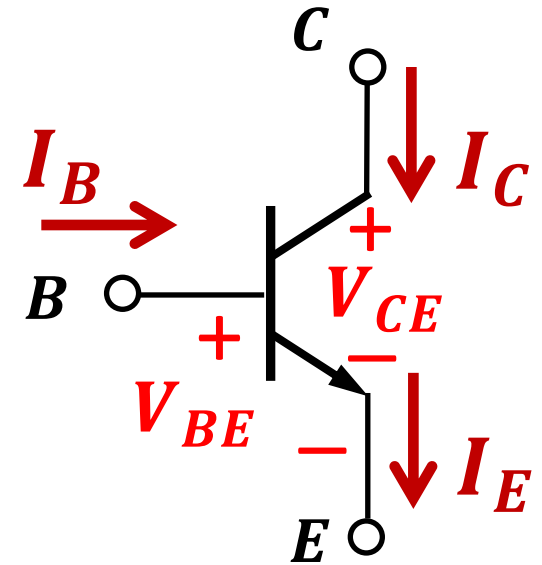
$$I_E = \frac{I_C}{\beta} + I_C = \frac{\beta + 1}{\beta} I_C = \frac{1}{\alpha} I_C$$



$$\alpha = \frac{\beta}{\beta + 1} = \frac{I_C}{I_E}$$



$$I_C = \alpha I_E$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

Current transfer ratio

Quantifies the % of electrons (holes in *p-n-p* BJT) originating from the emitter which are able to reach the collector


Common Emitter I-V curves Example

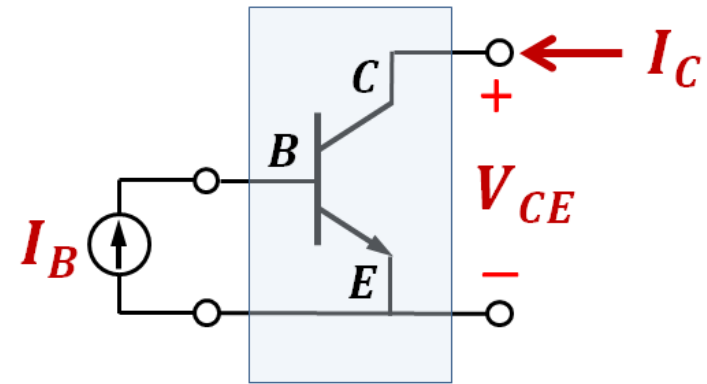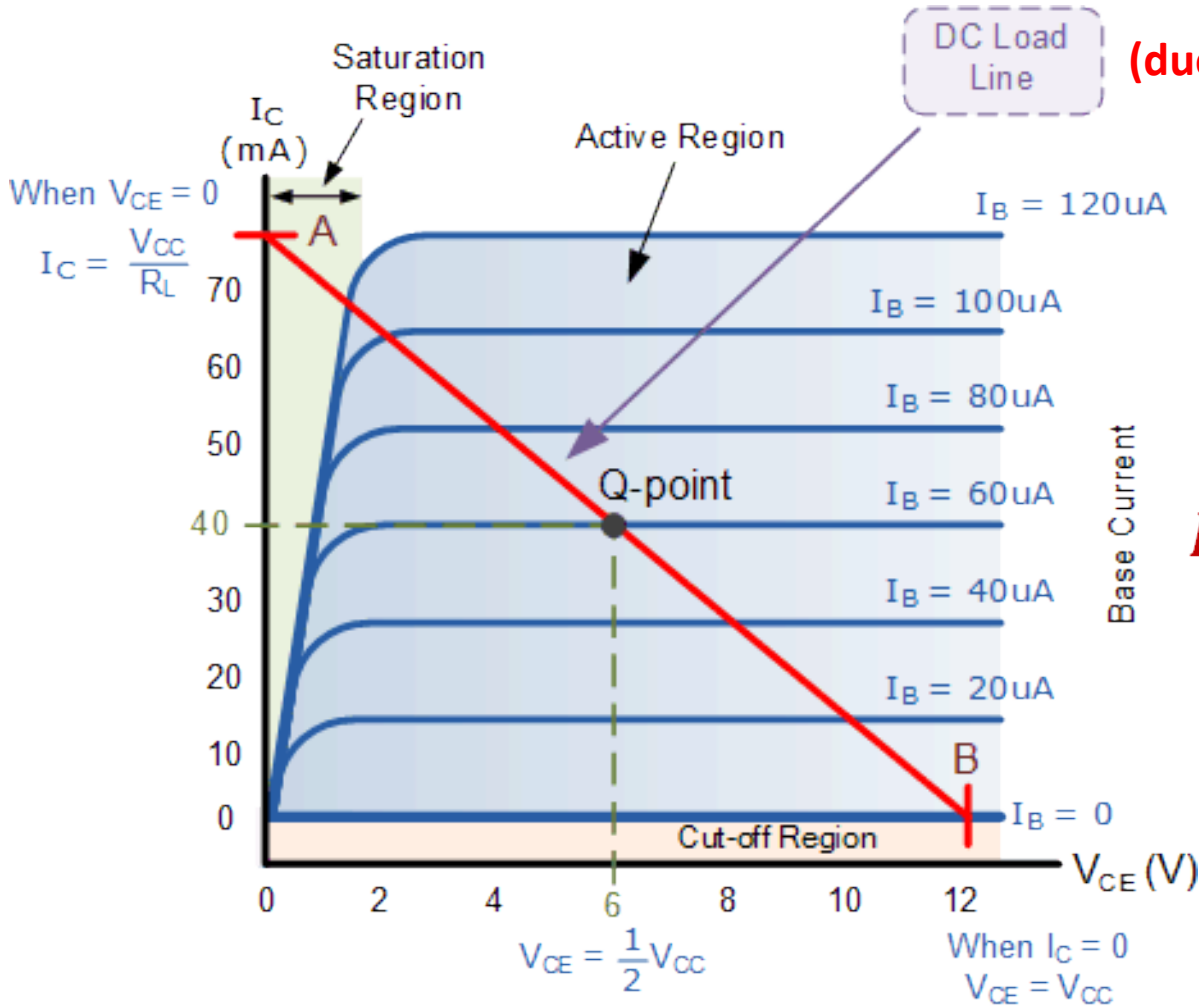


V_{CC} = Collector bias voltage

One curve for each value of I_B

BJT as amplifier or as logic switch

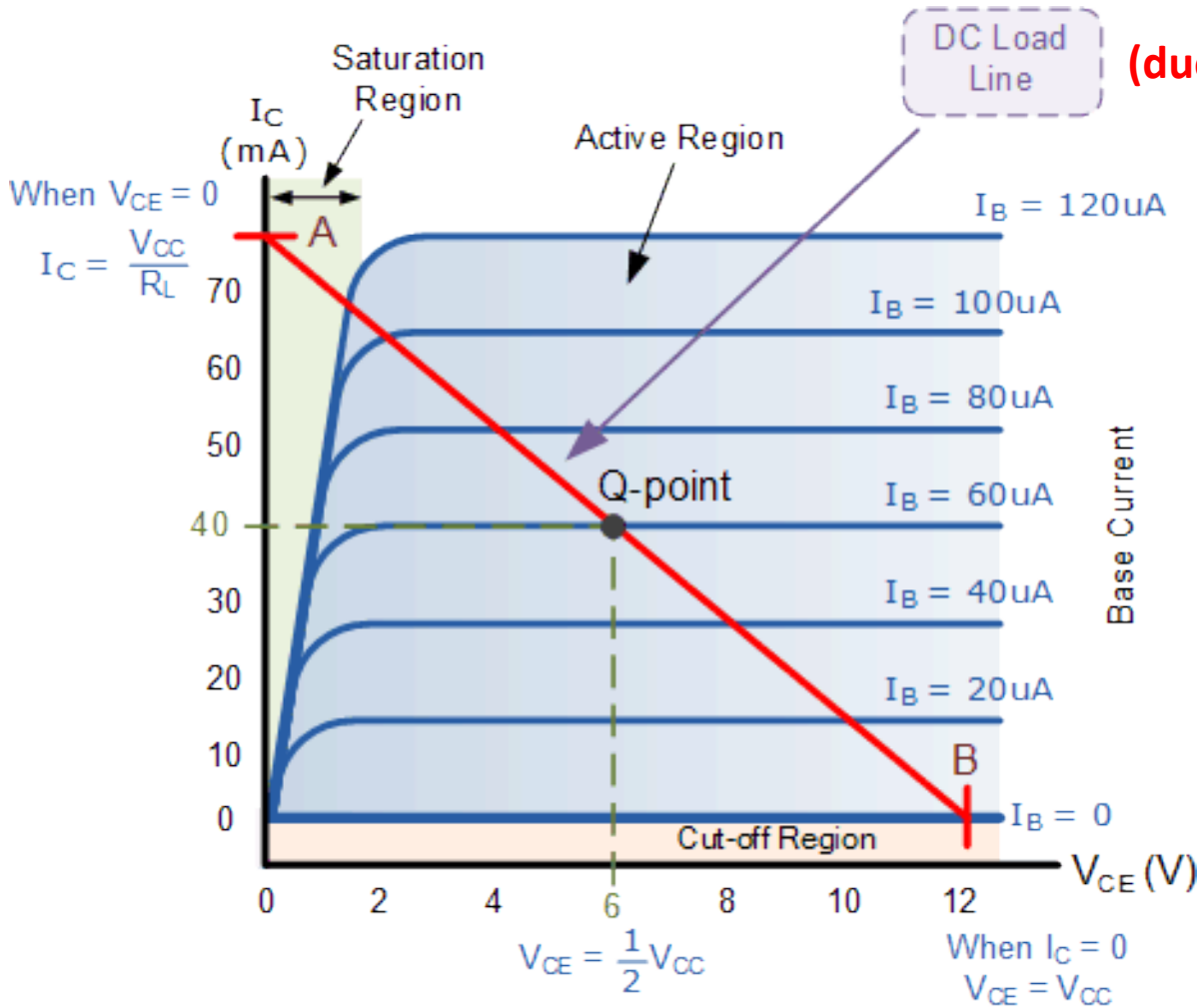



(due to the collector circuit)

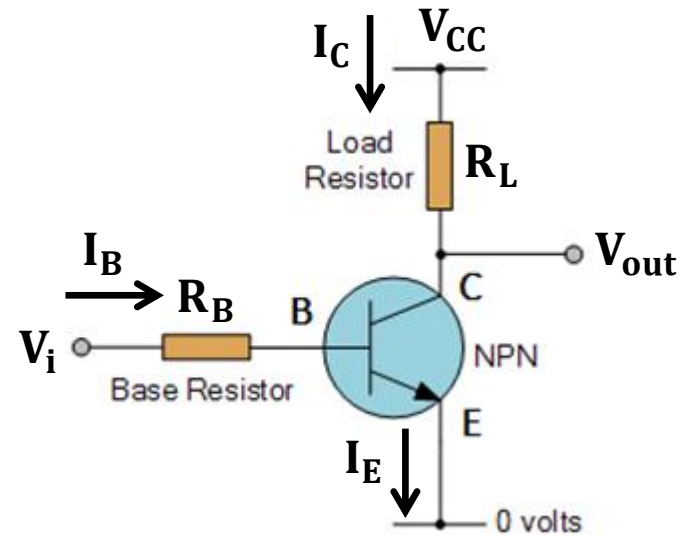

V_{CC} = Collector bias voltage

Q bias point – Amplifier
A and B points – Logic Inverter

BJT Circuit Representations

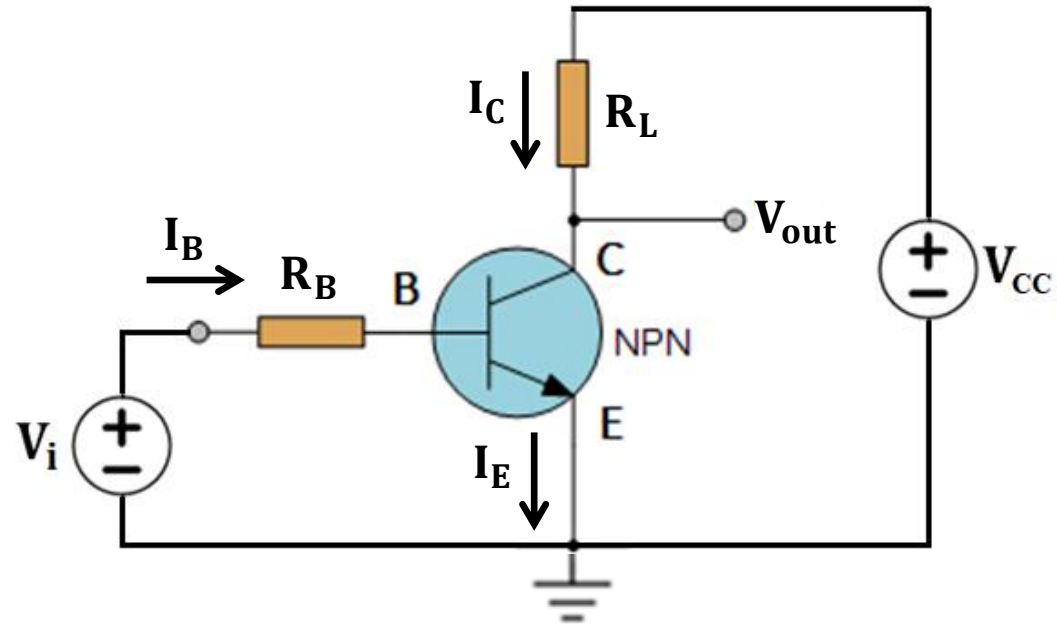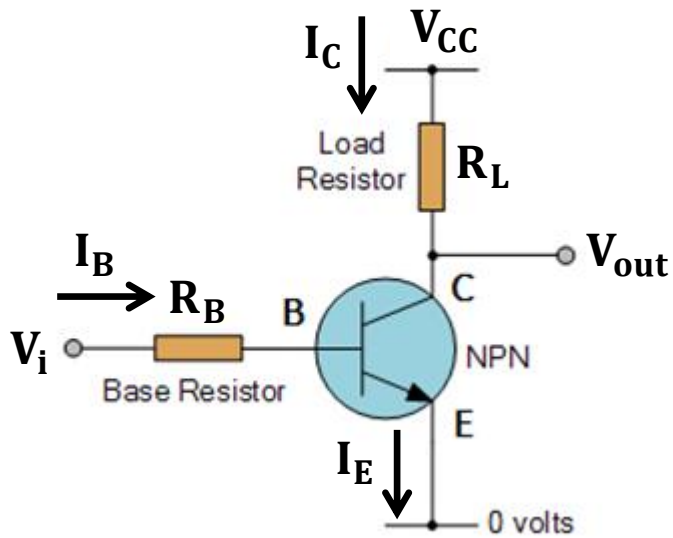

Common BJT circuit
representation in technical
schematics




Equivalent to this circuit


Conventional $V_{CE}(\text{sat})$

- Manufacturers provide device specs, with an “average” measured value for $V_{CE}(\text{sat})$.
- Simple models assume that for any base current, this specific average $V_{CE}(\text{sat})$ value is established in all practical application.
- Of course, this is a model approximation, but usually a very acceptable one.

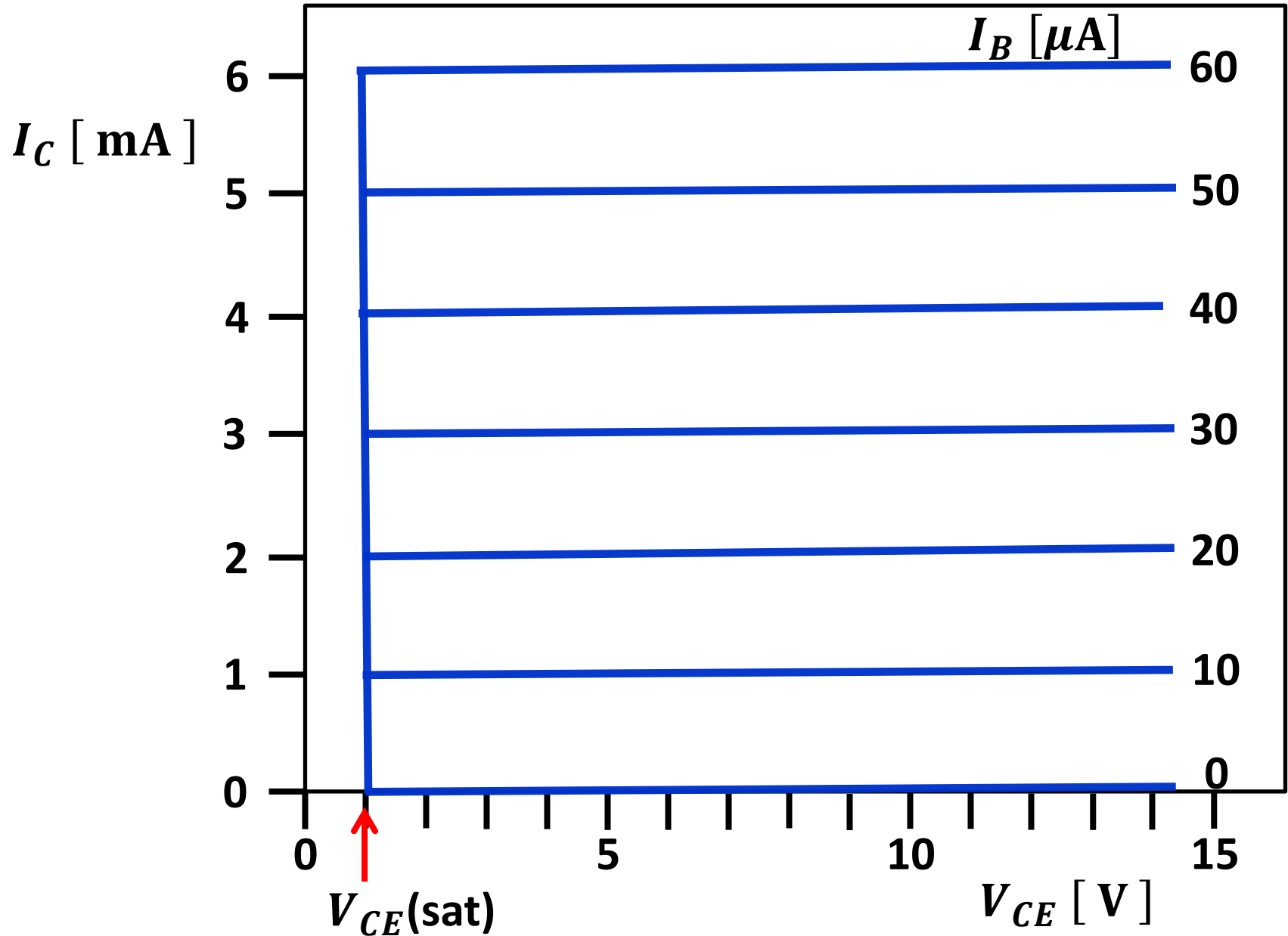
Simplified I-V curves corresponding to the approximate BJT model



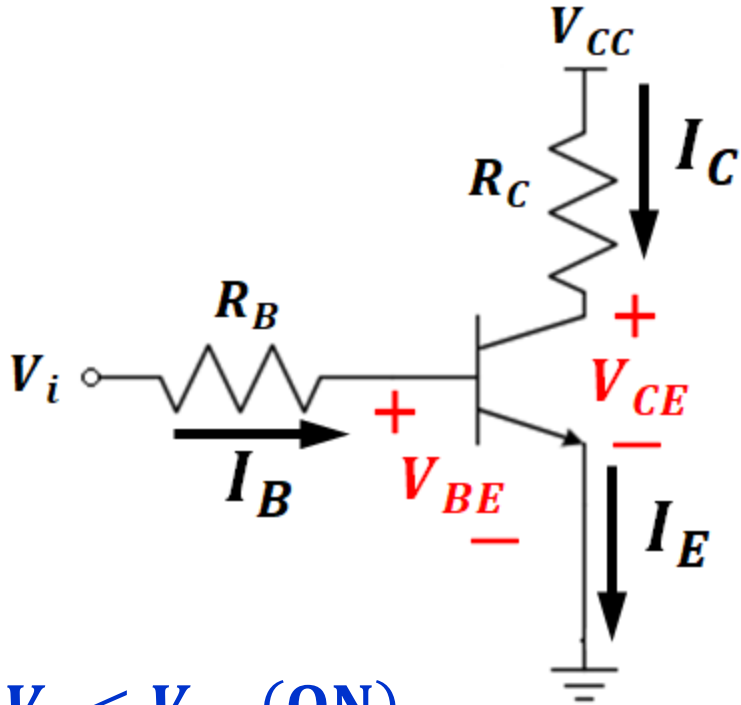Emitter connected to ground (Common emitter configuration)



I_C [mA]

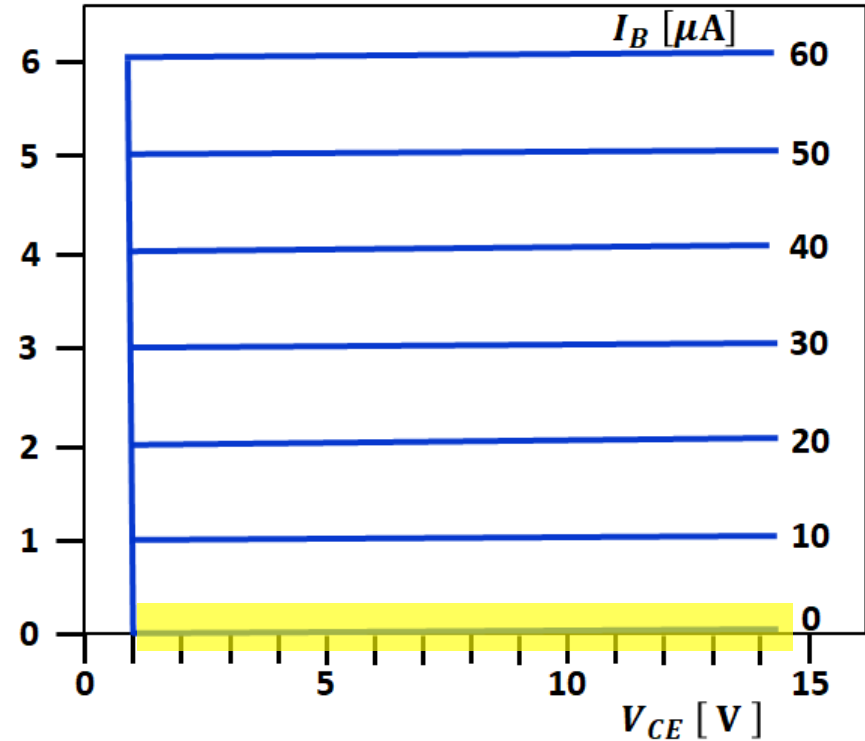

$V_i < V_{BE(\text{ON})}$

$V_{CE} = V_{CC}$

$I_B = I_C = 0$

$V_{BE} < V_{BE(\text{ON})}$

$V_{BE} \geq V_{BE(\text{ON})}$


$V_{BE} \geq V_{BE(\text{ON})}$

$V_{CE} \geq V_{CE(\text{sat})}$


$V_{CE} < V_{CE(\text{sat})}$

CUT-OFF

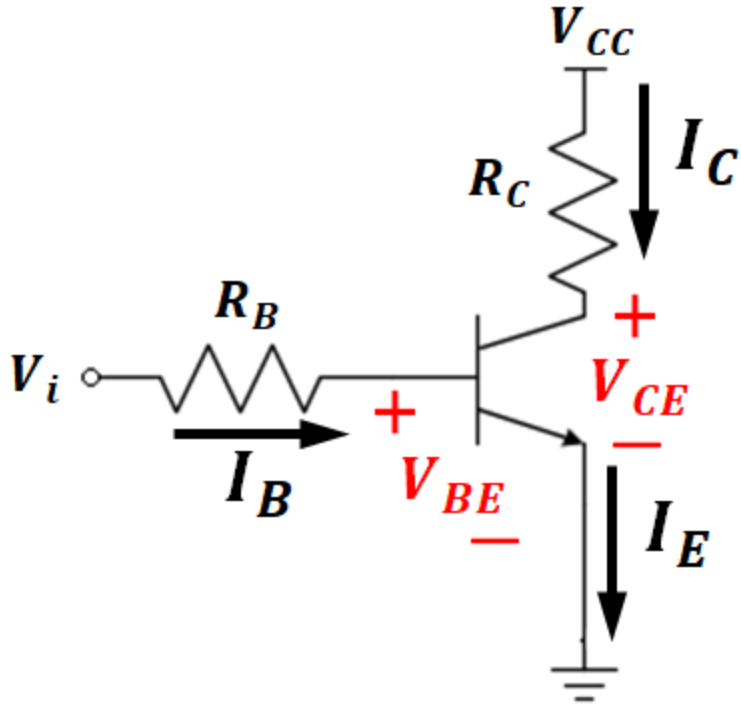Emitter connected to ground (Common emitter configuration)



I_C [mA]

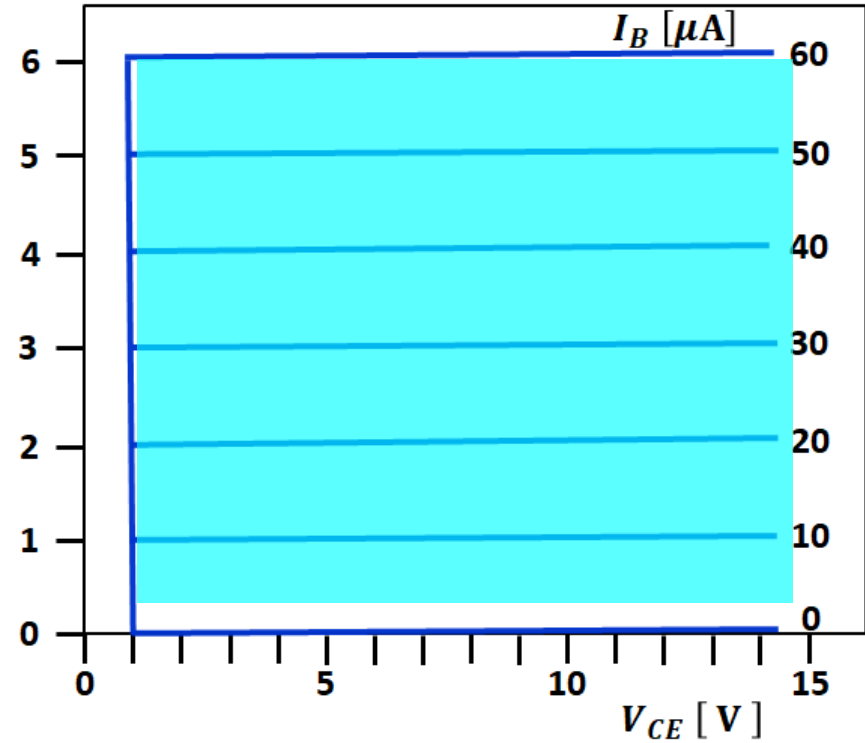

$$V_i > V_{BE(ON)}$$

$$I_C = \beta I_B$$

$$V_{BE} < V_{BE(ON)}$$

$$V_{BE} \geq V_{BE(ON)}$$



$$V_{BE} \geq V_{BE(ON)}$$

$$V_{CE} \geq V_{CE(sat)}$$

$$V_{CE} < V_{CE(sat)}$$

FORWARD-ACTIVE

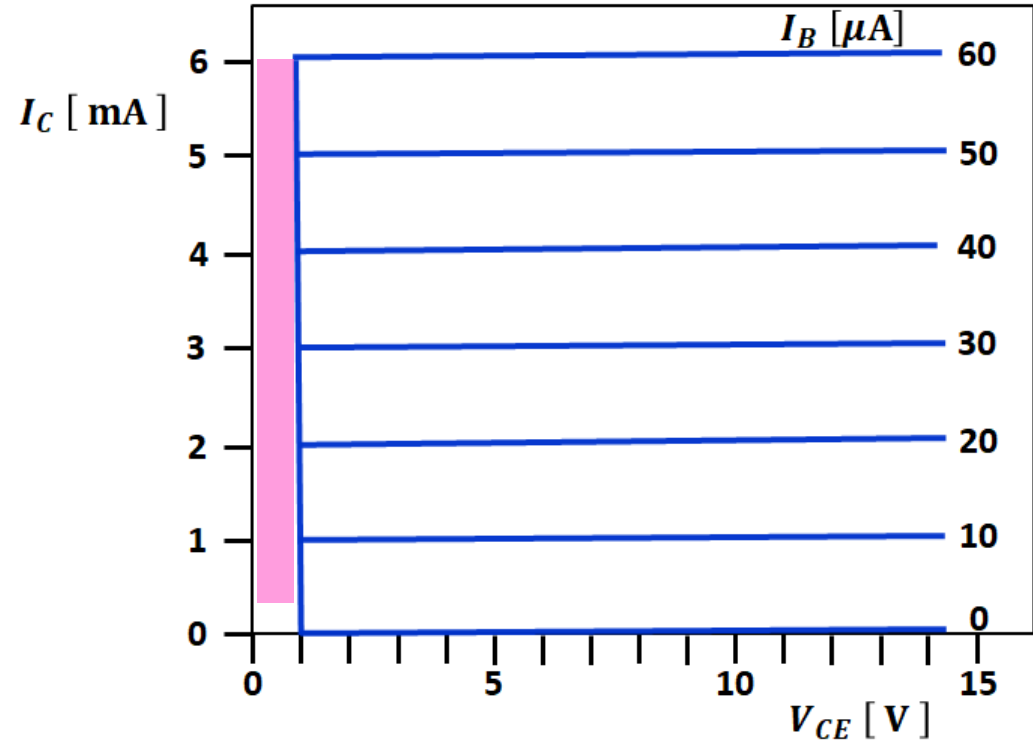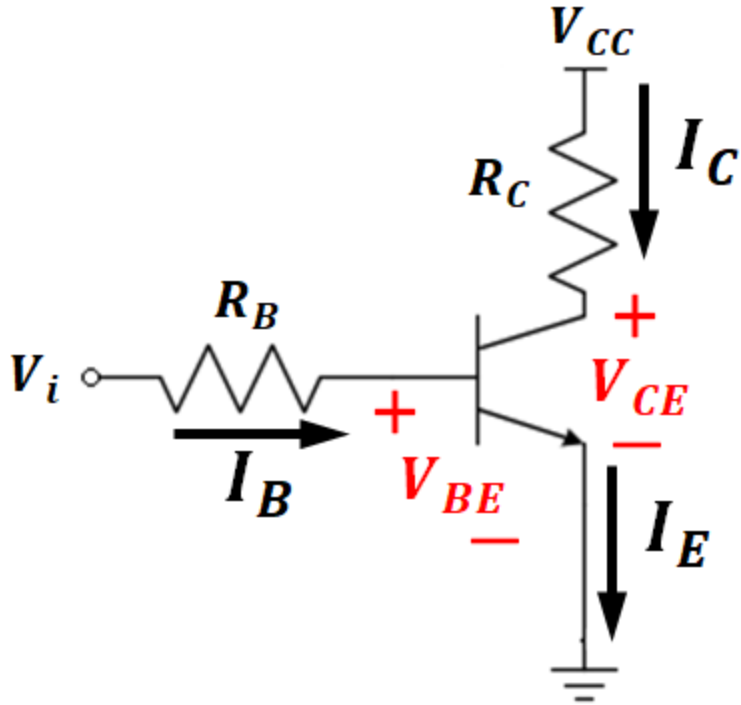Emitter connected to ground (Common emitter configuration)



$$V_i > V_{BE(ON)}$$

$$I_C = I_C(sat)$$

$$V_{BE} < V_{BE(ON)}$$

$$V_{BE} \geq V_{BE(ON)}$$

$$V_{BE} \geq V_{BE(ON)}$$

$$V_{CE} \geq V_{CE(sat)}$$

$$V_{CE} < V_{CE(sat)}$$

SATURATION

BJT solution strategy – SUMMARY on single slide

STEP 1 – Check if the BJT is ON

The voltage applied in input must turn on the $p-n$ junction (diode) between base and emitter so that

$$V_{BE} = V_{BE}(\text{on})$$

$$I_B \neq 0$$

If BJT is OFF → STOP here. If BJT is ON → PROCEED to STEP 2

STEP 2 – Assume that the BJT is in Forward Active state

$$V_{BE} = V_{BE}(\text{on})$$

$$I_C = \beta I_B$$

If circuit analysis shows that $V_{CE} > V_{CE}(\text{sat})$ the assumption is verified.

If assumption is verified → STOP here. If not → PROCEED to STEP 3

STEP 3 – Select Saturation state

If the result from circuit analysis at STEP 2 is that $V_{CE} < V_{CE}(\text{sat})$ then the calculated collector current is excessive.

Set $V_{CE} = V_{CE}(\text{sat})$ and calculate the corresponding $I_C = I_C(\text{sat})$

BJT solution strategy

STEP 1 – Check if the BJT is ON

The voltage applied in input must turn on the p - n junction (diode) between base and emitter so that

$$V_{BE} = V_{BE}(\text{on})$$

$$I_B \neq 0$$

If BJT is OFF → STOP here.

If BJT is ON → PROCEED to STEP 2

BJT solution strategy

STEP 2 – Assume BJT is in Forward Active state

$$V_{BE} = V_{BE}(\text{on})$$

$$I_C = \beta I_B$$

If circuit analysis shows that assumption is verified.

$$V_{CE} > V_{CE}(\text{sat})$$

the

If assumption is verified → STOP here.

If not → PROCEED to STEP 3

BJT solution strategy

STEP 3 – Select Saturation state

If the result from circuit analysis at STEP 2 is that

$$V_{CE} < V_{CE}(\text{sat})$$

then the calculated collector current is excessive.

Set $V_{CE} = V_{CE}(\text{sat})$

and calculate the corresponding

$$I_C = I_C(\text{sat})$$

$V_{BE} < V_{BE}(\text{ON})?$

YES

NO

BJT *OFF*

$V_{CE} > V_{CE}(\text{sat}) ?$

YES

NO

Forward Active



$$I_C = \beta I_B$$

Saturation

$$V_{CE} = V_{CE}(\text{sat})$$



$$I_C = I_C(\text{sat})$$

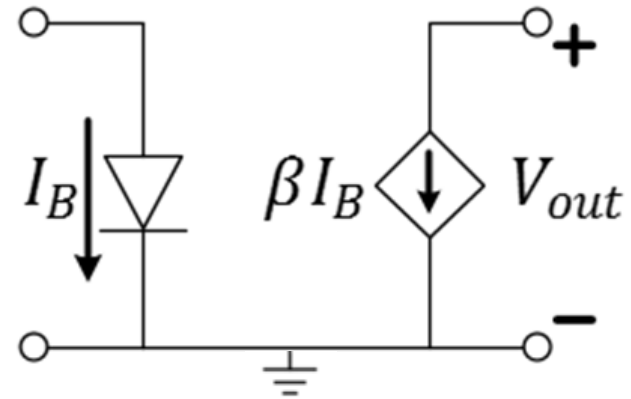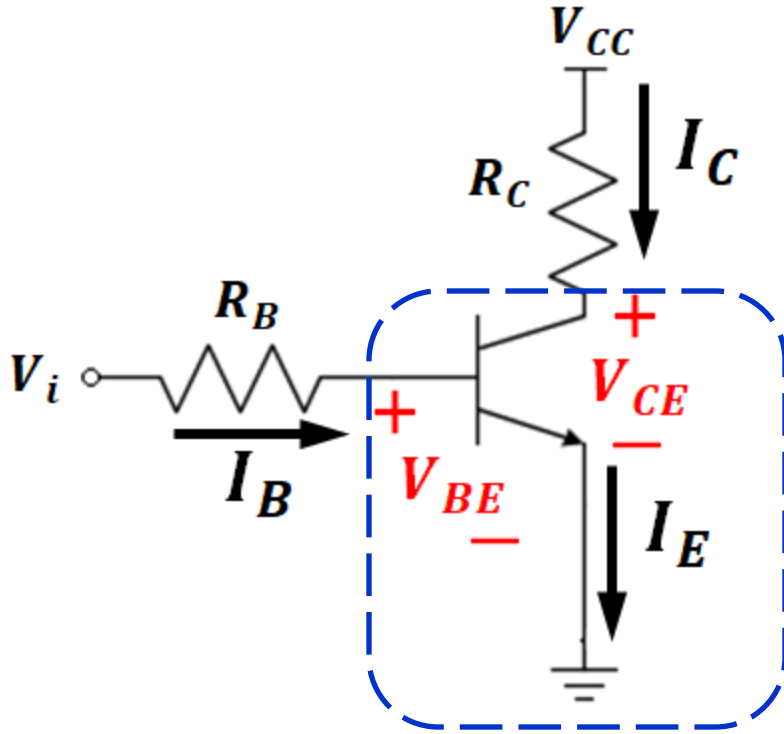Emitter connected to ground (Common emitter configuration)



The left and right portions of the circuit are only coupled by the amplification factor β which controls the collector current controlled current source in output.

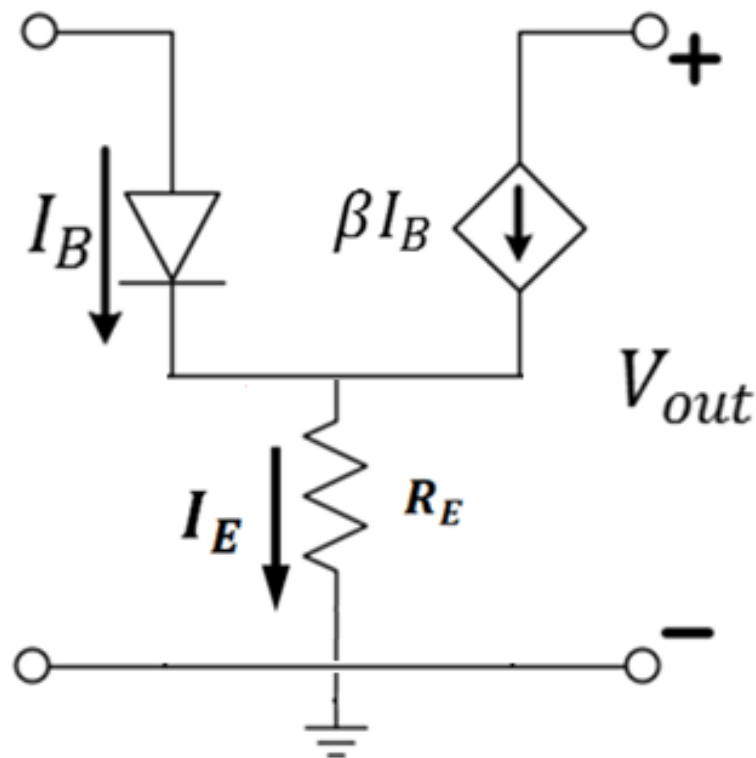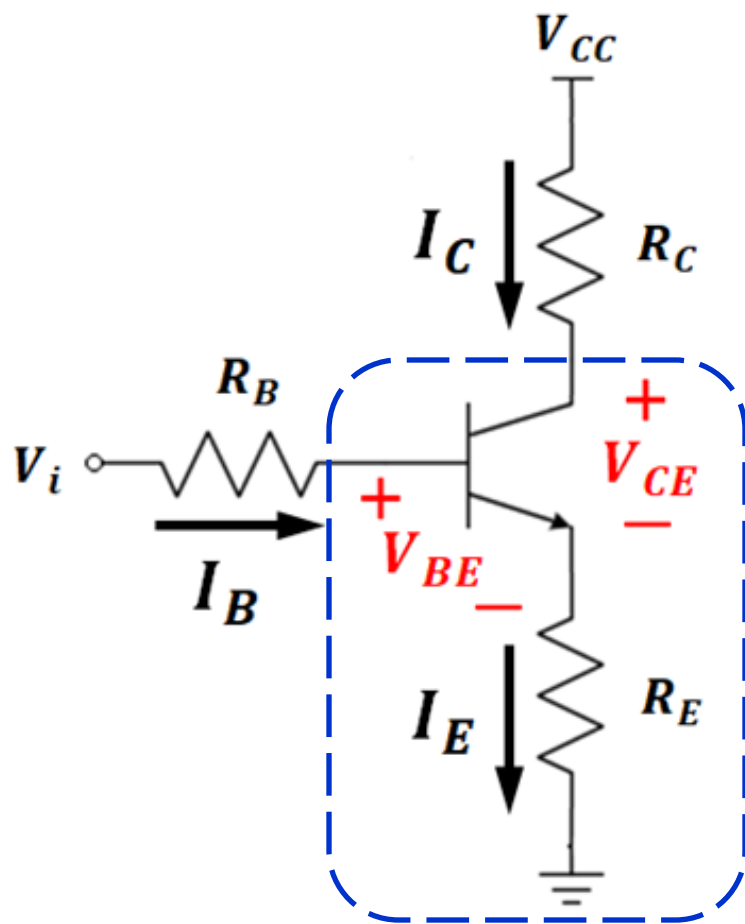Addition of a resistor between emitter and ground




The emitter resistor R_E introduces also a coupling feedback between left and right, since the potential drop on R_E is shared by the KVL's. In saturation conditions, I_C is not constant, as a consequence.

Example 1: Find the BJT mode of operation

$$V_{BE}(\text{on}) = 0.6\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 100$$

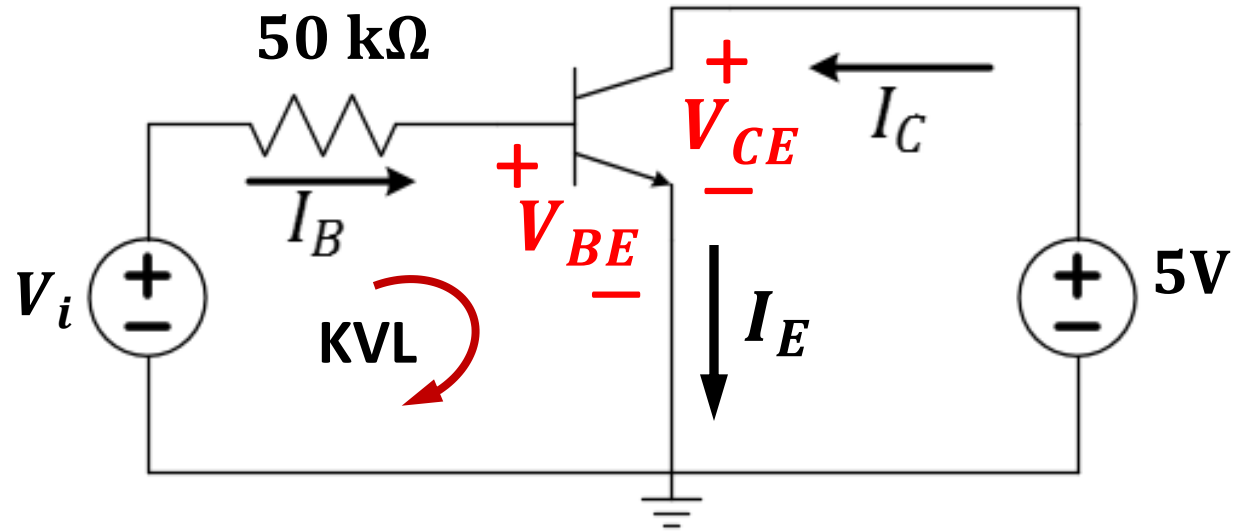

$$(a) V_i = 0.5\text{V}$$


$$(b) V_i = 2.0\text{V}$$

Example 1: Find the BJT mode of operation

$$V_{BE(\text{on})} = 0.6\text{V}$$

$$V_{CE(\text{sat})} = 0.2\text{V}$$

$$\beta = 100$$

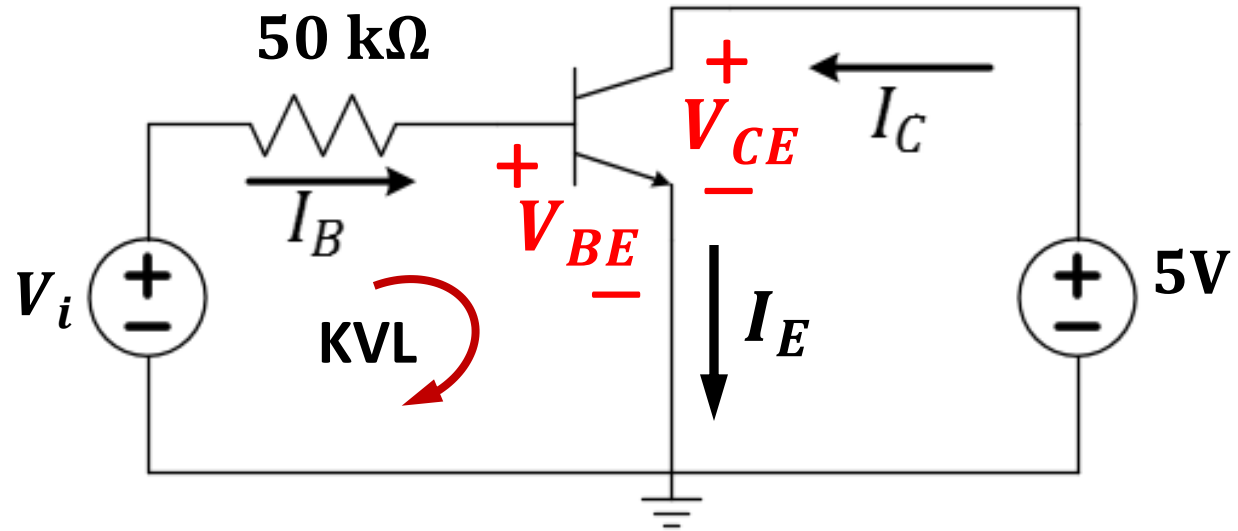

$$(a) V_i = 0.5\text{V}$$

BJT is OFF since

$$V_i < V_{BE(\text{on})}$$


Cut-off mode

$$V_{BE}(\text{on}) = 0.6\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 100$$

$$(b) V_i = 2.0\text{V}$$

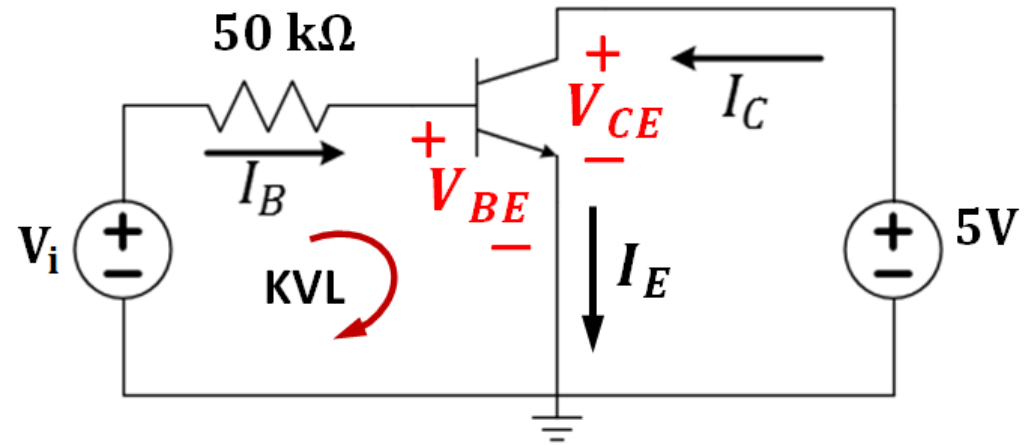

BJT is ON since $V_i > V_{BE}(\text{on})$

Assume Forward Active mode


$$V_{CE} = 5\text{V} > V_{CE}(\text{sat})$$

$$V_{BE}(\text{on}) = 0.6\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 100$$

$$(b) V_i = 2.0\text{V}$$

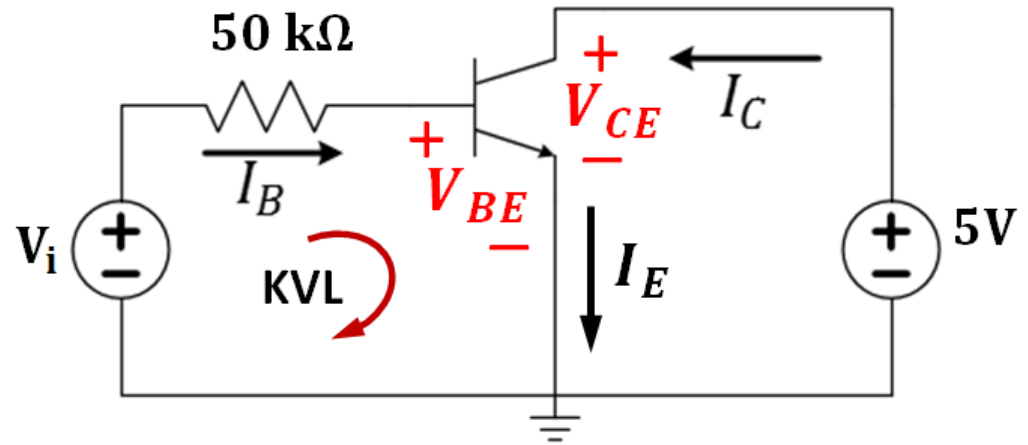

BJT is ON since $V_i > V_{BE}(\text{on})$

Assume Forward Active mode

$$V_{CE} = 5\text{V} > V_{CE}(\text{sat})$$

$$-V_i + I_B R_B + V_{BE}(\text{on}) = 0$$


$$-2 + I_B \times 50\text{k}\Omega + 0.6 = 0$$

$$I_B = \frac{1.4}{50\text{k}} = 0.028\text{mA}$$

$$V_{BE}(\text{on}) = 0.6\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 100$$

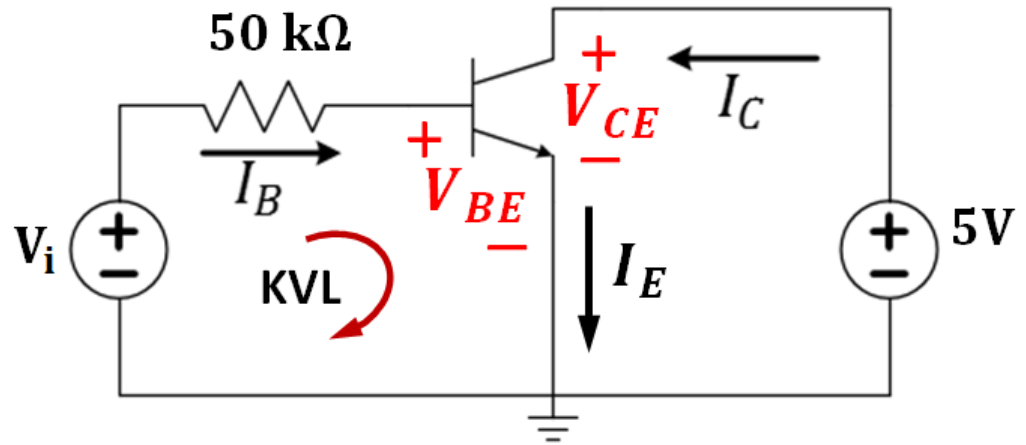

$$(b) V_i = 2.0\text{V}$$

BJT is ON since $V_i > V_{BE}(\text{on})$

Assume Forward Active mode

$$V_{CE} = 5\text{V} > V_{CE}(\text{sat})$$

$$-V_i + I_B R_B + V_{BE}(\text{on}) = 0$$

$$-2 + I_B \times 50\text{k}\Omega + 0.6 = 0$$

$$I_B = \frac{1.4}{50\text{k}} = 0.028\text{mA}$$

Let's check collector and emitter currents

$$I_C = \beta I_B = 100 \times 0.028 = 2.8\text{mA}$$

$$I_E = I_B + I_C = 2.8 + 0.028 = \frac{\beta + 1}{\beta} I_C = 2.828\text{mA}$$

Example 2: Find the BJT mode of operation


$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(a) V_i = 0.5\text{V}$$

$$(b) V_i = 3.5\text{V}$$

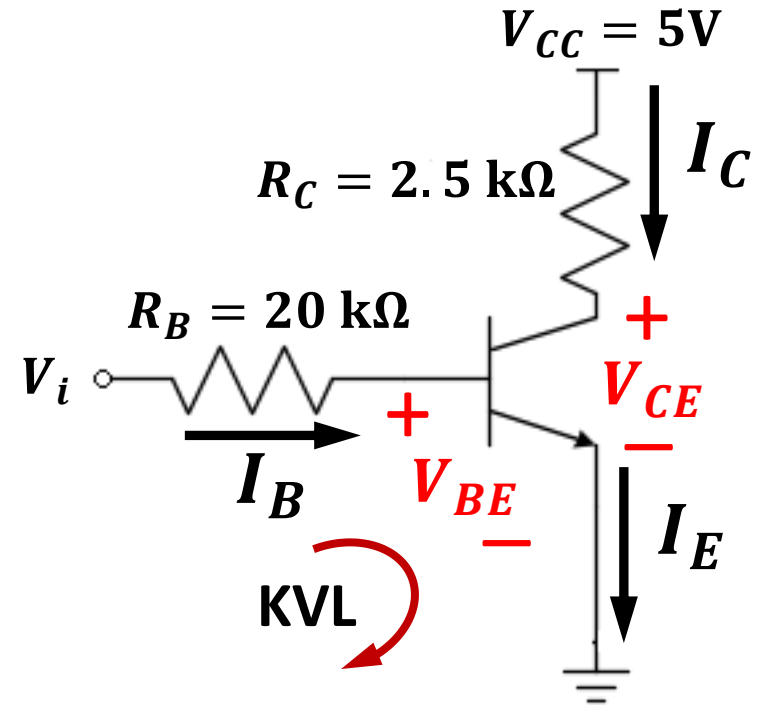

$$V_{BE(\text{on})} = 0.7\text{V}$$

$$V_{CE(\text{sat})} = 0.2\text{V}$$


$$\beta = 200$$

$$(a) V_i = 0.5\text{V}$$

BJT is OFF since

$$V_i < V_{BE(\text{on})}$$

Cut-off mode

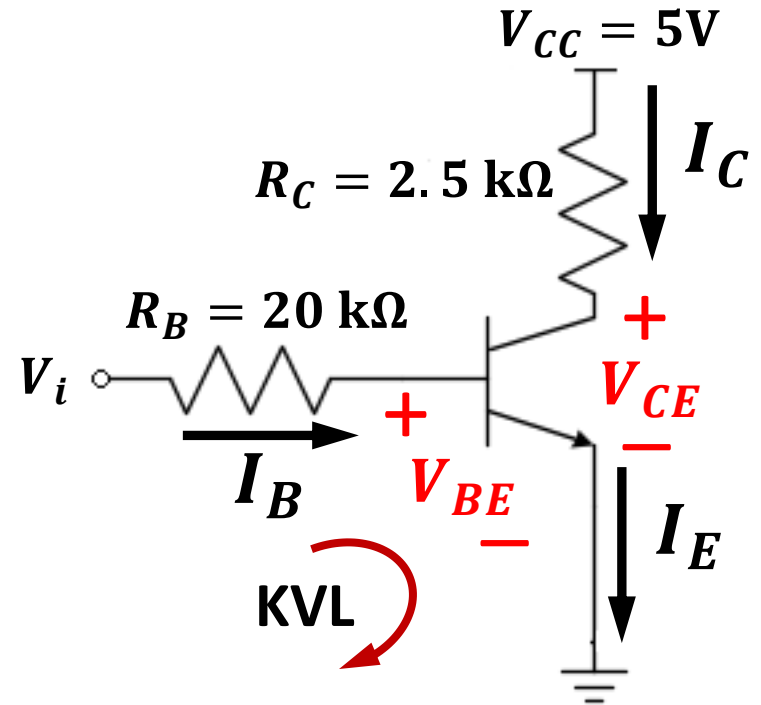

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$


$$(b) V_i = 3.5\text{V}$$

BJT is ON since $V_i > V_{BE}(\text{on})$

Assume forward active mode and check the collector behavior

$$\text{KVL} \quad -3.5 + I_B \times 20\text{k}\Omega + 0.7 = 0$$
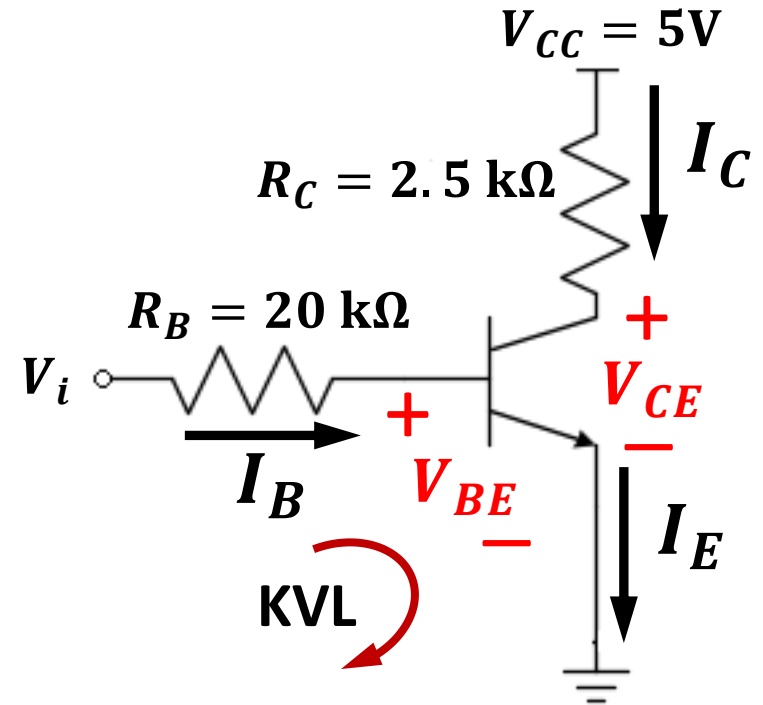
$$I_C = \beta I_B = 200 \times 0.14 = 28\text{mA}$$



$$I_B = 0.14\text{mA}$$

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$


BJT is ON since $V_i > V_{BE}(\text{on})$

Assume forward active mode and check the collector behavior

$$\text{KVL} \quad -3.5 + I_B \times 20\text{k}\Omega + 0.7 = 0$$

$$I_C = \beta I_B = 200 \times 0.14 = 28\text{mA}$$
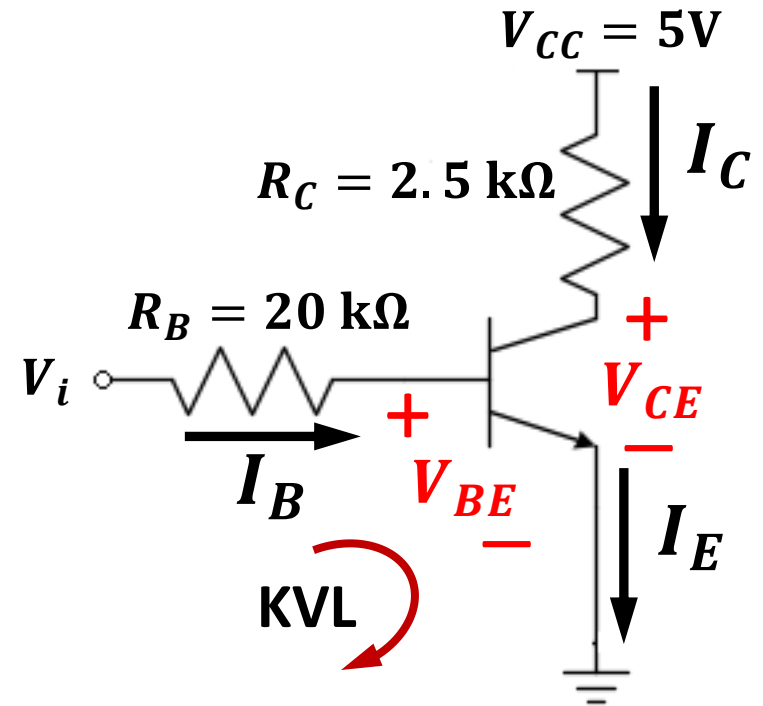
$$V_{CE} = V_{CC} - I_C R_C = 5 - 28\text{m} \times 2.5\text{k} = -65\text{V} < 0.2\text{V}$$



$$I_B = 0.14\text{mA}$$

Contradiction

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$

BJT is ON since $V_i > V_{BE}(\text{on})$

Assume forward active mode and check the collector behavior


$$\text{KVL} \quad -3.5 + I_B \times 20\text{k}\Omega + 0.7 = 0$$

$$I_B = 0.14\text{mA}$$

$$I_C = \beta I_B = 200 \times 0.14 = 28\text{mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 5 - 28\text{m} \times 2.5\text{k} = -65\text{V} < 0.2\text{V}$$
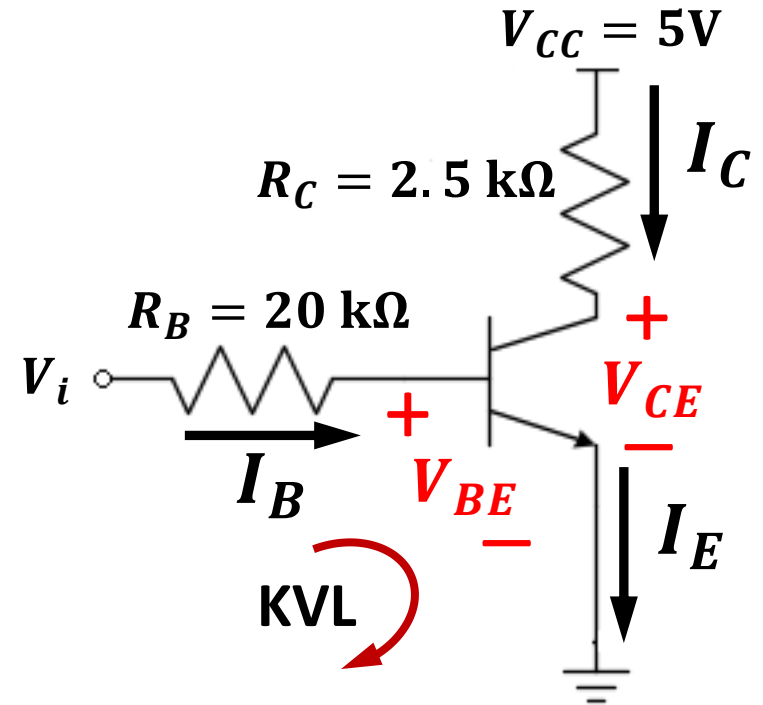
$$V_{CE} = V_{CE}(\text{sat}) = 0.2\text{V} \quad \text{Saturation mode}$$



Contradiction

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$


BJT is ON since $V_i > V_{BE}(\text{on})$

Let's find the collector current at onset of saturation

$$I_B = 0.14\text{mA}$$

$$I_C = \beta I_B = 28\text{mA}$$

Under Forward-Active assumption

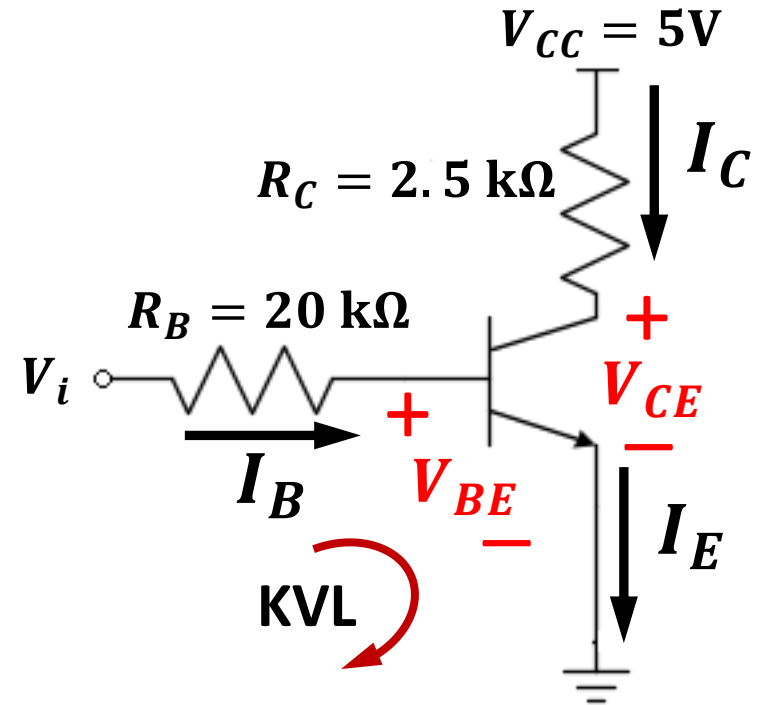

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$


BJT is ON since $V_i > V_{BE}(\text{on})$

Let's find the collector current at onset of saturation

$$I_B = 0.14\text{mA}$$

$$I_C = \beta I_B = 28\text{mA}$$
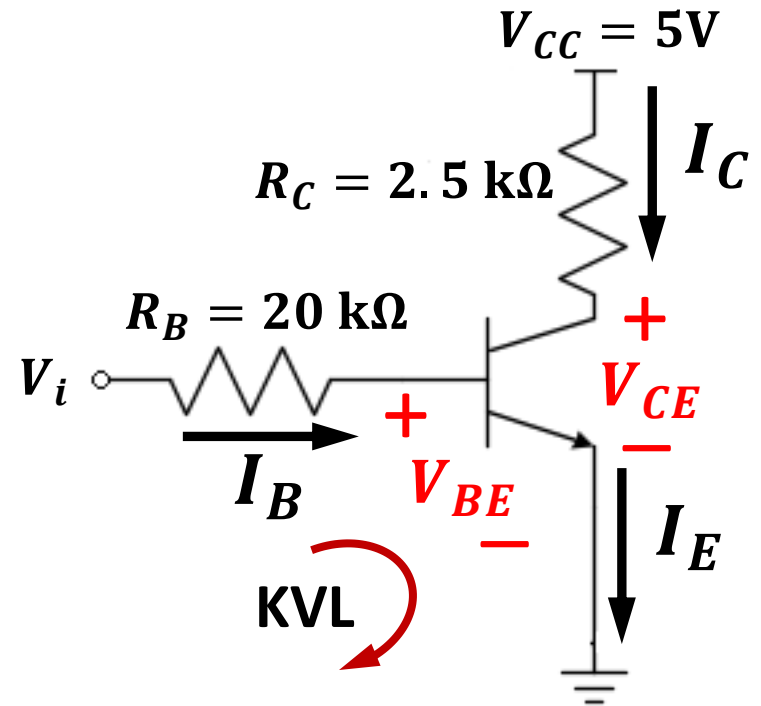
$$\text{KVL} \quad 5 + (-I_C(\text{sat}) \times 2.5\text{k}\Omega) - V_{CE}(\text{sat}) = 0$$



$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$

BJT is ON since $V_i > V_{BE}(\text{on})$


Let's find the collector current at onset of saturation

$$I_B = 0.14\text{mA}$$

$$I_C = \beta I_B = 28\text{mA}$$

KVL $5 + (-I_C(\text{sat}) \times 2.5\text{k}\Omega) - V_{CE}(\text{sat}) = 0$
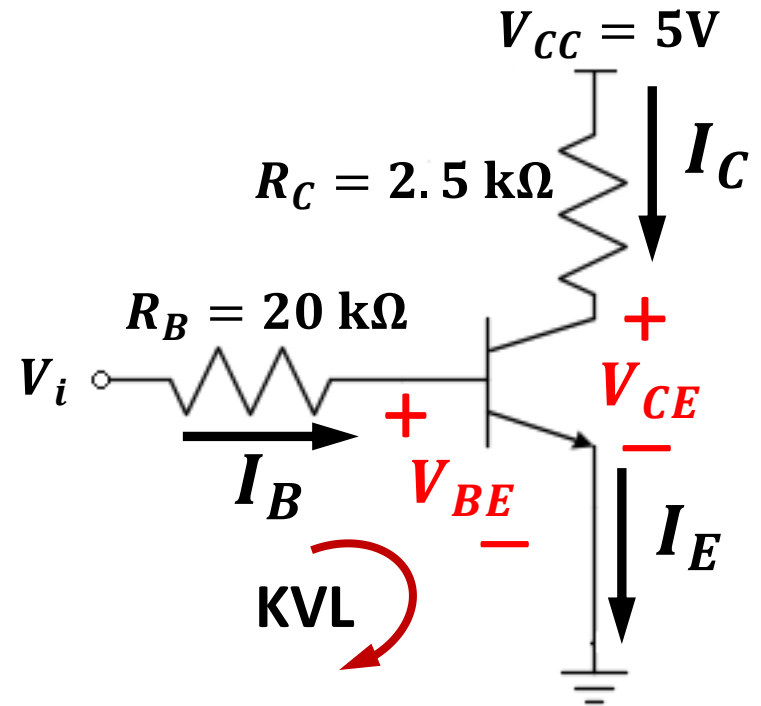
$$I_C(\text{sat}) = 4.8\text{V}/2.5\text{k}\Omega = 1.92\text{mA} \ll \beta I_B$$



$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$

BJT is ON since $V_i > V_{BE}(\text{on})$

Let's find the collector current at onset of saturation

$$I_B = 0.14\text{mA}$$


$$I_C = \beta I_B = 28\text{mA}$$

KVL $5 + (-I_C(\text{sat}) \times 2.5\text{k}\Omega) - V_{CE}(\text{sat}) = 0$

$$I_C(\text{sat}) = 4.8\text{V}/2.5\text{k}\Omega = 1.92\text{mA} \ll \beta I_B$$

$$V_{CE} = V_{CE}(\text{sat}) = 0.2\text{V}$$

Saturation mode

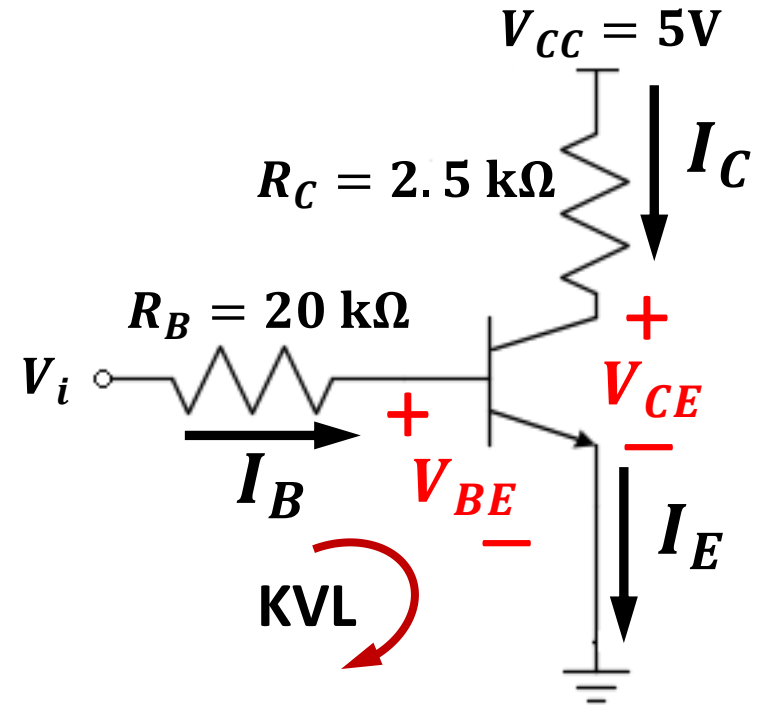

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$


$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$

Let's find the base current at onset of saturation

$$I_B(\text{at onset of saturation}) = \frac{I_C(\text{sat})}{\beta} = 9.6 \mu\text{A}$$
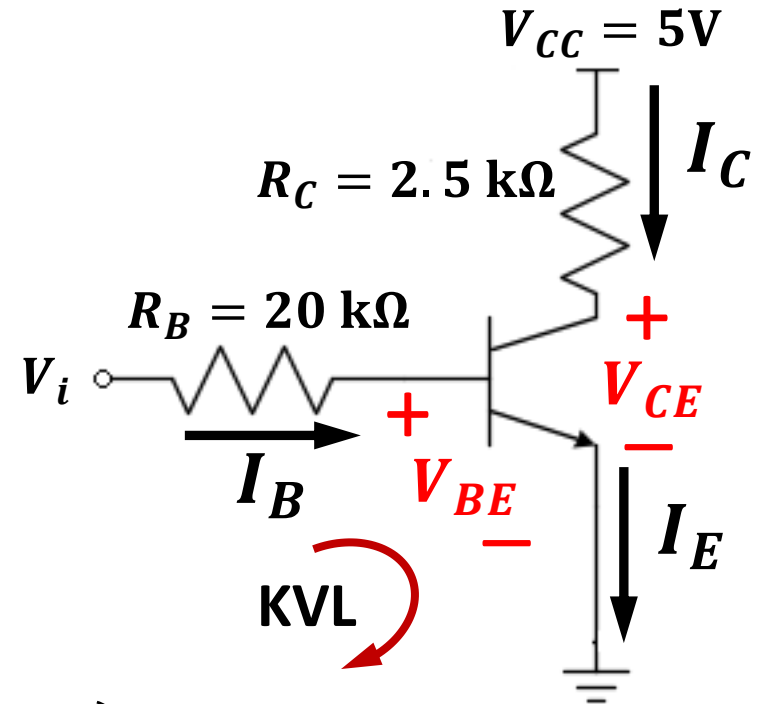
$$V_i(\text{at onset of saturation}) = 9.6 \mu\text{A} \times 20\text{k}\Omega + 0.7 = 0.892\text{V}$$



The base current can be increased further, but the collector current remains at the saturation value $I_C(\text{sat})$.

Example 3: BJT with emitter resistor

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$


$$\beta = 100$$

$$I_E = (\beta + 1)I_B$$

Assume forward active mode

Base-emitter KVL

$$-V_i + I_B R_B + V_{BE} + I_E R_E = 0$$

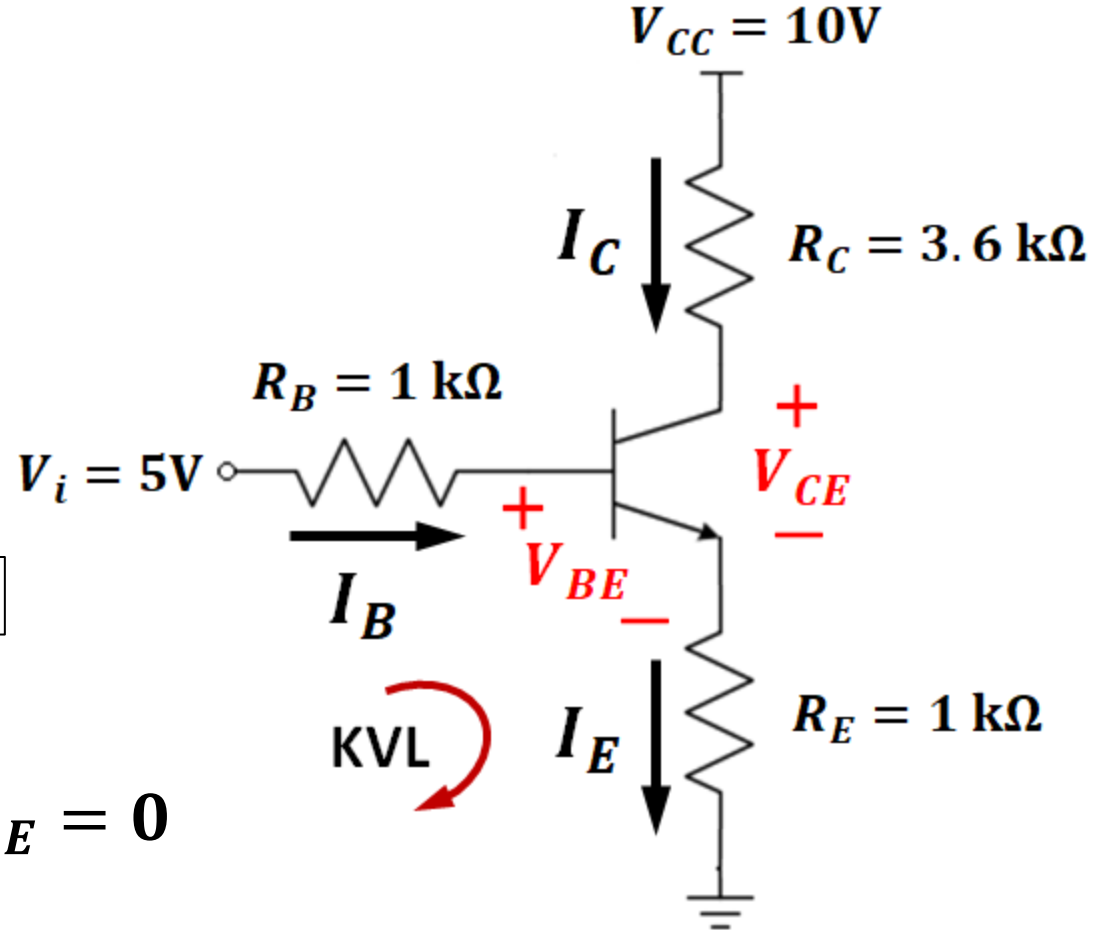

Example 3: BJT with emitter resistor

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 100$$

$$I_E = (\beta + 1)I_B$$


Assume forward active mode

Base-emitter KVL

$$-V_i + I_B R_B + V_{BE} + I_E R_E = 0$$

$$-5 + I_B \times 1\text{k} + 0.7 + (\beta + 1)I_B \times 1\text{k} = 0$$

$$I_B = \frac{4.3}{1\text{k} + (\beta + 1)1\text{k}} = \frac{4.3}{102\text{k}} = 0.0422\text{mA} = 42.2\mu\text{A}$$

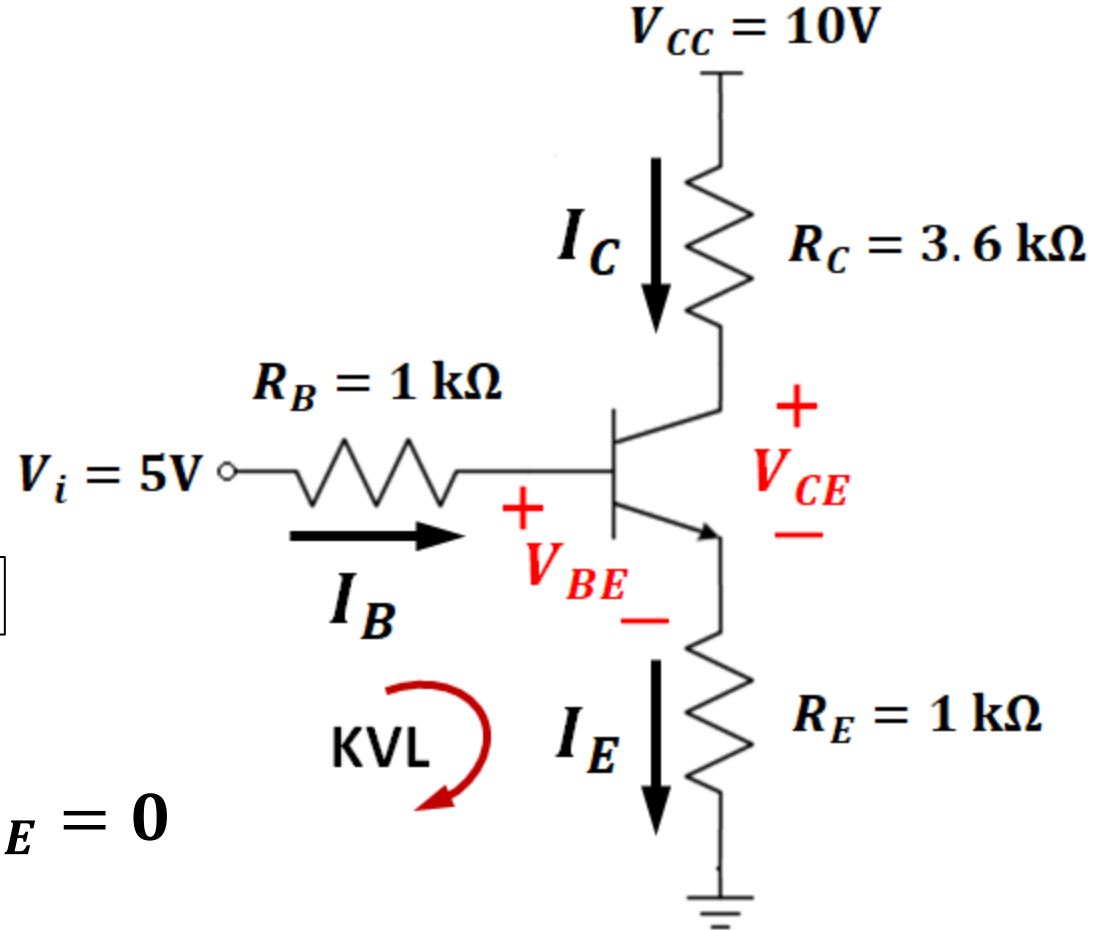


Example 3: BJT with emitter resistor

$$I_B = 0.0422\text{mA}$$

$$I_E = (\beta + 1)I_B = 4.26\text{mA}$$

$$I_C = \beta I_B = 4.22\text{mA}$$

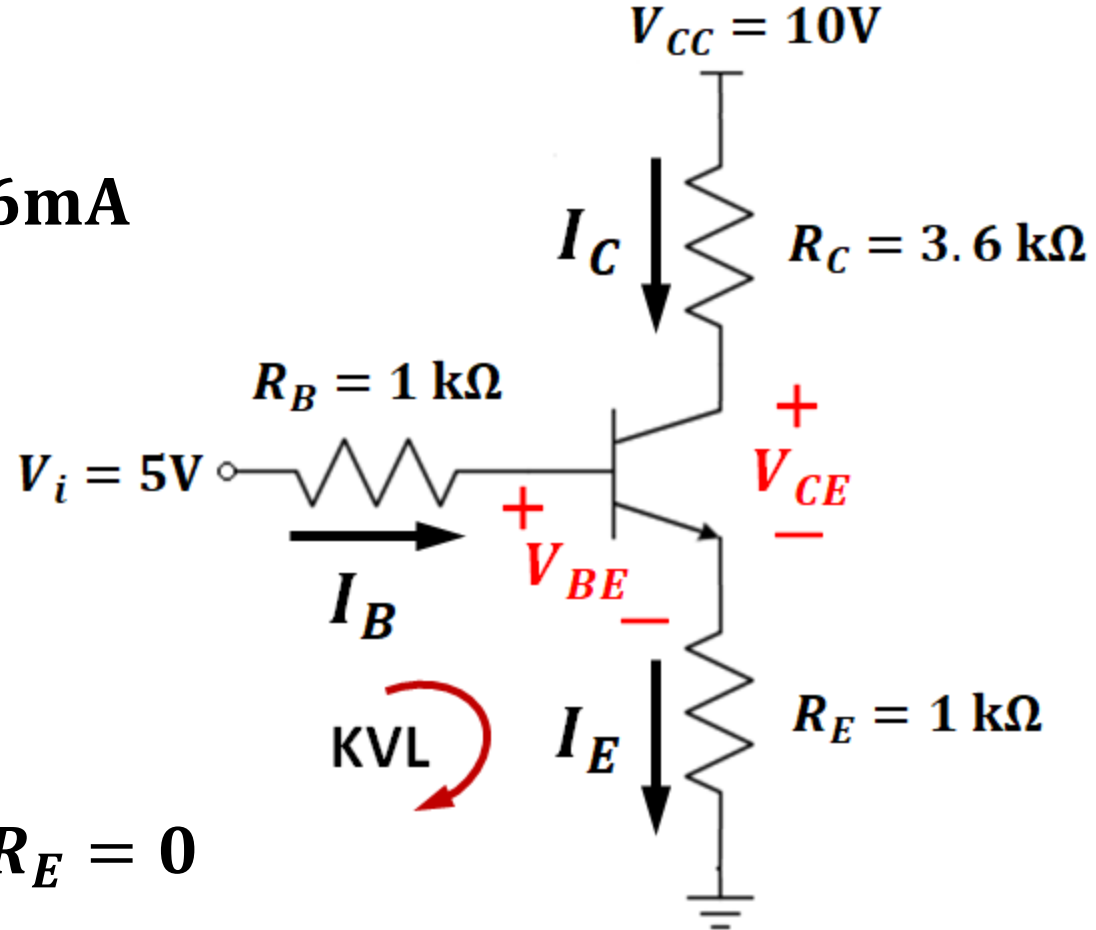

Now, check for saturation

Collector-emitter KVL


$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

Example 3: BJT with emitter resistor

$$I_B = 0.0422\text{mA}$$

$$I_E = (\beta + 1)I_B = 4.26\text{mA}$$

$$I_C = \beta I_B = 4.22\text{mA}$$

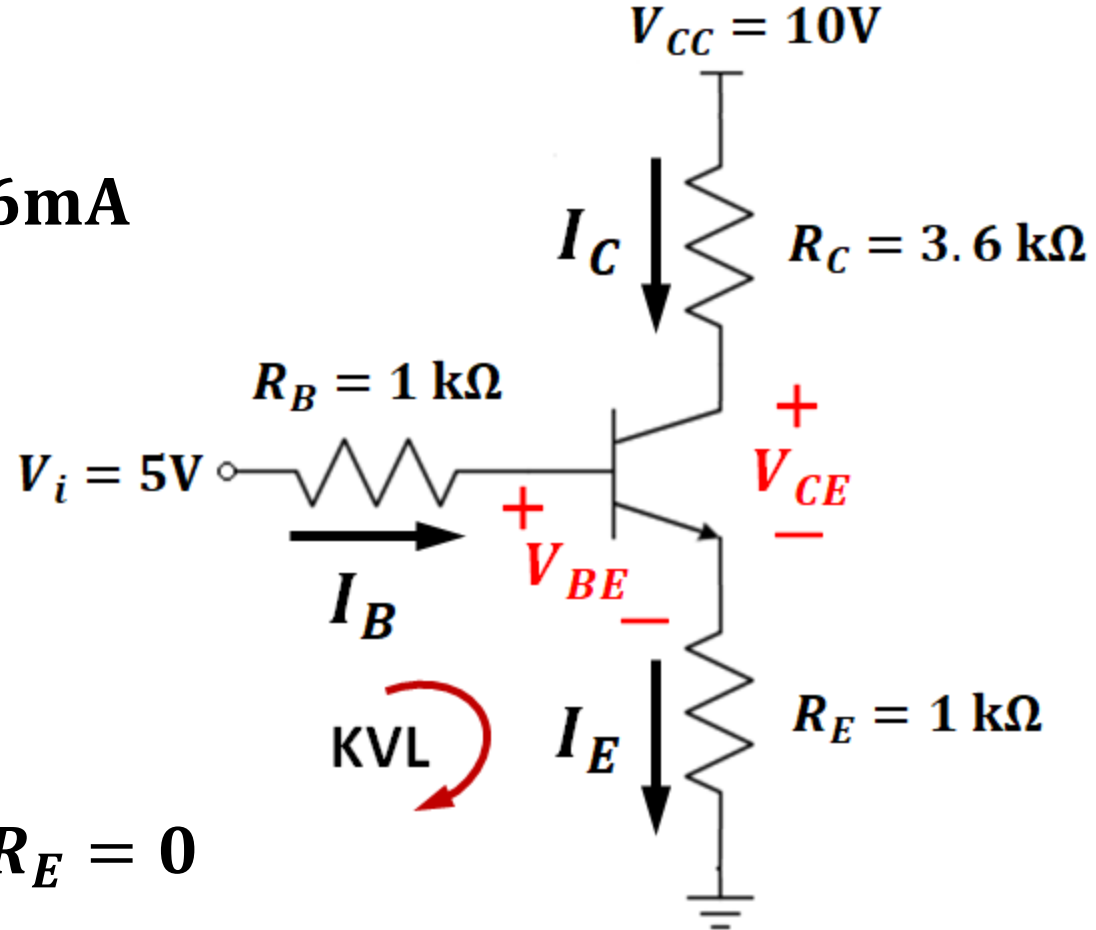

Now, check for saturation

Collector-emitter KVL

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$-10 + 4.22\text{m} \times 3.6\text{k} + V_{CE} + 4.26 \times 1\text{k} = 0$$


$$V_{CE} = 10 - 15.192 - 4.26 = -9.452\text{ V} \ll V_{CE}(\text{sat})$$

Example 3: BJT with emitter resistor

$$I_B = 0.0422\text{mA}$$

$$I_E = (\beta + 1)I_B = 4.26\text{mA}$$

$$I_C = \beta I_B = 4.22\text{mA}$$

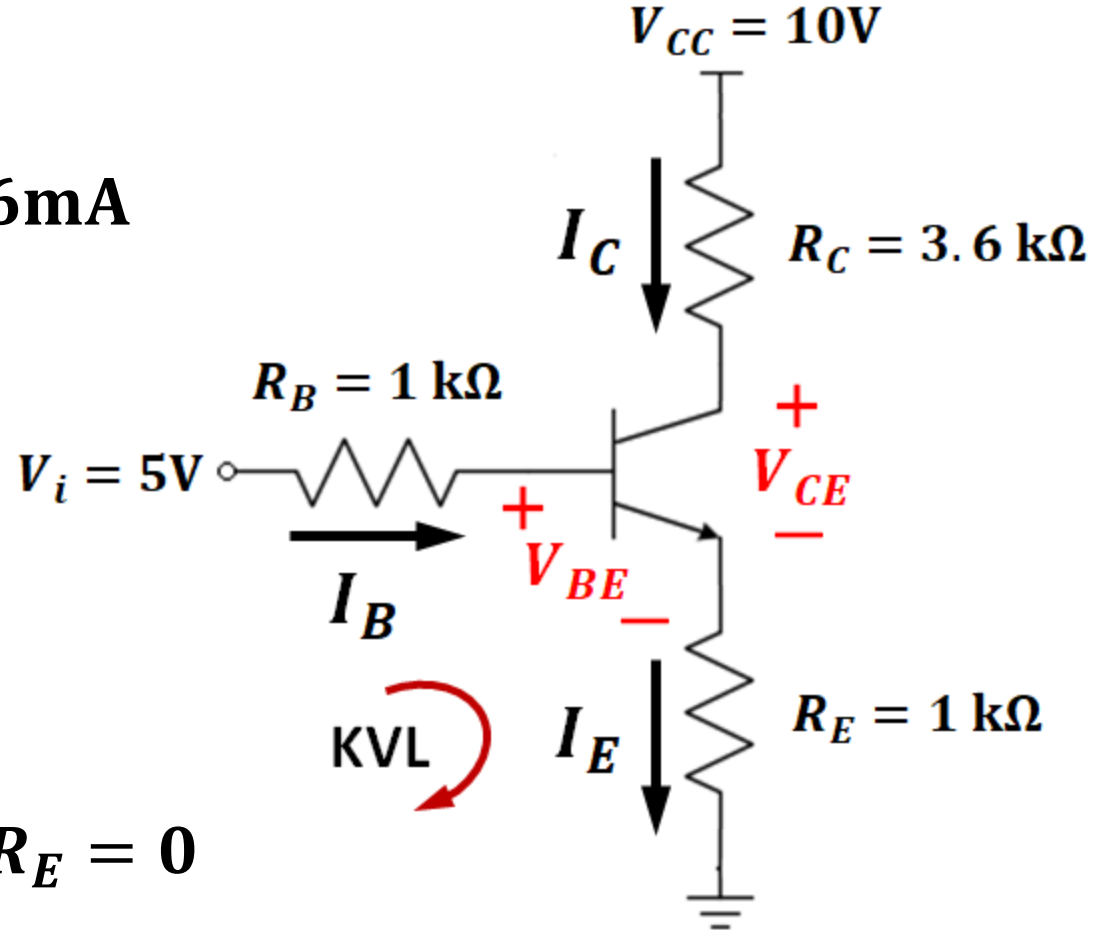

Now, check for saturation

Collector-emitter KVL

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$-10 + 4.22\text{m} \times 3.6\text{k} + V_{CE} + 4.26 \times 1\text{k} = 0$$

$$V_{CE} = 10 - 15.192 - 4.26 = -9.452\text{V} \ll V_{CE}(\text{sat})$$

Assumption is invalid.



$$V_{CE} = V_{CE}(\text{sat}) = 0.2\text{V}$$

Previous results for currents are invalid


⇒ $V_{CE} = V_{CE}(\text{sat}) = 0.2 \text{ V}$

Remember

$$I_E = \frac{\beta + 1}{\beta} I_C = 1.01 I_C$$

(valid up to onset of saturation)

$V_i = ?$

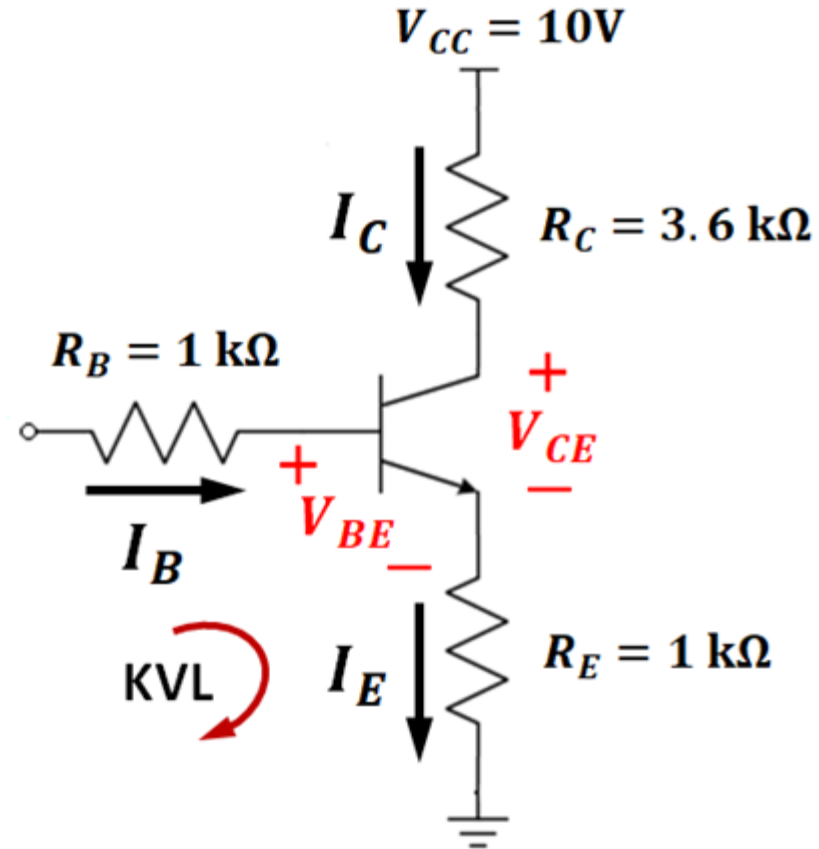

Previous results for currents are invalid

$$V_{CE} = V_{CE}(\text{sat}) = 0.2 \text{ V}$$

Remember


$$I_E = \frac{\beta + 1}{\beta} I_C = 1.01 I_C$$

(valid up to onset of saturation)

Recalculate collector-emitter KVL

$$-V_{CC} + I_C(\text{onsat})R_C + V_{CE}(\text{onsat}) + I_ER_E = 0$$
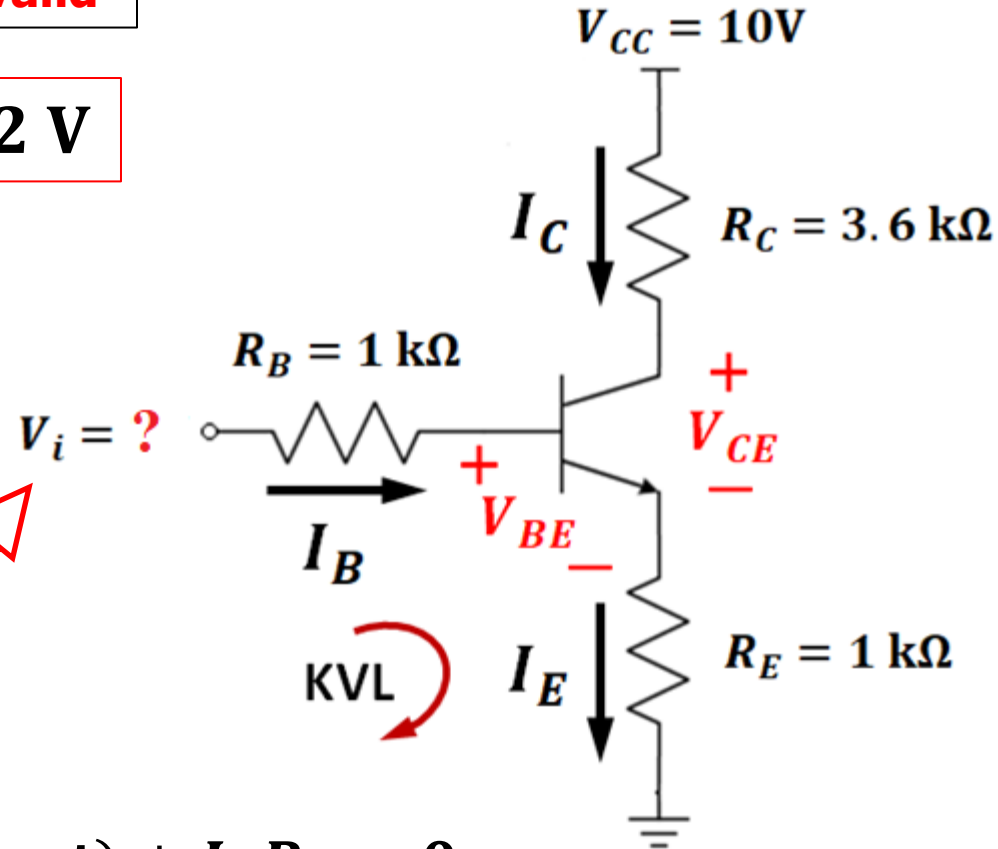
$$-10 + I_C(\text{onsat}) \times 3.6\text{k} + 0.2 + 1.01 \times I_C(\text{onsat}) \times 1\text{k} = 0$$



Previous results for currents are invalid

$$V_{CE} = V_{CE}(\text{sat}) = 0.2 \text{ V}$$

Remember

$$I_E = \frac{\beta + 1}{\beta} I_C = 1.01 I_C$$

(valid up to onset of saturation)

Recalculate collector-emitter KVL


$$-V_{CC} + I_C(\text{onsat})R_C + V_{CE}(\text{onsat}) + I_ER_E = 0$$

$$-10 + I_C(\text{onsat}) \times 3.6\text{k} + 0.2 + 1.01 \times I_C(\text{onsat}) \times 1\text{k} = 0$$

$$I_C(\text{onsat}) = 9.8 / 4.61\text{k} = 2.13 \text{ mA}$$

$$I_E(\text{onsat}) = 1.01 I_C = 2.15 \text{ mA}$$

At onset of saturation

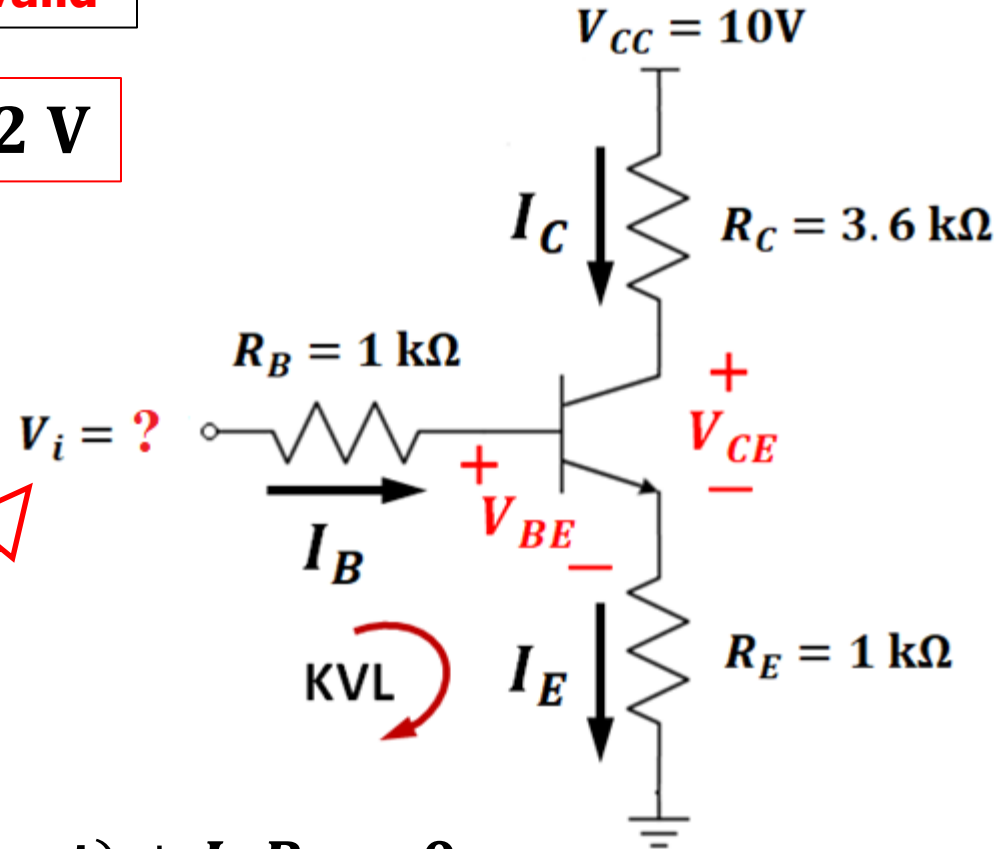


ATTENTION – Relevant for HW10-PL

$$I_E = \frac{\beta + 1}{\beta} I_C$$

is valid **ONLY** up to the point of saturation onset

Deeper in saturation one must keep using

$$I_E = I_B + I_C$$

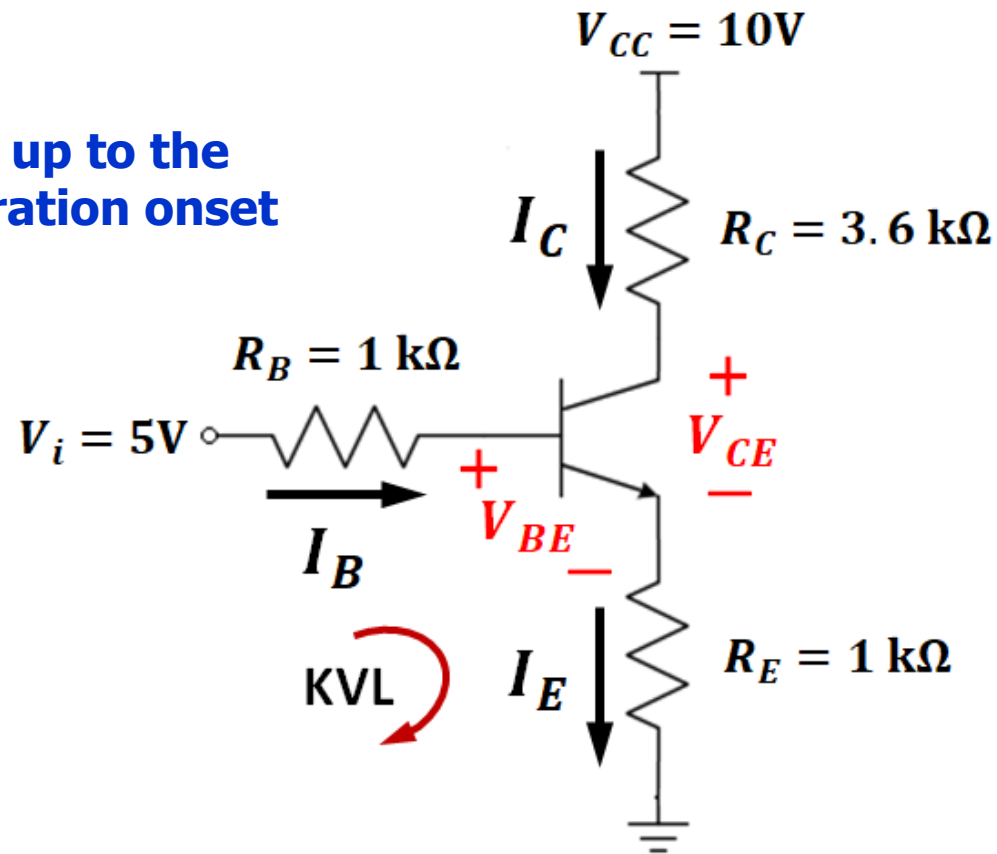

AGAIN: The derivations in the previous slide **ARE NOT VALID** in deeper saturation but only at the **onset point** where the device transitions from Forward-Active mode to Saturation mode

When the base current is increased beyond onset, the voltage drop in the emitter resistor changes, since


$$I_E = I_B + I_C$$

If we assume that the saturation $V_{CE}(\text{sat})$ remains at the value specified by the manufacturer throughout, in saturation

$$V_{CC} - V_{CE}(\text{sat}) = R_C I_C + R_E I_E$$

This equation has to be solved simultaneously with the base circuit KVL

$$V_i - V_{BE} = R_B I_B + R_E I_E$$

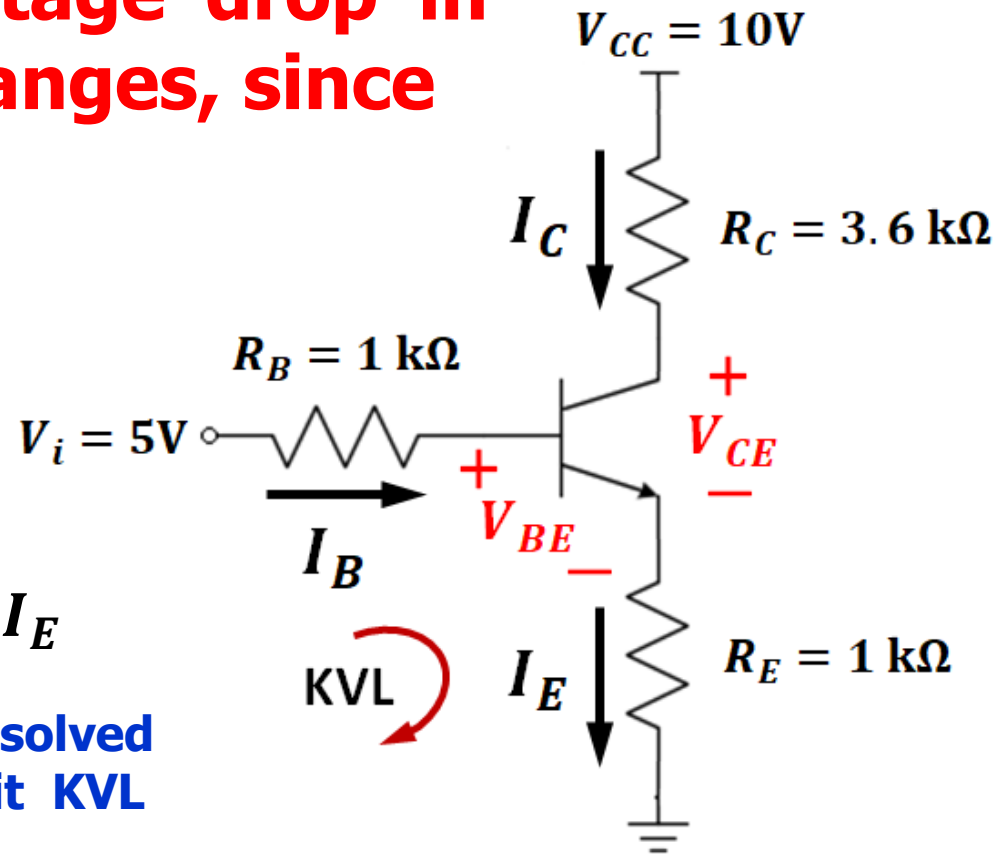


Recalculated currents

$$I_C(\text{onsat}) = 9.8 / 4.61\text{k} = 2.13 \text{ mA}$$

$$I_E(\text{onsat}) = 1.01 I_C = 2.15 \text{ mA}$$

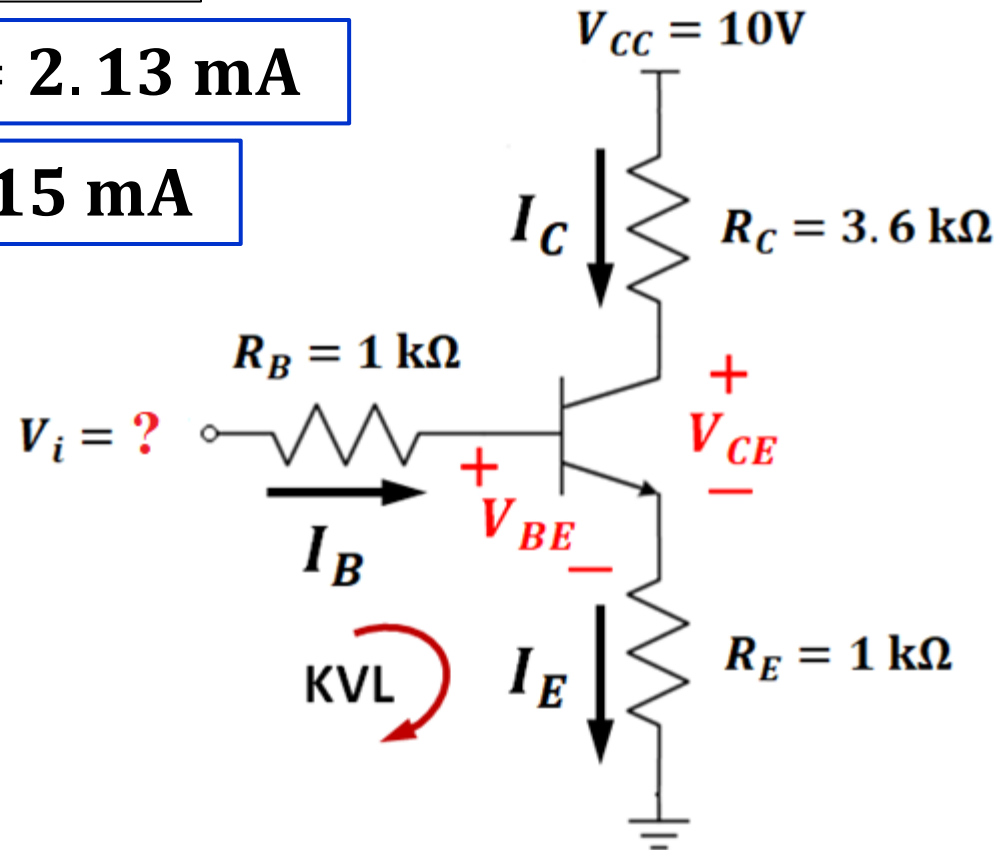Find base voltage at **onset** of saturation



Recalculated currents


$$I_C(\text{onsat}) = 9.8 / 4.61\text{k} = 2.13 \text{ mA}$$

$$I_E(\text{onsat}) = 1.01 I_C = 2.15 \text{ mA}$$

Find base voltage at **onset** of saturation


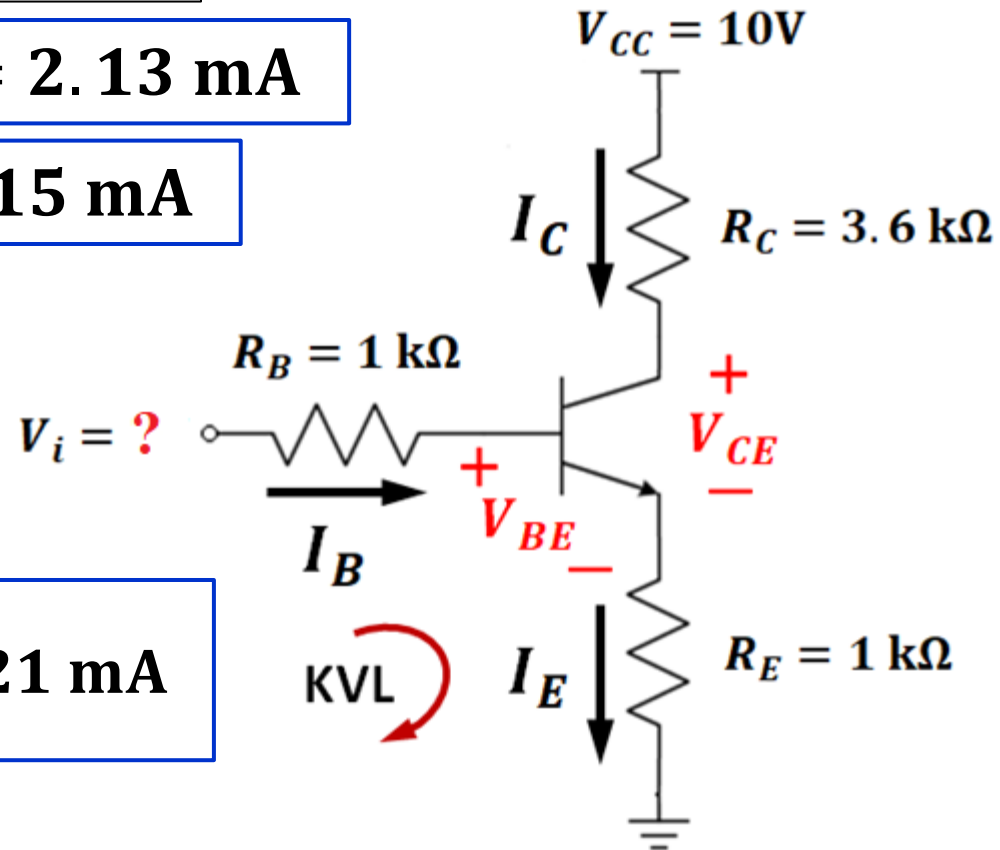
$$I_B(\text{onsat}) = \frac{I_C(\text{onsat})}{\beta} = 0.021 \text{ mA}$$



Recalculated currents

$$I_C(\text{onsat}) = 9.8 / 4.61\text{k} = 2.13 \text{ mA}$$

$$I_E(\text{onsat}) = 1.01 I_C = 2.15 \text{ mA}$$

Find base voltage at **onset** of saturation




$$I_B(\text{onsat}) = \frac{I_C(\text{onsat})}{\beta} = 0.021 \text{ mA}$$

Base circuit KVL

$$-V_i(\text{onsat}) + I_B(\text{onsat})R_B + V_{BE} + I_E(\text{onsat})R_E = 0$$
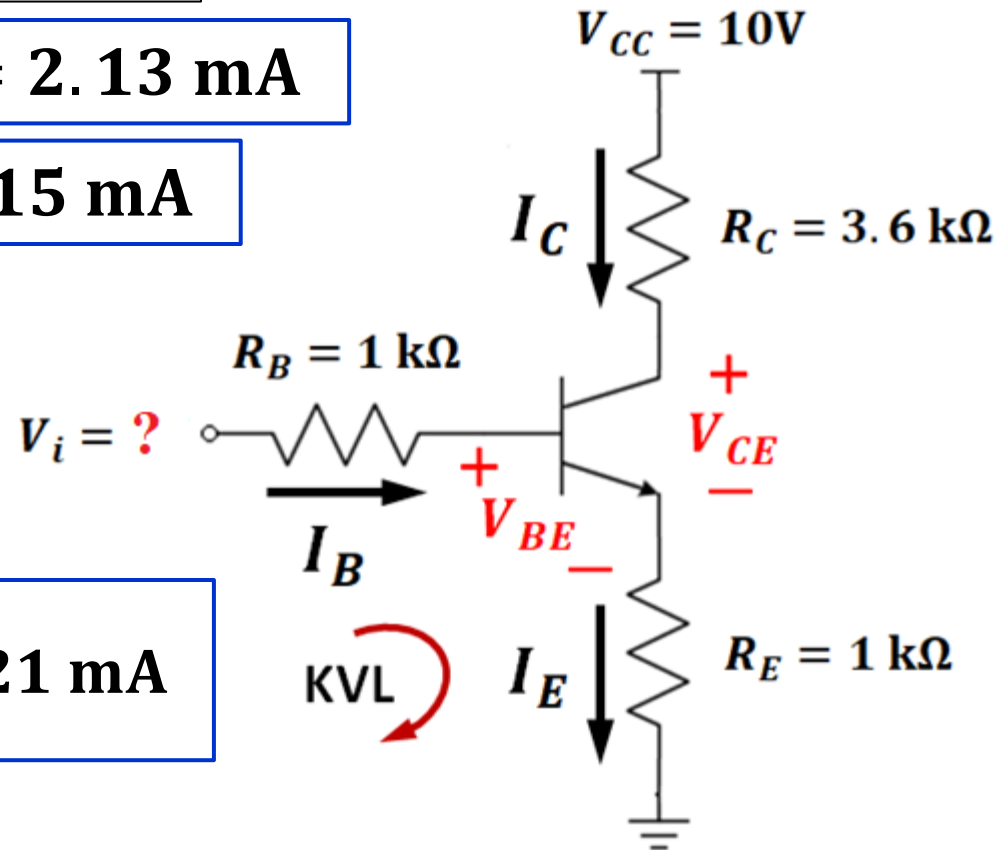
$$V_i(\text{onsat}) = 0.021\text{m} \times 1\text{k} + 0.7 + 2.15\text{m} \times 1\text{k}$$



Recalculated currents

$$I_C(\text{onsat}) = 9.8 / 4.61\text{k} = 2.13 \text{ mA}$$

$$I_E(\text{onsat}) = 1.01 I_C = 2.15 \text{ mA}$$

Find base voltage at **onset** of saturation



$$I_B(\text{onsat}) = \frac{I_C(\text{onsat})}{\beta} = 0.021 \text{ mA}$$


Base circuit KVL

$$-V_i(\text{onsat}) + I_B(\text{onsat})R_B + V_{BE} + I_E(\text{onsat})R_E = 0$$

$$V_i(\text{onsat}) = 0.021\text{m} \times 1\text{k} + 0.7 + 2.15\text{m} \times 1\text{k}$$

$$V_i(\text{onsat}) = 2.87 \text{ V}$$

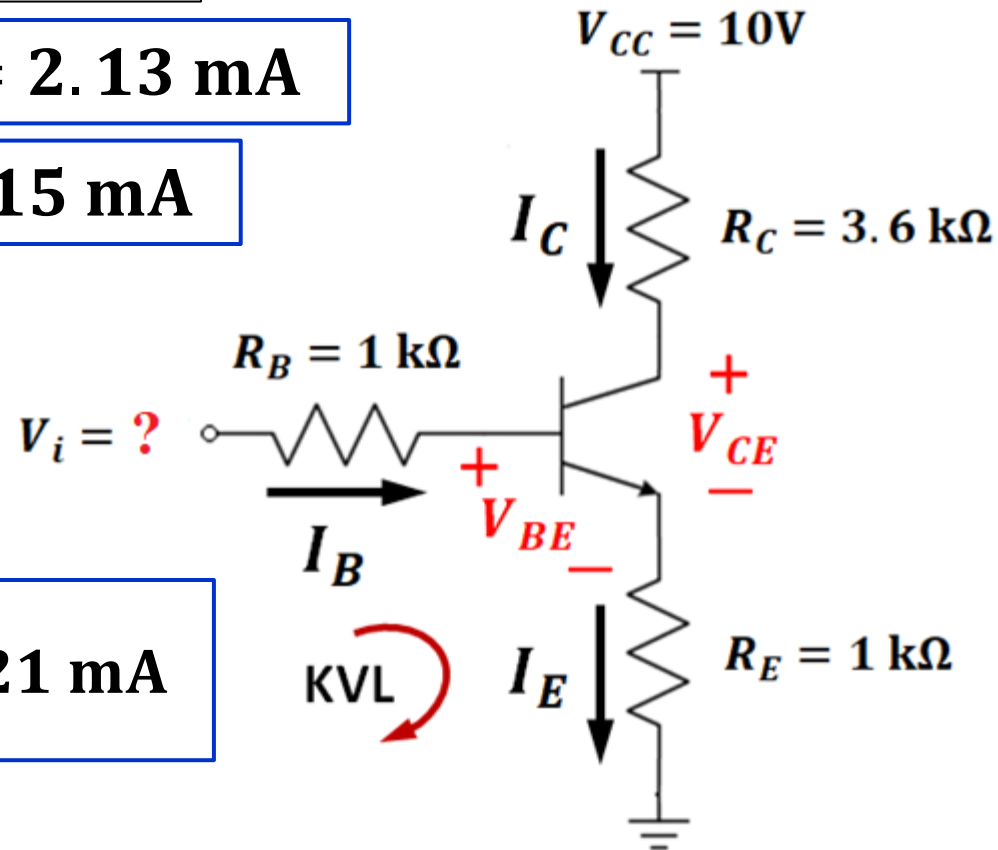At this input voltage on the base resistor, the BJT starts saturating



Resistor on emitter changes the saturation behavior

$$V_{BE}(\text{on}) \leq V_B < V_i(\text{onsat}) = 2.87 \text{ V}$$


Forward-Active mode

$$V_B = V_i(\text{onsat}) = 2.87 \text{ V}$$


Onset of saturation
(FA mode equations are still valid)

$$V_B > V_i(\text{onsat}) = 2.87 \text{ V}$$

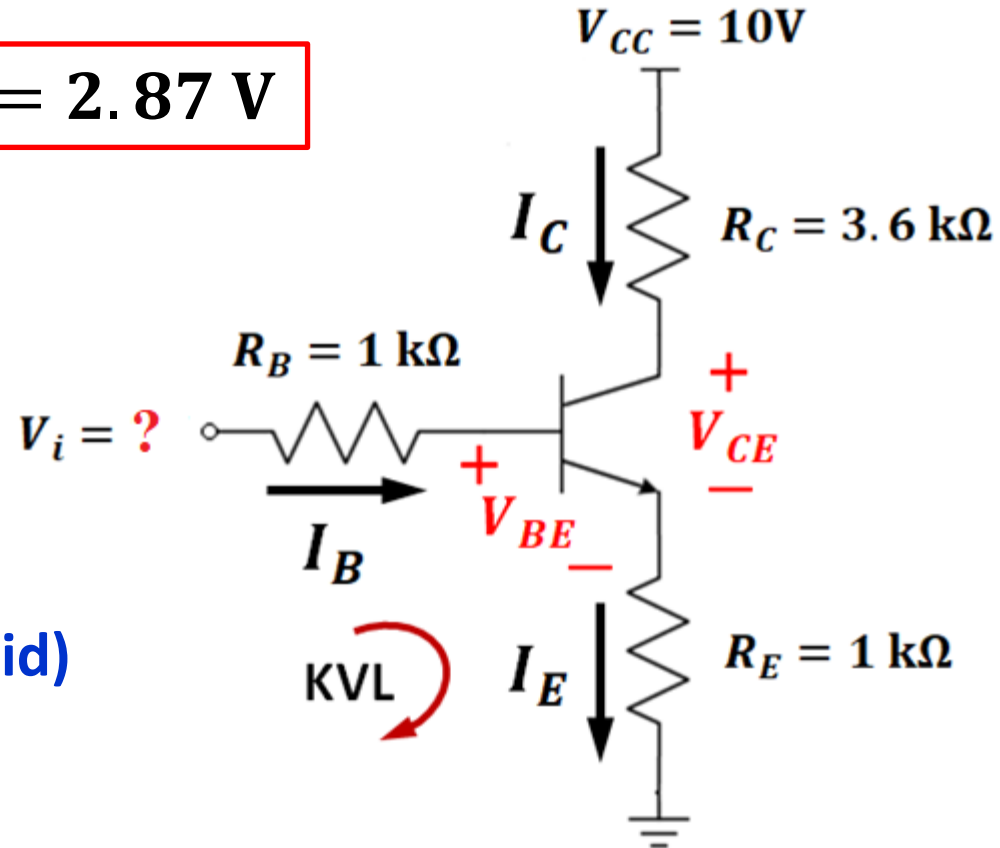“Deeper” saturation
(FA mode equations are NOT valid)



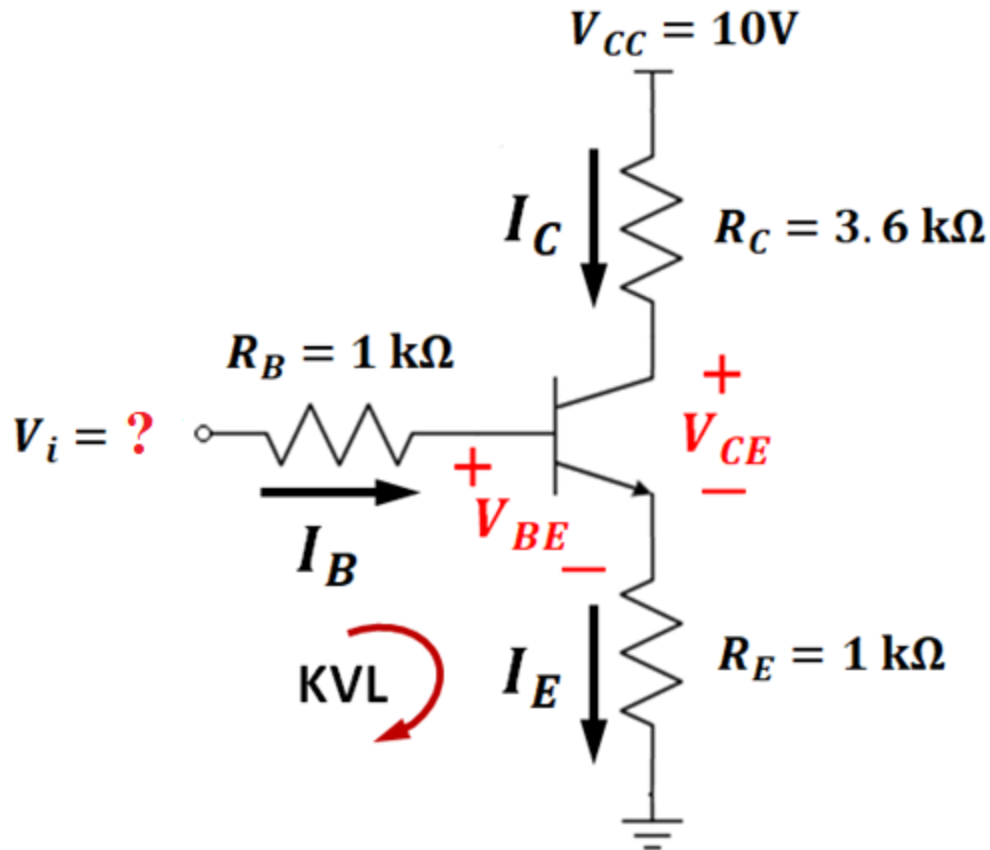In deeper saturation, collector current decreases somewhat



$$V_{CC} = 10 \text{ V}$$

$$I_C R_C$$

assume constant

$$V_{CE} = V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$I_E R_E = (I_B + I_C) R_E$$


I_B keeps increasing in deeper saturation

$$V_B > V_i(\text{onsat}) = 2.87 \text{ V}$$

$$I_C < I_C(\text{onsat}) = 2.13 \text{ mA}$$

MUST SOLVE FOR COUPLED KVL'S IN BASE AND COLLECTOR LOOPS

$$V_i = 5\text{ V}$$

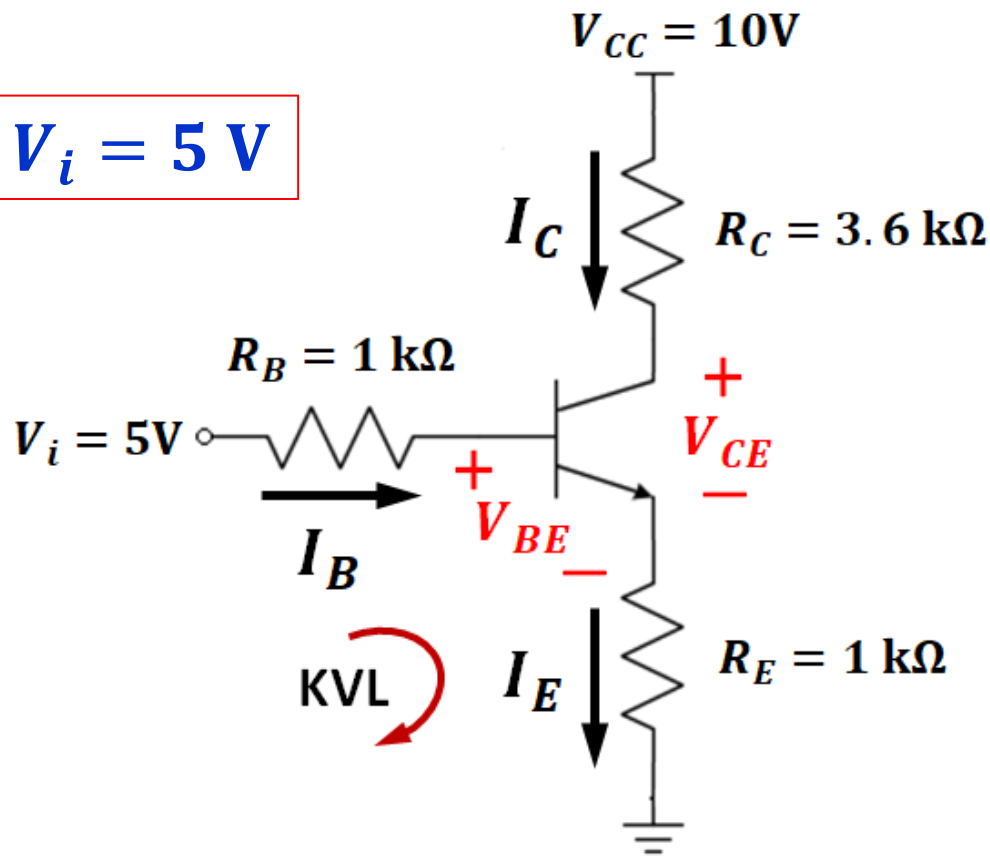

$$V_{CC} = 10\text{ V}$$

$$I_C R_C$$

assume constant


$$V_{CE} = V_{CE}(\text{sat}) = 0.2\text{ V}$$

$$I_E R_E = (I_B + I_C) R_E$$

$$V_i = I_B R_B + V_{BE}(\text{on}) + I_E R_E$$

$$V_{CC} = I_C R_C + V_{CE}(\text{sat}) + I_E R_E$$

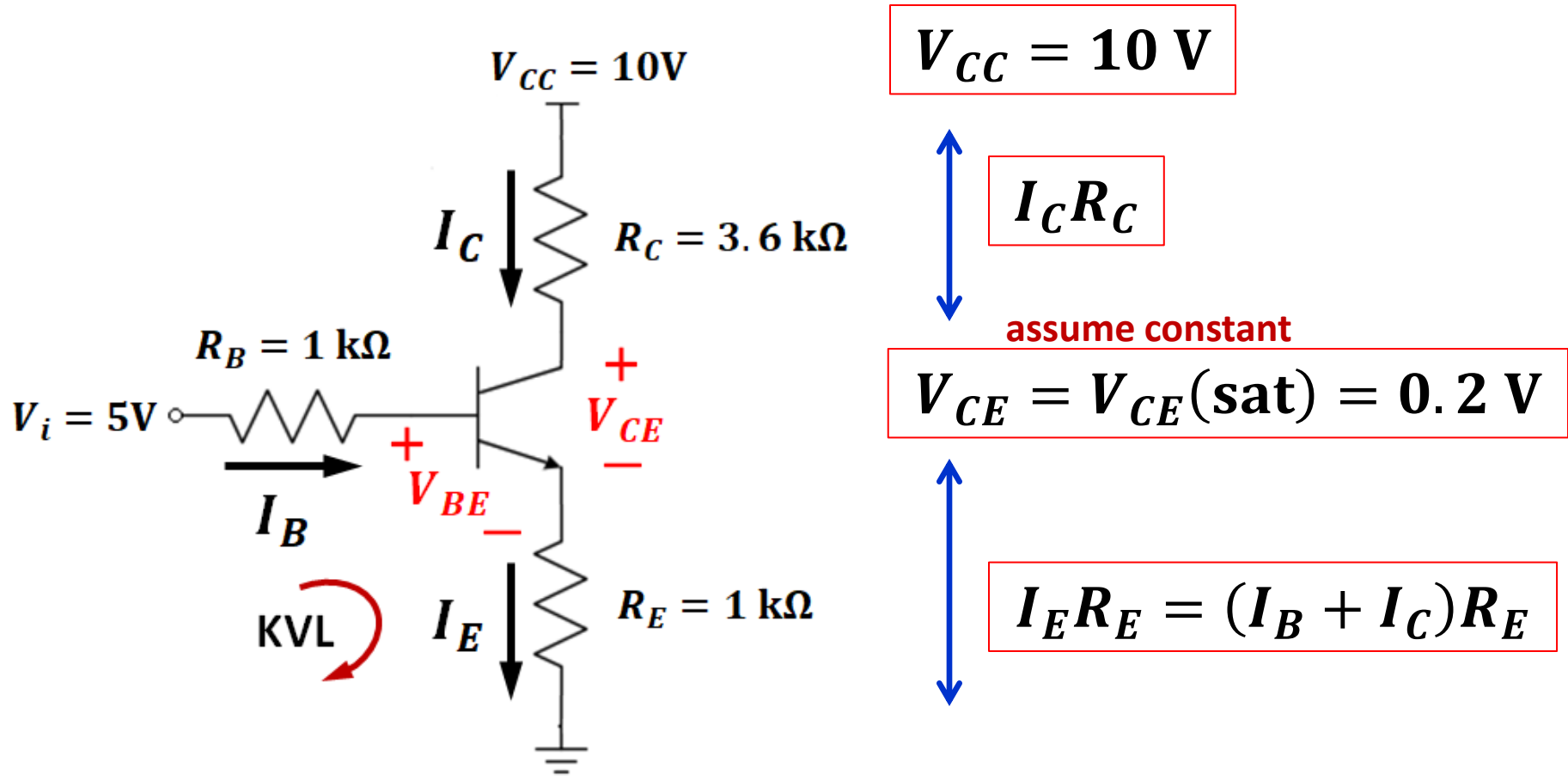
MUST SOLVE FOR COUPLED KVL'S IN BASE AND COLLECTOR LOOPS



$$5 = 1\text{k} I_B + 0.7 + (I_B + I_C)1\text{k}$$

$$10 = 3.6\text{k} I_C + 0.2 + (I_B + I_C)1\text{k}$$

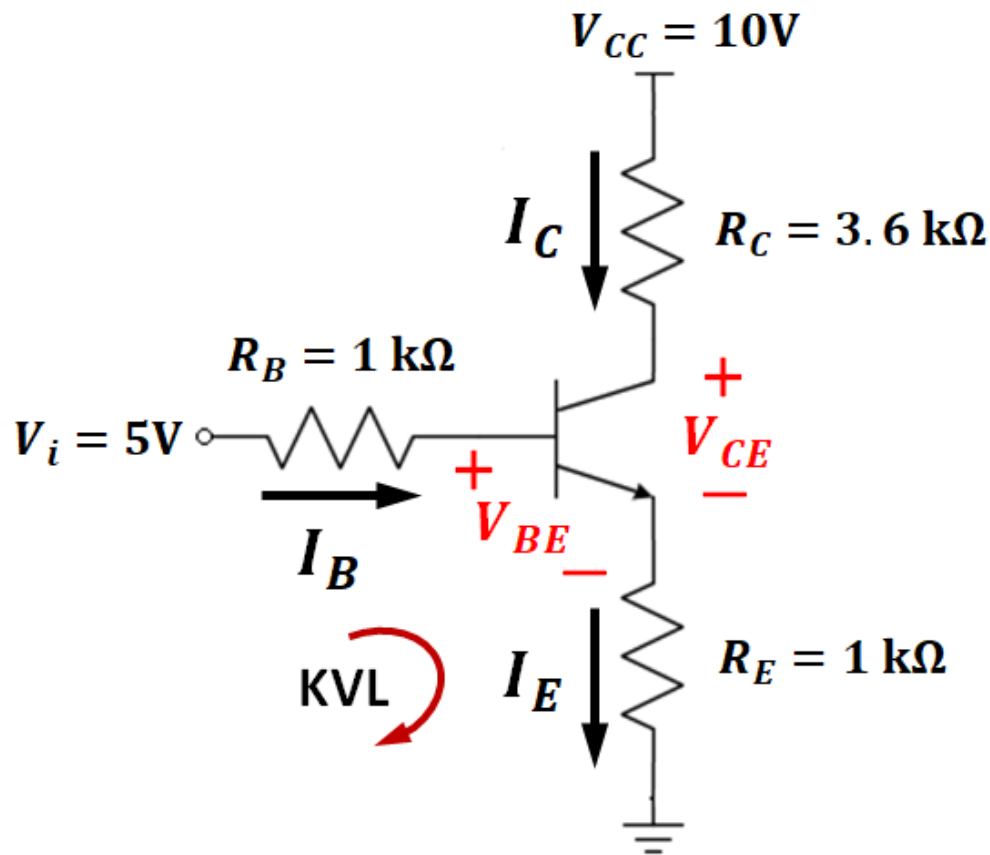MUST SOLVE FOR COUPLED KVL'S IN BASE AND COLLECTOR LOOPS



$$V_{CC} = 10\text{ V}$$

$$I_C R_C = 6.717\text{ V}$$

assume constant

$$V_{CE} = V_{CE}(\text{sat}) = 0.2\text{ V}$$

$$I_E R_E = (I_B + I_C) R_E = 3.083\text{ V}$$

$$2\text{k } I_B + 1\text{k } I_C = 4.3$$

$$1\text{k } I_B + 4.6\text{k } I_C = 9.8$$

$$I_B = 1.217\text{ mA}$$

$$I_C = 1.866\text{ mA} < I_C(\text{onsat})$$

$$I_C(\text{onsat}) = 2.13\text{ mA}$$