

ECE 205 “Electrical and Electronics Circuits”

Spring 2024 – LECTURE 26

MWF – 12:00pm

Prof. Umberto Ravaioli

2062 ECE Building

Lecture 26 – Summary

Learning Objectives

1. More BJT practice
2. Transistor as diode
3. Graphical use of I - V curves

Example 2: Find the BJT mode of operation


$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(a) V_i = 0.5\text{V}$$

$$(b) V_i = 3.5\text{V}$$

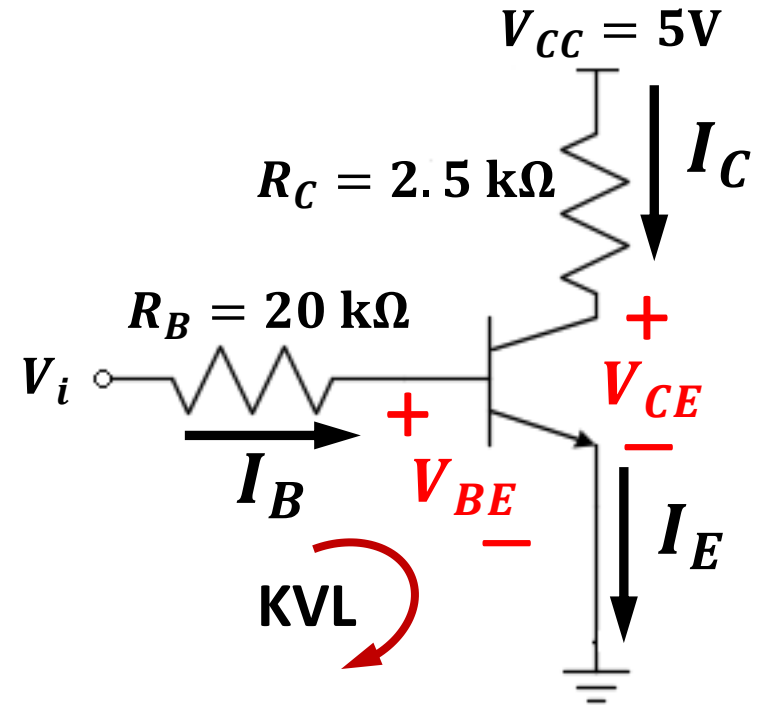

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$


$$\beta = 200$$

$$(a) V_i = 0.5\text{V}$$

BJT is OFF since

$$V_i < V_{BE}(\text{on})$$

Cut-off mode

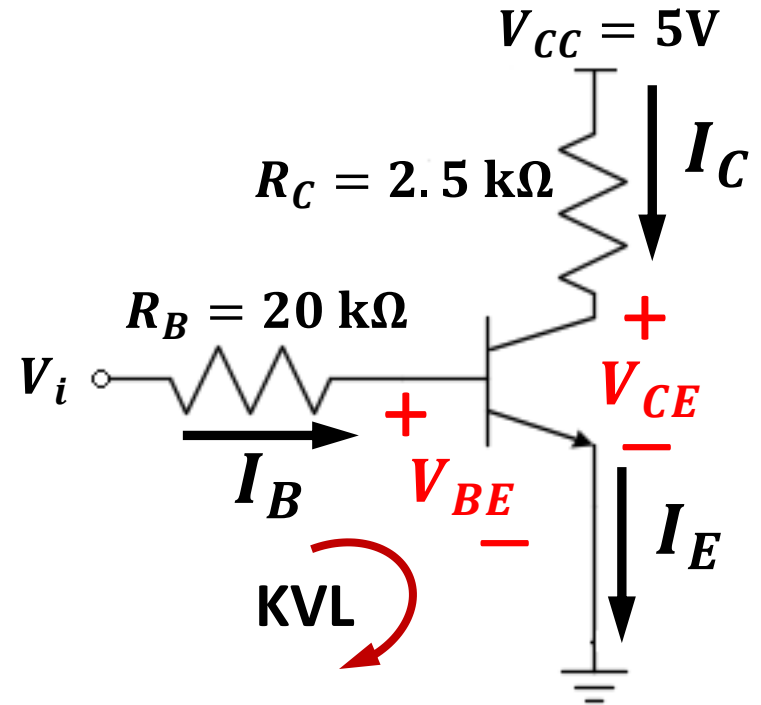

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$


$$(b) V_i = 3.5\text{V}$$

BJT is ON since $V_i > V_{BE}(\text{on})$

Assume forward active mode and check the collector behavior

$$\text{KVL} \quad -3.5 + I_B \times 20\text{k}\Omega + 0.7 = 0$$
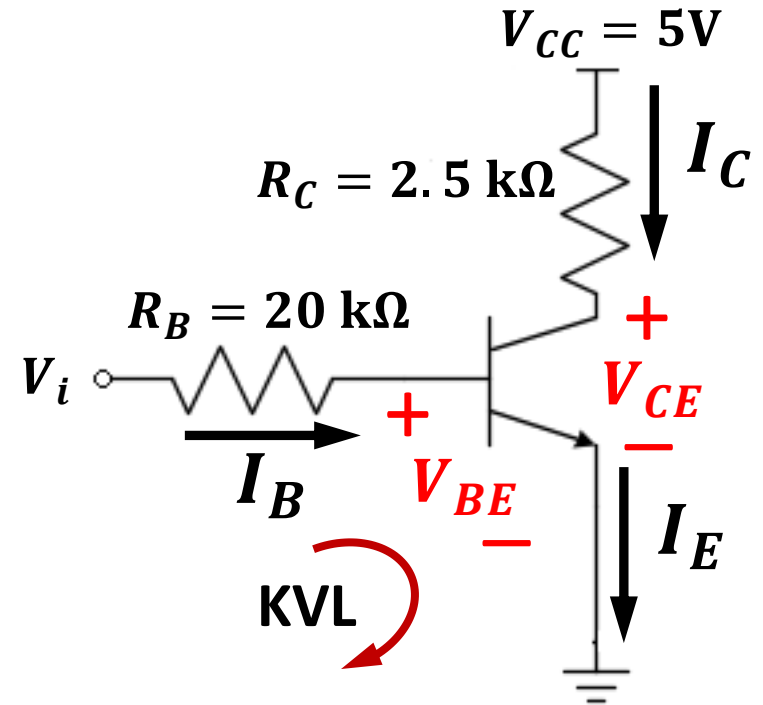
$$I_C = \beta I_B = 200 \times 0.14 = 28\text{mA}$$



$$I_B = 0.14\text{mA}$$

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$


BJT is ON since $V_i > V_{BE}(\text{on})$

Assume forward active mode and check the collector behavior

$$\text{KVL} \quad -3.5 + I_B \times 20\text{k}\Omega + 0.7 = 0$$

$$I_C = \beta I_B = 200 \times 0.14 = 28\text{mA}$$
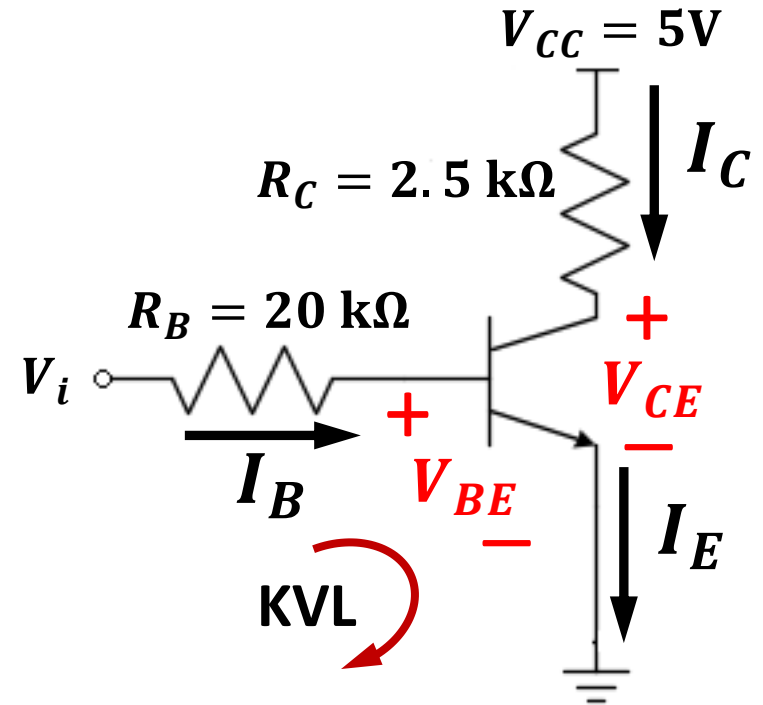
$$V_{CE} = V_{CC} - I_C R_C = 5 - 28\text{m} \times 2.5\text{k} = -65\text{V} < 0.2\text{V}$$



$$I_B = 0.14\text{mA}$$

Contradiction

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$

BJT is ON since $V_i > V_{BE}(\text{on})$


Assume forward active mode and check the collector behavior

$$\text{KVL} \quad -3.5 + I_B \times 20\text{k}\Omega + 0.7 = 0$$

$$I_C = \beta I_B = 200 \times 0.14 = 28\text{mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 5 - 28\text{m} \times 2.5\text{k} = -65\text{V} < 0.2\text{V}$$
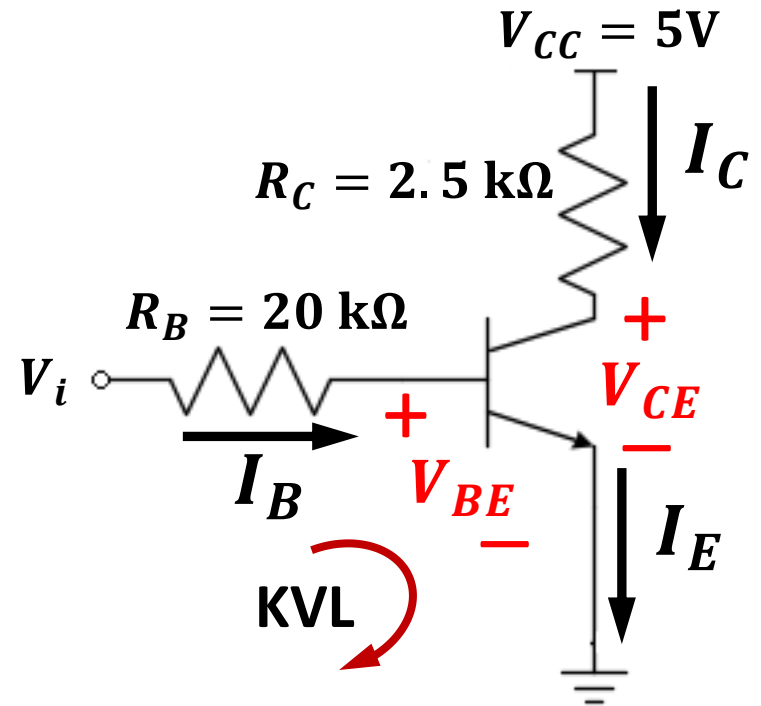
$$V_{CE} = V_{CE}(\text{sat}) = 0.2\text{V} \quad \text{Saturation mode}$$



$$I_B = 0.14\text{mA}$$

Contradiction

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$


BJT is ON since $V_i > V_{BE}(\text{on})$

Let's find the collector current at onset of saturation

$$I_B = 0.14\text{mA}$$

$$I_C = \beta I_B = 28\text{mA}$$

Under Forward-Active assumption we had

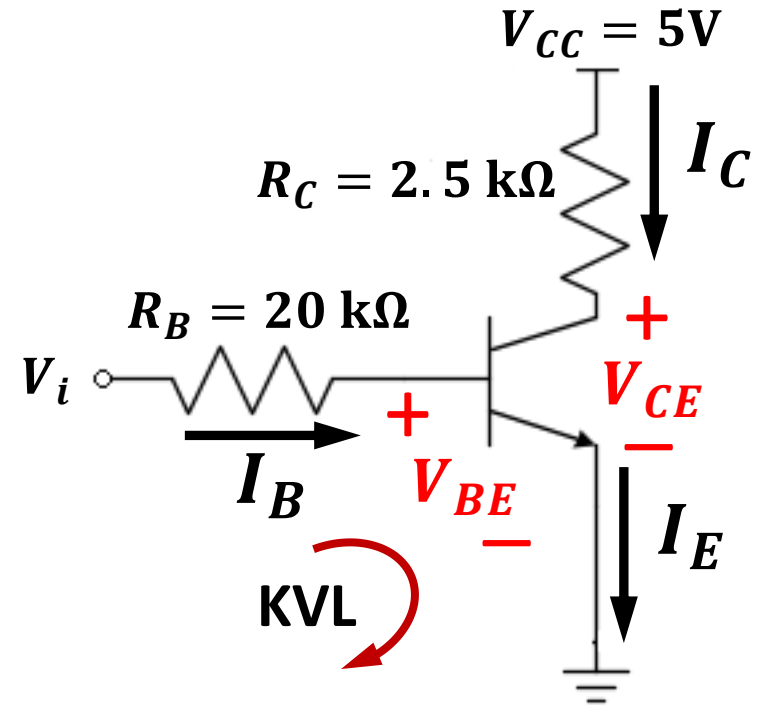

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$

BJT is ON since $V_i > V_{BE}(\text{on})$


Let's find the collector current at onset of saturation

$$I_B = 0.14\text{mA}$$

$$I_C = \beta I_B = 28\text{mA}$$

Under Forward-Active assumption we had
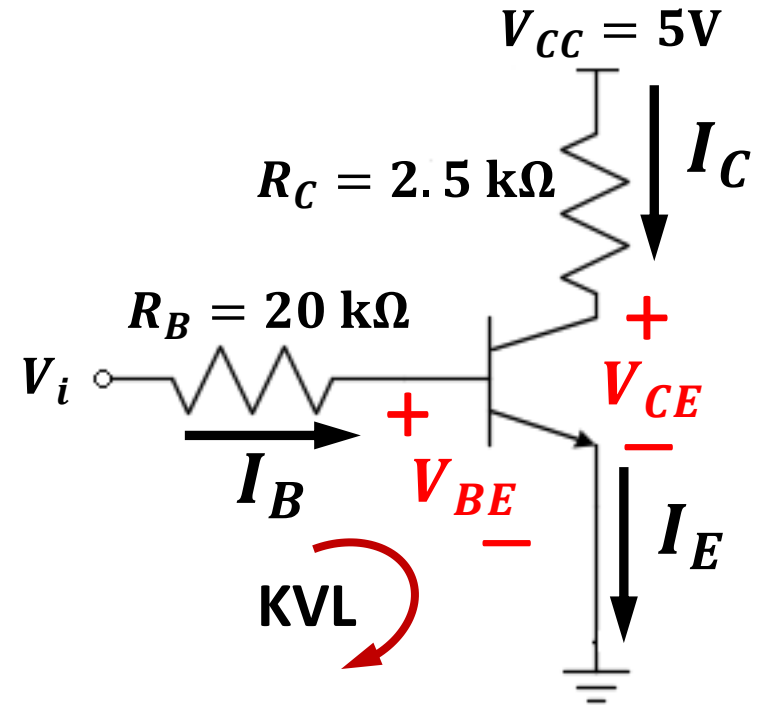
$$\text{KVL} \quad 5 + (-I_C(\text{sat}) \times 2.5\text{k}\Omega) - V_{CE}(\text{sat}) = 0$$



$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$

BJT is ON since $V_i > V_{BE}(\text{on})$

Let's find the collector current at onset of saturation


$$I_B = 0.14\text{mA}$$

$$I_C = \beta I_B = 28\text{mA}$$

Under Forward-Active assumption we had

$$\text{KVL} \quad 5 + (-I_C(\text{sat}) \times 2.5\text{k}\Omega) - V_{CE}(\text{sat}) = 0$$
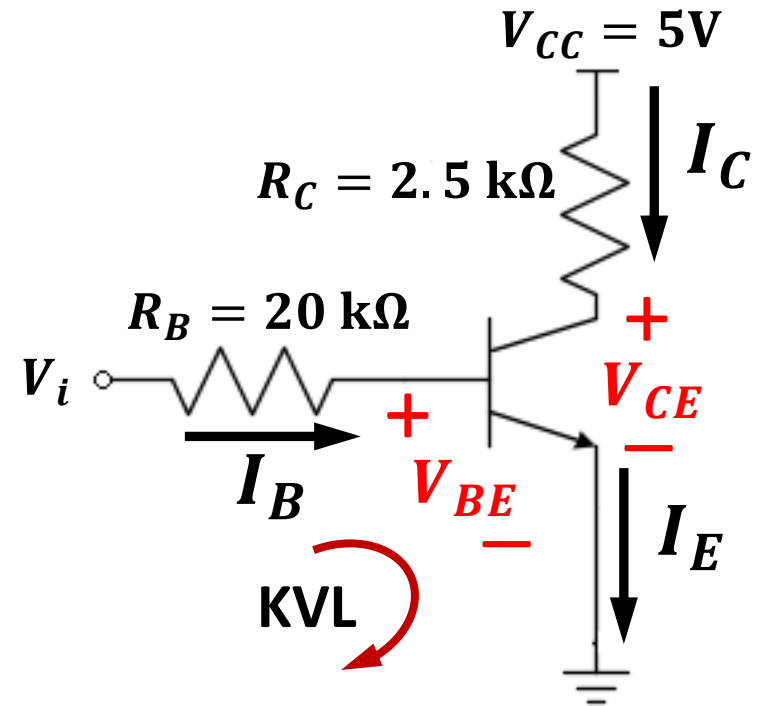
$$I_C(\text{sat}) = 4.8\text{V}/2.5\text{k}\Omega = 1.92\text{mA} \ll \beta I_B$$



$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$

BJT is ON since $V_i > V_{BE}(\text{on})$

Let's find the collector current at onset of saturation

$$I_B = 0.14\text{mA}$$

$$I_C = \beta I_B = 28\text{mA}$$


Under Forward-Active assumption we had

$$\text{KVL} \quad 5 + (-I_C(\text{sat}) \times 2.5\text{k}\Omega) - V_{CE}(\text{sat}) = 0$$

$$I_C(\text{sat}) = 4.8\text{V}/2.5\text{k}\Omega = 1.92\text{mA} \ll \beta I_B$$

$$V_{CE} = V_{CE}(\text{sat}) = 0.2\text{V}$$

Saturation mode

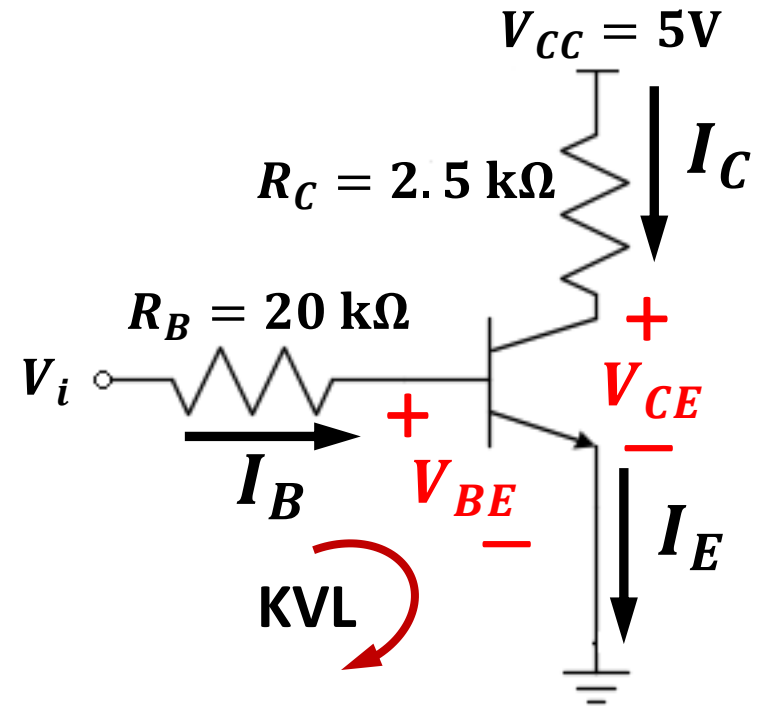

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$


$$\beta = 200$$

$$(b) V_i = 3.5\text{V}$$

Let's find the base current at onset of saturation

$$I_B(\text{at onset of saturation}) = \frac{I_C(\text{sat})}{\beta} = 9.6 \mu\text{A}$$
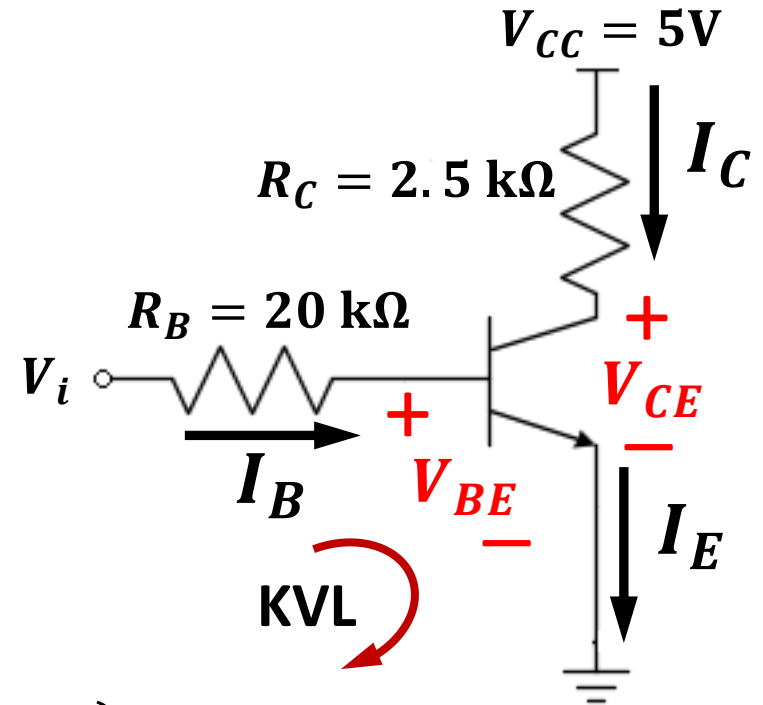
$$V_i(\text{at onset of saturation}) = 9.6 \mu\text{A} \times 20\text{k}\Omega + 0.7 = 0.892\text{V}$$



The base current can be increased further, but the collector current remains at the saturation value $I_C(\text{sat})$.


Example 3: BJT with emitter resistor

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 100$$

$$I_E = (\beta + 1)I_B$$

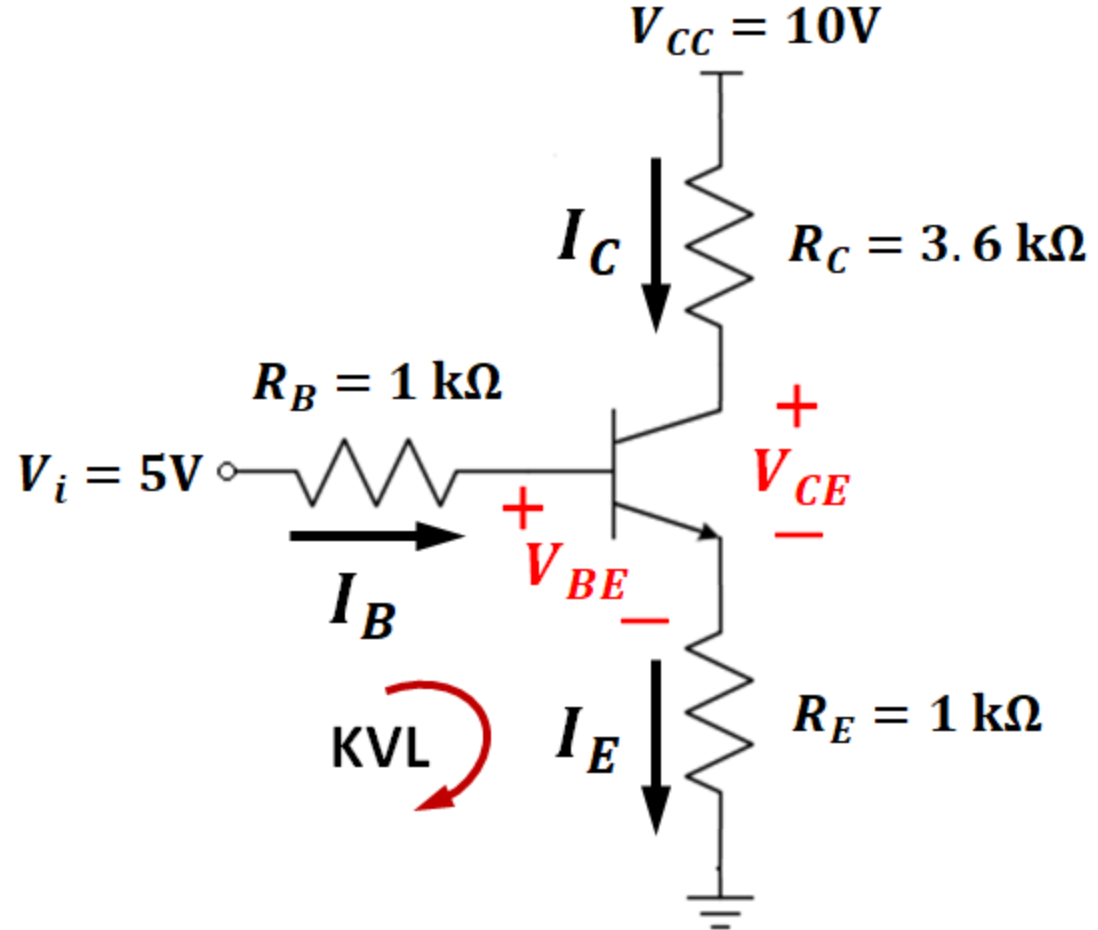

Example 3: BJT with emitter resistor

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$


$$\beta = 100$$

$$I_E = (\beta + 1)I_B$$

Assuming forward active mode

Base-emitter KVL

$$-V_i + I_B R_B + V_{BE} + I_E R_E = 0$$

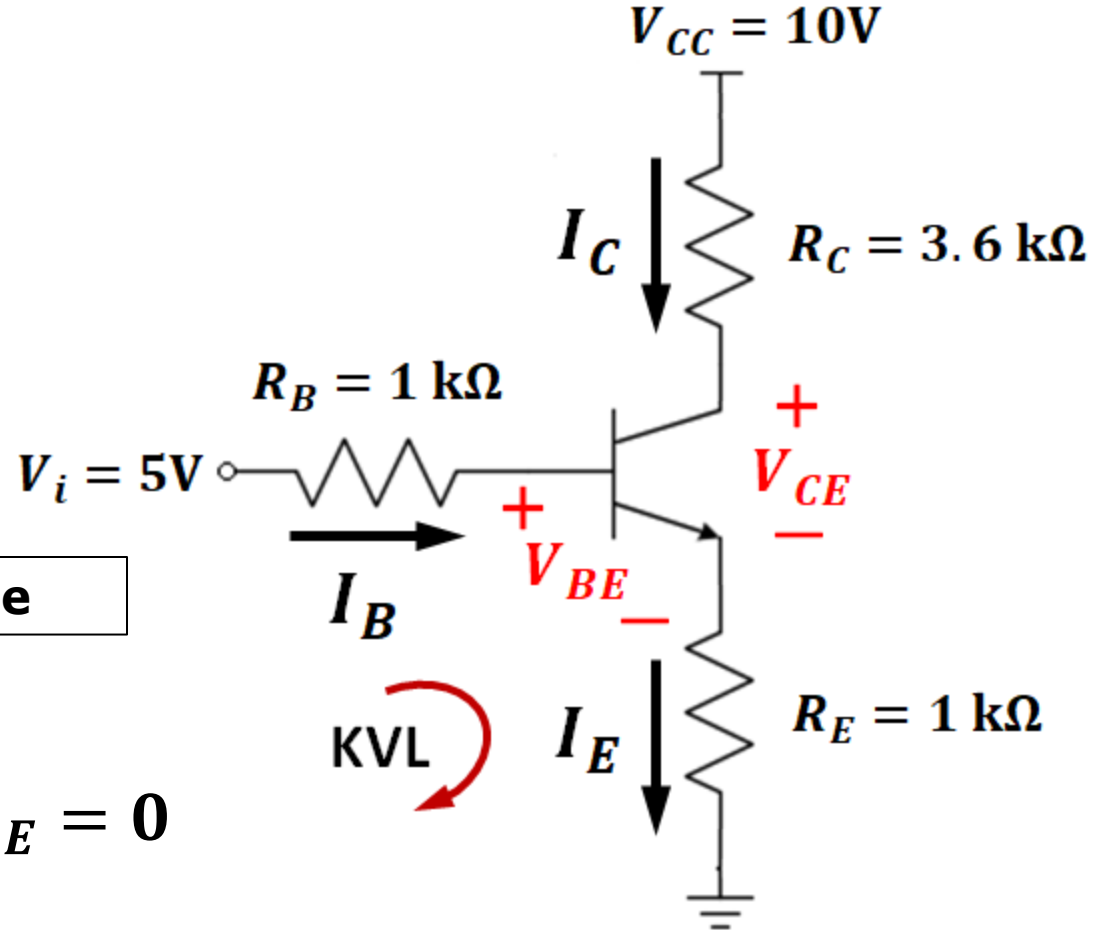

Example 3: BJT with emitter resistor

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 100$$

$$I_E = (\beta + 1)I_B$$


Assuming forward active mode

Base-emitter KVL

$$-V_i + I_B R_B + V_{BE} + I_E R_E = 0$$

$$-5 + I_B \times 1\text{k} + 0.7 + (\beta + 1)I_B \times 1\text{k} = 0$$

$$I_B = \frac{4.3}{1\text{k} + (\beta + 1)1\text{k}} = \frac{4.3}{102\text{k}} = 0.0422\text{mA} = 42.2\mu\text{A}$$

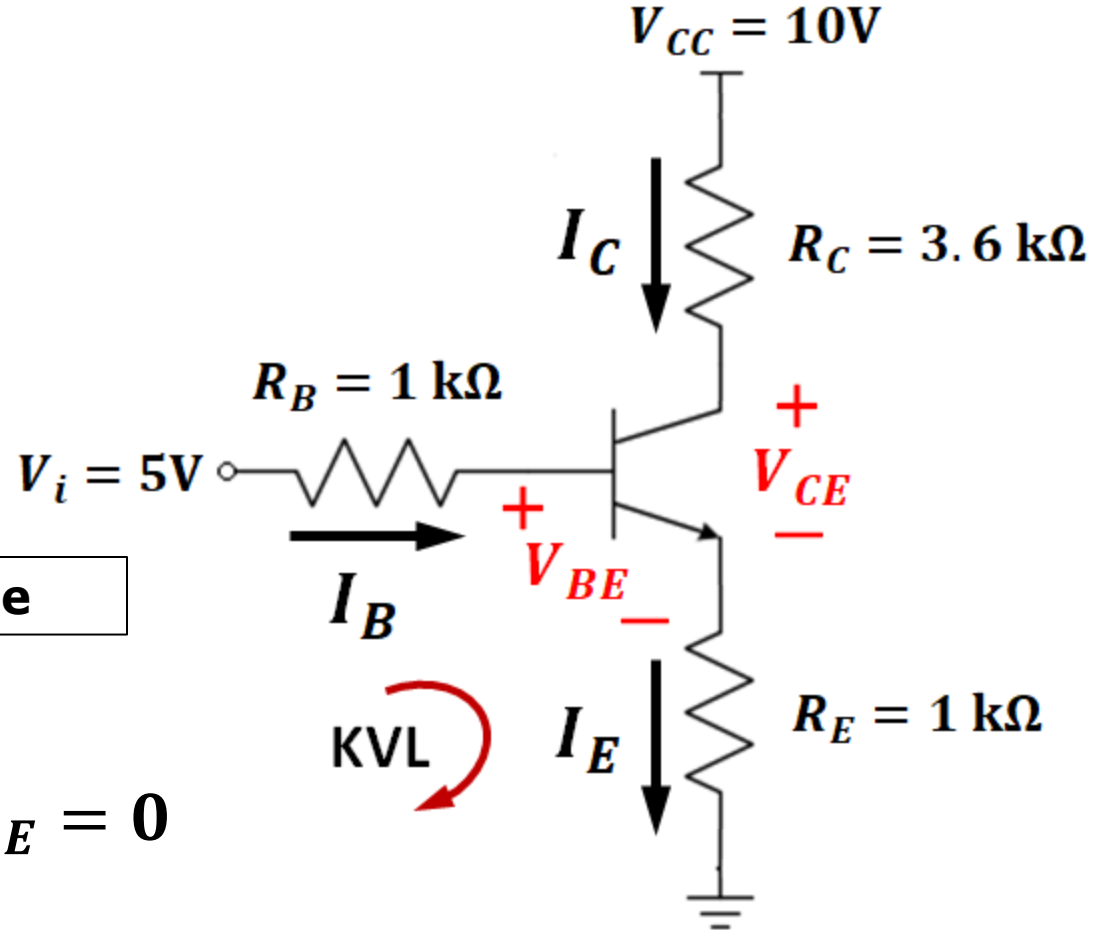


Example 3: BJT with emitter resistor

Assuming forward active mode

$$I_B = 0.0422\text{mA}$$

$$I_E = (\beta + 1)I_B = 4.26\text{mA}$$

$$I_C = \beta I_B = 4.22\text{mA}$$

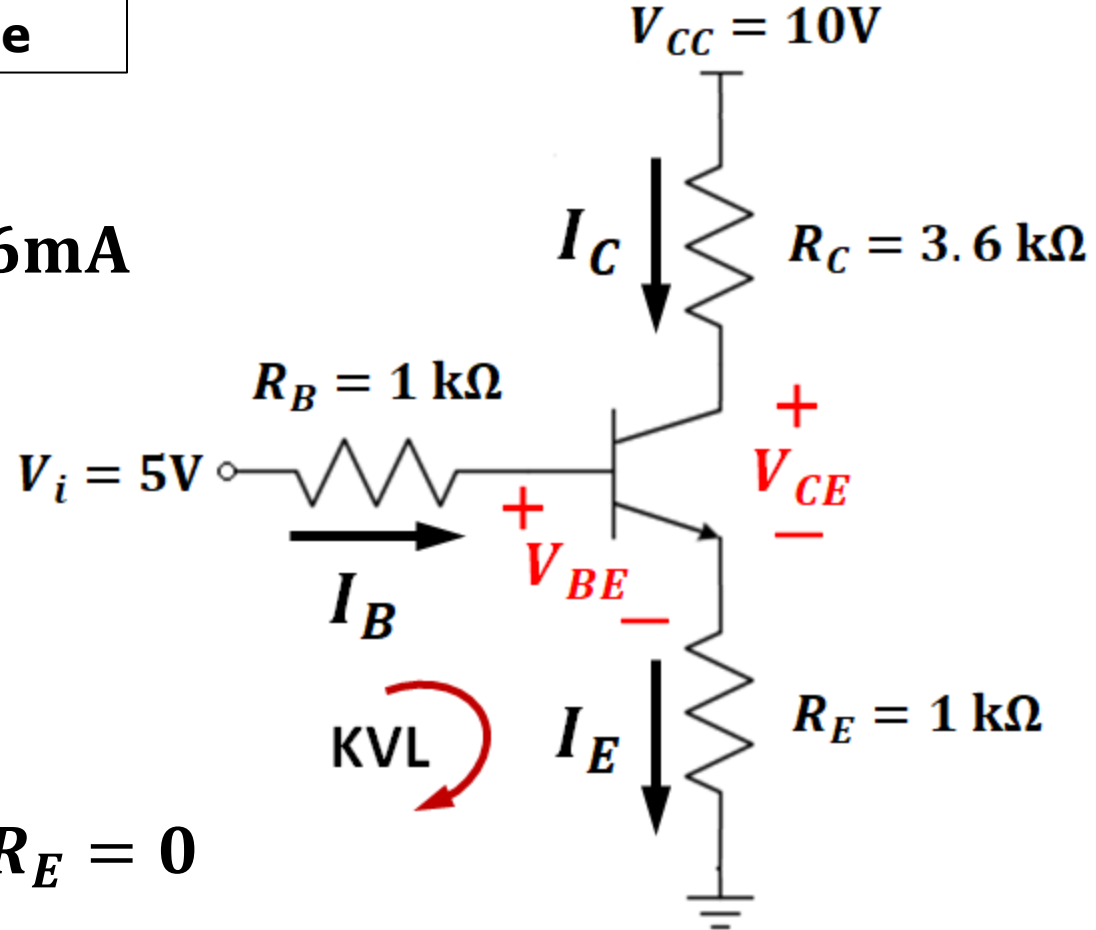

Now, check for saturation

Collector-emitter KVL

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$


Example 3: BJT with emitter resistor

Assuming forward active mode

$$I_B = 0.0422\text{mA}$$

$$I_E = (\beta + 1)I_B = 4.26\text{mA}$$

$$I_C = \beta I_B = 4.22\text{mA}$$

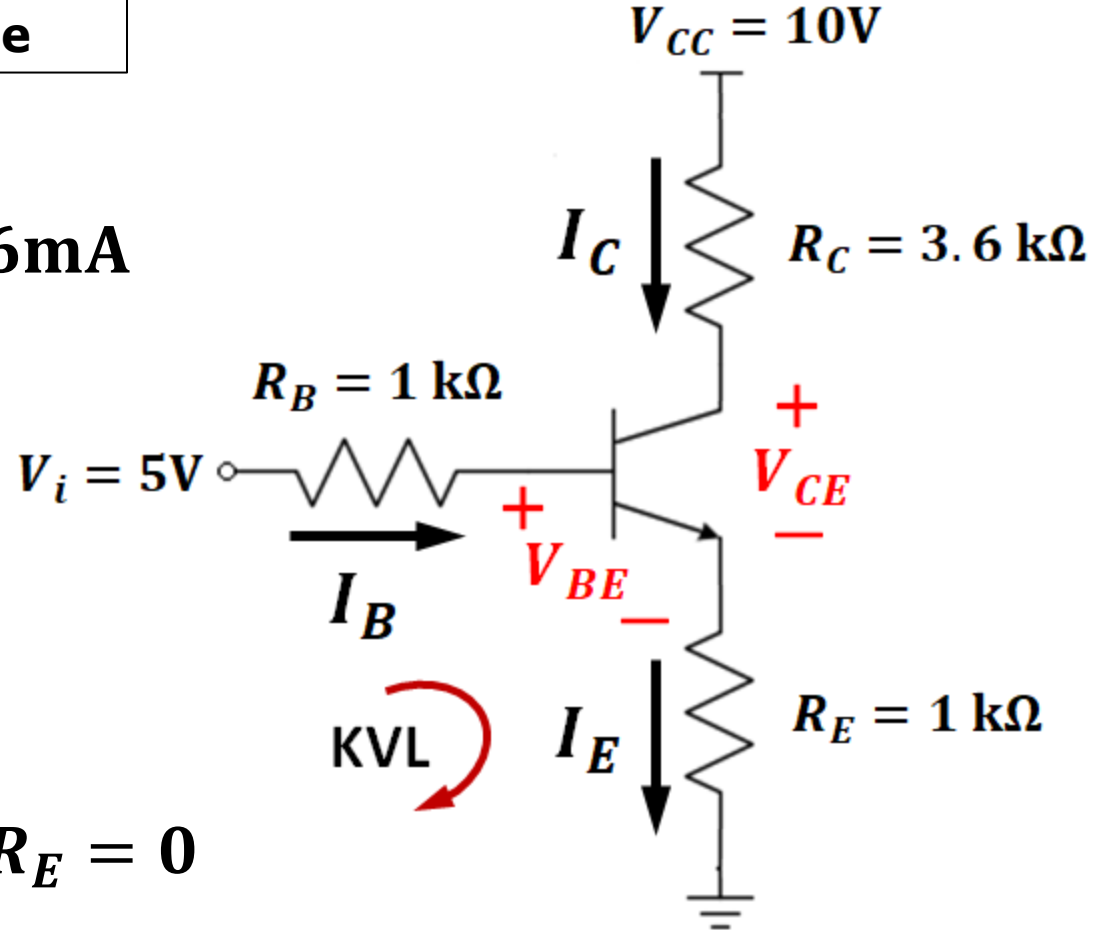

Now, check for saturation

Collector-emitter KVL

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$-10 + 4.22\text{m} \times 3.6\text{k} + V_{CE} + 4.26 \times 1\text{k} = 0$$

$$V_{CE} = 10 - 15.192 - 4.26 = -9.452\text{V} \ll V_{CE}(\text{sat})$$


Example 3: BJT with emitter resistor

Assuming forward active mode

$$I_B = 0.0422\text{mA}$$

$$I_E = (\beta + 1)I_B = 4.26\text{mA}$$

$$I_C = \beta I_B = 4.22\text{mA}$$

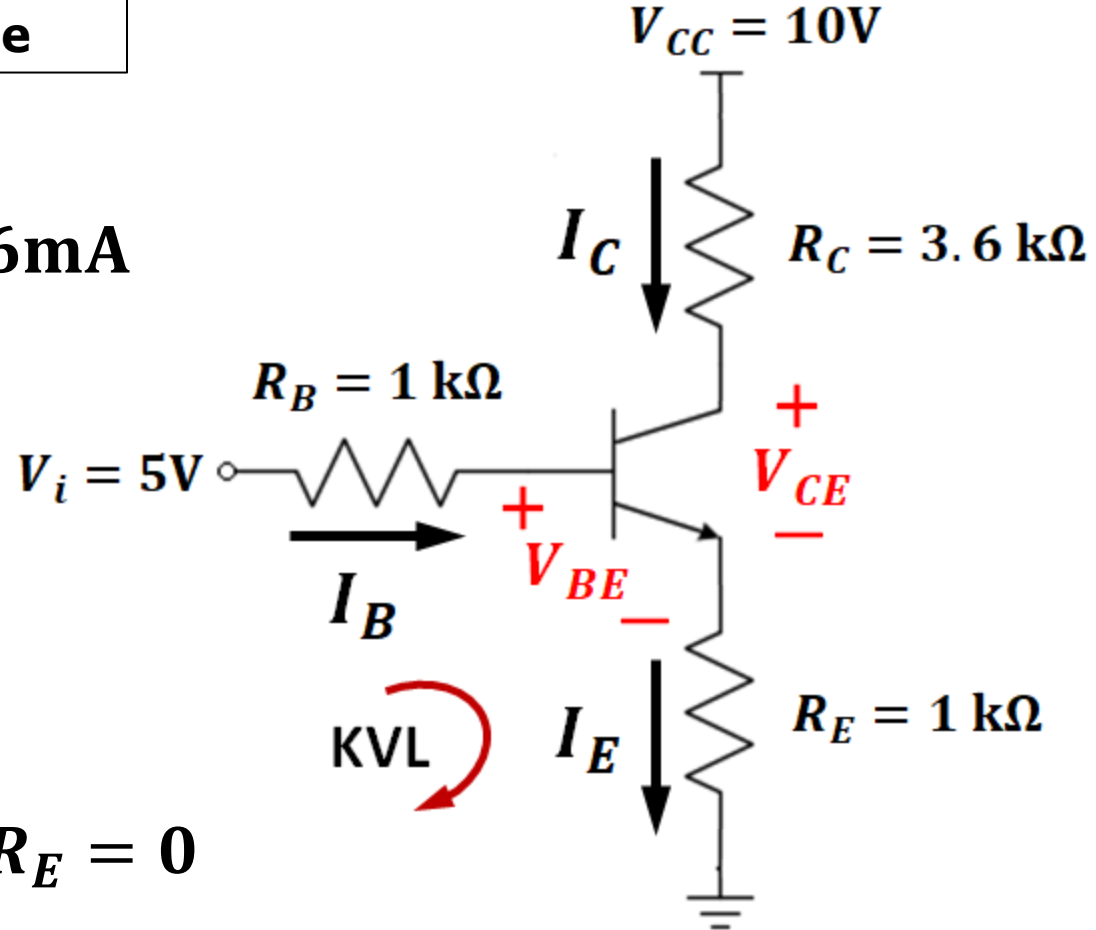

Now, check for saturation

Collector-emitter KVL

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$-10 + 4.22\text{m} \times 3.6\text{k} + V_{CE} + 4.26 \times 1\text{k} = 0$$

$$V_{CE} = 10 - 15.192 - 4.26 = -9.452\text{V} \ll V_{CE}(\text{sat})$$

Assumption is invalid.



$$V_{CE} = V_{CE}(\text{sat}) = 0.2\text{V}$$

Previous results for currents are invalid


⇒ $V_{CE} = V_{CE}(\text{sat}) = 0.2 \text{ V}$

Remember

$$I_E = \frac{\beta + 1}{\beta} I_C = 1.01 I_C$$

(valid up to onset of saturation)

$V_i = ?$

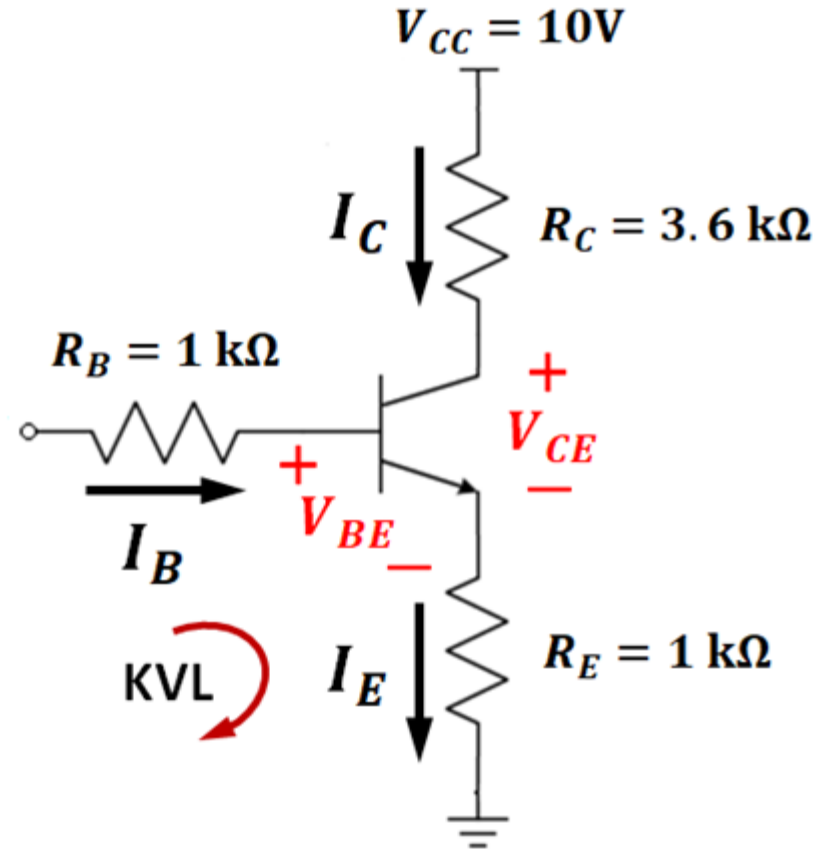

Previous results for currents are invalid

$$V_{CE} = V_{CE}(\text{sat}) = 0.2 \text{ V}$$

Remember


$$I_E = \frac{\beta + 1}{\beta} I_C = 1.01 I_C$$

(valid up to onset of saturation)

Recalculate collector-emitter KVL

$$-V_{CC} + I_C(\text{onsat})R_C + V_{CE}(\text{onsat}) + I_ER_E = 0$$
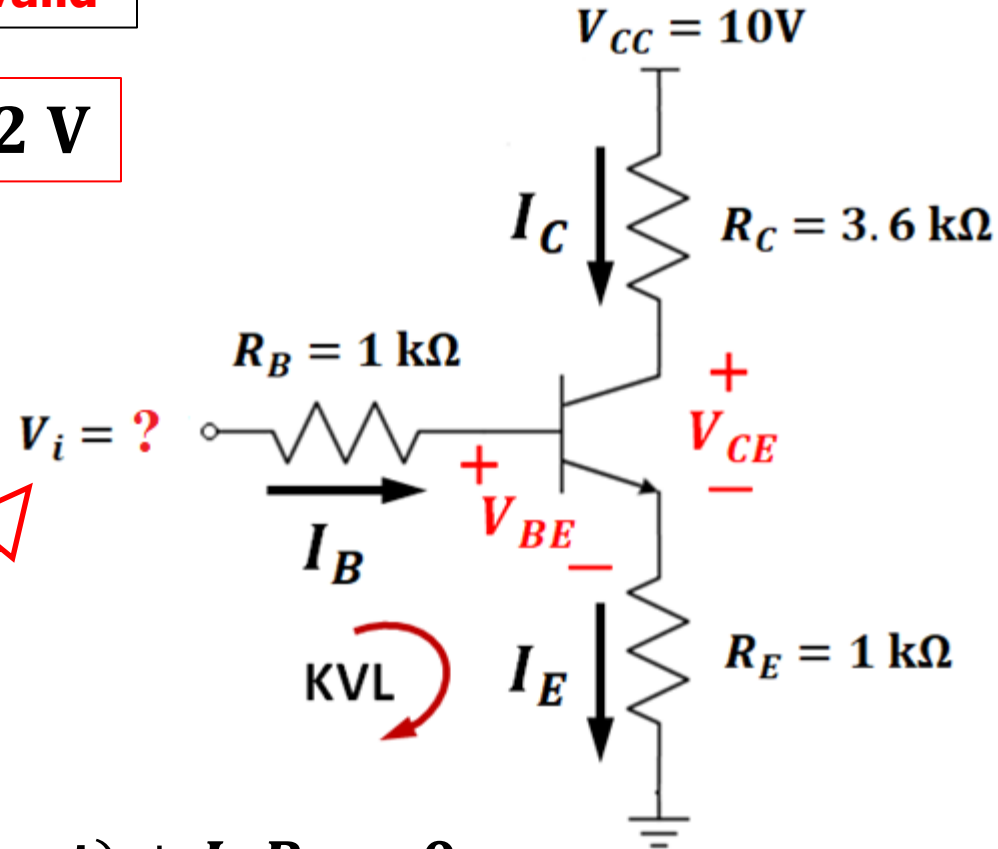
$$-10 + I_C(\text{onsat}) \times 3.6\text{k} + 0.2 + 1.01 \times I_C(\text{onsat}) \times 1\text{k} = 0$$



Previous results for currents are invalid

$$V_{CE} = V_{CE}(\text{sat}) = 0.2 \text{ V}$$

Remember

$$I_E = \frac{\beta + 1}{\beta} I_C = 1.01 I_C$$

(valid up to onset of saturation)

Recalculate collector-emitter KVL


$$-V_{CC} + I_C(\text{onsat})R_C + V_{CE}(\text{onsat}) + I_ER_E = 0$$

$$-10 + I_C(\text{onsat}) \times 3.6\text{k} + 0.2 + 1.01 \times I_C(\text{onsat}) \times 1\text{k} = 0$$

$$I_C(\text{onsat}) = 9.8 / 4.61\text{k} = 2.13 \text{ mA}$$

$$I_E(\text{onsat}) = 1.01 I_C = 2.15 \text{ mA}$$

At onset of saturation

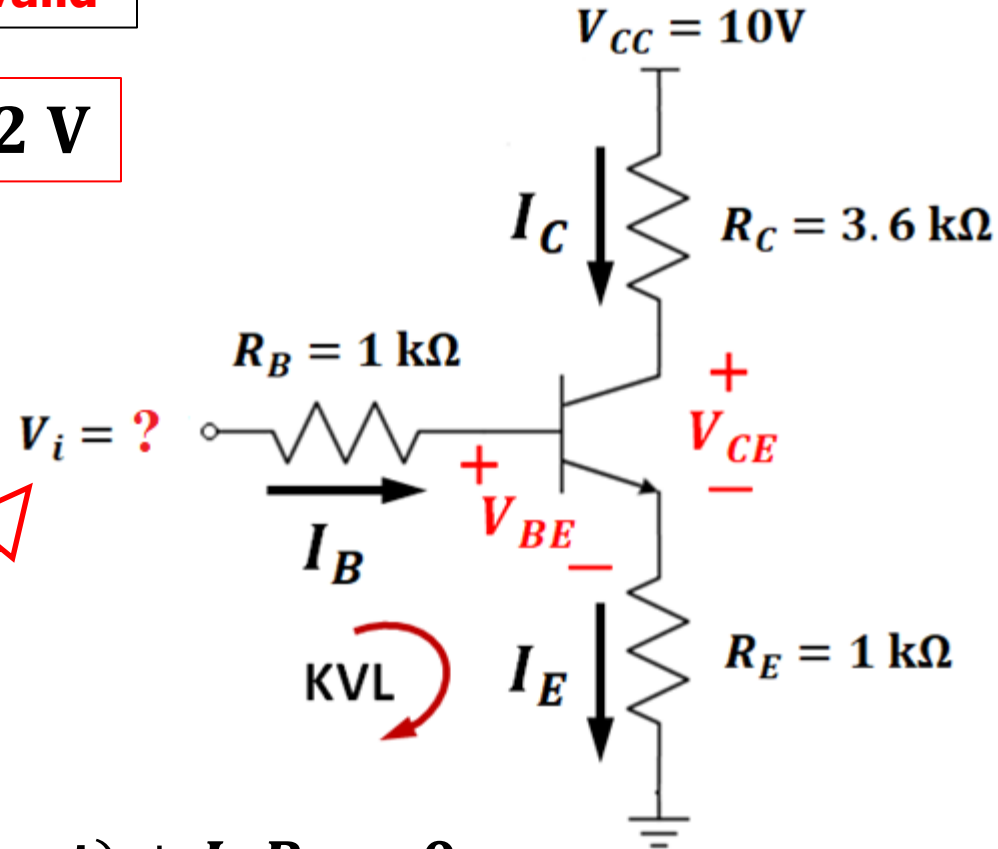


ATTENTION – Relevant for HW9-PL

$$I_E = \frac{\beta + 1}{\beta} I_C$$

is valid **ONLY** up to the point of saturation onset

Deeper in saturation one must keep using

$$I_E = I_B + I_C$$

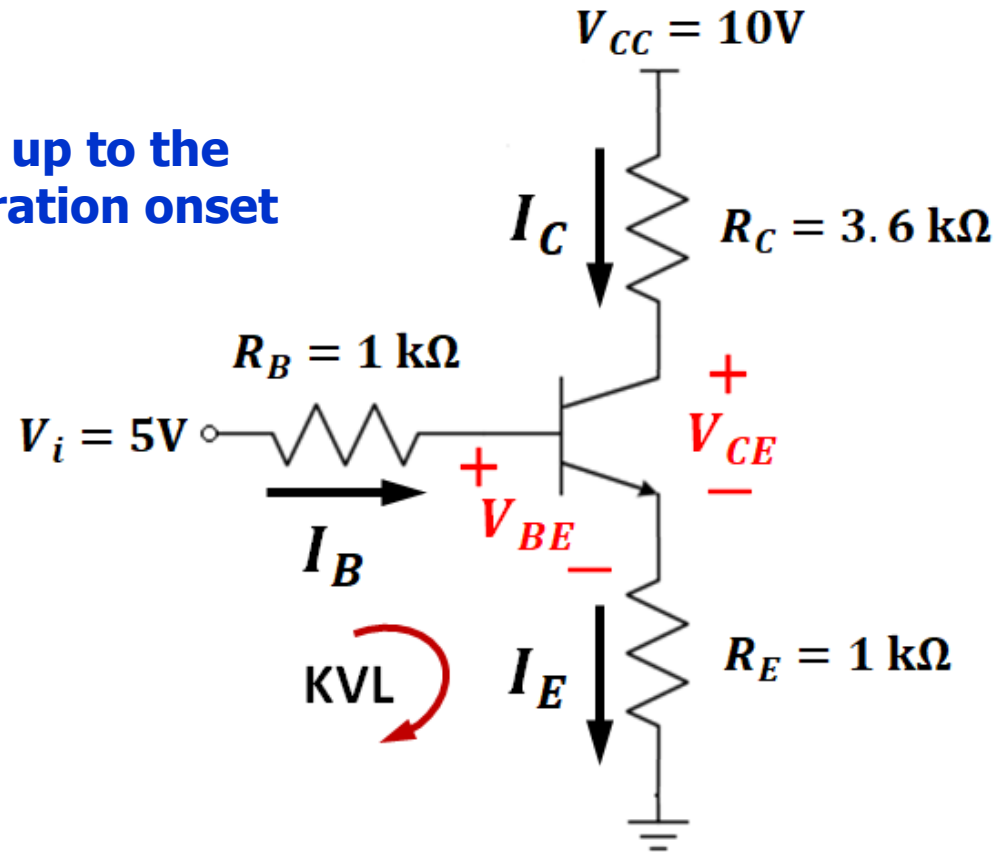

AGAIN: The derivations in the previous slide **ARE NOT VALID** in deeper saturation but only at the **onset point** where the device transitions from Forward-Active mode to Saturation mode

When the base current is increased beyond onset, the voltage drop in the emitter resistor changes, since


$$I_E = I_B + I_C$$

If we assume that the saturation $V_{CE}(\text{sat})$ remains at the value specified by the manufacturer throughout, in saturation

$$V_{CC} - V_{CE}(\text{sat}) = R_C I_C + R_E I_E$$

This equation has to be solved simultaneously with the base circuit KVL

$$V_i - V_{BE} = R_B I_B + R_E I_E$$

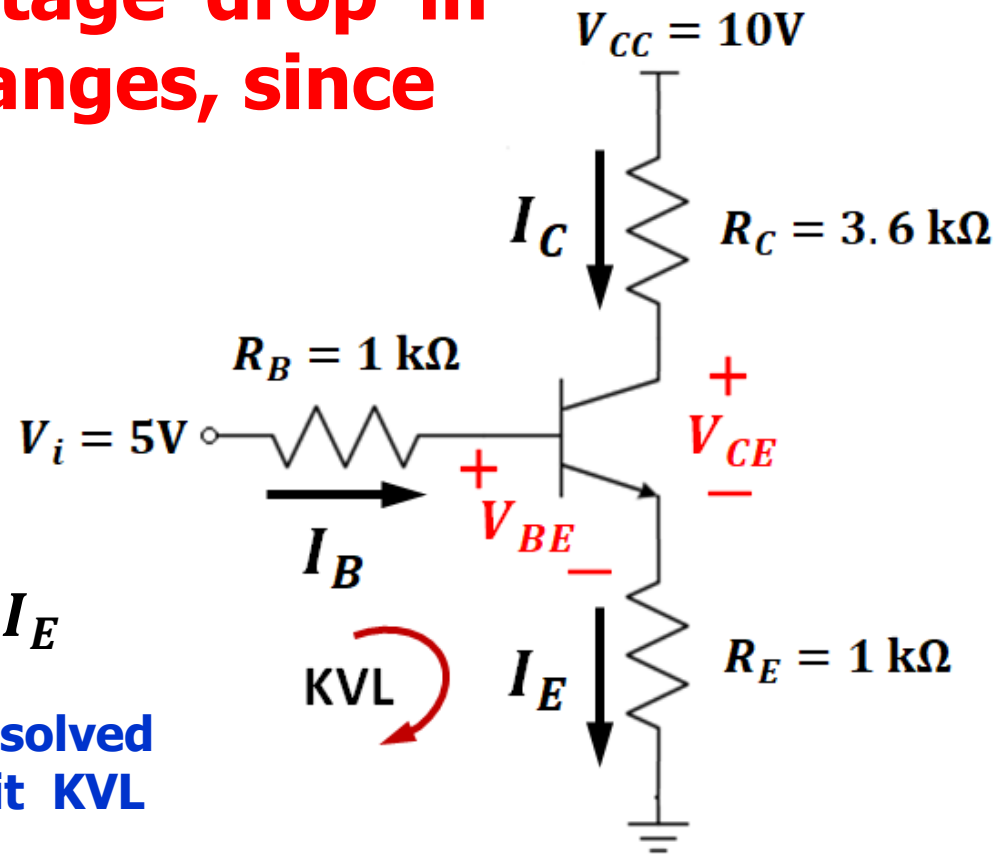


Recalculated currents

$$I_C(\text{onsat}) = 9.8 / 4.61\text{k} = 2.13 \text{ mA}$$

$$I_E(\text{onsat}) = 1.01 I_C = 2.15 \text{ mA}$$

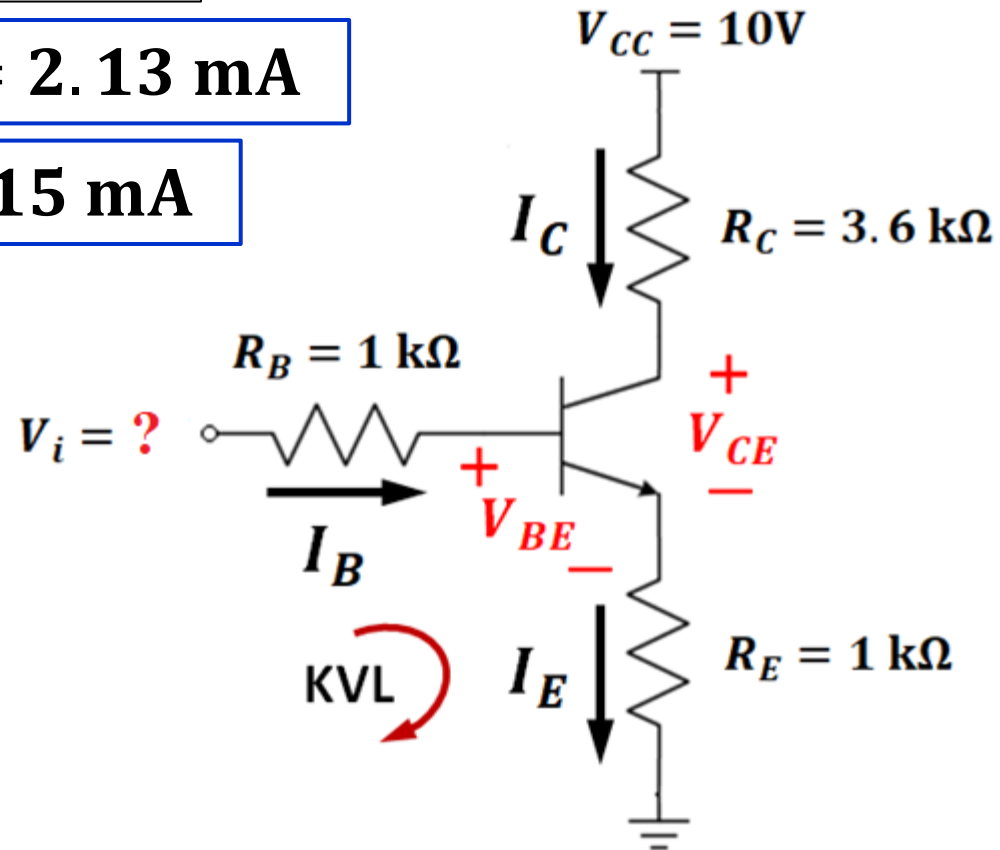Find base voltage at **onset** of saturation



Recalculated currents


$$I_C(\text{onsat}) = 9.8 / 4.61\text{k} = 2.13 \text{ mA}$$

$$I_E(\text{onsat}) = 1.01 I_C = 2.15 \text{ mA}$$

Find base voltage at **onset** of saturation


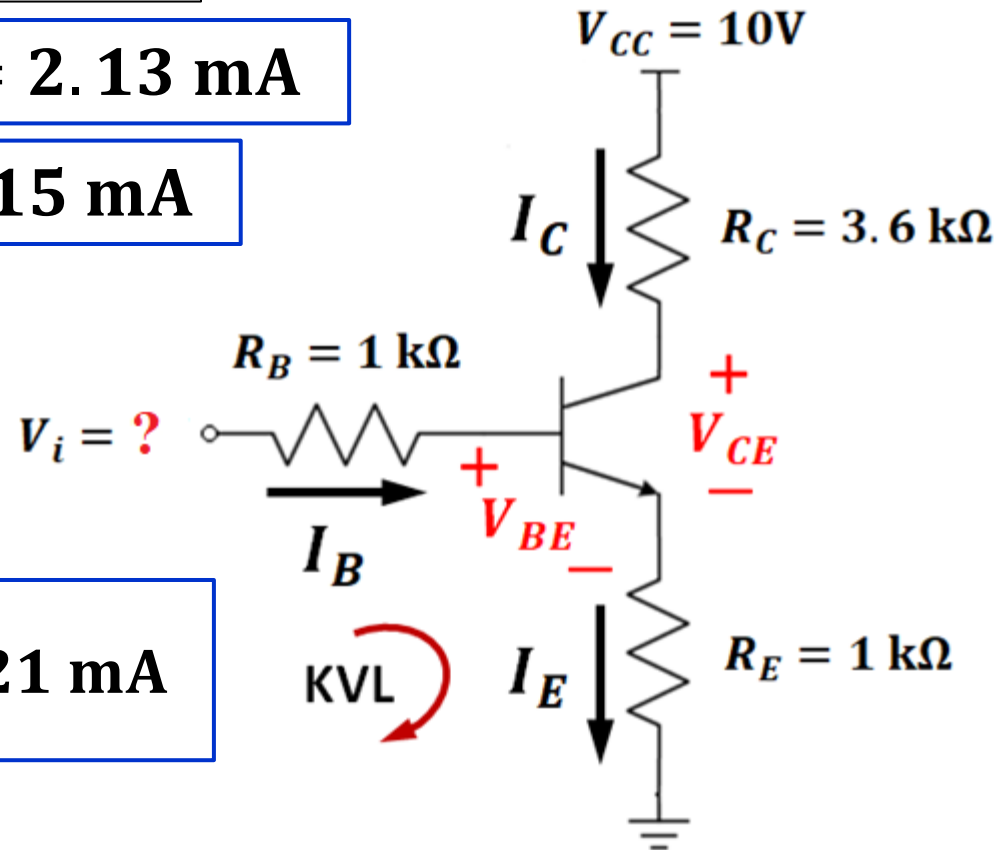
$$I_B(\text{onsat}) = \frac{I_C(\text{onsat})}{\beta} = 0.021 \text{ mA}$$



Recalculated currents

$$I_C(\text{onsat}) = 9.8 / 4.61\text{k} = 2.13 \text{ mA}$$

$$I_E(\text{onsat}) = 1.01 I_C = 2.15 \text{ mA}$$

Find base voltage at **onset** of saturation




$$I_B(\text{onsat}) = \frac{I_C(\text{onsat})}{\beta} = 0.021 \text{ mA}$$

Base circuit KVL

$$-V_i(\text{onsat}) + I_B(\text{onsat})R_B + V_{BE} + I_E(\text{onsat})R_E = 0$$
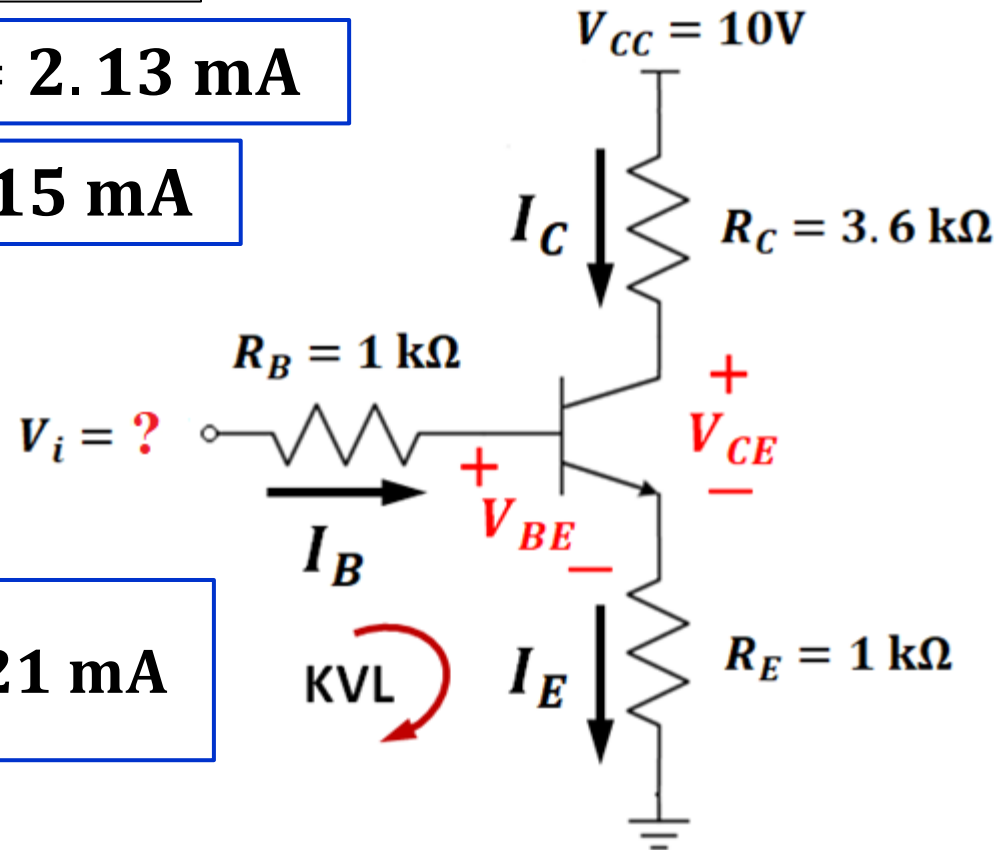
$$V_i(\text{onsat}) = 0.021\text{m} \times 1\text{k} + 0.7 + 2.15\text{m} \times 1\text{k}$$



Recalculated currents

$$I_C(\text{onsat}) = 9.8 / 4.61\text{k} = 2.13 \text{ mA}$$

$$I_E(\text{onsat}) = 1.01 I_C = 2.15 \text{ mA}$$

Find base voltage at **onset** of saturation



$$I_B(\text{onsat}) = \frac{I_C(\text{onsat})}{\beta} = 0.021 \text{ mA}$$


Base circuit KVL

$$-V_i(\text{onsat}) + I_B(\text{onsat})R_B + V_{BE} + I_E(\text{onsat})R_E = 0$$

$$V_i(\text{onsat}) = 0.021\text{m} \times 1\text{k} + 0.7 + 2.15\text{m} \times 1\text{k}$$

$$V_i(\text{onsat}) = 2.87 \text{ V}$$

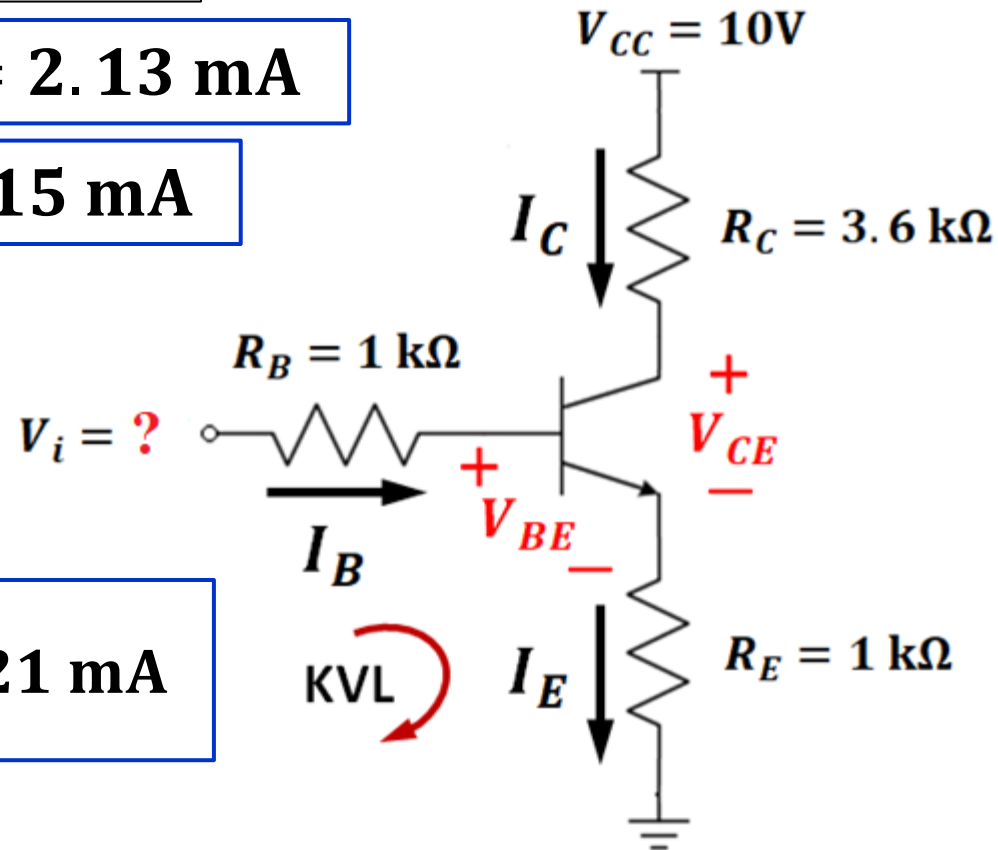At this input voltage on the base resistor, the BJT starts saturating



Resistor on emitter changes the saturation behavior

$$V_{BE}(\text{on}) \leq V_B < V_i(\text{onsat}) = 2.87 \text{ V}$$


Forward-Active mode

$$V_B = V_i(\text{onsat}) = 2.87 \text{ V}$$


Onset of saturation
(FA mode equations are still valid)

$$V_B > V_i(\text{onsat}) = 2.87 \text{ V}$$

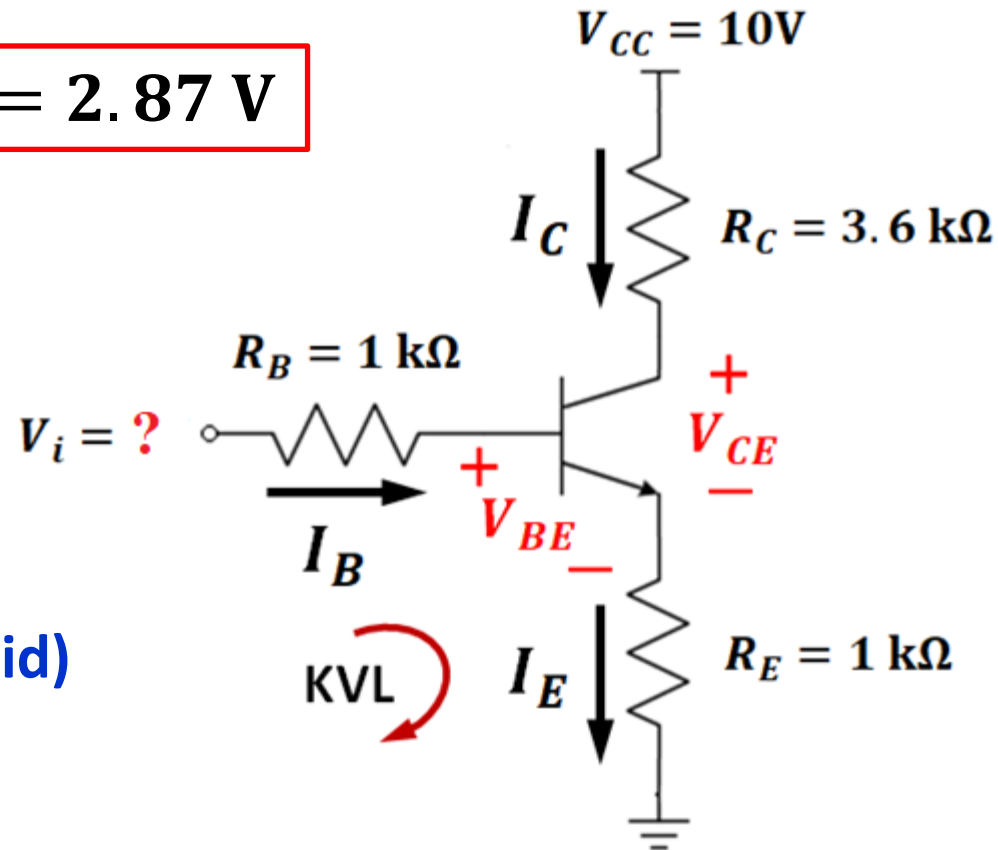“Deeper” saturation
(FA mode equations are NOT valid)



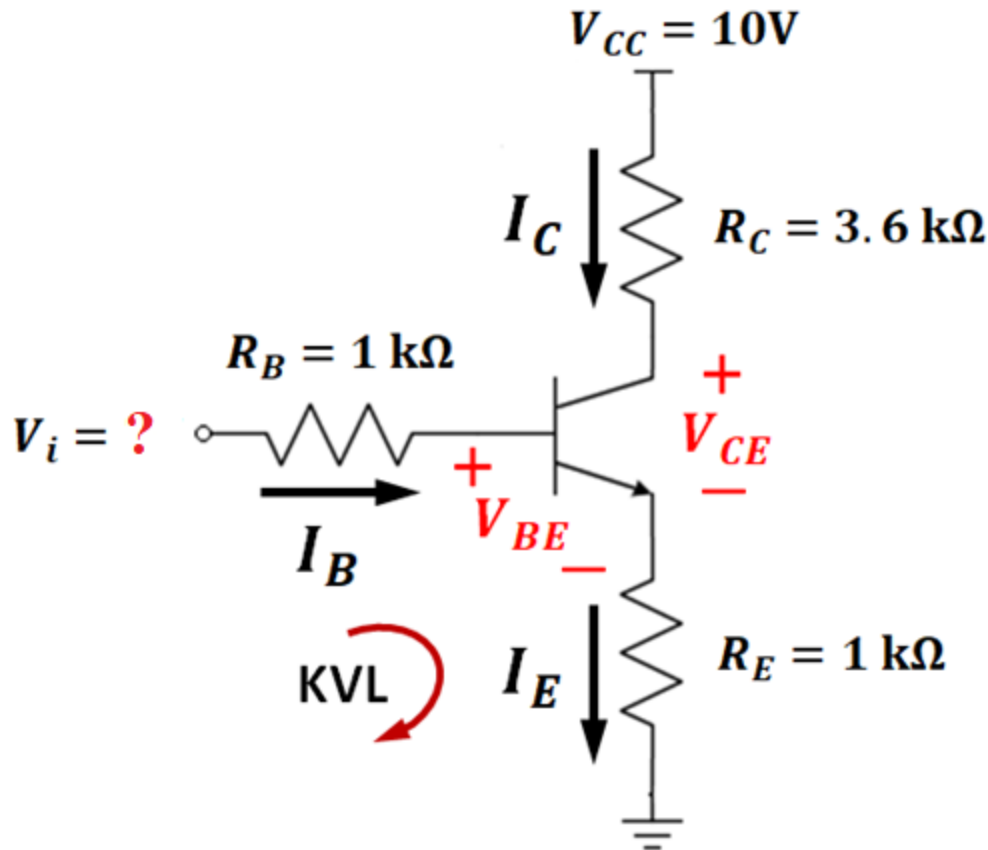In deeper saturation, collector current decreases somewhat



$$V_{CC} = 10 \text{ V}$$

$$I_C R_C$$

assume constant

$$V_{CE} = V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$I_E R_E = (I_B + I_C) R_E$$


I_B keeps increasing in deeper saturation

$$V_B > V_i(\text{onsat}) = 2.87 \text{ V}$$

$$I_C < I_C(\text{onsat}) = 2.13 \text{ mA}$$

MUST SOLVE FOR COUPLED KVL'S IN BASE AND COLLECTOR LOOPS

$$V_i = 5\text{ V}$$

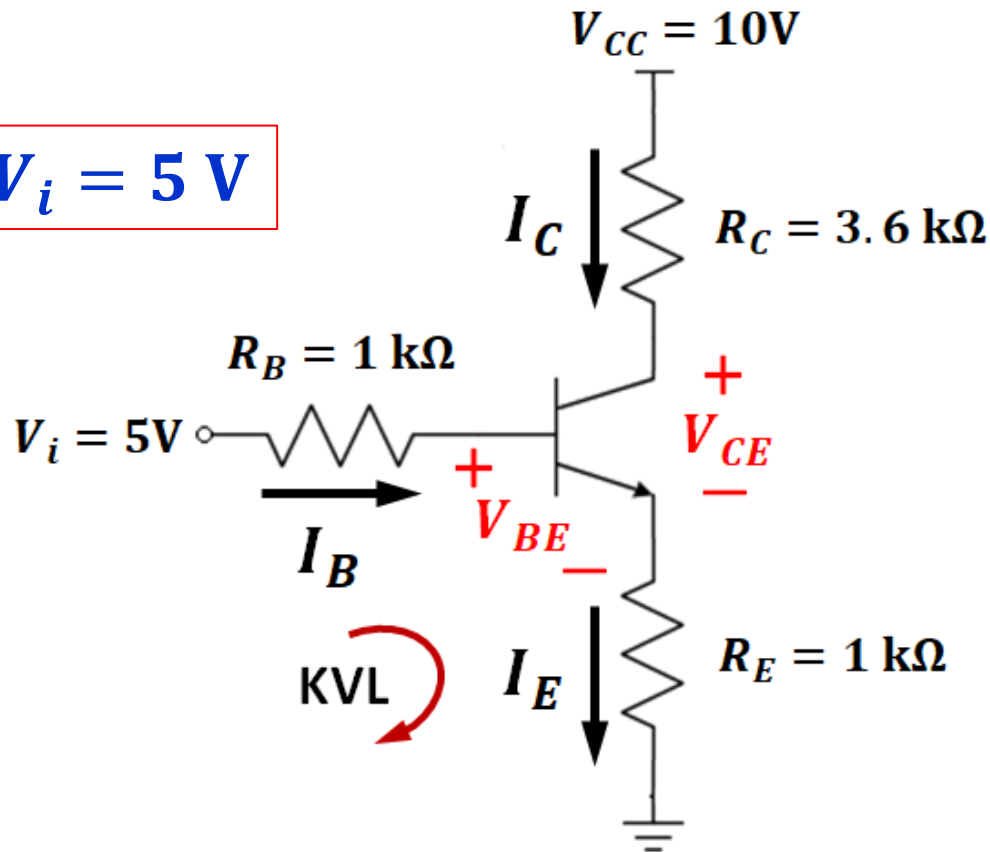

$$V_{CC} = 10\text{ V}$$

$$I_C R_C$$

assume constant

$$V_{CE} = V_{CE}(\text{sat}) = 0.2\text{ V}$$


$$I_E R_E = (I_B + I_C) R_E$$

$$V_i = I_B R_B + V_{BE}(\text{on}) + I_E R_E$$

$$V_{CC} = I_C R_C + V_{CE}(\text{sat}) + I_E R_E$$

MUST SOLVE FOR COUPLED KVL'S IN BASE AND COLLECTOR LOOPS

$$V_i = 5 \text{ V}$$

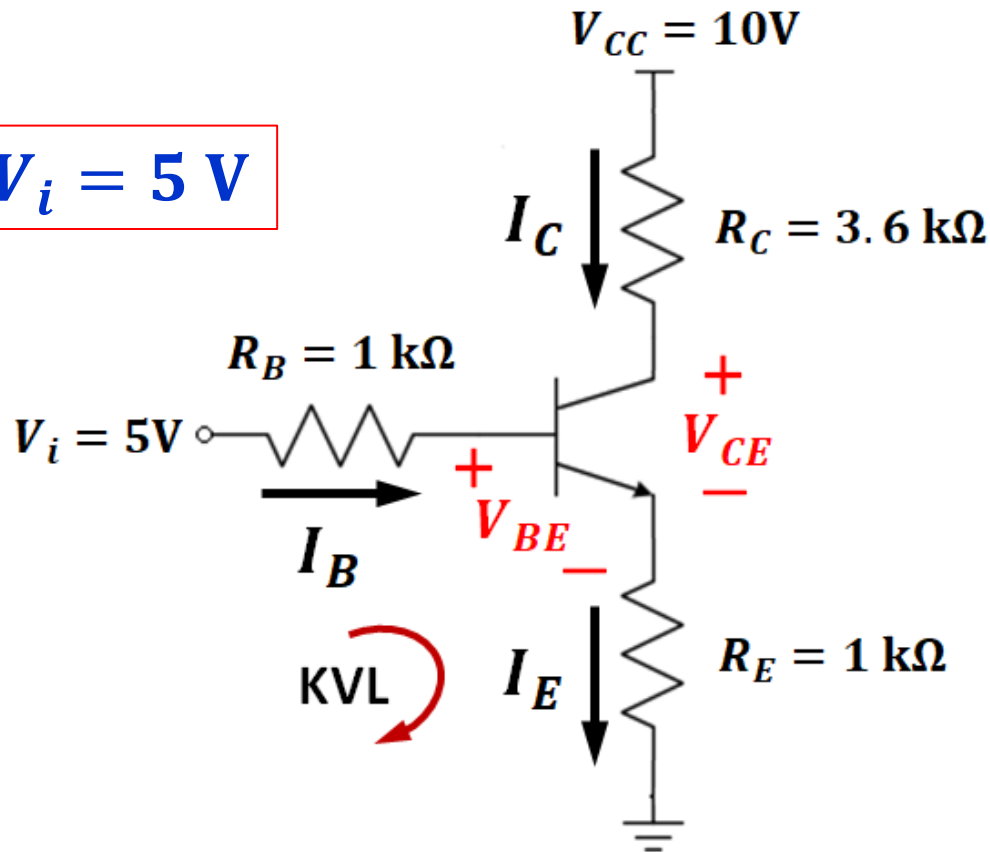

$$V_{CC} = 10 \text{ V}$$

$$I_C R_C$$

assume constant

$$V_{CE} = V_{CE}(\text{sat}) = 0.2 \text{ V}$$


$$I_E R_E = (I_B + I_C) R_E$$

$$5 = 1\text{k} I_B + 0.7 + (I_B + I_C) 1\text{k}$$

$$10 = 3.6\text{k} I_C + 0.2 + (I_B + I_C) 1\text{k}$$

MUST SOLVE FOR COUPLED KVL'S IN BASE AND COLLECTOR LOOPS

$V_i = 5\text{ V}$

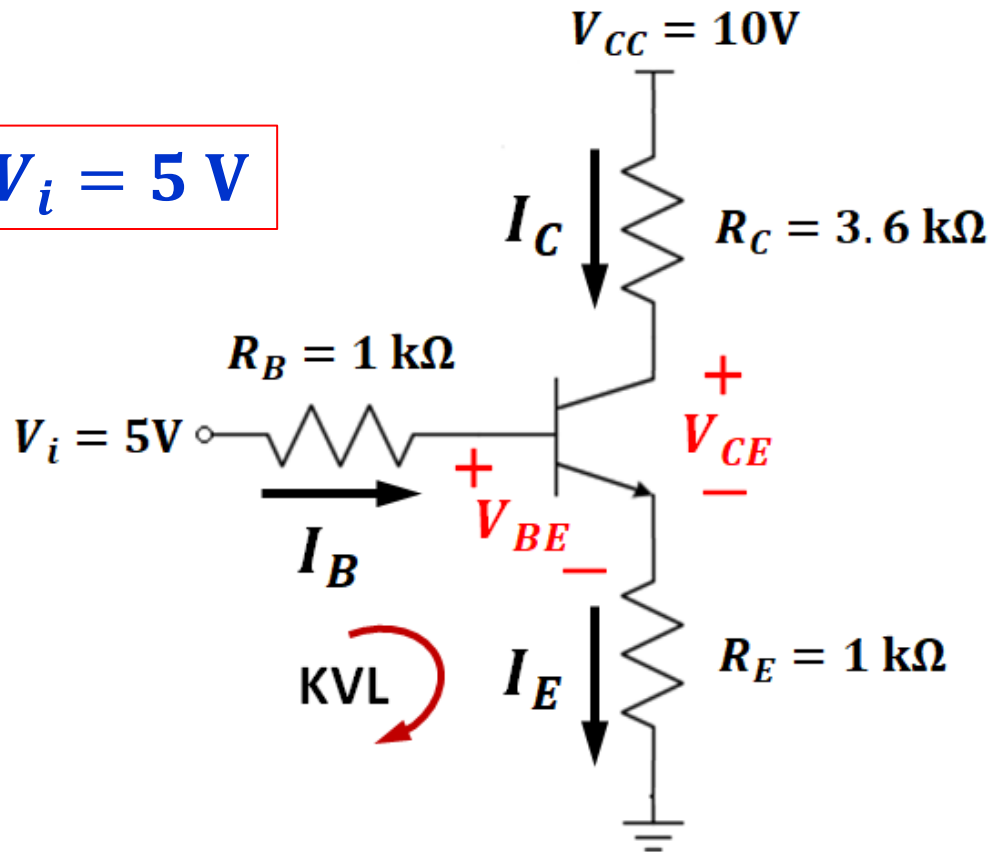

$V_{CC} = 10\text{ V}$

$I_C R_C = 6.717\text{ V}$

assume constant

$V_{CE} = V_{CE}(\text{sat}) = 0.2\text{ V}$

$I_E R_E = (I_B + I_C) R_E = 3.083\text{ V}$

$2\text{k} I_B + 1\text{k} I_C = 4.3$

$1\text{k} I_B + 4.6\text{k} I_C = 9.8$

$I_B = 1.217\text{ mA}$

$I_C = 1.866\text{ mA} < I_C(\text{onsat})$

$I_C(\text{onsat}) = 2.13\text{ mA}$

RECAPITULATING: For BJT with added resistor on the emitter

To analyze deeper in saturation, one needs to solve the coupled KVL equations for base and collector loops with


$$I_E = I_B + I_C$$

V_{CC} is fixed. Since I_E increases, I_C must decrease to maintain the collector KVL valid.

In our model we assume that V_{CE} remains fixed at $V_{CE}(\text{sat})$.

This is an approximation. As I_C decreases, $V_{CE}(\text{sat})$ decreases slowly toward zero.

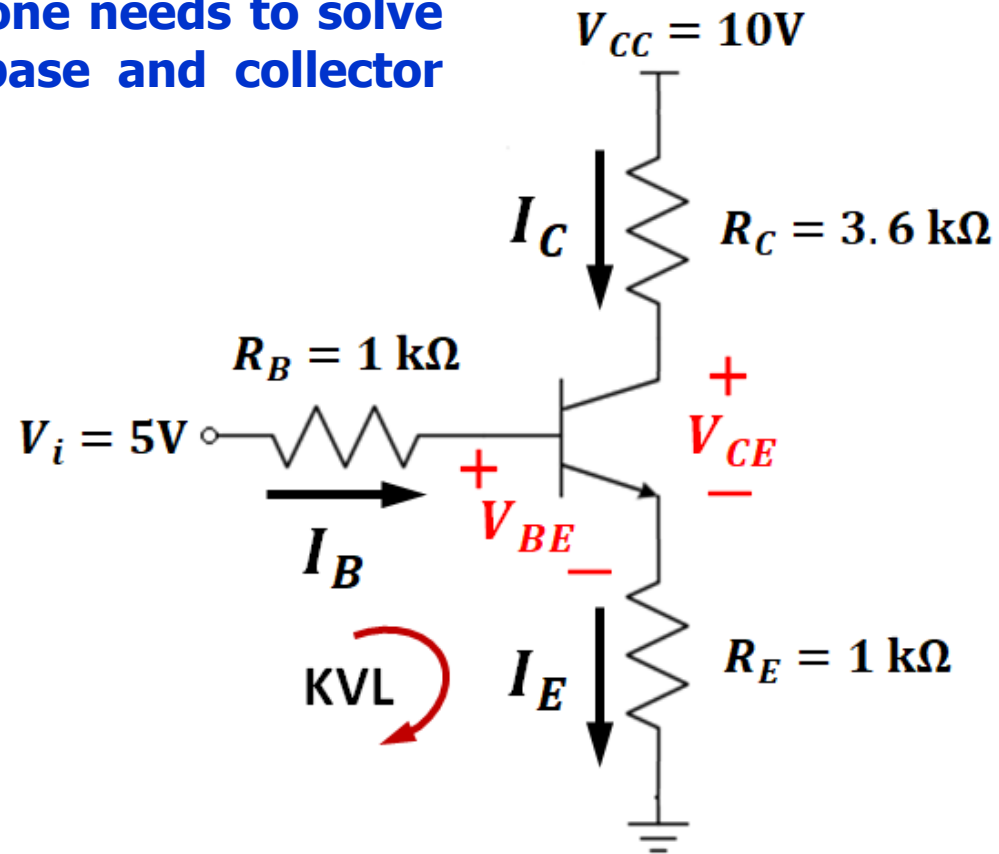Some even simpler models just set $V_{CE}(\text{sat}) = 0$.



$V_{BE} < V_{BE}(\text{ON})?$

YES

NO

BJT *OFF*

$V_{BE} = V_{BE}(\text{ON})$

$V_{CE} > V_{CE}(\text{sat}) ?$

YES

NO

Forward Active

$$I_C = \beta I_B$$


Saturation

$$V_{CE} = V_{CE}(\text{sat})$$


$$I_C = I_C(\text{sat})$$

BJT I - V curves are measured on actual devices

Measurements are made by ramping the V_{CE} at specific values of base current I_B

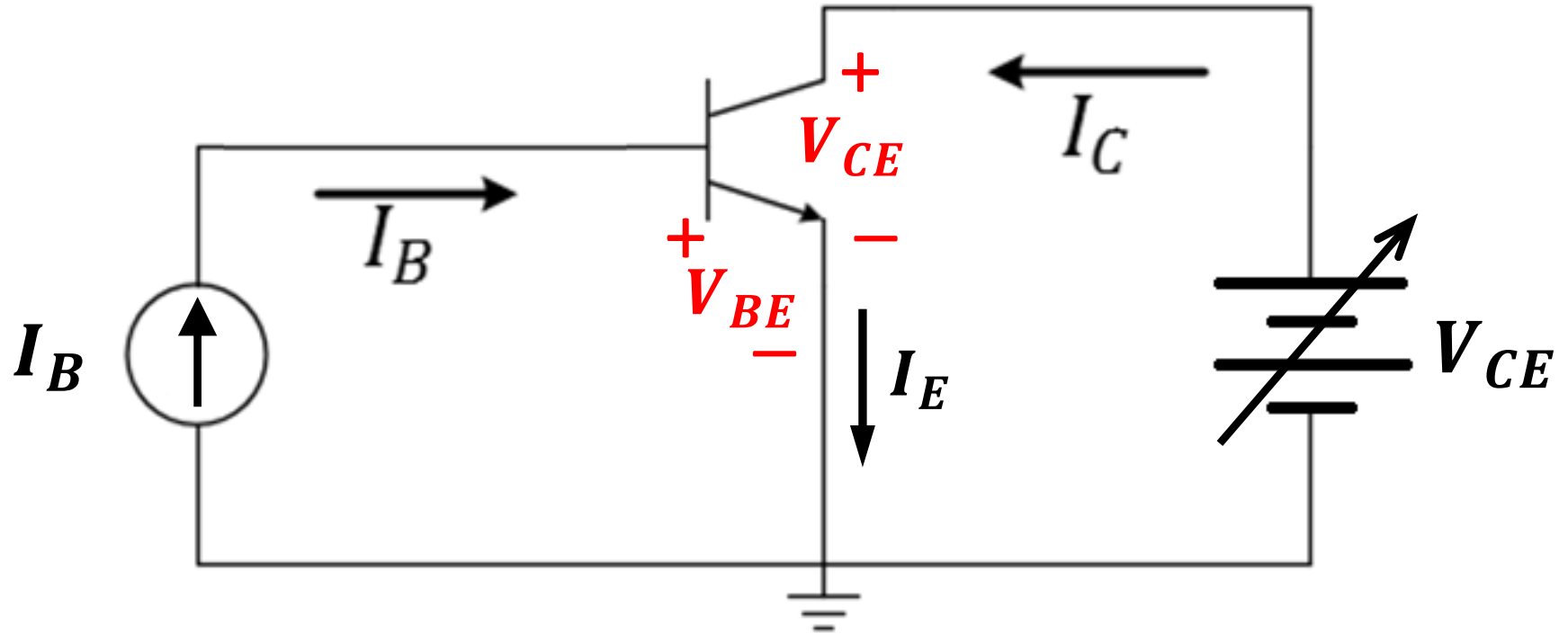

BJT I - V curves

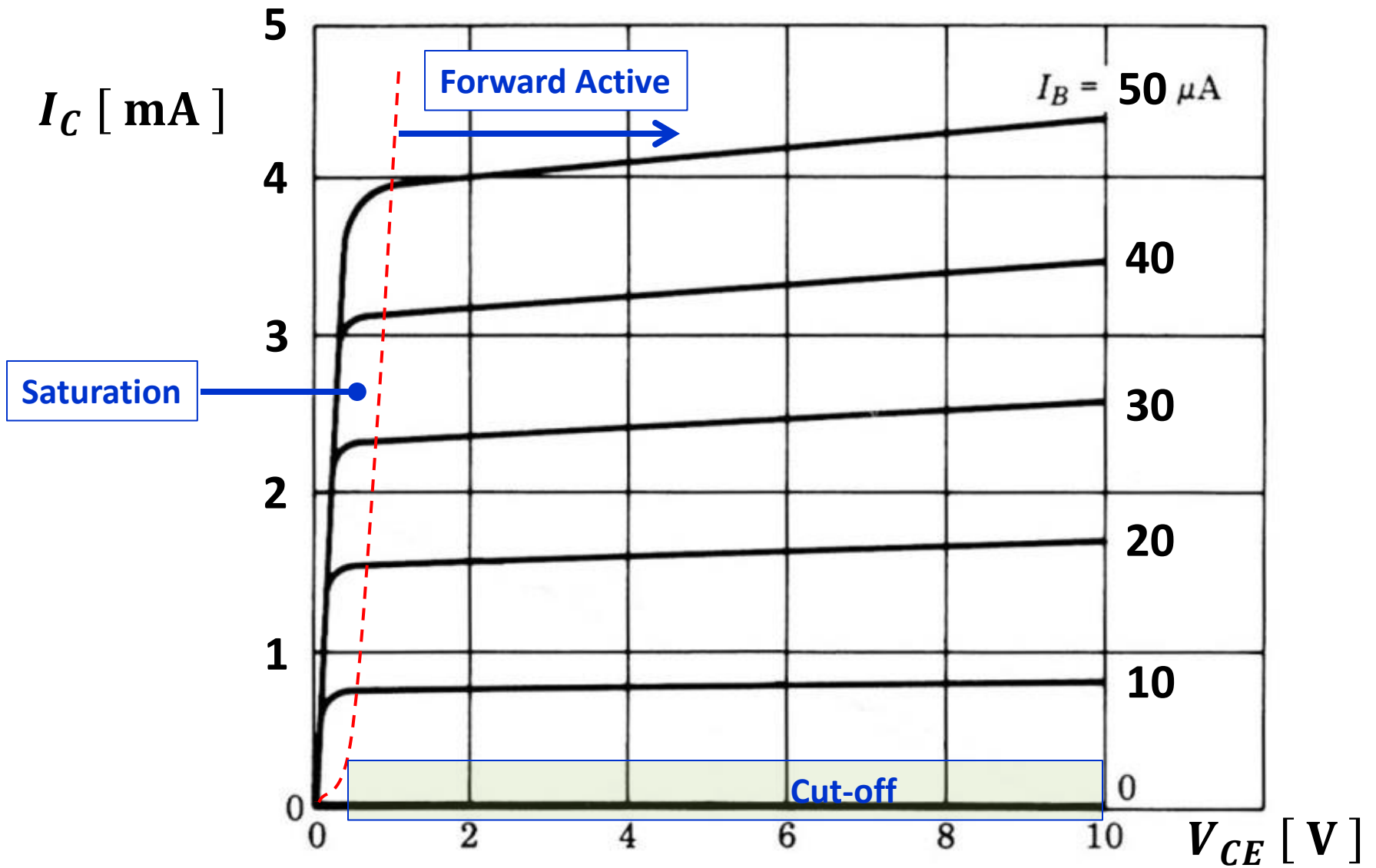


Example of graphical use of BJT I - V curves

$$V_{BE(\text{on})} = 0.7\text{V}$$

$$\beta = 100$$
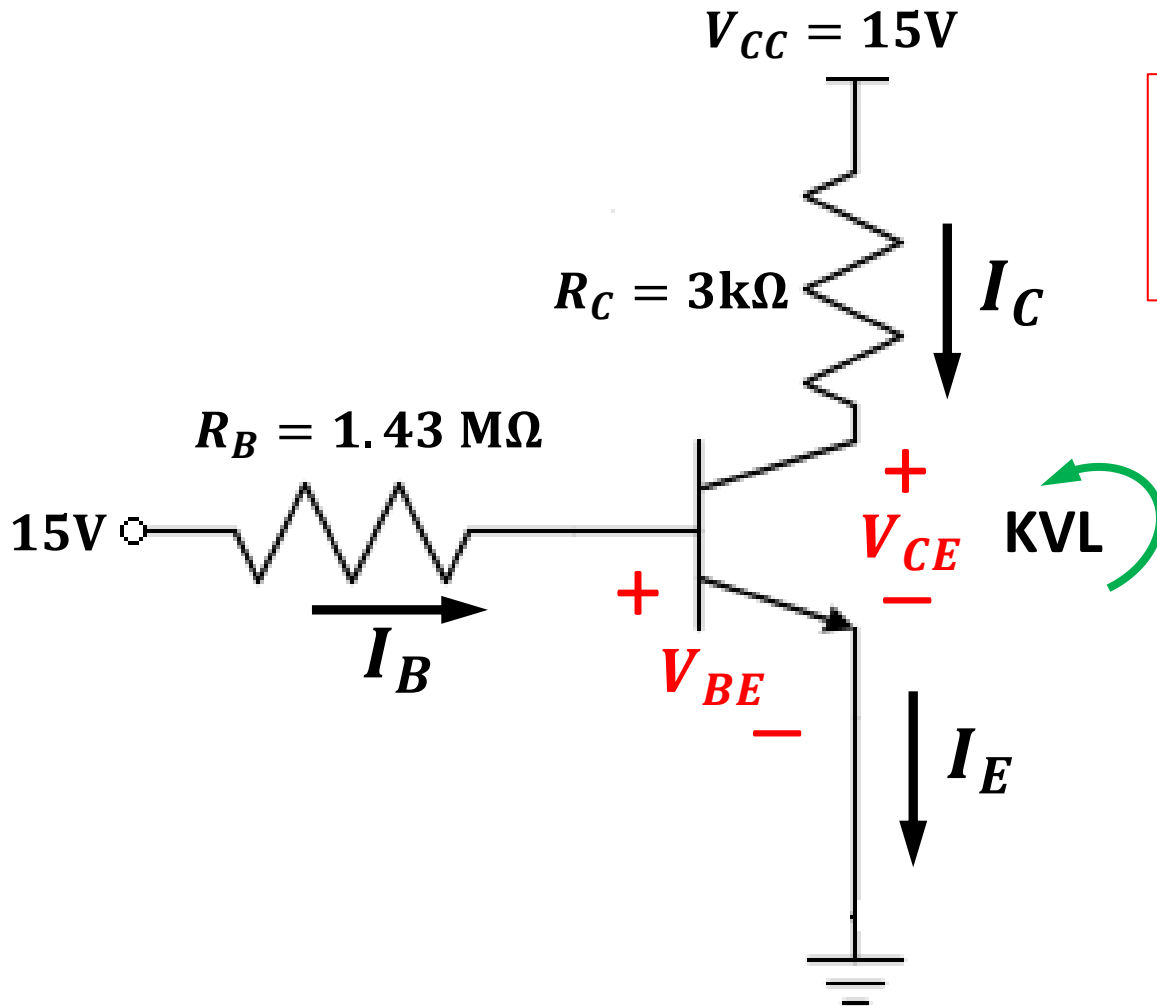
$$\boxed{\text{KVL}} \quad V_{CE} = V_{CC} - I_C R_C$$



Let's write I_C as a function of V_{CE}

Example of graphical use of BJT I - V curves


$$V_{BE(\text{on})} = 0.7\text{V}$$

$$\beta = 100$$

$$\boxed{\text{KVL}} \quad V_{CE} = V_{CC} - I_C R_C$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$
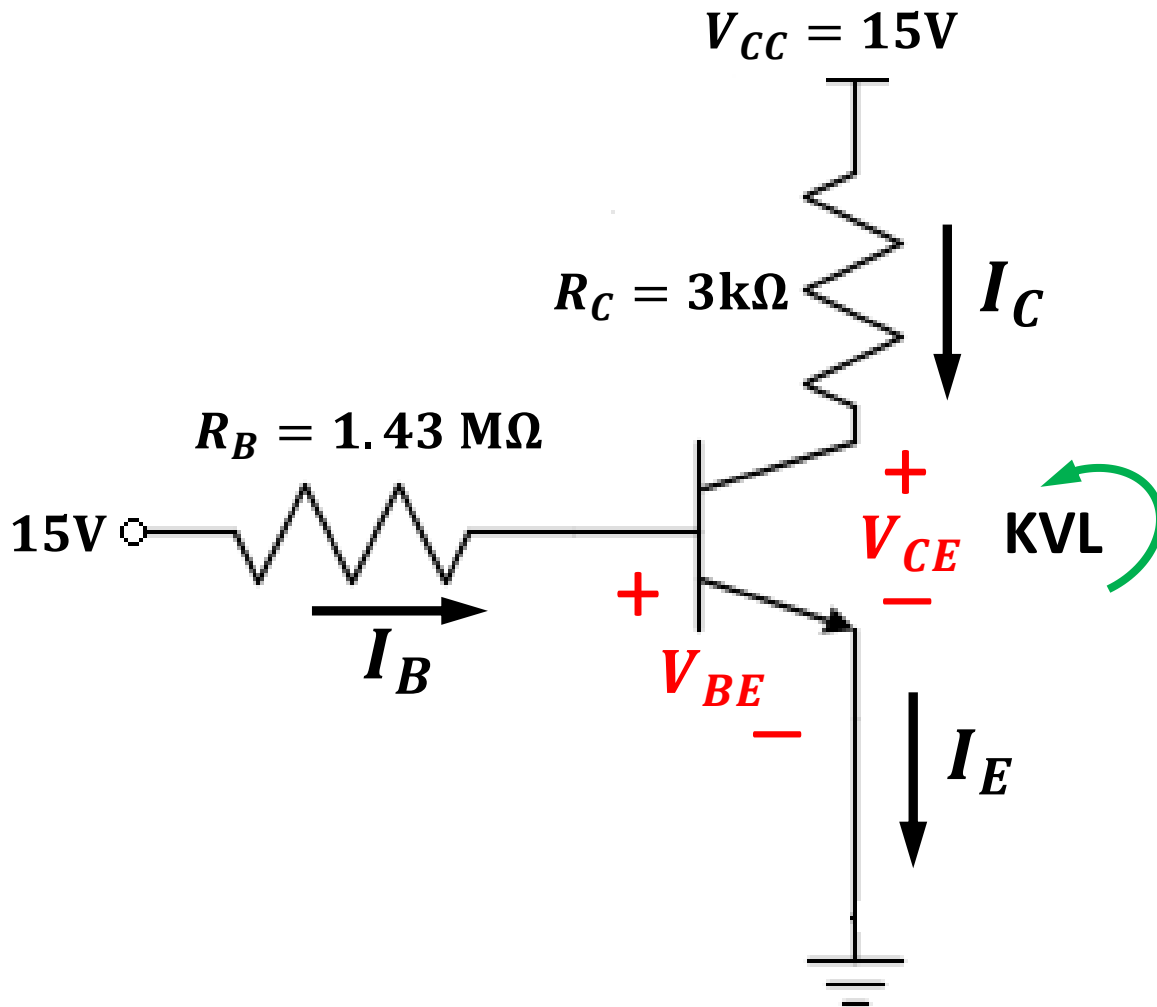
$$I_C = \frac{15 - V_{CE}}{3\text{k}\Omega}$$



Example of graphical use of BJT I - V curves

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$\beta = 100$$

$$\boxed{\text{KVL}} \quad V_{CE} = V_{CC} - I_C R_C$$


$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$I_C = \frac{15 - V_{CE}}{3\text{k}\Omega}$$

$$I_C = 5\text{mA} - \frac{V_{CE}}{3\text{k}\Omega}$$

Equation of a straight line

V_{CE}	I_C
0V	5mA
15V	0mA

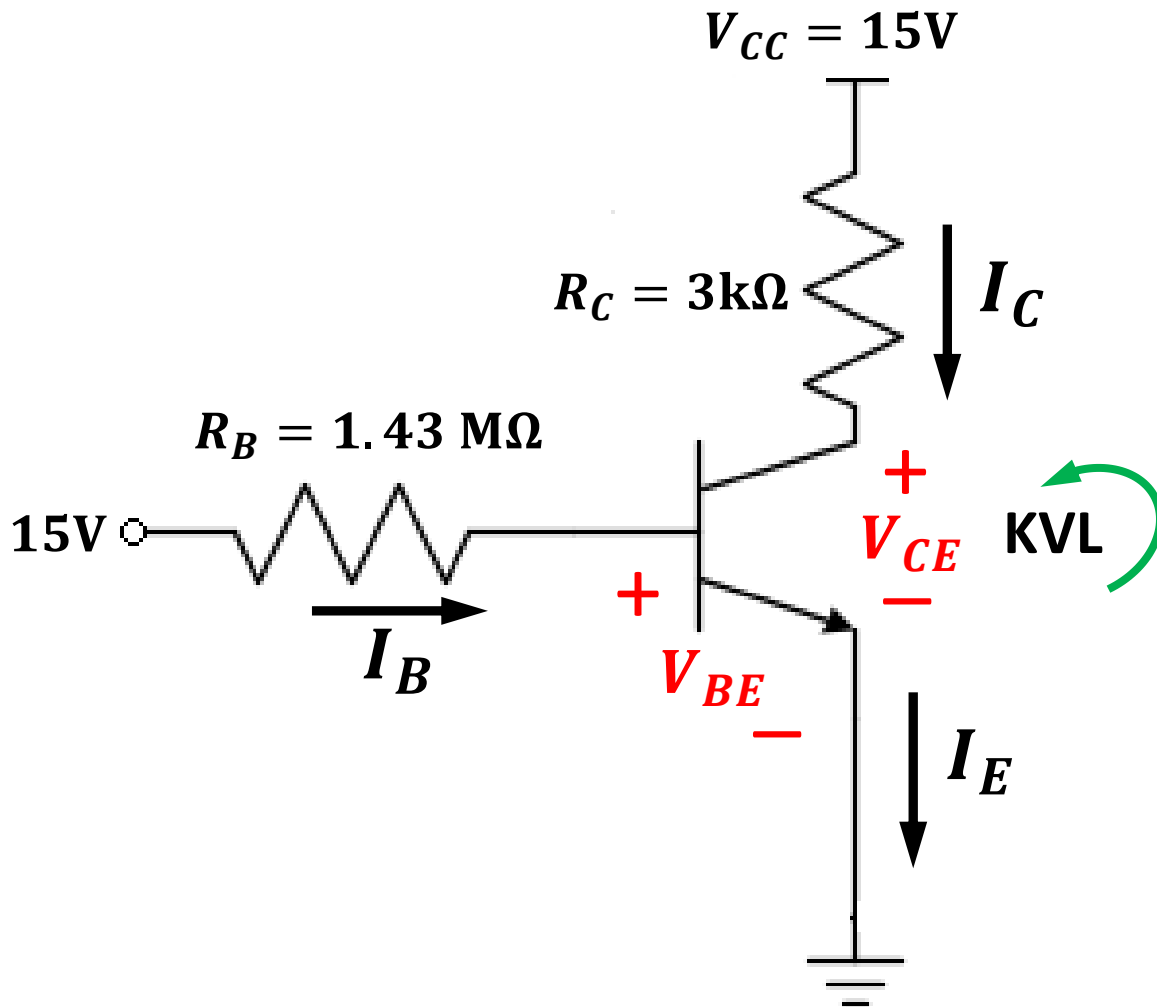


Example of graphical use of BJT I - V curves


$$V_{BE(\text{on})} = 0.7\text{V}$$

$$\beta = 100$$

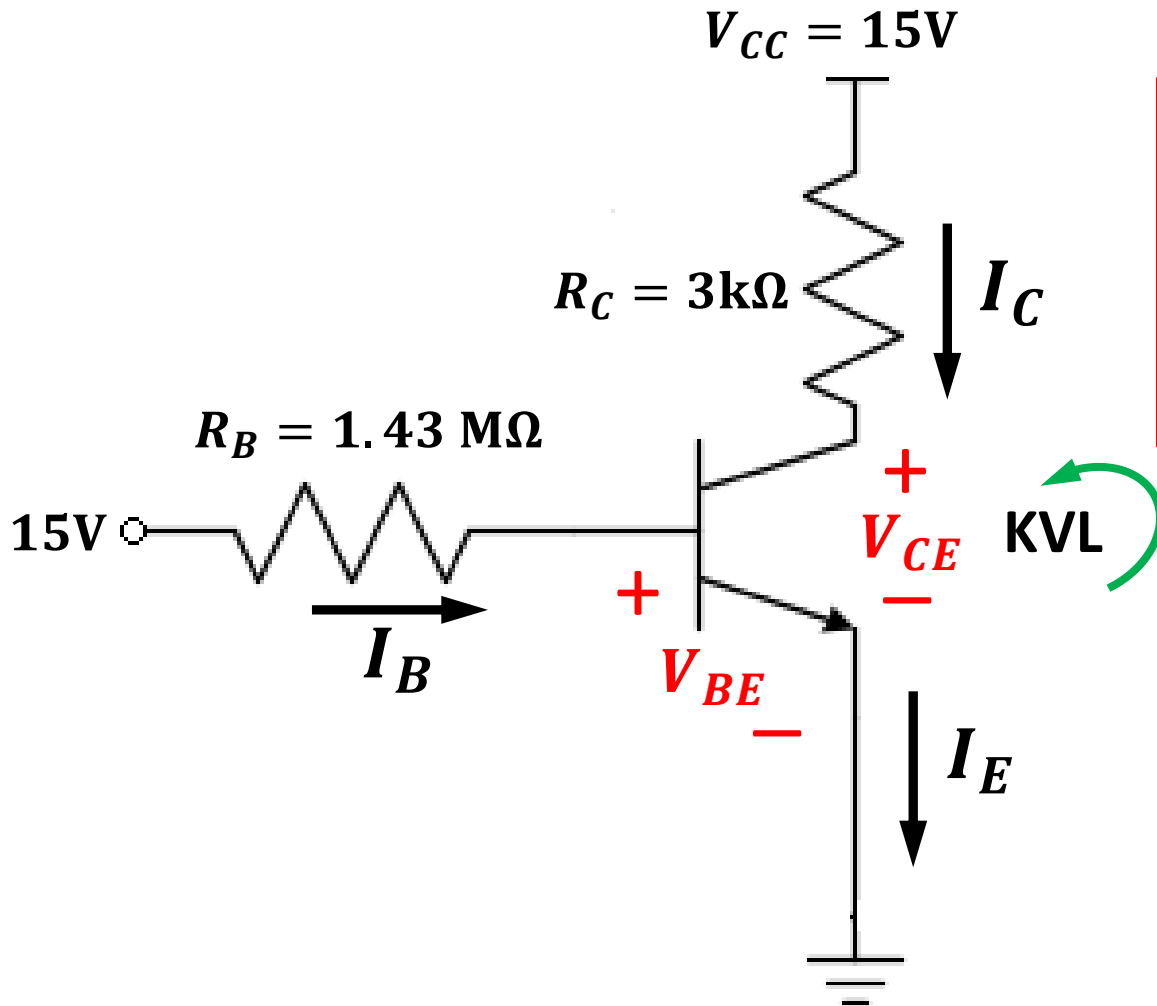
$$I_C = 5\text{mA} - \frac{V_{CE}}{3\text{k}\Omega}$$



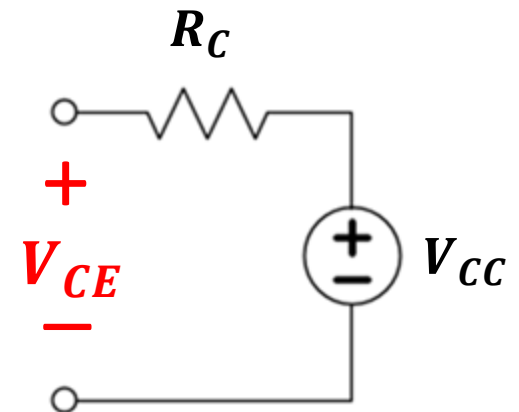
This equation just describes the collector biasing network as a Thevenin source. Here, V_{CE} and I_C depend on the behavior of the BJT, which is a non-linear load



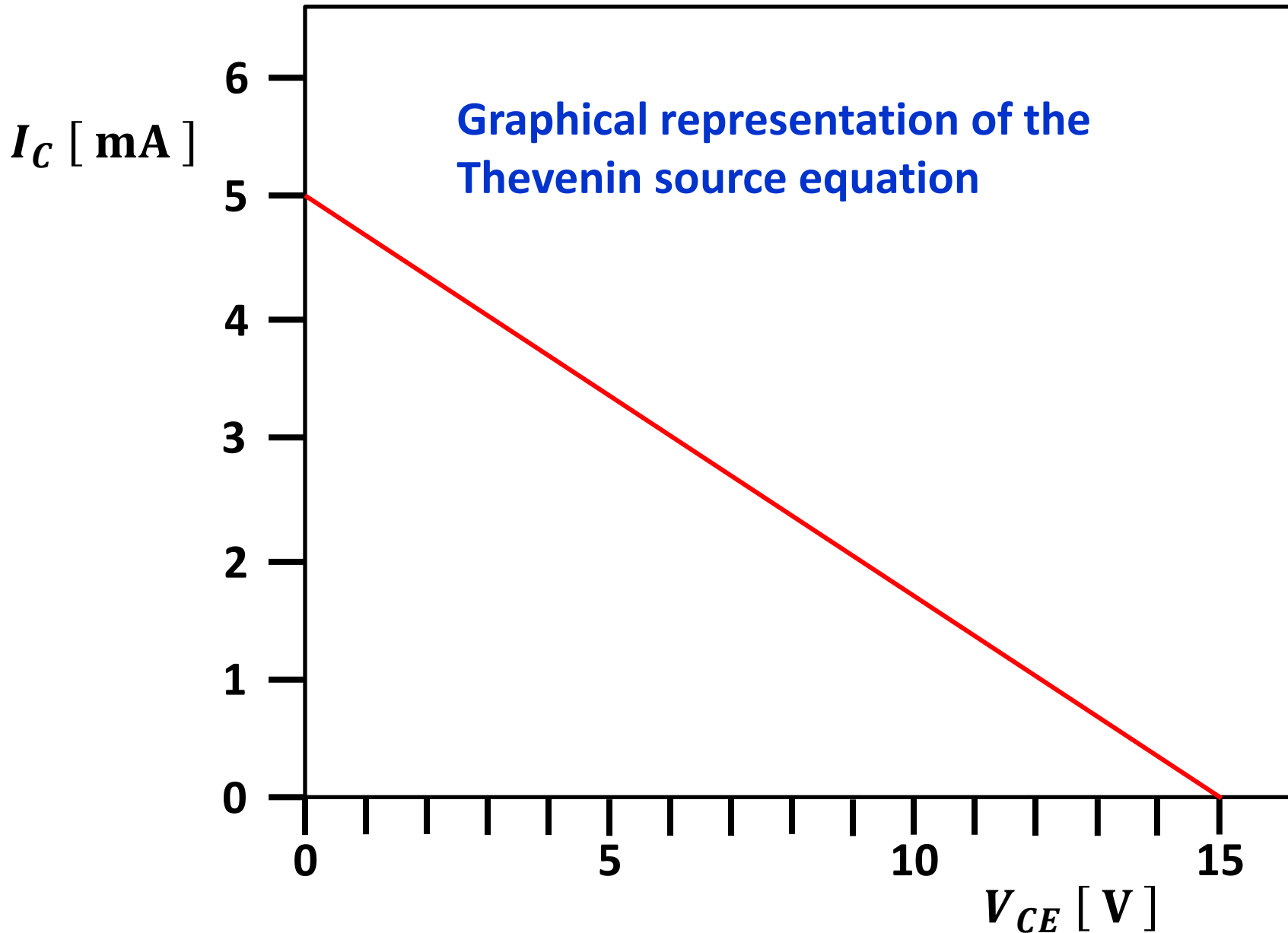
Example of graphical use of BJT I - V curves



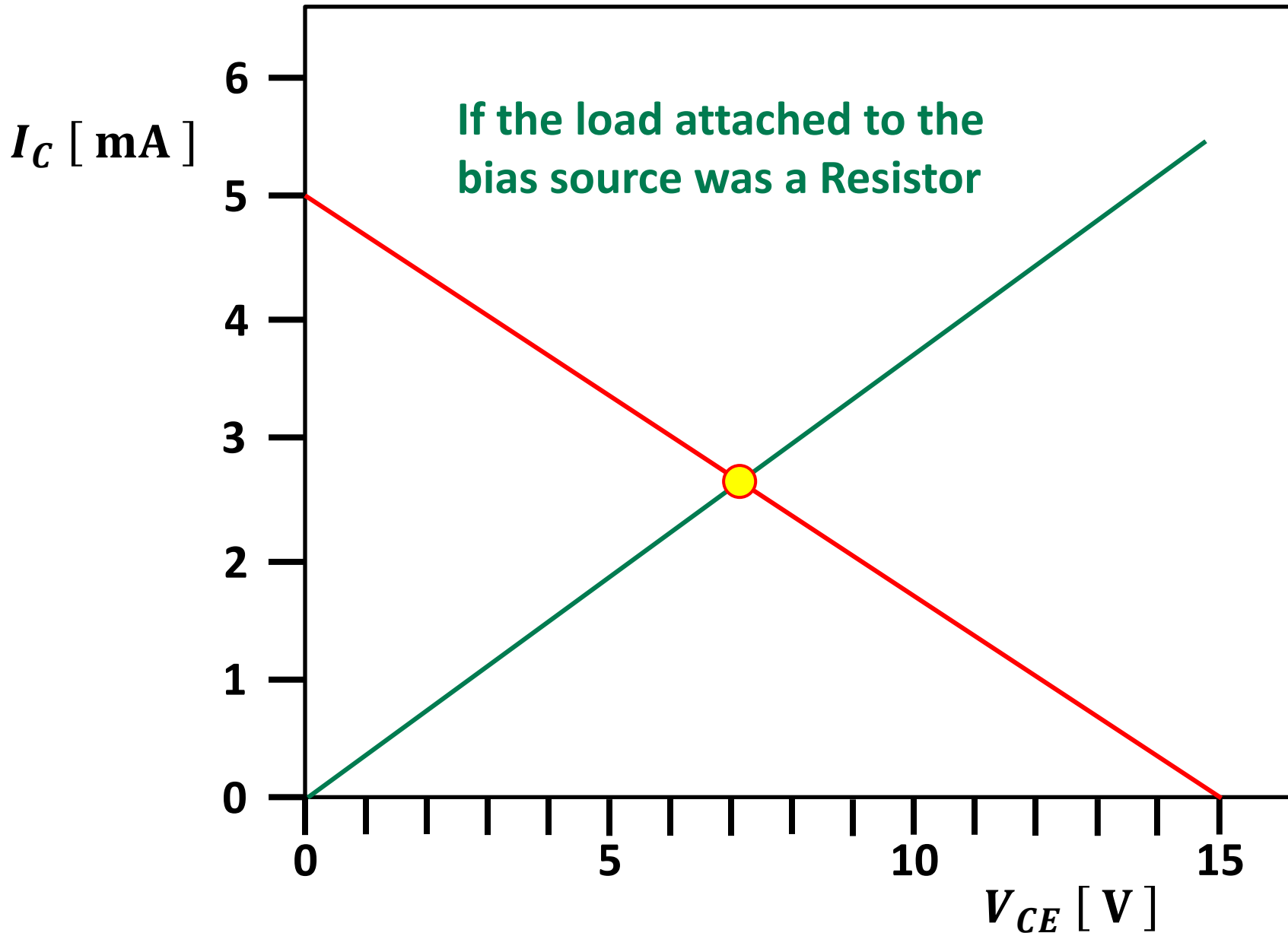Example of graphical use of BJT I - V curves



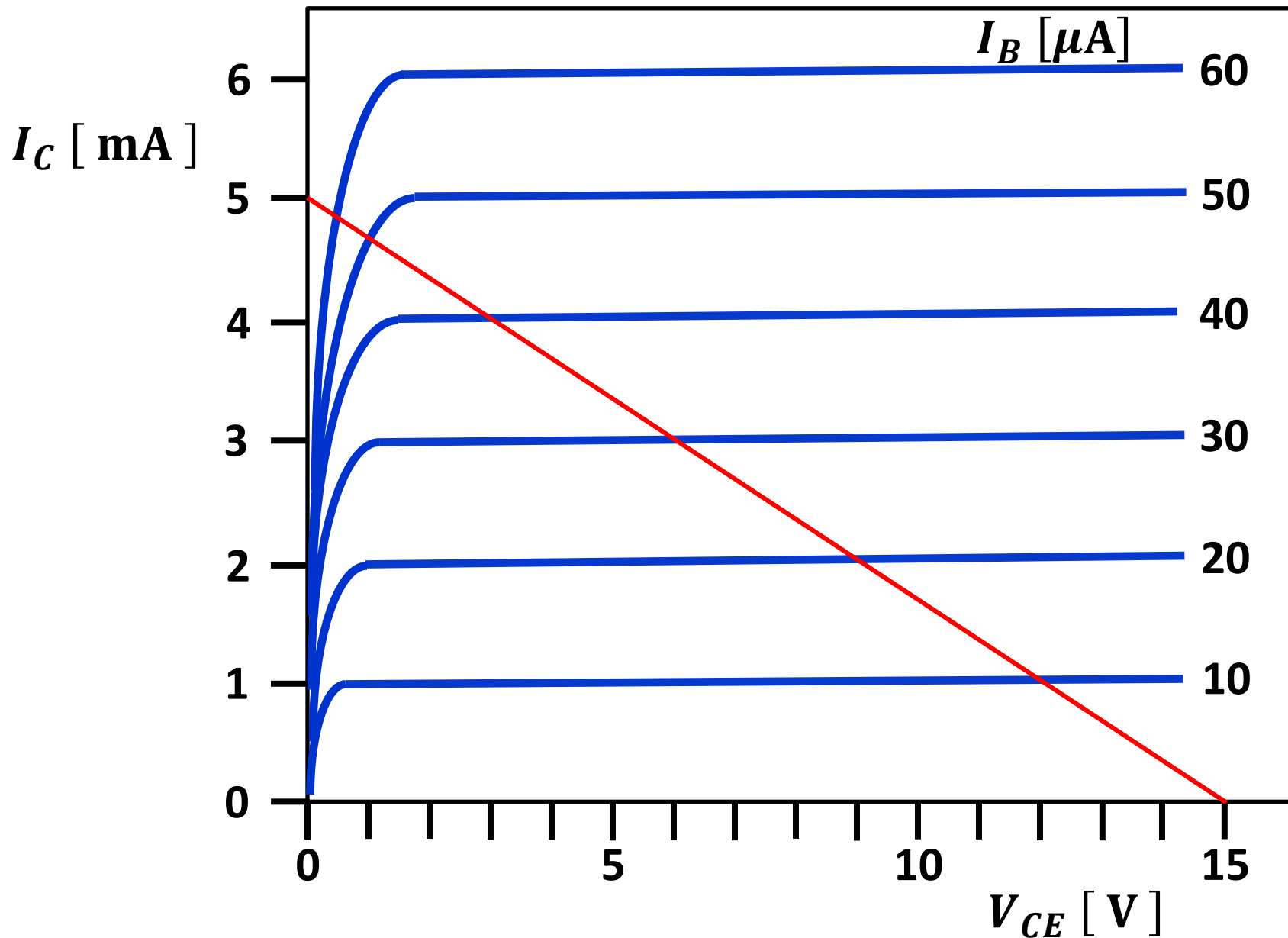Example of graphical use of BJT I - V curves




Example of graphical use of BJT I - V curves

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$\beta = 100$$

Let's examine the Base circuit:

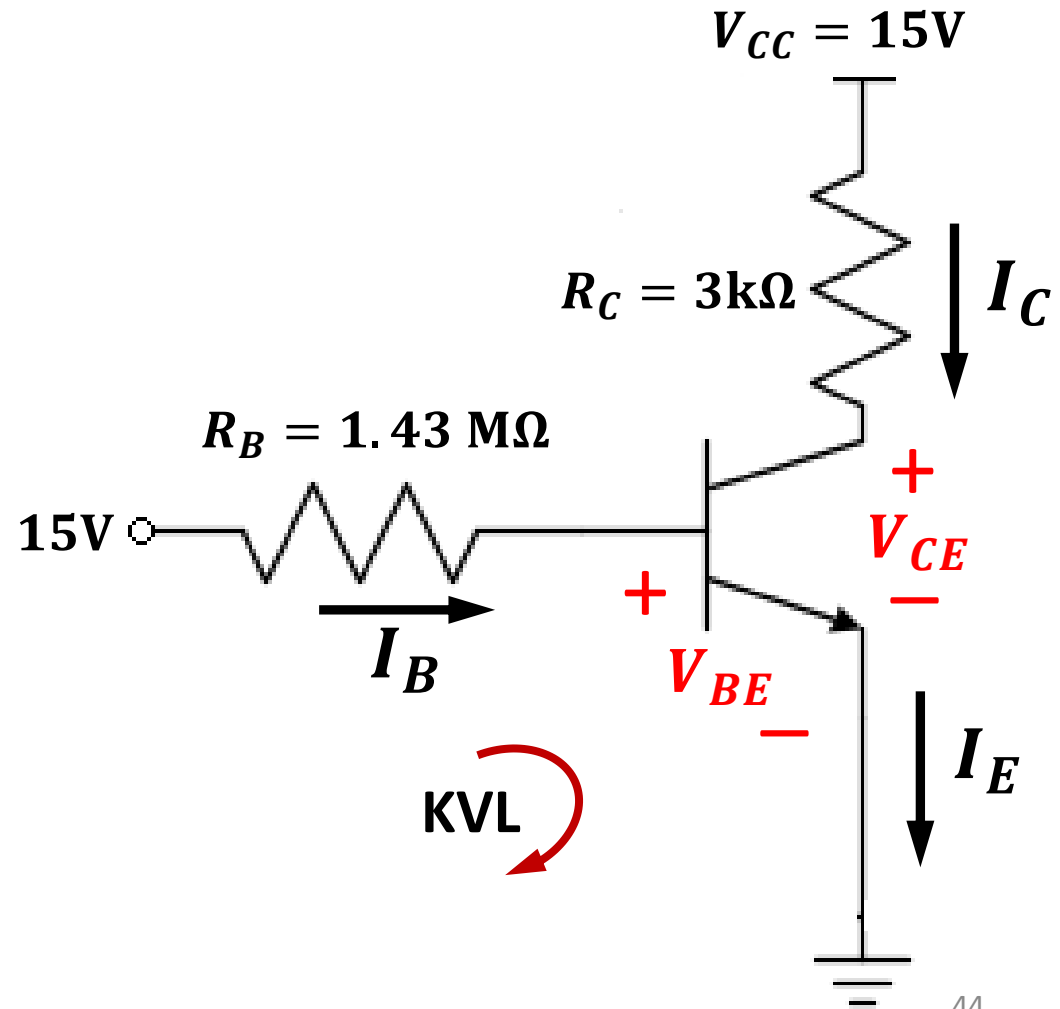

Example of graphical use of BJT I - V curves


$$V_{BE(\text{on})} = 0.7\text{V}$$

$$\beta = 100$$

Let's examine the Base circuit:

$$-15 + I_B R_B + V_{BE} = 0$$
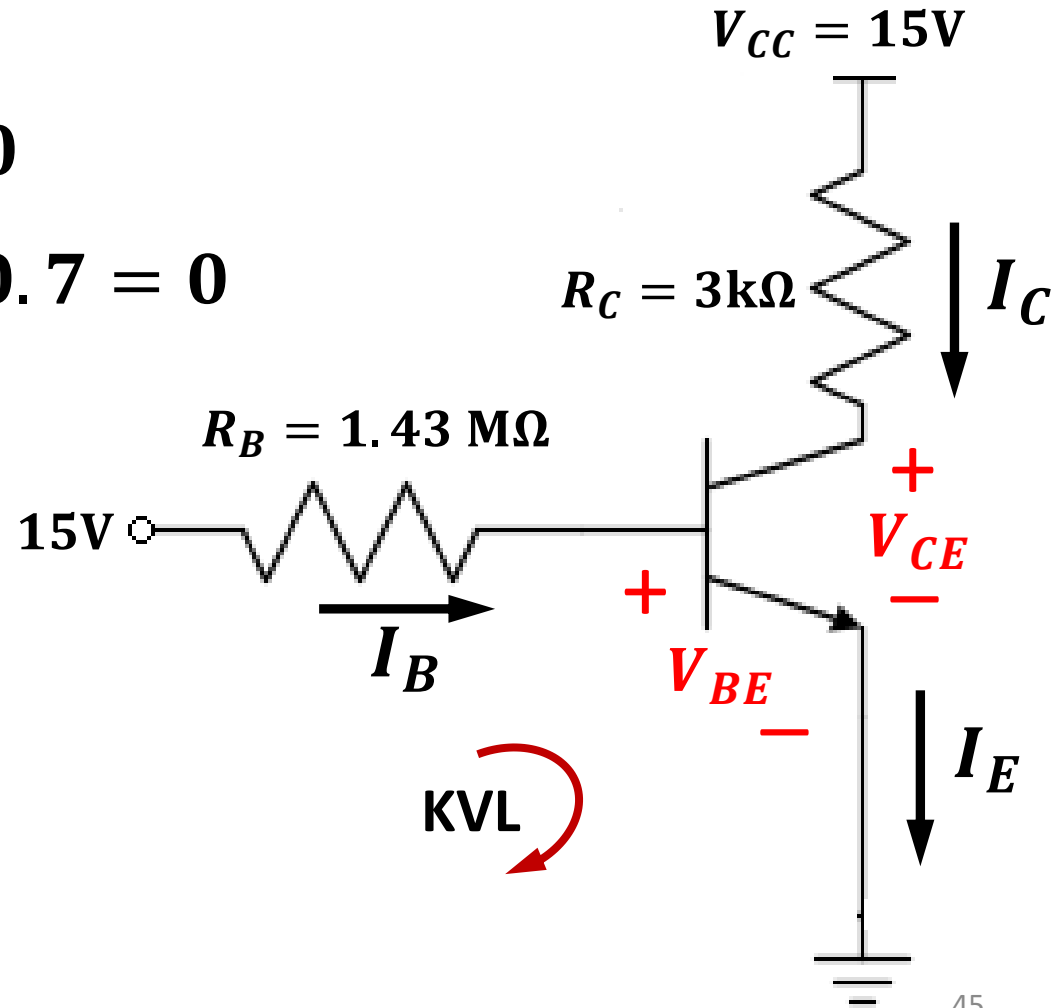
$$-15 + 1.43\text{M} \times I_B + 0.7 = 0$$



Example of graphical use of BJT I - V curves

$$V_{BE(\text{on})} = 0.7\text{V}$$


$$\beta = 100$$

Let's examine the Base circuit:

$$-15 + I_B R_B + V_{BE} = 0$$

$$-15 + 1.43\text{M} \times I_B + 0.7 = 0$$
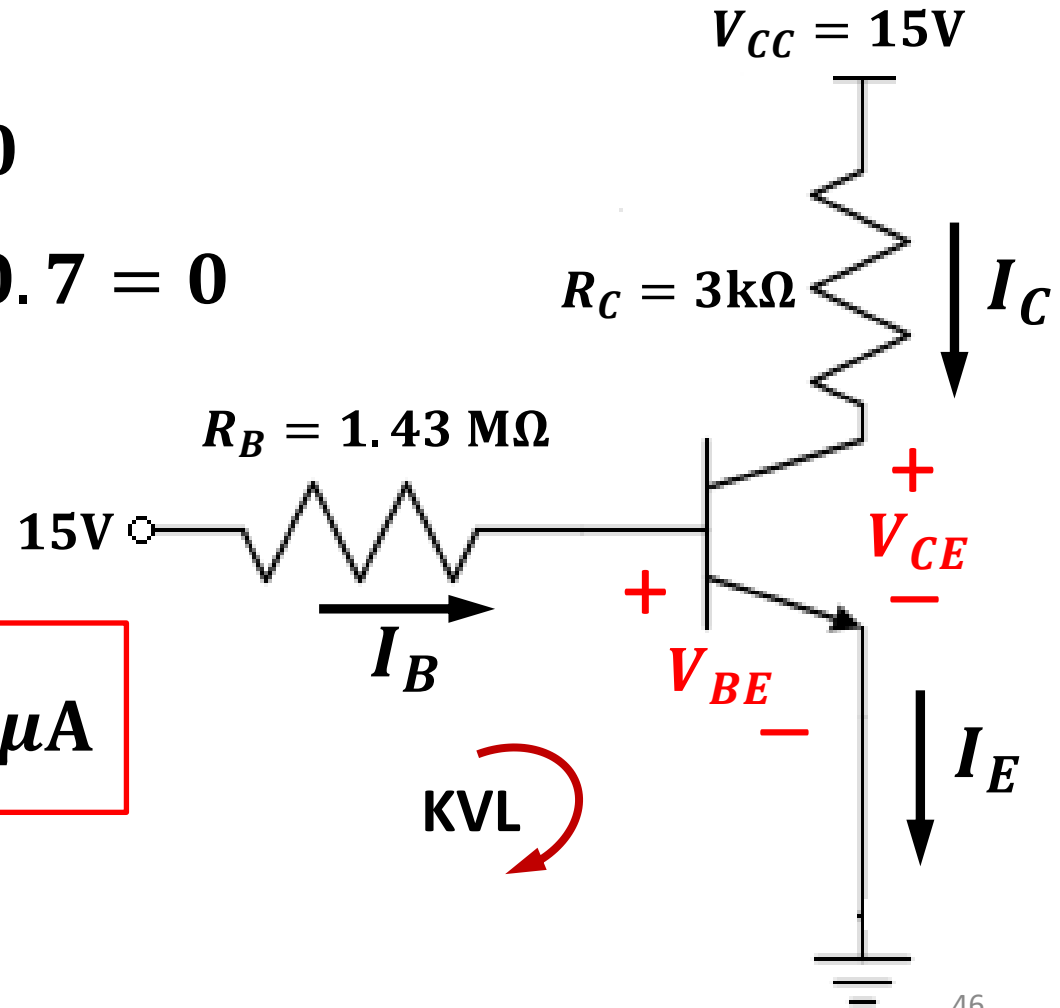
$$I_B = \frac{14.3}{1.43 \times 10^6} = 10\mu\text{A}$$



Example of graphical use of BJT I - V curves

$$V_{BE(\text{on})} = 0.7\text{V}$$

$$\beta = 100$$

Let's examine the Base circuit:

$$-15 + I_B R_B + V_{BE} = 0$$


$$-15 + 1.43\text{M} \times I_B + 0.7 = 0$$

$$I_B = \frac{14.3}{1.43 \times 10^6} = 10\mu\text{A}$$


From the curves

$$I_C = 1\text{mA}$$

$$V_{CE} = 12\text{V}$$

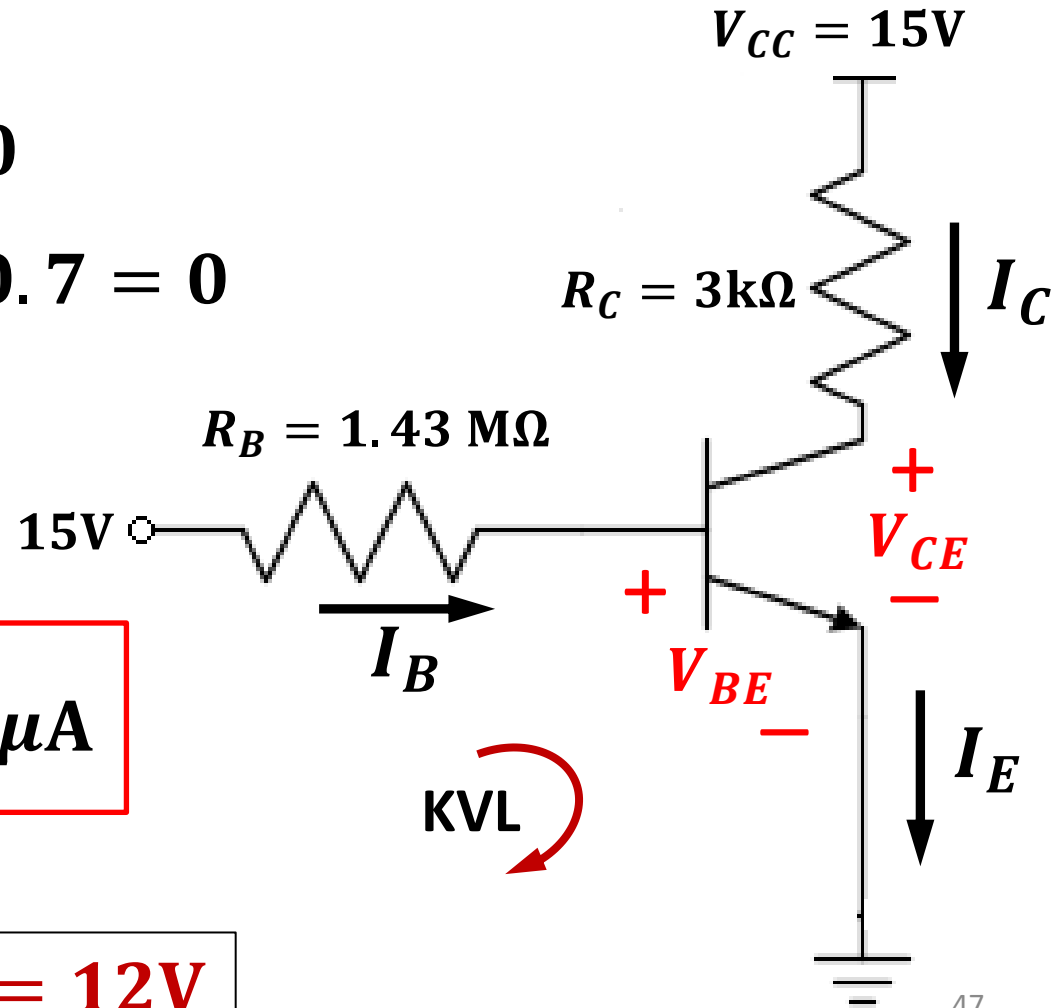

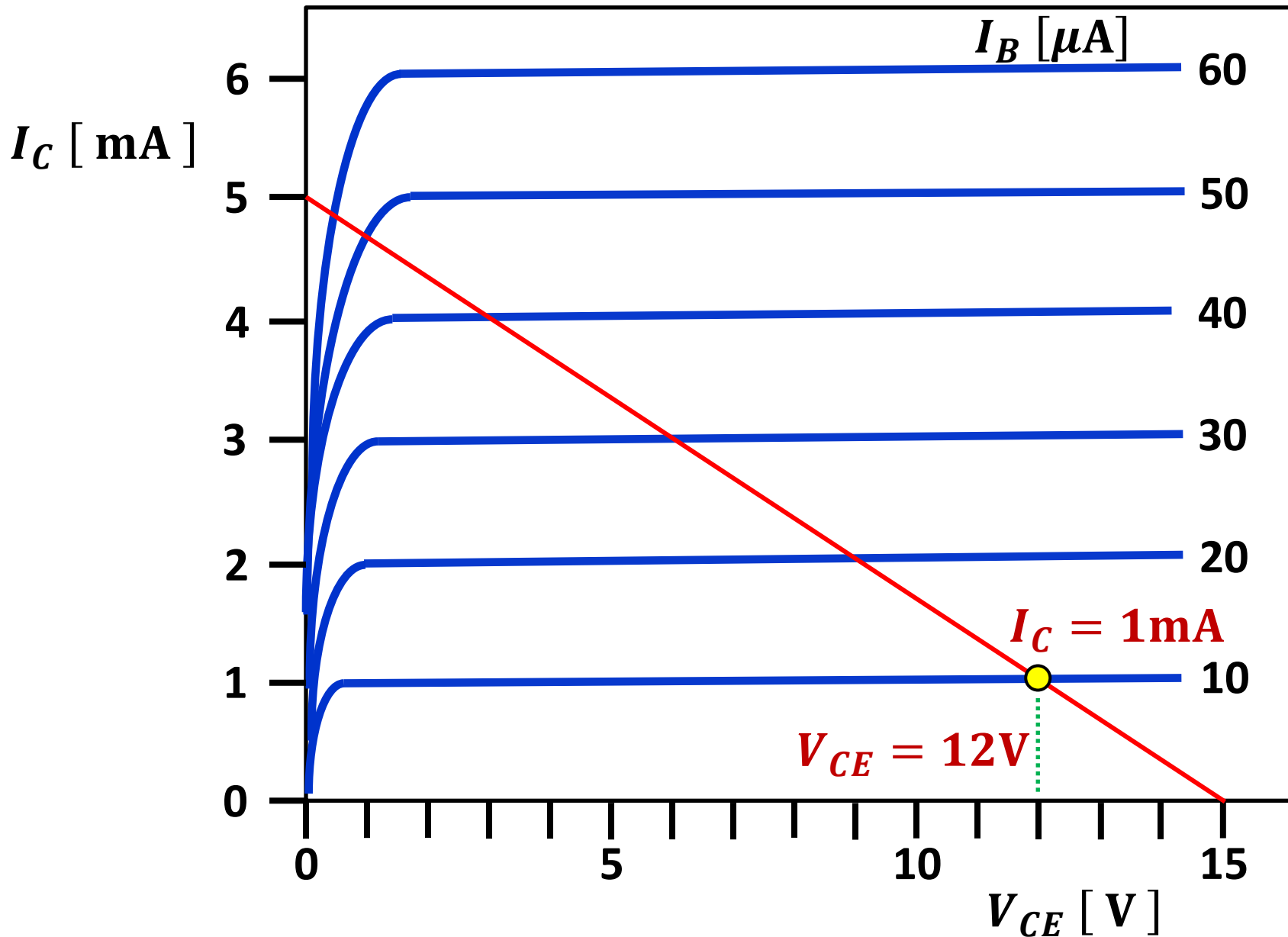Example of graphical use of BJT I - V curves




BJT wired as a diode


$$-V_1 + R_1 I_1 + V_{BE} = 0$$

$$I_1 = \frac{V_1 - V_{BE}}{R_1}$$

As long as $V_1 > V_{BE}(\text{on})$, the BJT is in Forward-Active mode.

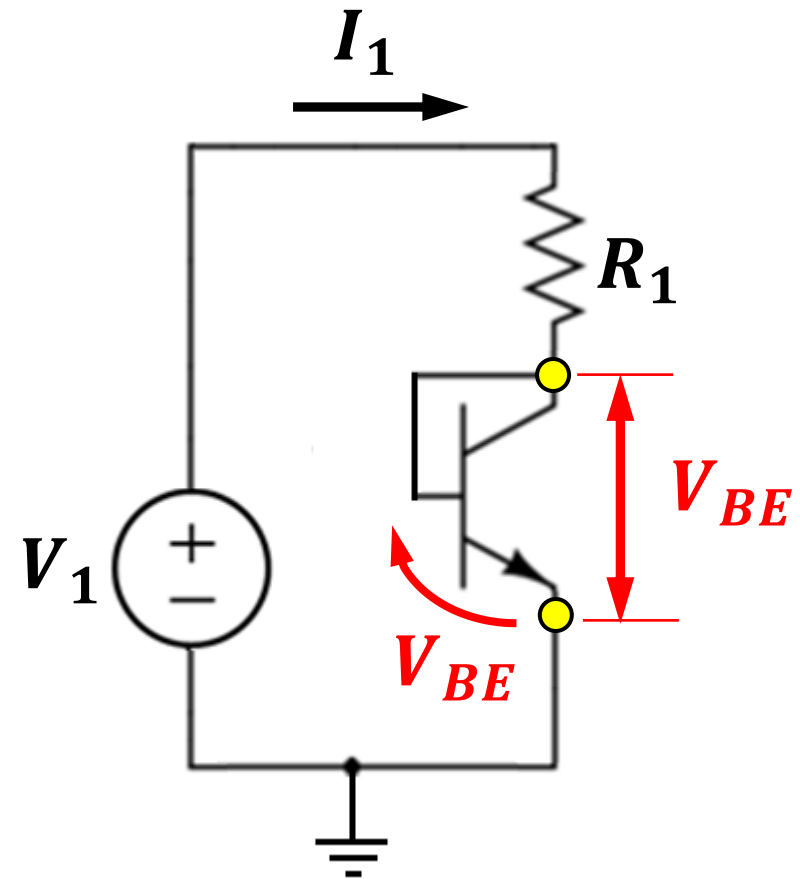BJT's wired as in the diagram, are often adopted in integrated circuits, to obtain ultra-low leakage diodes and for design of circuits which are temperature compensating.



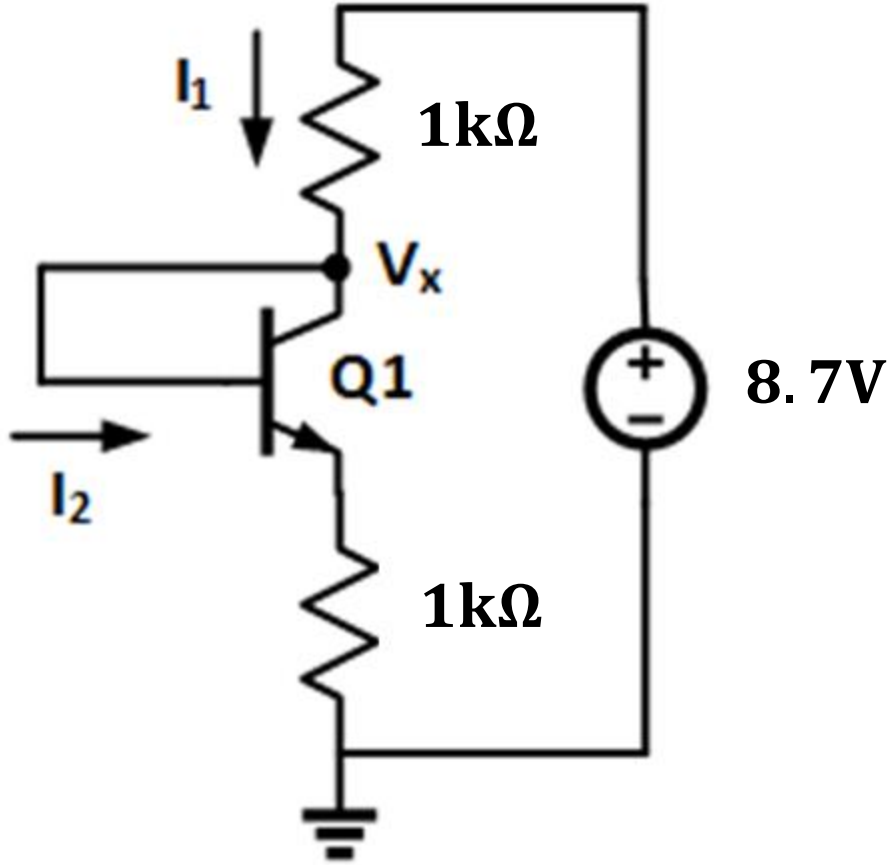


$$\beta = 100$$
$$V_{BE}(on) = 0.7\text{V}$$
$$V_{CE}(sat) = 0.2\text{V}$$

$$\beta = 100$$

$$V_{BE}(on) = 0.7V$$

$$V_{CE}(sat) = 0.2V$$

Assume: BJT ON

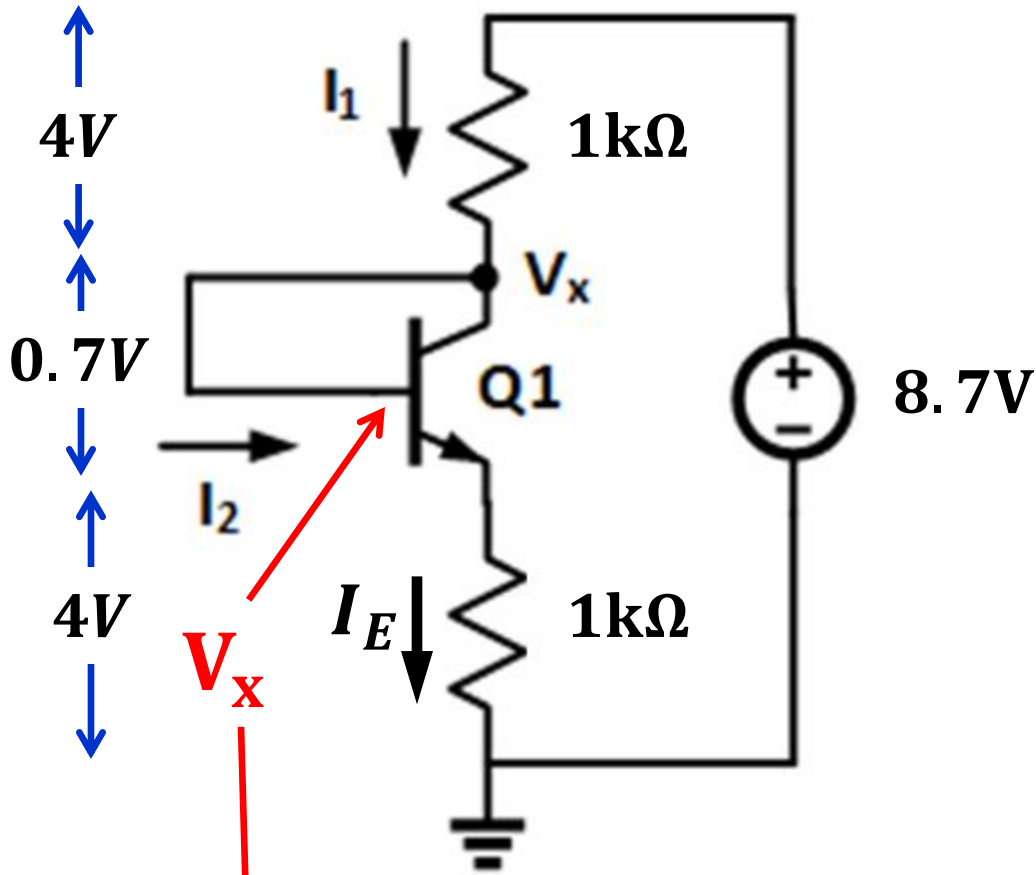


$$V_{BE} = V_{CE} = 0.7V$$

$$V_x = V_{CE} + 4V = 4.7V$$

$$\beta = 100$$

$$V_{BE}(on) = 0.7V$$

$$V_{CE}(sat) = 0.2V$$

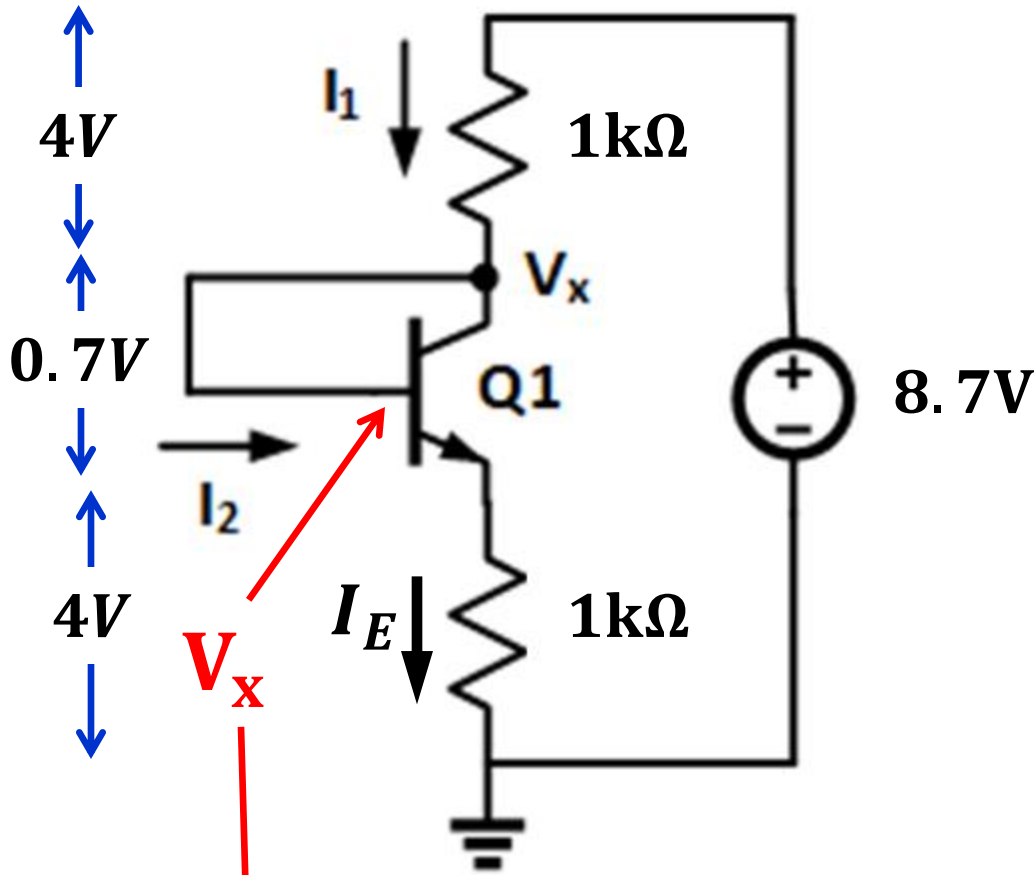

Assume: BJT ON

$$\begin{aligned} I_1 &= I_C + I_2 \\ &= I_C + I_B \end{aligned}$$

$$I_1 = I_E$$

$$\begin{aligned} I_1 &= 1k\Omega \times 4V \\ &= 4mA \end{aligned}$$

$$\begin{aligned} I_E &= 1k\Omega \times 4V \\ &= 4mA \end{aligned}$$

$$V_{BE} = V_{CE} = 0.7V$$

$$V_x = V_{CE} + 4V = 4.7V$$