

# **ECE 205 “Electrical and Electronics Circuits”**


**Spring 2022 – LECTURE 29**

MWF – 12:00pm

**Prof. Umberto Ravaioli**

2062 ECE Building

# Quiz 3 – Score Distribution

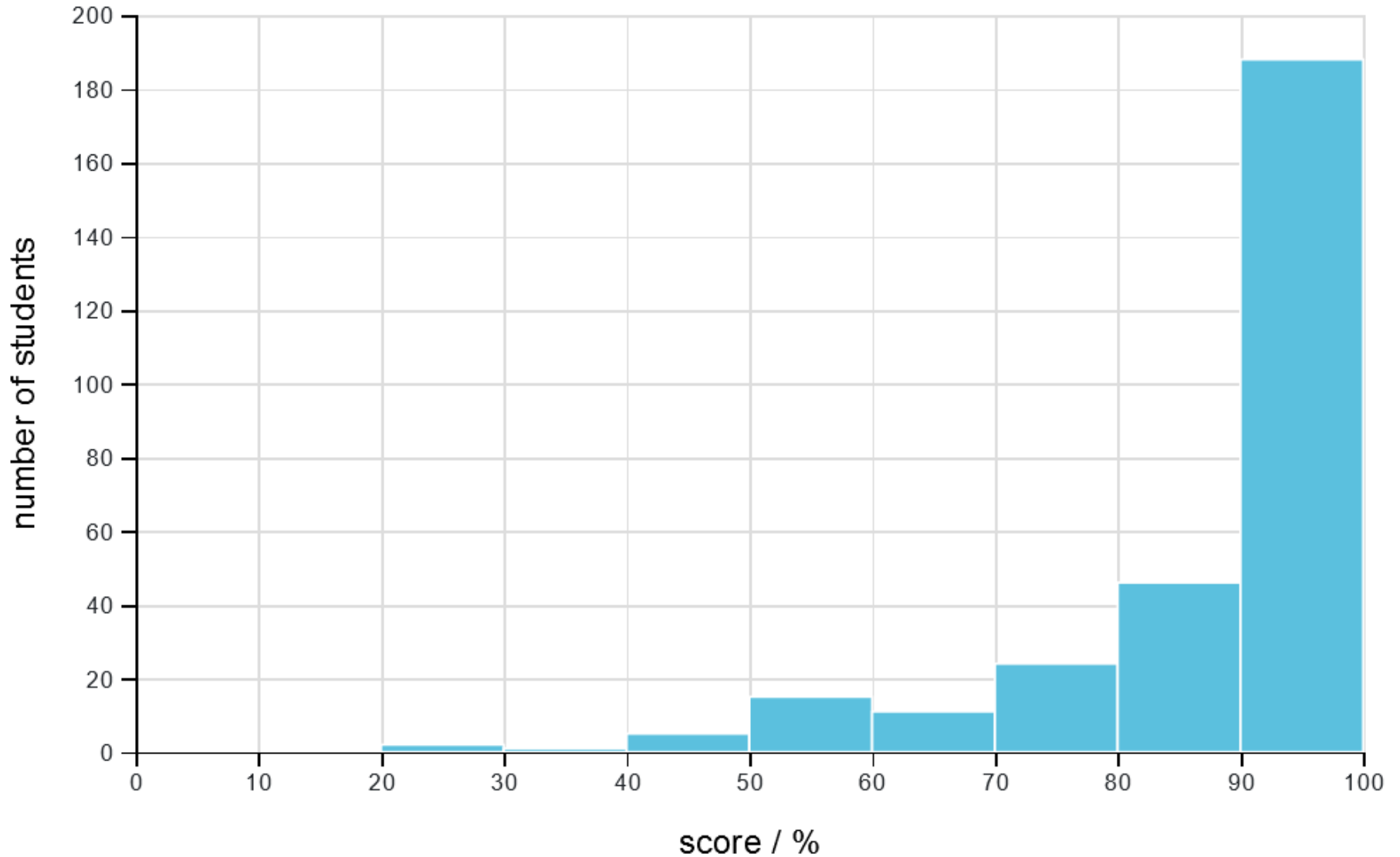

## Quiz 3 – Statistics

Number of students	292
Mean score	88%
Standard deviation	14%
Median score	95%
Minimum score	28%
Maximum score	100%
Number of 0%	0 (0% of class)
Number of 100%	28 (10% of class)

# Lecture 29 – Summary


## Learning Objectives

1. Power in Transistors
2. Binary logic
3. Elementary logic operators
4. Boolean algebra

# Power in Transistors
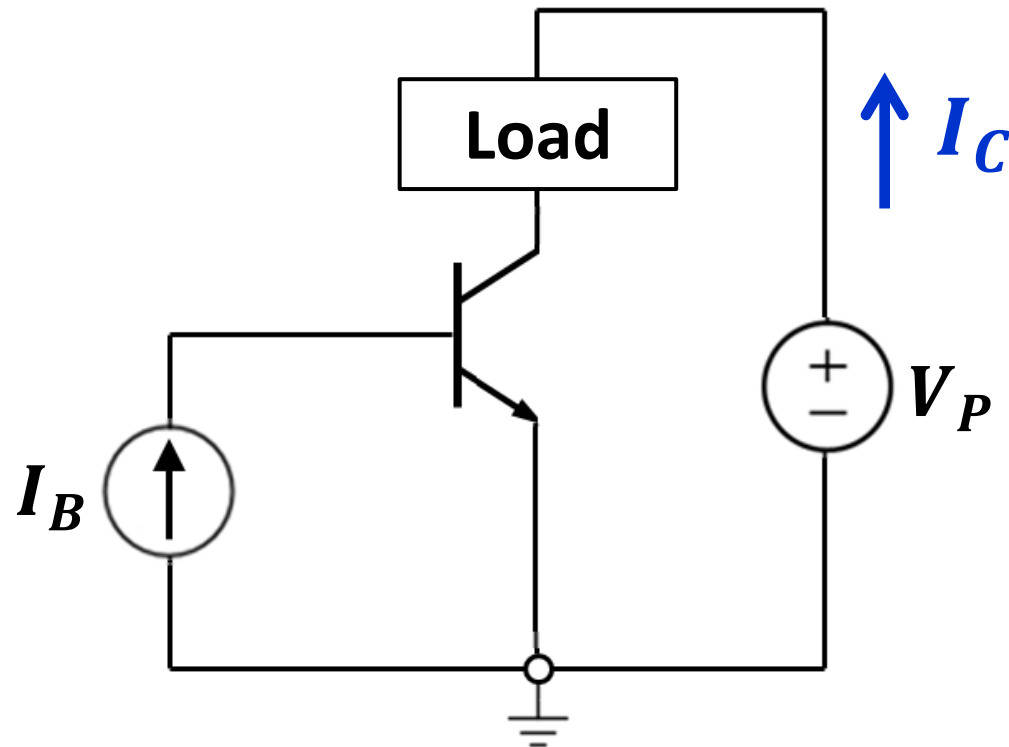
## BJT as a switch


The BJT has important applications as a current controlled “valve” or as a “logic” element



We wish to switch ON and OFF power consumption by the load using a BJT instead of a mechanical switch.
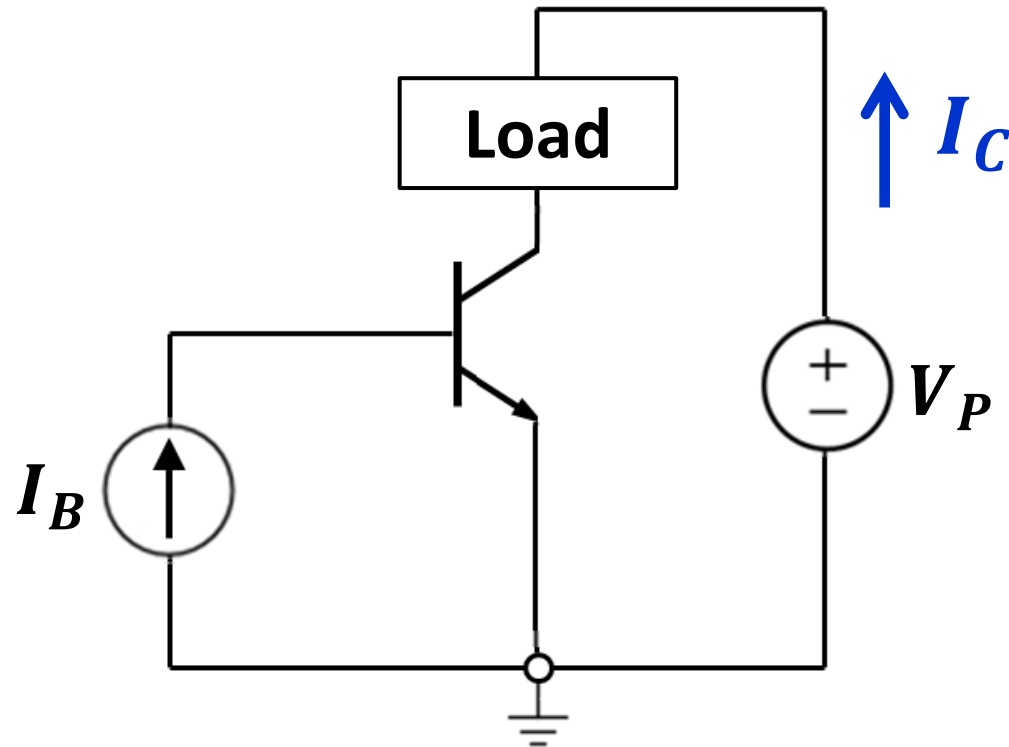
## BJT as a switch

Power consumed by the transistor is lost  
(it is part of operations costs)




$$P_{BJT} = V_{BE} \times I_B + V_{CE} \times I_C$$

## Example: Find $P_{BJT}$ and $P_{Load}$

$$V_{BE(\text{on})} = 0.7\text{V}$$

$$V_{CE(\text{sat})} = 0.2\text{V}$$

$$\beta = 50$$

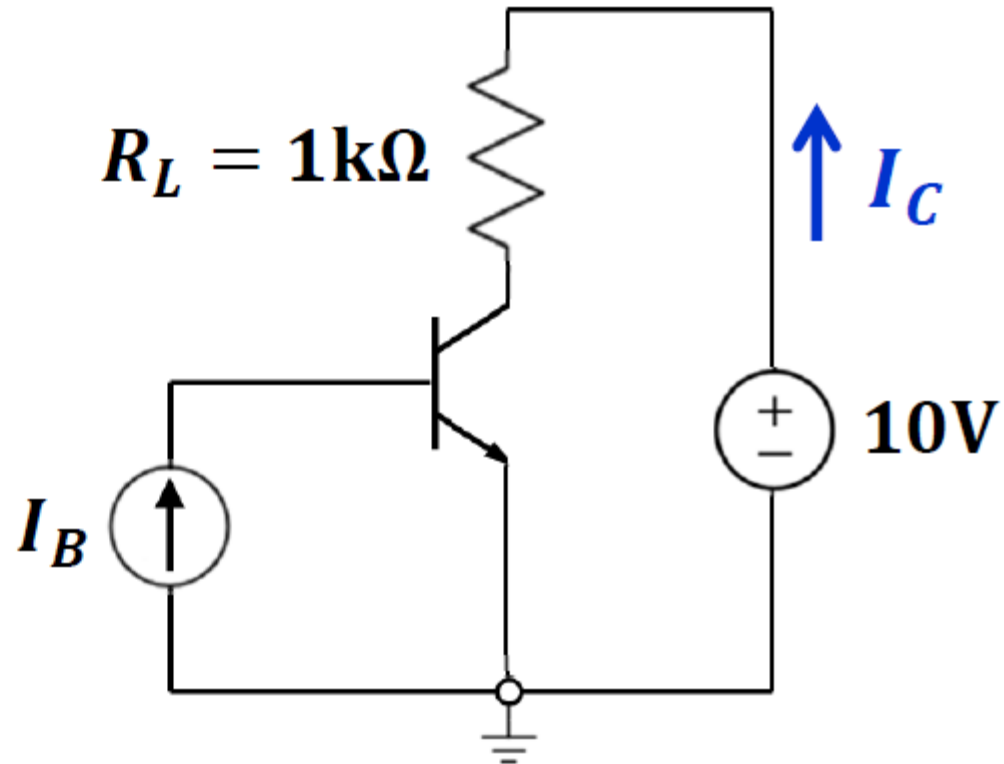

1.  $I_B = 0\text{ mA}$

2.  $I_B = 0.1\text{ mA}$

3.  $I_B = 0.5\text{ mA}$



## Example: Find $P_{BJT}$ and $P_{Load}$

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$


$$\beta = 50$$

1.  $I_B = 0\text{ mA}$

**BJT is OFF**

$$P_{BJT} = 0\text{ W}$$

$$P_{Load} = 0\text{ W}$$

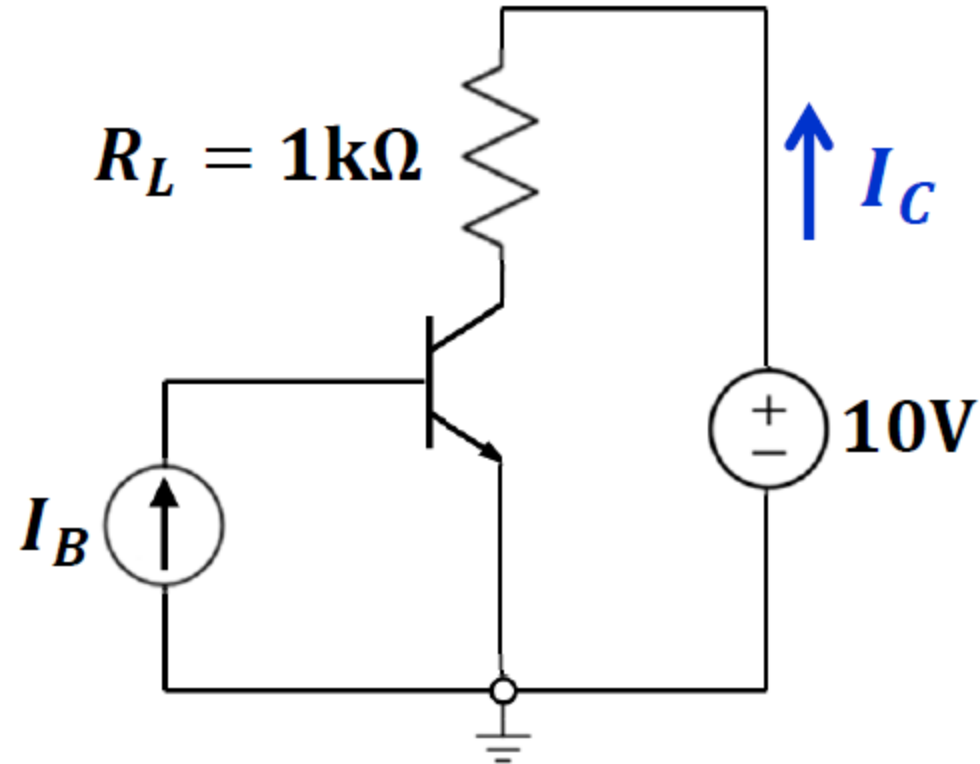

This is the state in which the transistor switch is OPEN and the load is idle. In reality, there will be some current leakage in the non-ideal p-n junctions consuming minute amount of power, but this is negligible in circuits with a small number of transistors.

**Now we CLOSE the switch, to let current flow through the load  $R_L$ .**

**Which state of operation should we prefer for the BJT to be ON, in order to minimize the power consumed by the switch itself?**

## Example: Find $P_{BJT}$ and $P_{Load}$

$$V_{BE}(\text{on}) = 0.7\text{V}$$

$$V_{CE}(\text{sat}) = 0.2\text{V}$$

$$\beta = 50$$

$$2. \quad I_B = 0.1 \text{ mA}$$

Assume Forward Active mode


$$I_C = \beta I_B = 5 \text{ mA}$$

$$V_{CE} = 10 - I_C R_L = 5\text{V}$$

$$P_{BJT} = V_{BE} \times I_B + V_{CE} \times I_C = 0.7 \times 0.1 \text{ m} + 5 \times 5 \text{ m}$$

$$P_{BJT} = 25.07 \text{ mW}$$
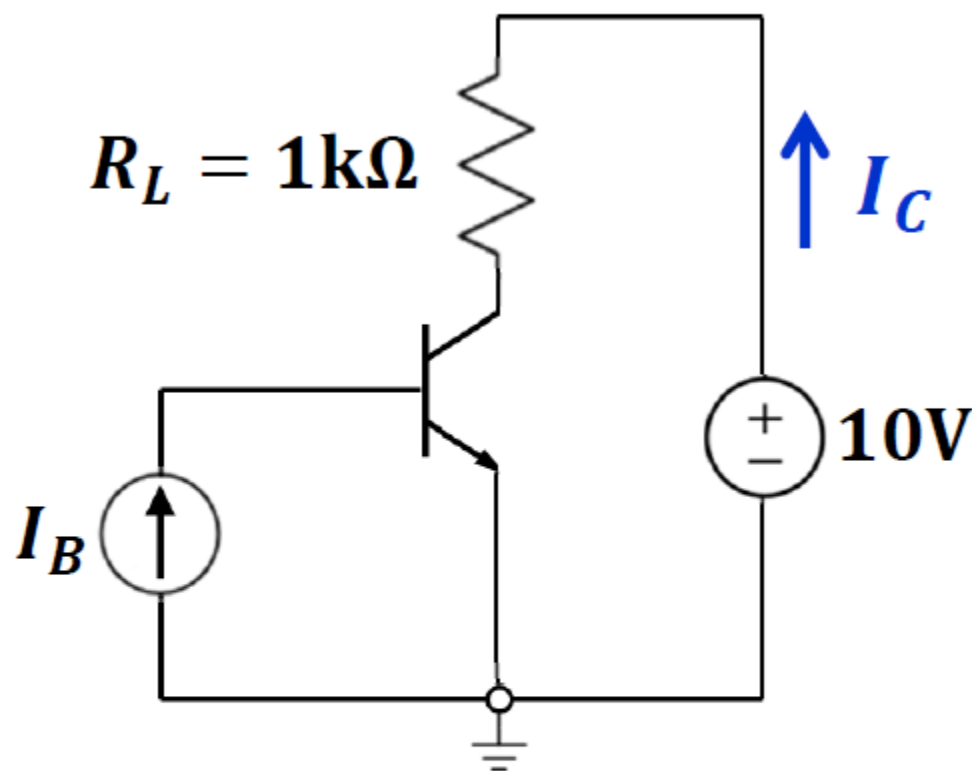
$$P_{Load} = I_C^2 R_L = (5 \text{ mA})^2 \times 1 \text{ k}\Omega = 25 \text{ mW}$$



## Example: Find $P_{BJT}$ and $P_{Load}$

$$V_{BE(\text{on})} = 0.7\text{V}$$


$$V_{CE(\text{sat})} = 0.2\text{V}$$

$$\beta = 50$$

### 3. $I_B = 0.5\text{ mA}$

BJT is in Saturation

$$I_C(\text{sat}) = 9.8\text{ mA}$$

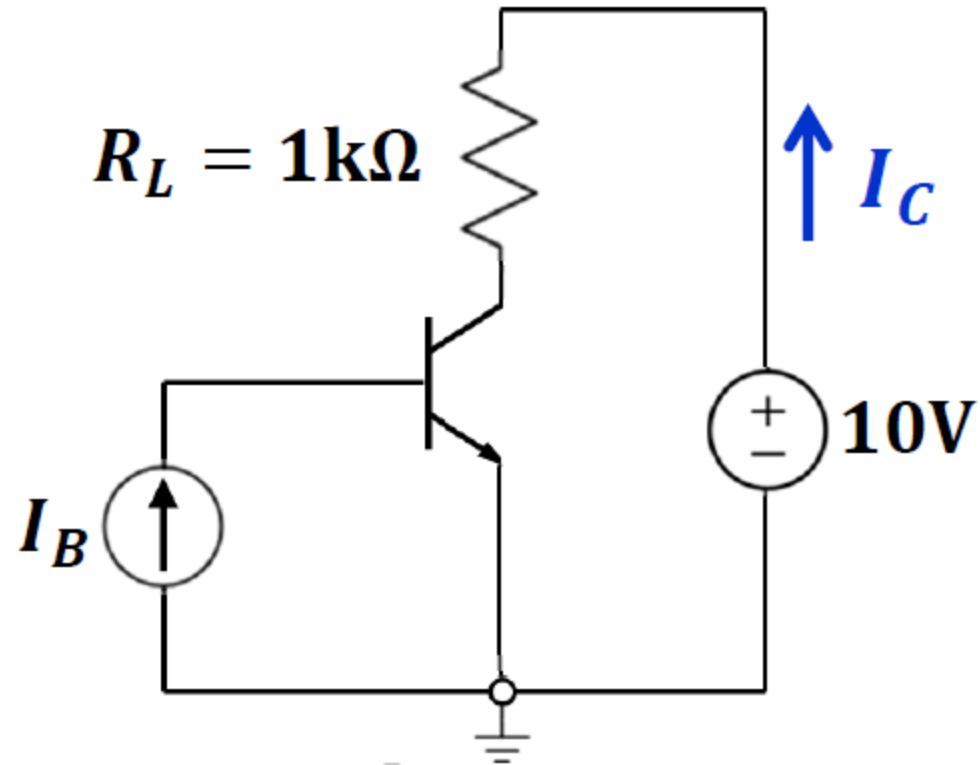

$$P_{BJT} = 0.7 \times 0.5\text{ m} + 0.2 \times 9.8\text{ m} = 2.31\text{ mW}$$

$$P_{Load} = I_C^2 R_L = (9.8\text{ mA})^2 \times 1\text{ k}\Omega = 96.04\text{ mW}$$

**BJT is most efficient as a switch in Saturation**

# Introduction to Digital Logic

# Binary Computer Logic

Logic is a science which studies the reasoning needed to reach a conclusion or make a decision.

Computer operations are based on a form of logic which considers two possible states: **TRUE** or **FALSE**.

In a computer, these states are encoded into numbers.

For instance:

**FALSE = 0**

**TRUE = 1**

# Binary Number System

The total number of digits, used to express numbers, is called the “base”. We normally use the base-10 (or decimal) number system, with digits from 0 to 9.

Similarly, the complete number system can be constructed with a base of two numbers: 0 and 1. This is the base-2 or “binary” system.


## Examples:

DECIMAL	BINARY
5	101
13	1101
24	11000
100	1100100

↑ ↑ ↑  
64 32 4
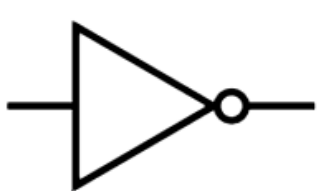
# Logic Operations


Binary logic is based on a set of **seven** elementary logical operations with two inputs and one output. The elements which accomplish these operations are called “Logic Gates”. They are represented with the symbols below in a **logic circuit**.




**NOT**




**AND**

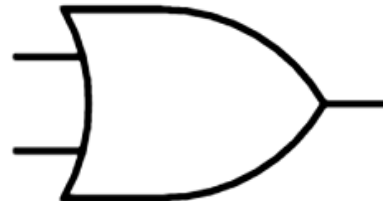

**OR**

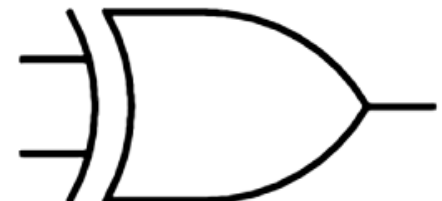


**XOR**

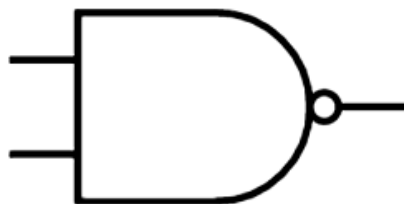

**NAND**



**NOR**

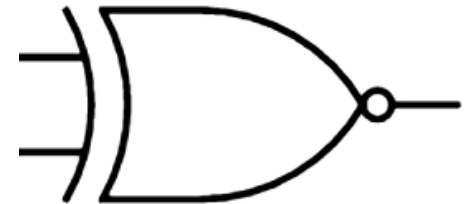

**XNOR**




# NOT

(inverter)

INPUT


OUTPUT

TRUTH TABLE

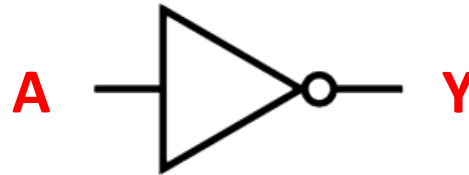


A	Y
0	1
1	0

# AND

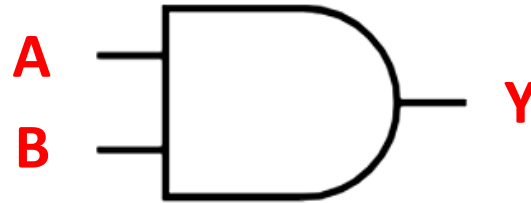

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

# OR

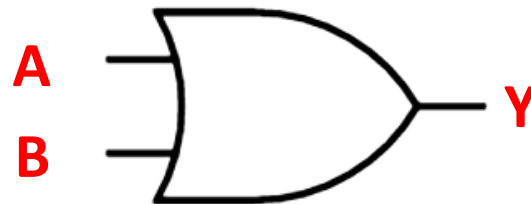


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

# NAND

INPUT


OUTPUT

TRUTH TABLE

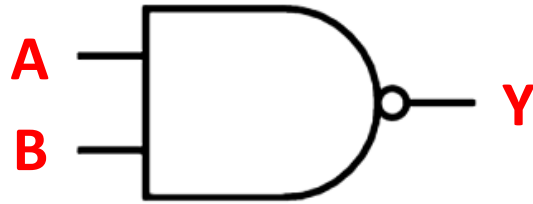

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

# NOR

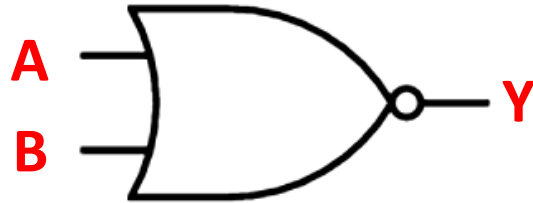

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


INPUT

OUTPUT

TRUTH TABLE

# XOR

(exclusive OR)

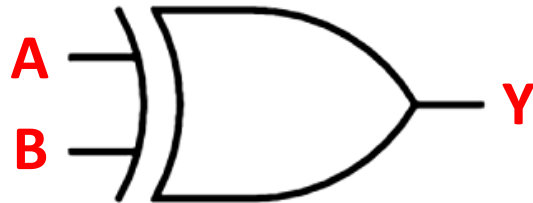

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

# XNOR



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

# Boolean Algebra

Logic operations can be represented with formulas, using a special formalism called Boolean Algebra. The following table shows the Boolean notation.

OPERATOR	BOOLEAN ALGEBRA
NOT	$Y = \bar{A}$
AND	$Y = A B$
OR	$Y = A + B$
NAND	$Y = \overline{A B}$
NOR	$Y = \overline{A + B}$
XOR	$Y = A \oplus B$
XNOR	$Y = \overline{A \oplus B}$

**NOTE:** Some authors use  $A.B$  for  $A B$  and  $A'$  for  $\bar{A}$


# Boolean Algebra Simplifications Table

When a logic circuit is designed to obtain the desired behavior, it can be simplified by using the following laws to minimize the number of gates.

LAWS	AND	OR
Identity	$1 A = A$	$0 + A = A$
Null	$0 A = 0$	$1 + A = 1$
Idempotent	$A A = A$	$A + A = A$
Inverse	$A \bar{A} = 0$	$A + \bar{A} = 1$
Commutative	$A B = B A$	$A + B = B + A$
Associative	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption	$A(A + B) = A$	$A + AB = A$ $A + \bar{A}B = A + B$

## Involution Law

$$\overline{\overline{A}} = A$$

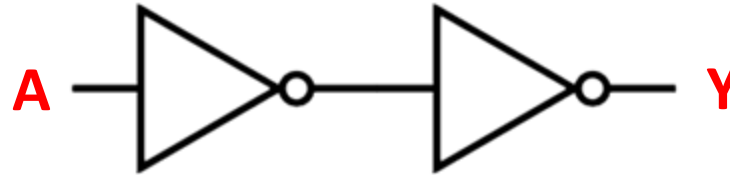

**AND VERY IMPORTANT:**

## De Morgan Theorem


$$1) \quad \overline{A + B} = \overline{A} \overline{B}$$

$$2) \quad \overline{A B} = \overline{A} + \overline{B}$$

# Circuit implementation

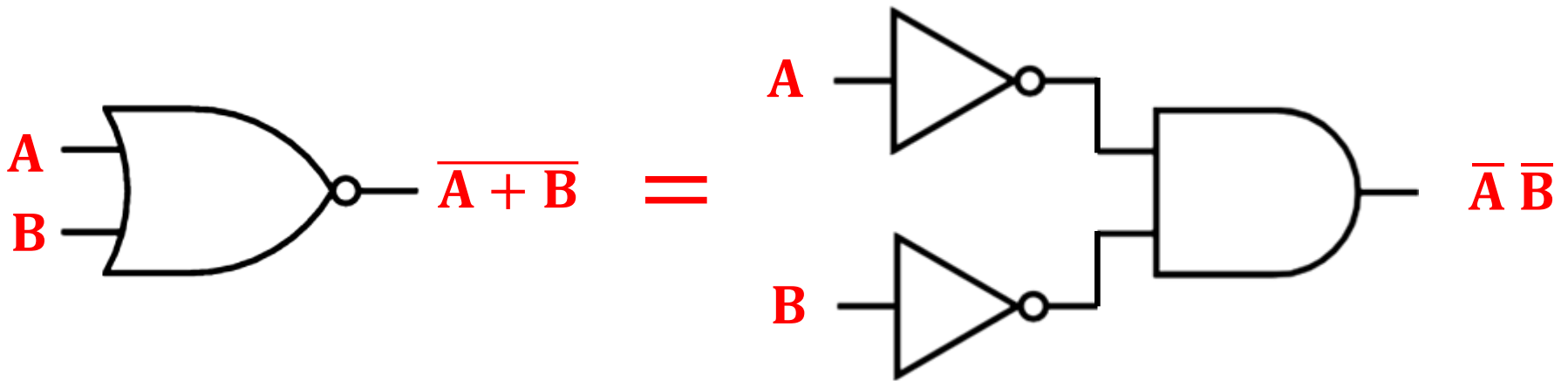
## De Morgan Theorem

$$1) \quad \overline{A + B} = \bar{A} \bar{B}$$



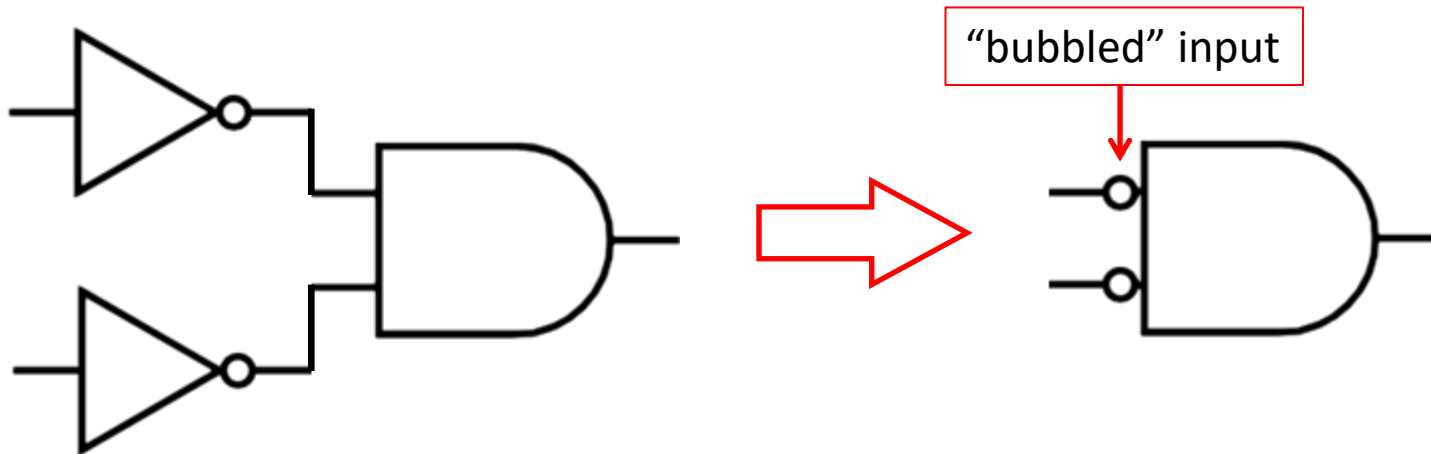
# Note

In the practice it is not uncommon to simplify digital circuit layouts by expressing a NOT gate with a “bubble” in a connected element, for example :



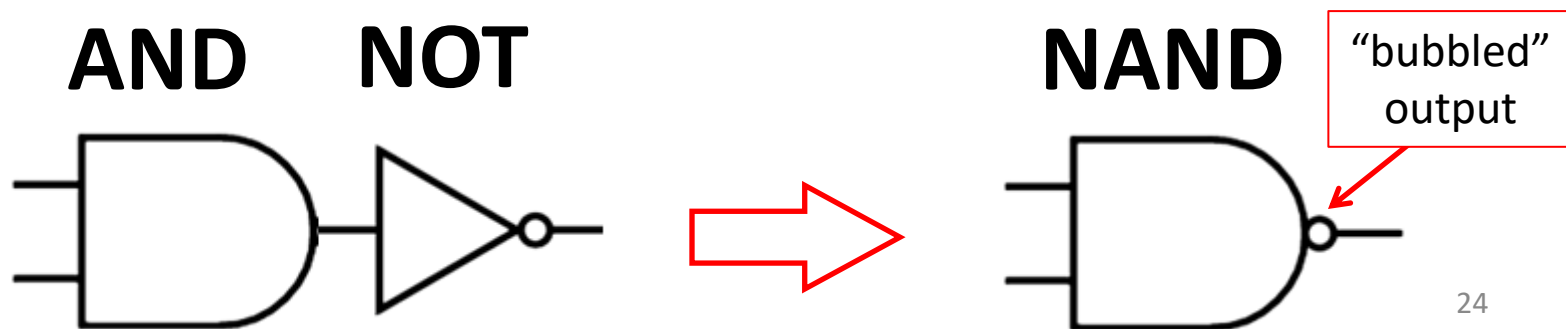as done already in elementary gate definitions:






# Circuit implementation
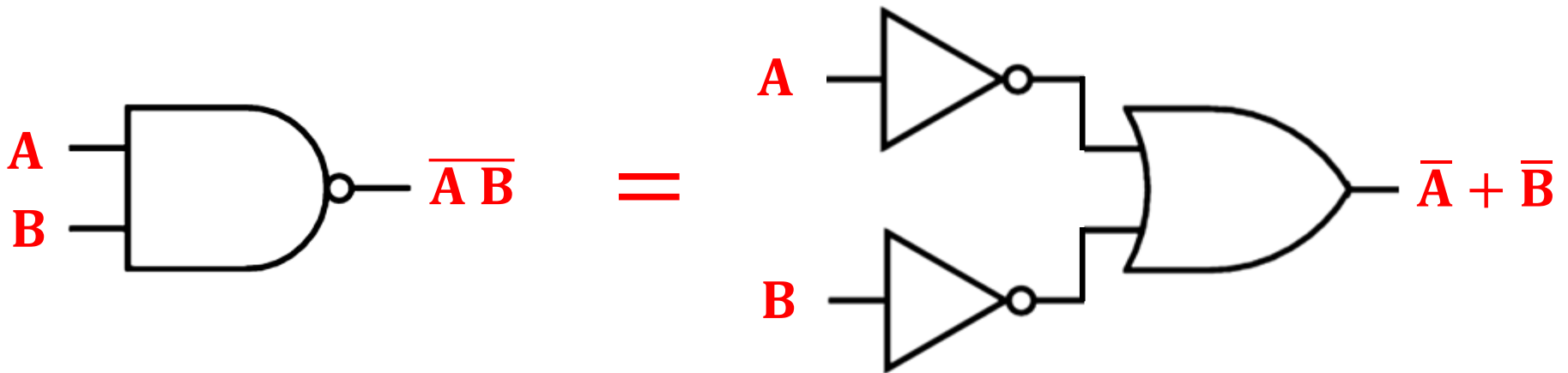
## De Morgan Theorem

$$2) \quad \overline{A B} = \bar{A} + \bar{B}$$



# AND Absorption Law (Proof)

Apply OR Distributive Law

$$A(B + C) = AB + AC$$

Apply Idempotent Law

$$A A = A$$

Apply Identity Law

$$1 A = A$$

Apply OR Distributive Law

$$A(B + C) = AB + AC$$

Apply Null Law

$$1 + A = 1$$

Apply Identity Law

$$1 A = A$$

$$A(A + B)$$

$$AA + AB$$

$$A + AB$$


$$A1 + AB$$

$$A(\underbrace{1 + B}_{=1})$$

$$A(1)$$

$$A$$

# Logic Circuit Realization

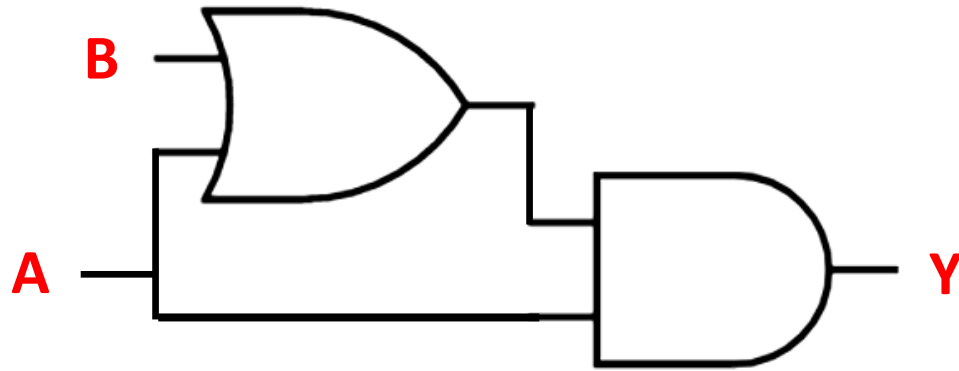

$$A(A + B)$$



**A**

# AND Distributive Law (Proof)

$$(A + B)(A + C)$$

Apply OR Distributive Law twice

$$A(B + C) = AB + AC$$

$$AA + AC + BA + BC$$

Idempotent Law

$$A A = A$$

$$A + AC + BA + BC$$

Apply OR Absorption Law

$$A + AB = A$$



$$A + AB + BC$$

Apply Commutative Law

Apply OR Absorption Law


$$A + BC$$

# Logic Circuit Realization

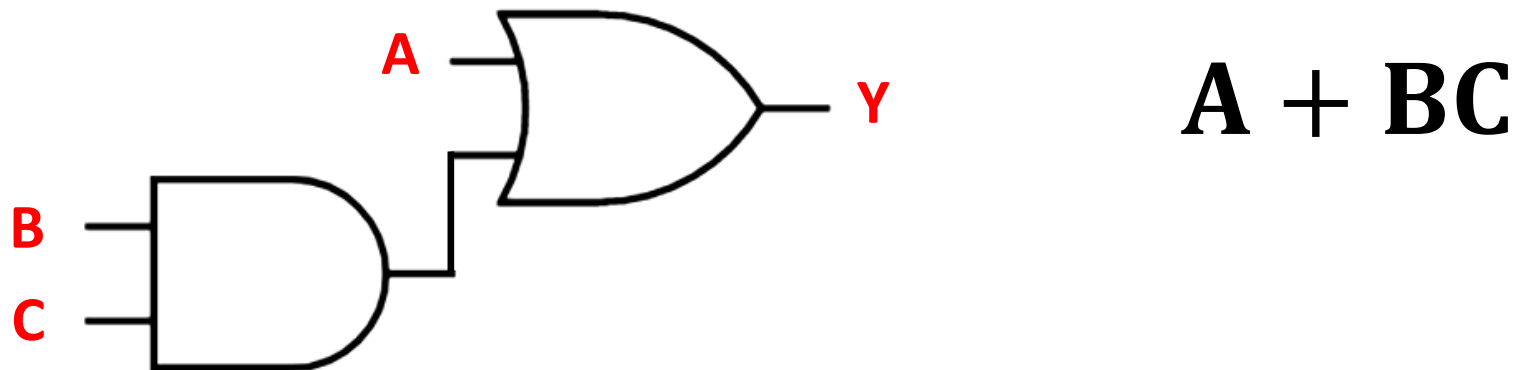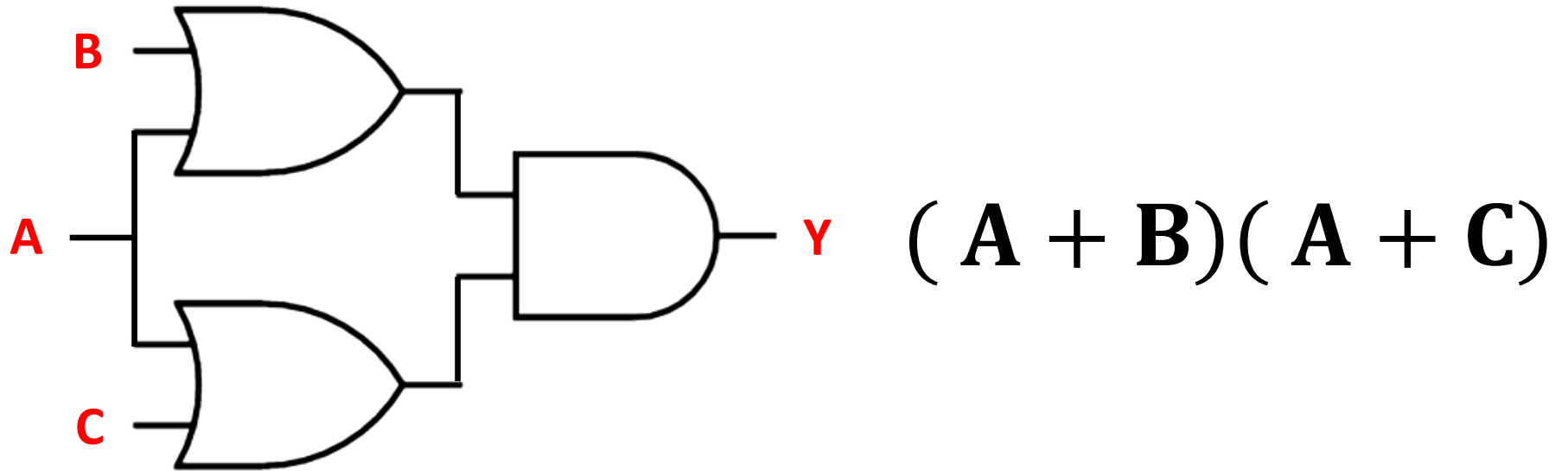

# OR Absorption Law (Proof)

$$A + \bar{A}B$$

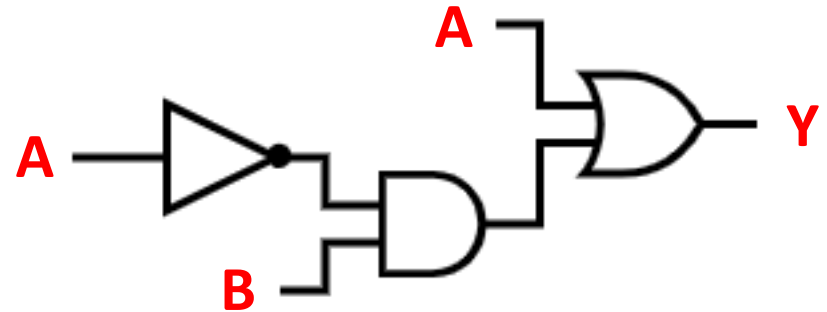

Apply OR Distributive Law

$$A + BC = (A + B)(A + C)$$

$$(A + \bar{A})(A + B)$$

Apply Null Law

$$1(A + B)$$

Apply Identity Law

$$A + B$$



# Example 1

Apply Distributive Law

$$AB(\bar{B}C + AC)$$

Apply Commutative Law

$$AB\bar{B}C + ABAC$$

Apply Idempotent Law

$$AB\bar{B}C + AABC$$

Apply Inverse Law  
(a.k.a. Complement Law)

$$AB\bar{B}C + ABC$$

Apply Null Law

$$A0C + ABC$$


Apply Identity Law

$$0 + ABC$$



$$ABC$$

# Example 1

$$AB(\bar{B}C + AC)$$

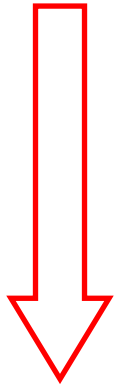


$$ABC$$

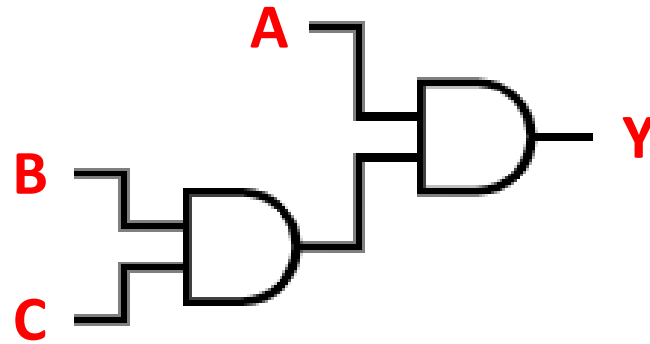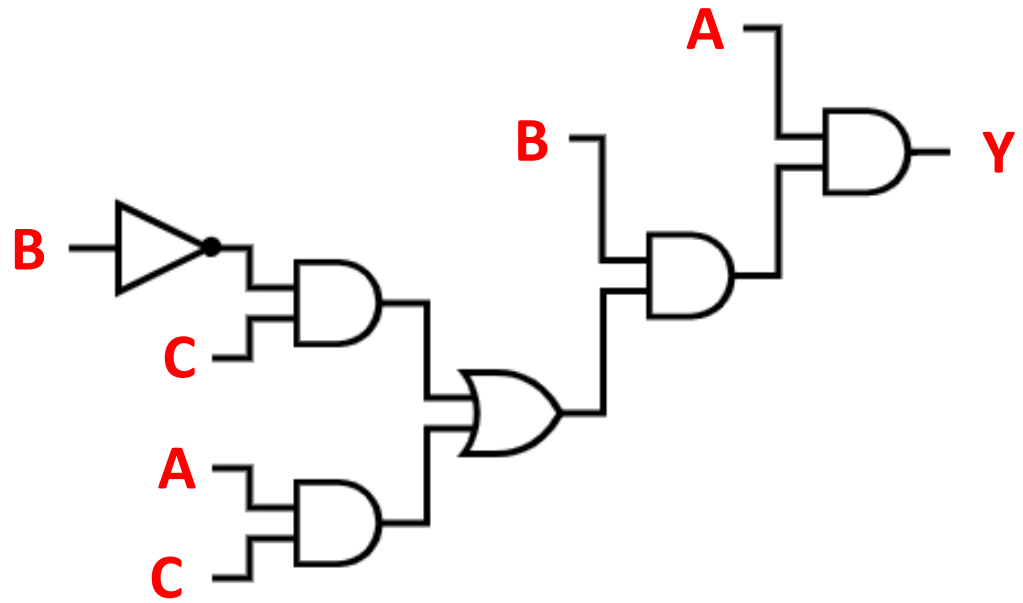



# Example 1

**ABC**

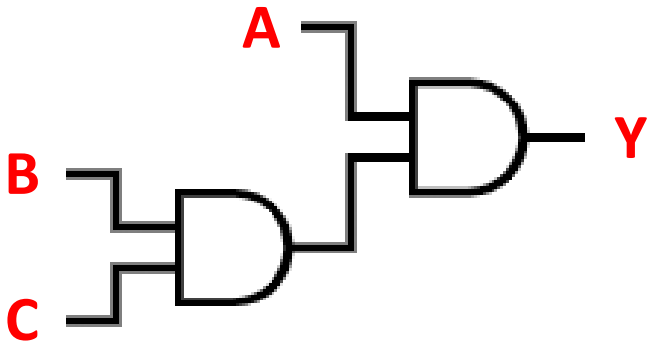


**TRUTH TABLE**

<b>A</b>	<b>B</b>	<b>C</b>	<b>Y</b>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1
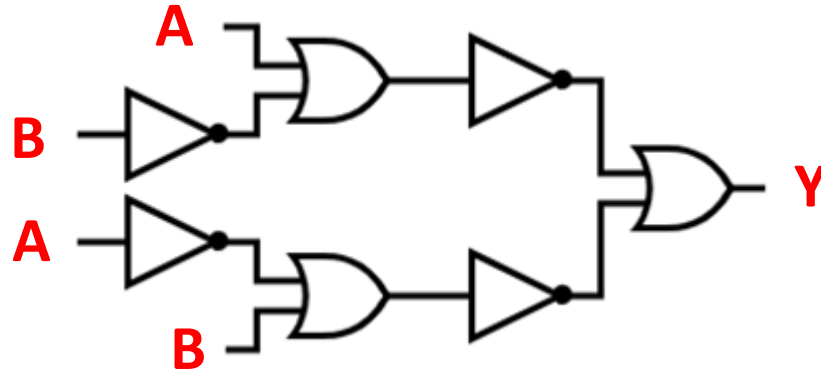
## Example 2

$$\overline{A + \overline{B}} + \overline{\overline{A} + B}$$



Apply De Morgan Theorem  
on both terms


$$\overline{A + B} = \overline{A} \overline{B}$$

Apply Involution Law

$$\overline{\overline{A}} \overline{\overline{B}} + \overline{\overline{\overline{A}}} \overline{\overline{B}}$$


↓                      ↓
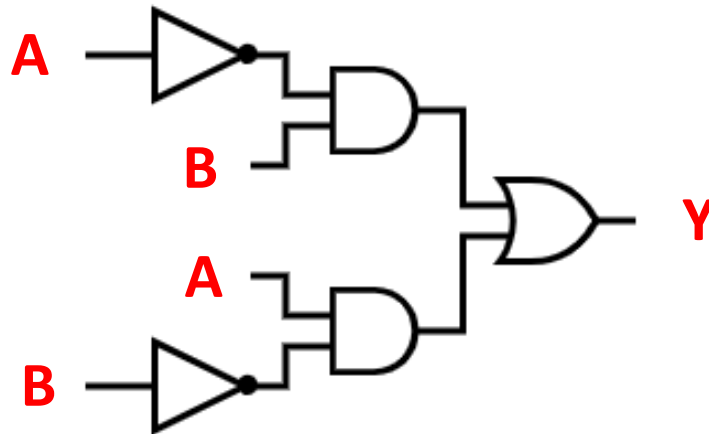
$$\overline{A} \overline{B} + A \overline{B}$$



# Example 2

$$\bar{A} B + A \bar{B}$$

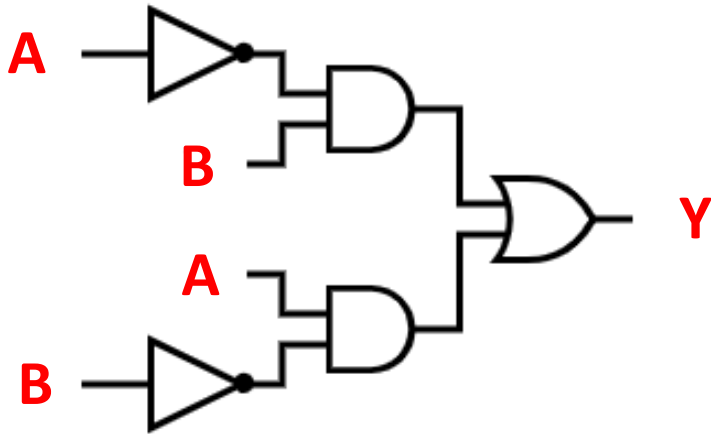


TRUTH TABLE

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

This is the Truth Table of the XOR

$$\overline{A B} + A B$$

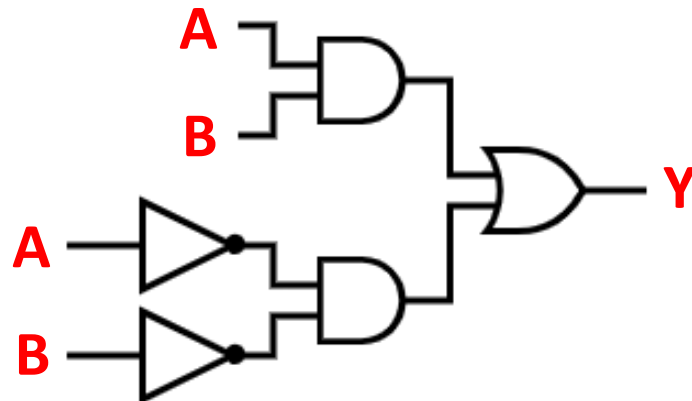
An equivalent realization giving the same truth table



# Example 2

# Other equivalent circuits

$$\bar{A} B + A \bar{B}$$

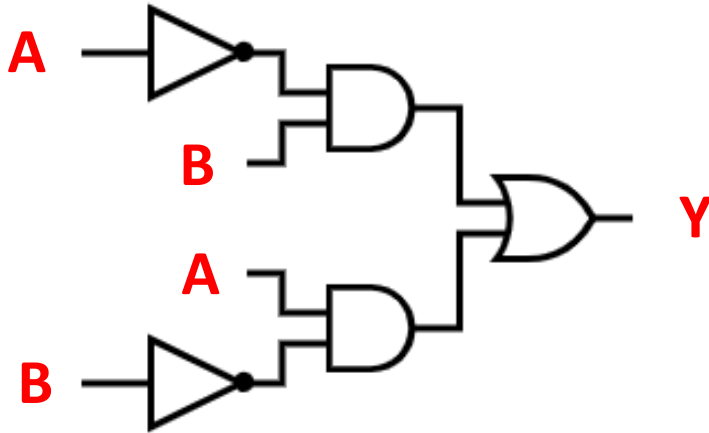


TRUTH TABLE


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

This is the Truth Table of the XOR

Realization only with NAND Gates

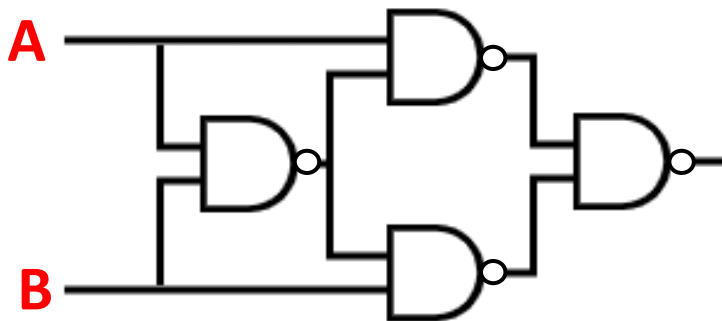

$$(A + B) \overline{(AB)}$$

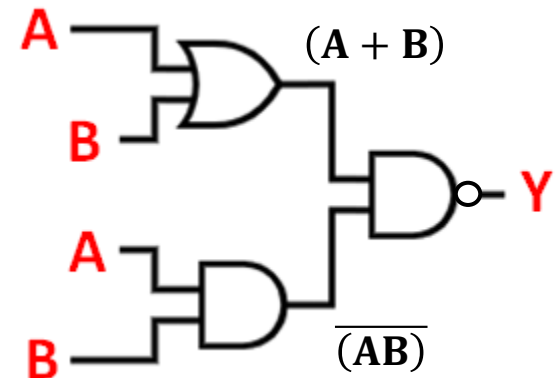

## Example 2

Prove

$$(A + B) \overline{(AB)} \Rightarrow \bar{A}B + A\bar{B}$$

Apply De Morgan Theorem

$$\overline{AB} = \bar{A} + \bar{B}$$

$$(A + B)(\bar{A} + \bar{B})$$

Apply Distribution Law

$$(\bar{A} + \bar{B})A + (\bar{A} + \bar{B})B$$

Apply Distribution Law

$$A\bar{A} + A\bar{B} + \bar{A}B + B\bar{B}$$

Apply Inverse Law

$$A\bar{A} = 0$$

$$0 + A\bar{B} + \bar{A}B + 0$$


Apply Identity Law

$$0 + A = A$$

$$\bar{A}B + A\bar{B}$$

# Example 2

$$\bar{A} B + A \bar{B}$$

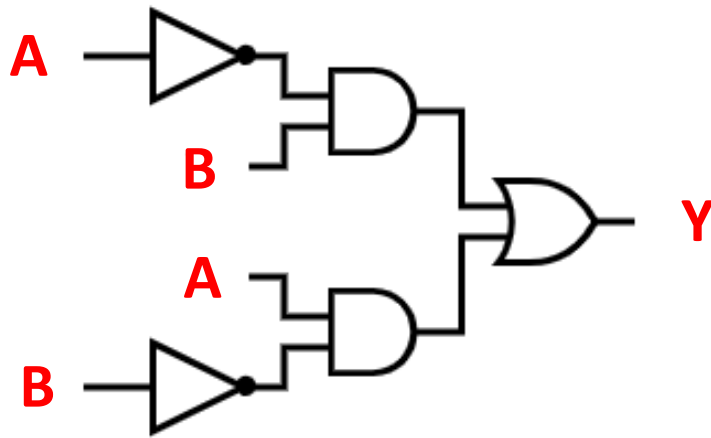



TRUTH TABLE

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

This is the Truth Table of the XOR


$$Y = A \oplus B$$

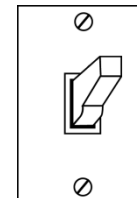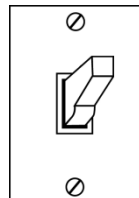We have just designed one possible logic circuit to operate a light with two switches



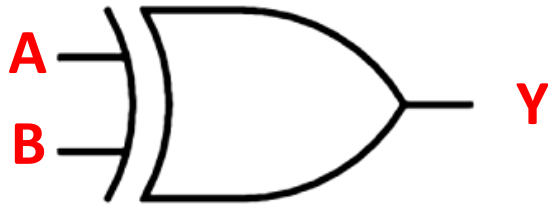
# Example 2

Here is how an electrician implements the wiring of **XOR** with two-way switches



TRUTH TABLE

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

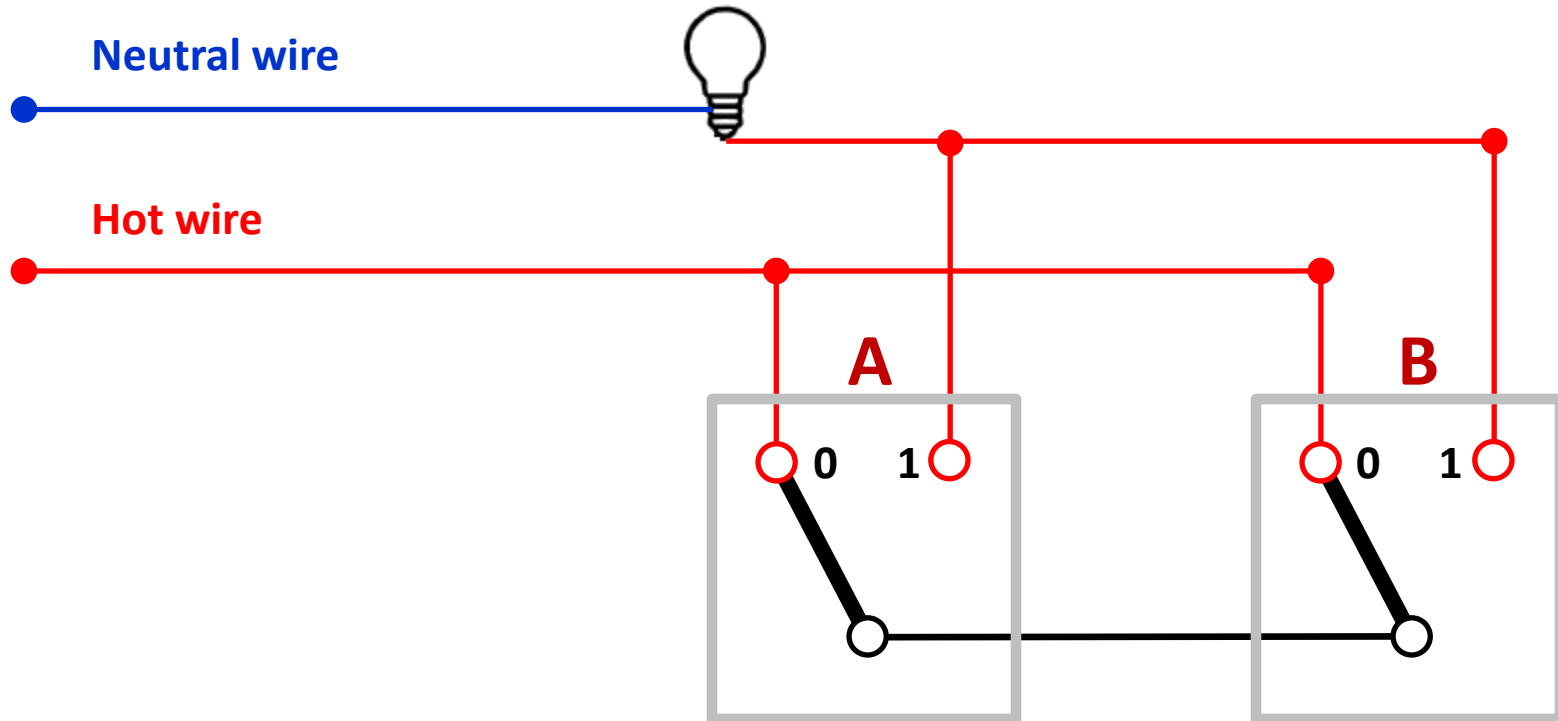

# Example 2

Here is how an electrician implements the wiring of **XNOR** with two-way switches



TRUTH TABLE

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

