

ECE 205 “Electrical and Electronics Circuits”

Spring 2024 – LECTURE 30

MWF – 12:00pm

Prof. Umberto Ravaioli

2062 ECE Building


Lecture 30 – Summary

Learning Objectives

 1. Boolean algebra
2. Logic network minimization practice
3. Universal gates combine to realize any other logic function

Logic Operations


Binary logic is based on a set of **seven** elementary logical operations with two inputs and one output. The elements which accomplish these operations are called “Logic Gates”. They are represented with the symbols below in a **logic circuit**.




NOT




AND

 


OR

 

XOR

 

NAND

 

NOR



XNOR

Boolean Algebra

Logic operations can be represented with formulas, using a special formalism called Boolean Algebra. The following table shows the Boolean notation.

OPERATOR	BOOLEAN ALGEBRA
NOT	$Y = \bar{A}$
AND	$Y = A \cdot B$
OR	$Y = A + B$
NAND	$Y = \bar{A} \cdot \bar{B}$
NOR	$Y = \overline{A + B}$
XOR	$Y = A \oplus B$
XNOR	$Y = \overline{A \oplus B}$

NOTE: Some authors use $A \cdot B$ for $A \cdot B$ and A' for \bar{A}


Boolean Algebra Simplifications Table

When a logic circuit is designed to obtain the desired behavior, it can be simplified by using the following laws to minimize the number of gates.

LAWS	AND	OR
Identity	$1 A = A$	$0 + A = A$
Null	$0 A = 0$	$1 + A = 1$
Idempotent	$A A = A$	$A + A = A$
Inverse (Complement)	$A \bar{A} = 0$	$A + \bar{A} = 1$
Commutative	$A B = B A$	$A + B = B + A$
Associative	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption	$A(A + B) = A$	$A + AB = A$ $A + \bar{A}B = A + B$

Involution Law

$$\overline{\overline{A}} = A$$

 

AND VERY IMPORTANT:

De Morgan Theorem

$$1) \quad \overline{A + B} = \overline{A} \overline{B}$$

$$2) \quad \overline{AB} = \overline{A} + \overline{B}$$

Example 1

Apply Distributive Law

$$AB(\bar{B}C + AC)$$

$$AB\bar{B}C + ABAC$$



$$AB\bar{B}C + \textcolor{red}{AABC}$$



$$\textcolor{blue}{AB}\bar{B}C + \textcolor{red}{ABC}$$



$$\textcolor{red}{A}\textcolor{blue}{0}C + ABC$$



$$\underbrace{0}_{\textcolor{pink}{+}} \underbrace{ABC}_{\textcolor{pink}{+}}$$

$$ABC$$

Apply Idempotent Law


Apply Inverse Law
(a.k.a Complement Law)

Apply Null Law



Apply Identity Law

Example 1

$$AB(\bar{B}C + AC)$$

 


ABC

  

Example 1


TRUTH TABLE

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 

This is a 3-inputs AND. Only when all inputs are TRUE, the output is TRUE.

Example 2

 


Apply De Morgan Theorem
on both terms

$$\overline{A + B} = \overline{A} \overline{B}$$


Apply Involution Law

$$\begin{aligned} &\overline{\overline{A} \overline{B}} + \overline{\overline{A} \overline{B}} \\ &\downarrow \quad \downarrow \\ &\overline{\overline{A} B} + \overline{A} \overline{\overline{B}} \end{aligned}$$

 

Example 2

$$\bar{A}B + A\bar{B}$$

 


TRUTH TABLE

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

This is the Truth Table of the XOR

An equivalent realization giving
the same truth table


$$\overline{\bar{A}\bar{B}} + \overline{AB}$$

 

Example 2

Other equivalent circuits

$$\overline{A}B + A\overline{B}$$

 


TRUTH TABLE


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

This is the Truth Table of the XOR

Realization only with NAND Gates

 

$$\overline{(A(\overline{AB}))} (\overline{B(\overline{AB}))}$$

 

Example 2

Prove

$$(A + B)\overline{(AB)} \quad \longrightarrow \quad \bar{A}B + A\bar{B}$$

Apply De Morgan Theorem

$$\overline{AB} = \bar{A} + \bar{B}$$

$$(A + B)(\bar{A} + \bar{B})$$

Apply Distribution Law

$$(\bar{A} + \bar{B})A + (\bar{A} + \bar{B})B$$

Apply Distribution Law

$$A\bar{A} + A\bar{B} + \bar{A}B + B\bar{B}$$

Apply Inverse Law

$$A\bar{A} = 0$$

$$0 + A\bar{B} + \bar{A}B + 0$$



Apply Identity Law

$$0 + A = A$$

$$\bar{A}B + A\bar{B}$$


Example 2 $(A + B)\overline{(AB)}$

XOR circuit realization with BJT

 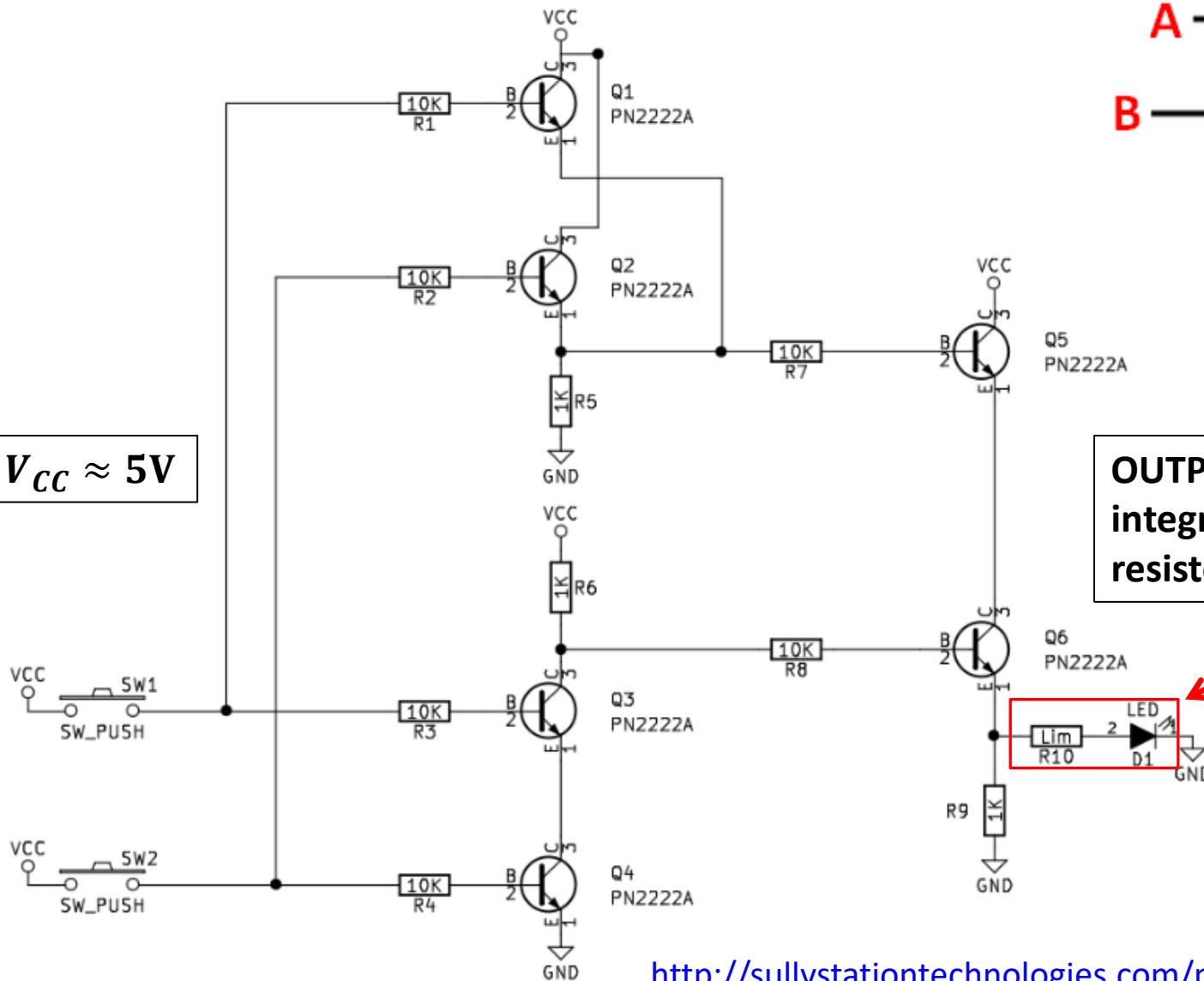

Example 2

$$\bar{A}B + A\bar{B}$$

 



TRUTH TABLE

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

This is the Truth Table of the XOR


$$Y = A \oplus B$$

We have just designed one possible logic circuit to operate a light with two switches

  

 Example 2

Here is how an electrician implements the wiring of **XOR** with two-way switches



TRUTH TABLE



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Example 2

Here is how an electrician implements the wiring of XNOR with two-way switches

TRUTH TABLE

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

  


Example 2 XOR

TRUTH TABLE





www.ti.com

5 Pin Configuration and Functions

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

  

 Example 2 XNOR


$$Y = \overline{A \oplus B} = AB + \overline{A} \overline{B}$$



TRUTH TABLE

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Realization only with NAND Gates

 

$$\overline{\overline{AB}} \quad \overline{\overline{A}} \overline{\overline{B}}$$

De Morgan Theorem

$$\overline{\overline{AB}} + \overline{\overline{A}} \overline{\overline{B}}$$

Involution Law

$$AB + \overline{A} \overline{B}$$

Example 3

$$(A + \bar{B} + \bar{C})(A + \bar{B} + C) (A + B + \bar{C})$$

Apply Distributive Law

$$A(A + \bar{B} + C)(A + B + \bar{C}) + \text{ Apply Absorption Law Twice}$$

$$\bar{B}(A + \bar{B} + C)(A + B + \bar{C}) + \text{ Apply Absorption Law}$$

$$\bar{C}(A + \bar{B} + C)(A + B + \bar{C}) \text{ Apply Absorption Law}$$

$$A +$$

$$\bar{B}(A + B + \bar{C}) +$$

$$\bar{C}(A + \bar{B} + C)$$

$$A +$$

$$(\bar{B}A + \cancel{\bar{B}B} + \bar{B}\bar{C}) +$$

$$(\bar{C}A + \cancel{\bar{C}B} + \cancel{\bar{C}C})$$

Apply Inverse Law

$$A\bar{A} = 0$$

Apply Distributive Law

Example 3

$$A + (A\bar{B} + \bar{B}\bar{C}) + (A\bar{C} + \bar{B}\bar{C})$$

All OR operations, so parentheses can go away

Idempotent Law $A + A = A$

$$A + A\bar{B} + \bar{B}\bar{C} + A\bar{C} + \bar{B}\bar{C}$$

$\underbrace{A + A\bar{B}}_{\text{Absorption Law}} + A\bar{C} + \bar{B}\bar{C}$


Absorption Law
 $A + AB = A$

$$\underbrace{A + A\bar{C}}_{\text{Absorption Law}} + \bar{B}\bar{C}$$


$$A + \bar{B}\bar{C}$$

 Example 3

$$(A + \bar{B} + \bar{C})(A + \bar{B} + C) (A + B + \bar{C})$$




$$A + \bar{B}\bar{C}$$

 

Example 3

$$A + \overline{B}\overline{C}$$

 

TRUTH TABLE

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Example 4

$$B C + (C \bar{D} + A B) D$$

Apply Distributive Law

$$B C + (D C \bar{D} + D A B)$$

Apply Inverse (Complement) Law

$$B C + 0 C + D A B$$

Apply Null Law $0 A = 0$


$$B C + 0 + D A B$$

Apply Identity Law $0 + A = A$


$$B C + D A B$$

Example 4

$$B C + (C \bar{D} + A B) D$$

 


$$B C + DA B$$

 

Example 4

TRUTH TABLE

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

 

Example 5

$$\overline{A(\overline{B} + \overline{C})}$$

De Morgan Theorem

$$\overline{A} + \overline{\overline{B} + \overline{C}}$$

Involution Law

$$\overline{\overline{A}} + B + C$$

Example 5

$$\overline{A(B + C)}$$

COMPLETE THE TRUTH TABLE

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

EASIER TO USE →

$$\overline{A} + B + C$$

Example 5

$$\overline{A(B + C)}$$

COMPLETE THE TRUTH TABLE

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

$\bar{A} = 1$

$\bar{A} = 0$

ALWAYS AT LEAST
ONE INPUT = 1

$$\overline{\bar{A} + B + C}$$

Example 5


$$\overline{A(B + C)}$$

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


$$\overline{A} + \overline{B} + \overline{C}$$

Example 5

$$\overline{A(\overline{B} + C)}$$

 

 
$$\overline{\overline{A}} + \overline{B} + \overline{C}$$



Using standard gates to construct other logic functions

NOR and NAND are considered universal gates for the purpose of constructing other ones.


Construct the NOT gate

 


NOT

A	Y
0	1
1	0

Using NOR gates

 


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


Construct the NOT gate

 


NOT

A	Y
0	1
1	0

Using NAND gates

 


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0



Construct the BUFFER gate

 


BUFFER

A	Y
0	0
1	1

Using NOR gates

  



Construct the BUFFER gate

 


BUFFER

A	Y
0	0
1	1

Using NAND gates

  


Construct the AND gate

 


AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Using NAND gates

 


Construct the AND gate

 

AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Using NOR gates

 


Construct the NAND gate




A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Using NOR gates

 


Construct the OR gate

 


OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Using NOR gates

 


Construct the OR gate

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Using NAND gates

 


Construct the NOR gate

 

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Using NAND gates

 

Logic Gates using BJT's

We consider logic gates made with BJTs connected by resistors (Resistor-Transistor-Logic or **RTL**). This was the earliest digital logic family for **integrated circuits**.

While there are much higher performance designs for BJT chips (e.g., Transistor-Transistor-Logic or **TTL**), RTL is still a good approach to prototype simple logic circuits with **discrete components** that can handle a fair amount of power in servo-mechanisms.

Intermediate between RTL and TTL, there was the Diode-Transistor-Logic (**DTL**) where inputs run through *p-n* junctions.

$V_{BE} < V_{BE}(\text{ON})?$

YES

BJT ***OFF***

NO

$V_{CE} > V_{CE}(\text{sat}) ?$

YES

Forward Active

$$V_{BE} = V_{BE}(\text{ON})$$

$$I_C = \beta I_B$$

NO

Saturation

$$V_{BE} = V_{BE}(\text{ON})$$

$$V_{CE} = V_{CE}(\text{sat})$$

$$I_C = I_C(\text{sat})$$


Consider two cases

Assume

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$


$$\beta = 10$$

 

$$V_{BE} < V_{BE}(\text{ON})$$

$$V_0 = V_{CC} = 10\text{V}$$

Q_1 OFF

 

$$I_B = \frac{10 - 0.7}{10\text{k}\Omega} = 0.93\text{mA}$$

$$I_C = \beta I_B = 9.3\text{mA} \quad \text{Assuming FA mode}$$

$$I_C(\text{sat}) = \frac{10 - 0.2}{2\text{k}\Omega} = 4.8\text{mA}$$

Q_1 SATURATION


$$V_0 = 0.2 \text{ V}$$

Basic principle to design logic gates with BJT:

Two states of operation

0 LOW V_{in} → HIGH V_0 1

Q_1 OFF

 

10V

8V

5V

For a given technology one has to set reference voltage levels to accept logical states 0 and 1.

1V

0V

0

Basic principle to design logic gates with BJT:


Two states of operation

0 LOW V_{in} → HIGH V_0 1

Q_1 OFF



1 HIGH V_{in} → LOW V_0 0

Q_1 SATURATION


 


  For a given technology one has to set reference voltage levels to accept logical states 0 and 1.






Transistors are like switches

  

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

 

$$V_0 = V_{CC} = 10\text{V}$$


1

V_{in}	V_0
0 V	10 V

$$V_{BE(\text{ON})} = 0.7 \text{ V}$$


$$V_{CE(\text{sat})} = 0.2 \text{ V}$$

$$\beta = 10$$

 

$$V_0 = V_{CC} = 10 \text{ V}$$
1

V _{in}	V ₀
0 V	0 1
10V	10 V 1

 

$$I_C(\text{sat}) = \frac{10 - 0.2}{1\text{k}\Omega} = 9.8 \text{ mA}$$

$$I_B = \frac{10 - 0.7}{1\text{k}\Omega} = 9.3 \text{ mA}$$

$$I_C = \beta I_B = 93 \text{ mA} \gg I_C(\text{sat})$$

$$V_0 = 0.2 \text{ V}$$
0

On the I - V curves

