

# **ECE 205 “Electrical and Electronics Circuits”**

**Spring 2024 – LECTURE 31**

MWF – 12:00pm

**Prof. Umberto Ravaioli**

2062 ECE Building

# Lecture 31 – Summary


## Learning Objectives

1. Universal gates combine to realize any other logic function
2. Logic gates realized physically with BJT's


# Using standard gates to construct other logic functions

**NOR and NAND are considered universal gates for the purpose of constructing other ones.**


# Construct the NOT gate

 

A	Y
0	1
1	0

 


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


# Construct the NOT gate

 

A	Y
0	1
1	0

 


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

# Construct the BUFFER gate

 


**BUFFER**

A	Y
0	0
1	1

 
 


# Construct the BUFFER gate

 


**BUFFER**

A	Y
0	0
1	1

  


# Construct the AND gate

 


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Use NAND gates

 




# Construct the AND gate

 


<b>A</b>	<b>B</b>	<b>Y</b>
<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>0</b>
<b>1</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>1</b>

Use NOR gates

 


# Construct the AND gate

 

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

## PROOF

 

$$Y = \overline{\bar{A} + \bar{B}}$$

Apply De Morgan Theorem


$$\bar{A} + \bar{B} = \overline{A B}$$

$$Y = \overline{\overline{A B}} = A B$$




Apply Involution Law


# Construct the NAND gate

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 


# Construct the OR gate

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Use NOR gates

 


# Construct the OR gate

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Use NAND gates

 

# Construct the OR gate

 

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

## PROOF

$$Y = \overline{\overline{A} \overline{B}}$$


Apply De Morgan Theorem

$$\overline{\overline{A} \overline{B}} = \overline{\overline{A + B}}$$


$$Y = \overline{\overline{\overline{A + B}}} = A + B$$




Apply Involution Law

 

# Construct the NOR gate

 

<b>A</b>	<b>B</b>	<b>Y</b>
<b>0</b>	<b>0</b>	<b>1</b>
<b>0</b>	<b>1</b>	<b>0</b>
<b>1</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>0</b>

 

# Logic Gates using BJT's

We consider logic gates made with BJTs connected by resistors (Resistor-Transistor-Logic or **RTL**). This was the earliest digital logic family for **integrated circuits**.

While there are much higher performance designs for BJT chips (e.g., Transistor-Transistor-Logic or **TTL**), RTL is still a good approach to prototype simple logic circuits with **discrete components** that can handle a fair amount of power in servo-mechanisms.

Intermediate between RTL and TTL, there was the Diode-Transistor-Logic (DTL) where inputs run through *p-n* junctions.



$V_{BE} < V_{BE}(\text{ON})?$

YES

NO

BJT *OFF*

$V_{CE} > V_{CE}(\text{sat}) ?$

YES

NO

Forward Active

$$V_{BE} = V_{BE}(\text{ON})$$

$$I_C = \beta I_B$$

Saturation

$$V_{BE} = V_{BE}(\text{ON})$$


$$V_{CE} = V_{CE}(\text{sat})$$

$$I_C = I_C(\text{sat})$$

Consider two cases

Assume  $V_{BE}(\text{ON}) = 0.7 \text{ V}$   
 $V_{CE}(\text{sat}) = 0.2 \text{ V}$

$$\beta = 10$$

 

$$V_{BE} < V_{BE}(\text{ON})$$


$$V_0 = V_{CC} = 10 \text{ V}$$

$Q_1$  OFF

Consider two cases

Assume  $V_{BE}(\text{ON}) = 0.7 \text{ V}$   
 $V_{CE}(\text{sat}) = 0.2 \text{ V}$


$$\beta = 10$$

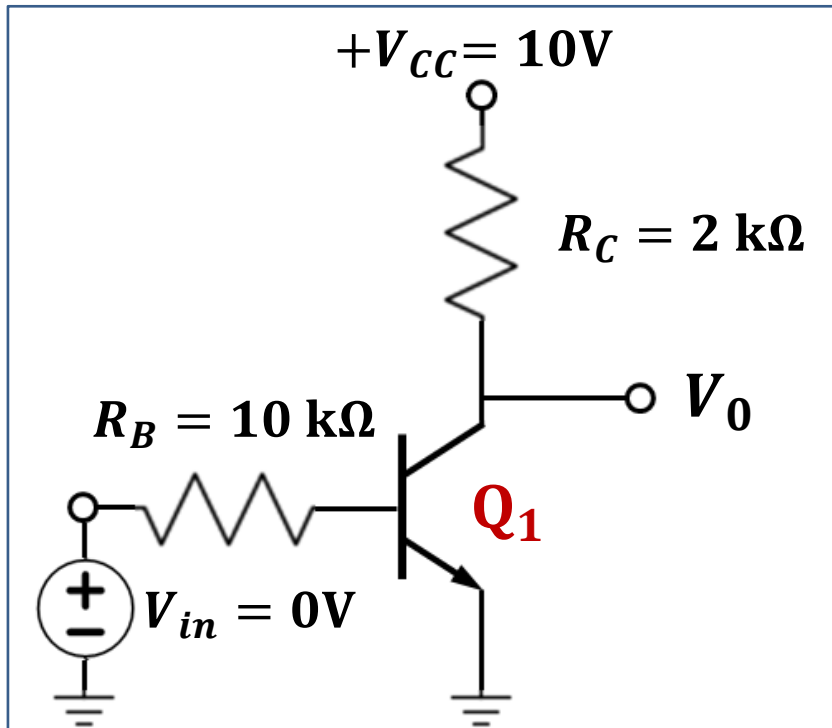

$$V_{BE} < V_{BE}(\text{ON})$$

$$V_0 = V_{CC} = 10 \text{ V}$$

**$Q_1$  OFF**

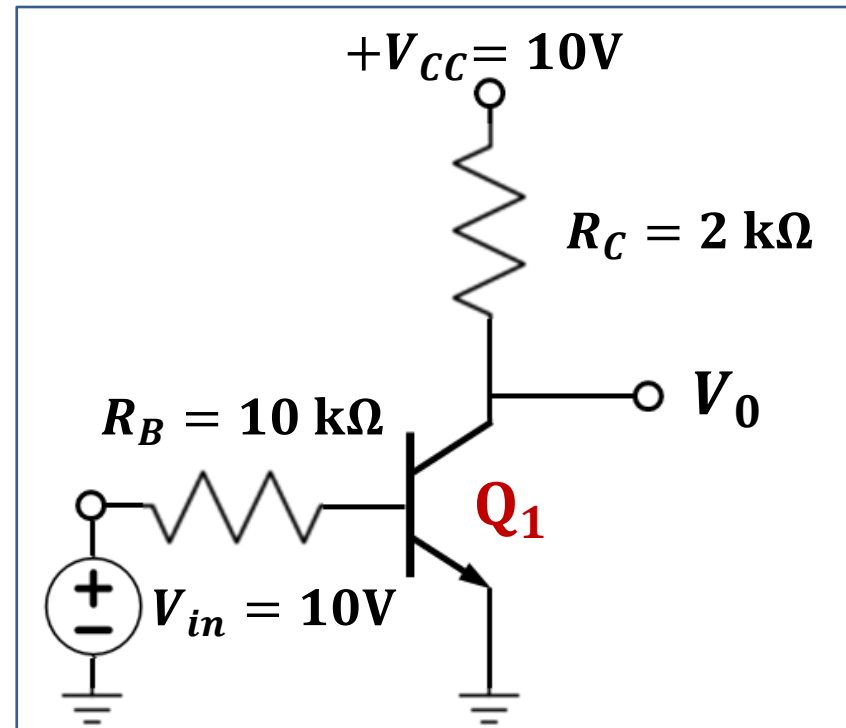

$$I_B = \frac{10 - 0.7}{10 \text{ k}\Omega} = 0.93 \text{ mA}$$

$$I_C = \beta I_B = 9.3 \text{ mA} \quad \text{Assuming FA mode}$$

$$I_C(\text{sat}) = \frac{10 - 0.2}{2 \text{ k}\Omega} = 4.8 \text{ mA}$$

**$Q_1$  SATURATION**


$$V_0 = 0.2 \text{ V}$$

# Basic principle to design logic gates with BJT:


## Two states of operation

① LOW  $V_{in} \rightarrow$  HIGH  $V_0$  ②

$Q_1$  OFF

 

 For a given technology one has to set reference voltage levels to accept logical states 0 and 1.



# Basic principle to design logic gates with BJT:


## Two states of operation

0 LOW  $V_{in}$  → HIGH  $V_0$  1


$Q_1$  OFF



1 HIGH  $V_{in}$  → LOW  $V_0$  0

$Q_1$  SATURATION


 


 For a given technology one has to set reference voltage levels to accept logical states 0 and 1.



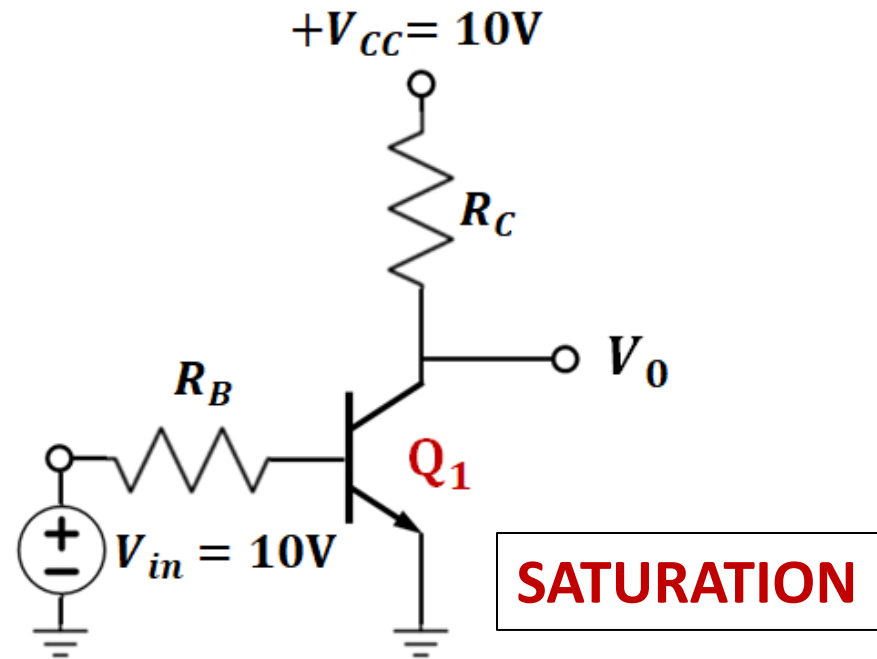 

Transistors are like switches

  


# Basic Inverter (NOT) implementation

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

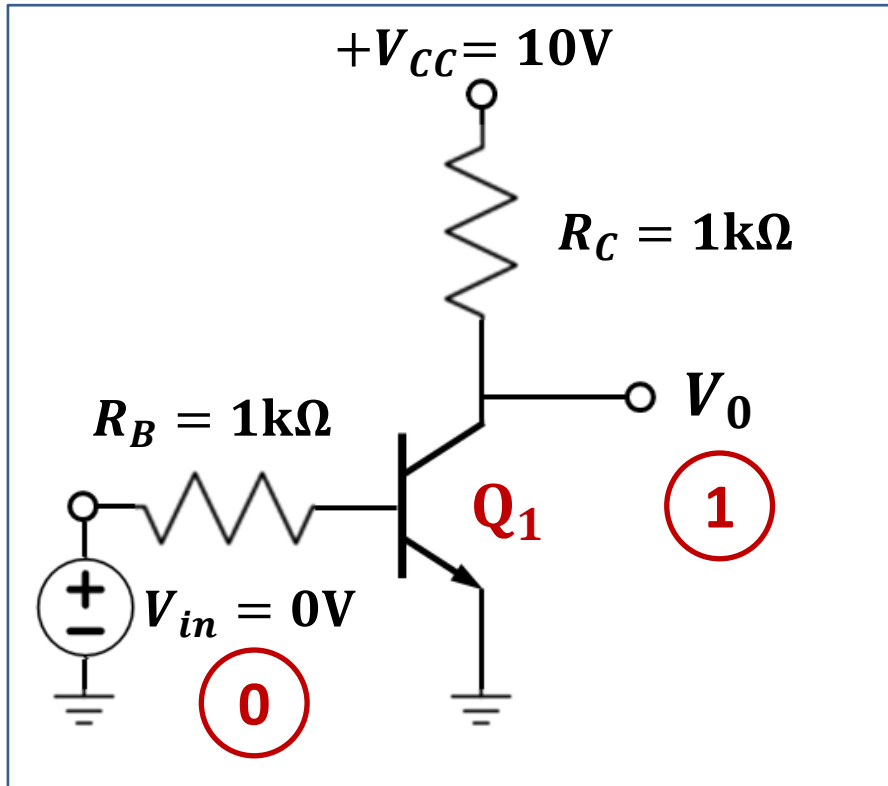

$$V_0 = V_{CC} = 10\text{V}$$



$V_{in}$	$V_0$
0 V (0)	10 V (1)



$$V_{BE(ON)} = 0.7 \text{ V}$$

$$V_{CE(sat)} = 0.2 \text{ V}$$

$$\beta = 10$$

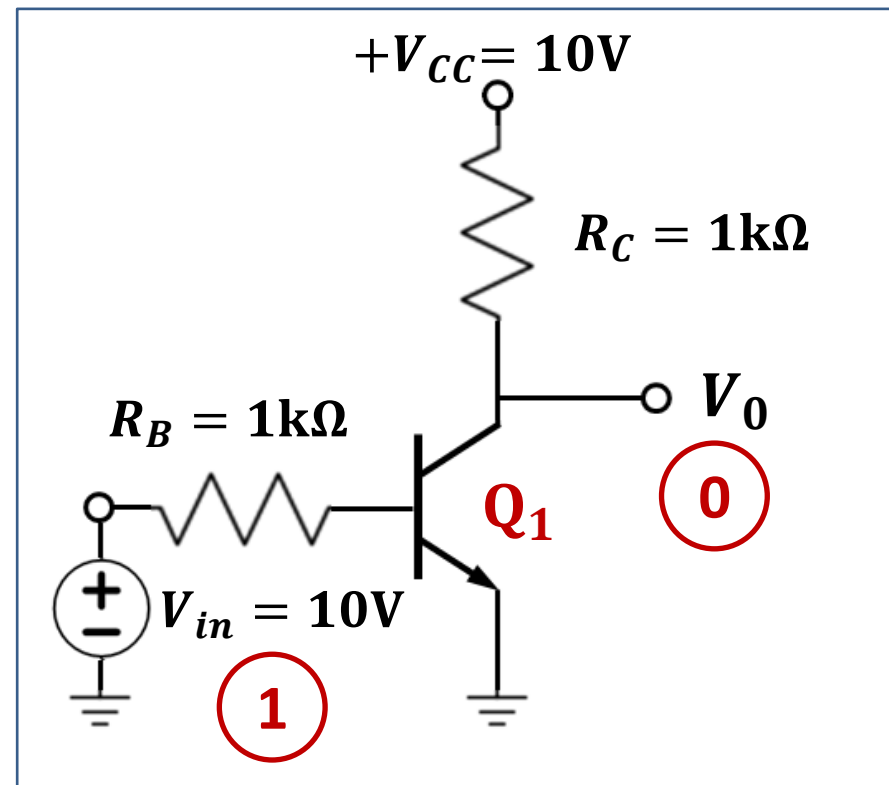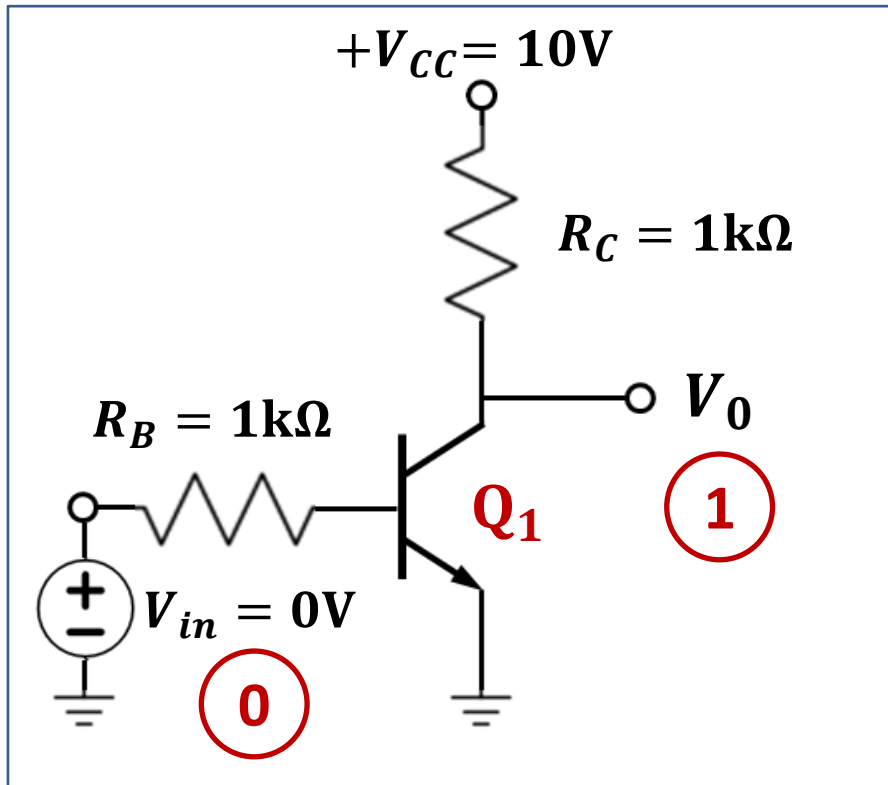

$$V_0 = V_{CC} = 10\text{V} \quad \text{(1)}$$

$$I_C(\text{sat}) = \frac{10 - 0.2}{1\text{k}\Omega} = 9.8\text{mA}$$


$$I_B = \frac{10 - 0.7}{1\text{k}\Omega} = 9.3\text{mA}$$

$$I_C = \beta I_B = 93\text{mA} \gg I_C(\text{sat})$$

$$V_0 = 0.2 \text{ V} \quad \text{(0)}$$

$V_{in}$	$V_0$
0 V (0)	10 V (1)
10V (1)	0.2 V (0)

# On the $I$ - $V$ curves

 



## BJT inverter circuit

Another example, realized with  $\pm V_{CC}$  bias

# Example: Realization of inverter circuit with *n-p-n* BJT (positive logic)


Assume  $V_{BE}(\text{ON}) = 0.7 \text{ V}$

$V_{CE}(\text{sat}) = 0.2 \text{ V}$

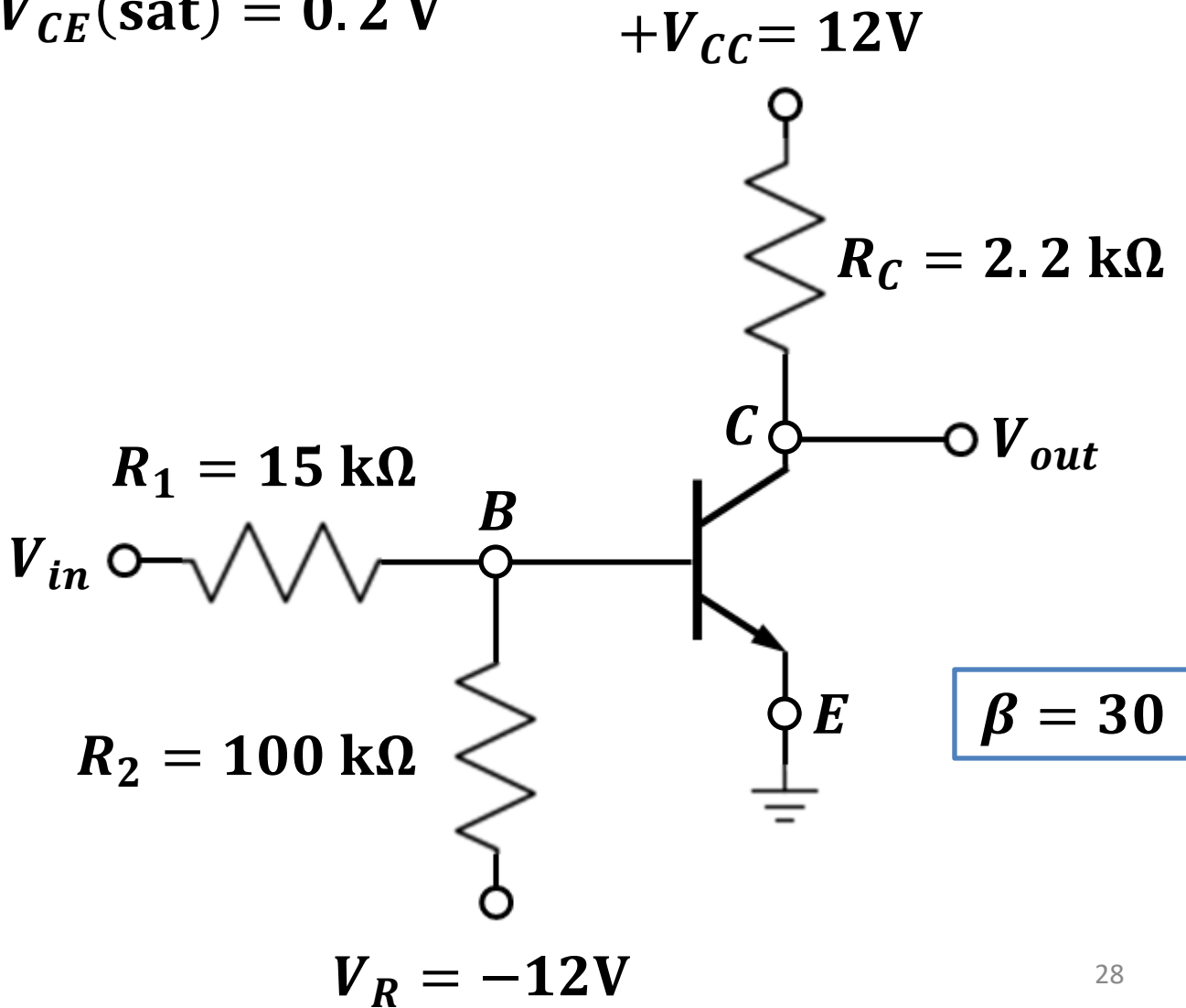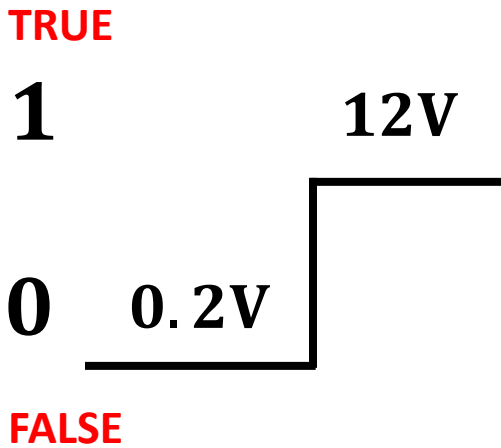

## Base circuit

### Node Voltage method

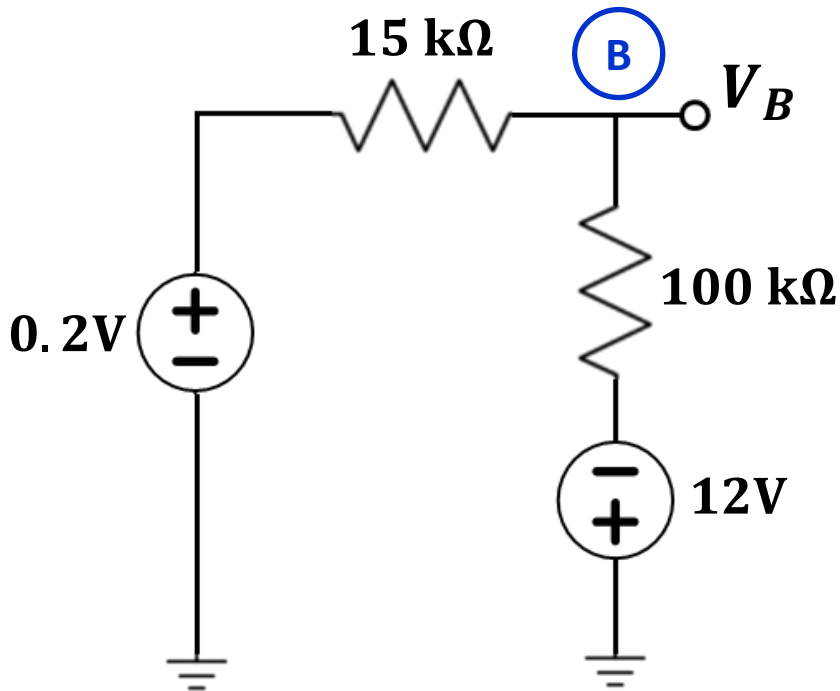

Input voltage

$$V_{in} = 0.2 \text{ V}$$

Assume

$$I_B = 0 \text{ V}$$

### Thevenin equivalent source:

Node voltage at



$$\frac{V_B - 0.2}{15\text{k}} + \frac{V_B - (-12)}{100\text{k}} = 0$$

$$20\text{k} V_B - 4\text{k} + 3\text{k} V_B + 36\text{k} = 0$$

$$V_B = -1.391 \text{ V}$$

The base *p-n* junction is OFF and as a consequence the transistor is in CUT-OFF mode. Base and collector currents are zero and

$$V_{out} = V_{CC} = 12 \text{ V}$$

# Another way to solve the base circuit

Input voltage

$$V_{in} = 0.2 \text{ V}$$

Assume

$$I_B = 0 \text{ V}$$

## Thevenin equivalent source:

Superposition of two voltage divider results

$$V_B = -12 \times \frac{15}{100 + 15} + 0.2 \times \frac{100}{100 + 15}$$
$$= -1.391 \text{ V}$$

TRUE


1

12V

0

0.2V

FALSE

 


$R_2 = 100 \text{ k}\Omega$

$V_R = -12 \text{ V}$

$+V_{CC} = 12 \text{ V}$

$R_C = 2.2 \text{ k}\Omega$

 

$\beta = 30$

# Base circuit

Input voltage


$$V_{in} = 12 \text{ V}$$

## Thevenin equivalent source:

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$


$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

Node voltage at **(B)** in open circuit

 

$$\frac{V_B - 12}{15\text{k}} + \frac{V_B - (-12)}{100\text{k}} = 0$$
$$20\text{k} V_B - 240\text{k} + 3\text{k} V_B + 36\text{k} = 0$$
$$V_B = 8.87 \text{ V}$$
 
$$R_{\text{eff}} = \left( \frac{1}{15\text{k}} + \frac{1}{100\text{k}} \right)^{-1} = 13.04\text{k}\Omega$$



$$I_B = \frac{8.87 - 0.7}{13.04 \text{ k}} \approx 0.63 \text{ mA}$$

## Collector circuit

Input voltage

$$V_{in} = 12 \text{ V}$$

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$I_B \approx 0.63 \text{ mA}$$


Assuming Forward-Active mode

$$I_C = \beta I_B = 19.9 \text{ mA}$$

Check for saturation

$$\begin{aligned} I_C(\text{sat}) &= \frac{V_{CC} - V_{CE}(\text{sat})}{R_C} \\ &= \frac{11.8}{2.2\text{k}} = 5.36 \text{ mA} \end{aligned}$$
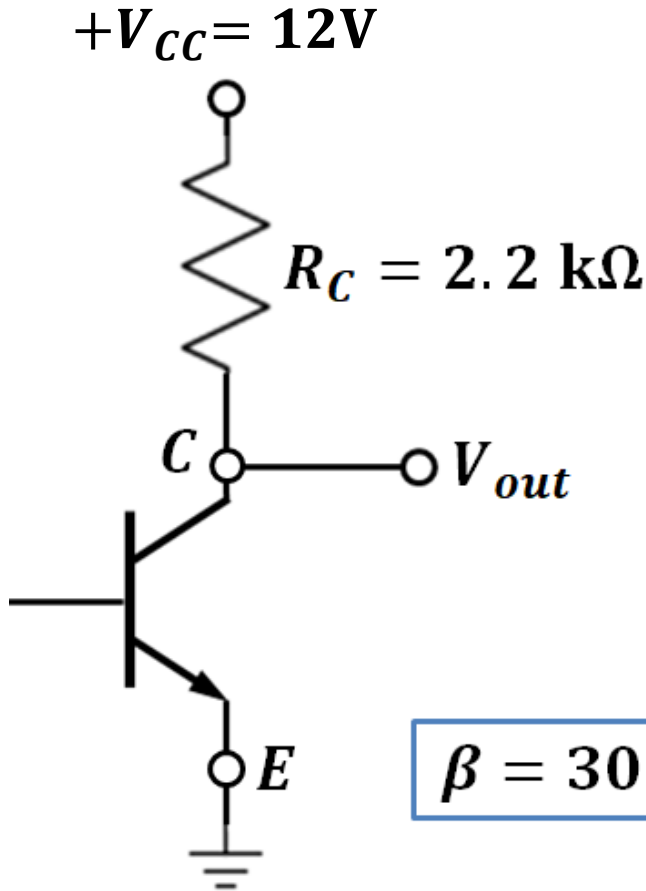
$$I_B(\text{sat}) = I_C / \beta = 0.179 \text{ mA}$$




The base current exceeds the value at onset of saturation

 **SATURATION mode**

$$I_C = I_C(\text{sat}) = 5.36 \text{ mA}$$



Indeed, this circuit behaves like a logic inverter



$V_{in}$	$V_{out}$
0.2 V	12 V
12 V	0.2 V

TRUE

1

12V

0

0.2V

FALSE

$+V_{CC} = 12V$

$R_C = 2.2 \text{ k}\Omega$

$V_{out}$

$R_1 = 15 \text{ k}\Omega$

$V_{in}$

$B$

$R_2 = 100 \text{ k}\Omega$

$E$

$\beta = 30$

$V_R = -12V$


# Simple logic gate design with BJT's

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

## Two BJT's in cascade

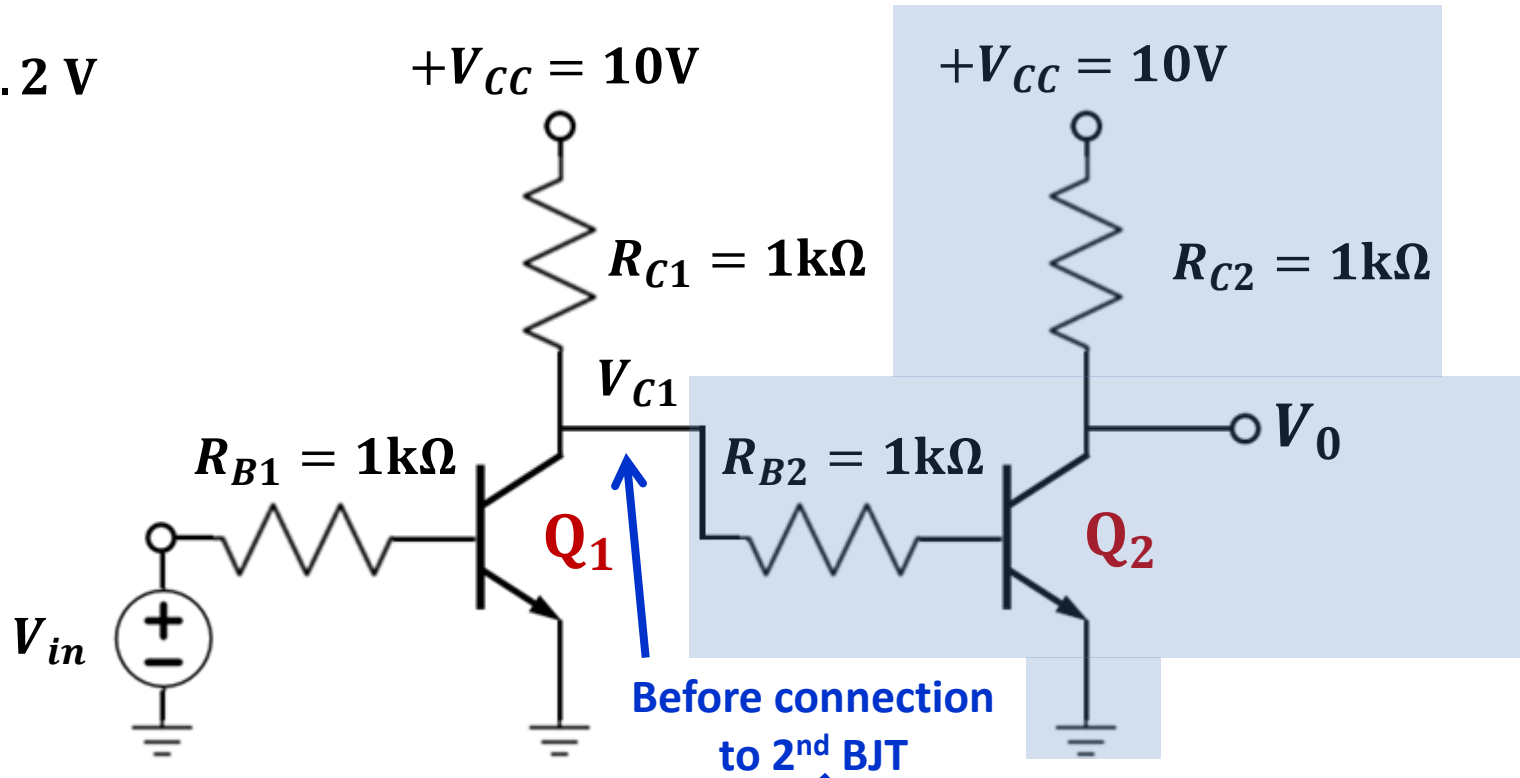

$V_{in}$	$Q_1$	$V_{C1}$		
0 V (0)	OFF	10 V (1)		
10V (1)	SAT	0.2 V (0)		

→ See next

## Two BJT's in cascade

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$


$Q_1 = \text{OFF}$

$$V_{C1} = 5.35 \text{ V}$$

$$4.65 \text{ V}$$

$$4.65 \text{ V}$$

$$0.7 \text{ V}$$

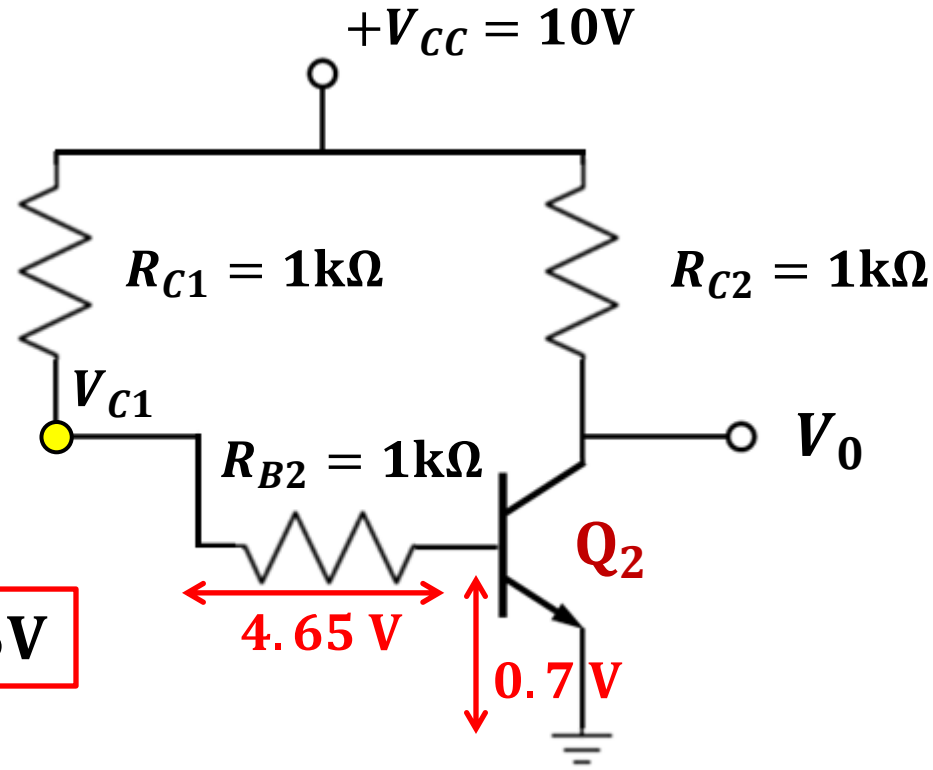

$$V_{CC} - (R_{C1} + R_{B2})I_{B2} - V_{BE}(\text{ON}) = 0$$

$$10 - 2\text{k}\Omega I_{B2} - 0.7 = 0$$

$$I_{B2} = 9.3/2\text{k} = 4.65\text{mA}$$

$$I_{C2}(\text{sat}) = \frac{10 - 0.2}{1\text{k}} = 9.8\text{mA}$$

Assuming forward-active mode

$$I_{C2} = 46.5\text{mA}$$


$Q_2 = \text{SATURATION}$

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$


$$\beta = 10$$

## Two BJT's in cascade

 

$V_{in}$	$Q_1$	$V_{C1}$	$Q_2$	$V_0$
0 V (0)	OFF	5.35V (1)	SAT	0.2 V (0)
10V (1)	SAT	0.2 V (0)	OFF	10 V (1)

## Two NOT gates in series

 


# OR Logic Gate

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$


$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

## OR

 

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 


## OR Logic Gate

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

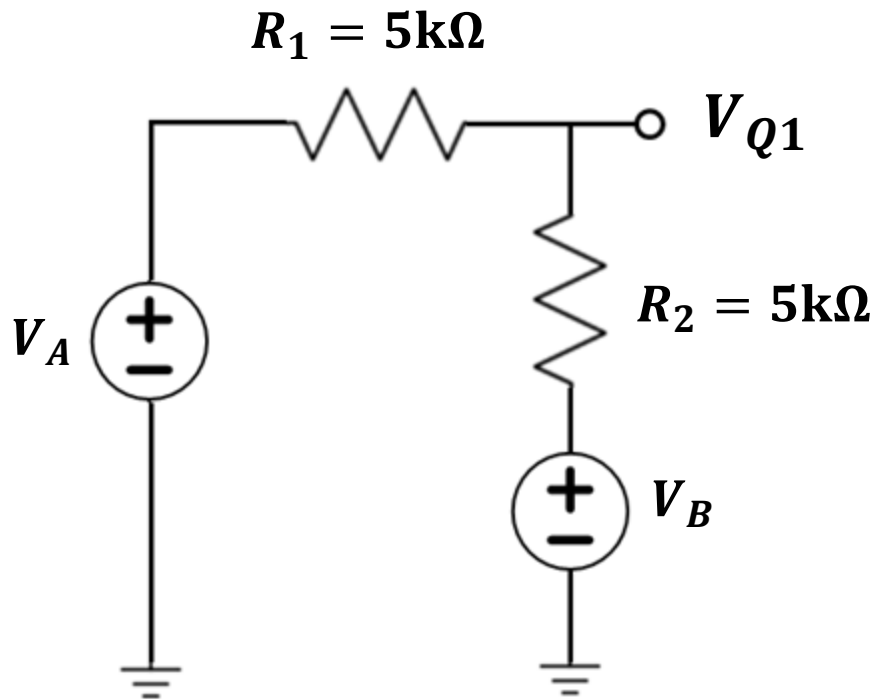

$$\frac{V_{Q1} - V_A}{5\text{k}} + \frac{V_{Q1} - V_B}{5\text{k}} = 0$$

$$V_{Q1} = \frac{V_A + V_B}{2}$$

$$V_A = 0 \quad V_B = 0$$

$$V_{Q1} = 0$$

$$V_A = 10\text{V} \quad V_B = 0$$

$$V_{Q1} = 5\text{V}$$





$$V_A = 0 \quad V_B = 10\text{V}$$

$$V_{Q1} = 5\text{V}$$

$$V_A = 10\text{V} \quad V_B = 10\text{V}$$

$$V_{Q1} = 10\text{V}$$

# Equivalent base circuit for $Q_1$

    




## OR Logic Gate

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

 

$$I_C(\text{sat}) = \frac{10 - 0.2}{1\text{k}\Omega} = 9.8\text{mA}$$

$$V_{Q1} = 0$$

$$V_1 = 10 \text{ V}$$

$$V_{Q1} = 5 \text{ V}$$

$$I_B = \frac{5 - 0.7}{2.5\text{k}\Omega} = 1.72\text{mA}$$

$$I_C = \beta I_B = 17.2\text{mA} \gg I_C(\text{sat})$$

$$V_1 = 0.2 \text{ V}$$

$$V_{Q1} = 10 \text{ V}$$

$$I_B = \frac{10 - 0.7}{2.5\text{k}\Omega} = 3.72\text{mA}$$

$$I_C = \beta I_B = 37.2\text{mA} \gg I_C(\text{sat})$$


$$V_1 = 0.2 \text{ V}$$

## OR Logic Gate

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

 

$$I_C(\text{sat}) = \frac{10 - 0.2}{1\text{k}\Omega} = 9.8\text{mA}$$

**Q<sub>1</sub> OFF**

$$I_B = \frac{10 - 0.7}{1\text{k}\Omega + 5\text{k}\Omega} = 1.55\text{mA}$$

$$I_C = \beta I_B = 15.5\text{mA} \gg I_C(\text{sat})$$

$$V_0 = 0.2 \text{ V}$$


**Q<sub>2</sub> SATURATION**

## OR Logic Gate

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

 

### $Q_1$ SATURATION

$$V_1 = V_{CE}(\text{sat}) \\ = 0.2\text{V} < V_{BE}(\text{ON})$$

$$I_B = 0$$

$$I_C = 0$$

$$V_0 = 10 \text{ V}$$


### $Q_2$ OFF

# OR Logic Gate

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

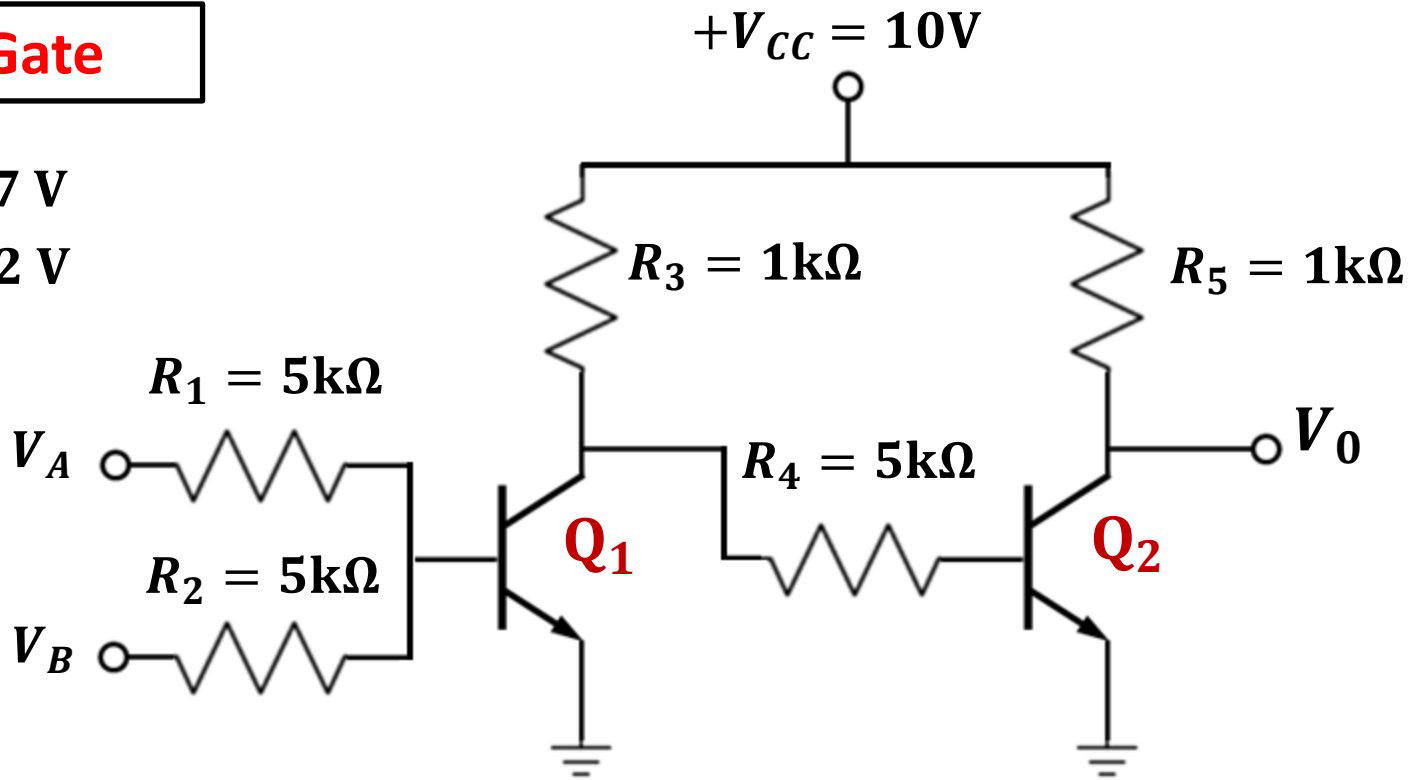


$V_A$	$V_B$	$Q_1$	$Q_2$	$V_0$
0V (0)	0V (0)	OFF	SAT	0.2 V (0)
0V (0)	10V (1)	SAT	OFF	10 V (1)
10V (1)	0V (0)	SAT	OFF	10V (1)
10V (1)	10V (1)	SAT	OFF	10V (1)

# OR Logic Gate

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$


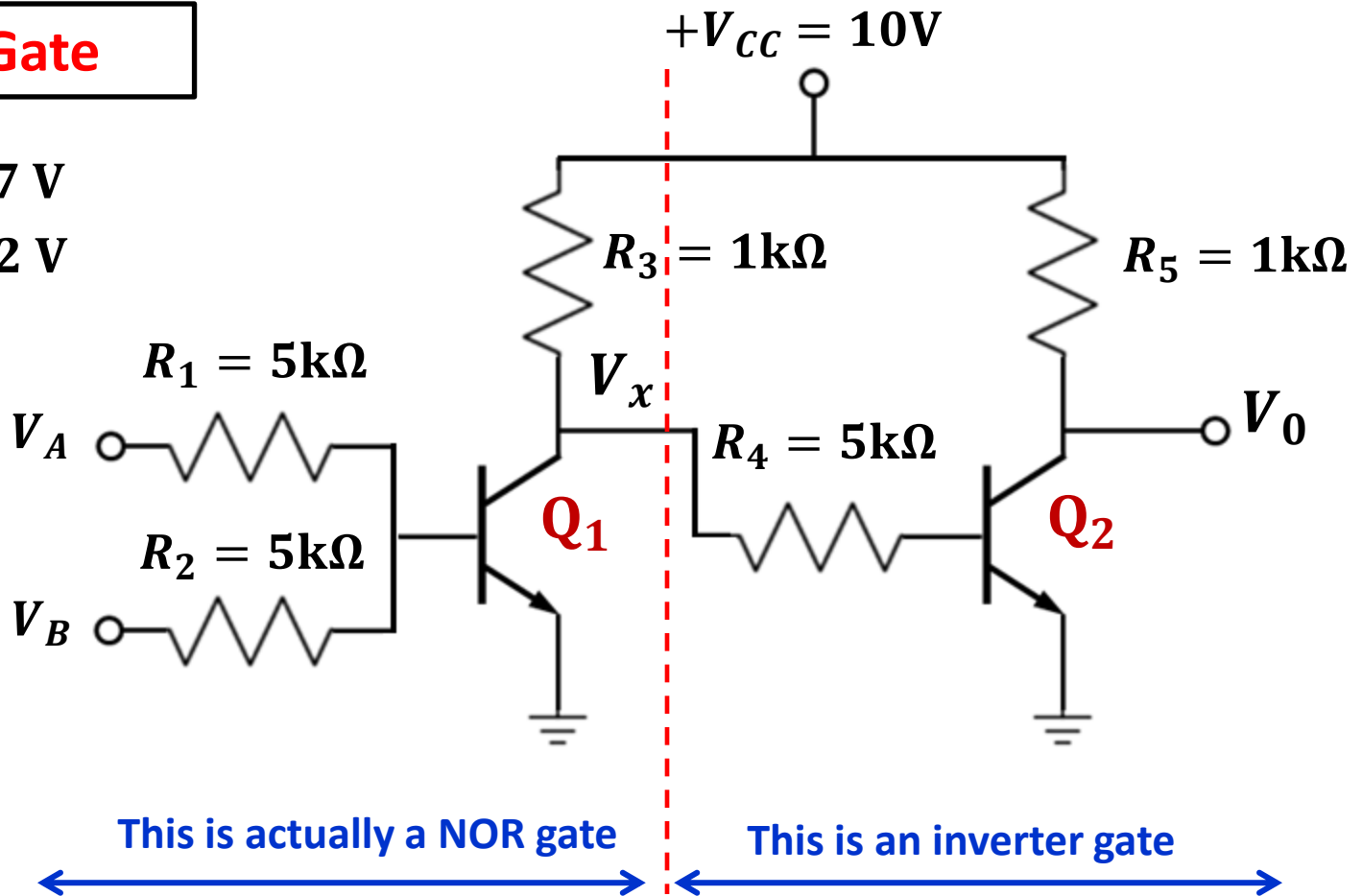


$V_A$	$V_B$	$Q_1$	$V_x$
0V	0V	OFF	10V
0V	10V	SAT	0.2V
10V	0V	SAT	0.2V
10V	10V	SAT	0.2V


After connection to  $Q_2$

$$V_x = 7.75 \text{ V}$$

# Other NOR implementations

  


Multi-transistor RTL Gate

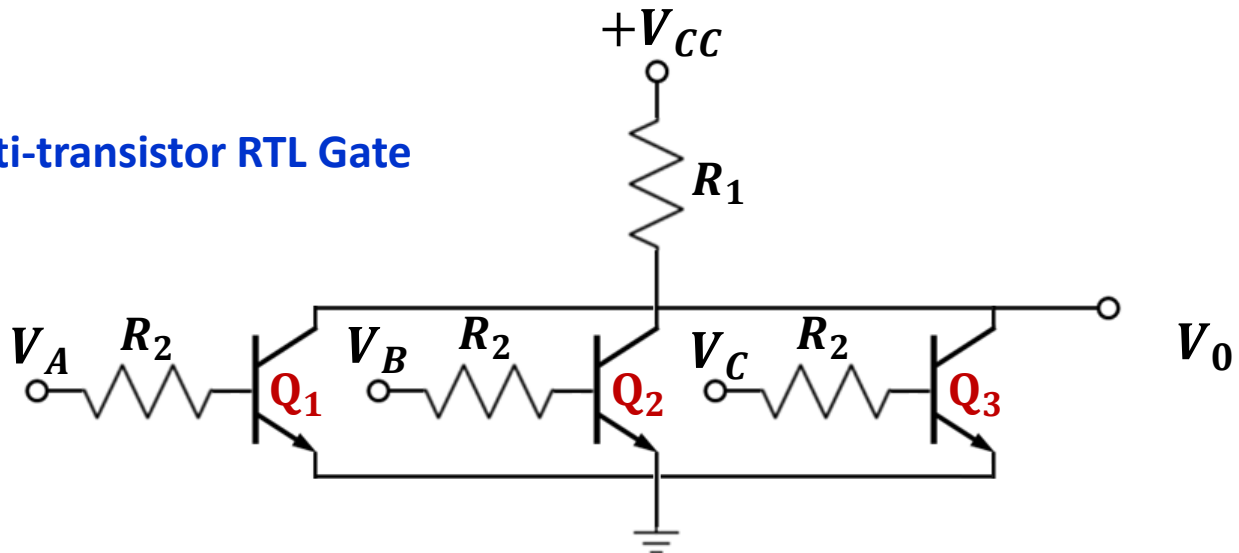


# NOR

$$V_{CC} = 10V$$

 




$V_A$	$V_B$	$Q_1$	$Q_2$	$V_0$
0V (0)	0V (0)	OFF	OFF	10 V (1)
0V (0)	10V (1)	OFF	SAT	0.2 V (0)
10V (1)	0V (0)	SAT	OFF	0.2 V (0)
10V (1)	10V (1)	SAT	SAT	0.2 V (0)

 **RTL-based NOR circuits were used in the Apollo Guidance Computer that went to the moon (the first computer using silicon integrated circuits)**





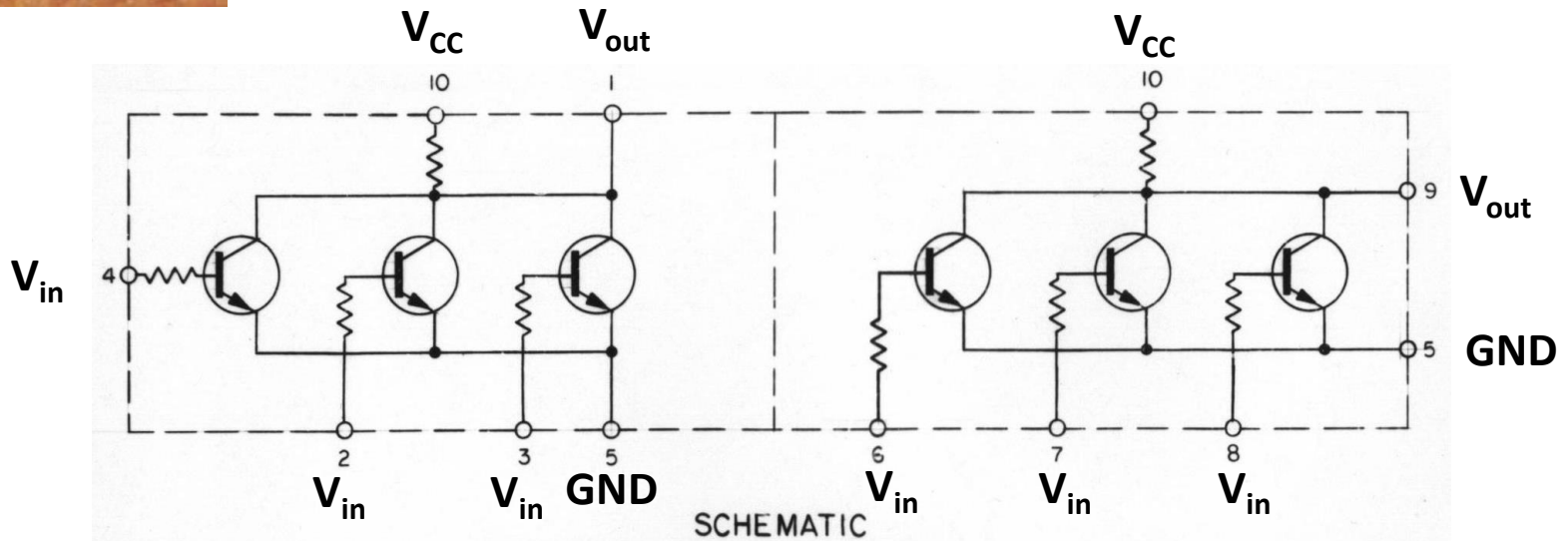  
# Silicon integrated circuit with two 3-inputs NOR gates, used in the Apollo Guidance computer.



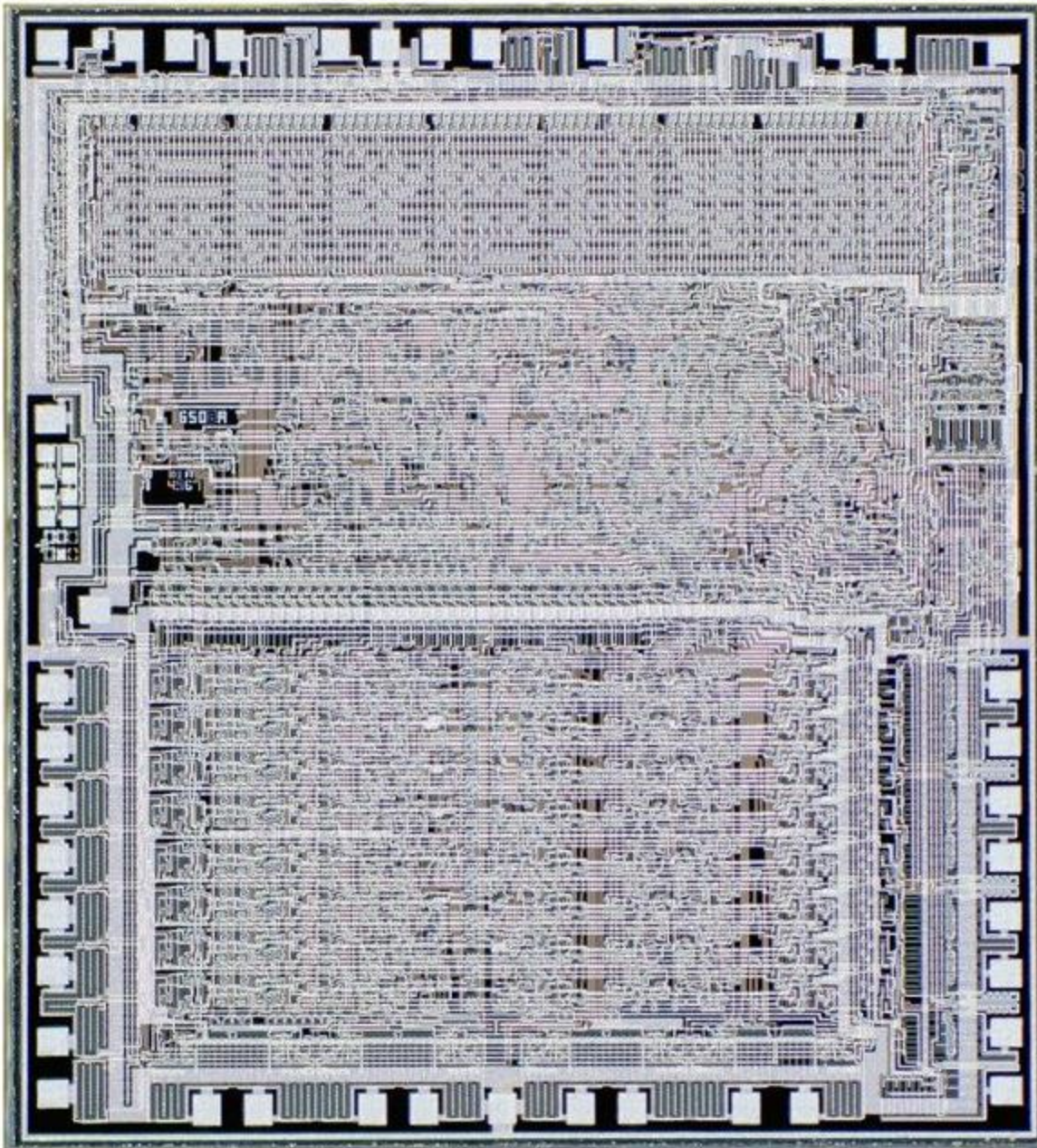THIS SCHEMATIC IS REPRESENTATIVE OF THE ELECTRICAL CHARACTERISTICS ONLY. THE PHYSICAL CIRCUITRY IS ENTIRELY CONTAINED WITHIN A MICRO NOR GATE FLAT PACK



## MOS Technology

**6502 8-bit microprocessor  
(1975)**

**3510 transistors (MOSFET)**

CPU of:

- Apple II
- Atari 400 & 800
- BBC Micro
- Commodore PET & VIC-20


# Semiconductor chips in consumer products have billions of transistors

Apple M2 Max has 67 billion MOSFETs (2023)

Apple M2 Ultra (2×M2 Max) has 134 billion MOSFETs

AMD's MI300X has 153 billion MOSFETs (2023)

 The **Wafer Scale Engine 2 (WS2)** deep-learning processor by Cerebras has 2.6 trillion MOSFETs



21.5 cm

**Cerebras WSE-2**

46,225mm<sup>2</sup> Silicon

2.6 Trillion transistors


**850,000 cores**

**Memory bandwidth = 20 Petabytes/sec**

<https://www.cerebras.net/product-chip/>
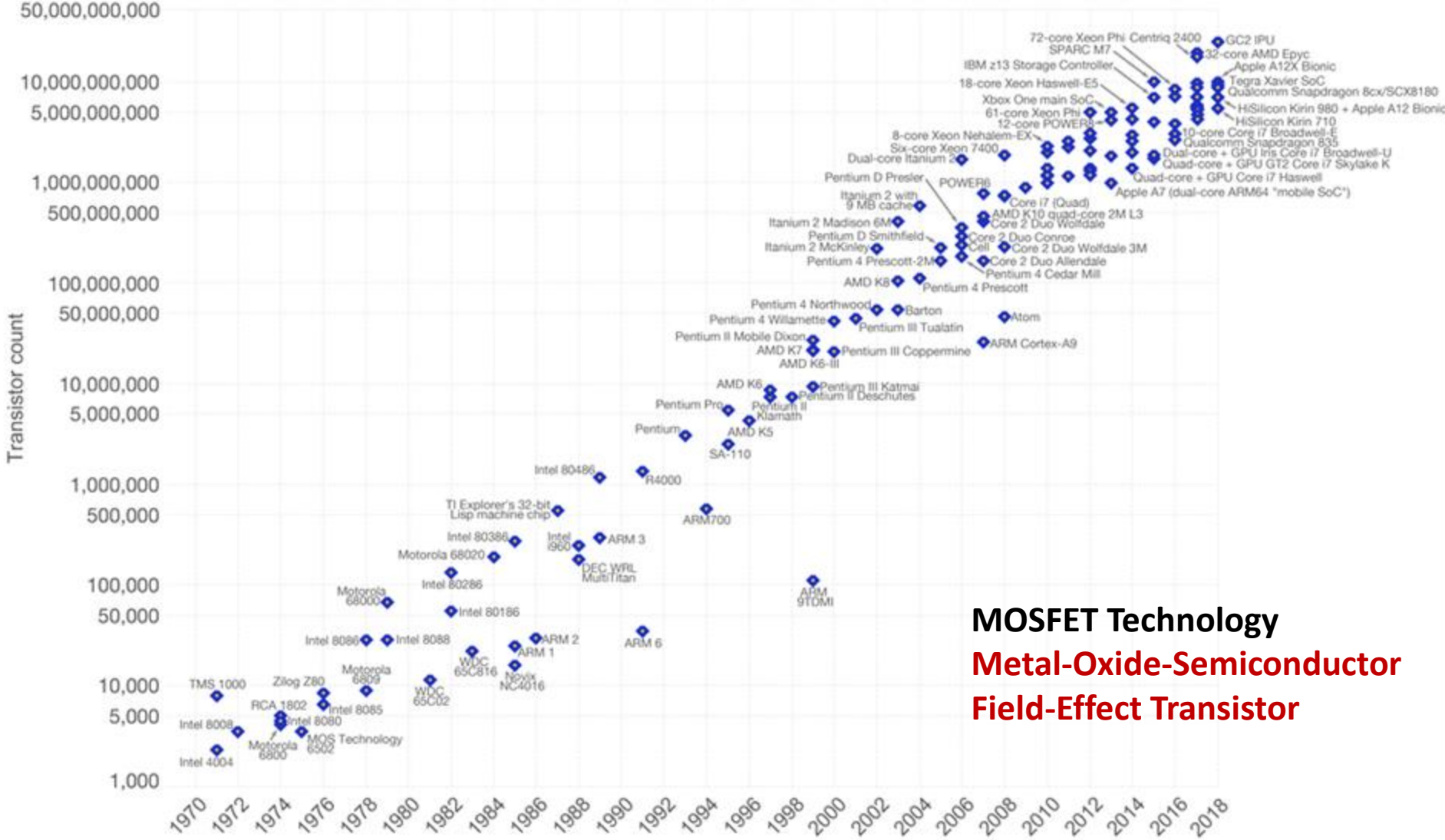
# Moore's Law – The number of transistors on integrated circuit chips (1971-2018)

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important as other aspects of technological progress – such as processing speed or the price of electronic products – are linked to Moore's law.



**MOSFET Technology**  
**Metal-Oxide-Semiconductor**  
**Field-Effect Transistor**

The data visualization is available at [OurWorldinData.org](https://ourworldindata.org).


- **Estimated number of grains of sand on Earth**  
 $\approx 7.5 \times 10^{18}$  (seven quintillion five hundred quadrillions grains)
  
- **Estimated number of transistors fabricated since 1947**  
 $\approx 2.9 \times 10^{21}$  (2.0 sextillion transistors) [2014]  
 $\approx 1.3 \times 10^{22}$  (13 sextillion transistors) [2022]
  
- **Estimated number of stars in the Universe visible with the Hubble telescope (2003)**
- **Estimated number of H<sub>2</sub>O molecules in 10 drops of water**  
 $\approx 7.0 \times 10^{22}$  (70 sextillions)

## Two transistors in series



$$V_{BE(\text{ON})} = 0.7 \text{ V}$$

$$V_{CE(\text{sat})} = 0.2 \text{ V}$$



$$\beta = 10$$

 

SLIDE #20 AGAIN

 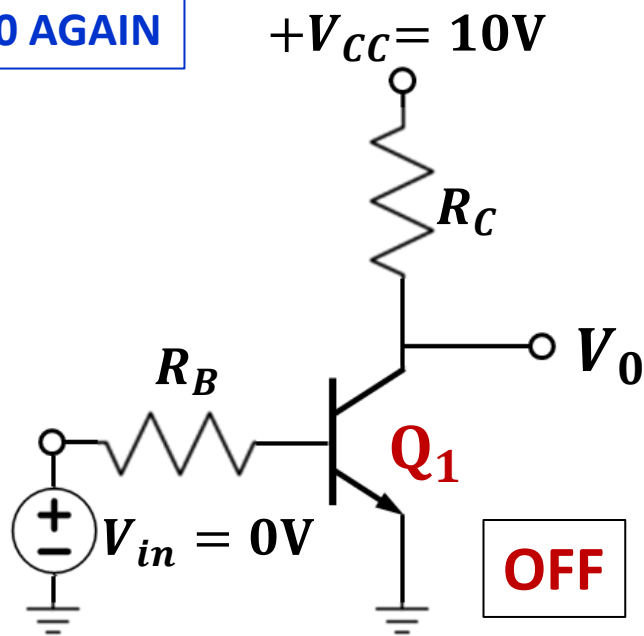

Transistors are like switches

 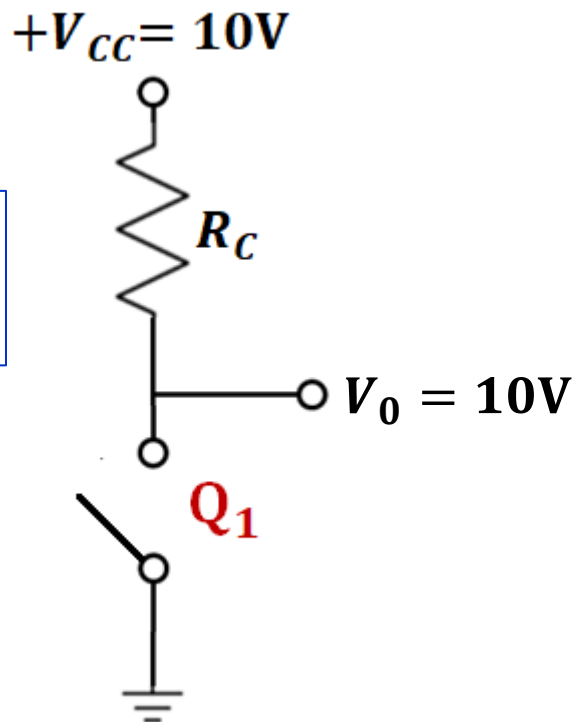



# Two transistors in series

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$

$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

$$V_A = V_B = 0 \text{ V}$$





$$V_A = 0 \text{ V}$$

$$V_B = 10 \text{ V}$$

$$V_A = 10 \text{ V}$$

$$V_B = 0 \text{ V}$$

$$V_A = V_B = 10 \text{ V}$$

 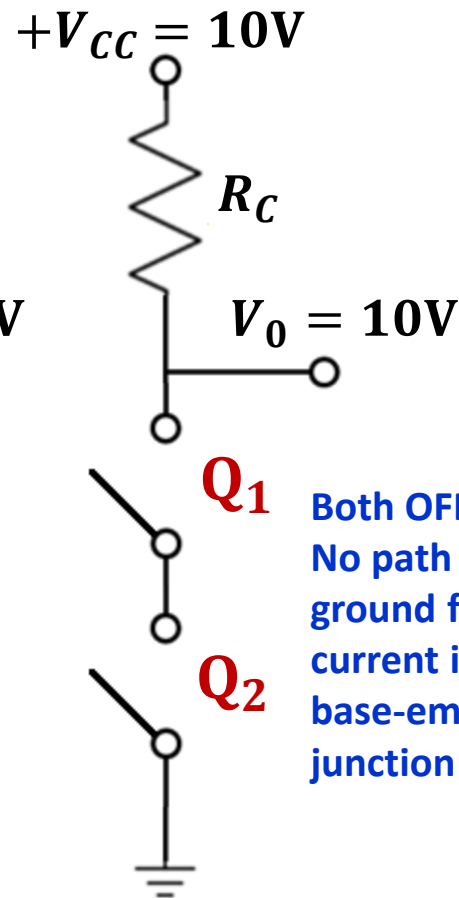  

# Two transistors in series

$$V_{BE}(\text{ON}) = 0.7 \text{ V}$$


$$V_{CE}(\text{sat}) = 0.2 \text{ V}$$

$$\beta = 10$$

## NAND



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

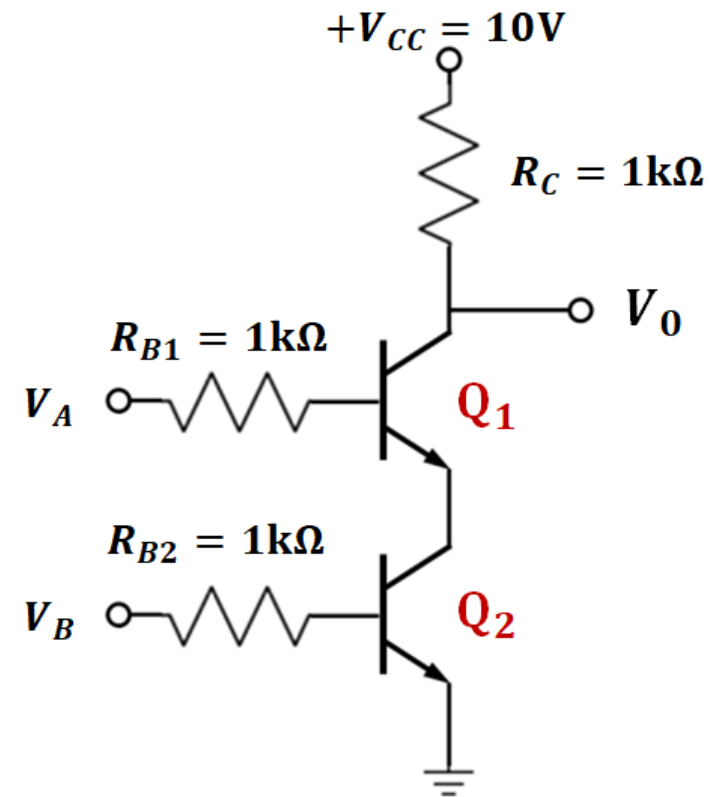


$V_A$	$V_B$	$Q_1$	$Q_2$	$V_0$
0V (0)	0V (0)	OFF	OFF	10 V (1)
0V (0)	10V (1)	OFF	SAT	10 V (1)
10V (1)	0V (0)	OFF	OFF	10V (1)
10V (1)	10V (1)	SAT	SAT	0.4V (0)

# NAND implementation with other BJT technologies


## Direct-Coupled-Transistor-Logic

### DCTL

 

## Diode-Transistor-Logic

### DTL

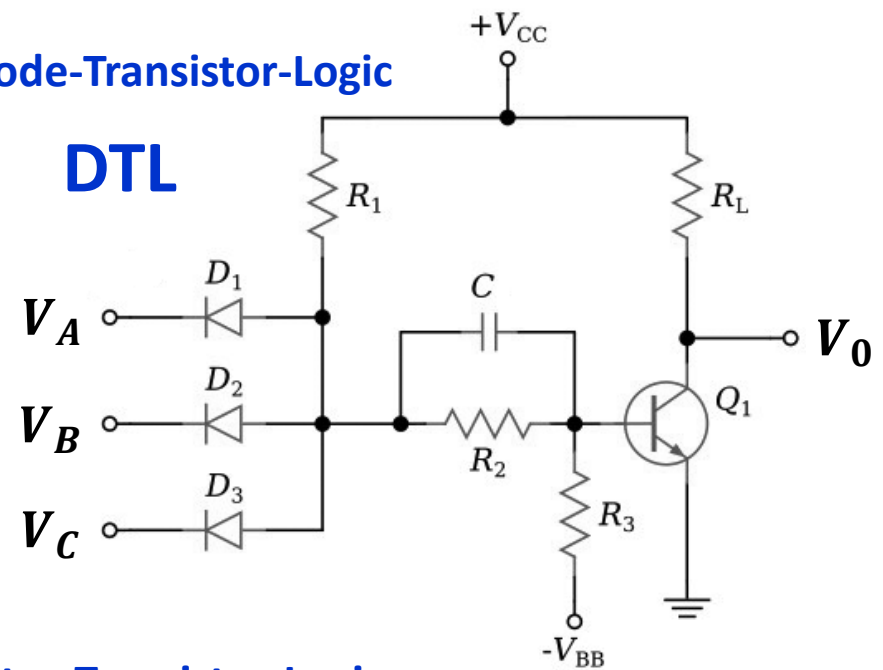

## Transistor-Transistor-Logic

### TTL

