

ECE 205 “Electrical and Electronics Circuits”

Spring 2024 – LECTURE 34

MWF – 12:00pm

Prof. Umberto Ravaioli

2062 ECE Building


Lecture 34 – Summary

Learning Objectives

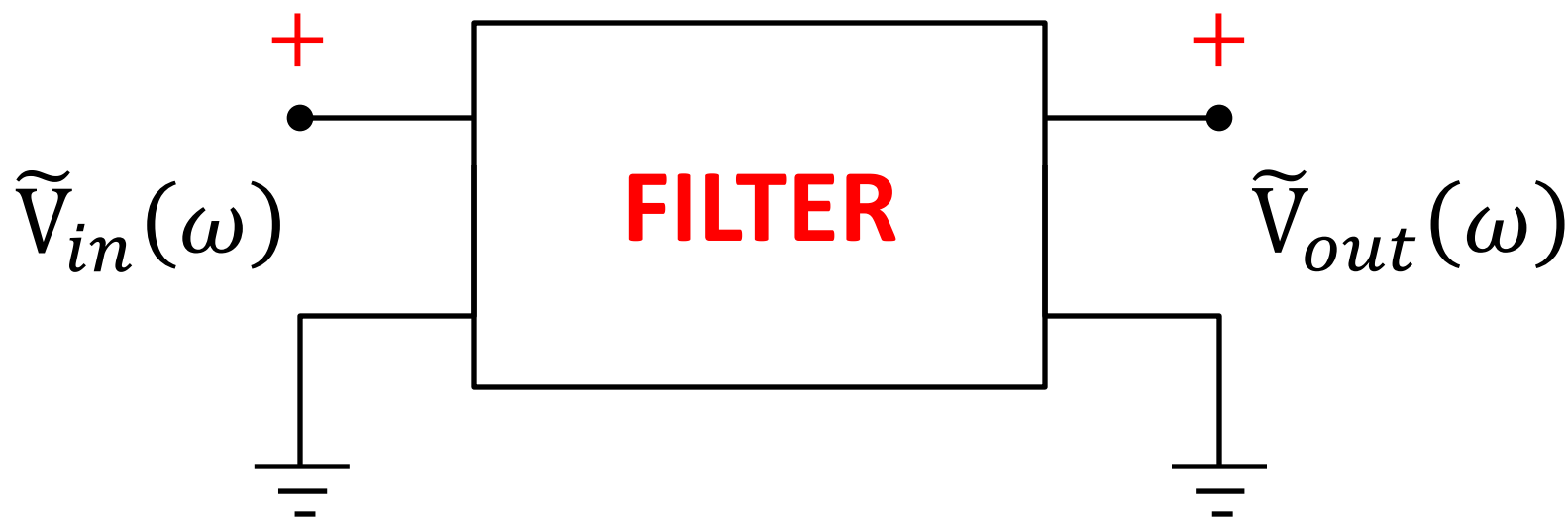1. Frequency Response of Circuits
2. Low-Pass Passives filters
3. High-Pass Passive filters

Filter

A circuit which manipulates a signal, typically by changing the relative amplitudes of the frequency components.



We will consider filters (systems) which are “single-input” and “single-output,” consisting of “linear” and “time-invariant” circuits.

Fourier transform

Converts a time domain signal $V(t)$ to a frequency domain signal $\tilde{V}(\omega)$

$$\tilde{V}(\omega) = \int_{-\infty}^{\infty} V(t) e^{-j\omega t} dt$$


In general, the Fourier Transform is a complex function

Anti-Transform

$$V(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} \tilde{V}(\omega) e^{j\omega t} d\omega$$

Transfer Function

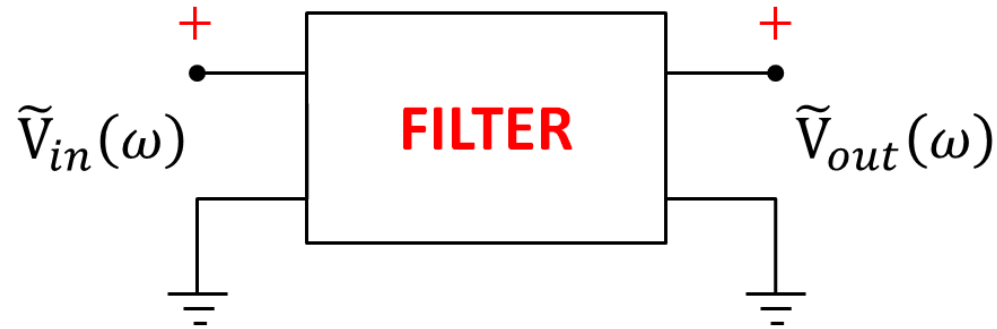The relationship linking the frequency-dependent input and output



$$\tilde{V}_{out}(\omega) = \mathbf{H}(\omega) \tilde{V}_{in}(\omega)$$

$$\mathbf{H}(\omega) = \frac{\tilde{V}_{out}(\omega)}{\tilde{V}_{in}(\omega)} = |\mathbf{H}(\omega)| \angle \theta(\omega)$$


Transfer
Function

Magnitude
Response

Phase
Response

1 – Voltage Divider

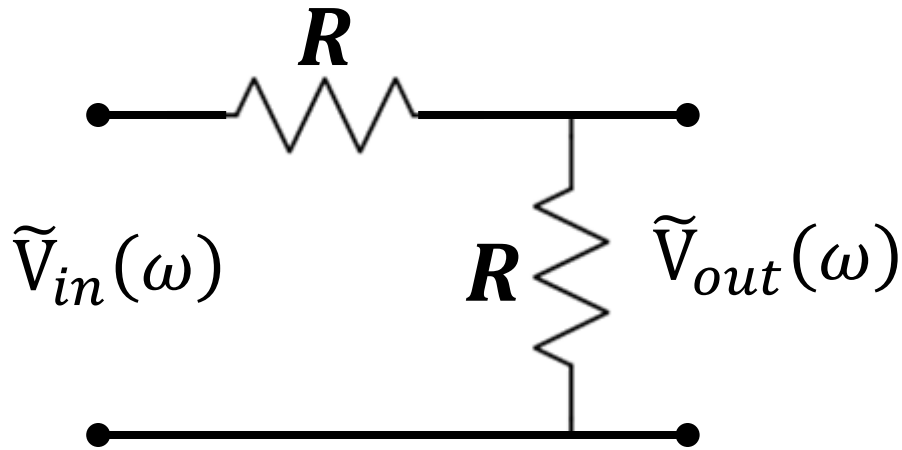
The voltage divider is a very simple filter



$$\tilde{V}_{out}(\omega) = \frac{1}{2} \tilde{V}_{in}(\omega)$$

$$\mathbf{H}(\omega) = |\mathbf{H}(\omega)| = \frac{1}{2}$$





Transfer Function

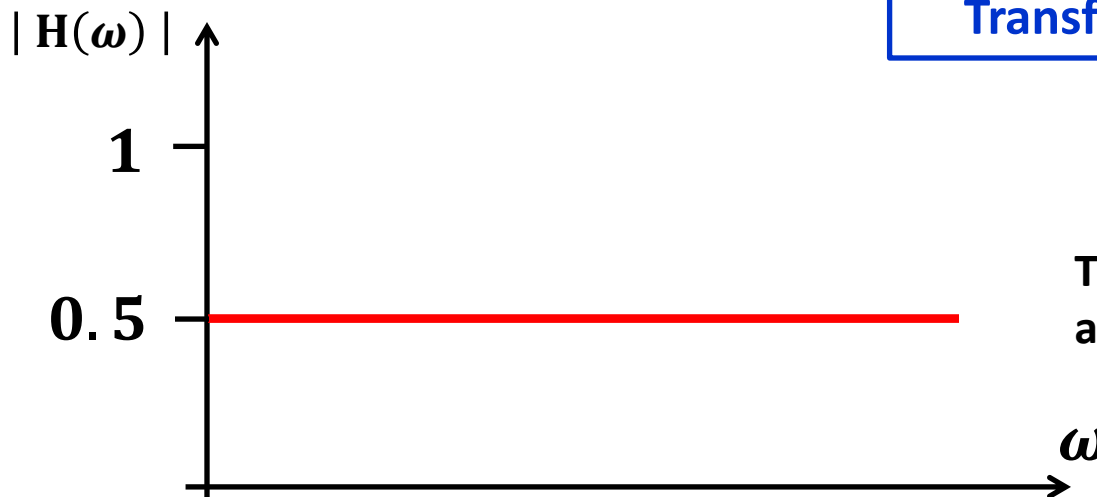

This circuit works as an “attenuator”



Behavior of Reactive Circuit Elements

Capacitor

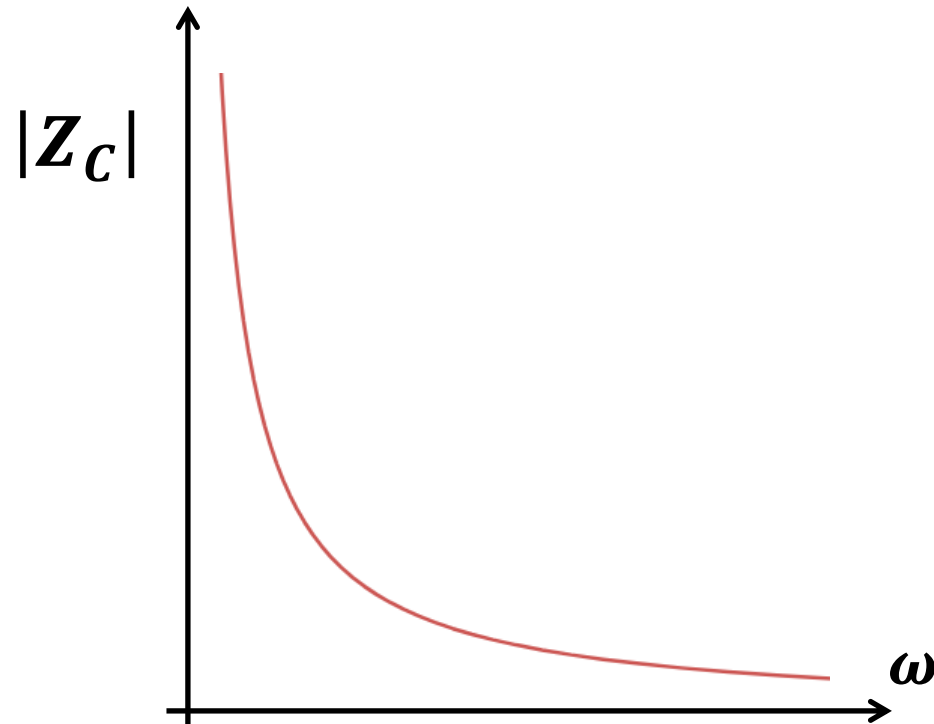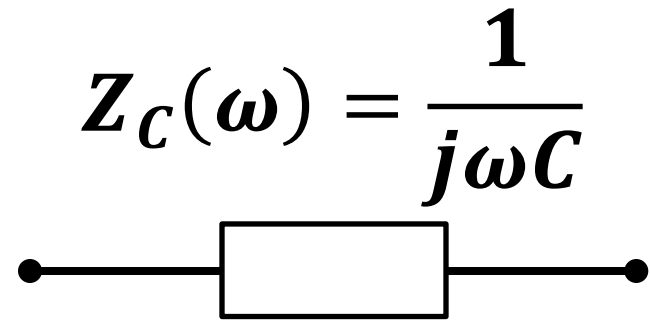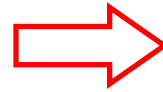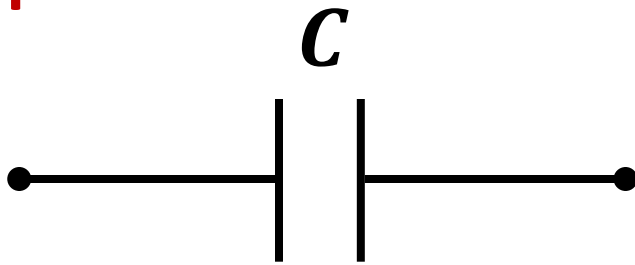



Behavior of Reactive Circuit Elements

Inductor

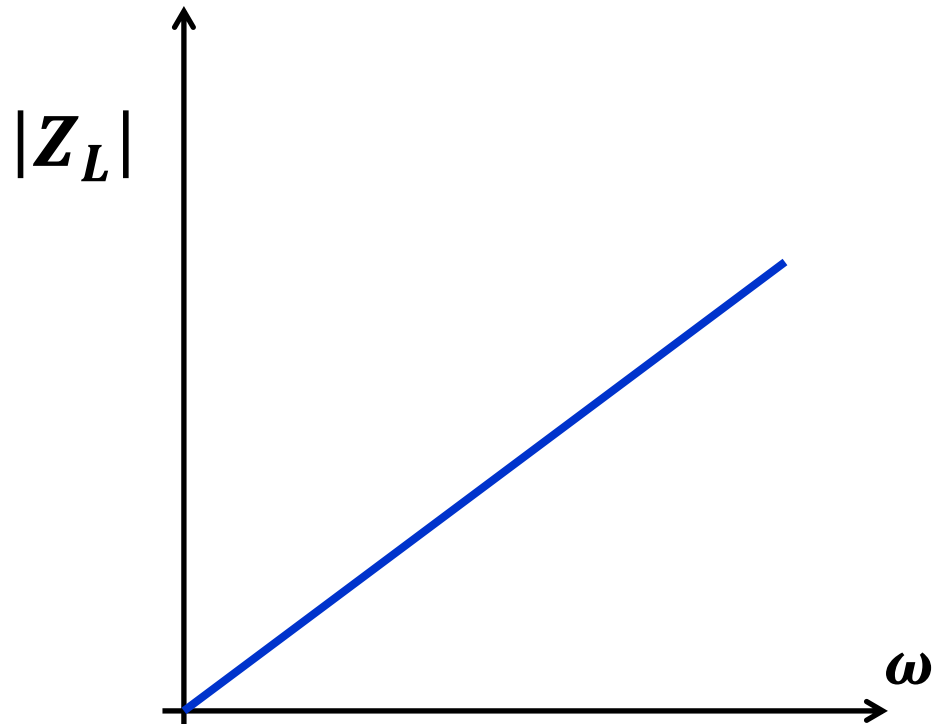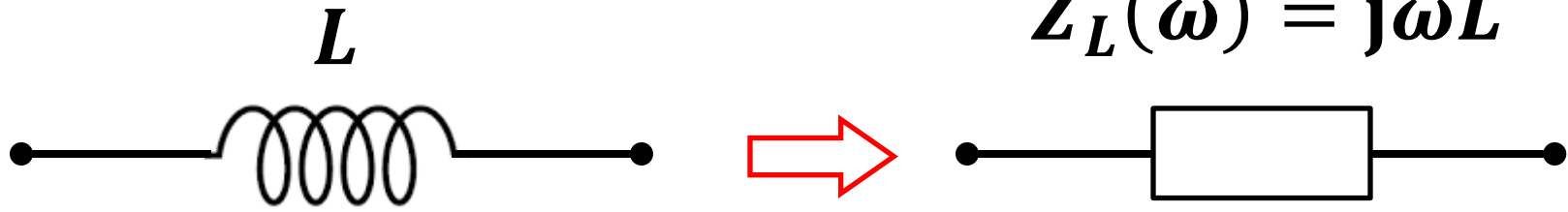



2 – Low Pass RC filter

RC filter
(1st order)

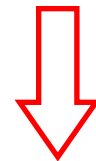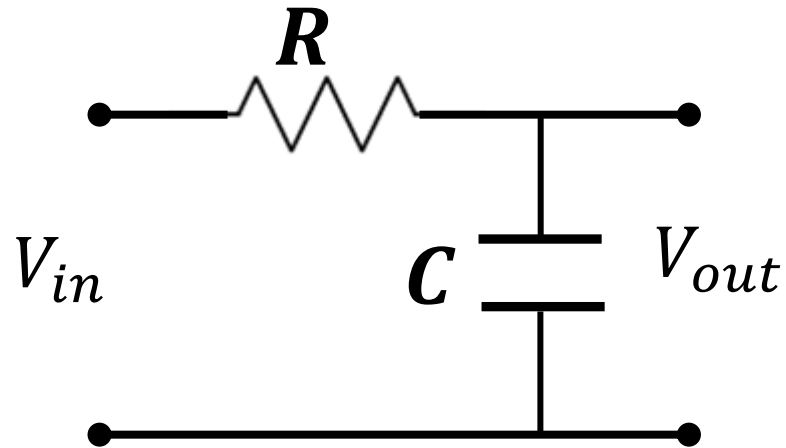

PHASORS

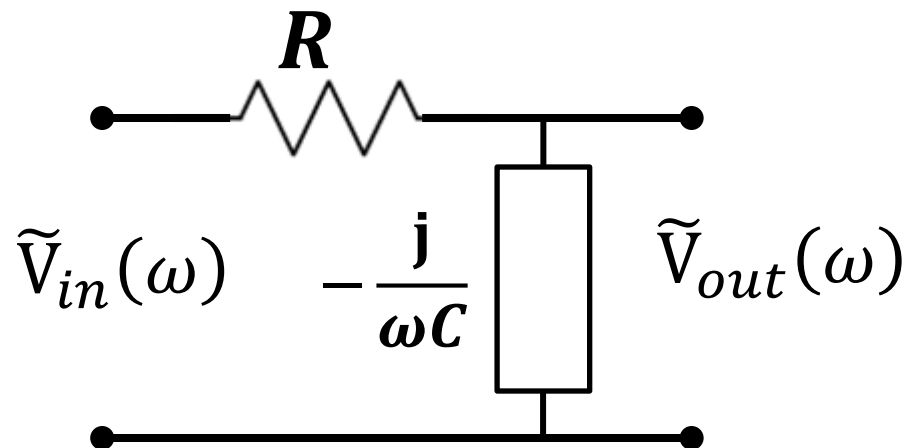

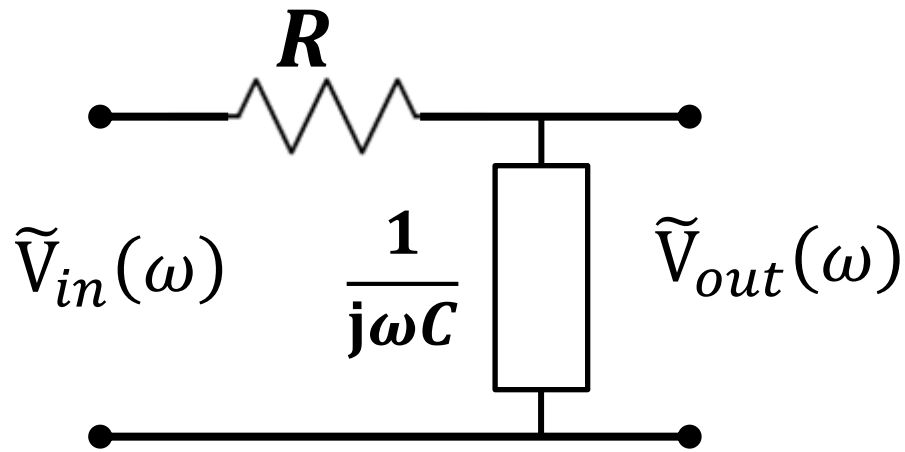

Let the input be a phasor of the form

$$\tilde{V}_{in}(\omega) = V_I \angle 0^\circ$$

$$\tilde{V}_{out}(\omega) = V_I \angle 0^\circ \frac{1/j\omega C}{R + 1/j\omega C} = \overbrace{V_I \angle 0^\circ}^{\tilde{V}_{in}(\omega)} \frac{1}{1 + j\omega RC}$$

$$\frac{\tilde{V}_{out}(\omega)}{\tilde{V}_{in}(\omega)} = \mathbf{H}(\omega) = \frac{1}{1 + j\omega RC}$$

Transfer Function

$$\mathbf{H(\omega) = \frac{1}{1 + j\omega RC}}$$

$$\mathbf{H(\omega) = \frac{1 - j\omega RC}{(1 + j\omega RC)(1 - j\omega RC)} = \frac{1 - j\omega RC}{1 + (\omega RC)^2}}$$

Cartesian Form

Magnitude

$$|\mathbf{H(\omega)}| = \frac{1}{|1 + j\omega RC|}$$


$$|\mathbf{H(\omega)}| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

Magnitude of $H(\omega)$ for RC low-pass filter

At $\omega = \omega_c$: $R = 1/\omega C$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$


$\omega_c RC = 1 \rightarrow |H(\omega_c)| = \frac{1}{\sqrt{1 + 1}} = \frac{1}{\sqrt{2}} = 0.707$

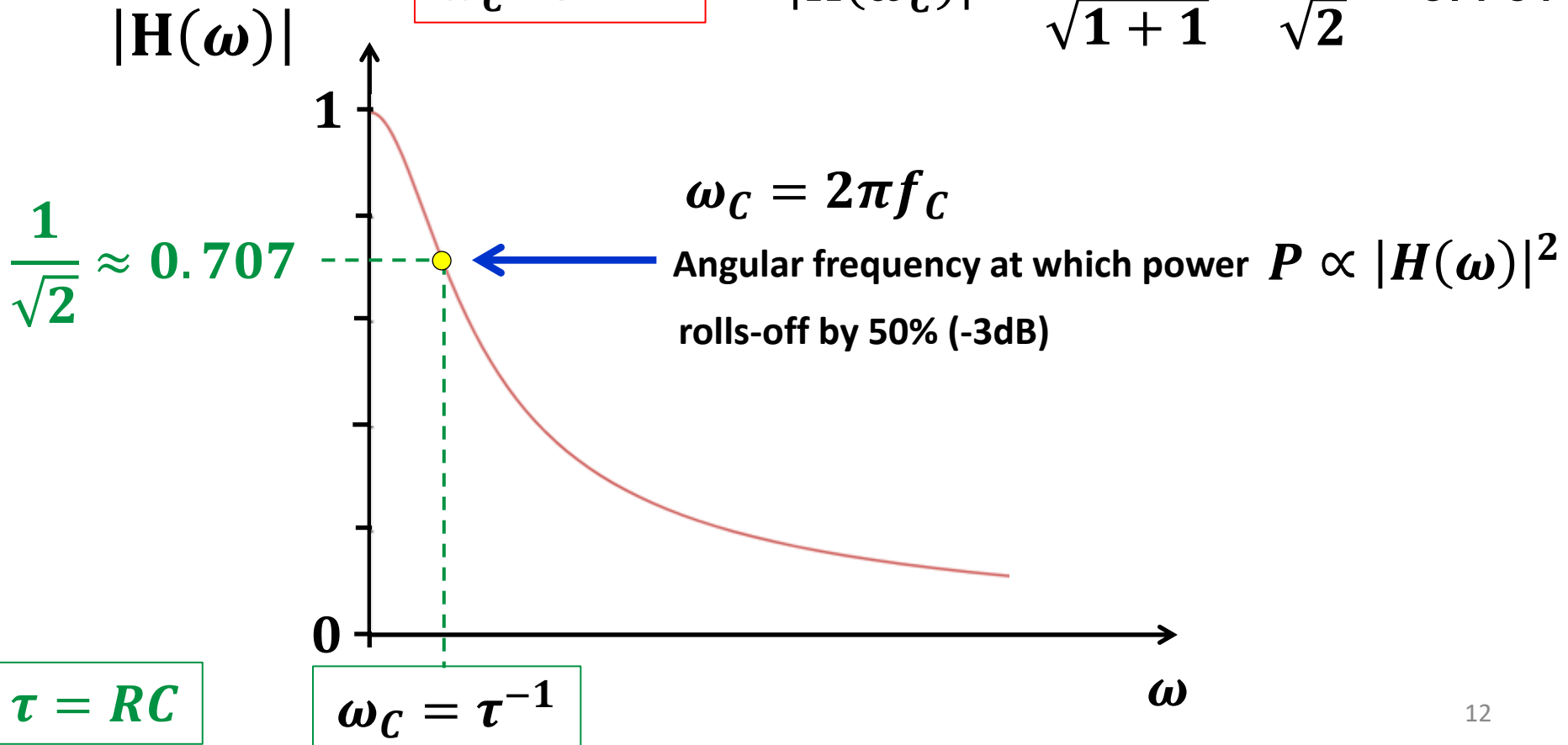

log-decibel representation – Bode Plot for magnitude

NOTE: This plot is normalized so that $\omega_C = 1$
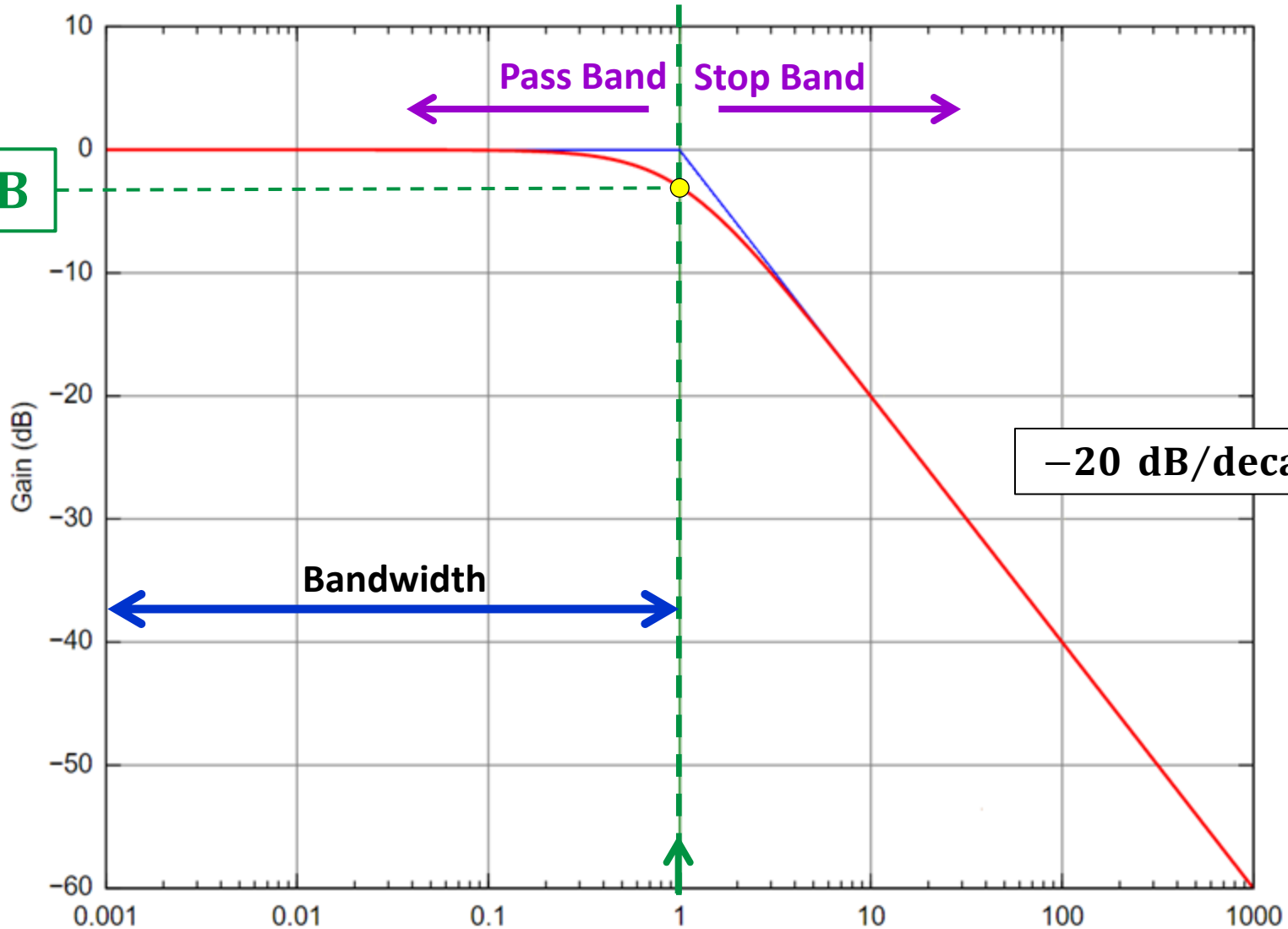
$$20 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$$




Cut-off frequency

$$\omega_C = 2\pi f_C$$

ω [rad/s]

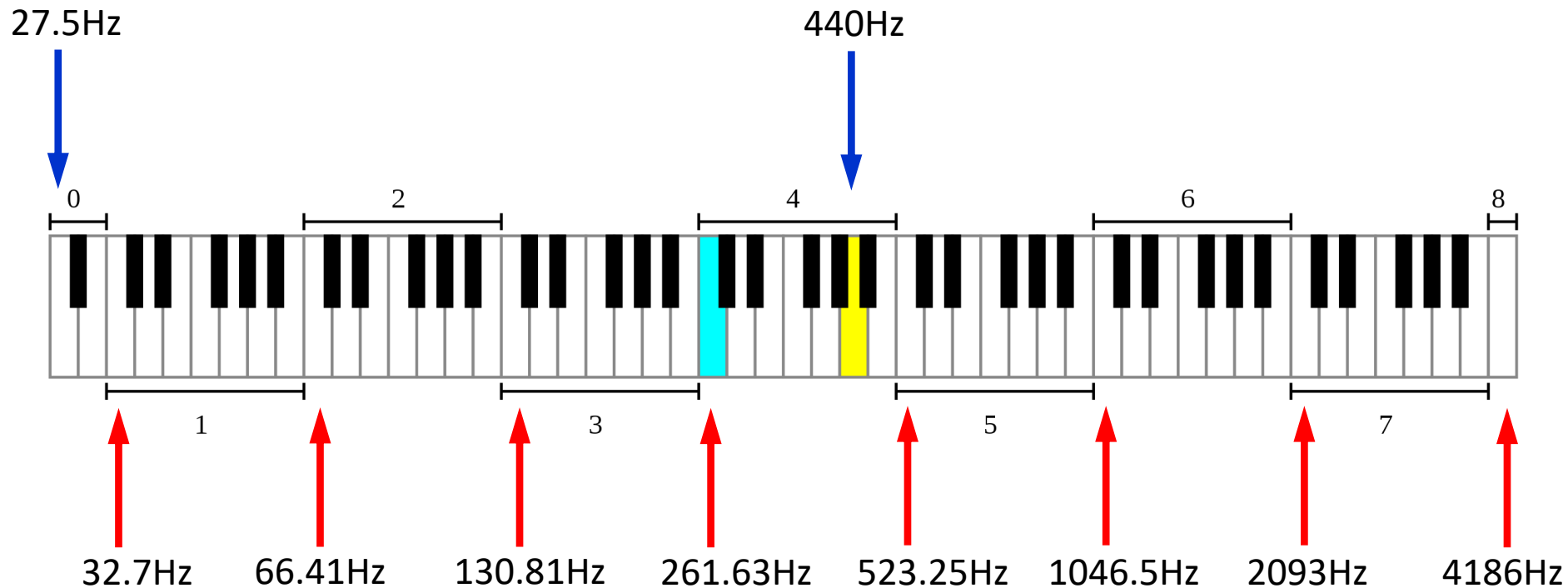The piano keyboard uses octaves (instead of decades)



Phase of $H(\omega)$ for RC low-pass filter

$$H(\omega) = \frac{1 - j\omega RC}{(1 + j\omega RC)(1 - j\omega RC)} = \frac{1 - j\omega RC}{\underbrace{1 + (\omega RC)^2}_{\text{Cartesian Form}}}$$

Phase of $H(\omega)$ for RC low-pass filter

$$H(\omega) = \frac{1 - j\omega RC}{(1 + j\omega RC)(1 - j\omega RC)} = \frac{1 - j\omega RC}{\underbrace{1 + (\omega RC)^2}_{\text{Cartesian Form}}}$$

$$\angle H(\omega) = \tan^{-1} \frac{\Im\{H(\omega)\}}{\Re\{H(\omega)\}} = \tan^{-1} \frac{-\omega RC / (1 + (\omega RC)^2)}{1 / (1 + (\omega RC)^2)}$$

Phase of $H(\omega)$ for RC low-pass filter

$$H(\omega) = \frac{1 - j\omega RC}{(1 + j\omega RC)(1 - j\omega RC)} = \frac{1 - j\omega RC}{\underbrace{1 + (\omega RC)^2}_{\text{Cartesian Form}}}$$

$$\angle H(\omega) = \tan^{-1} \frac{\Im\{H(\omega)\}}{\Re\{H(\omega)\}} = \tan^{-1} \frac{-\omega RC / (1 + (\omega RC)^2)}{1 / (1 + (\omega RC)^2)}$$

$$\angle H(\omega) = \tan^{-1}(-\omega RC) = -\tan^{-1}(\omega RC)$$


When $\omega = \omega_c$ we have $\omega_c RC = 1$

$$\angle H(\omega) = \tan^{-1}(-1) = -\frac{\pi}{4} = -45^\circ$$

Phase for RC low-pass filter

Linear scale representation

$\angle H(\omega)$ [rad]

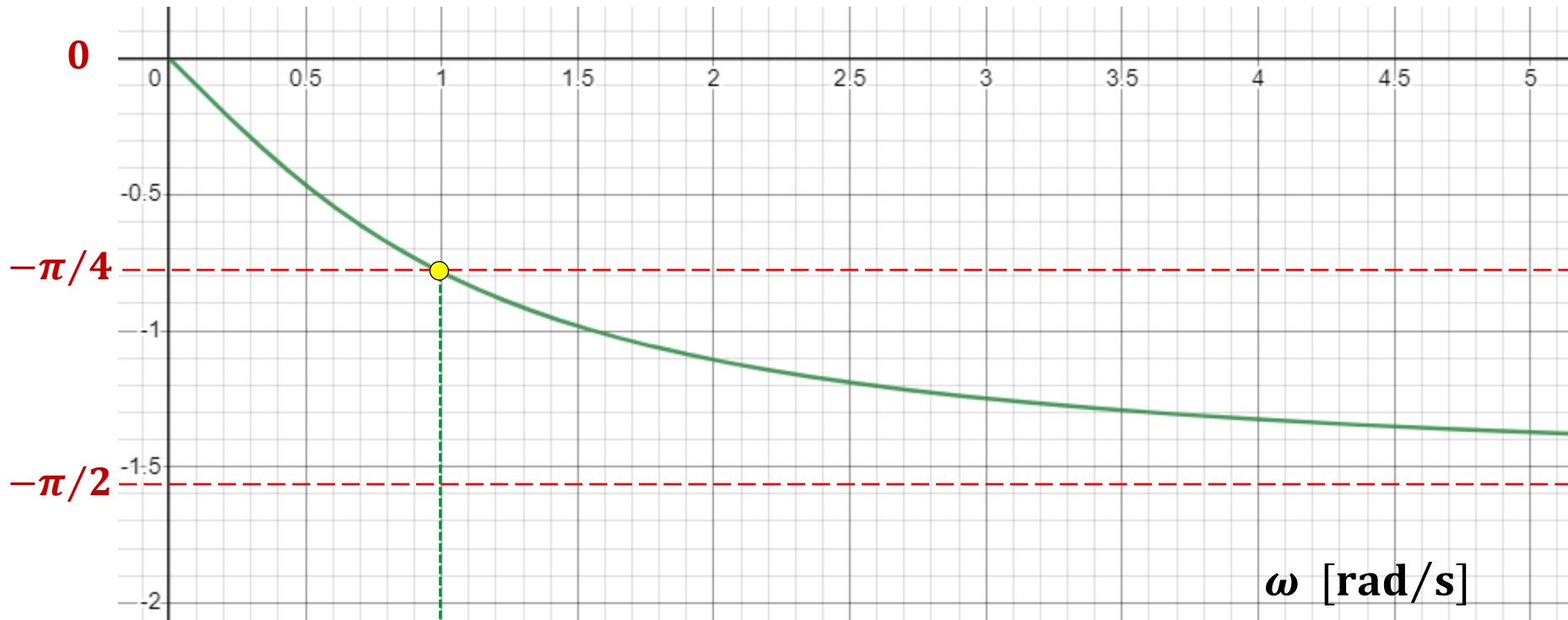


$$\omega_c = 2\pi f_c$$

Phase for RC low-pass filter

semi-log scale representation – Bode Plot for phase

NOTE: This plot is normalized so that $\omega_c = 1$

$\angle H(\omega)$

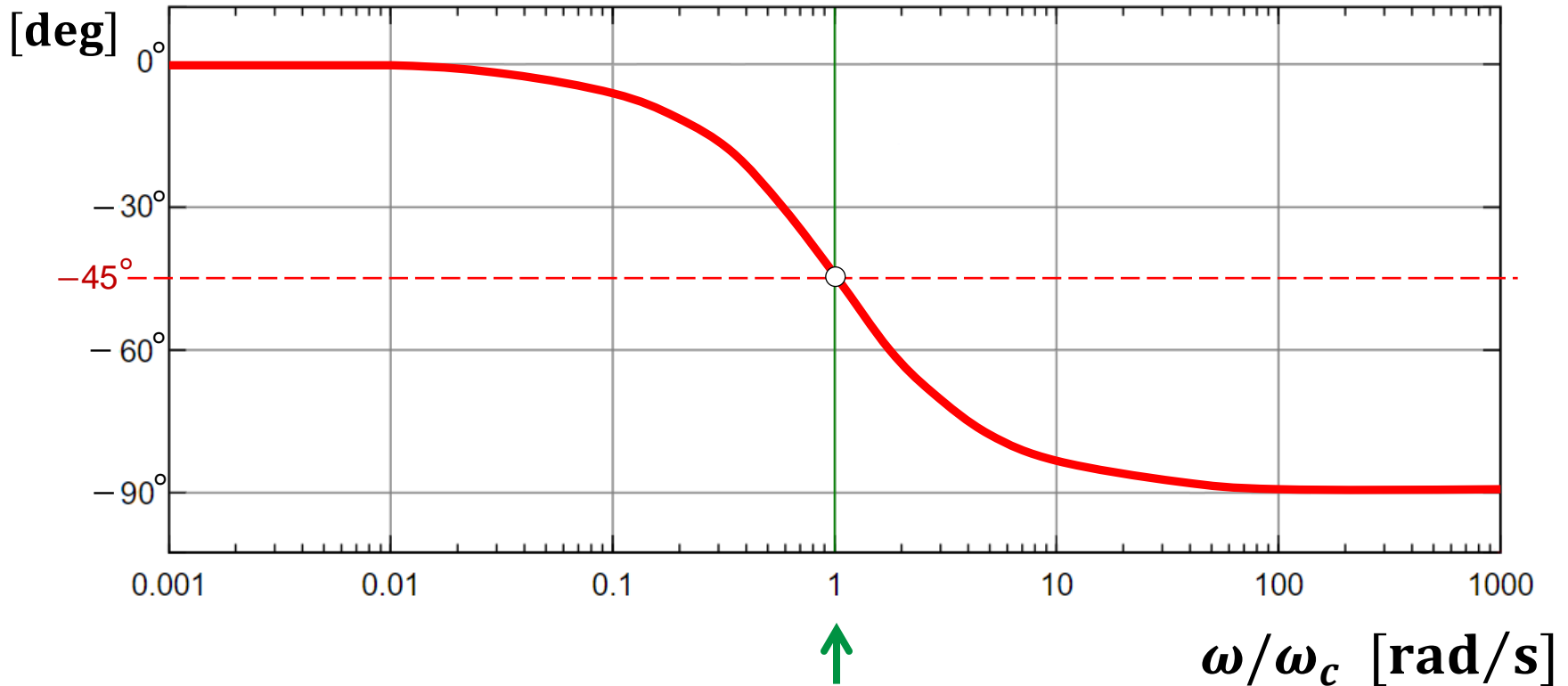

$$\omega_c = 2\pi f_c$$

Example - RC low-pass filter

ω_1

Consider $R = 2.5 \text{ k}\Omega$ and $C = 400 \text{ nF}$

$$\omega_c = 1/(RC) = (2.5\text{k} \times 400 \times 10^{-9})^{-1} = 10^3 \text{ rad/s}$$

$$f = 60\text{Hz}$$

$$\omega_1 \approx 377 \text{ rad/s}$$

Example - RC low-pass filter

ω_1

Consider $R = 2.5 \text{ k}\Omega$ and $C = 400 \text{ nF}$

$$\omega_c = 1/(RC) = (2.5\text{k} \times 400 \times 10^{-9})^{-1} = 10^3 \text{ rad/s}$$

$$f = 60\text{Hz}$$


$$\omega_1 \approx 377 \text{ rad/s}$$

$$\omega_1 RC = 2\pi \times 60 \times 2.5\text{k} \times 400 \times 10^{-9} \approx 377.0$$

$$|H(\omega_1)| = \frac{1}{\sqrt{1 + (\omega_1 RC)^2}} = 0.9357$$

$$|H(\omega_1)|_{\text{dB}} = 20 \log_{10}(0.9357) = -0.5772 \text{ dB}$$
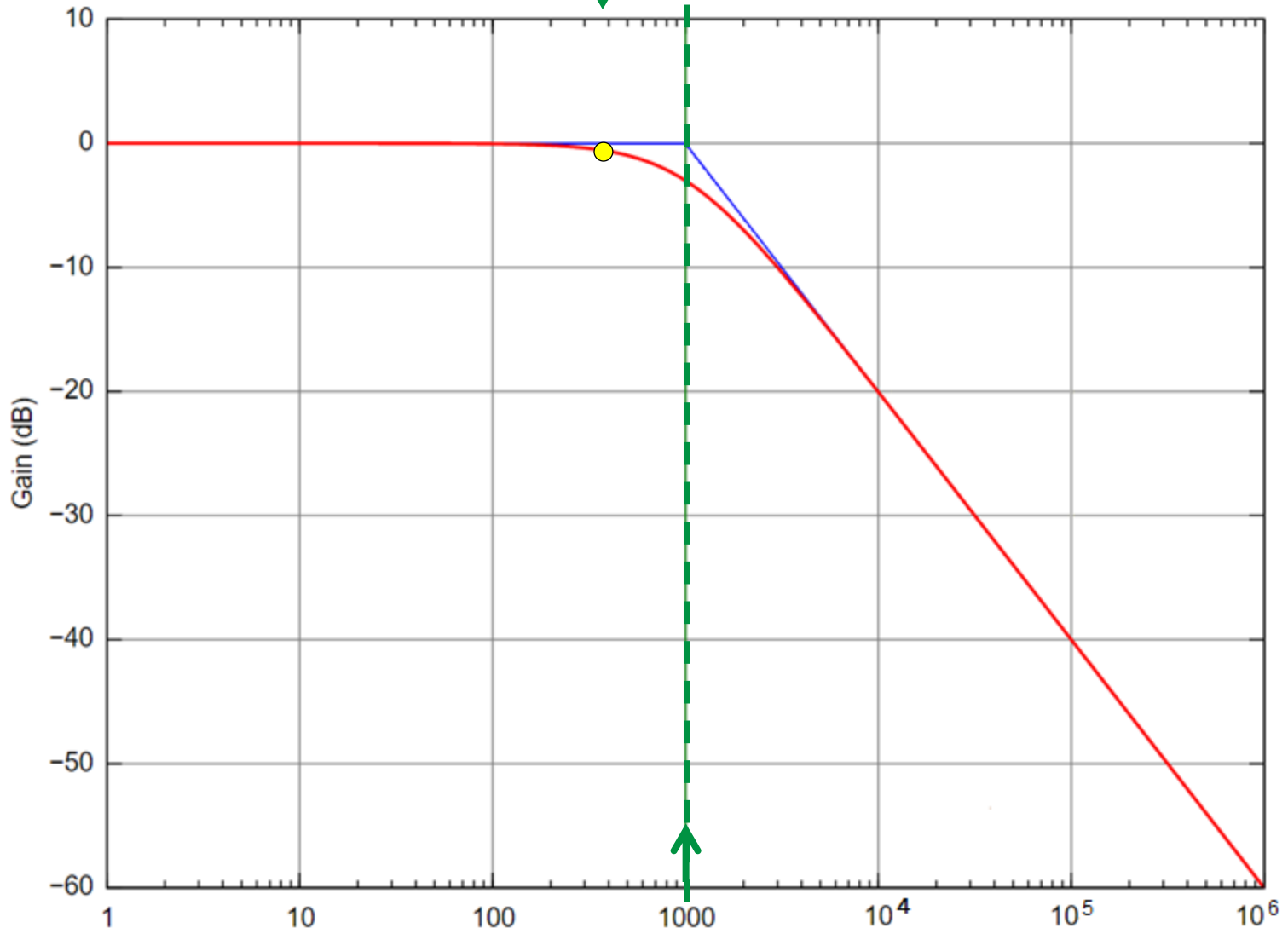
$$20 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$$



$$\omega_c = 2\pi f_c$$

Example - RC low-pass filter

ω_2

Consider $R = 2.5 \text{ k}\Omega$ and $C = 400 \text{ nF}$

$$\omega_c = 1/(RC) = (2.5\text{k} \times 400 \times 10^{-9})^{-1} = 10^3 \text{ rad/s}$$

$$f = 160\text{Hz}$$

$$\omega_2 = 1005.3 \text{ rad/s}$$

Example - RC low-pass filter

ω_2

Consider $R = 2.5 \text{ k}\Omega$ and $C = 400 \text{ nF}$

$$\omega_c = 1/(RC) = (2.5\text{k} \times 400 \times 10^{-9})^{-1} = 10^3 \text{ rad/s}$$

$$f = 160\text{Hz}$$


$$\omega_2 = 1005.3 \text{ rad/s}$$

$$\omega_2 RC = 2\pi \times 160 \times 2.5\text{k} \times 400 \times 10^{-9} \approx 1.0$$

$$|H(\omega_2)| = \frac{1}{\sqrt{1 + (\omega_2 RC)^2}} = 0.7052$$

$$|H(\omega_2)|_{\text{dB}} = 20 \log_{10}(0.7052) = -3.033 \text{ dB}$$
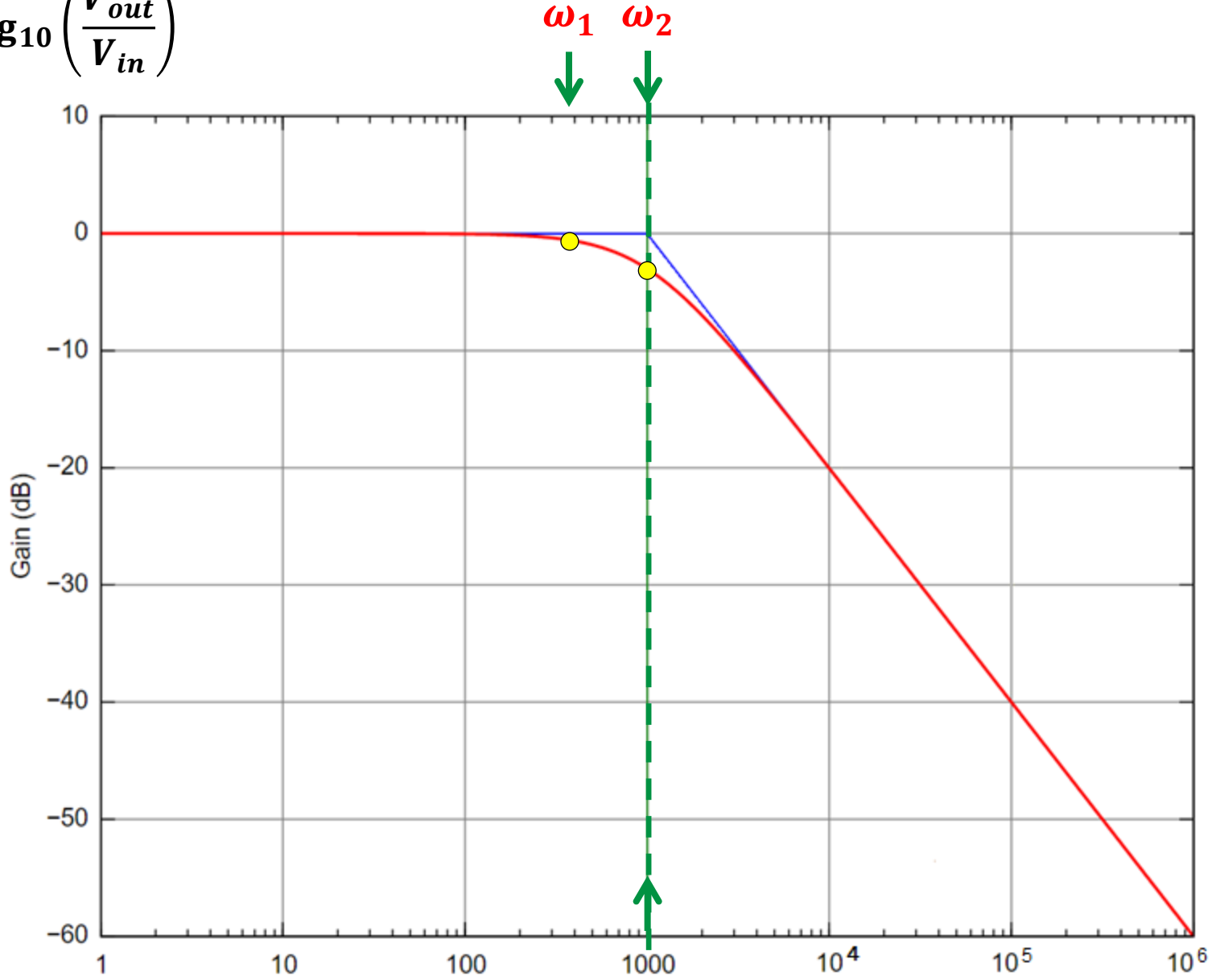
$$20 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$$



$$\omega_c = 2\pi f_c$$

Example - RC low-pass filter

ω_3

Consider $R = 2.5 \text{ k}\Omega$ and $C = 400 \text{ nF}$

$$\omega_c = 1/(RC) = (2.5\text{k} \times 400 \times 10^{-9})^{-1} = 10^3 \text{ rad/s}$$

$$f = 16 \text{ kHz}$$

$$\omega_3 = 100,530 \text{ rad/s}$$

Example - RC low-pass filter

ω_3

Consider $R = 2.5 \text{ k}\Omega$ and $C = 400 \text{ nF}$

$$\omega_c = 1/(RC) = (2.5\text{k} \times 400 \times 10^{-9})^{-1} = 10^3 \text{ rad/s}$$

$$f = 16 \text{ kHz}$$


$$\omega_3 = 100,530 \text{ rad/s}$$

$$\omega_3 RC = 2\pi \times 16\text{k} \times 2.5\text{k} \times 400 \times 10^{-9} \approx 100.53$$

$$|\mathbf{H}(\omega_3)| = \frac{1}{\sqrt{1 + (\omega_3 RC)^2}} = 0.0099$$


$$|\mathbf{H}(\omega_3)|_{\text{dB}} = 20 \log_{10}(0.0099) = -40.046 \text{ dB}$$
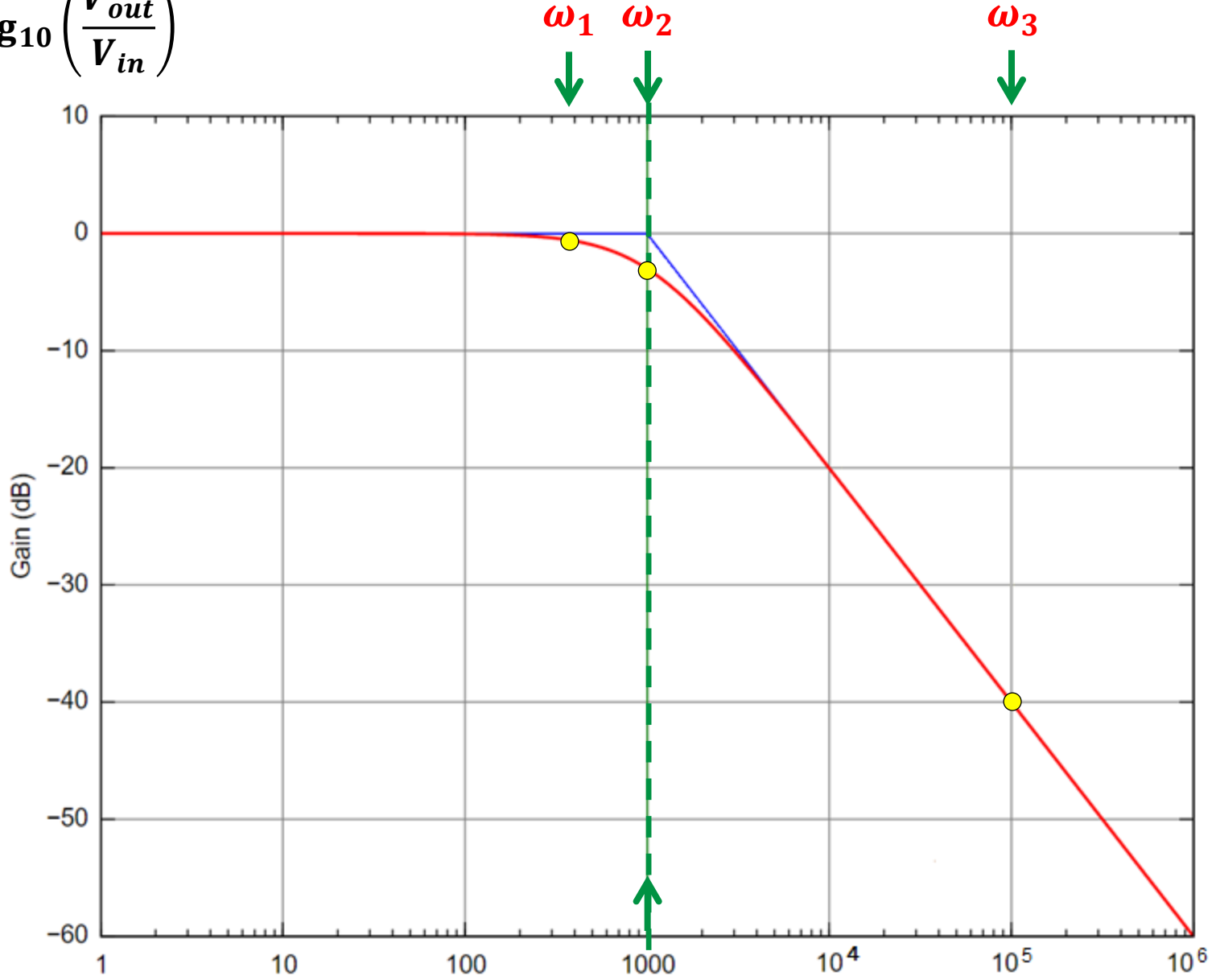
$$20 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$$




$$\omega_c = 2\pi f_c$$

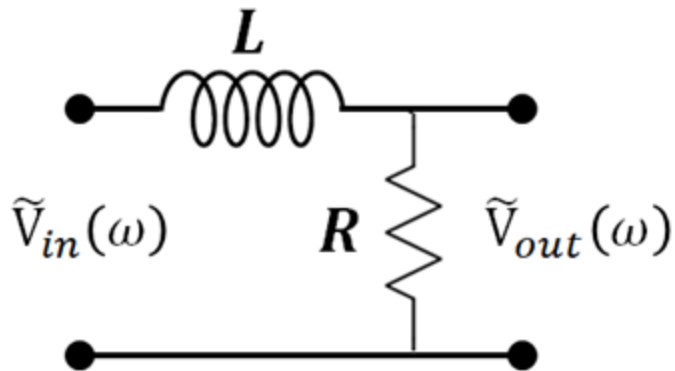
Other Low-Pass Passive filter configurations




RL filter (1st order)

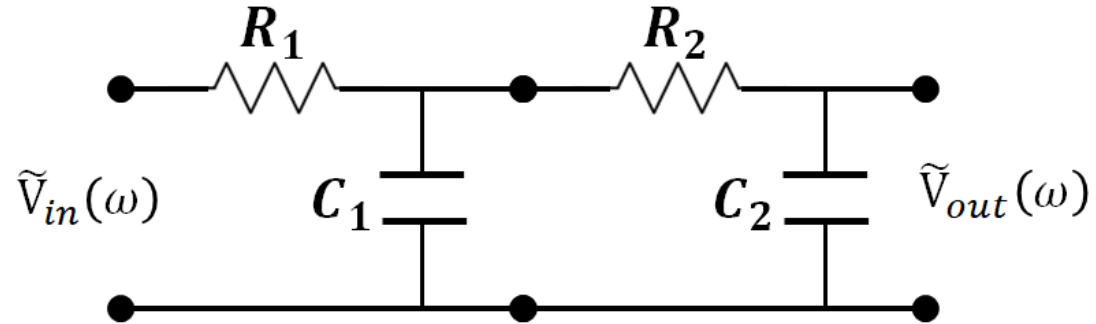

RC filter (2nd order)

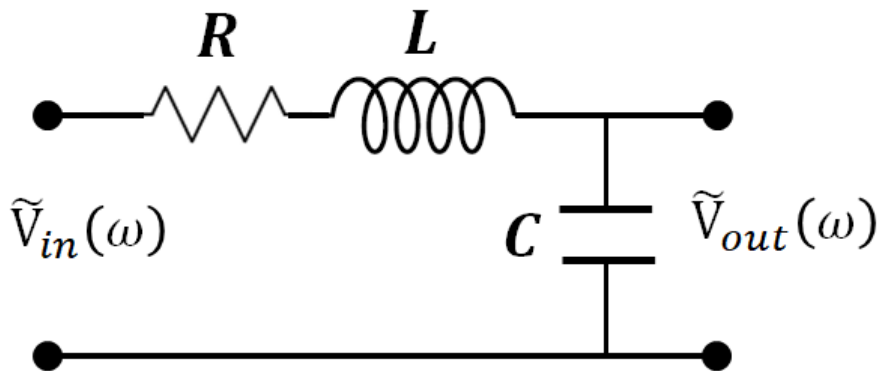

RLC filter (2nd order)

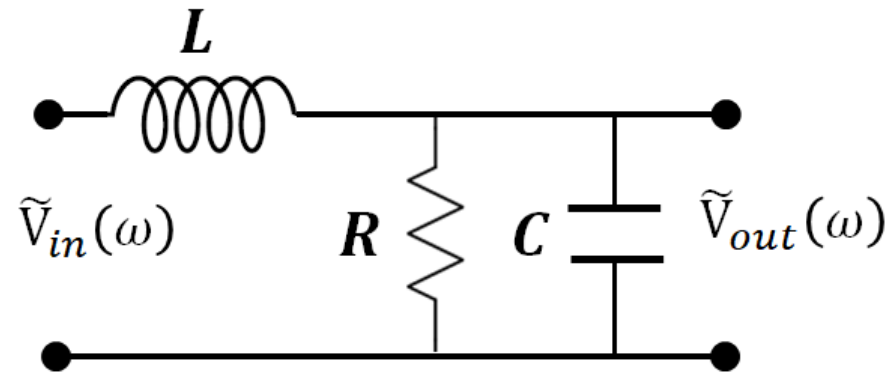


RLC filter (2nd order)

Sinusoidal input signal

$$V_{in}(t) = V_m \cos(\omega t + \theta_V)$$

$$H(\omega) = |H(\omega)| \angle H(\omega)$$

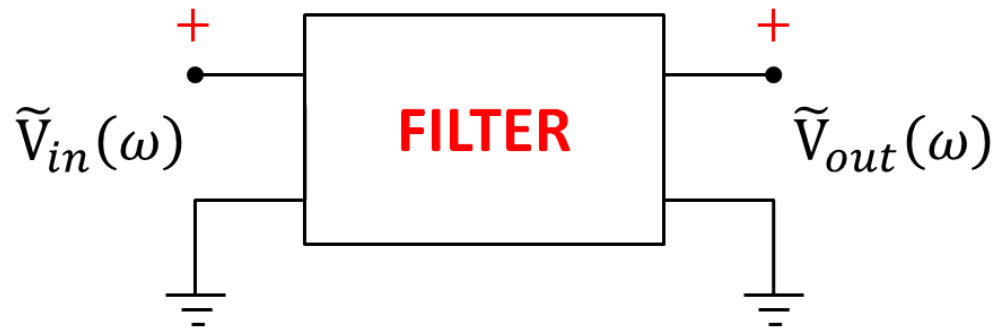

$$\tilde{V}_{out}(\omega) = H(\omega) \tilde{V}_{in}(\omega)$$

$$V_{out}(t) = |H(\omega)| V_m \cos(\omega t + \theta_V + \angle H(\omega))$$


Example – Low Pass RC filter

$$V_{in}(t) = 2 \cos(3000t)$$

Find $V_{out}(t)$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

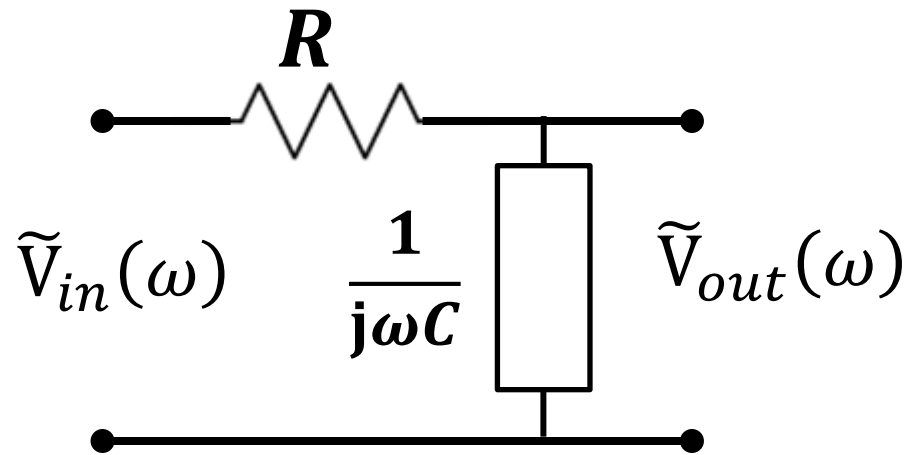Let $R = 1\text{k}\Omega$ and $C = 1\mu\text{F}$.



Example – Low Pass RC filter

$$V_{in}(t) = 2 \cos(3000t)$$

Find $V_{out}(t)$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

Let $R = 1\text{k}\Omega$ and $C = 1\mu\text{F}$.


$$\omega RC = 3000 \times 1\text{k} \times 1\mu = 3$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (3)^2}} = \frac{1}{\sqrt{10}} \text{ V}$$

$$\angle H(\omega) = -\tan^{-1}(\omega RC)$$
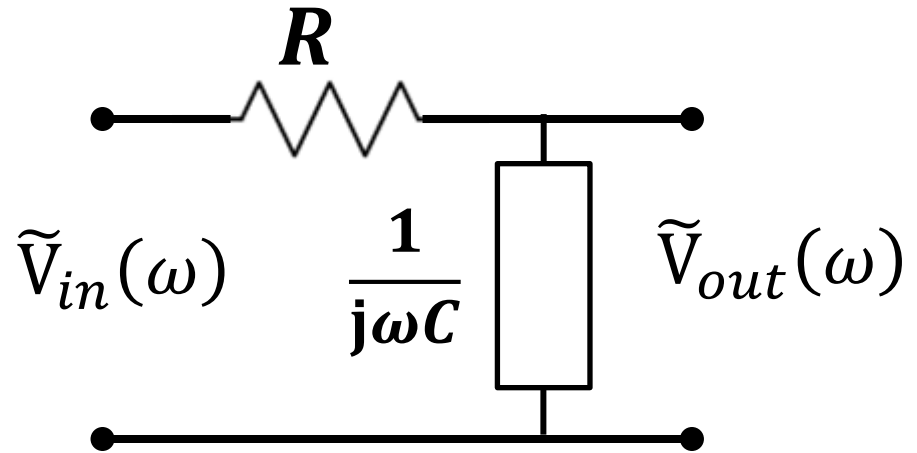
$$\angle H(\omega) = -\tan^{-1}(3) = -1.249 \text{ rad}$$



Example – Low Pass RC filter

$$V_{in}(t) = 2 \cos(3000t)$$

Find $V_{out}(t)$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

Let $R = 1\text{k}\Omega$ and $C = 1\mu\text{F}$.


$$|H(\omega)| = \frac{1}{\sqrt{1 + (3)^2}} = \frac{1}{\sqrt{10}} \text{ V}$$

$$\angle H(\omega) = -\tan^{-1}(3) = -1.249 \text{ rad}$$

$$V_{out}(t) = |H(\omega)| \times 2 \cos(3000t + \angle H(\omega))$$


$$V_{out}(t) = \frac{2}{\sqrt{10}} \cos(3000t - 1.249)$$

Valid for sinusoidal signals

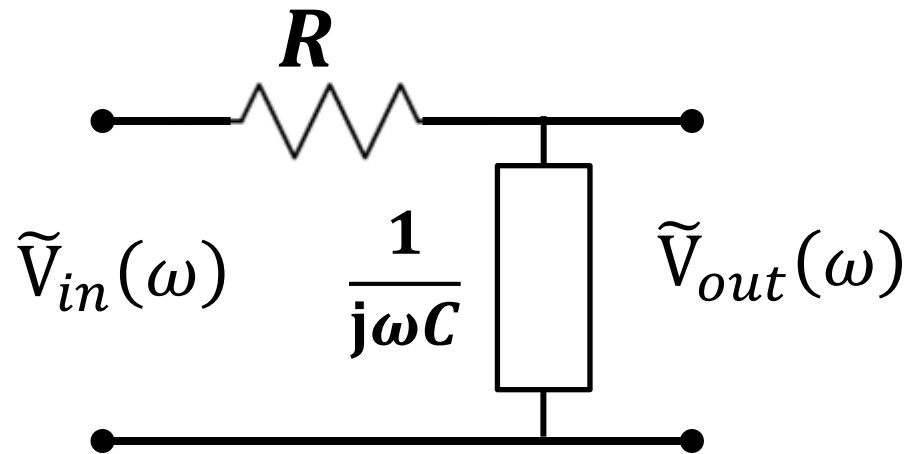

$$V_{in}(t) = 2 \cos(3000t)$$

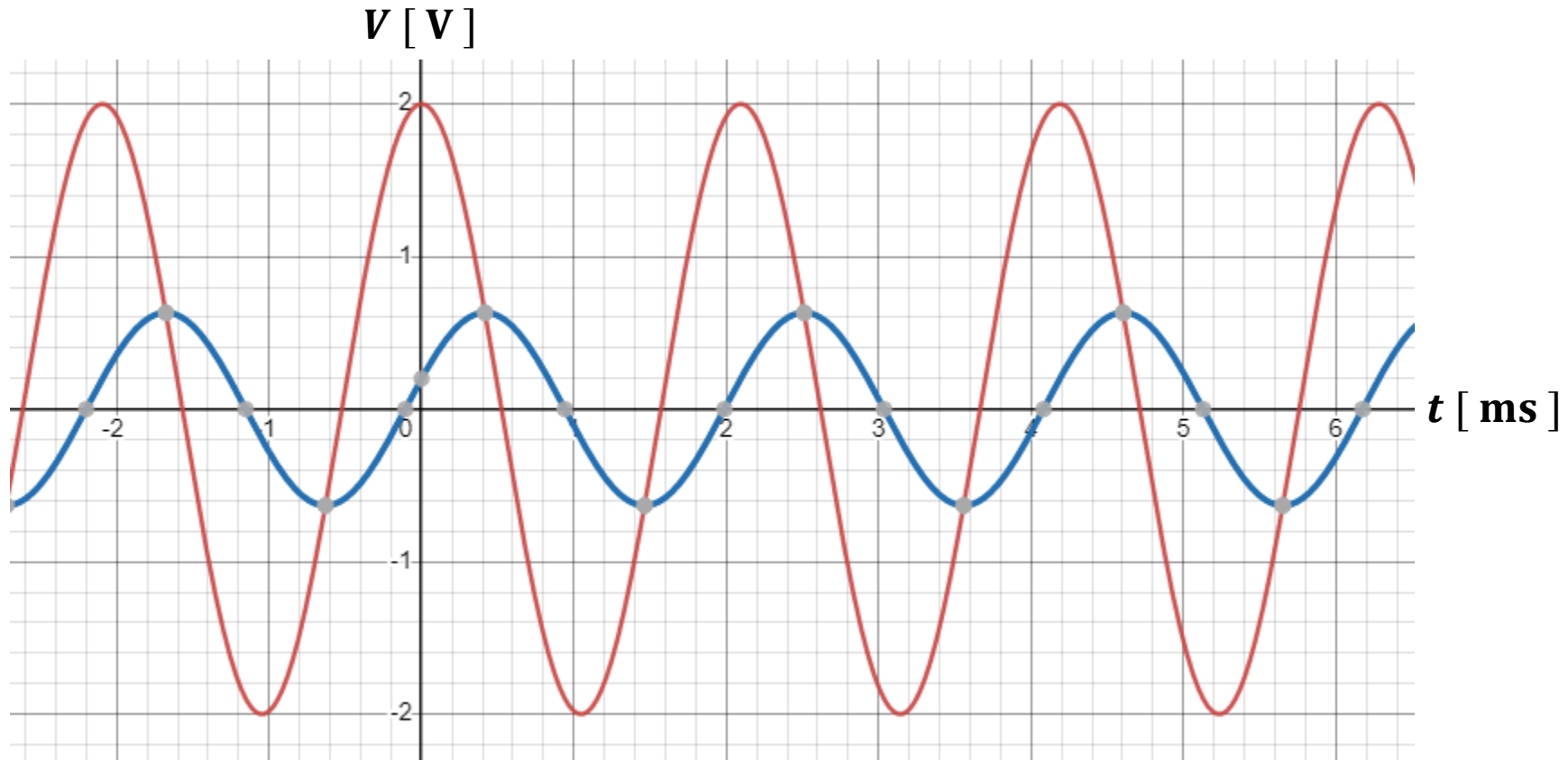
$$V_{out}(t) = \frac{2}{\sqrt{10}} \cos(3000t - 1.249)$$




The filter introduces a time delay for the output signal


High Pass RC filter

RC filter
(1st order)

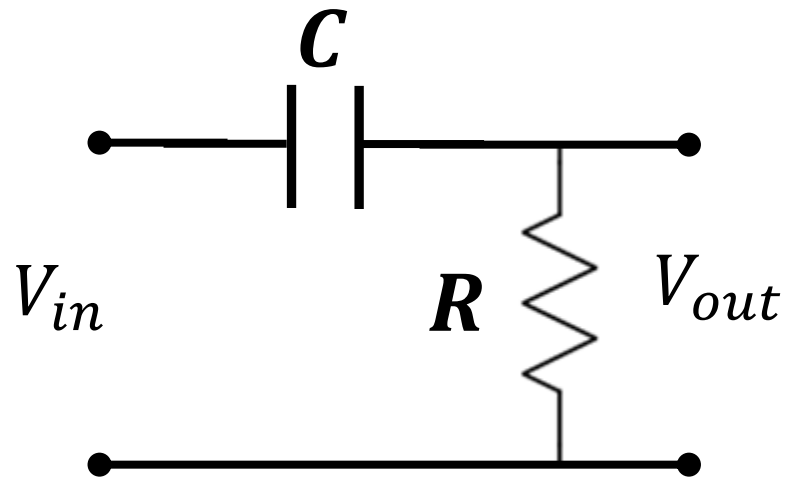

↓ PHASORS

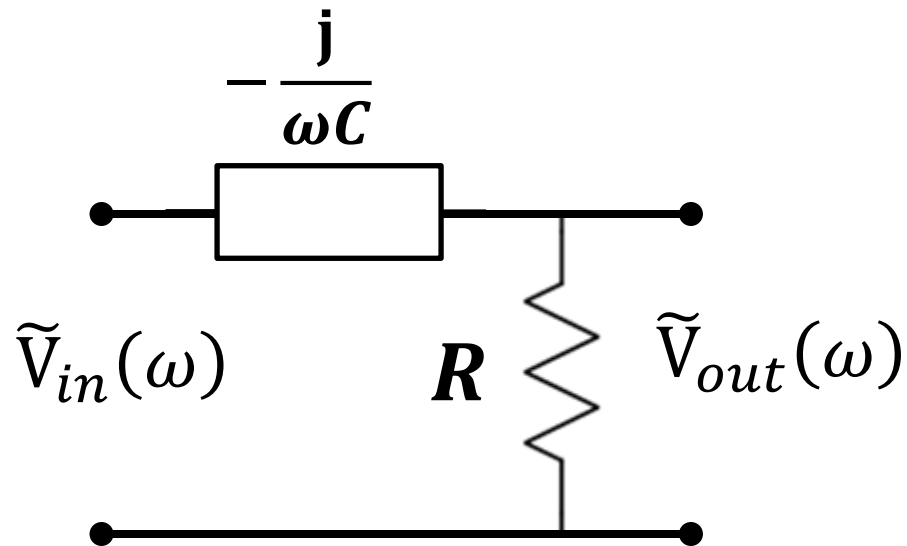

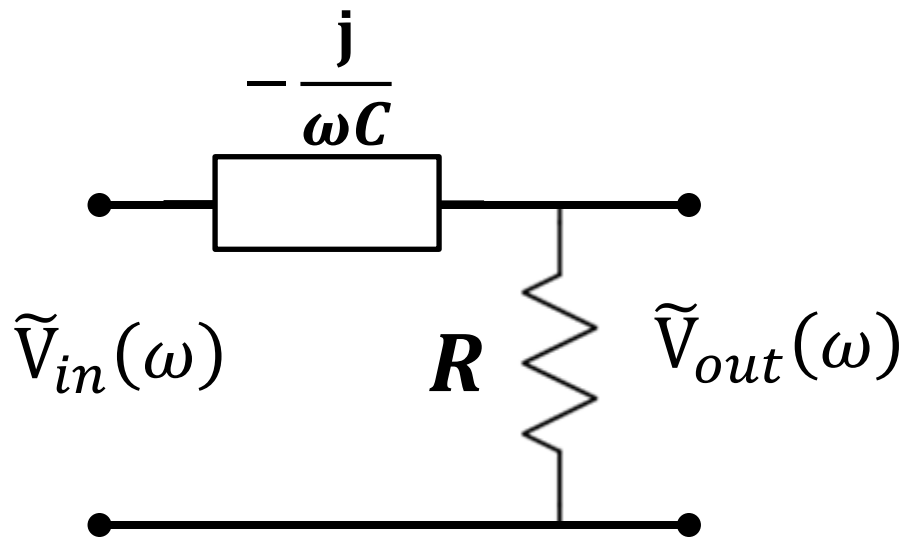

Let the input be a phasor of the form

$$\tilde{V}_{in}(\omega) = V_I \angle 0^\circ$$

$$\tilde{V}_{out}(\omega) = V_I \angle 0^\circ \frac{R}{R + 1/j\omega C} = \overbrace{V_I \angle 0^\circ}^{\tilde{V}_{in}(\omega)} \frac{j\omega RC}{1 + j\omega RC}$$

$$\frac{\tilde{V}_{out}(\omega)}{\tilde{V}_{in}(\omega)} = \mathbf{H}(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

Transfer Function

$$\mathbf{H}(\omega) = \frac{\mathbf{j}\omega RC}{\mathbf{1} + \mathbf{j}\omega RC}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{j}\omega RC(\mathbf{1} - \mathbf{j}\omega RC)}{(\mathbf{1} + \mathbf{j}\omega RC)(\mathbf{1} - \mathbf{j}\omega RC)} = \frac{(\omega RC)^2 + \mathbf{j}\omega RC}{\mathbf{1} + (\omega RC)^2}$$

Cartesian Form

Magnitude


$$|\mathbf{H}(\omega)| = \frac{|\mathbf{j}\omega RC|}{|\mathbf{1} + \mathbf{j}\omega RC|}$$

$$|\mathbf{H}(\omega)| = \frac{\omega RC}{\sqrt{\mathbf{1} + (\omega RC)^2}}$$

Magnitude of $H(\omega)$ for RC high-pass filter

$$|H(\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

$$\omega_c RC = 1 \rightarrow |H(\omega_c)| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$

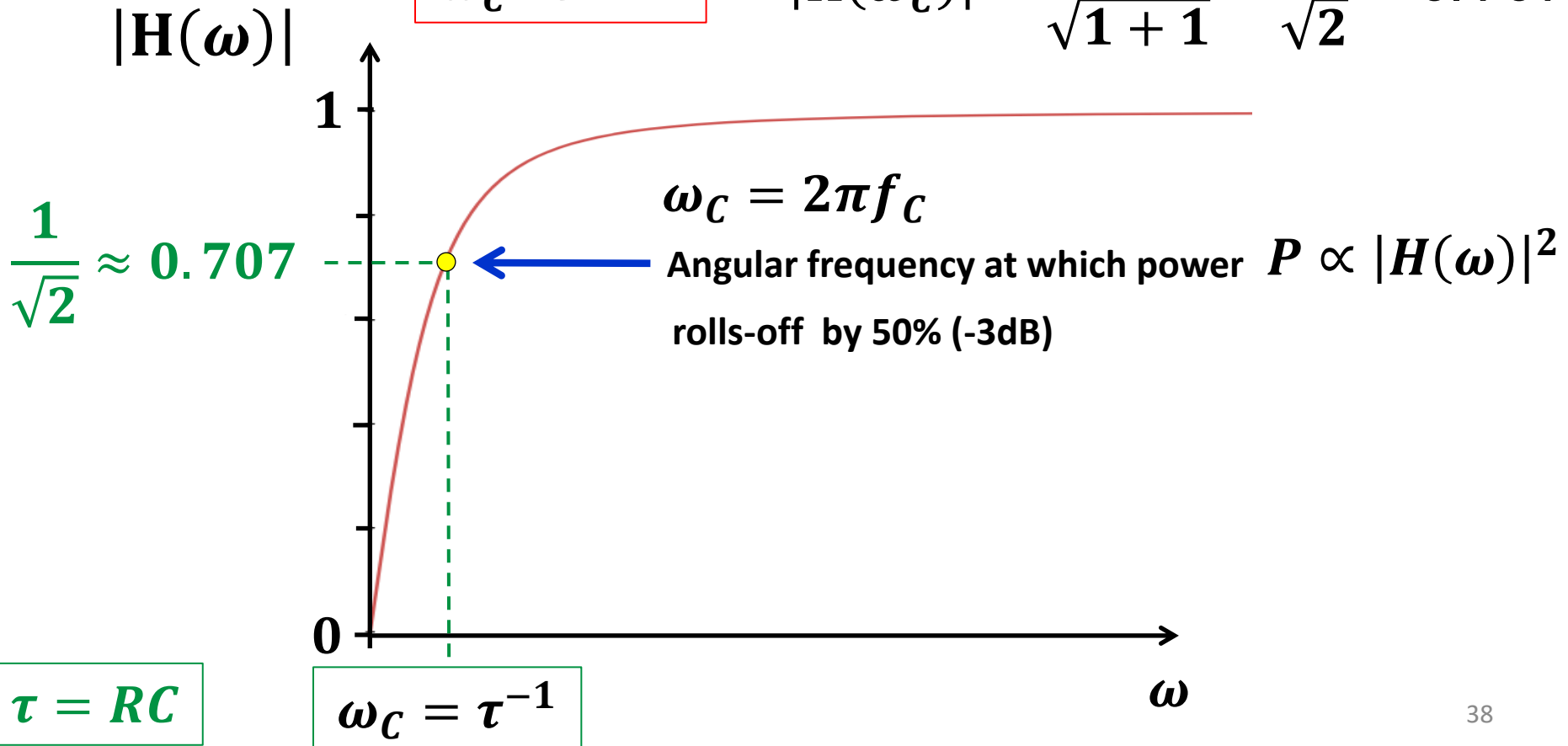


log-decibel representation – Bode Plot for magnitude

NOTE: This plot is normalized so that $\omega_C = 1$

$$20 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$$

-3dB

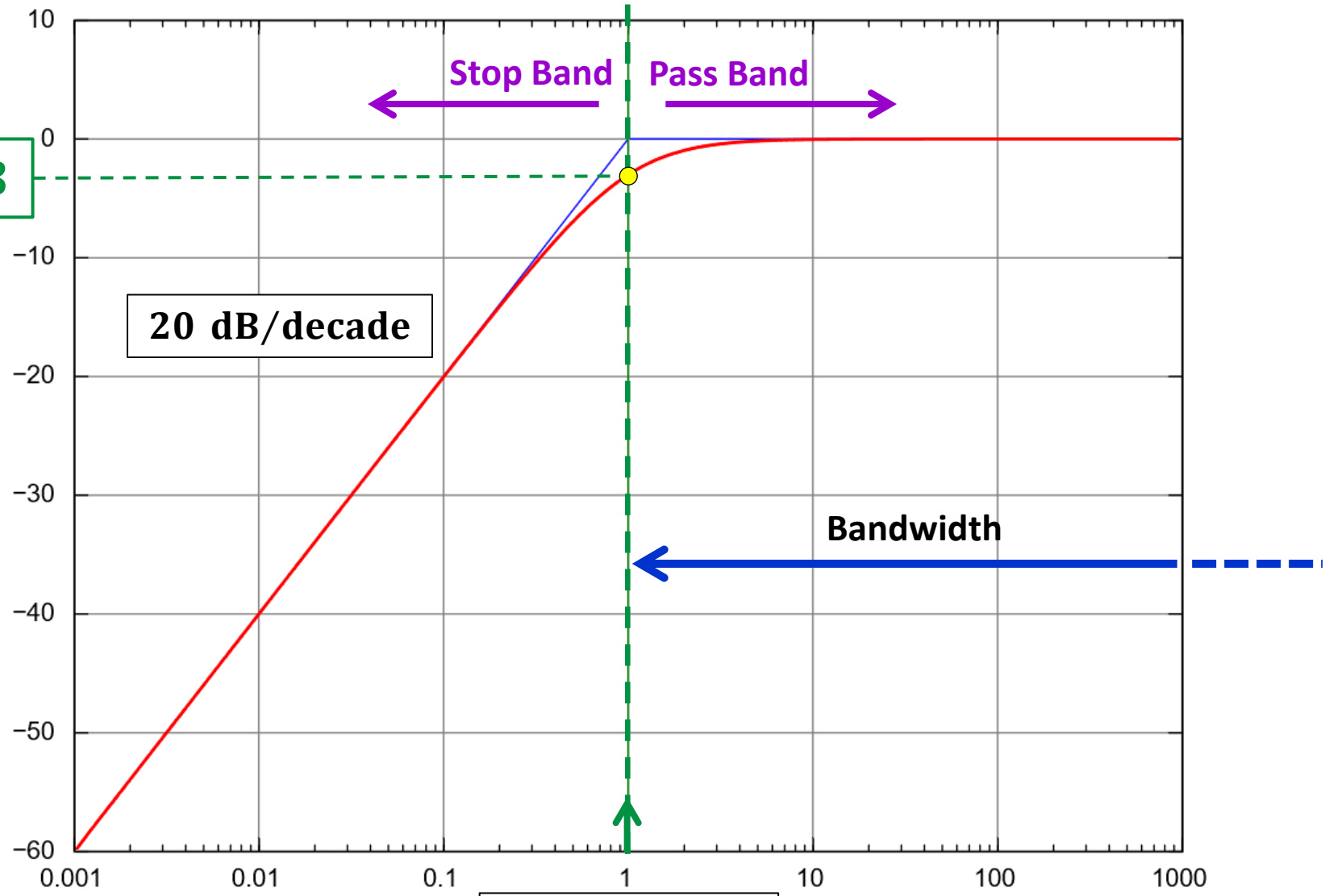

20 dB/decade

$$\omega_C = 2\pi f_C$$

$$\omega/\omega_C \text{ [rad/s]}$$

Phase of $H(\omega)$ for RC high-pass filter

$$H(\omega) = \frac{j\omega RC(1 - j\omega RC)}{(1 + j\omega RC)(1 - j\omega RC)} = \frac{(\omega RC)^2 + j\omega RC}{\underbrace{1 + (\omega RC)^2}_{\text{Cartesian Form}}}$$

$$\angle H(\omega) = \tan^{-1} \frac{\Im\{H(\omega)\}}{\Re\{H(\omega)\}} = \tan^{-1} \frac{\omega RC / (1 + (\omega RC)^2)}{(\omega RC)^2 / (1 + (\omega RC)^2)}$$

$$\angle H(\omega) = \tan^{-1} \left(\frac{1}{\omega RC} \right)$$


When $\omega = \omega_c$ we have $\omega_c RC = 1$

$$\angle H(\omega) = \tan^{-1}(1) = \frac{\pi}{4} = 45^\circ$$

Phase for RC high-pass filter

Linear scale representation

$\angle H(\omega)$ [rad]

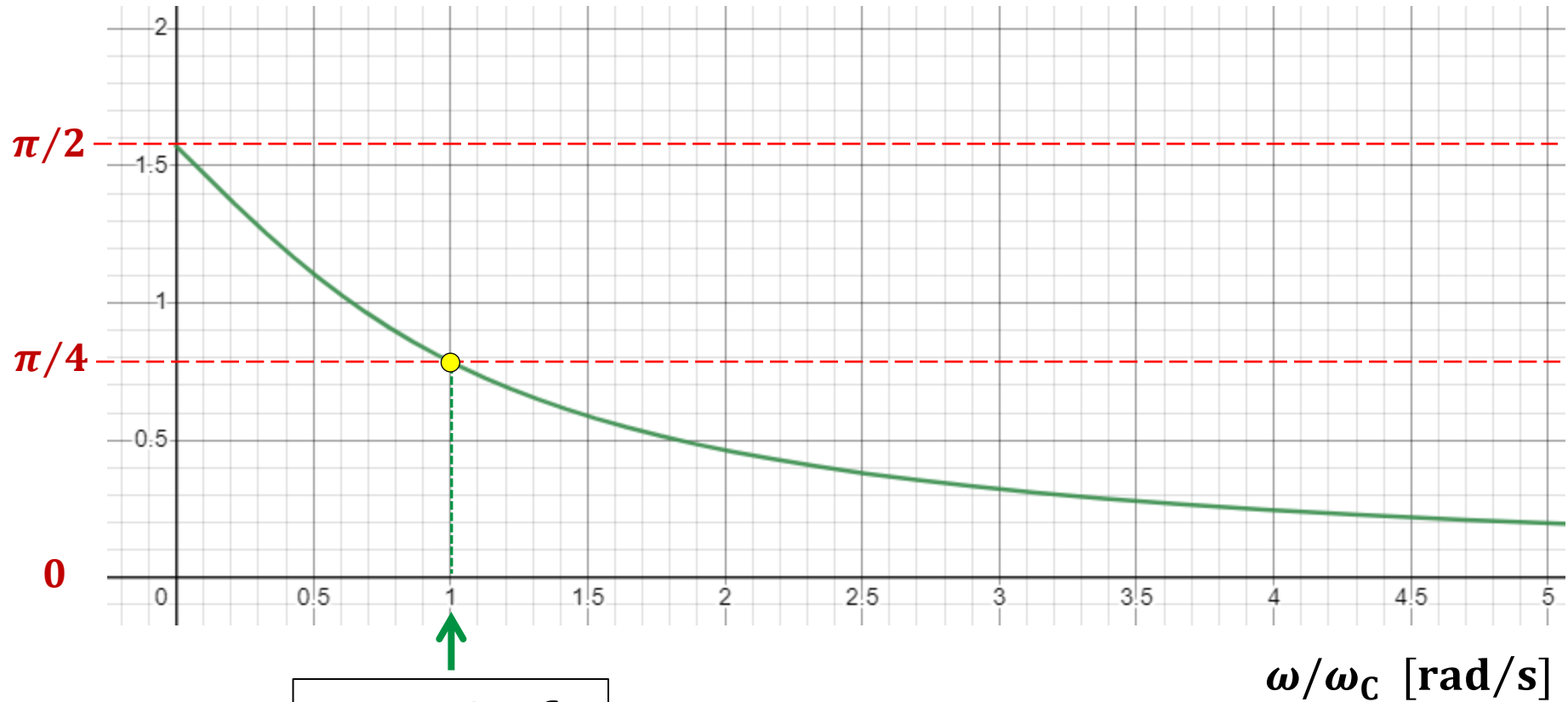

$$\omega_c = 2\pi f_c$$

ω/ω_c [rad/s]


Phase for RC high-pass filter

semi-log scale representation – Bode Plot for phase

NOTE: This plot is normalized so that $\omega_c = 1$


$\angle H(\omega)$

[deg]

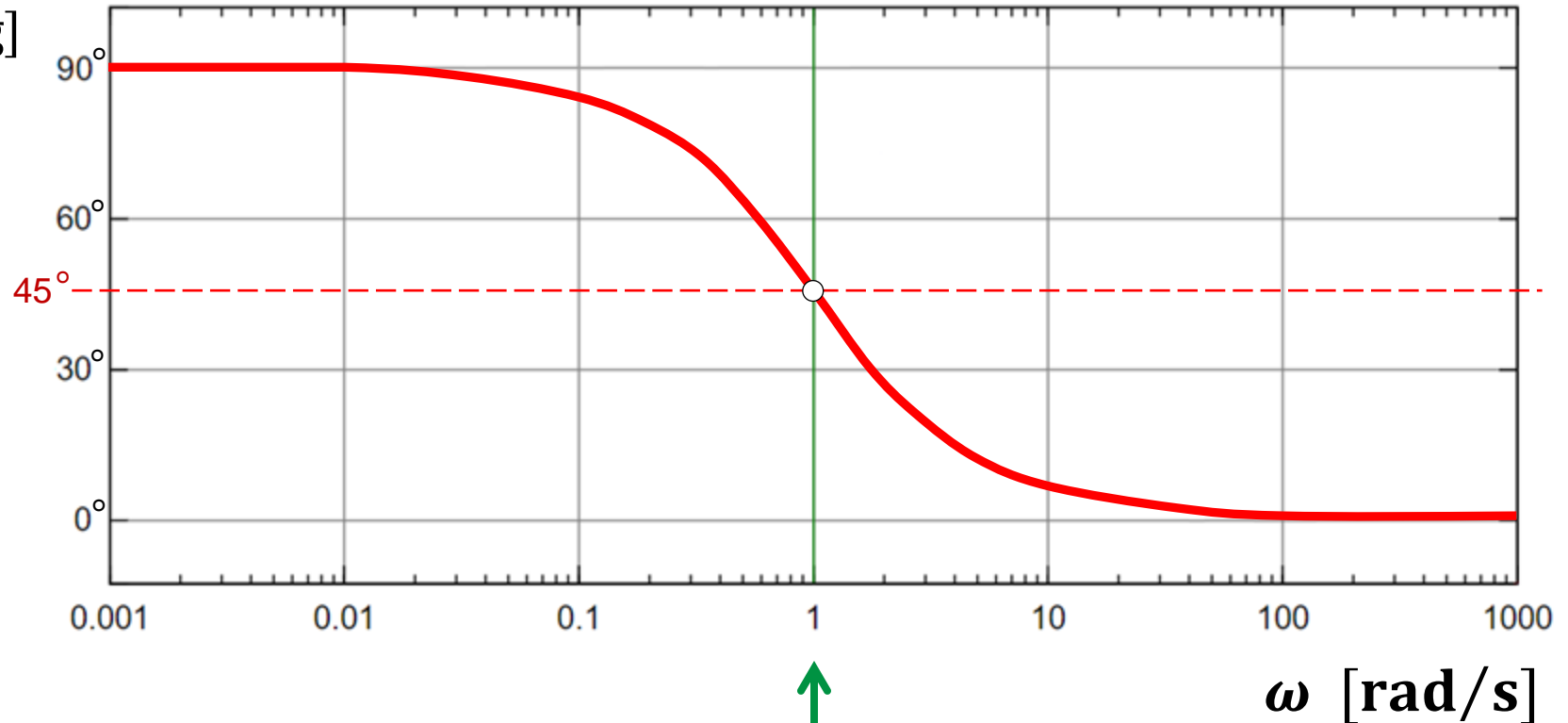


$$\omega_c = 2\pi f_c$$

Limitations of simple passive filters

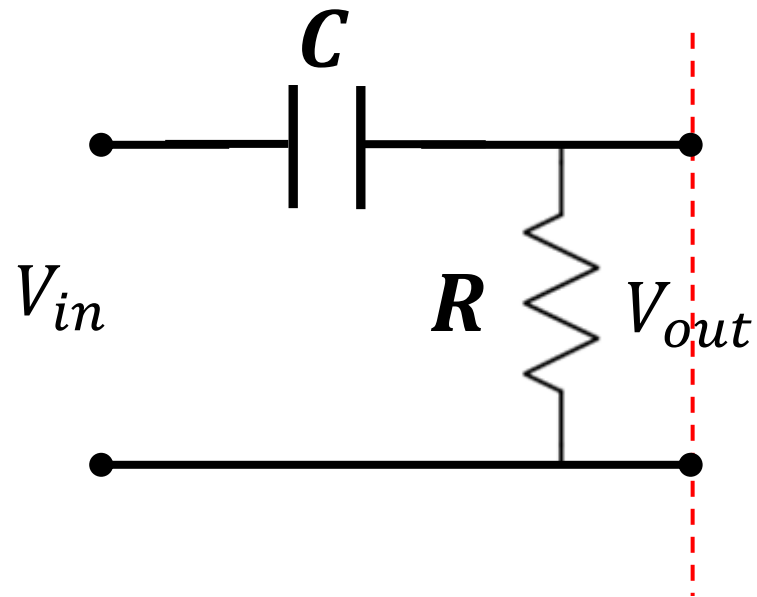

Limitations of simple passive filters

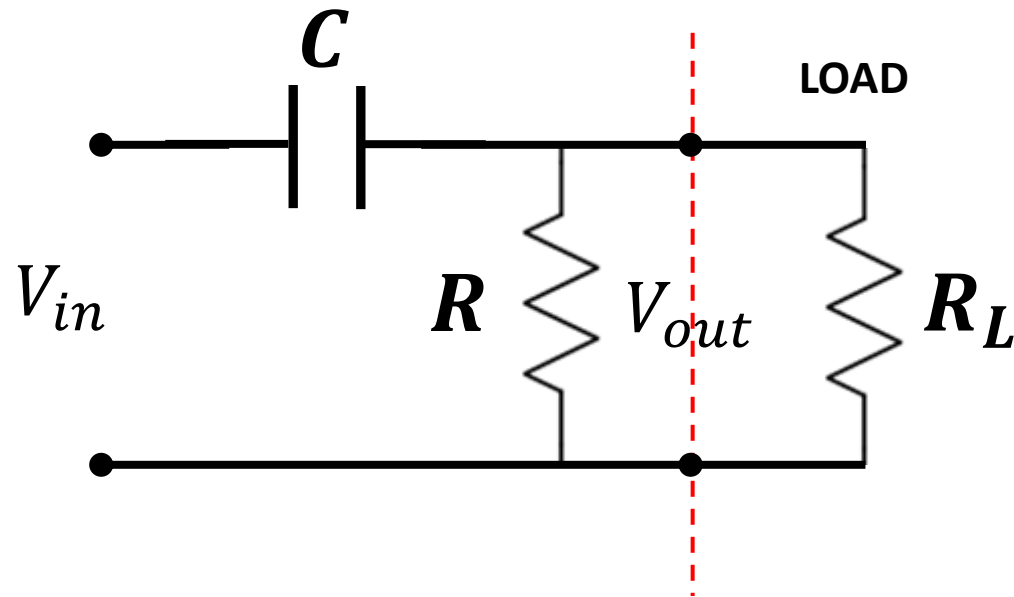
The response of a passive filter is affected by the load connected directly to it. For example, consider a high-pass RC filter:



The parallel $R_{\text{eff}} = R // R_L$ yields an equivalent resistance lower than either R or R_L . In particular, if connected to a small resistor R_L , the resulting cutoff frequency $\omega'_C = (R_{\text{eff}}C)^{-1}$ may change considerably with respect to the original $\omega_C = (RC)^{-1}$.

Overcome limitations by using active filters

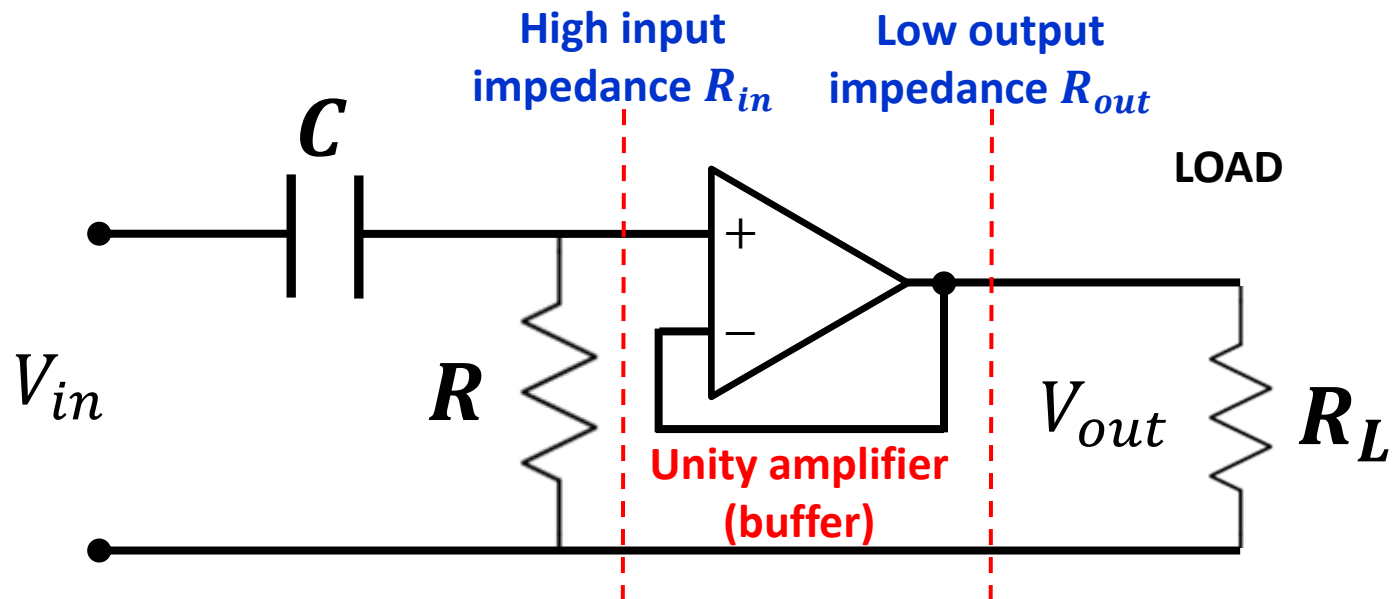
In the final part of the course, we will learn how a high input impedance operational amplifier can be used as an intermediate stage to improve the interconnection between filter and load.



The filter sees $R // R_{in} \approx R$ and is not affected. In output the voltage V_{out} drives a total resistance $R_{out} + R_L$. If R_{out} is much smaller, power is delivered mainly to the load R_L .

Band-Pass Filter

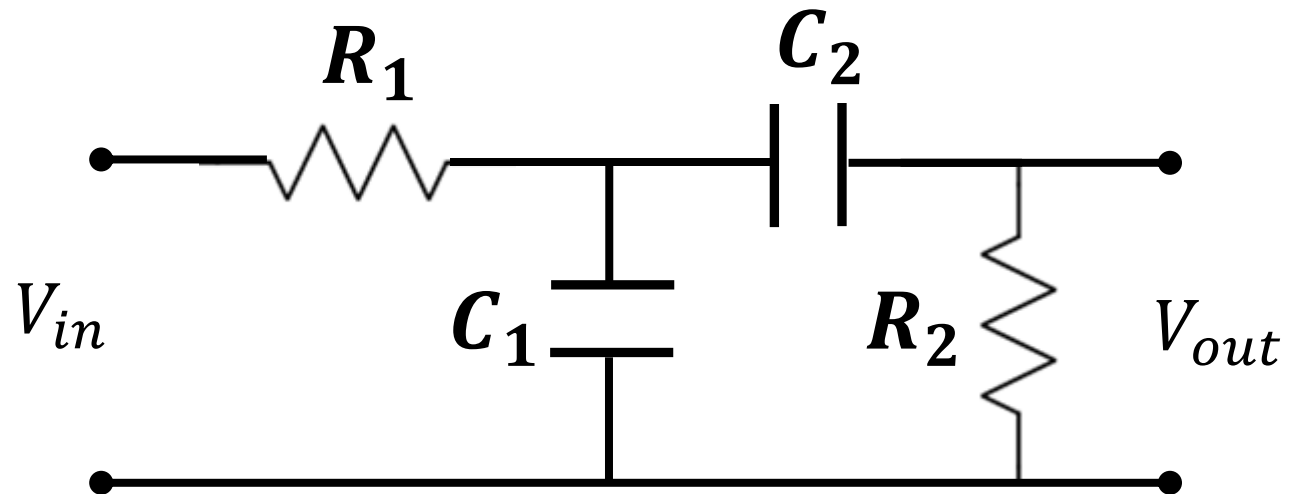
Cascade of a low pass and a high-pass filter can be designed so that $\omega_{CLP} > \omega_{CHP}$. The two filter characteristics combine, letting only an intermediate frequency band pass through.



Looking at frequency extremes, one can see that:


- $\omega = 0$ capacitors behave like open circuit $\rightarrow V_{out} = 0$
- $\omega \rightarrow \infty$ capacitors behave like short circuit $\rightarrow V_{out} = 0$

Band-Pass Filter

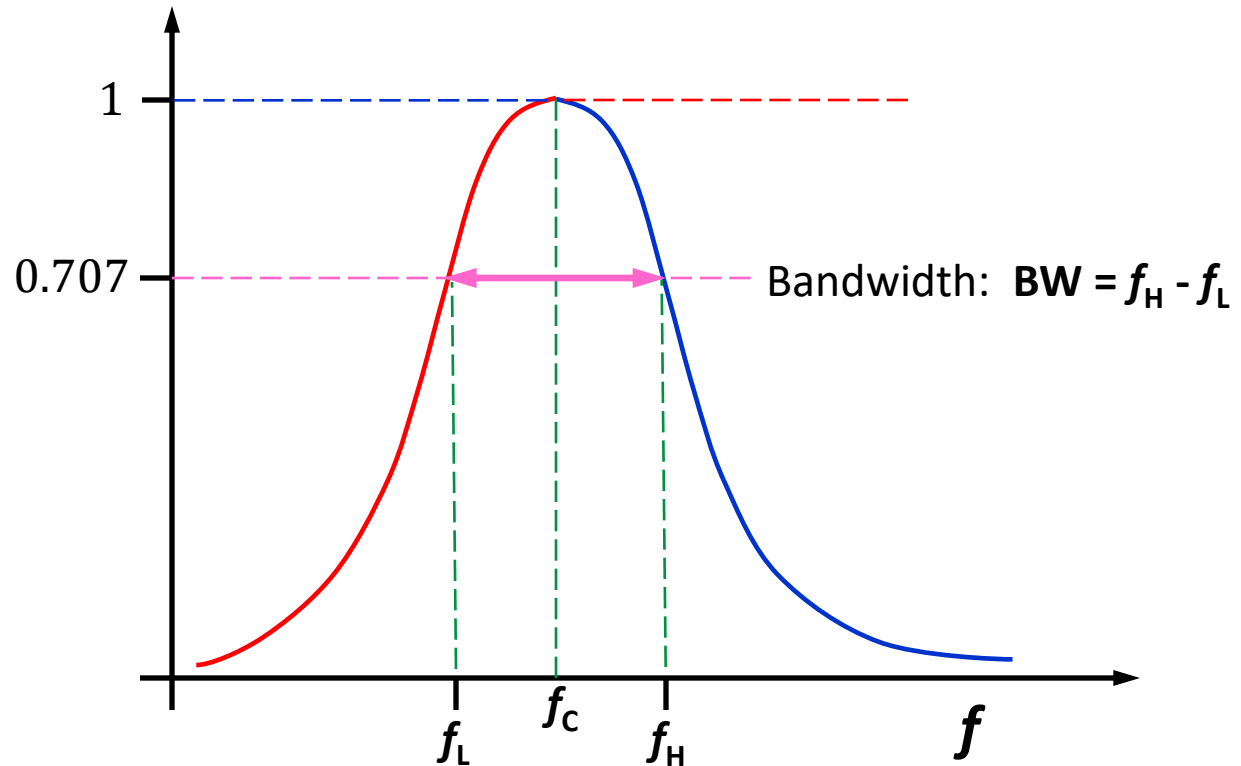


Frequencies $f < f_L$ and $f > f_H$ are strongly attenuated

Band-Stop Filter

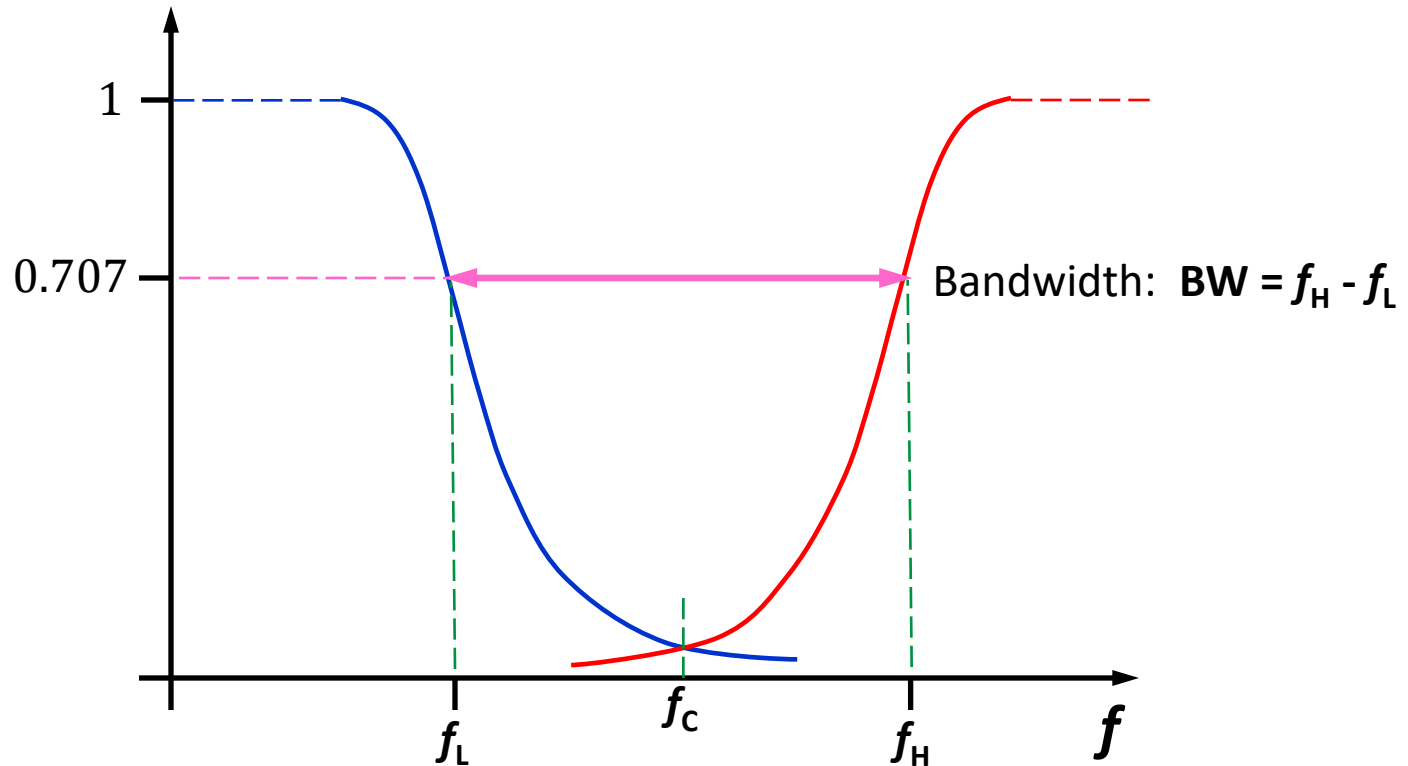


Frequencies $f_L < f < f_H$ are strongly attenuated

Notch Filter

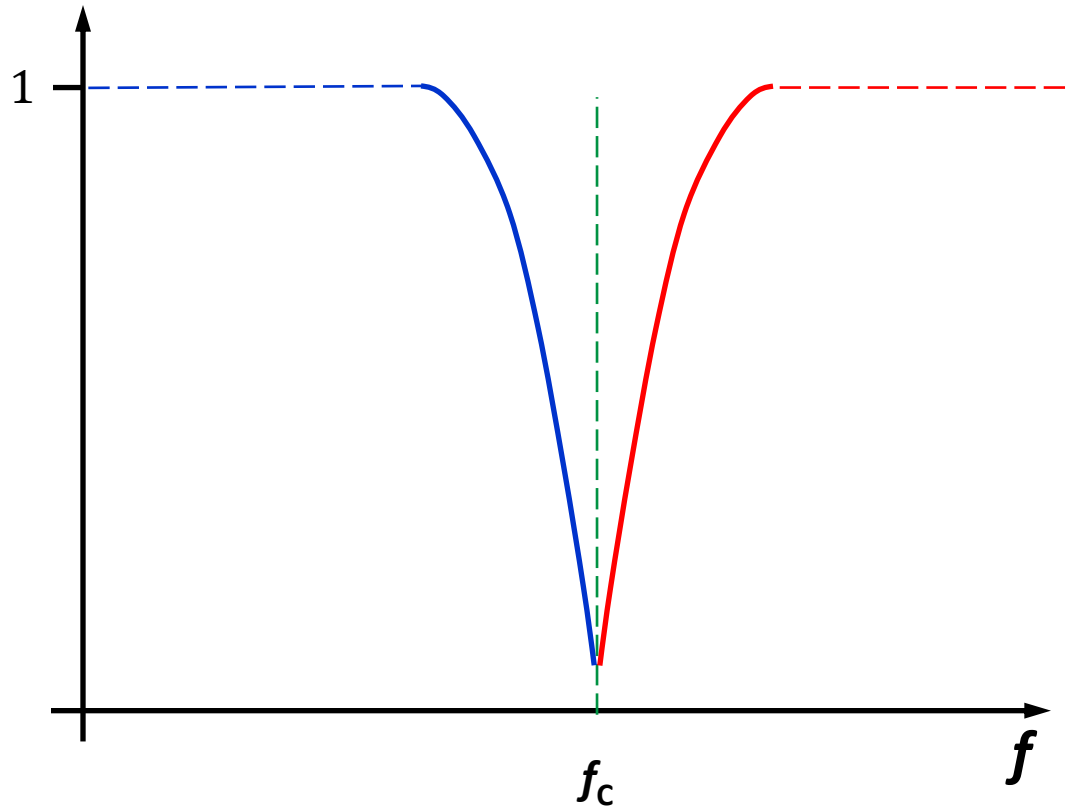

A very narrow band-stop filter, designed to reject a specific frequency, is called a **notch filter**.

Comb Filter

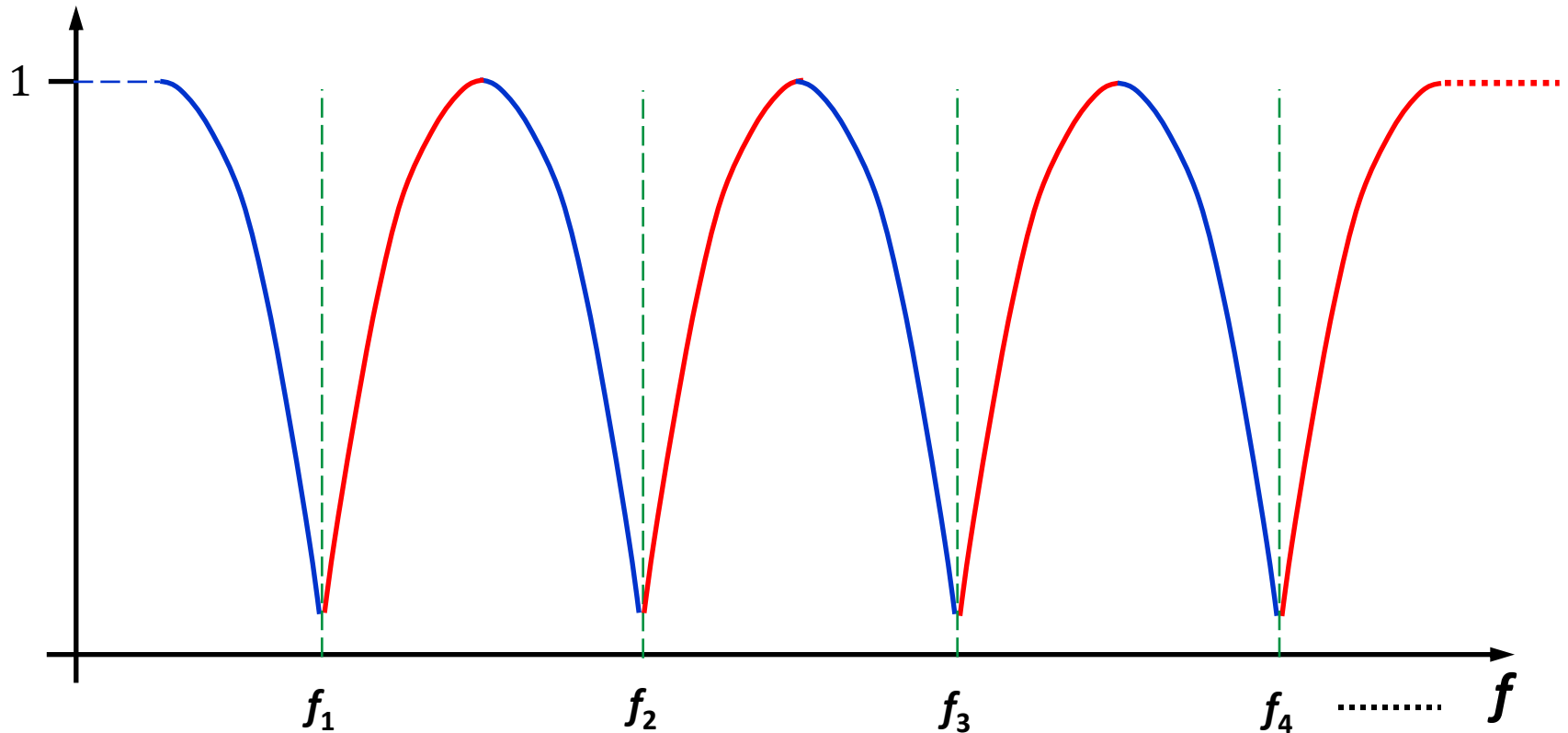

The comb filter consists of a series of regularly spaced notches and peaks (also called *teeth*).