

ECE 205 “Electrical and Electronics Circuits”

Spring 2024 – LECTURE 35

MWF – 12:00pm

Prof. Umberto Ravaioli

2062 ECE Building

Lecture 35 – Summary


Learning Objectives

1. Low-Pass and High-Pass Filters
2. Behavior of Operational Amplifiers

Sinusoidal input signal

$$V_{in}(t) = V_m \cos(\omega t + \theta_V)$$

$$H(\omega) = |H(\omega)| \angle H(\omega)$$

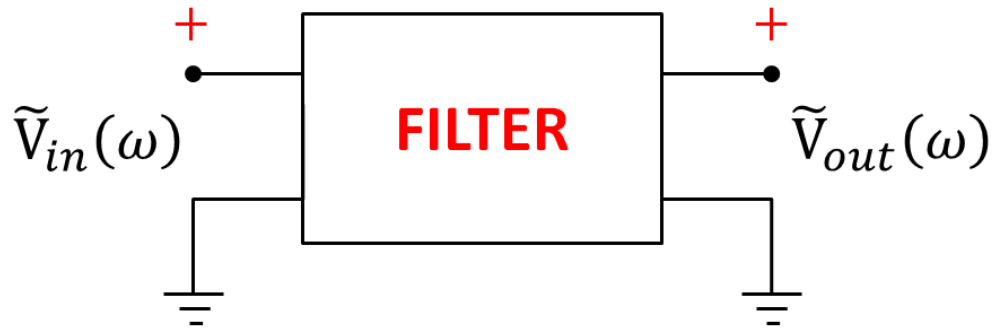

$$\tilde{V}_{out}(\omega) = H(\omega) \tilde{V}_{in}(\omega)$$

$$V_{out}(t) = |H(\omega)| V_m \cos(\omega t + \theta_V + \angle H(\omega))$$


Example – Low Pass RC filter

$$V_{in}(t) = 2 \cos(3000t)$$

Find $V_{out}(t)$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

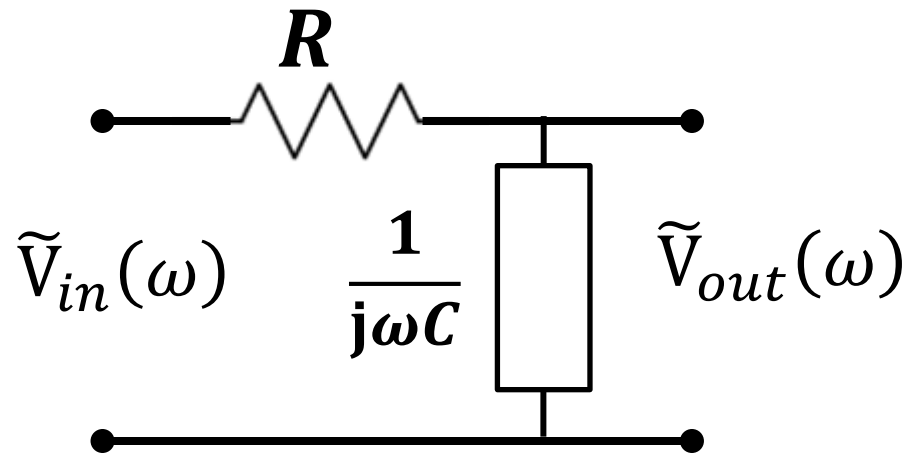Let $R = 1\text{k}\Omega$ and $C = 1\mu\text{F}$.



Example – Low Pass RC filter

$$V_{in}(t) = 2 \cos(3000t)$$

Find $V_{out}(t)$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

Let $R = 1\text{k}\Omega$ and $C = 1\mu\text{F}$.


$$\omega RC = 3000 \times 1\text{k} \times 1\mu = 3$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (3)^2}} = \frac{1}{\sqrt{10}} \text{ V}$$

$$\angle H(\omega) = -\tan^{-1}(\omega RC)$$
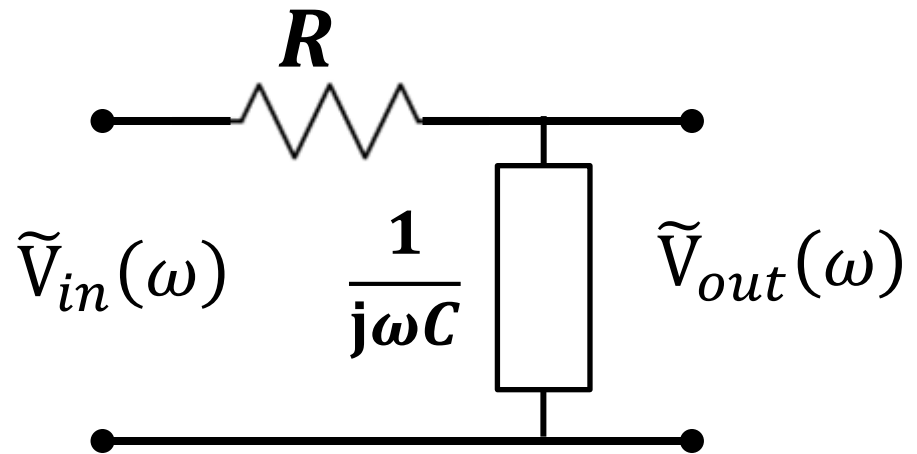
$$\angle H(\omega) = -\tan^{-1}(3) = -1.249 \text{ rad}$$



Example – Low Pass RC filter

$$V_{in}(t) = 2 \cos(3000t)$$

Find $V_{out}(t)$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

Let $R = 1\text{k}\Omega$ and $C = 1\mu\text{F}$.


$$|H(\omega)| = \frac{1}{\sqrt{1 + (3)^2}} = \frac{1}{\sqrt{10}} \text{ V}$$

$$\angle H(\omega) = -\tan^{-1}(3) = -1.249 \text{ rad}$$

$$V_{out}(t) = |H(\omega)| \times 2 \cos(3000t + \angle H(\omega))$$


$$V_{out}(t) = \frac{2}{\sqrt{10}} \cos(3000t - 1.249)$$

Valid for sinusoidal signals

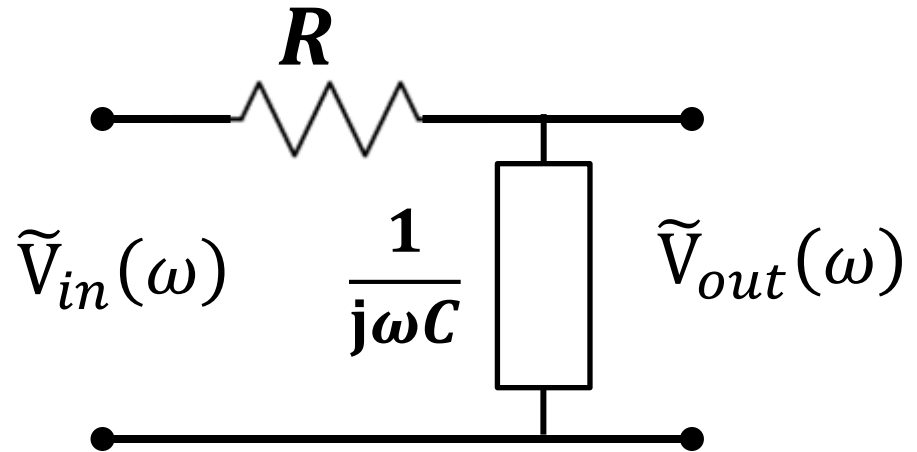

$$V_{in}(t) = 2 \cos(3000t)$$

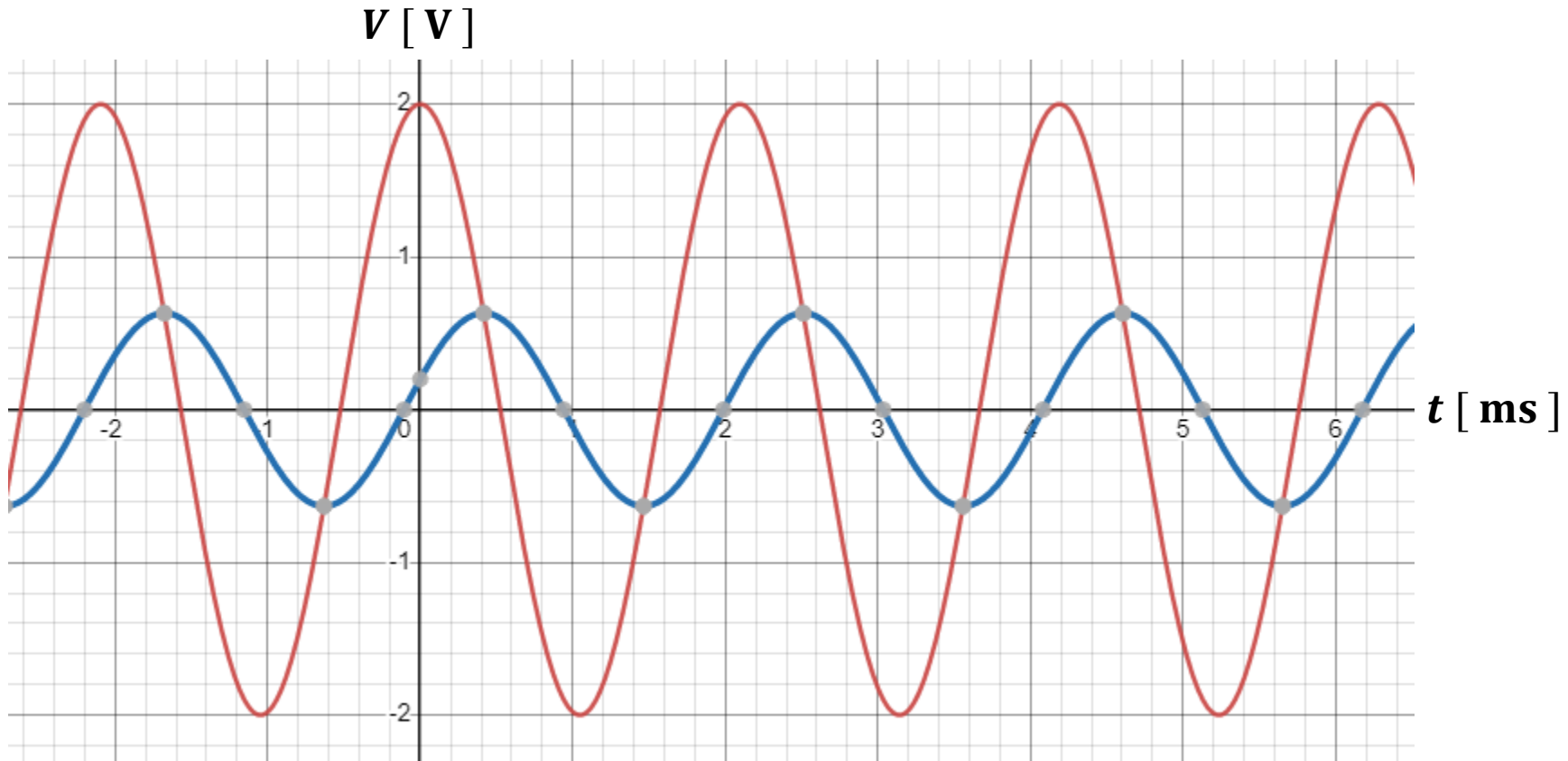
$$V_{out}(t) = \frac{2}{\sqrt{10}} \cos(3000t - 1.249)$$




The filter introduces a time delay for the output signal


High Pass RC filter

RC filter
(1st order)

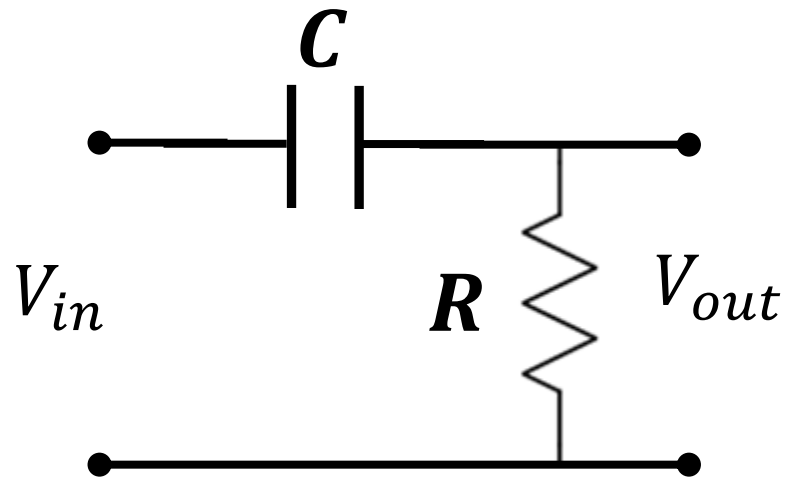

PHASORS

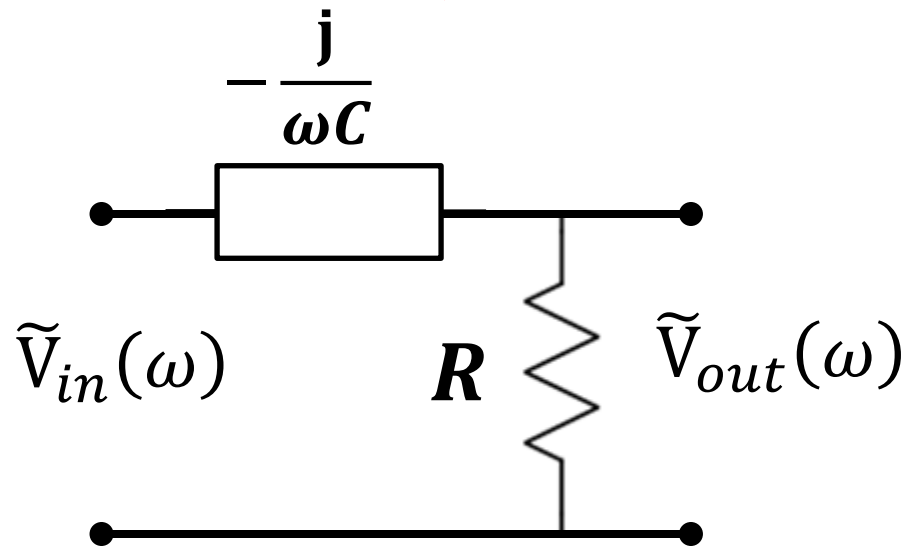

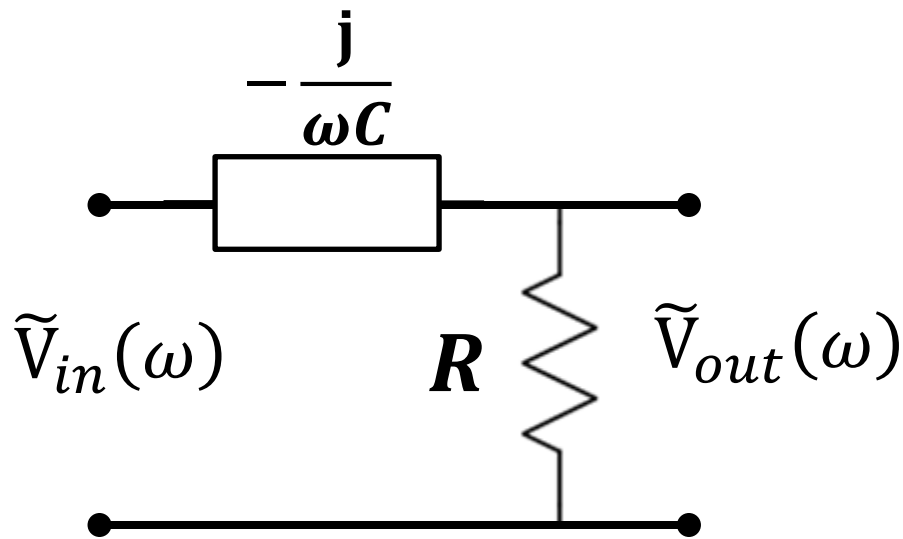

Let the input be a phasor of the form

$$\tilde{V}_{in}(\omega) = V_I \angle 0^\circ$$

$$\tilde{V}_{out}(\omega) = V_I \angle 0^\circ \frac{R}{R + 1/j\omega C} = \overbrace{V_I \angle 0^\circ}^{\tilde{V}_{in}(\omega)} \frac{j\omega RC}{1 + j\omega RC}$$

$$\frac{\tilde{V}_{out}(\omega)}{\tilde{V}_{in}(\omega)} = \mathbf{H}(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

Transfer Function

$$\mathbf{H}(\omega) = \frac{\mathbf{j}\omega RC}{\mathbf{1} + \mathbf{j}\omega RC}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{j}\omega RC(\mathbf{1} - \mathbf{j}\omega RC)}{(\mathbf{1} + \mathbf{j}\omega RC)(\mathbf{1} - \mathbf{j}\omega RC)} = \frac{(\omega RC)^2 + \mathbf{j}\omega RC}{\mathbf{1} + (\omega RC)^2}$$

Cartesian Form

Magnitude


$$|\mathbf{H}(\omega)| = \frac{|\mathbf{j}\omega RC|}{|\mathbf{1} + \mathbf{j}\omega RC|}$$

$$|\mathbf{H}(\omega)| = \frac{\omega RC}{\sqrt{\mathbf{1} + (\omega RC)^2}}$$

Magnitude of $H(\omega)$ for RC high-pass filter

$$|H(\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

$$\omega_c RC = 1 \rightarrow |H(\omega_c)| = \frac{1}{\sqrt{1 + 1}} = \frac{1}{\sqrt{2}} = 0.707$$

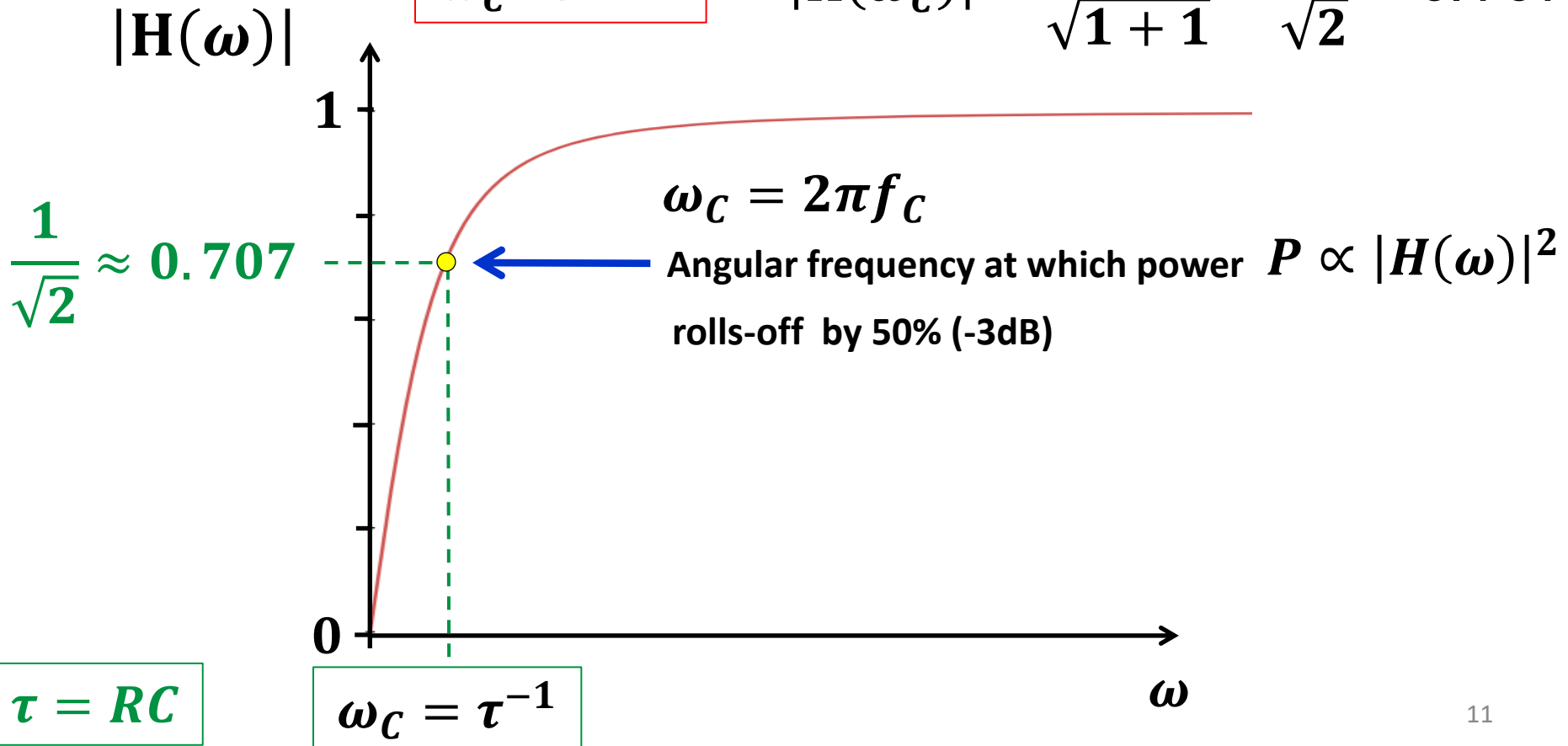


REMEMBER – for the RC low-pass filter:

$$\text{At } \omega = \omega_c : R = 1/\omega C$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\omega_c RC = 1 \rightarrow |H(\omega_c)| = \frac{1}{\sqrt{1 + 1}} = \frac{1}{\sqrt{2}} = 0.707$$

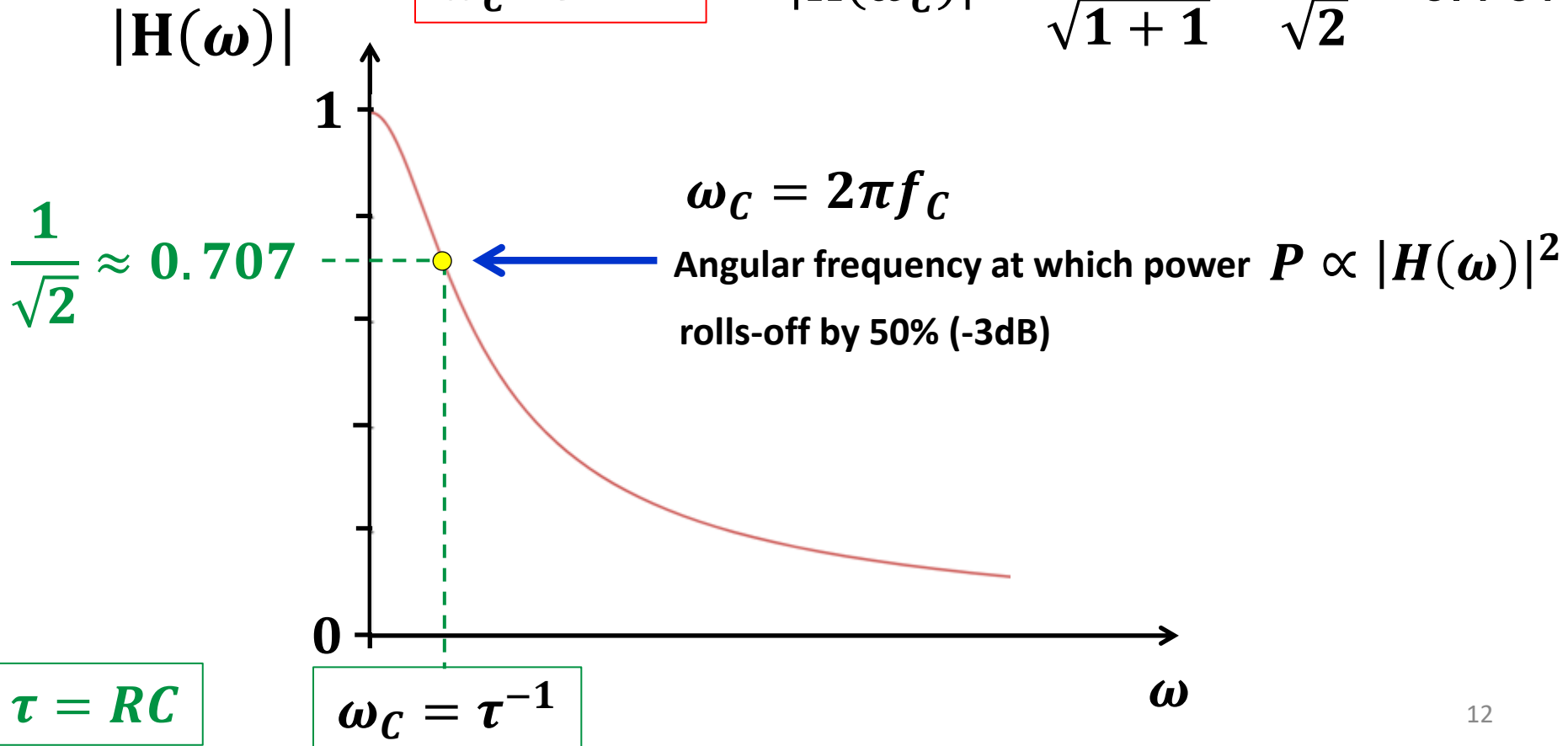


log-decibel representation – Bode Plot for magnitude

NOTE: This plot is normalized so that $\omega_C = 1$

$$20 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$$


-3dB

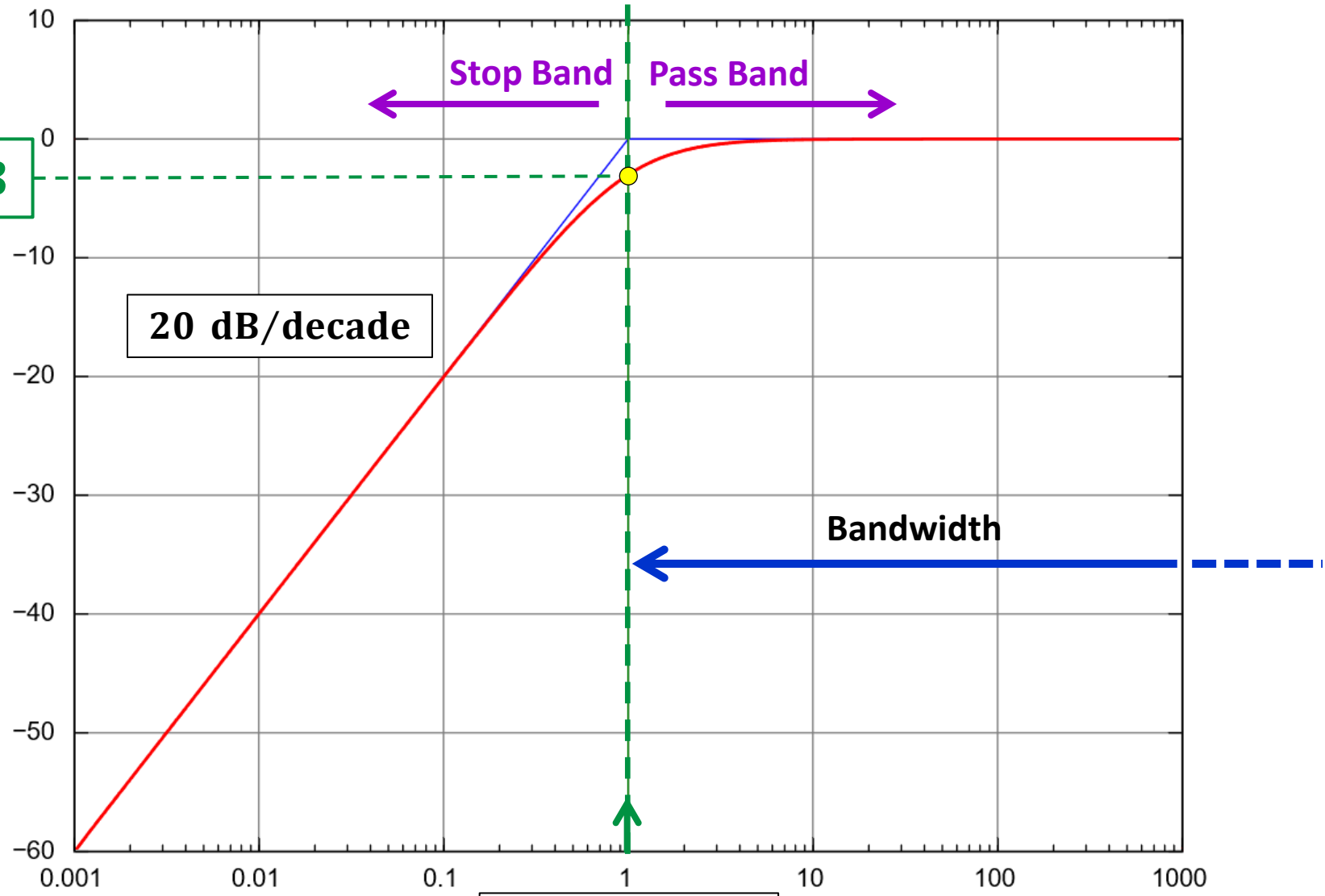

REMEMBER – for the low-pass filter:

NOTE: This plot is normalized so that $\omega_c = 1$
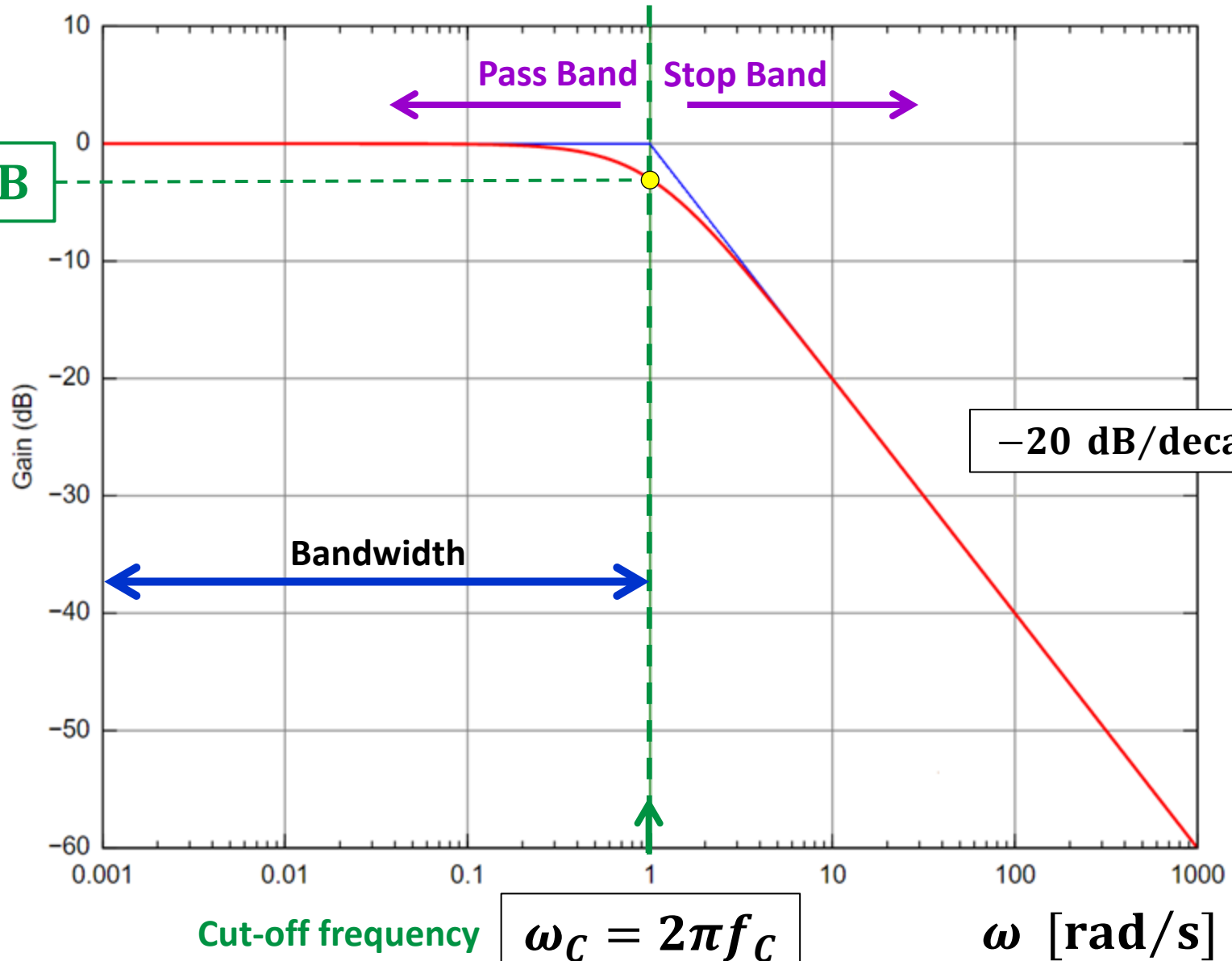
$$20 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$$



Phase of $H(\omega)$ for RC high-pass filter

$$H(\omega) = \frac{j\omega RC(1 - j\omega RC)}{(1 + j\omega RC)(1 - j\omega RC)} = \frac{(\omega RC)^2 + j\omega RC}{\underbrace{1 + (\omega RC)^2}_{\text{Cartesian Form}}}$$

$$\angle H(\omega) = \tan^{-1} \frac{\Im\{H(\omega)\}}{\Re\{H(\omega)\}} = \tan^{-1} \frac{\omega RC / (1 + (\omega RC)^2)}{(\omega RC)^2 / (1 + (\omega RC)^2)}$$

$$\angle H(\omega) = \tan^{-1} \left(\frac{1}{\omega RC} \right)$$


When $\omega = \omega_c$ we have $\omega_c RC = 1$

$$\angle H(\omega) = \tan^{-1}(1) = \frac{\pi}{4} = 45^\circ$$

Phase for RC high-pass filter

Linear scale representation

$\angle H(\omega)$ [rad]

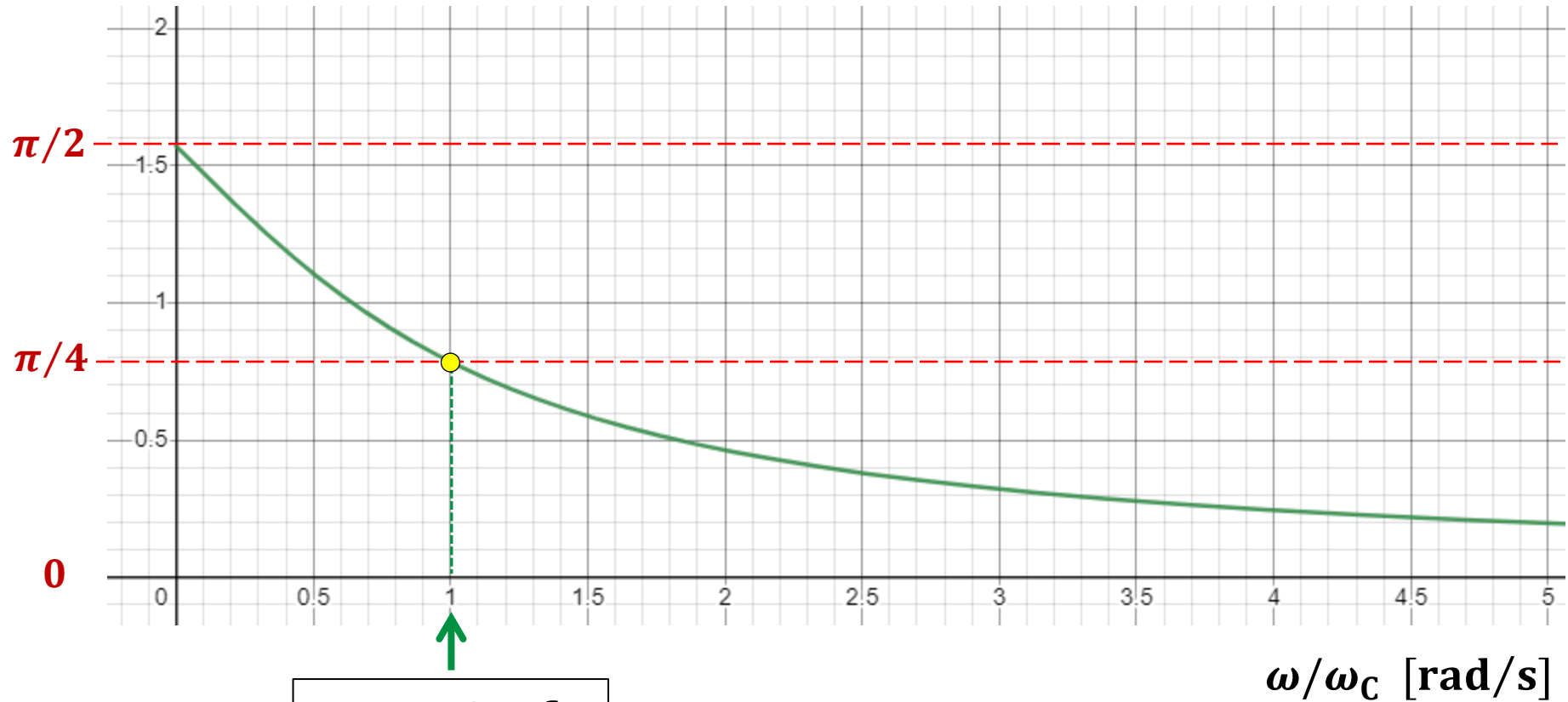

$$\omega_c = 2\pi f_c$$

ω/ω_c [rad/s]

REMEMBER – for the RC low-pass filter:

Linear scale representation

$\angle H(\omega)$ [rad]



$$\omega_c = 2\pi f_c$$


Phase for RC high-pass filter

semi-log scale representation – Bode Plot for phase

NOTE: This plot is normalized so that $\omega_c = 1$

$\angle H(\omega)$

[deg]

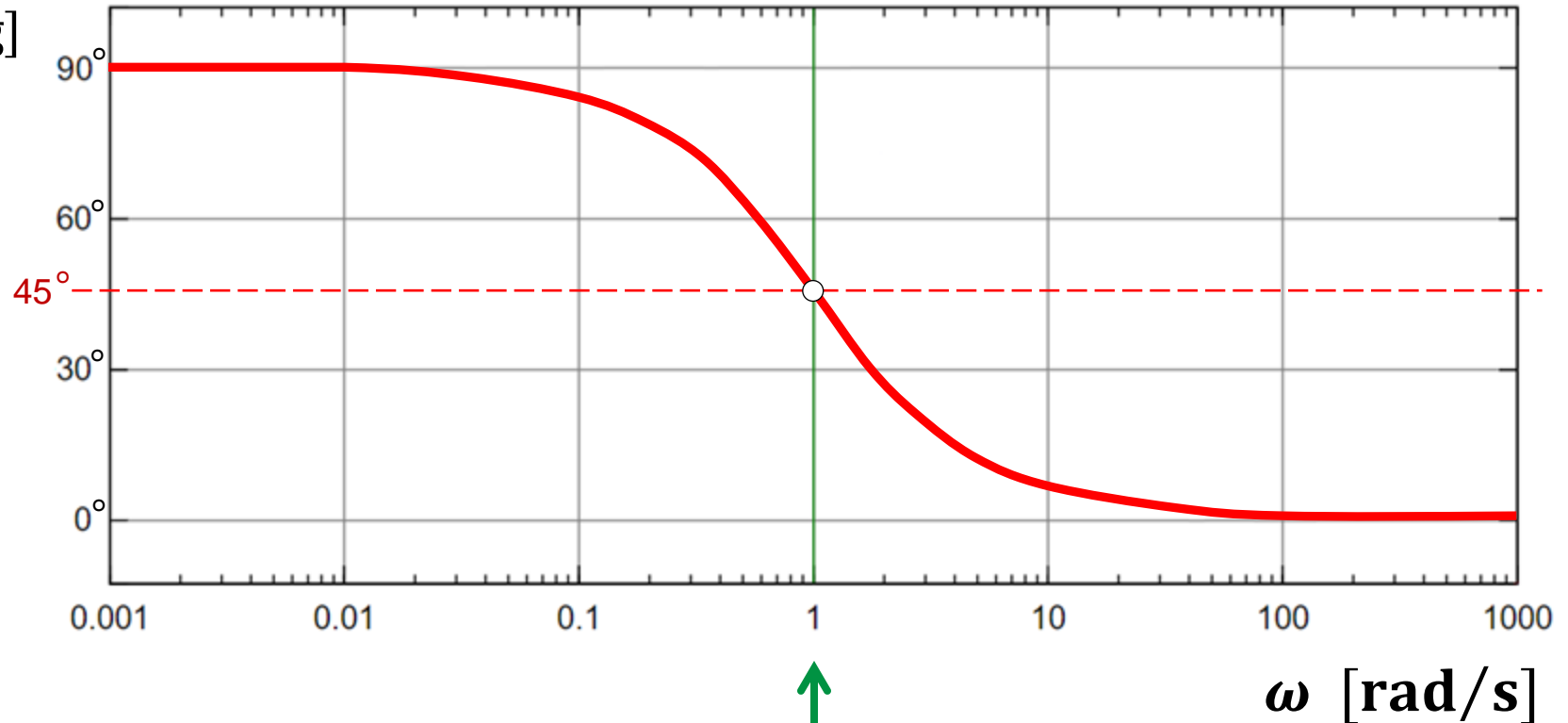


$$\omega_c = 2\pi f_c$$

REMEMBER – for the RC low-pass filter:

semi-log scale representation – Bode Plot for phase

NOTE: This plot is normalized so that $\omega_c = 1$


$\angle H(\omega)$

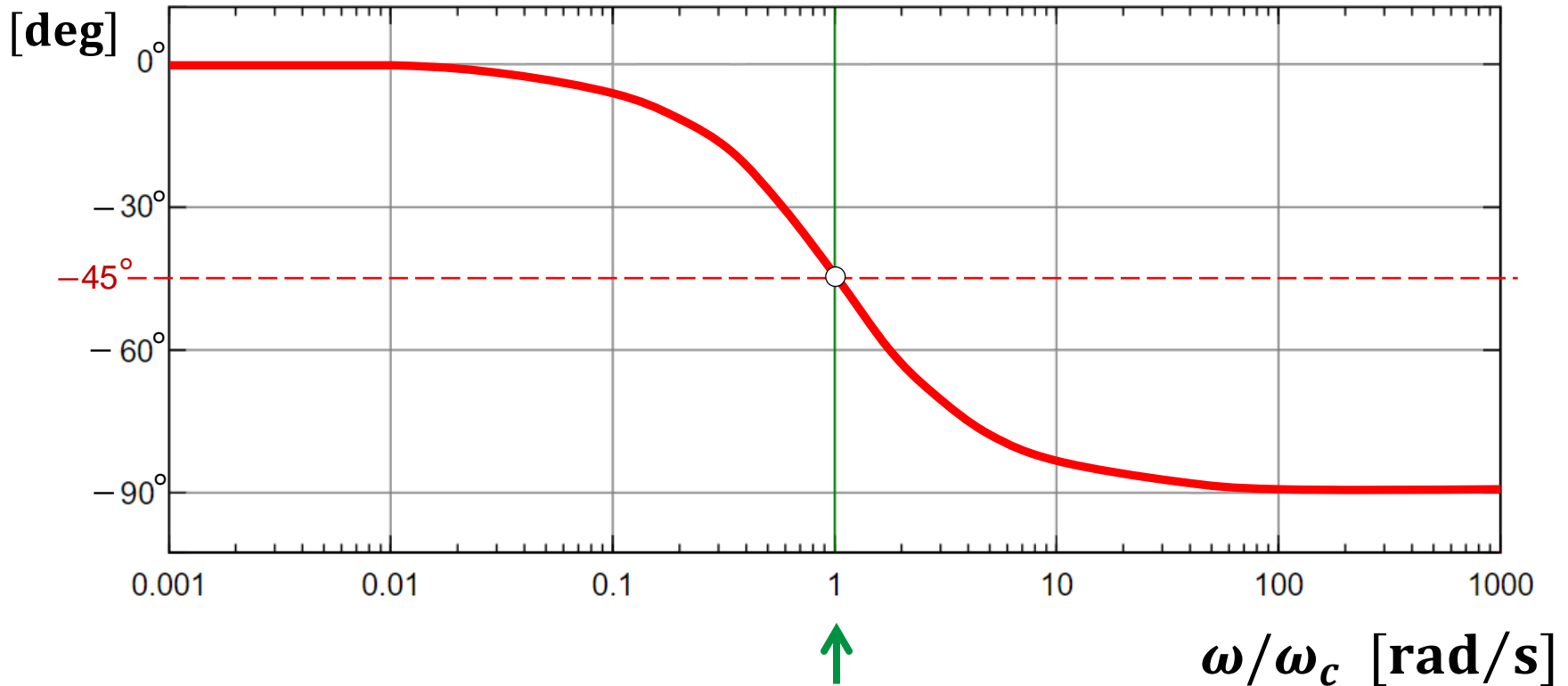

$$\omega_c = 2\pi f_c$$

Limitations of simple passive filters

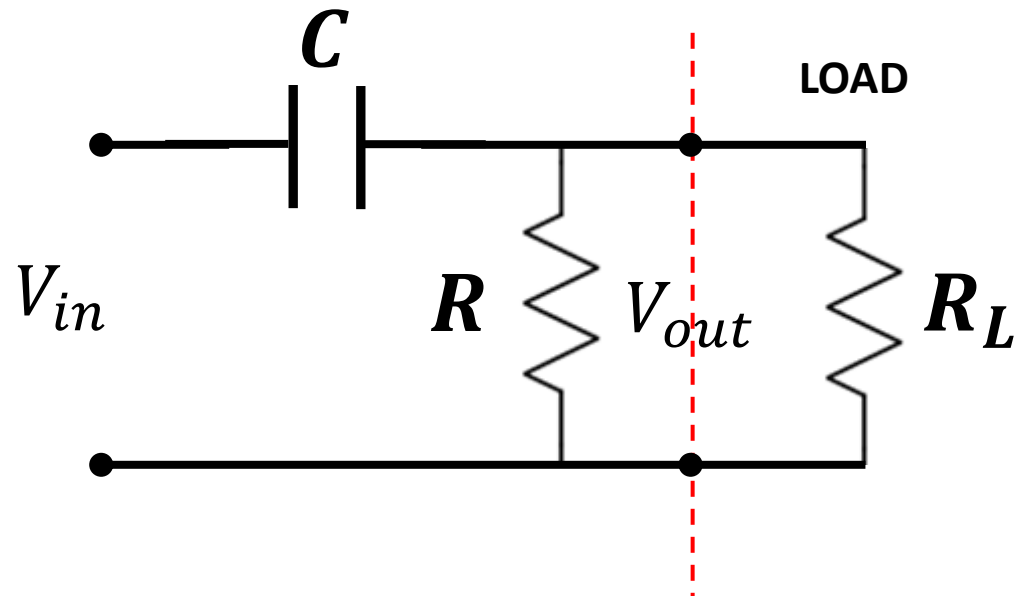
The response of a passive filter is affected by the load connected directly to it. For example, consider a high-pass RC filter:



The parallel $R_{\text{eff}} = R // R_L$ yields an equivalent resistance lower than either R or R_L . In particular, if connected to a small resistor R_L , the resulting cutoff frequency $\omega'_C = (R_{\text{eff}}C)^{-1}$ may change considerably with respect to the original $\omega_C = (RC)^{-1}$.

Overcome limitations by using active filters

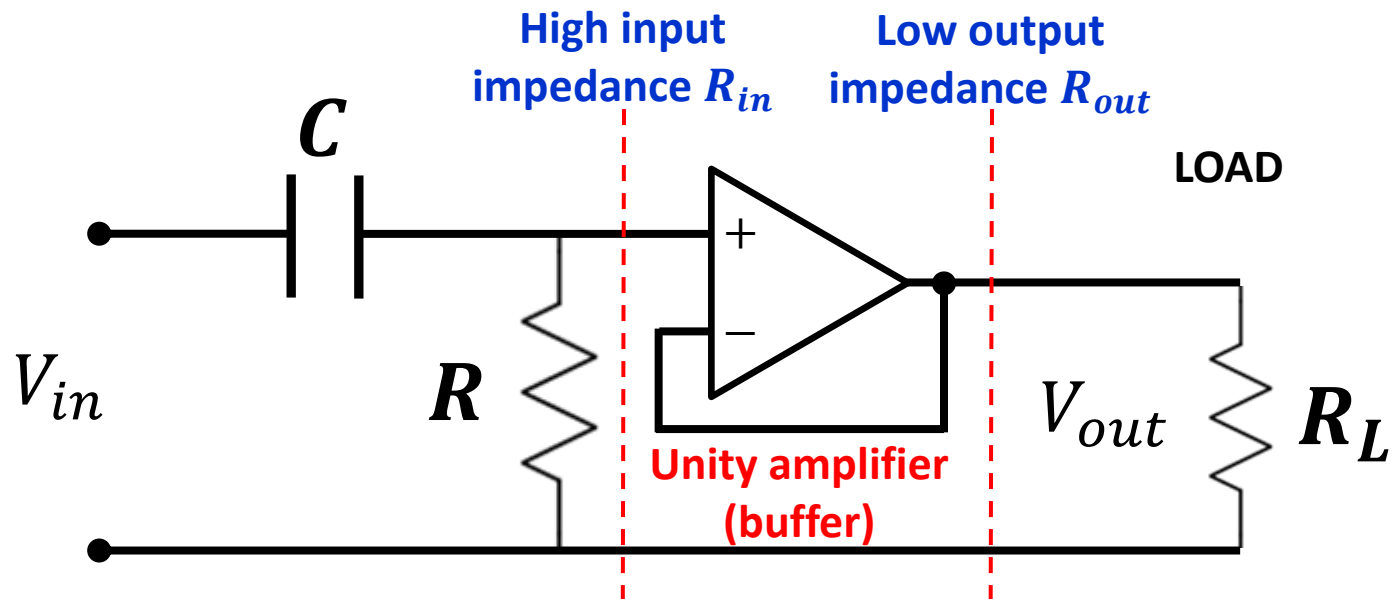
In the final part of the course, we will learn how a high input impedance operational amplifier can be used as an intermediate stage to improve the interconnection between filter and load.



The filter sees $R // R_{in} \approx R$ and is not affected. In output the voltage V_{out} drives a total resistance $R_{in} + R_L$. If R_{out} is much smaller, power is delivered mainly to the load R_L .

Band-Pass Filter

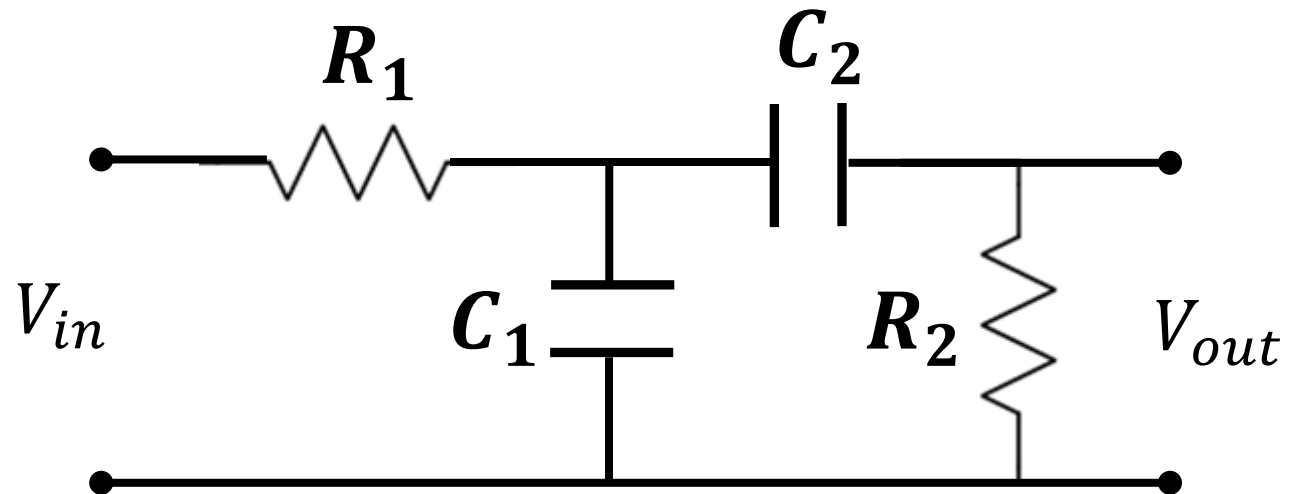
Cascade of a low pass and a high-pass filter can be designed so that $\omega_{CLP} > \omega_{CHP}$. The two filter characteristics combine, letting only an intermediate frequency band pass through.



Looking at frequency extremes, one can see that:


- $\omega = 0$ capacitors behave like open circuit $\rightarrow V_{out} = 0$
- $\omega \rightarrow \infty$ capacitors behave like short circuit $\rightarrow V_{out} = 0$

Band-Pass Filter

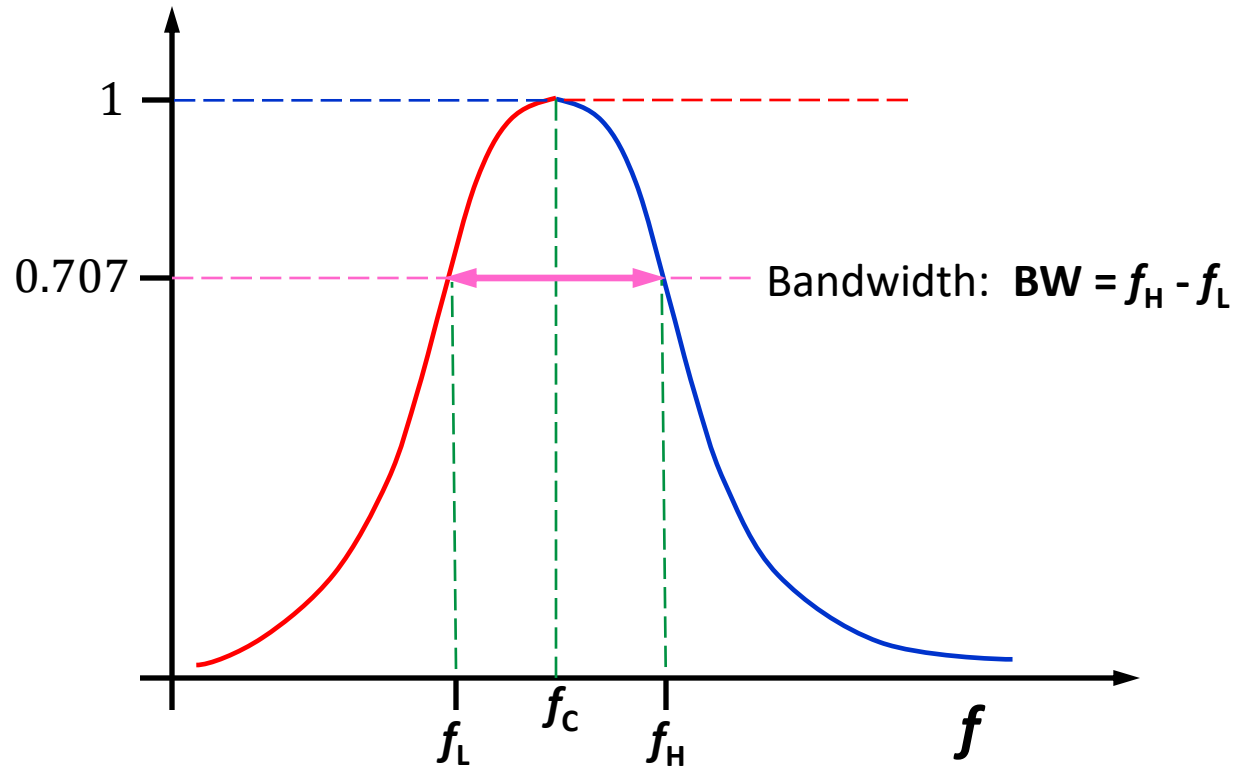


Frequencies $f < f_L$ and $f > f_H$ are strongly attenuated

Band-Stop Filter

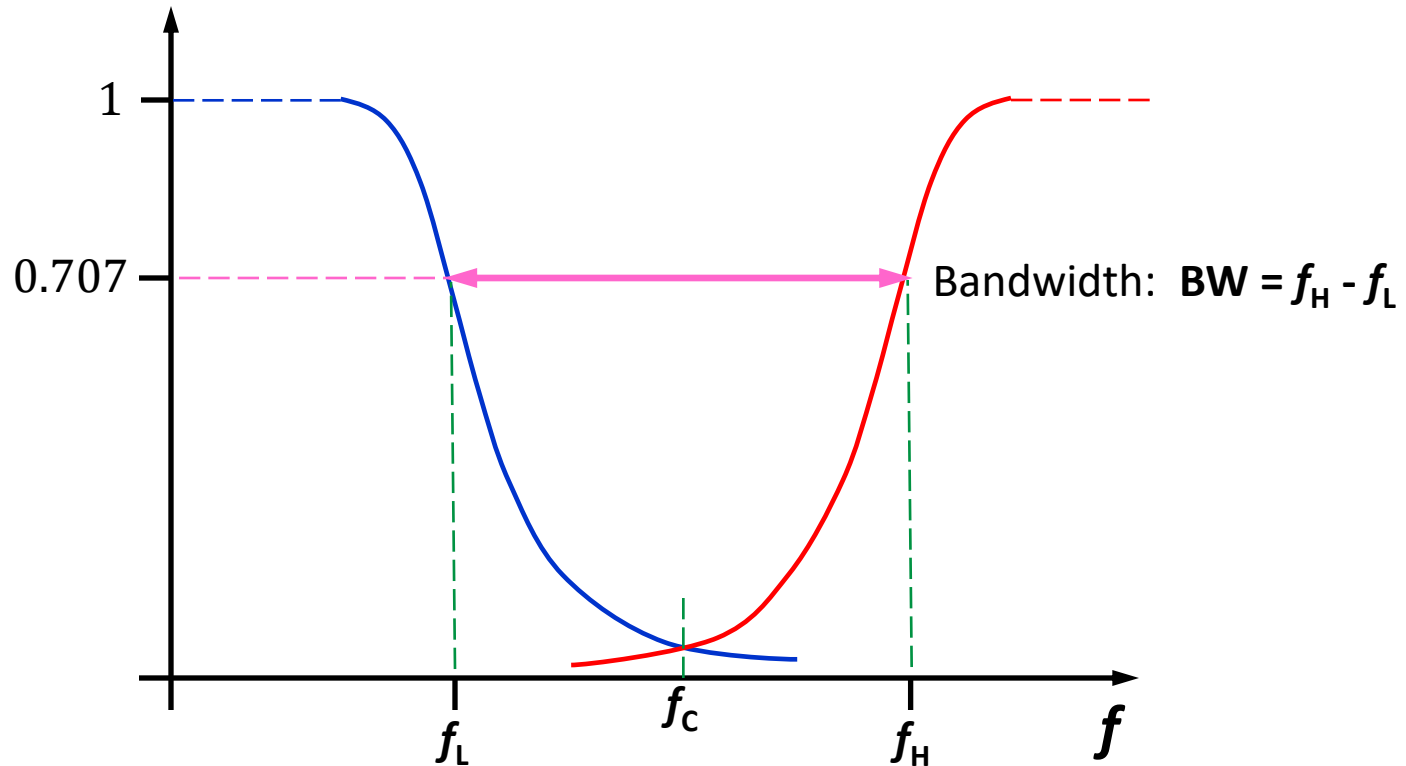


Frequencies and $f_L < f < f_H$ are strongly attenuated

Notch Filter

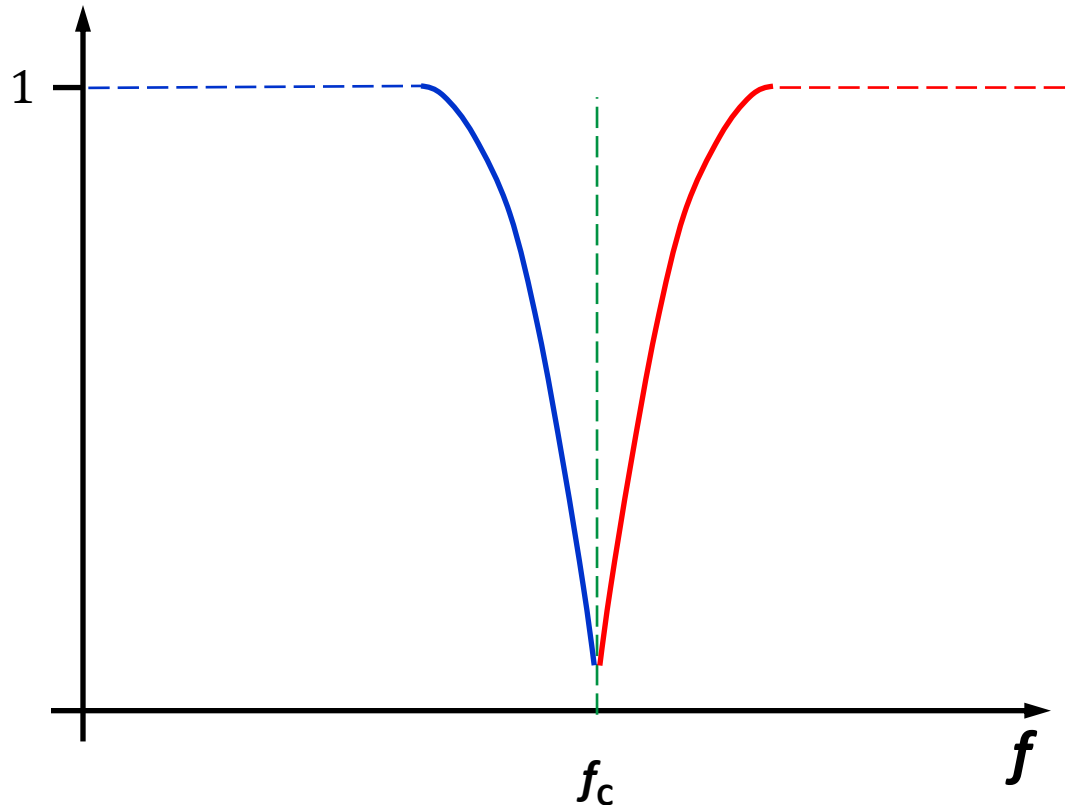

A very narrow band-stop filter, designed to reject a specific frequency, is called a **notch filter**.

Comb Filter

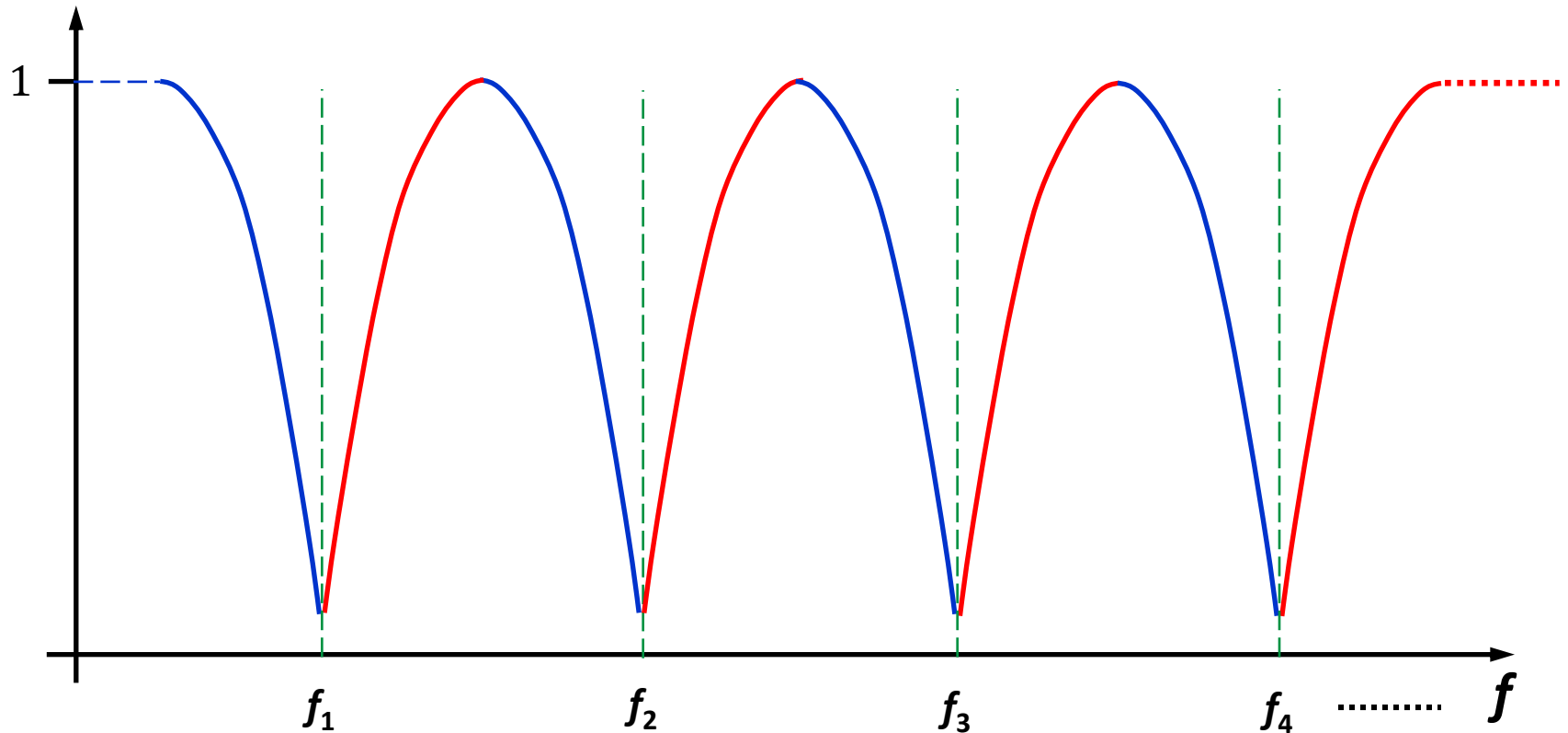

The comb filter consists of a series of regularly spaced notches and peaks (also called *teeth*).

Operational Amplifiers

Passive Circuit Response

The frequency response of passive circuits has notable limitations.


- The magnitude of the transfer function is always $|H(\omega)| \leq 1$
- When a load is applied, the frequency response changes

Operational amplifiers can be used to address these limitations.

Operational Amplifier


The Operational Amplifier (or **OP AMP**) is a versatile high gain circuit whose response characteristics can be controlled with the application of feedback.

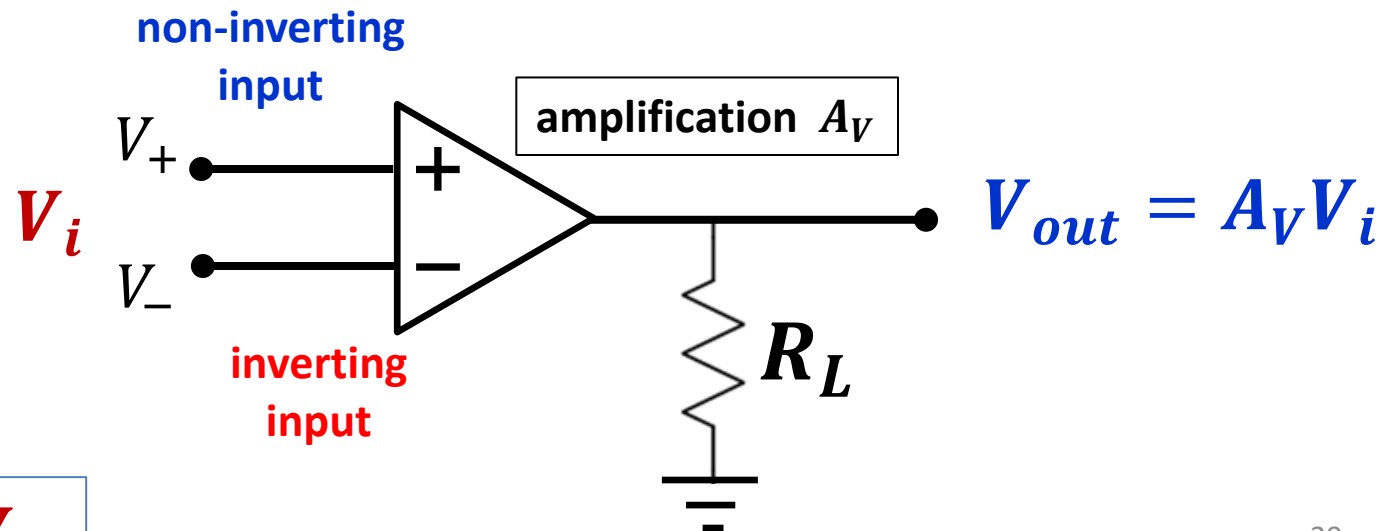It is commonly available in a compact integrated circuit package and it can be used as the basic building block for designing many analog circuit applications.




$$V_i = V_+ - V_-$$

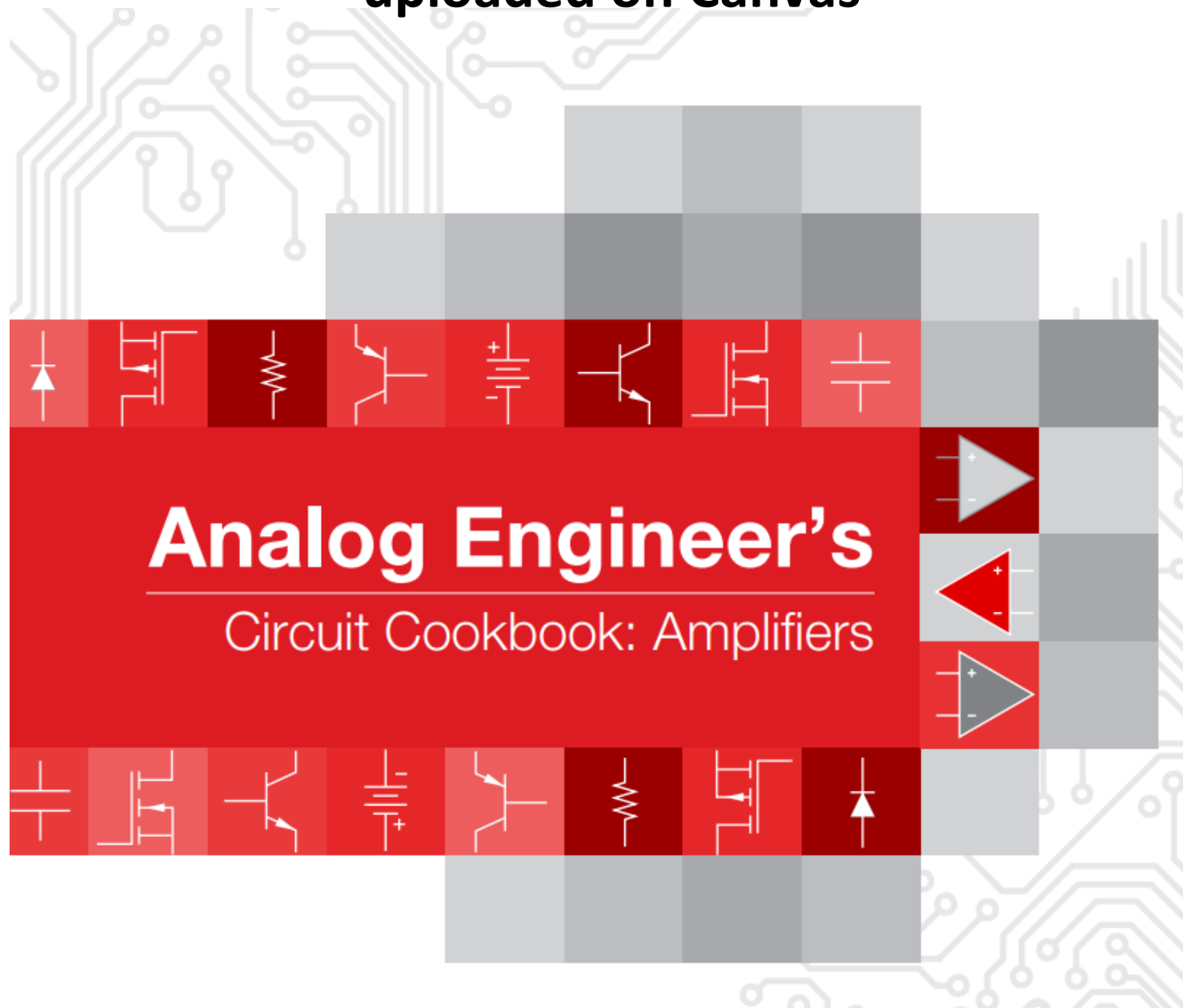Extensive technical reference from Texas Instruments uploaded on Canvas



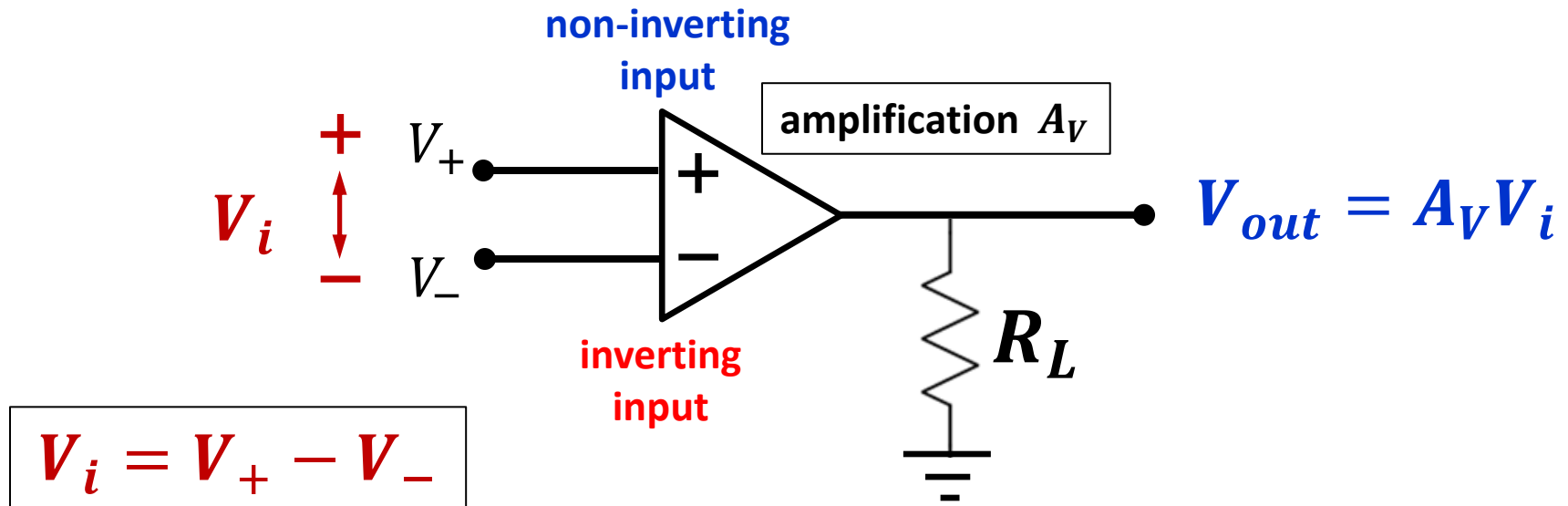The OP AMP has usually two inputs and one output




The gain between V_{out} and V_+ is positive (non-inverting)

$$\frac{V_{out}}{V_+} > 0$$

The gain between V_{out} and V_- is negative (inverting)

$$\frac{V_{out}}{V_-} < 0$$

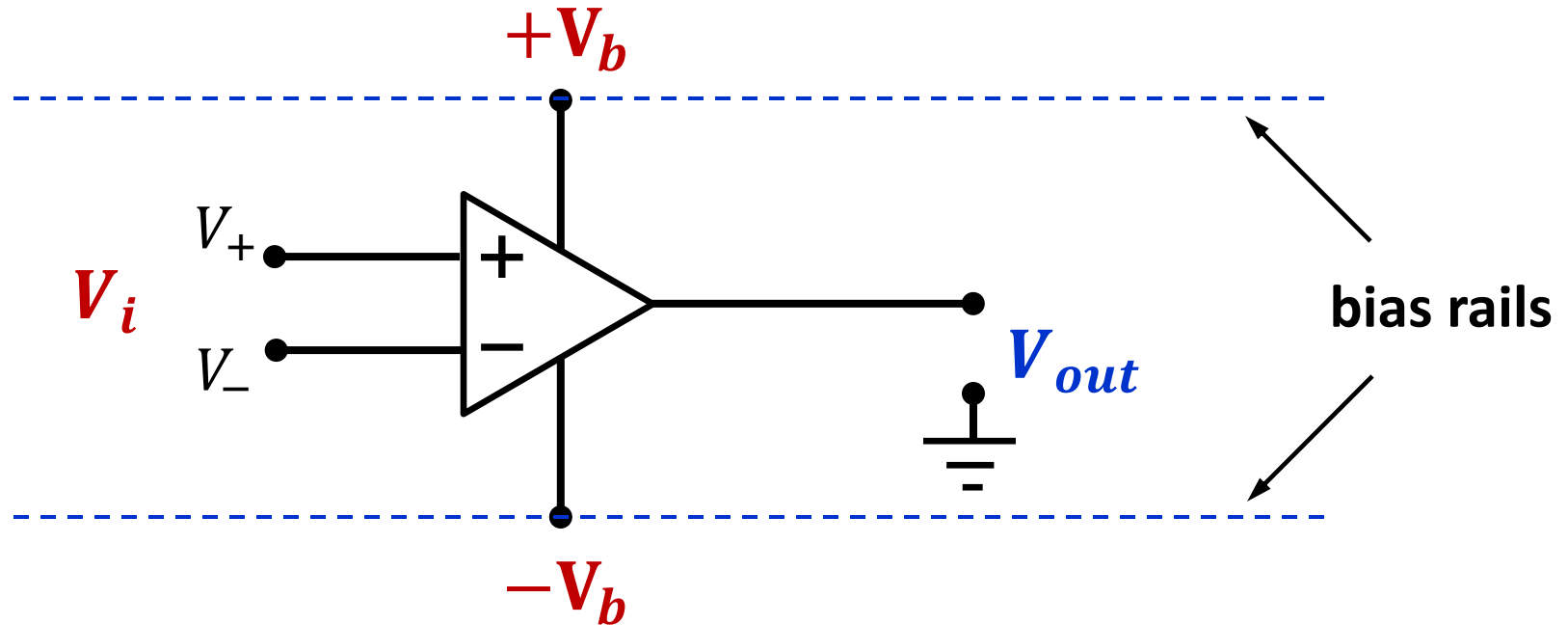The OP AMP is an active device requiring power from a DC power supply. A common design has two balanced $\pm V_b$ bias voltages.



The output signal V_{out} can swing between $\pm V_b$ but it will saturate if trying to exceed $|V_b|$.

NOTE: An OMP AMP is a “direct coupled” amplifier and it works also in DC conditions, not only AC.





A very popular general purpose Op Amp: the "741"



~ 20 transistors


LM741 Operational Amplifier

Metal Can Package

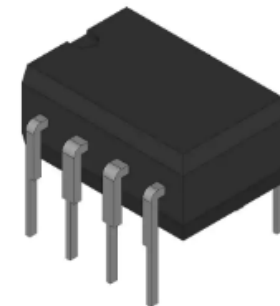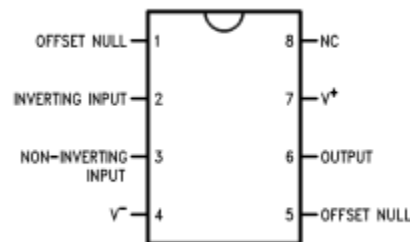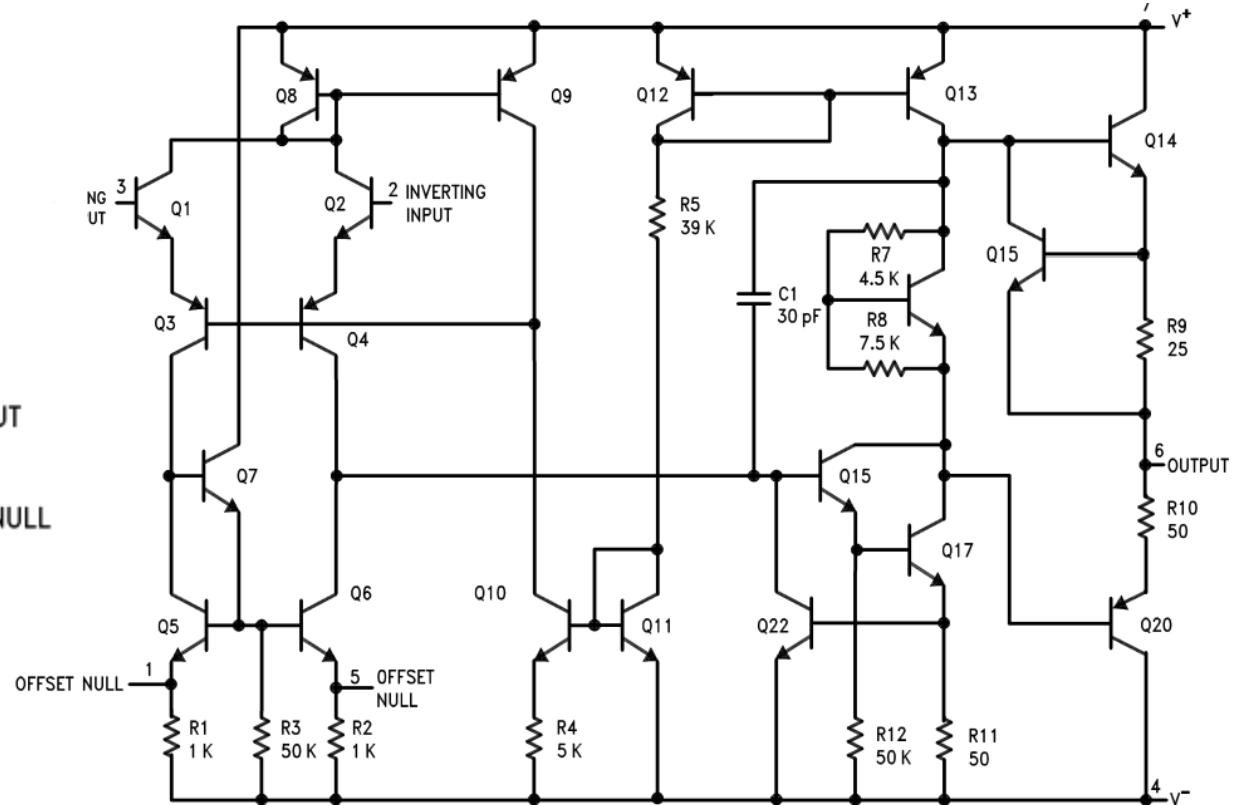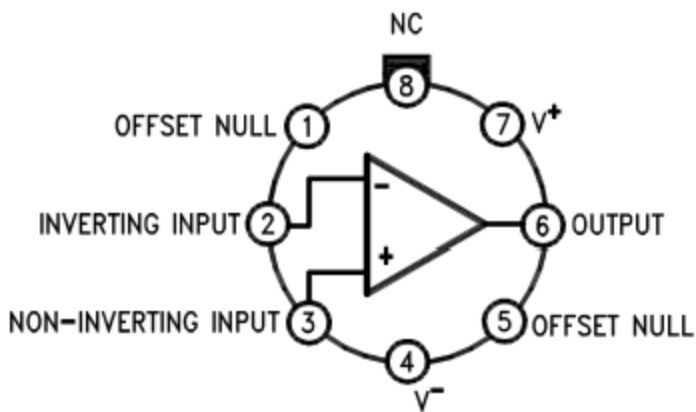

Ideal Operational Amplifier

Equivalent Circuit

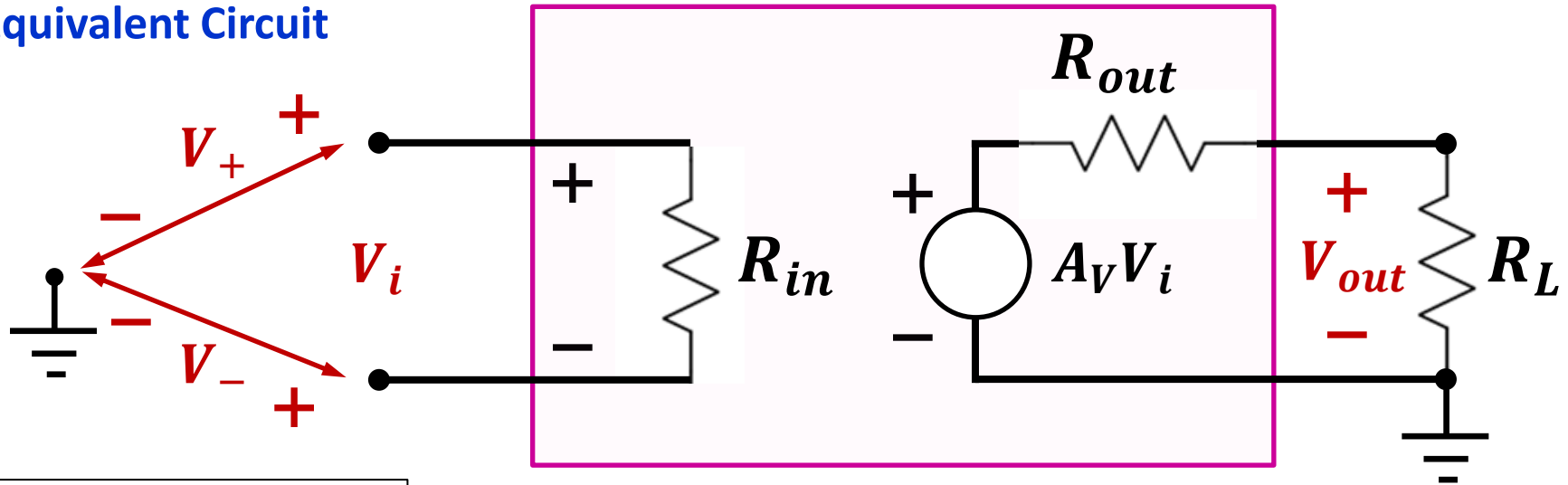


$$V_i = V_+ - V_-$$

open circuit voltage gain A_V


- Input Resistance $R_{in} \rightarrow \infty$
- Output Resistance $R_o \rightarrow 0$
- Open-circuit voltage gain $A_V \rightarrow -\infty$. In real devices $A_V \approx 10^6$.
- Bandwidth $\rightarrow \infty$ (same operation up to any frequency)
- $V_{out} = 0$ when $V_+ = V_-$
- Behavior is independent of temperature

Example 1

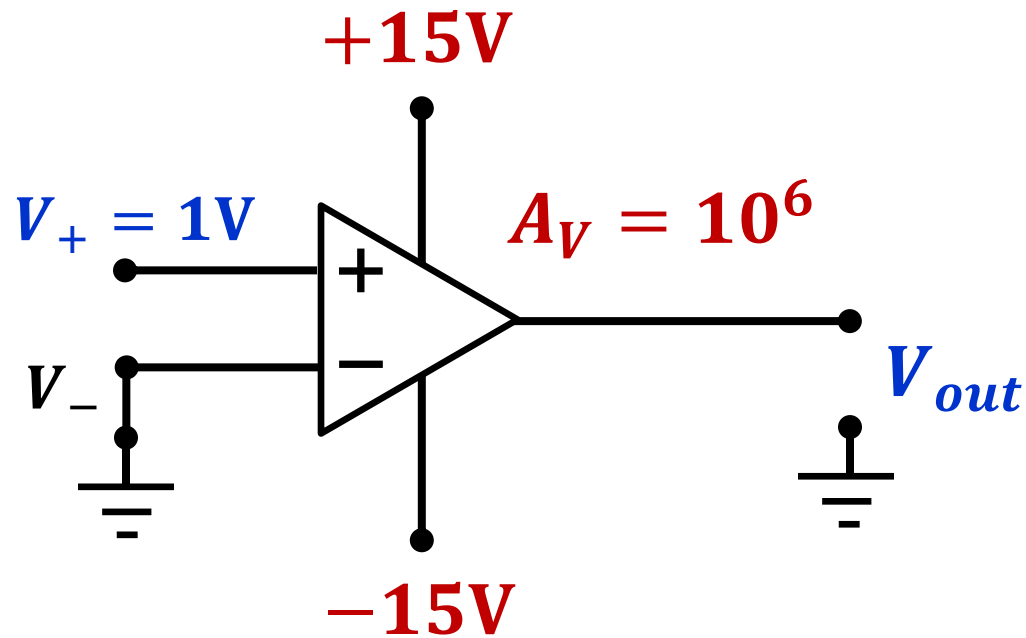


$$V_{out} = A_V \times (V_+ - V_-) = 10^6 (1 - 0) = 10^6 V$$


Saturation occurs at +15 Volts.

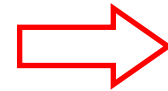

$$V_{out} = 15V$$

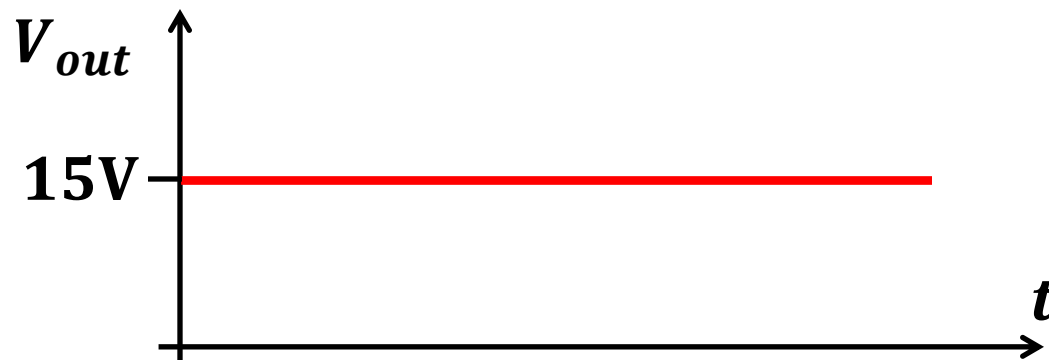


Example 2

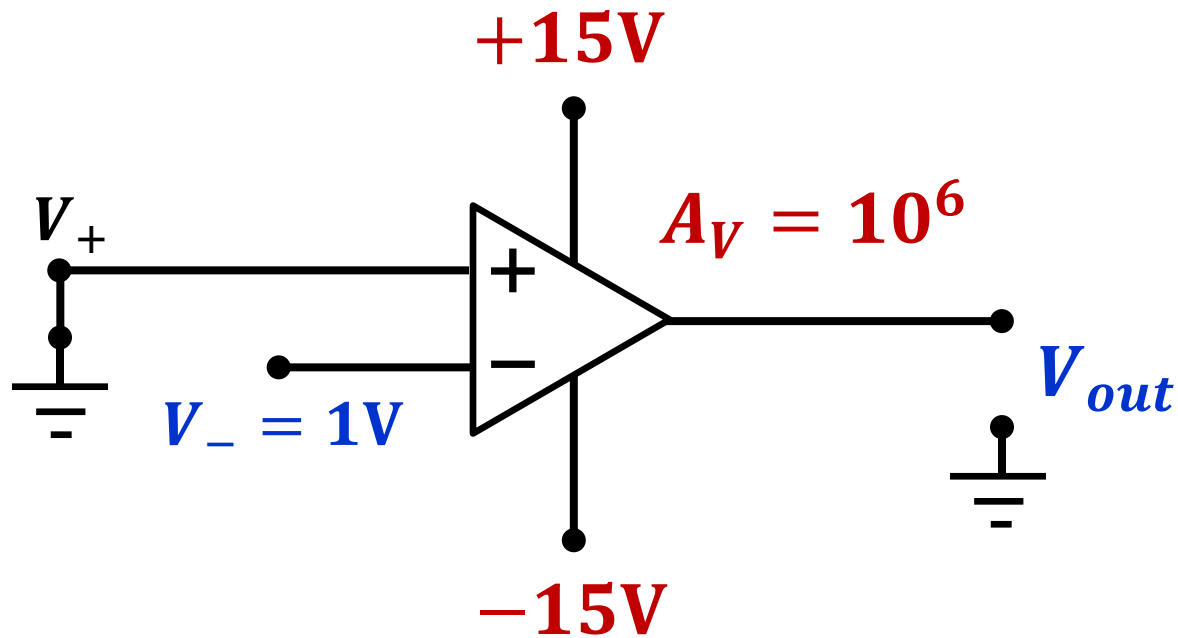


$$V_{out} = A_V \times (V_+ - V_-) = 10^6(0 - 1) = -10^6V$$




Saturation occurs at -15 Volts.

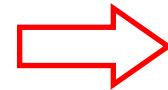


$$V_{out} = -15V$$

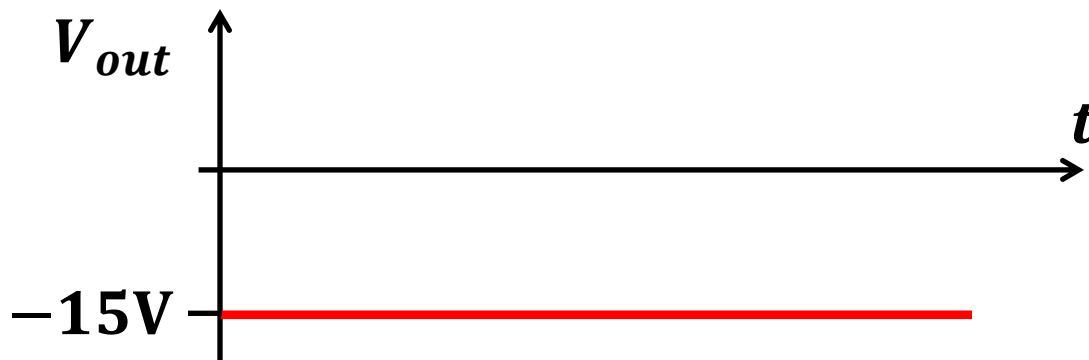

Example 3

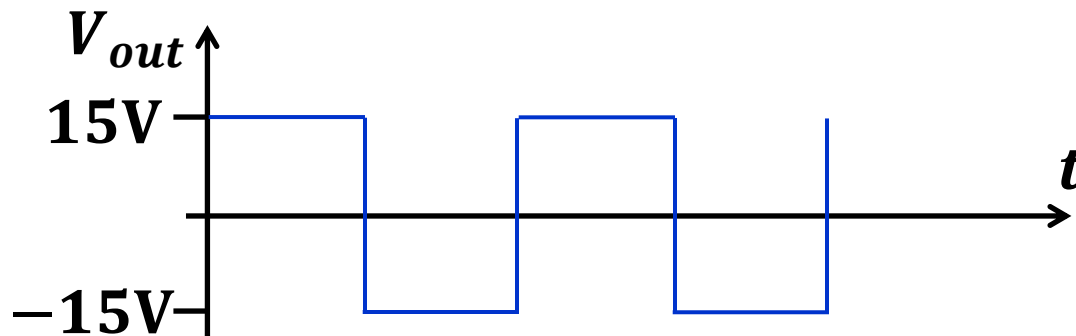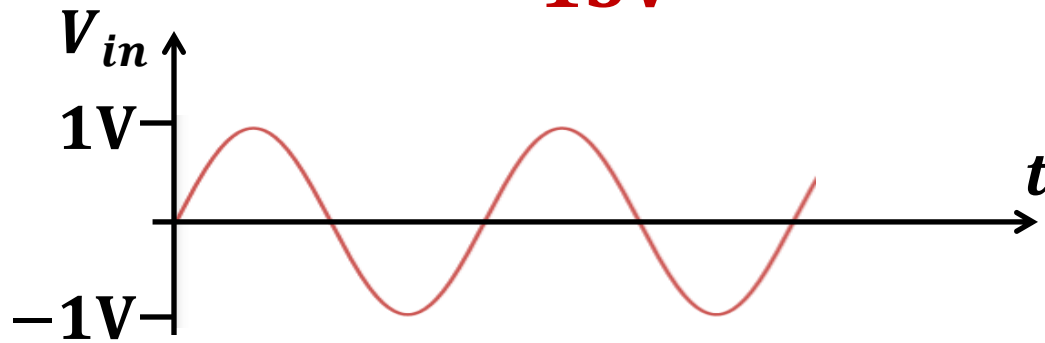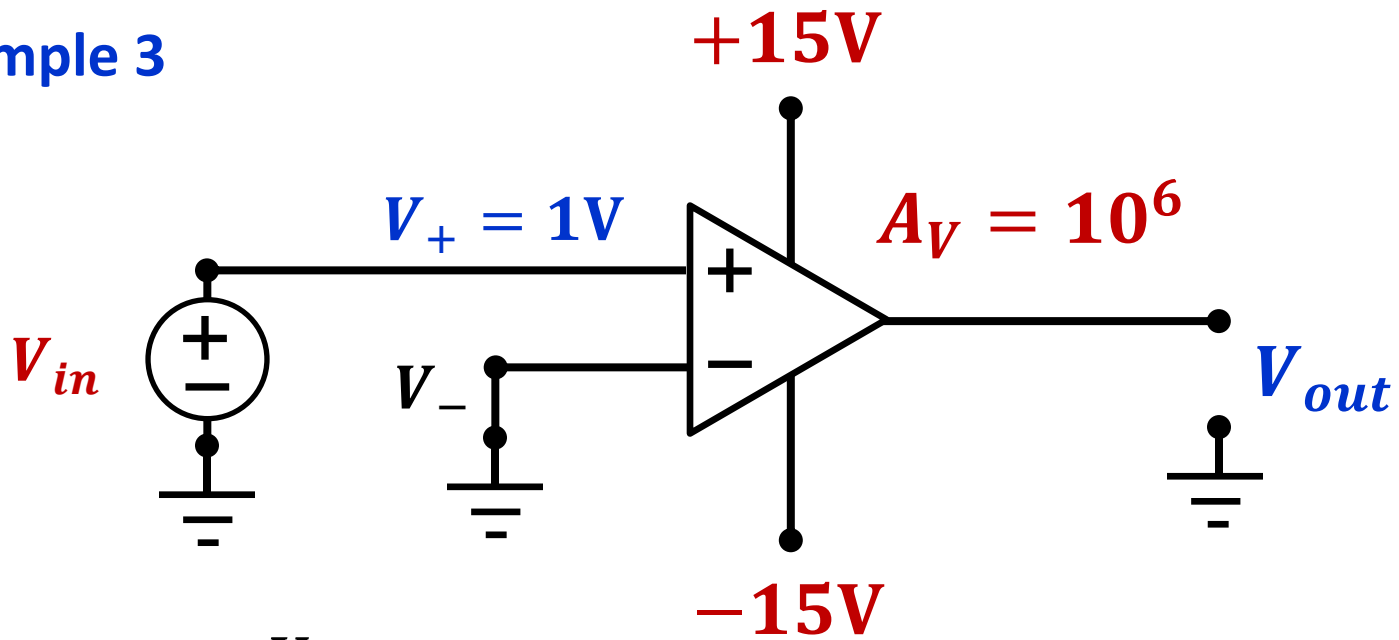

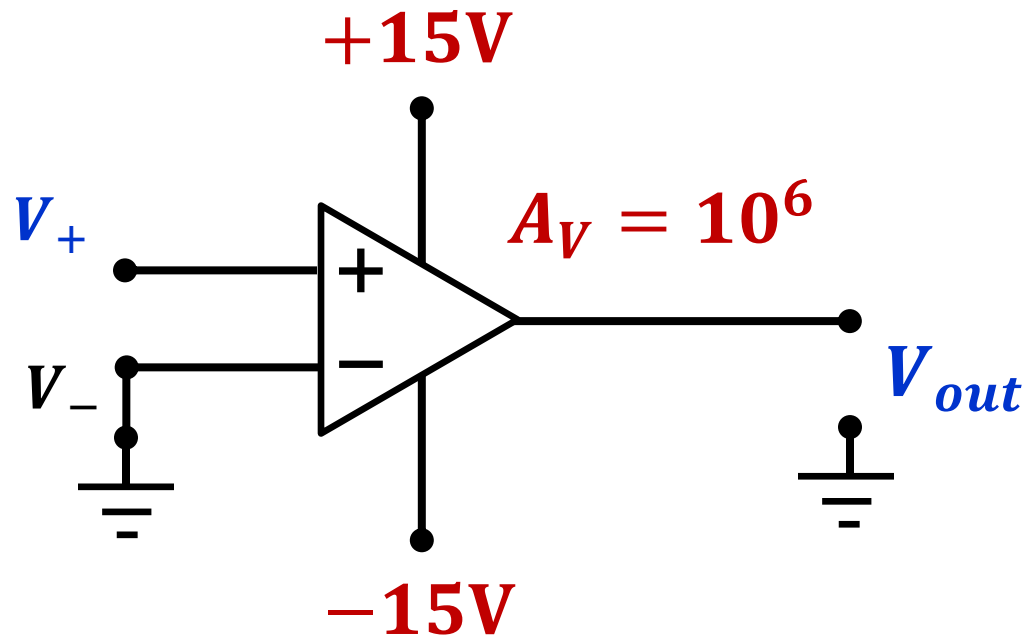

The circuit in Examples 1, 2, and 3 is called a “**COMPARATOR**”

$$V_{out} = +15V \quad \text{if} \quad V_+ > V_-$$

$$V_{out} = -15V \quad \text{if} \quad V_+ < V_-$$

$$V_{out} = 0V \quad \text{if} \quad V_+ = V_-$$

The gain A_V of the OP AMP is extremely large and the output saturates easily to $\pm V_b$.

This occurs even for minute values of the voltage between input terminals when

$$|(V_+ - V_-)| > V_b / A_V$$

Feedback

When $|(V_+ - V_-)| < V_b/A_V$, the output V_{out} does not saturate and follows the functional form of the input as

$$V_{out} = A_V(V_+ - V_-)$$

implying

$$V_+ \approx V_-$$

since the gain is so large.

To achieve these conditions, the OP AMPS are operated in **FEEDBACK** configuration.