

ECE 205 “Electrical and Electronics Circuits”

Spring 2024 – LECTURE 37

MWF – 12:00pm


Prof. Umberto Ravaioli
2062 ECE Building

Lecture 37 – Summary

Learning Objectives

- 1. Applications of Operational Amplifiers**

Quiz 4 – Grade distribution

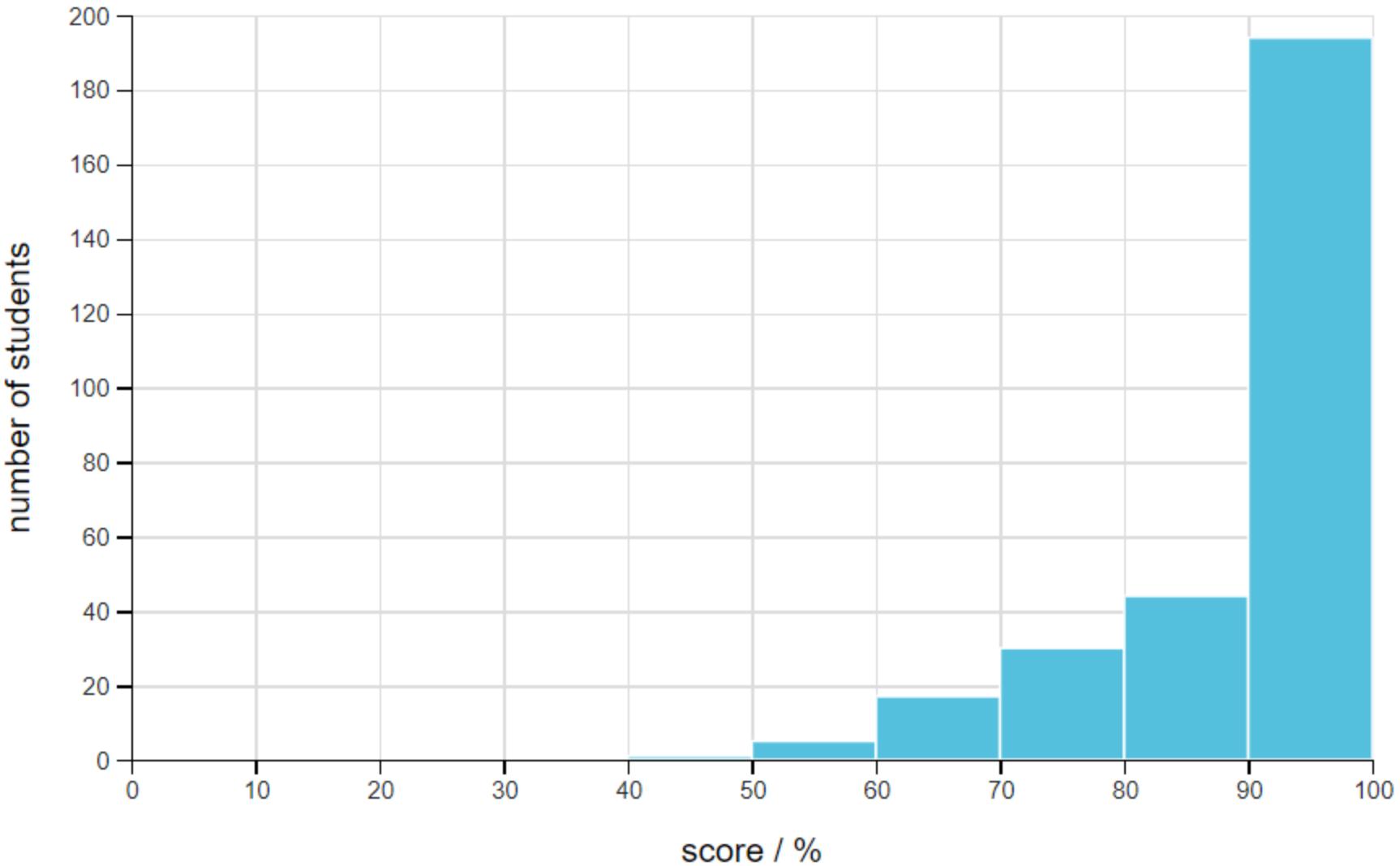


Quiz 4 – Statistics


| | |
|--------------------|-------------------|
| Number of students | 291 |
| Mean score | 90% |
| Standard deviation | 11% |
| Median score | 94% |
| Minimum score | 45% |
| Maximum score | 100% |
| Number of 0% | 0 (0% of class) |
| Number of 100% | 31 (11% of class) |

Voyager 1 probe

← $\approx 10 \text{ km/s}$

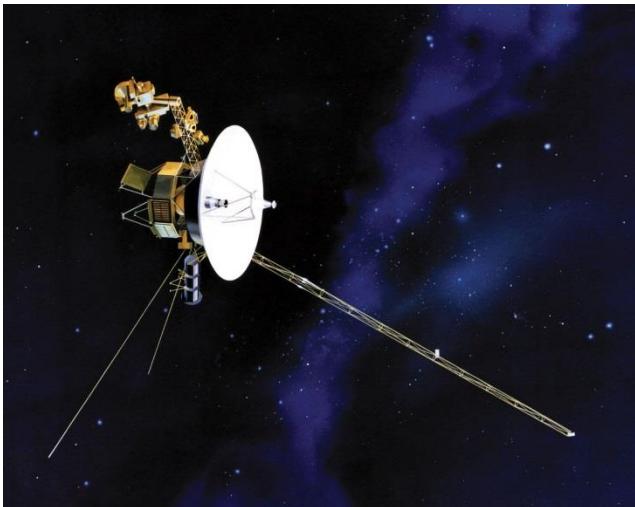

April 2024

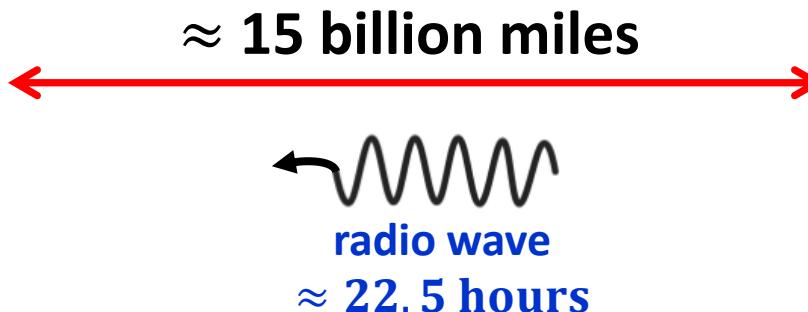

September 5, 1977

Went silent in November 2023 due to failure of one memory chip


NASA engineers have rerouted the code to another memory chips

This week communications have been reestablished

The onboard computer memory is 70 Kbytes


The digital tape recorder can store 67 Mbytes of data

Example 1

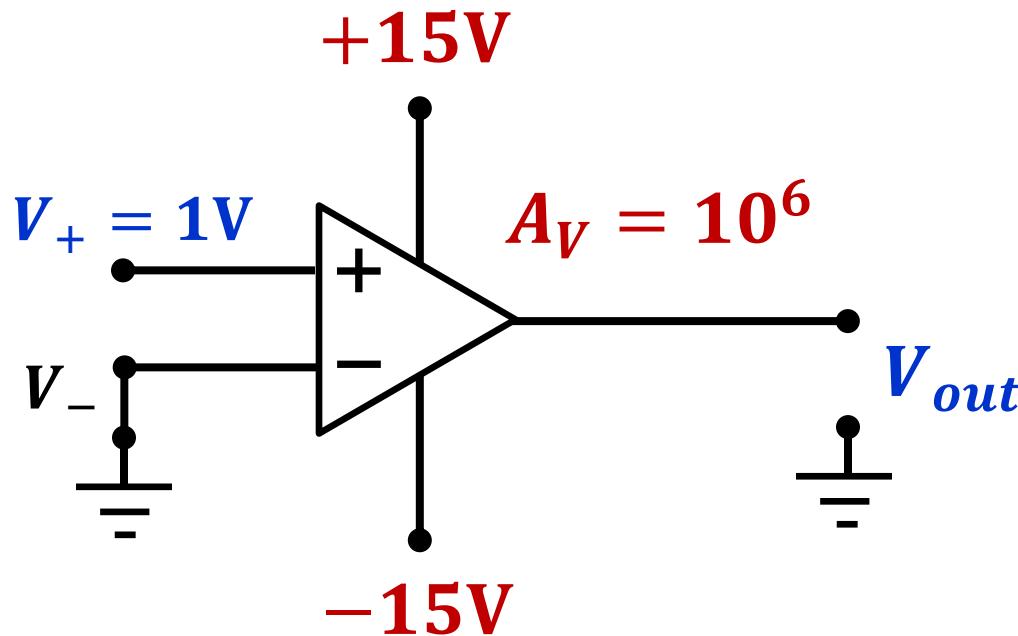


$$V_{out} = A_V \times (V_+ - V_-) = 10^6(1 - 0) = 10^6V$$


Saturation occurs at +15 Volts.

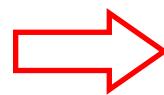

$$V_{out} = 15V$$

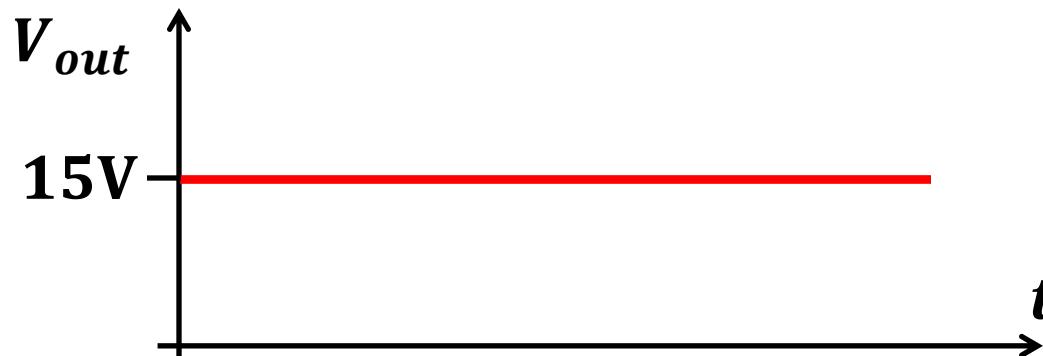


Example 2

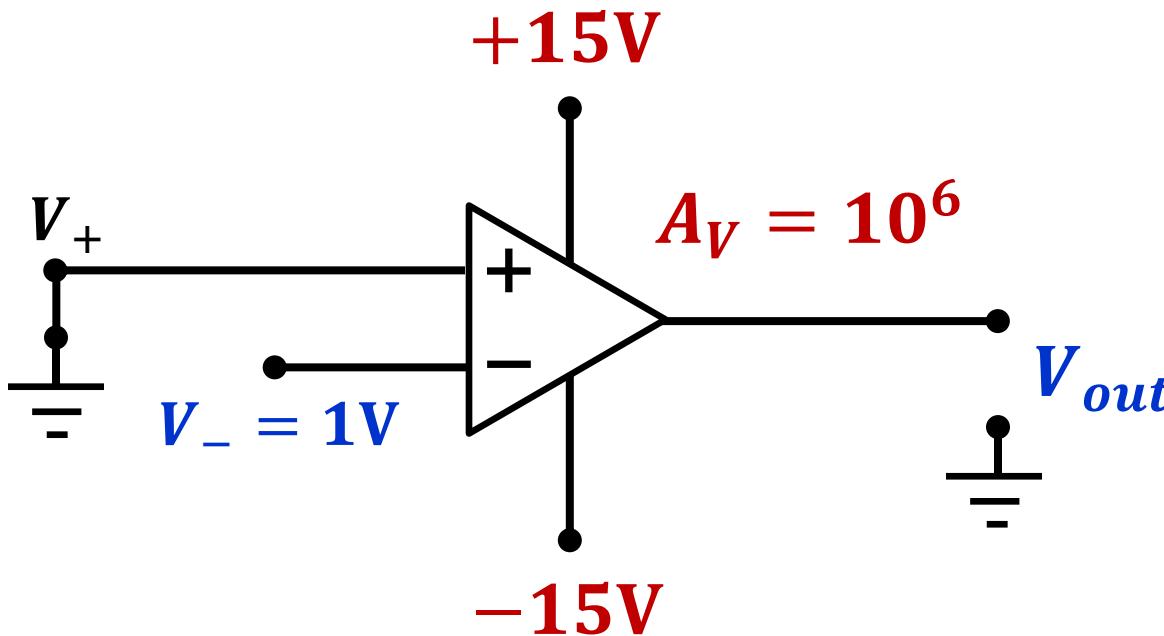

$$V_{out} = A_V \times (V_+ - V_-) = 10^6(0 - 1) = -10^6V$$




Saturation occurs at -15 Volts.

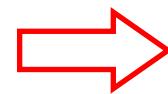


$$V_{out} = -15V$$



Example 3

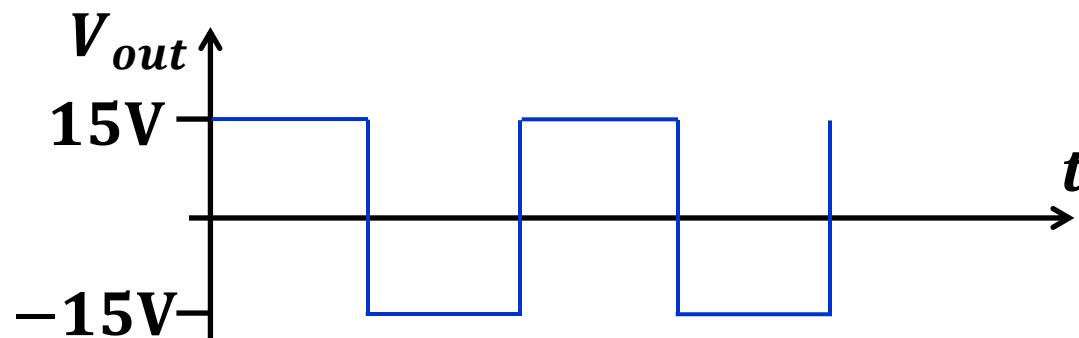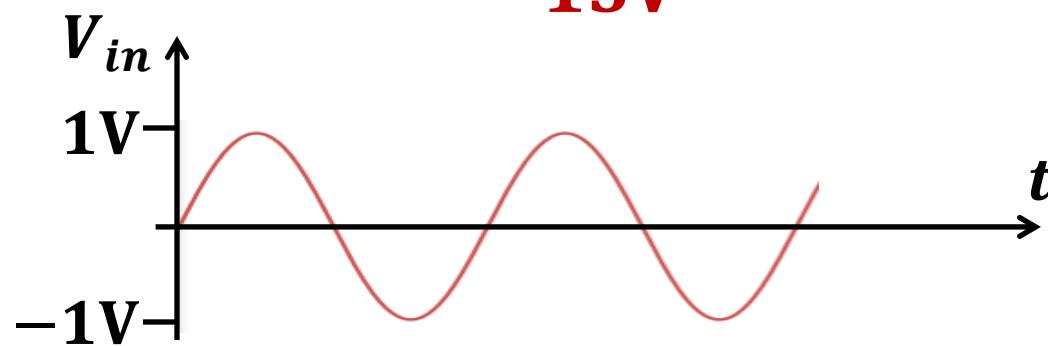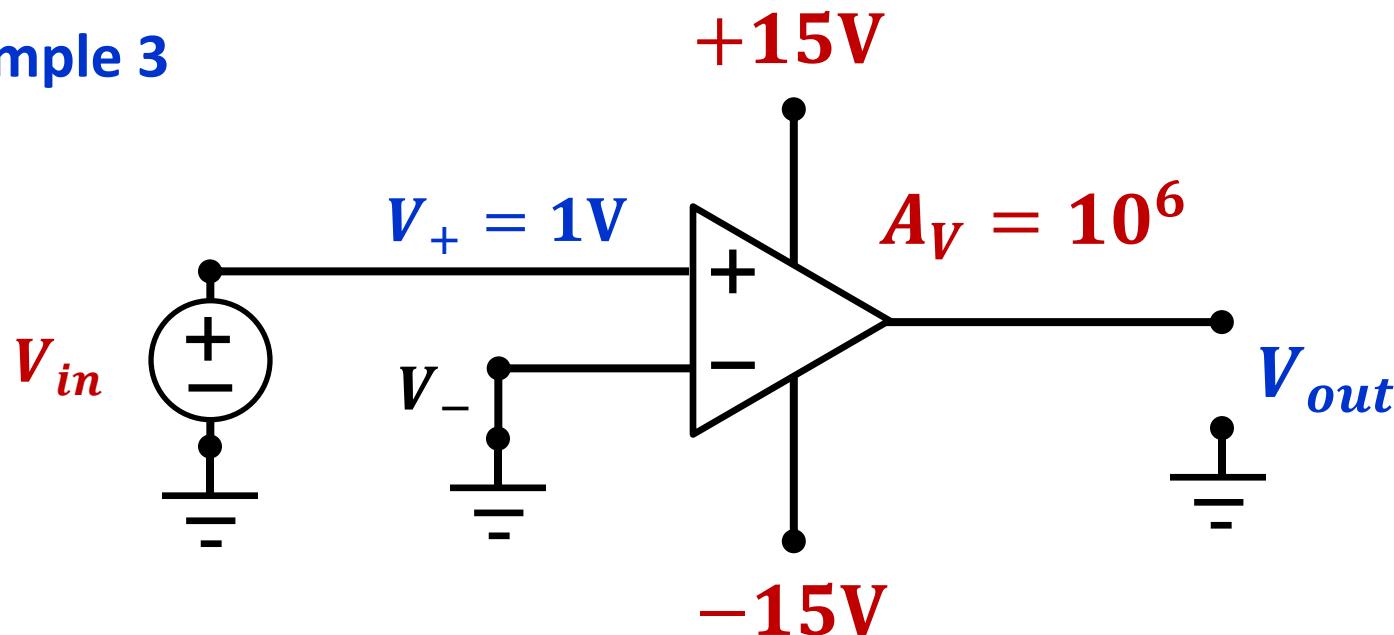


Ideal Inverting Amplifier

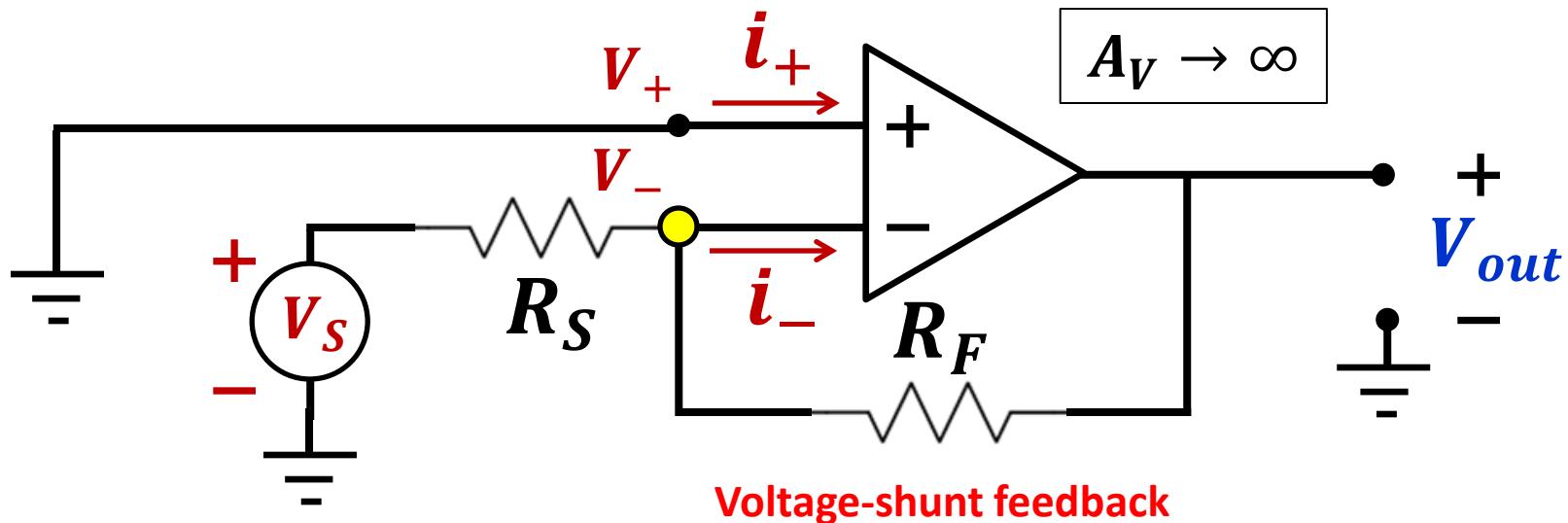

The **voltage gain with feedback** is

$$A_{VF} = \frac{V_{out}}{V_S} = -\frac{R_F}{R_S}$$

Ideal Non-inverting Amplifier

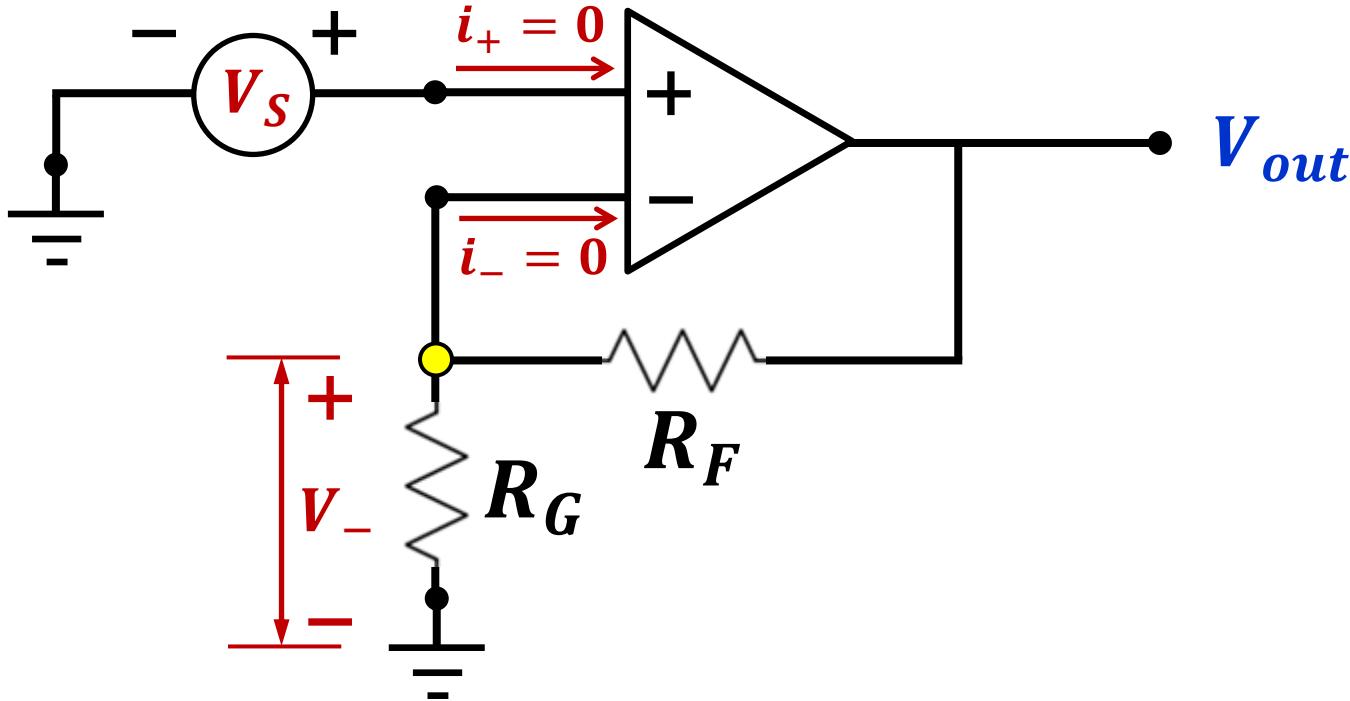

Gain is positive


$$A_{VF} = 1 + \frac{R_F}{R_G}$$

Input and output in phase

Amplifier operates in linear region when

$$1 + \frac{R_F}{R_G} < \left| \frac{V_{CC}}{V_S} \right|$$


Example 4

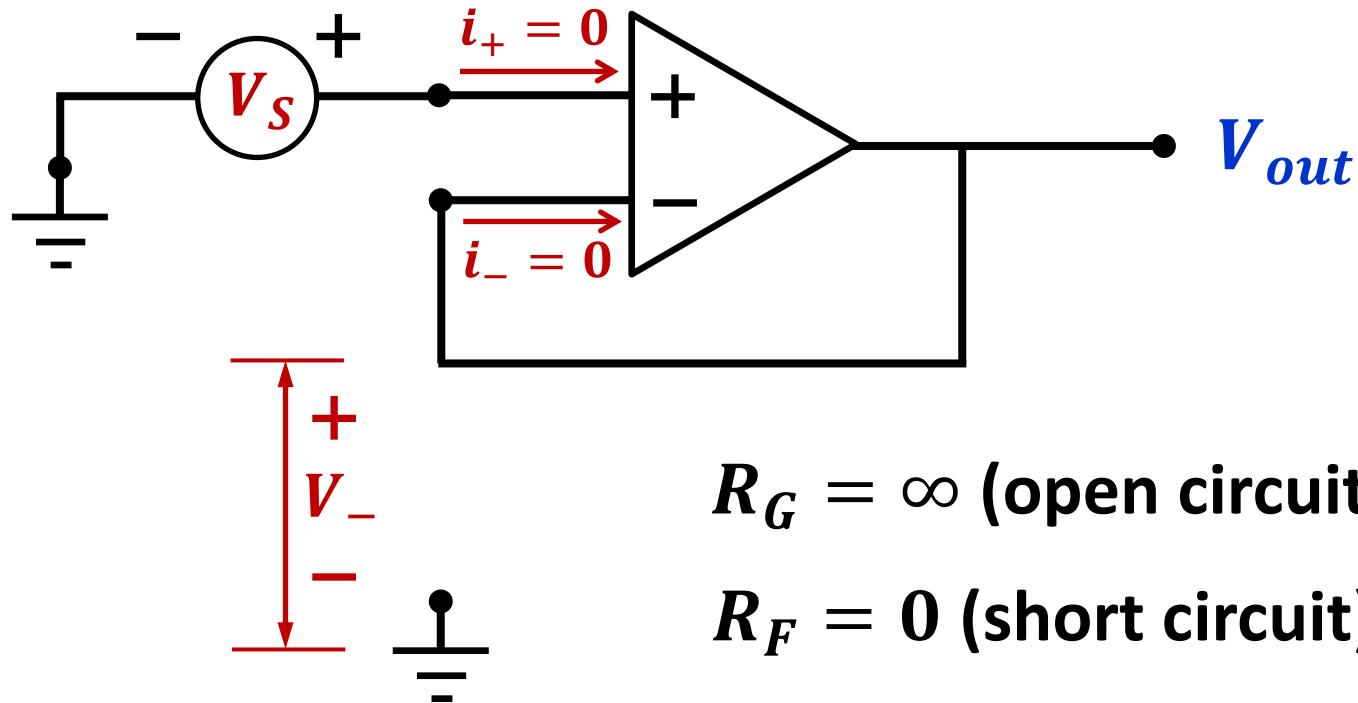

$$A_{VF} = \frac{V_{out}}{V_S} = \frac{V_{out}}{V_-} = \frac{R_G + R_F}{R_G} = 1 + \frac{\cancel{R_F}}{\cancel{R_G}}$$

$$\rightarrow V_{out} = V_S$$

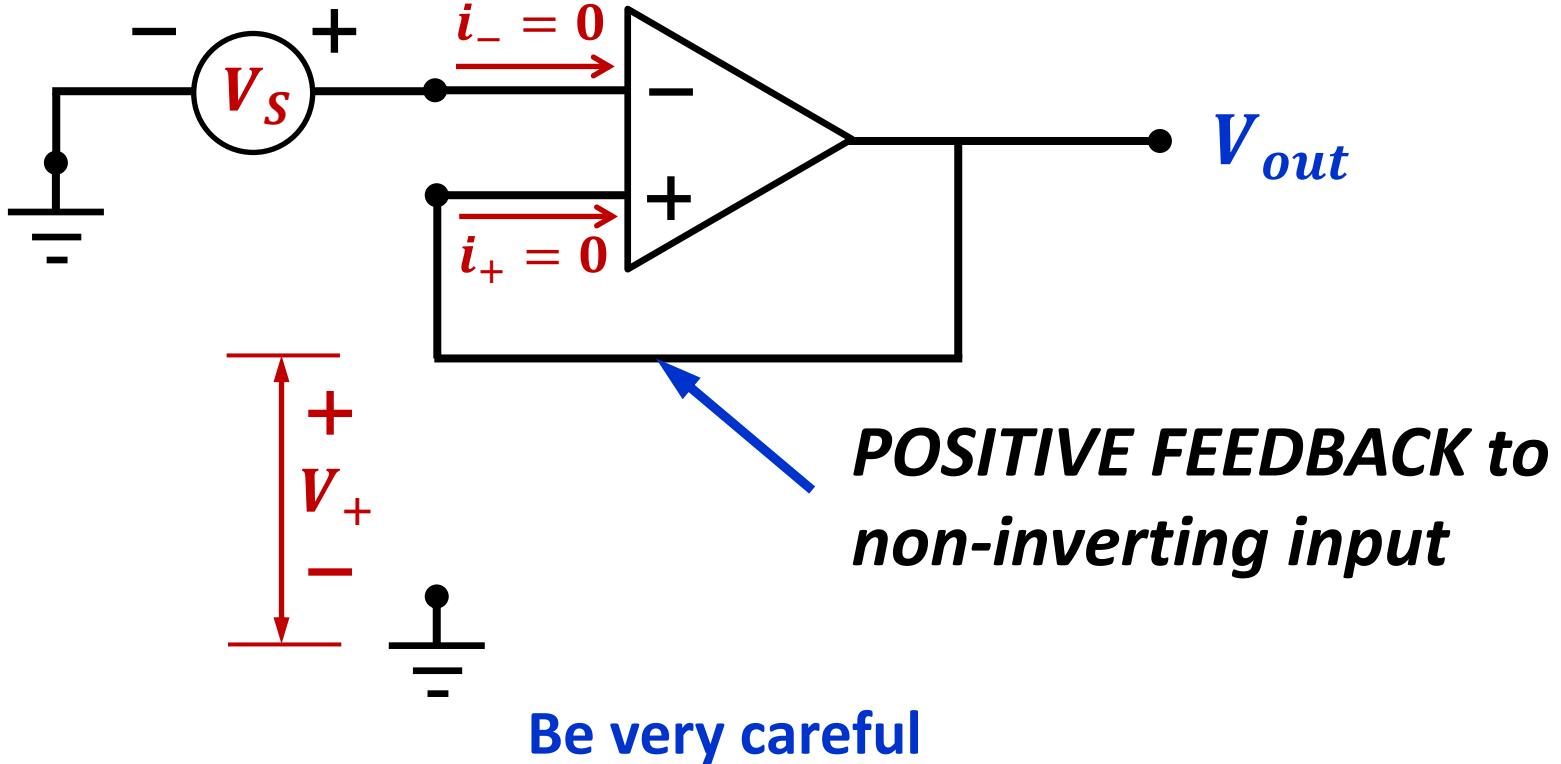
Unity amplifier (buffer) also called “*Voltage Follower*”



The configuration above is NOT a voltage follower, because the feedback loop connects to the non-inverting input


This Op Amp tends to saturate quickly to $\pm V_{CC}$ depending on polarity and magnitude of V_S (bistable circuit). This circuit DOES NOT OPERATE IN THE LINEAR RANGE AND DOES NOT DUPLICATE THE INPUT TO THE OUTPUT.

Example 5

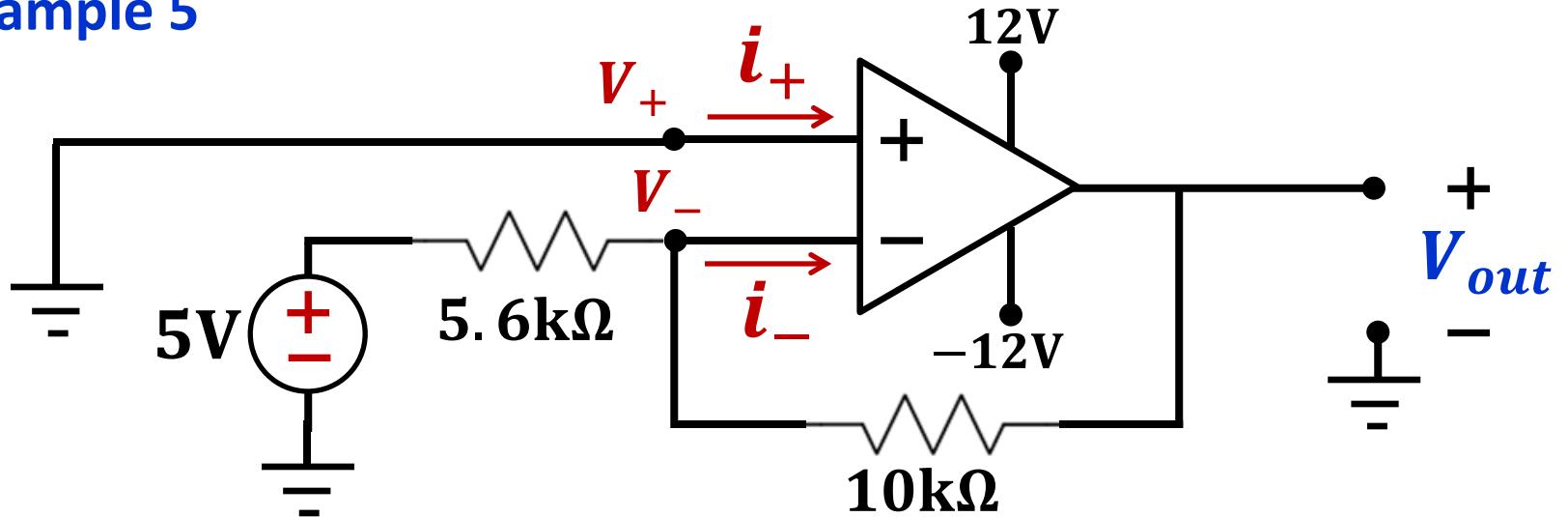


$$\frac{V_{out}}{V_S} = -\frac{R_F}{R_S}$$

Example 5

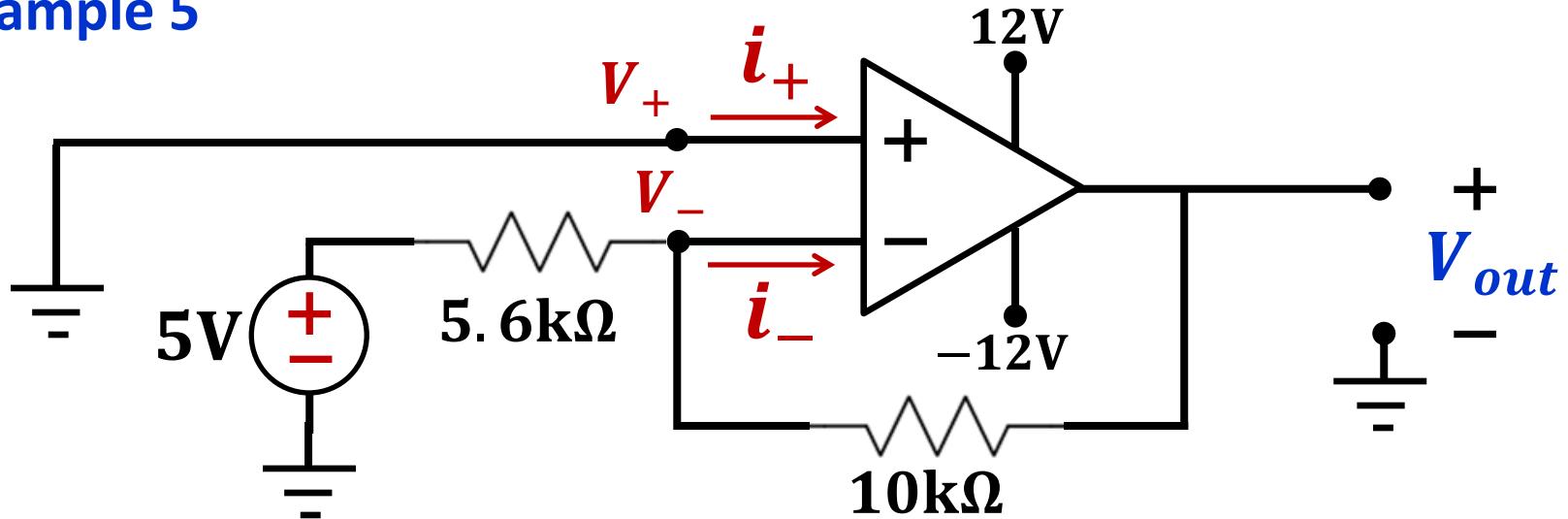

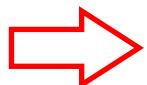
$$\frac{V_{out}}{V_S} = -\frac{R_F}{R_S}$$



$$V_{out} = -5 \frac{10k}{5.6k} = -8.93V$$


Since $|V_{out}| < |V_{CC}|$, the result obtained is valid.

Example 6

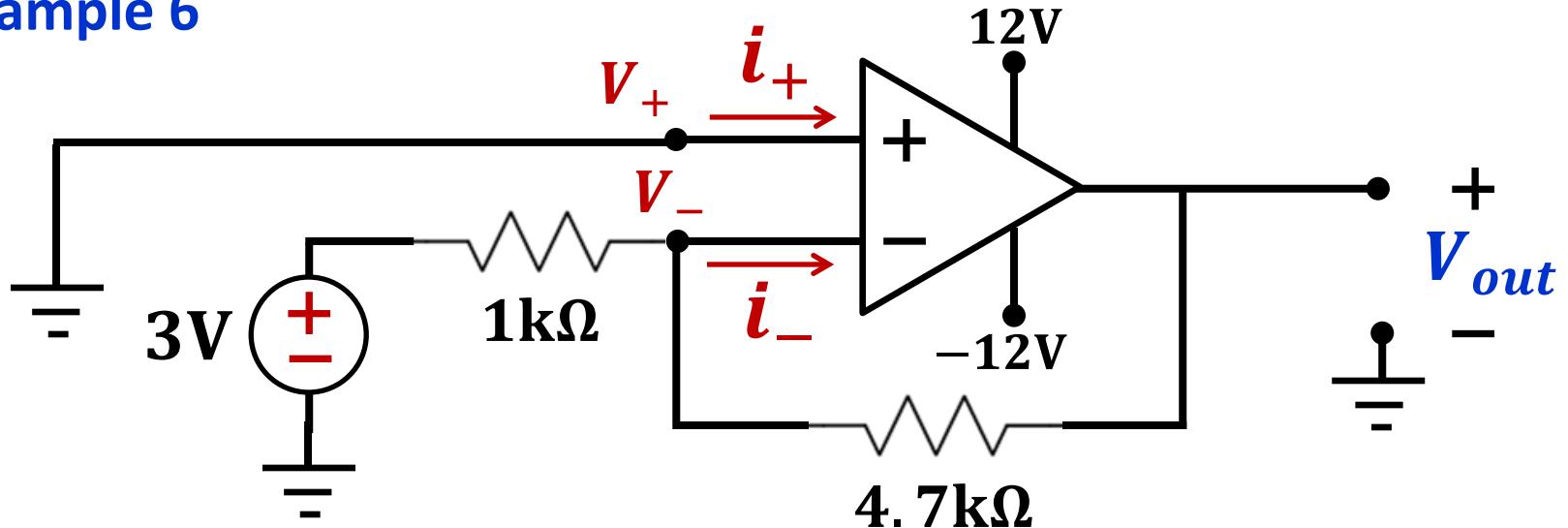


$$\frac{V_{out}}{V_S} = -\frac{R_F}{R_S}$$

Example 6

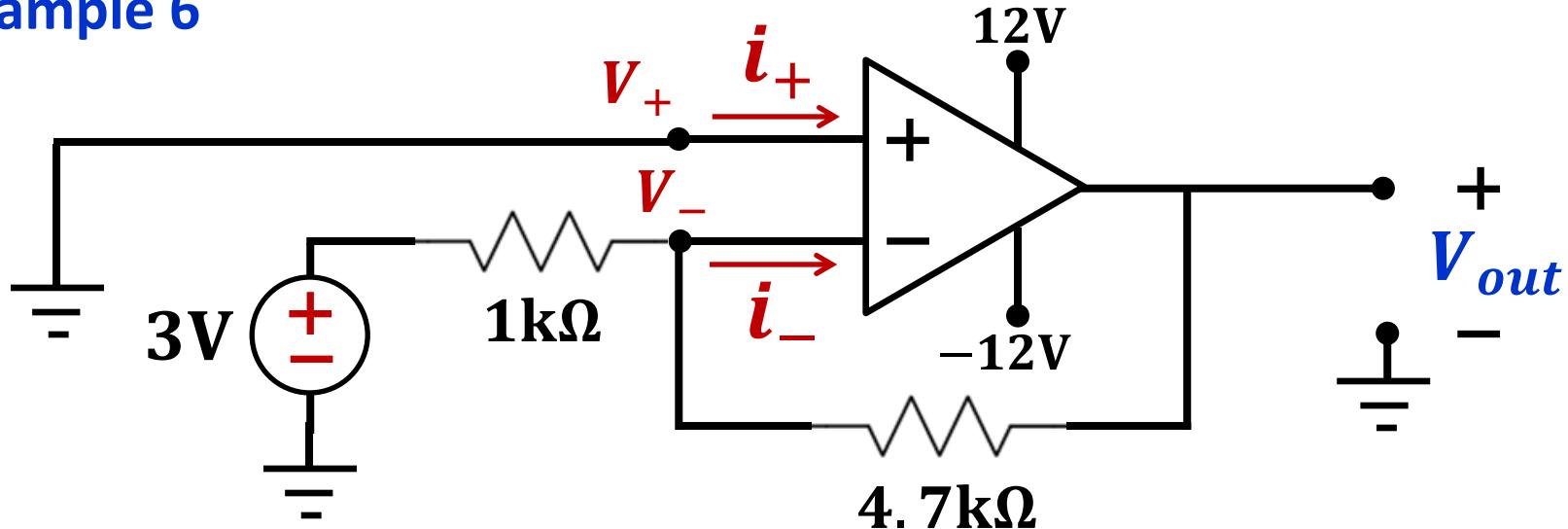

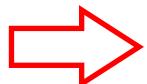
$$\frac{V_{out}}{V_s} = -\frac{R_F}{R_S}$$



$$V_{out} = -3 \frac{4.7\text{k}}{1\text{k}} = -14.1\text{V} < -V_b$$


Since $|V_{out}| > |V_{cc}|$, the output voltage saturates at -12V . 16

Example 7

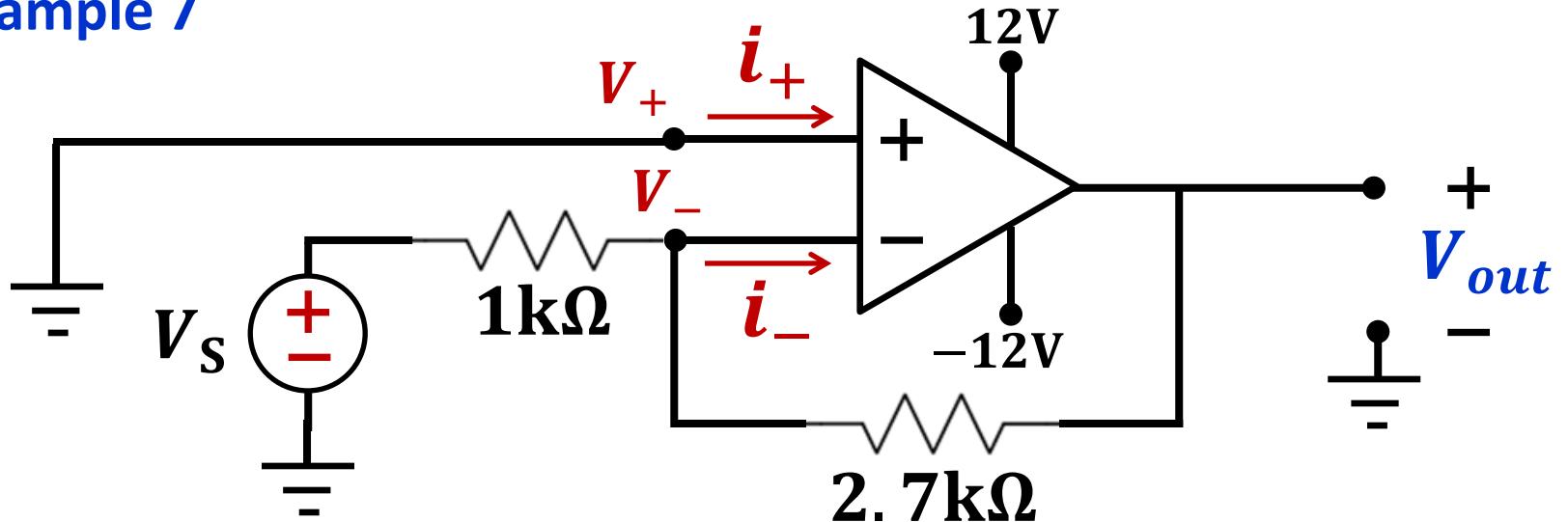

$$V_S = V_m \cos(\omega t) \quad V_m = 3\text{V}$$

Example 7

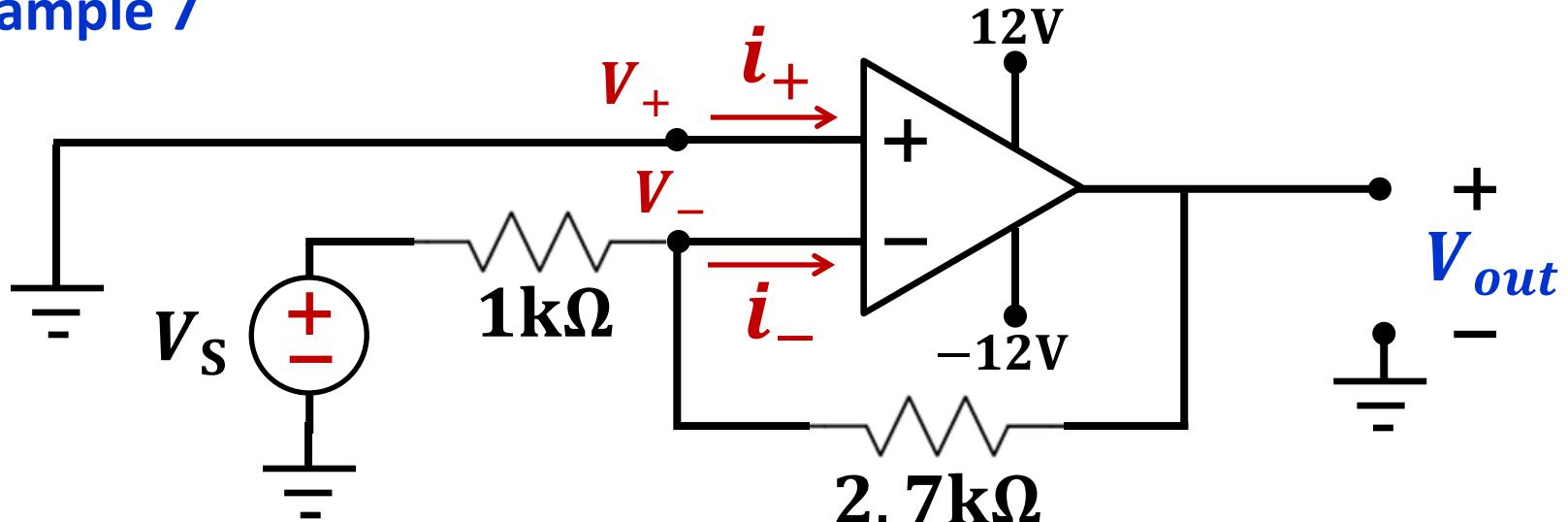


$$V_S = V_m \cos(\omega t) \quad V_m = 3\text{V}$$

$$\frac{V_{out}}{V_S} = -\frac{R_F}{R_S}$$

$$V_{out} = V_{mo} \cos(\omega t)$$


Example 7

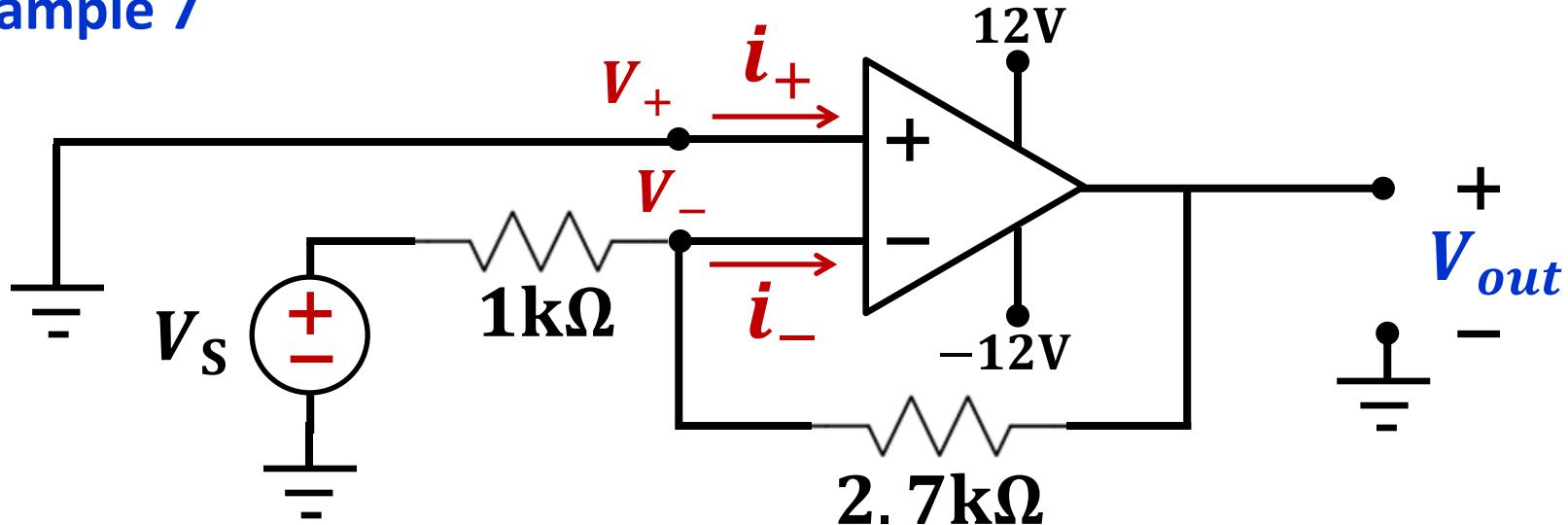

$$V_s = V_m \cos(\omega t) \quad V_m = 3\text{V}$$


$$\frac{V_{out}}{V_s} = -\frac{R_F}{R_S}$$

$$V_{out} = V_{mo} \cos(\omega t)$$

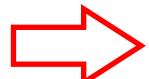


$$V_{mo} = -3 \frac{2.7\text{k}}{1\text{k}} = -8.1\text{V} > -V_b$$

Since $|V_{mo}| < |V_{cc}|$, the result obtained is valid.

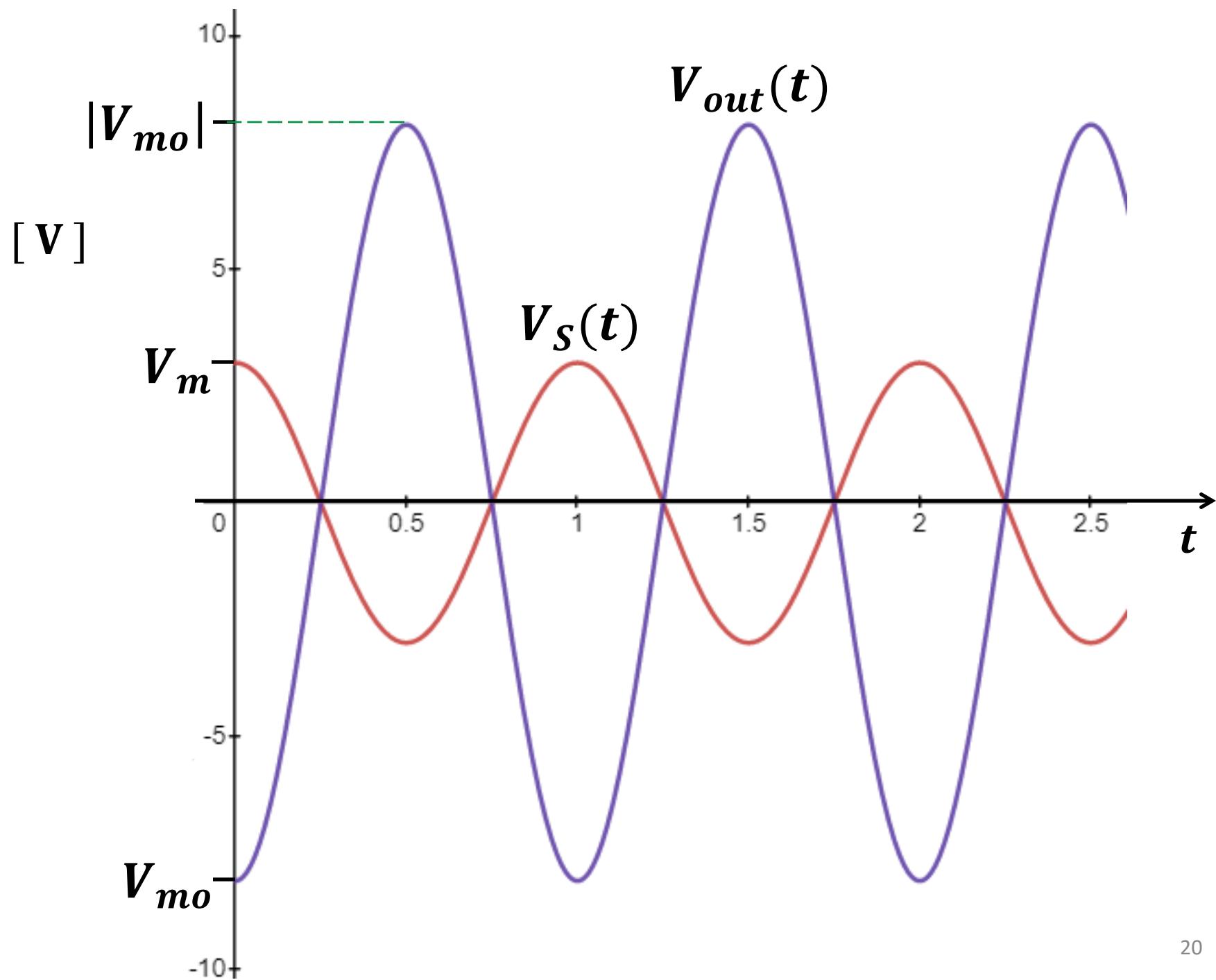


Example 8

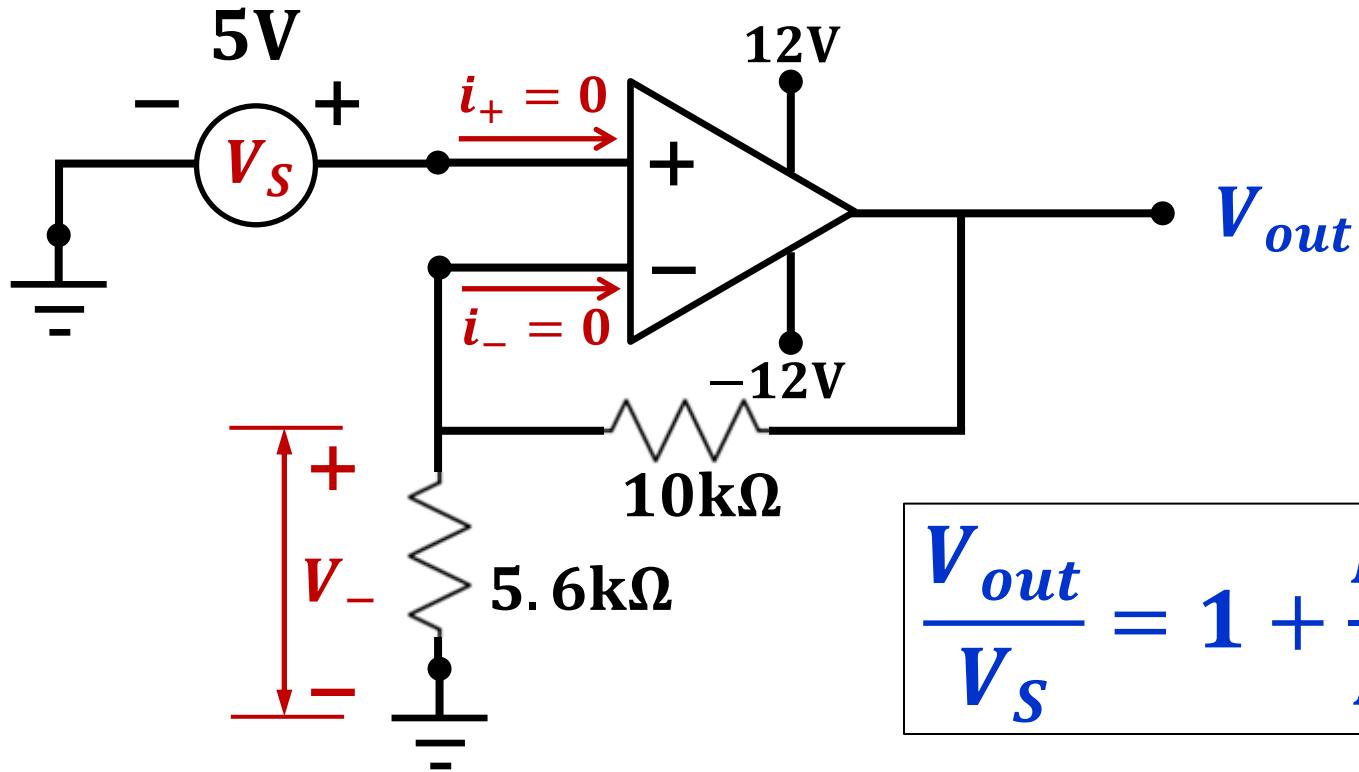

$$\frac{V_{out}}{V_S} = 1 + \frac{R_F}{R_S}$$

Example 8

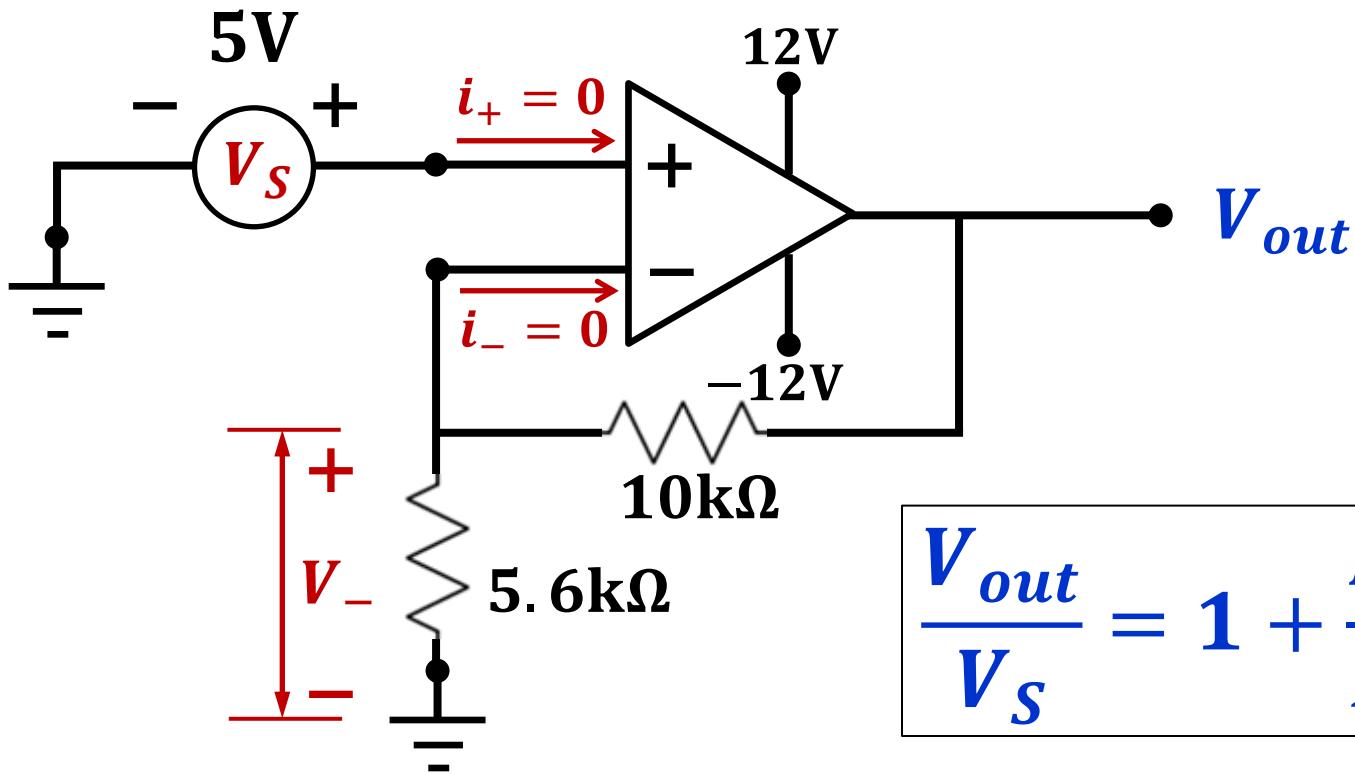


$$\frac{V_{out}}{V_S} = 1 + \frac{R_F}{R_S}$$


$$V_{out} = 5 \left(1 + \frac{10\text{k}}{5.6\text{k}} \right) = 13.93\text{V}$$

Since $|V_{out}| > |V_{CC}|$, the op-amp saturates at 12V . In Example 5, with the same resistors the inverting op-amp did not saturate.

Example 5 Again

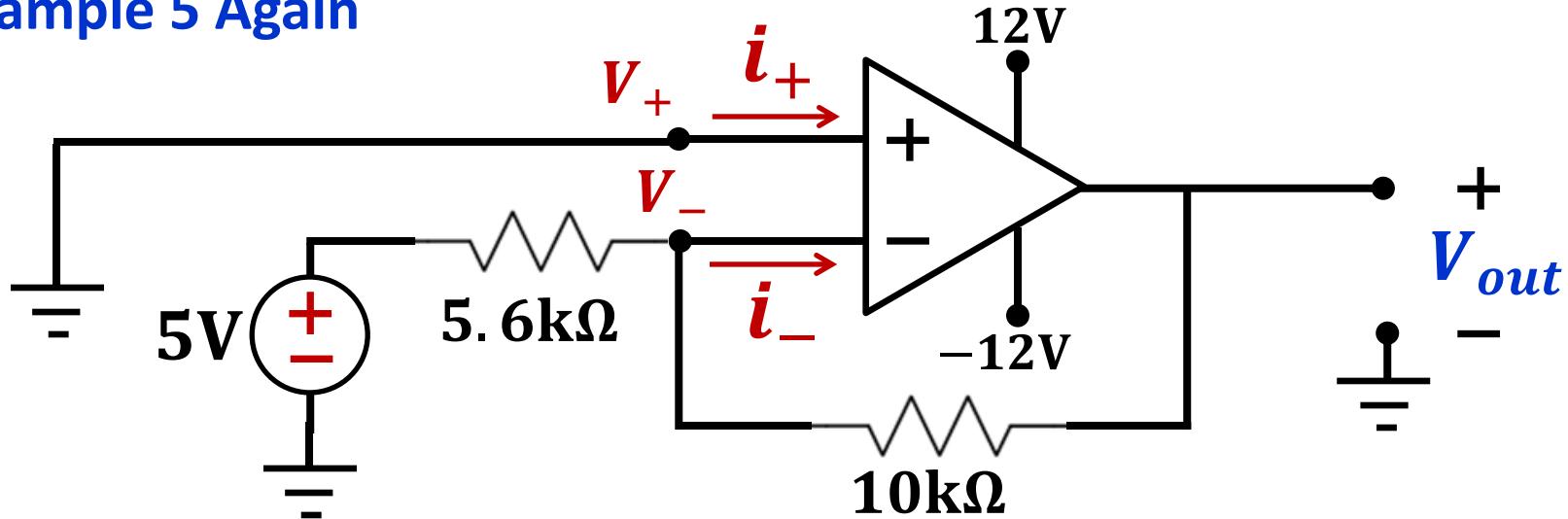
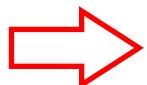
$$\frac{V_{out}}{V_S} = -\frac{R_F}{R_S}$$



$$V_{out} = -5 \frac{10k}{5.6k} = -8.93V$$

Since $|V_{out}| < |V_{CC}|$, the result obtained is valid.

We have seen earlier


The response of a passive filter is affected by the load connected directly to it. For example, consider a high-pass RC filter:

RC constant

$$\tau = R C$$


with load

$$\tau' = (R//R_L) C$$

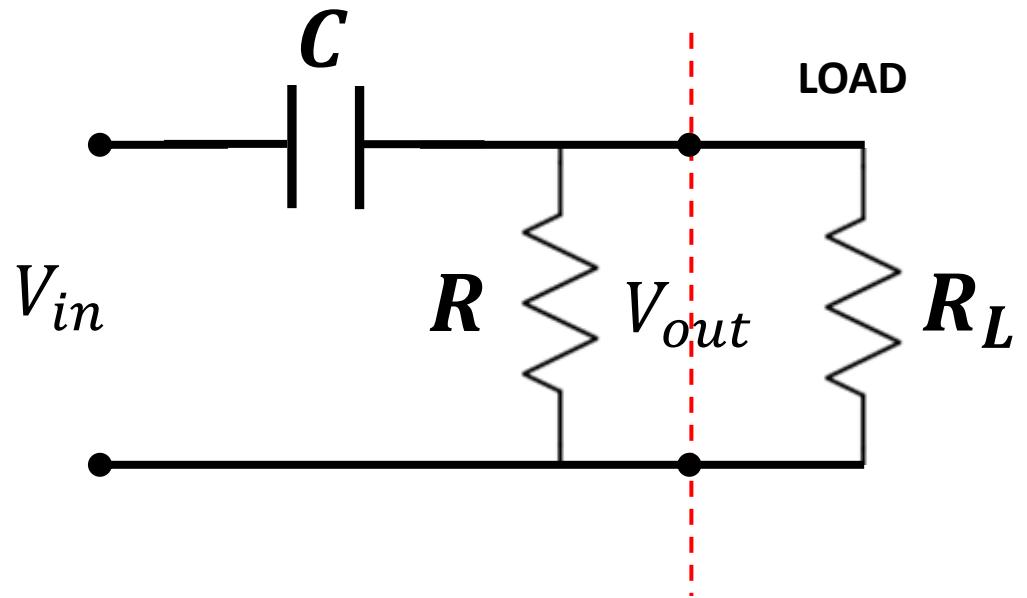

The parallel $R_{\text{eff}} = R//R_L$ yields an equivalent resistance lower than either R or R_L . In particular, if connected to a small resistor R_L , the resulting cutoff frequency $\omega'_C = (R_{\text{eff}}C)^{-1}$ may change considerably with respect to the original $\omega_C = (RC)^{-1}$.

Isolation of filter from load

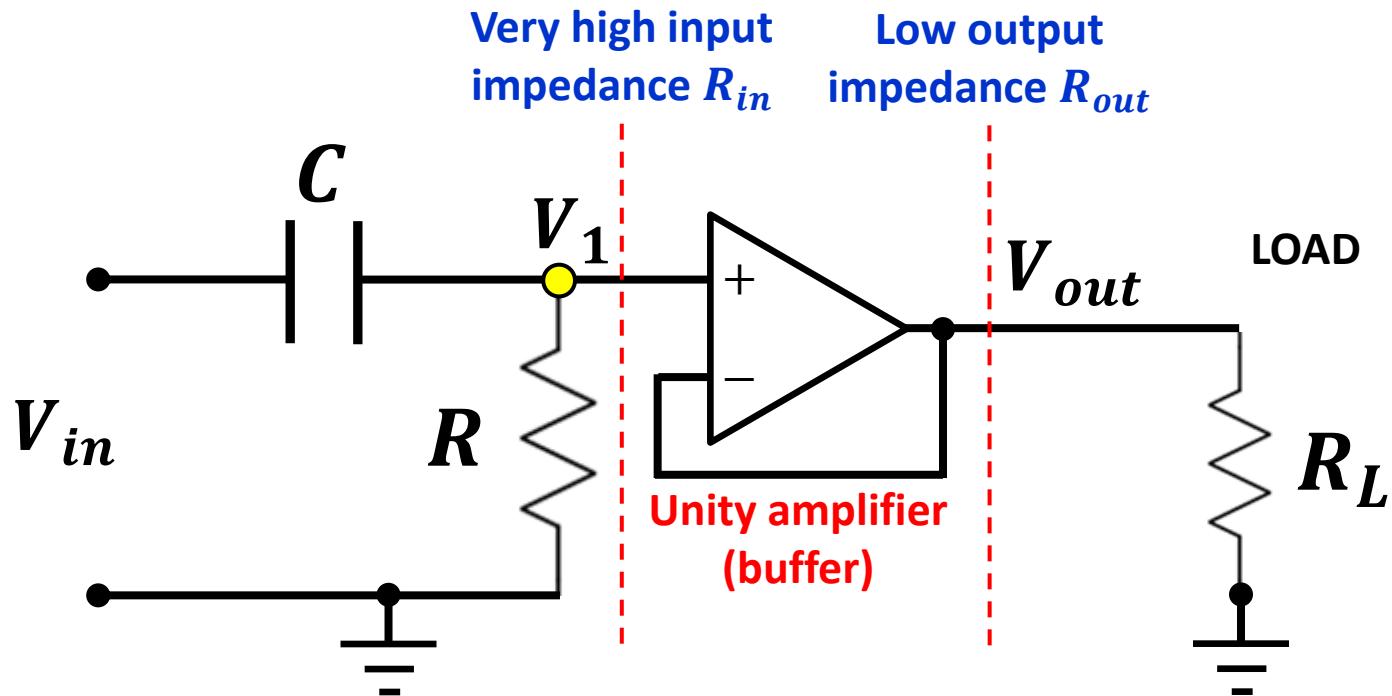


$$V_{out} = V_1$$

$$\tau' = (R//R_{in}) C \rightarrow (R//\infty) C = RC = \tau$$


Adder OP AMP

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

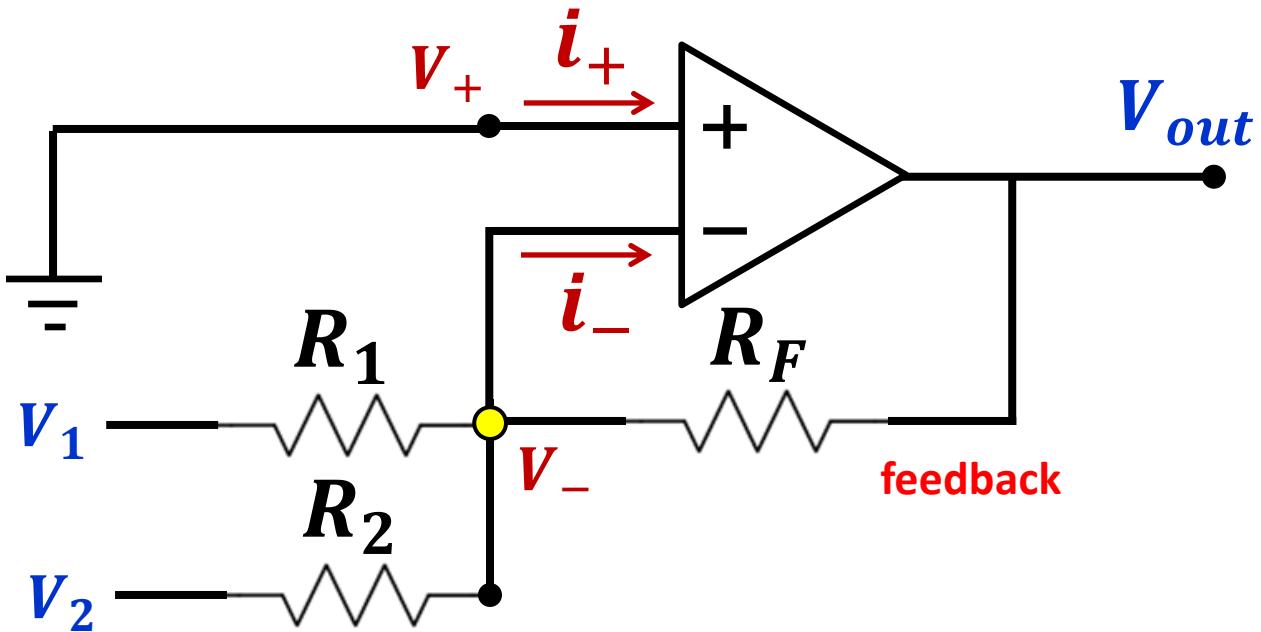

Adder OP AMP

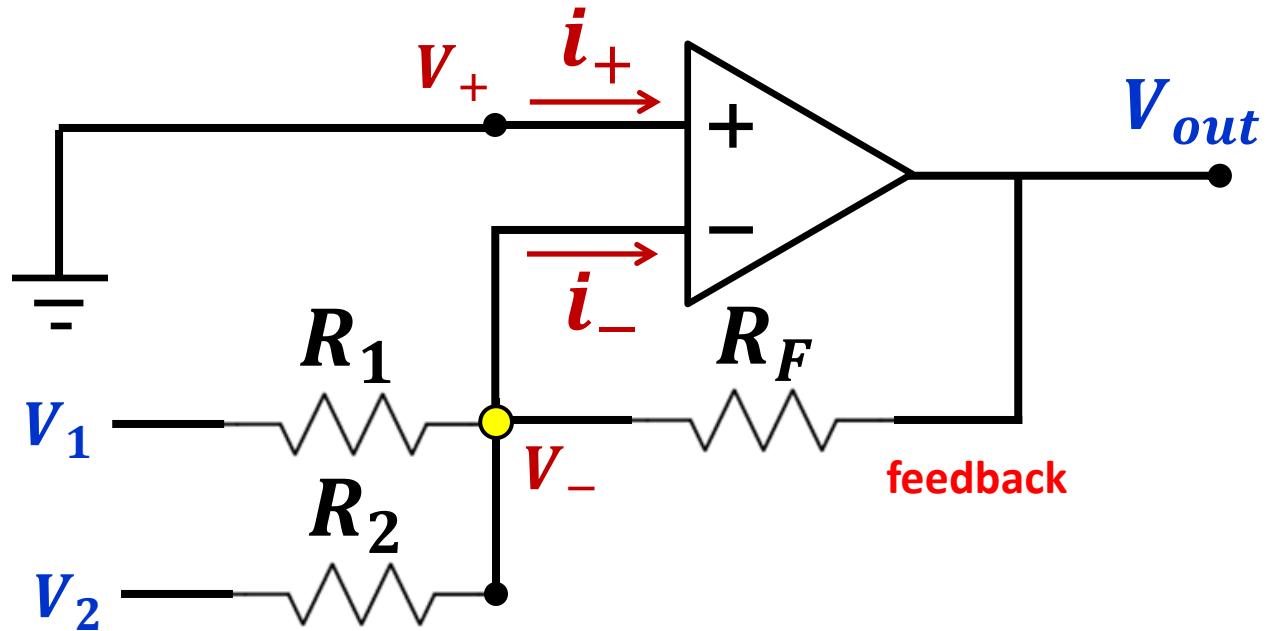

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

Node V_- ●


$$\frac{V_1 - V_-}{R_1} + \frac{V_2 - V_-}{R_2} + \frac{V_{out} - V_-}{R_F} = 0$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = -\frac{V_{out}}{R_F}$$

Adder OP AMP

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

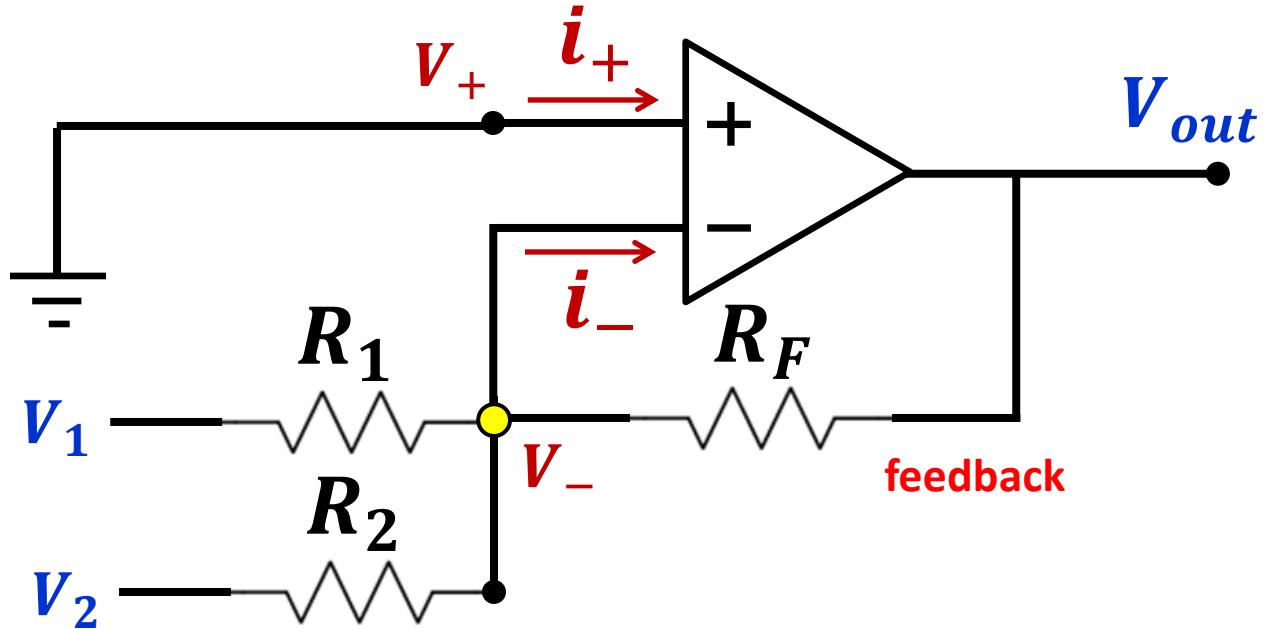

$$V_{out} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

If $R_1 = R_2 = R_F$

→ $V_{out} = -[V_1 + V_2]$


Adder OP AMP

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

For N inputs

If $R_k = R_F$
resistors all equal

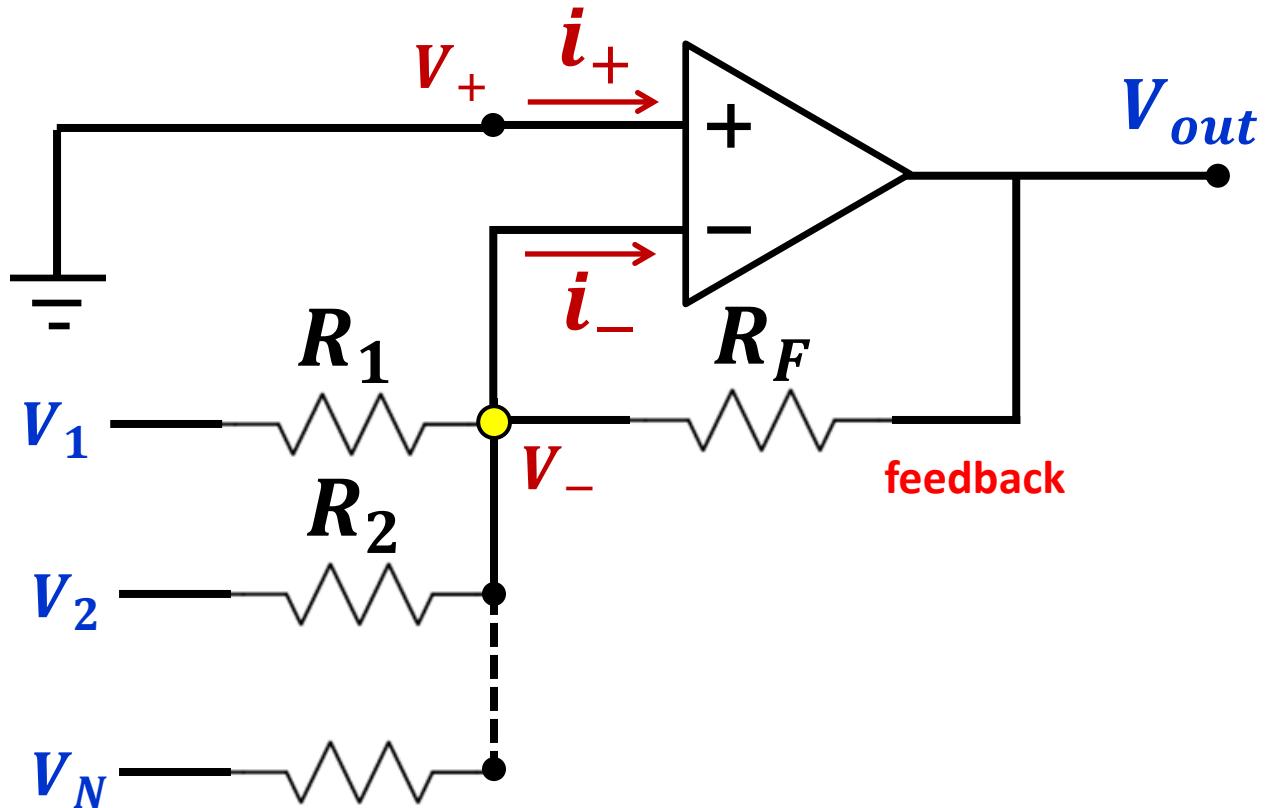


$$V_{out} = -R_F \sum_{k=1}^N \frac{V_k}{R_k}$$

→
$$V_{out} = - \sum_{k=1}^N V_k$$

Adder OP AMP

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

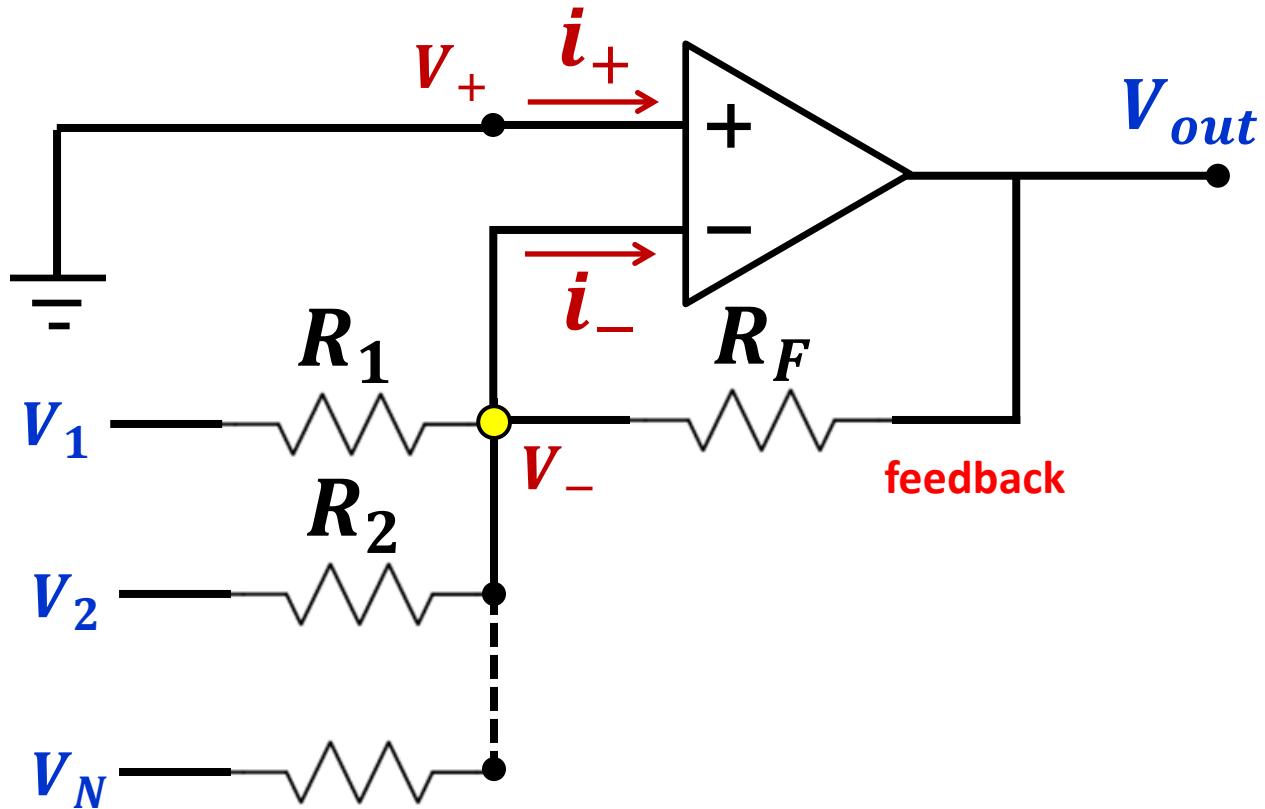

But one needs to verify that the output voltage does not exceed the rail bias

$$|V_{out}| \leq |V_{cc}|$$


Example – Four equal resistors in input

$$V_+ = V_- = 0$$

$$R = 1\text{k}\Omega$$

$$i_+ = i_- = 0$$

$$V_i \Big|_{\max} = 1\text{V}$$

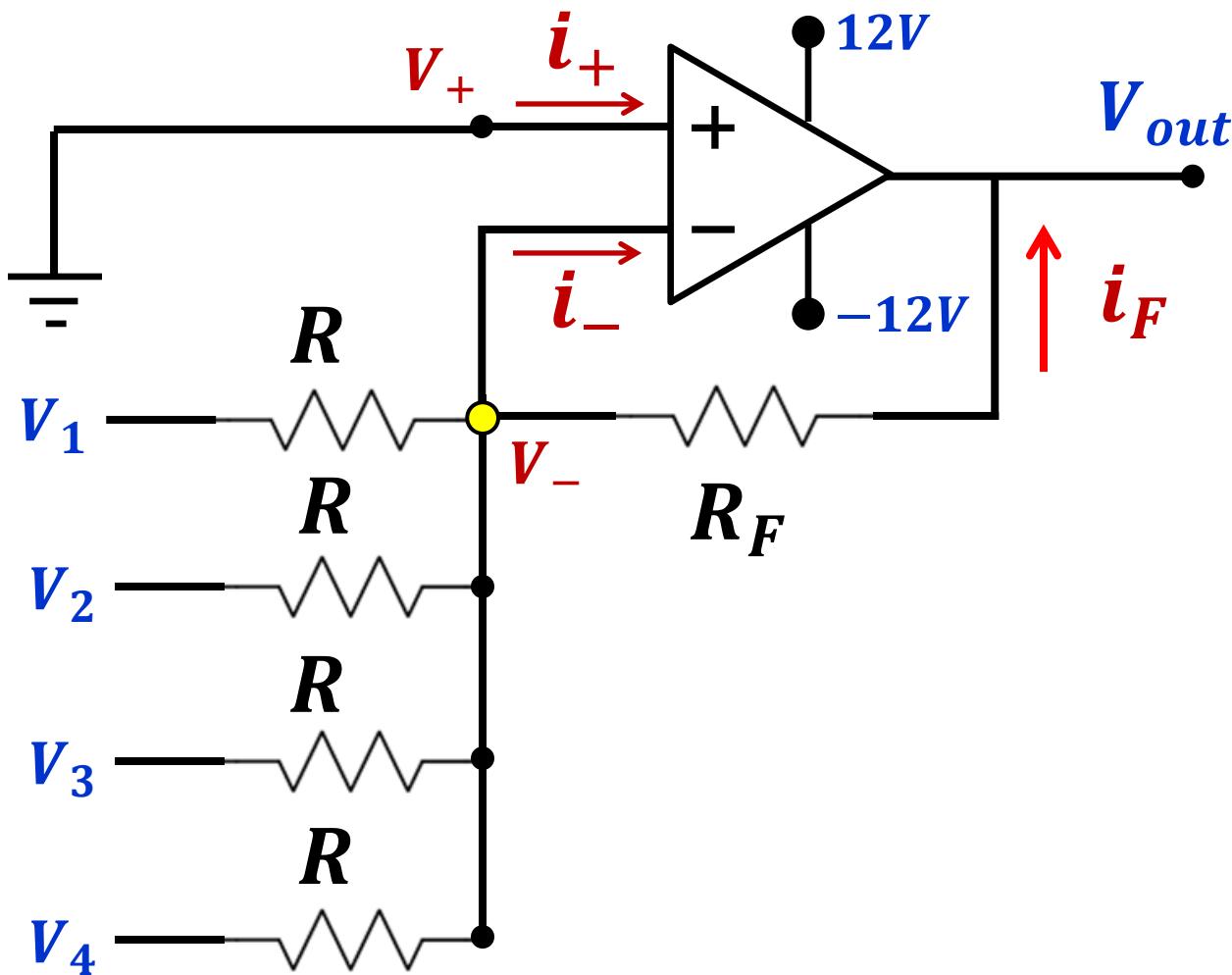


Example – Four equal resistors in input

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

$$R = 1\text{k}\Omega$$

$$V_i \Big|_{\max} = 1\text{V}$$

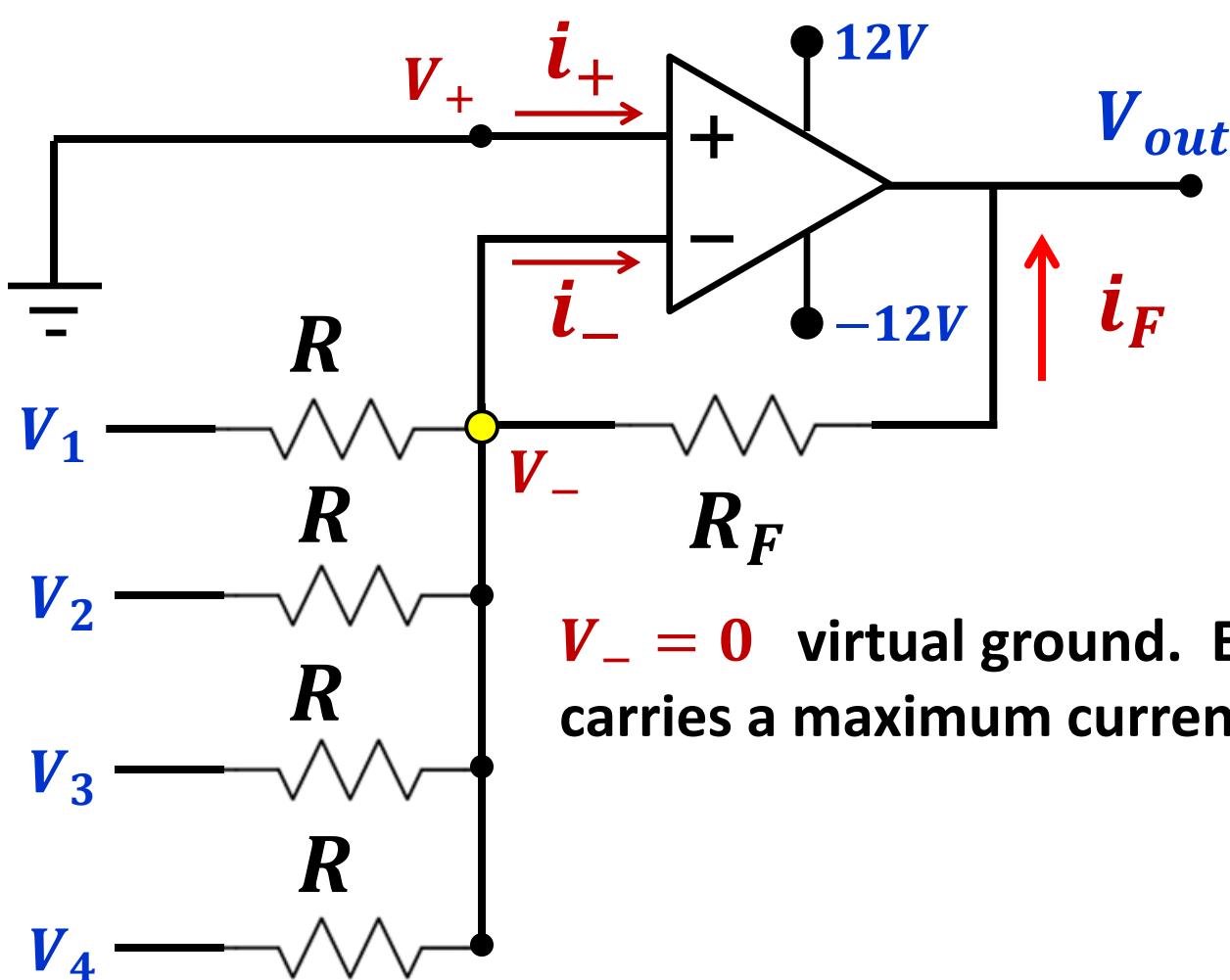


Example – Four equal resistors in input

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

$$R = 1\text{k}\Omega$$

$$V_i \Big|_{\max} = 1\text{V}$$

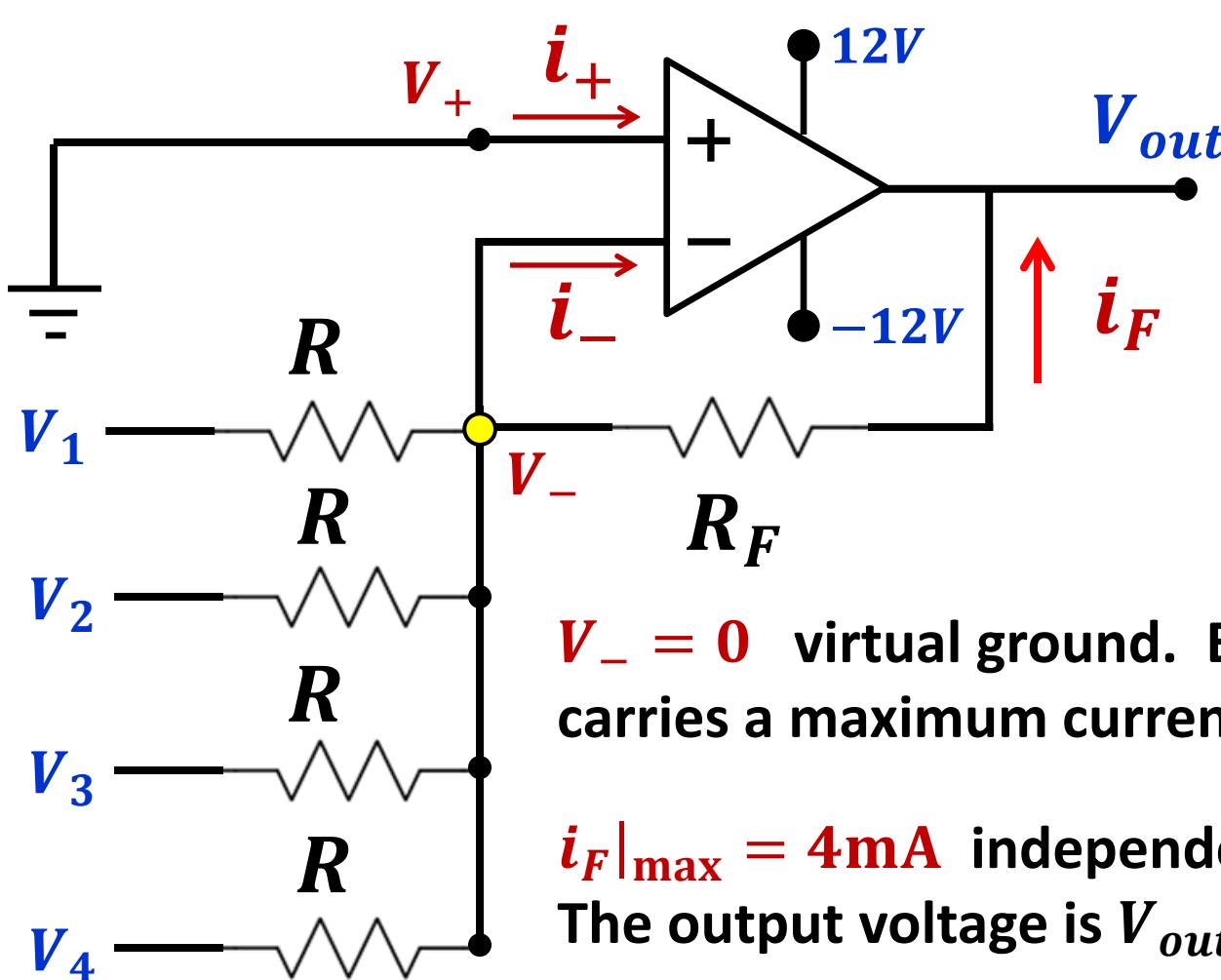

$V_- = 0$ virtual ground. Each input resistor carries a maximum current $i_k|_{\max} = 1\text{mA}$

$i_F|_{\max} = 4\text{mA}$ independent of R_F .

The output voltage is $V_{out} = R_F \times i_F|_{\max}$


Example – Equal input resistors

$$V_+ = V_- = 0$$

$$R = 1\text{k}\Omega$$

$$i_+ = i_- = 0$$

$$V_i \Big|_{\max} = 1\text{V}$$

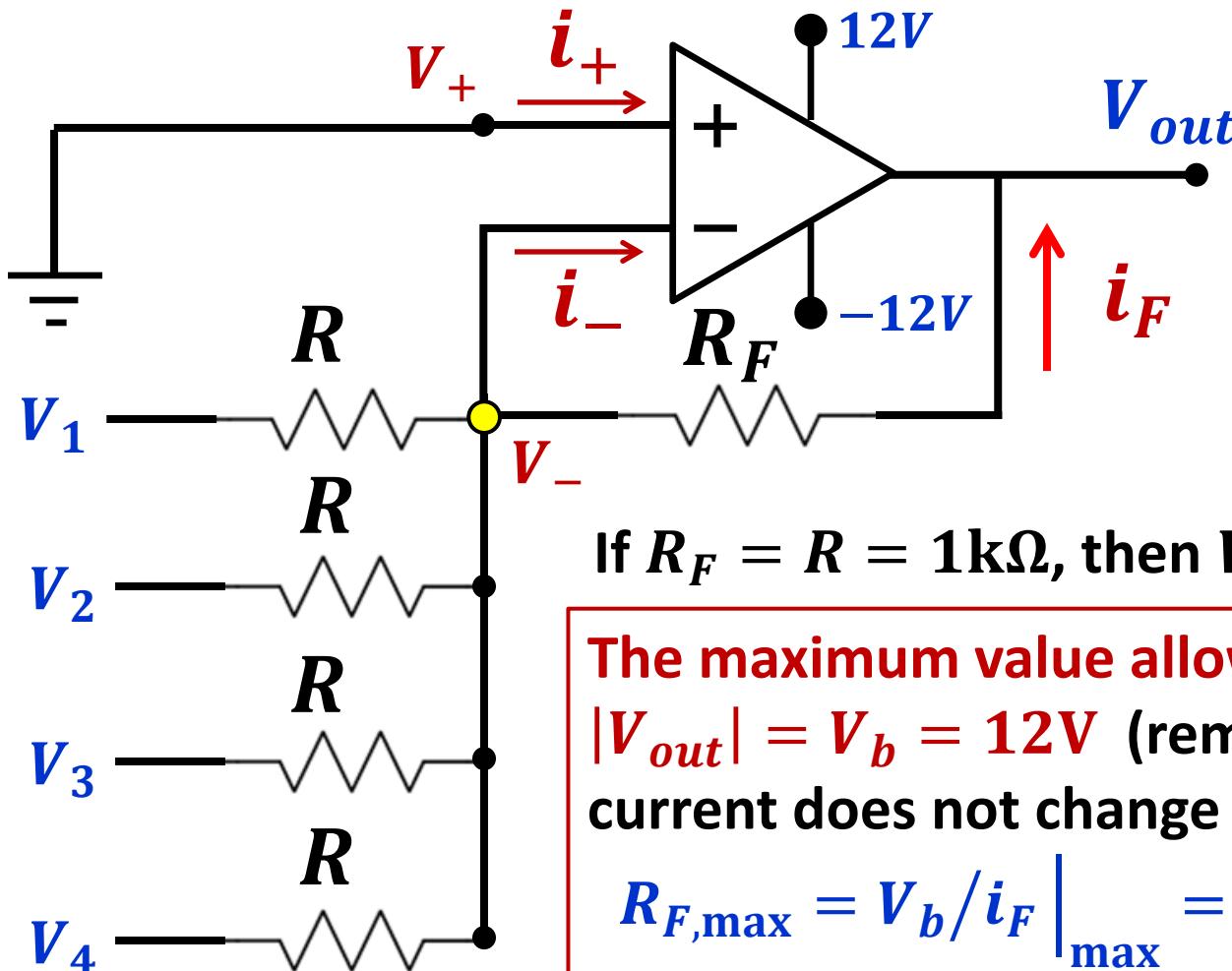


If $R_F = R = 1\text{k}\Omega$, then $V_{out} = 4\text{V}$ at most.

The maximum value allowed for R_F is when $|V_{out}| = V_b = 12\text{V}$ (remember, the input current does not change with R_F)


$$R_{F,\max} = V_b / i_F \Big|_{\max} = 12\text{V} / 4\text{mA} = 3\text{k}\Omega$$

Ideal Current Source

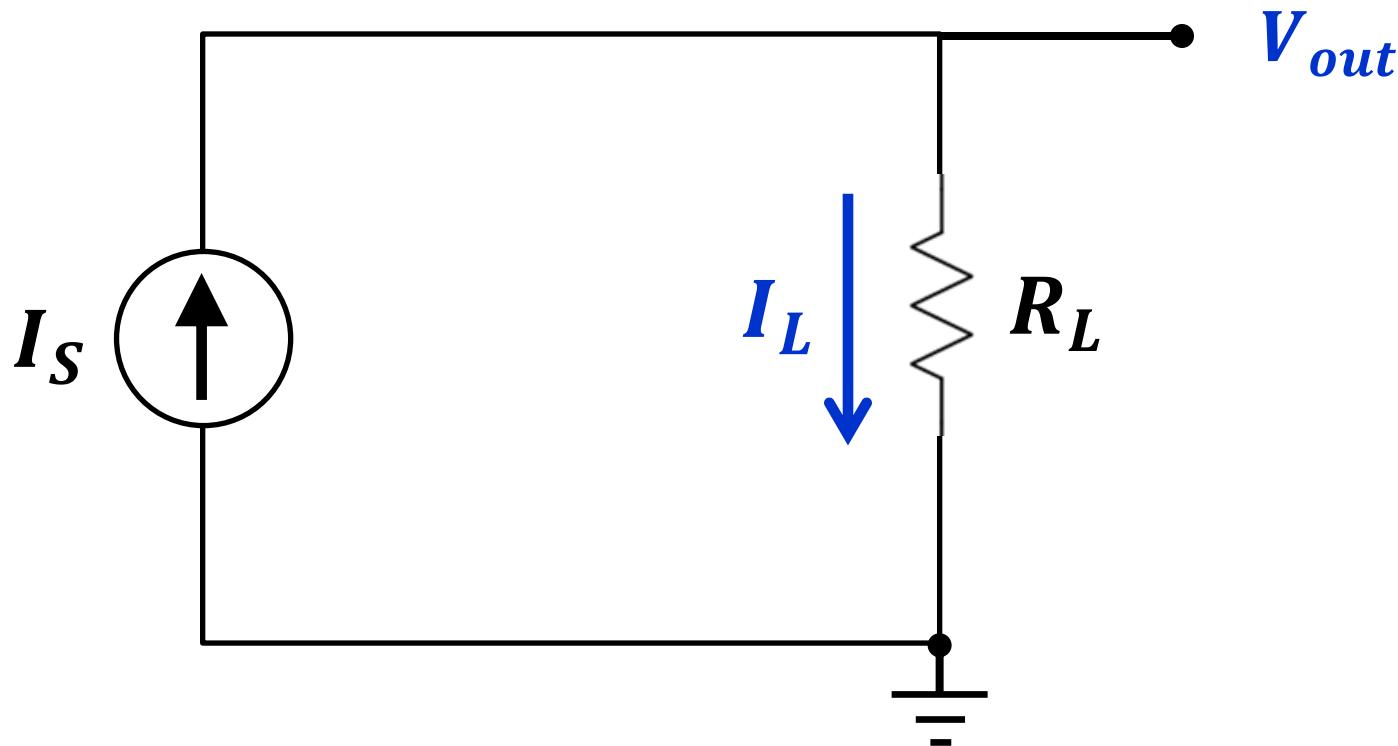


The current generated should be constant, independently of the load R_L

OP AMP Current Source

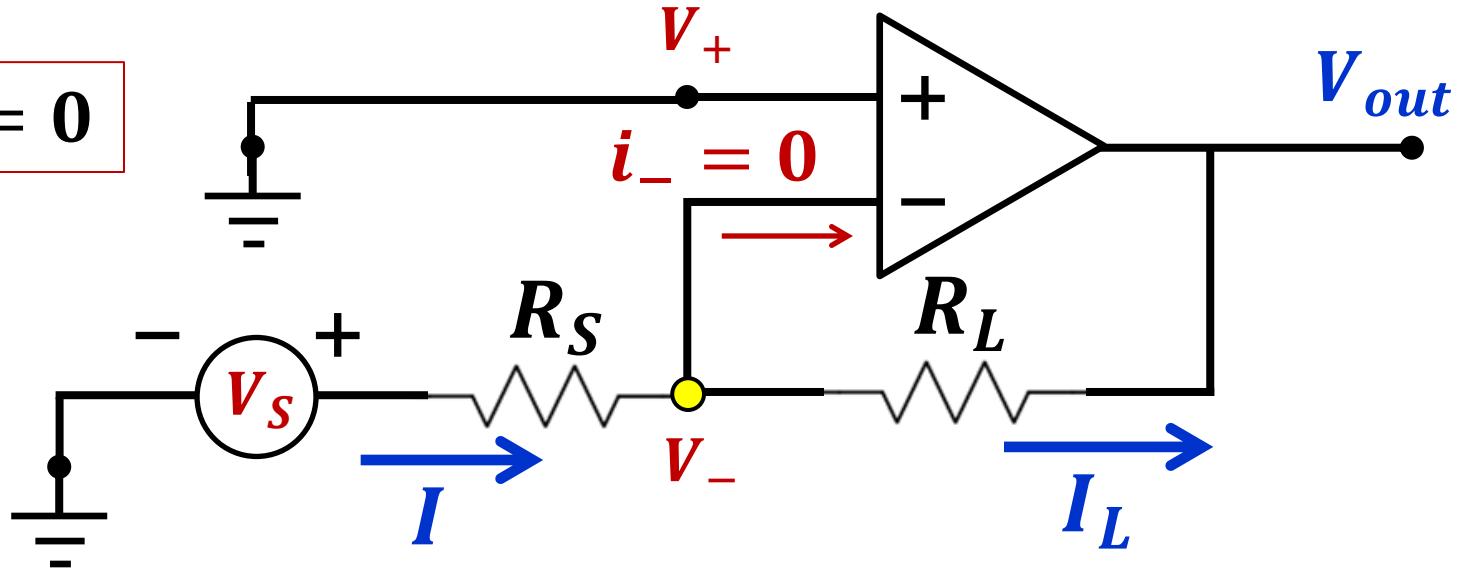

OP AMP Current Source

$$V_+ = V_- = 0$$

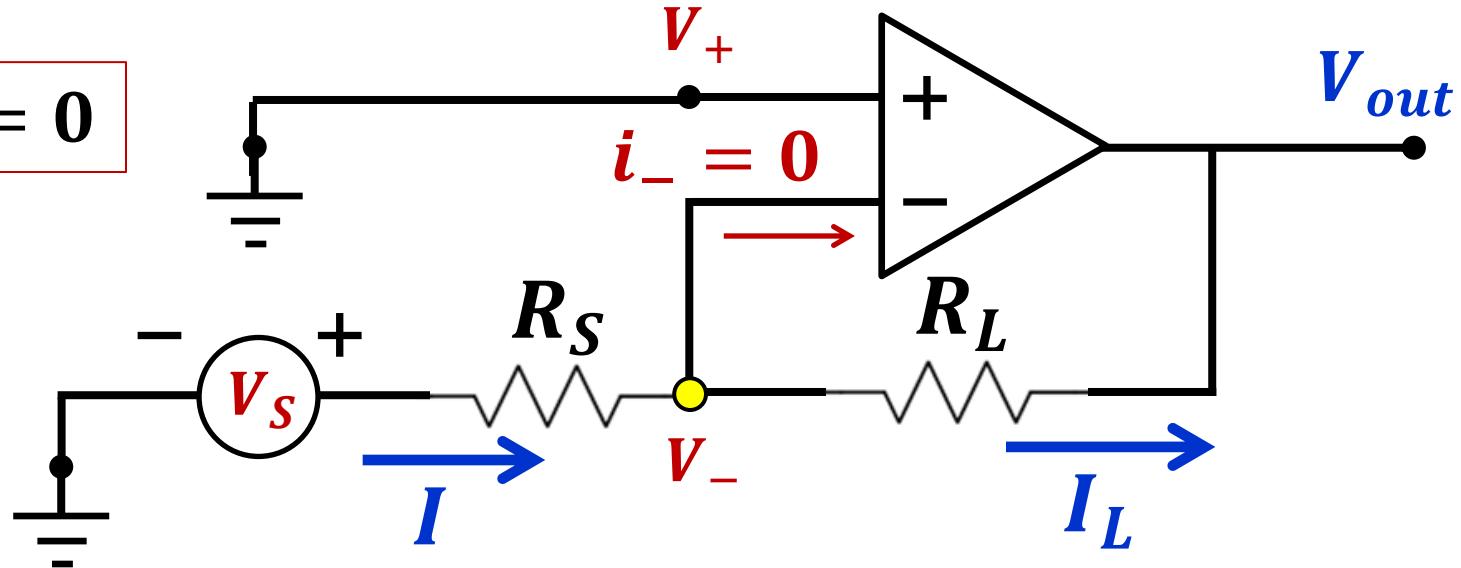


$$I = i_- + I_L = I_L$$

$$I_L = \frac{V_S - V_-}{R_S} = \frac{V_S}{R_S}$$

OP AMP Current Source

$$V_+ = V_- = 0$$

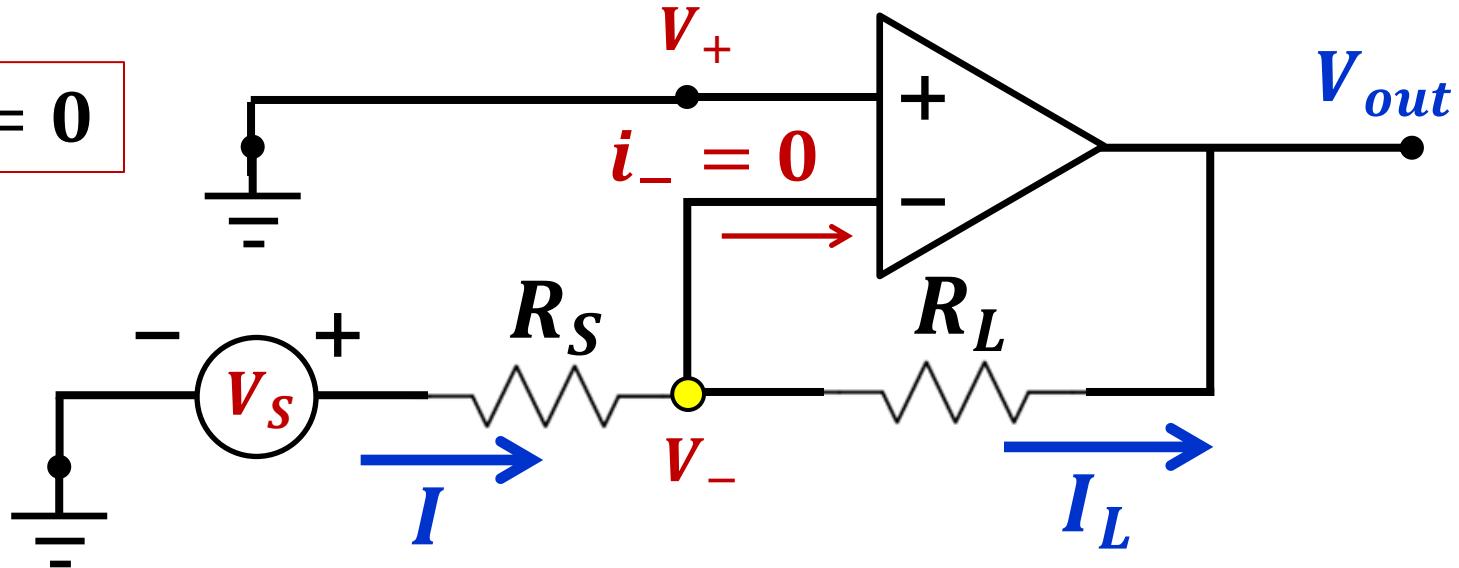

$$I = i_- + I_L = I_L$$


$$I_L = \frac{V_S - V_-}{R_S} = \frac{V_S}{R_S}$$

Example: $V_S = 1\text{V}$; $R_S = 1\text{k}\Omega$

$$\rightarrow I_L = \frac{1 - 0}{1\text{k}\Omega} = 1\text{mA}$$

Independent of R_L


Differential OP AMP

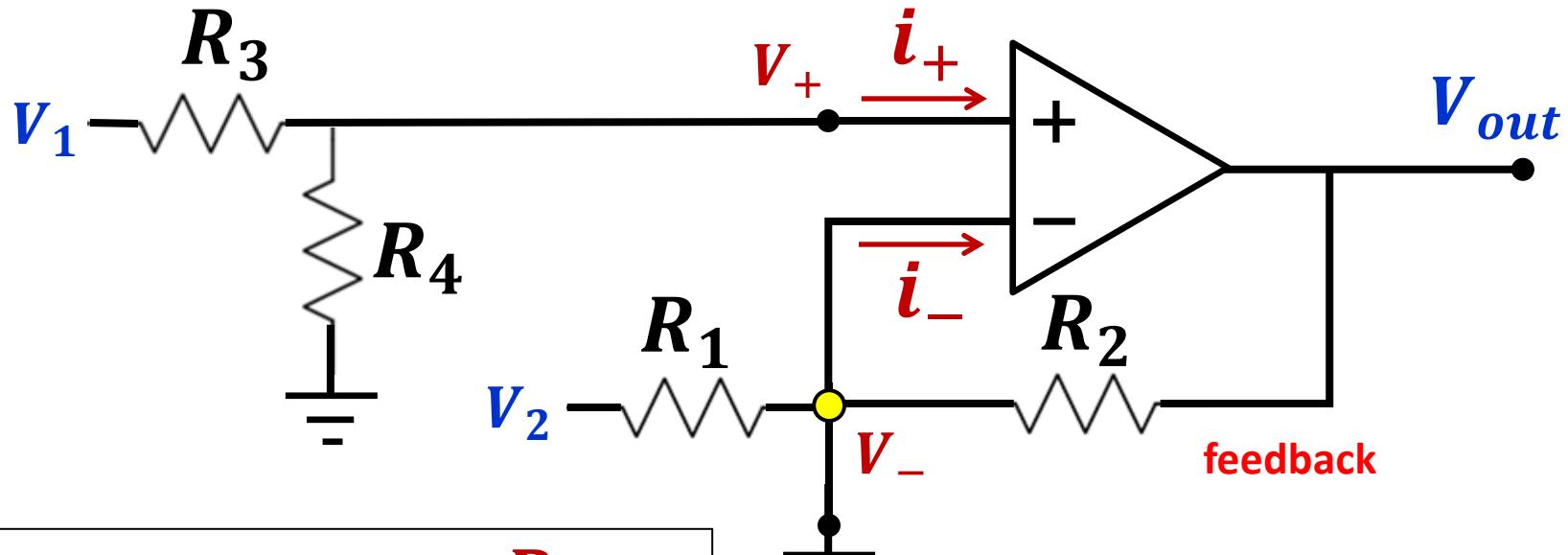

$$V_+ = V_- = V_1 \frac{R_4}{R_3 + R_4}$$

$$\begin{aligned}V_+ &= V_- \\i_+ &= i_- = 0\end{aligned}$$

Differential OP AMP

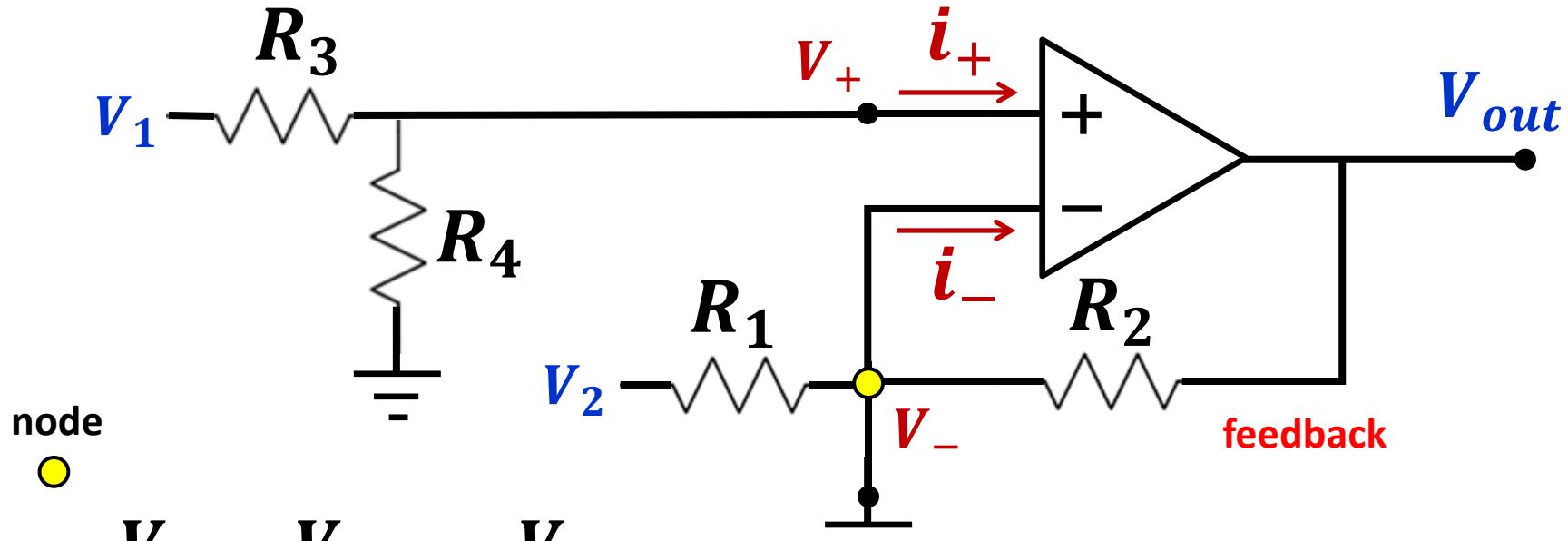


$$\frac{V_2 - V_-}{R_1} + \frac{V_{out} - V_-}{R_2} = 0$$

$$V_+ = V_-$$

$$i_+ = i_- = 0$$

$$\frac{V_{out}}{R_2} = -\frac{V_2 - V_-}{R_1} - \frac{-V_-}{R_2}$$

Differential OP AMP

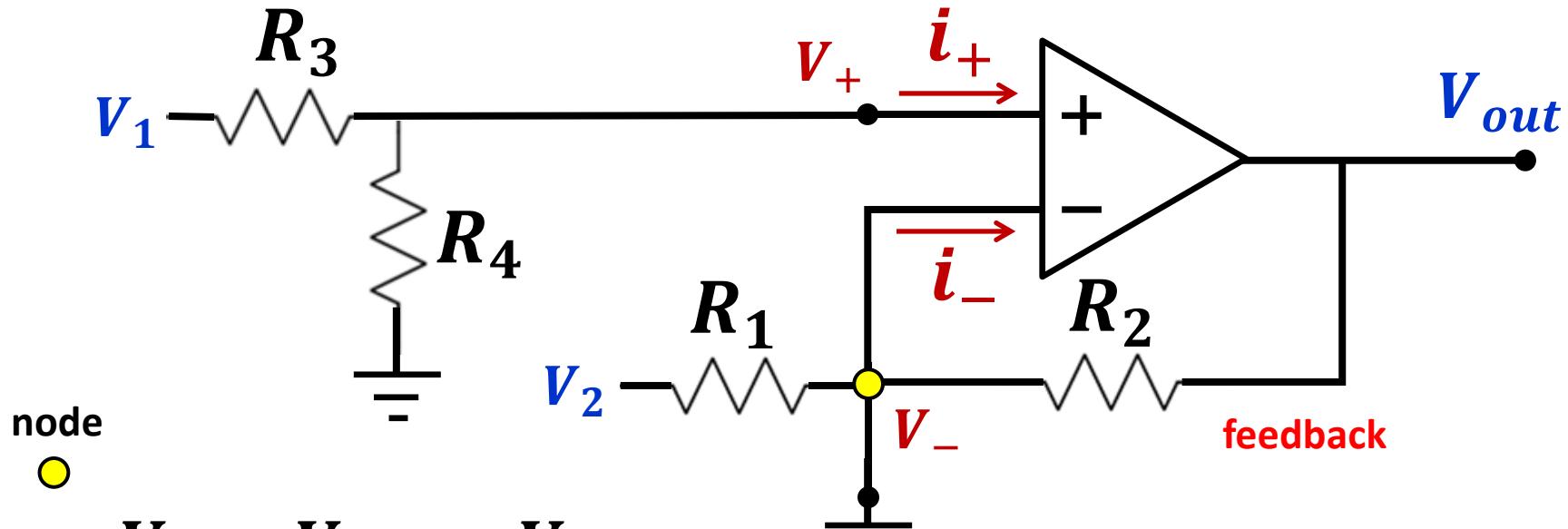


$$\frac{V_2 - V_-}{R_1} + \frac{V_{out} - V_-}{R_2} = 0$$

$$V_+ = V_-$$


$$i_+ = i_- = 0$$
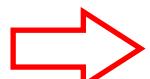
$$\frac{V_{out}}{R_2} = -\frac{V_2 - V_-}{R_1} - \frac{-V_-}{R_2}$$



$$V_{out} = \frac{R_2}{R_1} (V_- - V_2) + V_-$$


Differential OP AMP

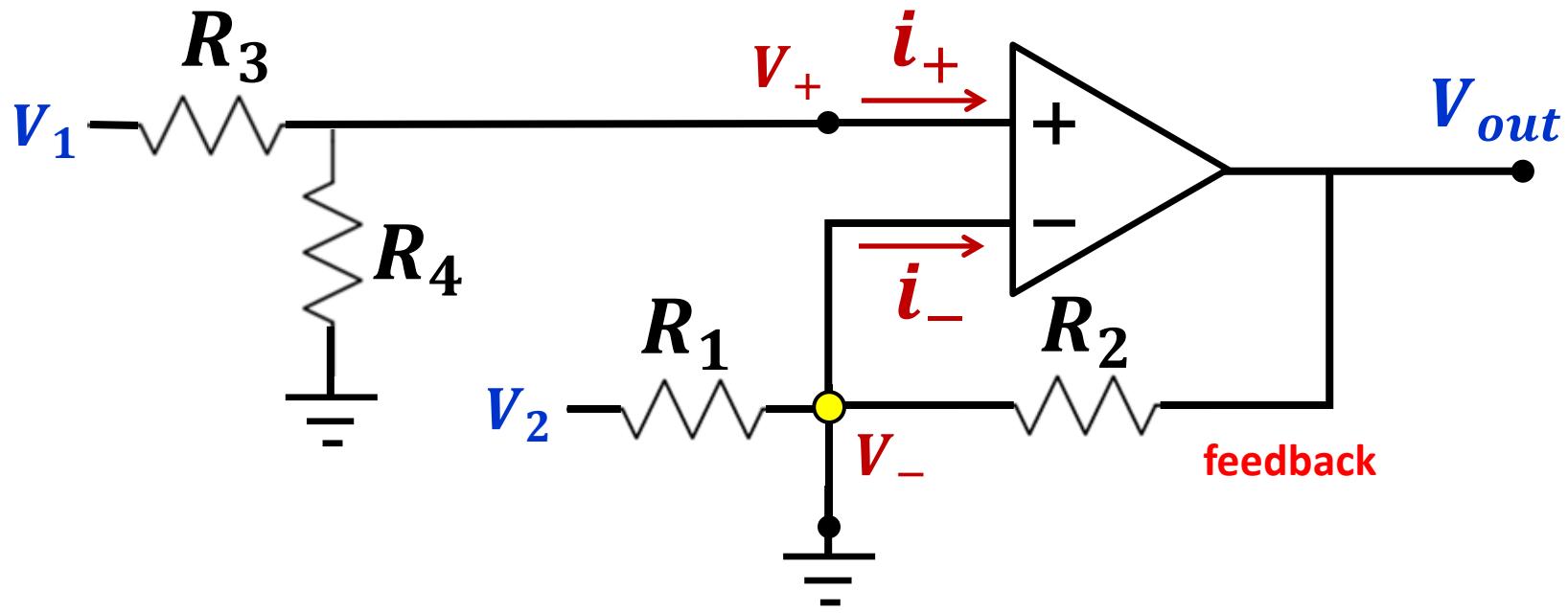

$$V_+ = V_- = V_1 \frac{R_4}{R_3 + R_4}$$

$$V_{out} = \frac{R_2}{R_1} (V_- - V_2) + V_-$$

Differential OP AMP

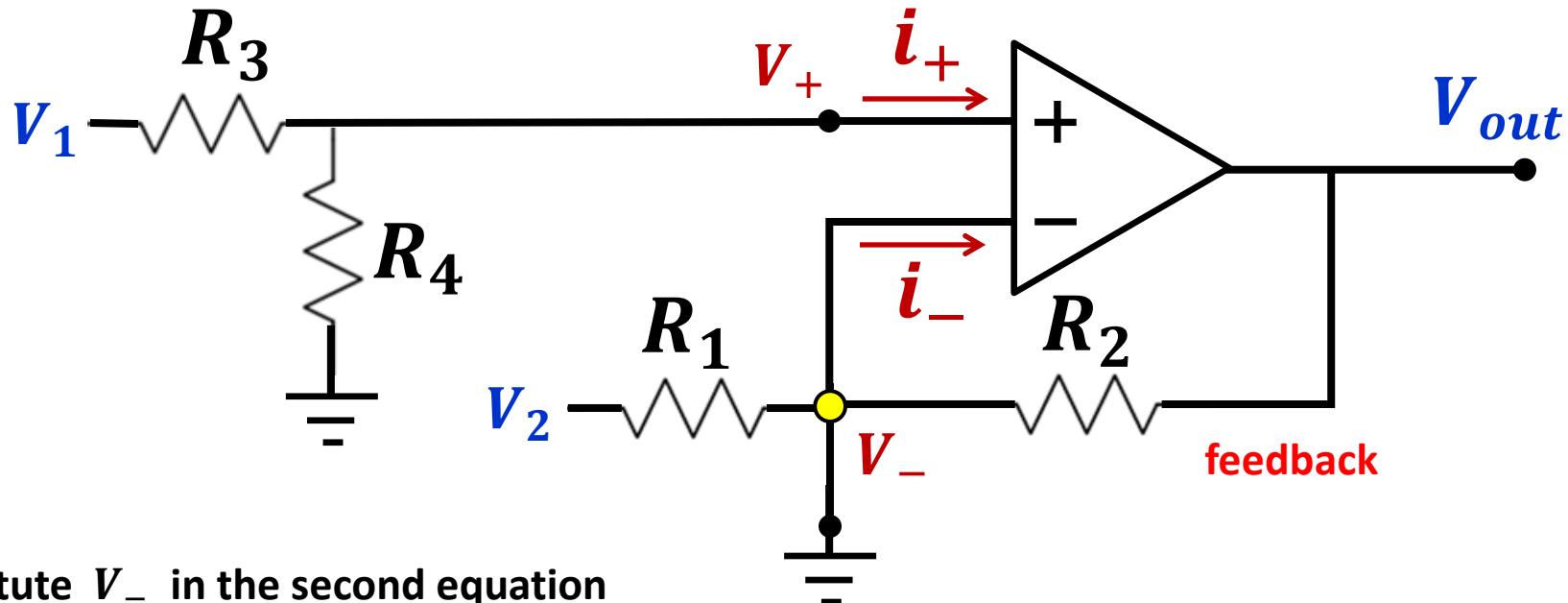


Substitute V_- in the second equation

$$V_+ = V_- = V_1 \frac{R_4}{R_3 + R_4}$$

$$V_{out} = \frac{R_2}{R_1} (V_- - V_2) + V_-$$

$$V_{out} = \frac{R_2}{R_1} \left(V_1 \frac{R_4}{R_3 + R_4} - V_2 \right) + V_1 \frac{R_4}{R_3 + R_4}$$


Differential OP AMP

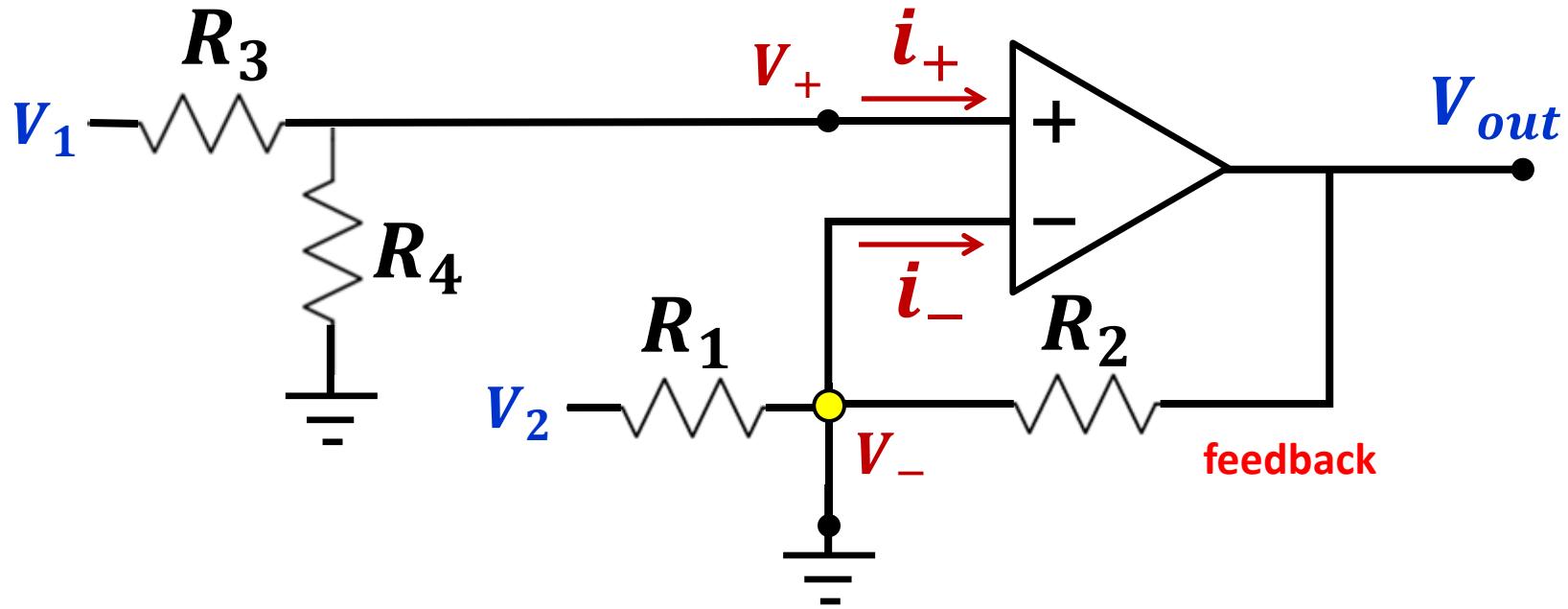


$$V_{out} = \frac{R_2}{R_1} \left(V_1 \frac{R_4}{R_3 + R_4} - V_2 \right) + V_1 \frac{R_4}{R_3 + R_4}$$

$$V_{out} = V_1 \frac{R_4}{R_3 + R_4} \left(\frac{R_2}{R_1} + 1 \right) - \frac{R_2}{R_1} V_2$$

Differential OP AMP

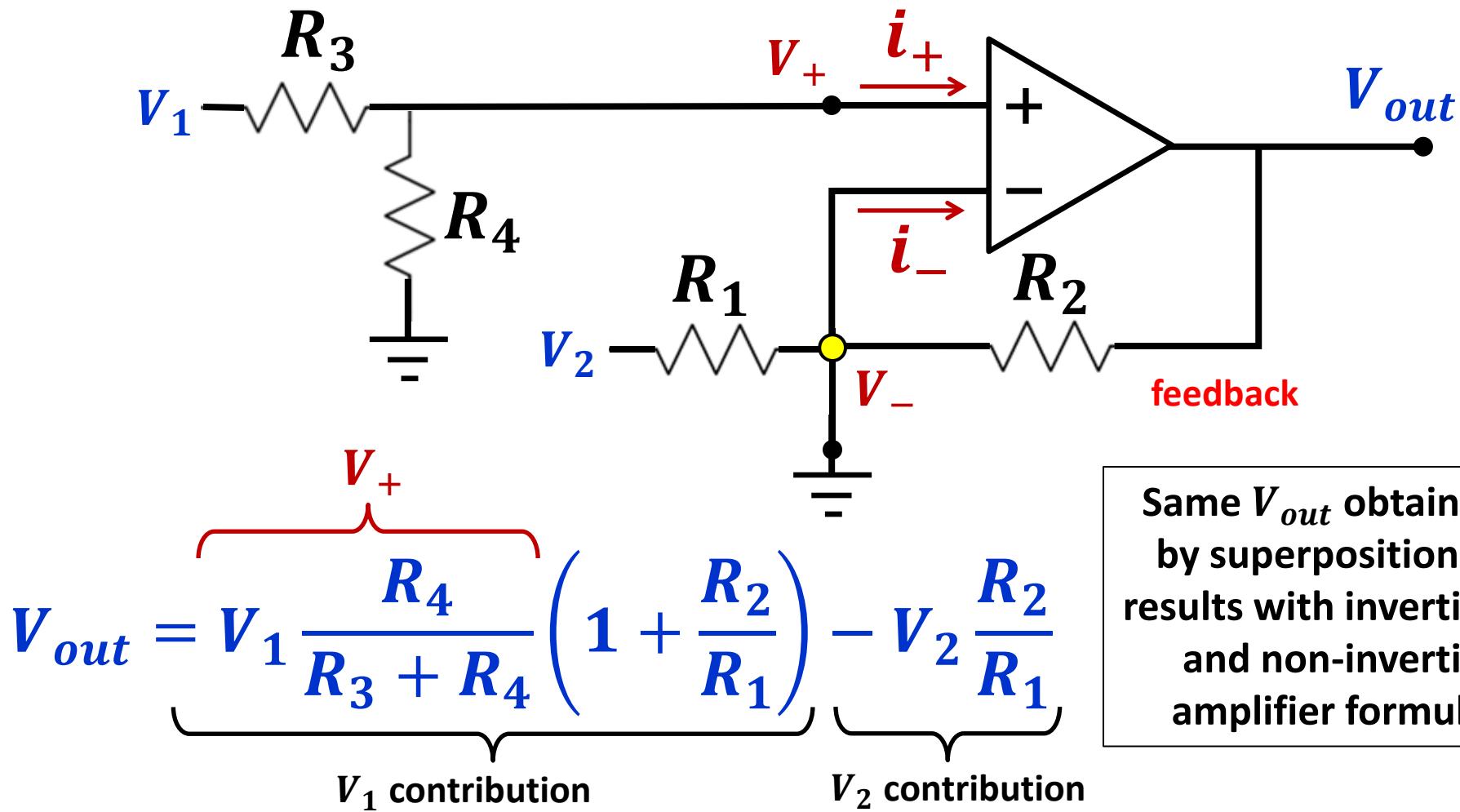


If $R_1 = R_2 = R_3 = R_4 = R$

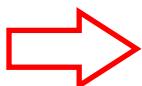

$$V_{out} = [V_1 - V_2]$$

Differential OP AMP

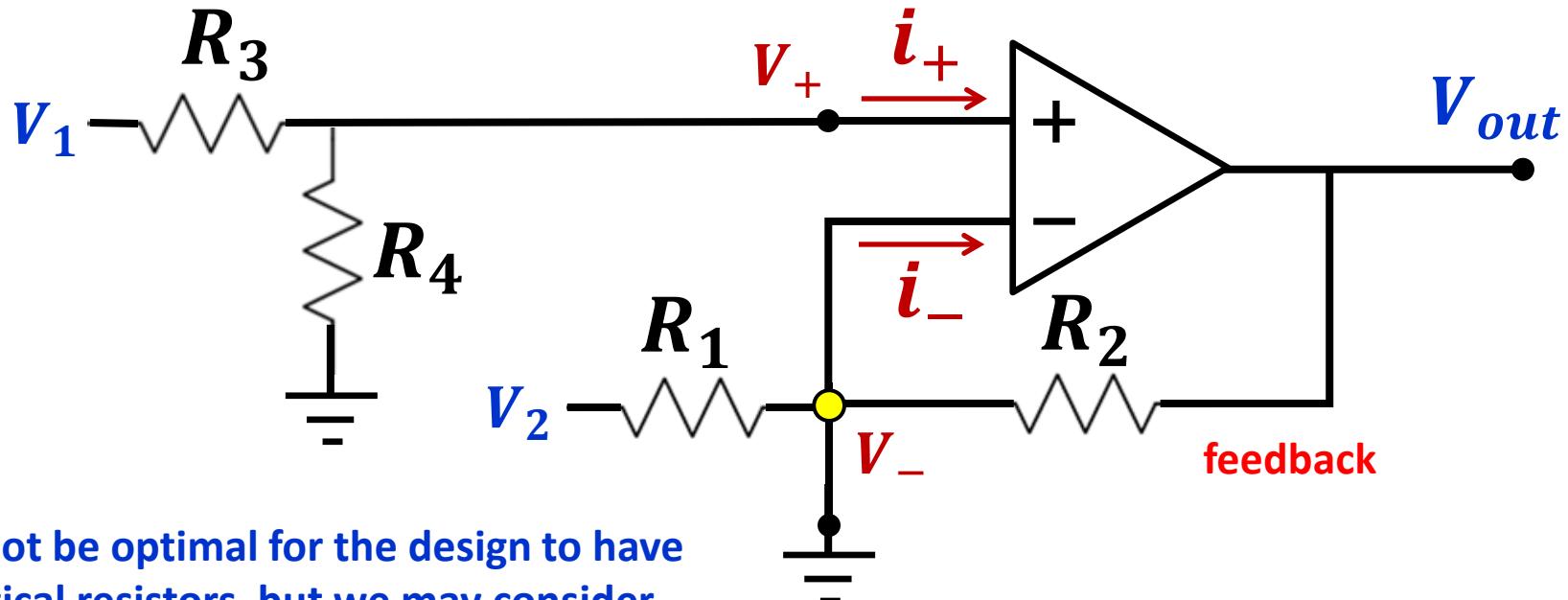

It may not be optimal for the design to have all identical resistors, but we may consider pairs of resistors with identical ratio

$$\text{If: } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$V_0 = \frac{R_4}{R_3 + R_4} \left(\frac{R_2}{R_1} + 1 \right) V_1 - \frac{R_2}{R_1} V_2$$

$$V_0 = \frac{R_4}{R_3 + R_4} \left(\frac{R_4 + R_3}{R_3} \right) V_1 - \frac{R_2}{R_1} V_2$$




$$V_0 = \frac{R_2}{R_1} (V_1 - V_2)$$

OP AMP Integrator

$$V_+ = V_- = 0$$


$$I = i_C$$

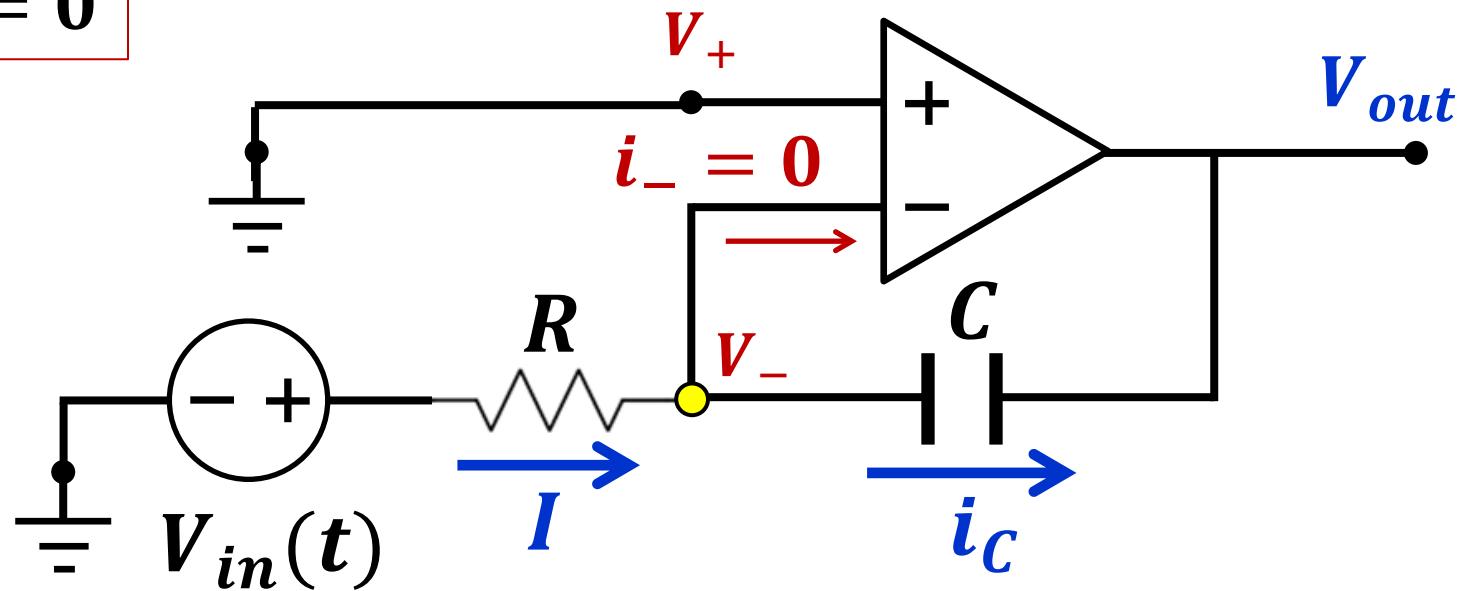

OP AMP Integrator

$$V_+ = V_- = 0$$

$$I = i_C$$

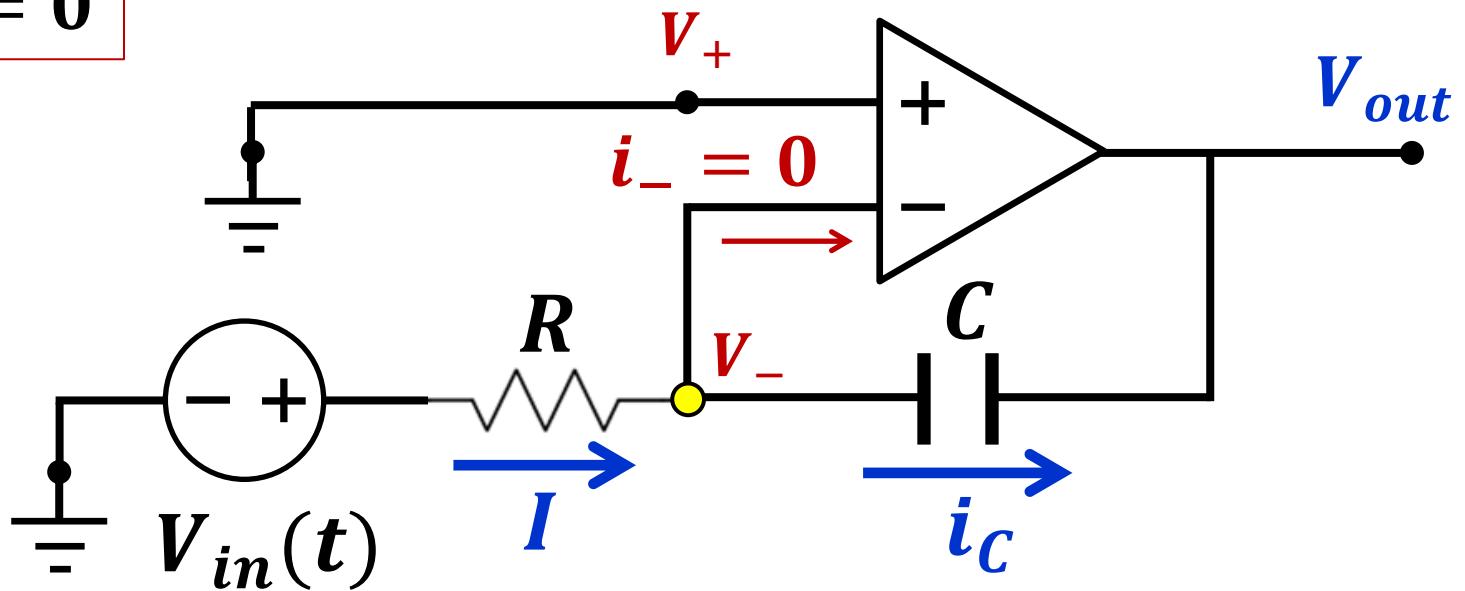


$$V_{out}(t) = -\frac{1}{C} \int_0^t i_C dt + V_{out}(0)$$

$$i_C = \frac{V_{in}(t)}{R}$$

OP AMP Integrator


$$V_+ = V_- = 0$$

$$I = i_C$$

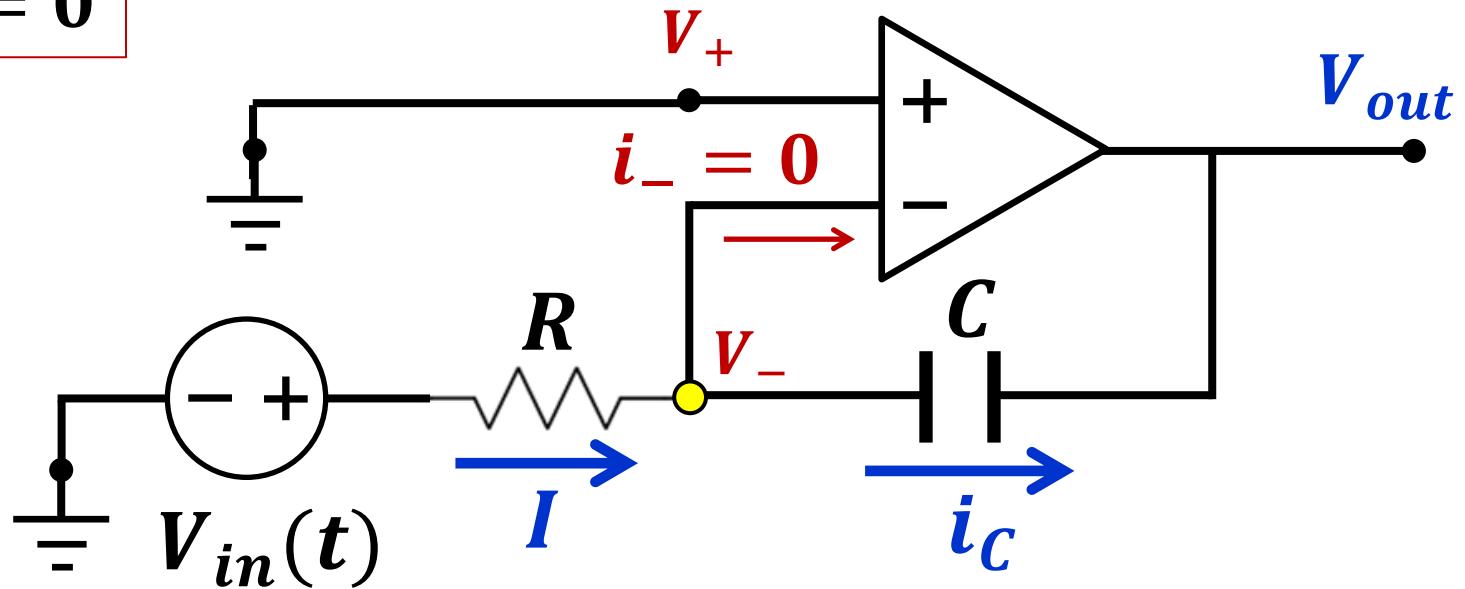


$$V_{out}(t) = -\frac{1}{C} \int_0^t i_C dt + V_{out}(0)$$

$$i_C = \frac{V_{in}(t)}{R}$$

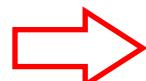


$$\boxed{V_{out}(t) = -\frac{1}{RC} \int_0^t V_{in}(t) dt + V_{out}(0)}$$

OP AMP differentiator

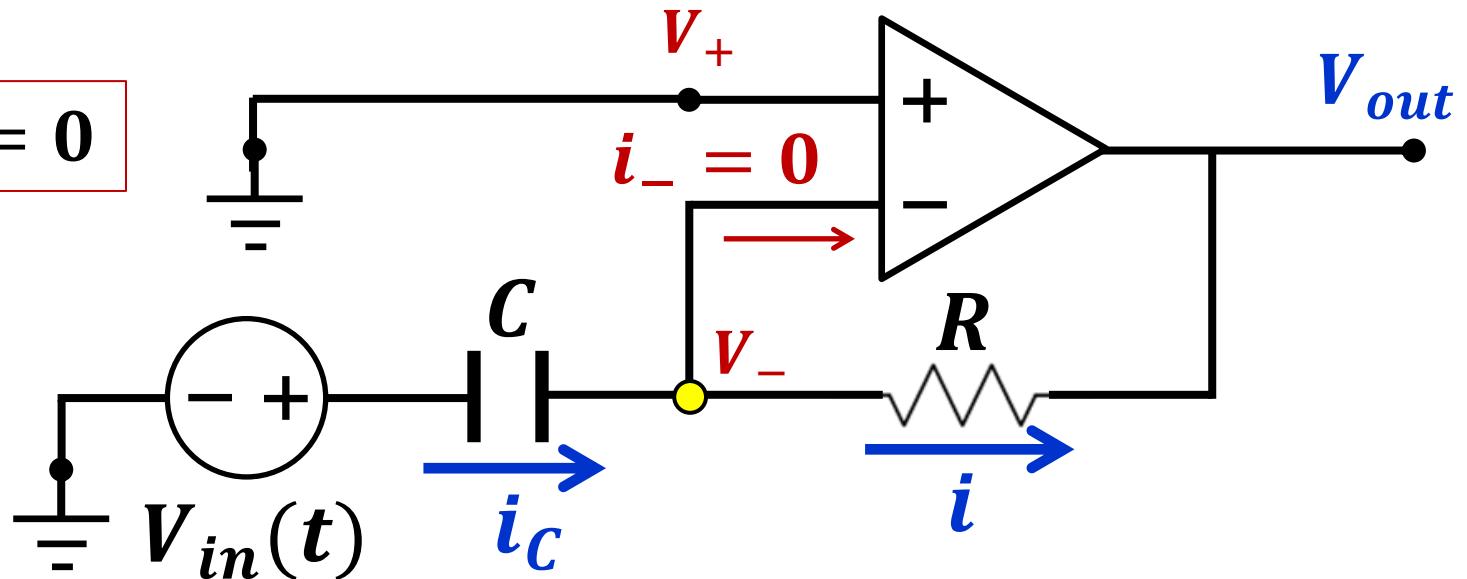

OP AMP differentiator

$$V_+ = V_- = 0$$

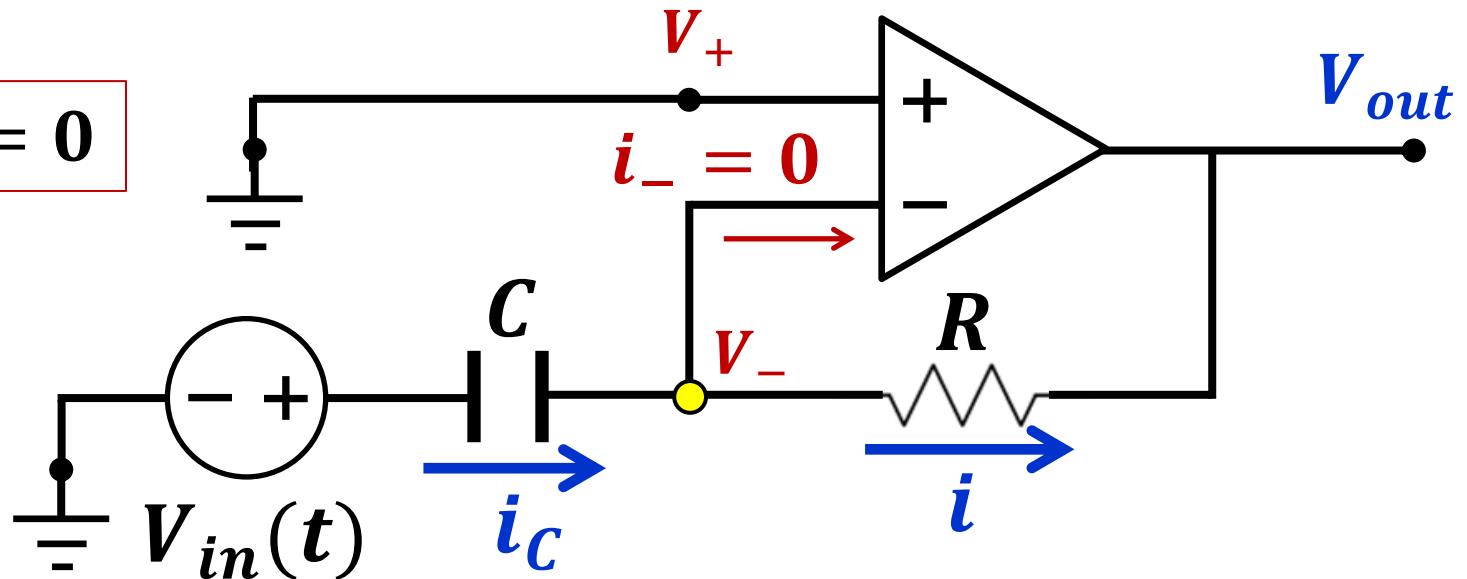


$$i_C = i = (V_{out} - V_-)/R$$

$$i_C = C \frac{d}{dt} V_{in}(t)$$

OP AMP differentiator


$$V_+ = V_- = 0$$

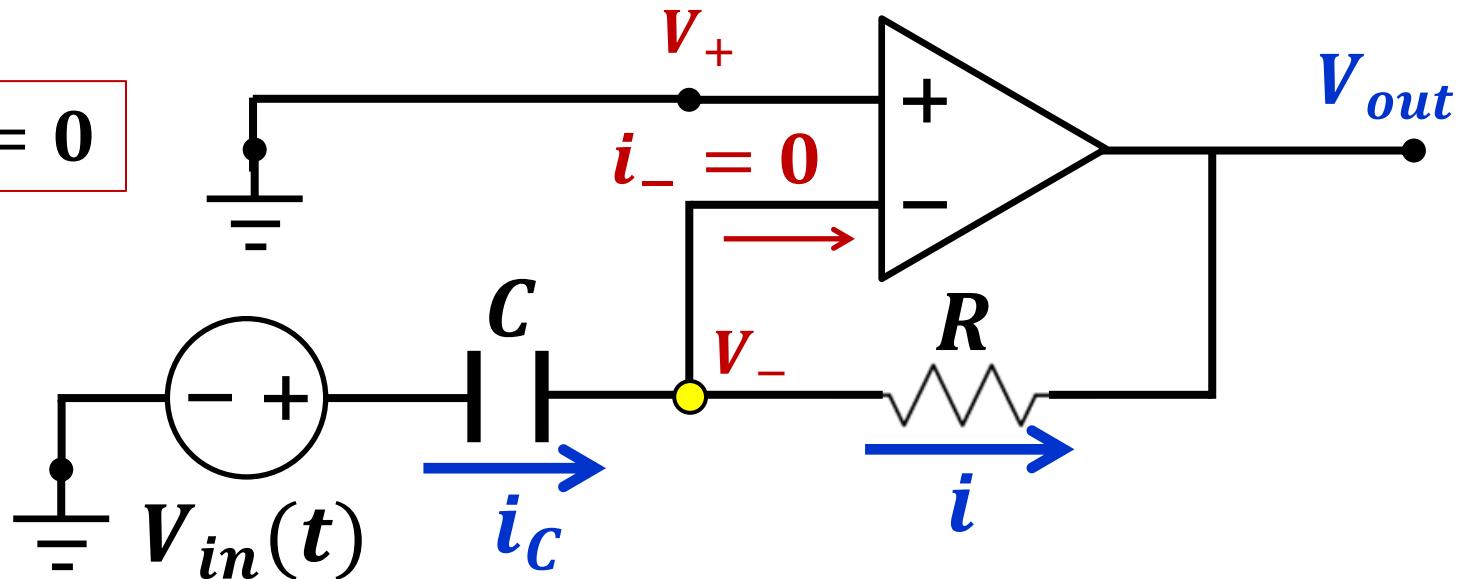

$$i_C = i = (V_{out} - V_-)/R$$

$$i_C = C \frac{d}{dt} V_{in}(t)$$

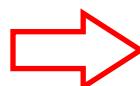
$$V_{out} = -R i_C = -RC \frac{d}{dt} V_{in}(t)$$




This basic circuit is typically sensitive to fluctuations and may not be very stable due to noise amplification.

Recall the basic Op Amp results

Inverting Amplifier

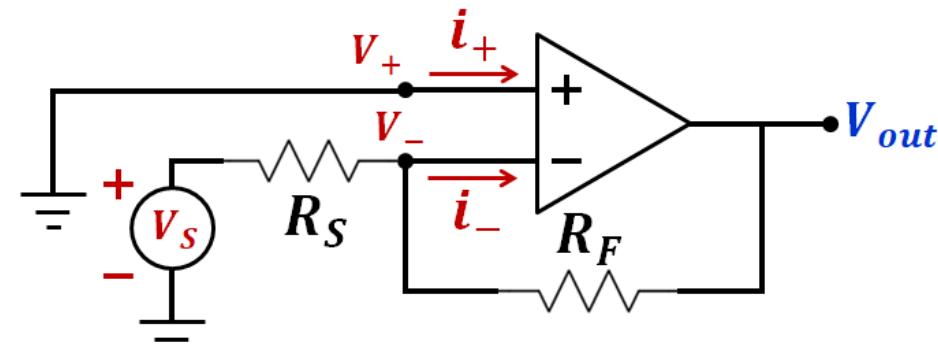

Non-inverting Amplifier

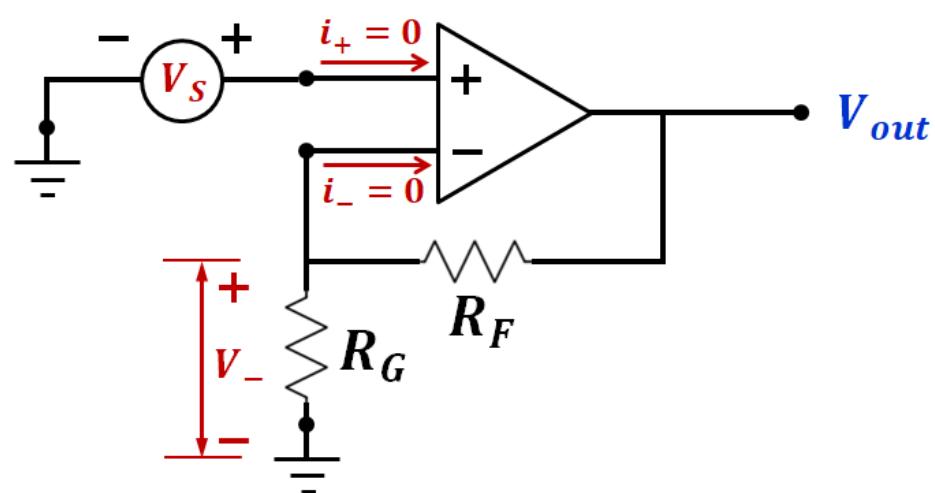

$$A_{VF} = -\frac{R_F}{R_S}$$

$$A_{VF} = 1 + \frac{R_F}{R_G}$$

Similar relationships are established in the OP AMP when simple resistors are replaced with impedances

- *Inverting amplifier*

$$A_{VF} = \frac{V_{out}}{V_S} = -\frac{Z_F}{Z_S}$$


- *Non-inverting amplifier*

$$A_{VF} = \frac{V_{out}}{V_S} = \frac{Z_G + Z_F}{Z_G} = 1 + \frac{Z_F}{Z_G}$$

OP AMP with impedances

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

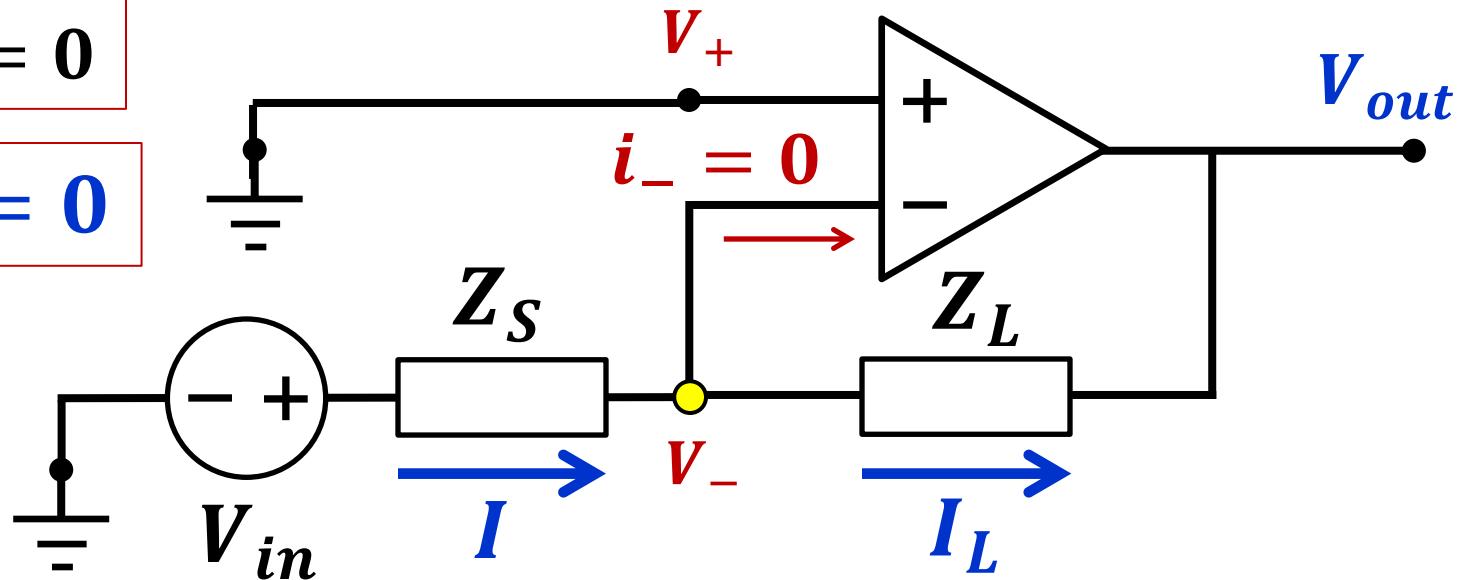


Now, voltages and currents are phasors

OP AMP with impedances


$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

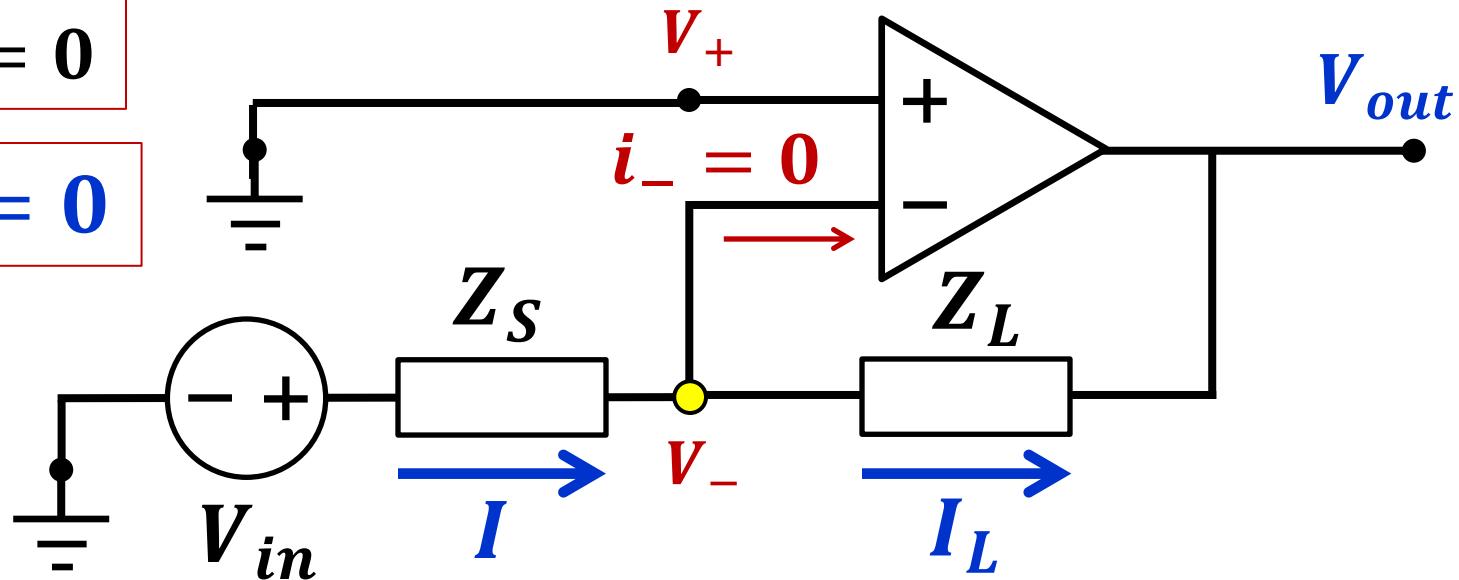

Now, voltages and currents are phasors
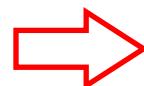
$$\frac{V_{in} - V_-}{Z_S} = \frac{V_- - V_{out}}{Z_L}$$




$$H(\omega) = \frac{V_{out}}{V_{in}} = -\frac{Z_L}{Z_S}$$

RC circuit – Inverting Op Amp

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

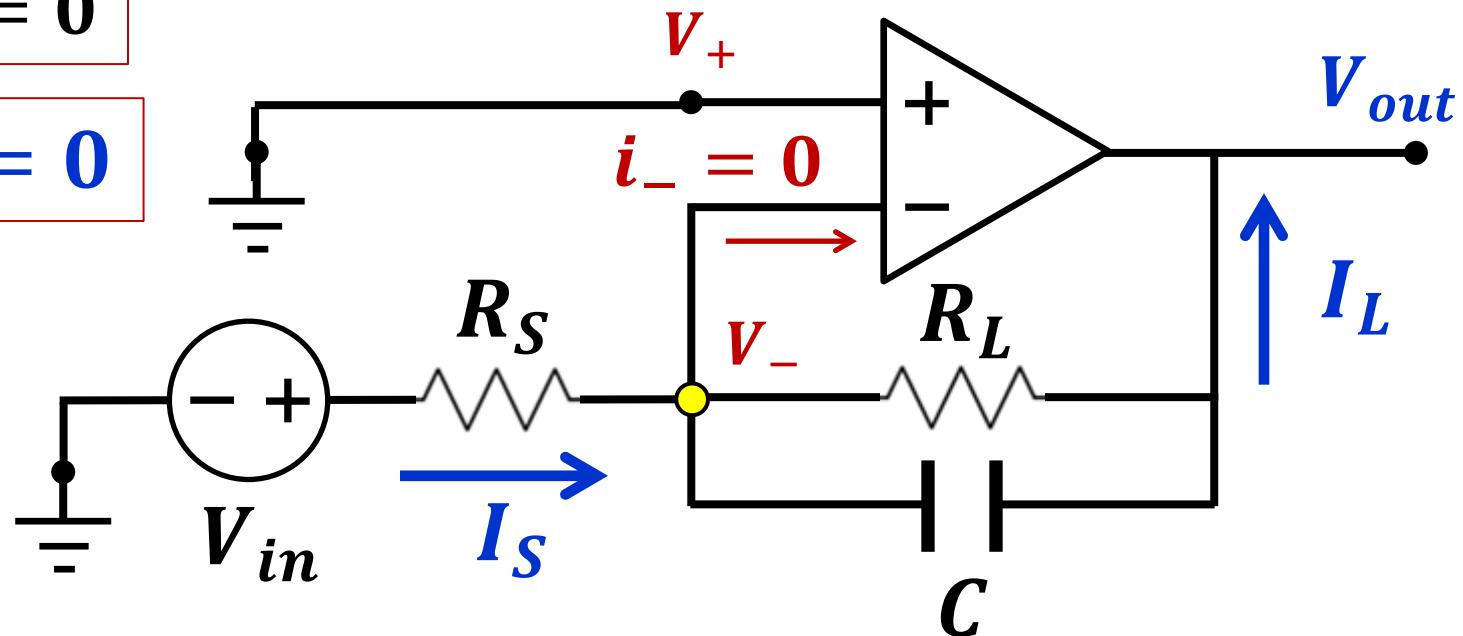

$$Z_S = R_S$$

$$Z_L = R_L // \frac{1}{j\omega C} = \left[\frac{1}{R_L} + j\omega C \right]^{-1} = \frac{R_L}{1 + j\omega R_L C}$$

V_{in} = sinusoidal

$$Z_S = R_S$$

$$Z_L = R_L // \frac{1}{j\omega C} = \left[\frac{1}{R_L} + j\omega C \right]^{-1} = \frac{R_L}{1 + j\omega R_L C}$$

$$H(\omega) = -\frac{Z_L}{Z_S} = -\frac{R_L/R_S}{1 + j\omega R_L C}$$

$$|H(\omega)| = \frac{R_L/R_S}{\sqrt{1 + \omega^2 R_L^2 C^2}}$$

$$|H(\omega)| = \frac{R_L/R_S}{\sqrt{1 + \omega^2 R_L^2 C^2}}$$

