

# **ECE 205 “Electrical and Electronics Circuits”**

**Fall 2023 – FINAL REVIEW**

MWF – 12:00pm

**Prof. Umberto Ravaioli**

2062 ECE Building

# Final Exam

**Exam is comprehensive. Duration: 1h 50m.**

**Expect 10 problems. Topics:**

- Circuit analysis (loop and/or node voltage) (1)**
- Equivalent circuit (Thevenin and/or Norton) (1)**
- Circuit analysis using phasors (1)**
- Transient analysis of RC and/or RL circuit (1)**
- Circuits with diodes and BJTs (2)**
- Digital logic (1)**
- RC Filters (1)**
- Operational Amplifier with resistors (1)**
- Operational Amplifier with impedance (1)**

- Help Sheet

**(a) Series:**  $R_{eq} = \sum_{k=1}^N R_k$

**(b) Parallel:**  $\frac{1}{R_{eq}} = \sum_{k=1}^N \frac{1}{R_k}$

$R_{eq} = R_1 + R_2$        $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

**OFF:**  $V_{BE} < V_{BE(on)}$ ,  $I_B = I_C = I_E = 0$

**FA:**  $V_{BE} = V_{BE(on)}$ ,  $I_C = \beta I_B$

**SAT:**  $V_{BE} = V_{BE(on)}$ ,  $V_{CE} = V_{CE(sat)}$

**Basic Gates:**

AND    NAND    OR    NOR    NOT

**Selected rules of boolean algebra:**

$(a.b).c = a.(b.c)$ ;  $(a + b) + c = a + (b + c)$

$a.b = b.a$ ;  $a + b = b + a$

$a.(b + c) = a.b + a.c$

**NOT(NOT(a)) = a**

$a + \bar{a}.b = a + b$ ;  $a + a.b = a$

**De Morgan Theorem**  $\overline{A + B} = \bar{A} \bar{B}$      $\overline{A B} = \bar{A} + \bar{B}$

**OFF:**  $V_D < V_{fr}$ ,  $I_D = 0$

**ON:**  $V_D = V_{fr}$ ,  $I_D > 0$

$i_C(t) = C \frac{dV_C(t)}{dt}$        $V_L(t) = L \frac{dI_L(t)}{dt}$

**RC and RL Circuits**

$\tau = RC$

$\tau = \frac{L}{R}$

**Voltage/Current Divider**

$V_1 = \frac{VR_1}{R_1 + R_2}$

$V_2 = \frac{VR_2}{R_1 + R_2}$

$I_1 = \frac{IR_2}{R_1 + R_2}$

$I_2 = \frac{IR_1}{R_1 + R_2}$

**Non-inverting amplifier:**  $H(\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1}$

**Inverting amplifier:**  $H(\omega) = \frac{V_{out}}{V_{in}} = -1 + \frac{Z_2}{Z_1}$


- Help sheet

**(a) Series:**


$$R_{eq} = \sum_{k=1}^N R_k$$

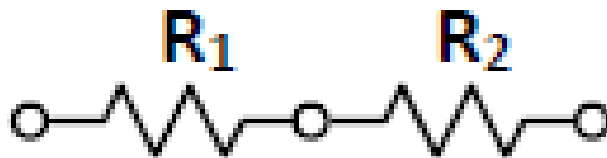**(b) Parallel:**

$$\frac{1}{R_{eq}} = \sum_{k=1}^N \frac{1}{R_k}$$




$$R_{eq} = R_1 + R_2$$

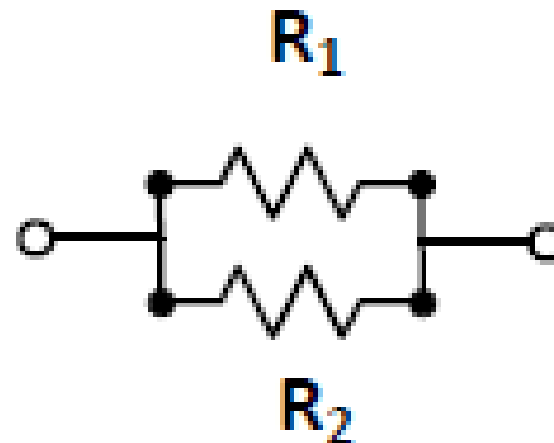


$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


- Help sheet

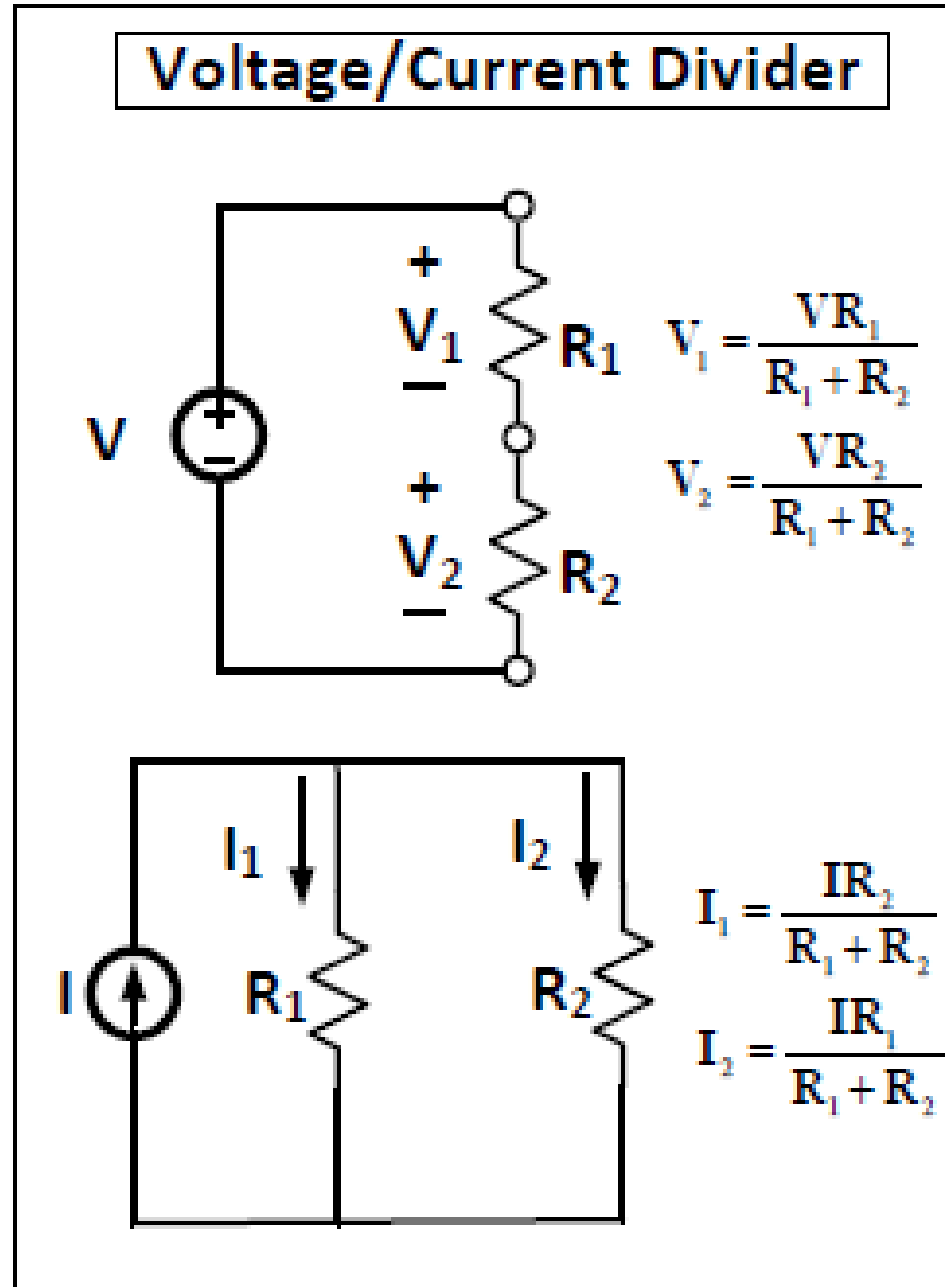


- Help sheet

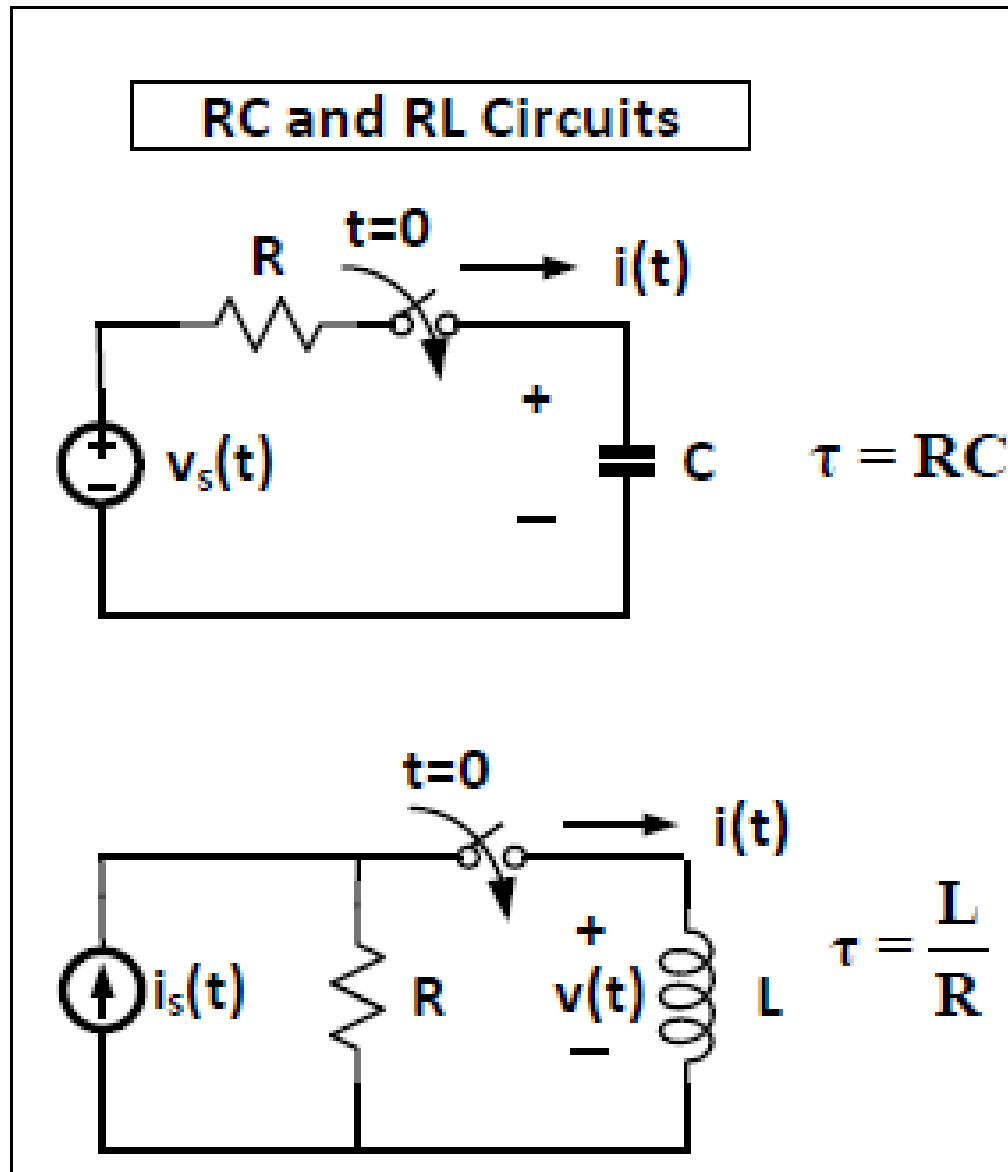

- Help sheet

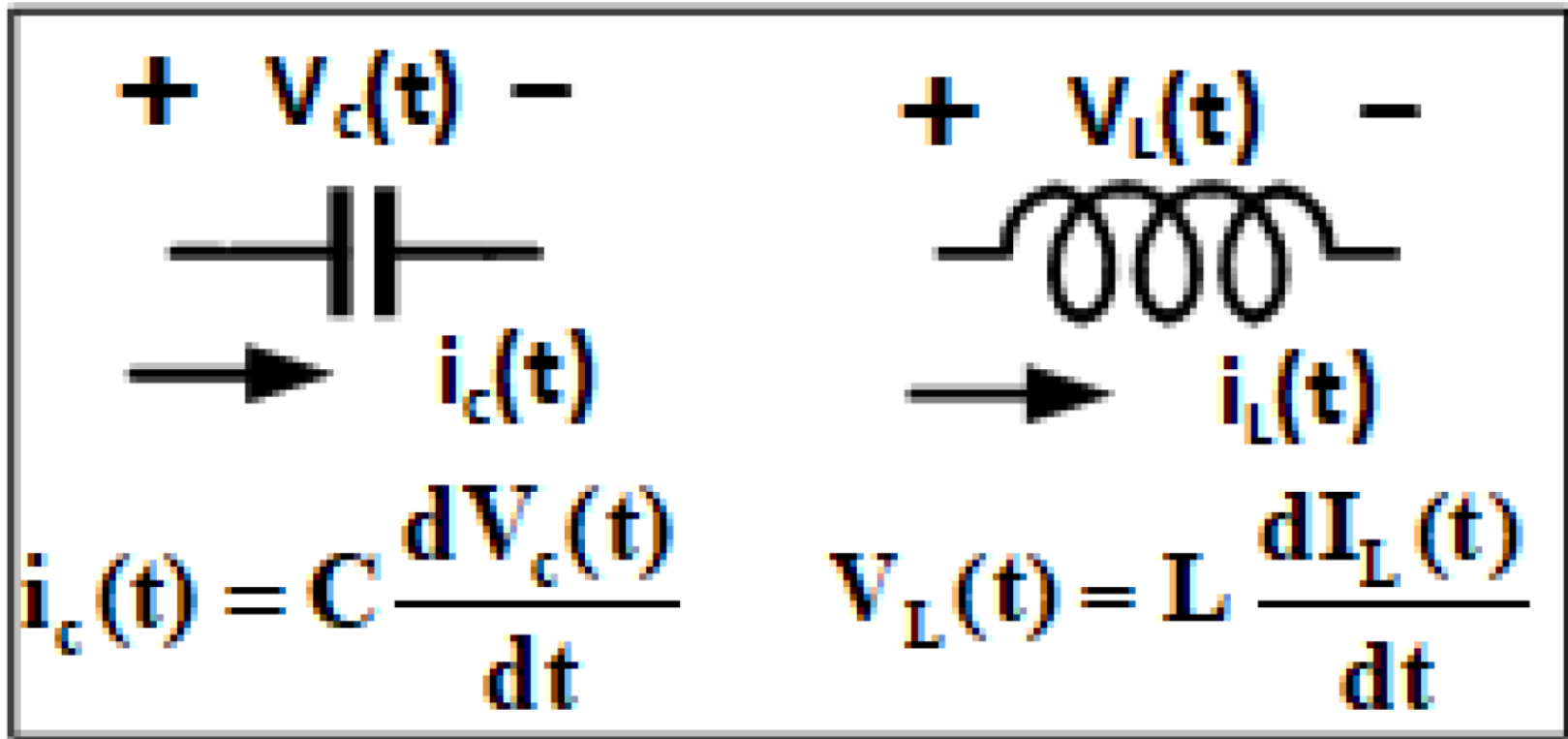


- Formula sheet

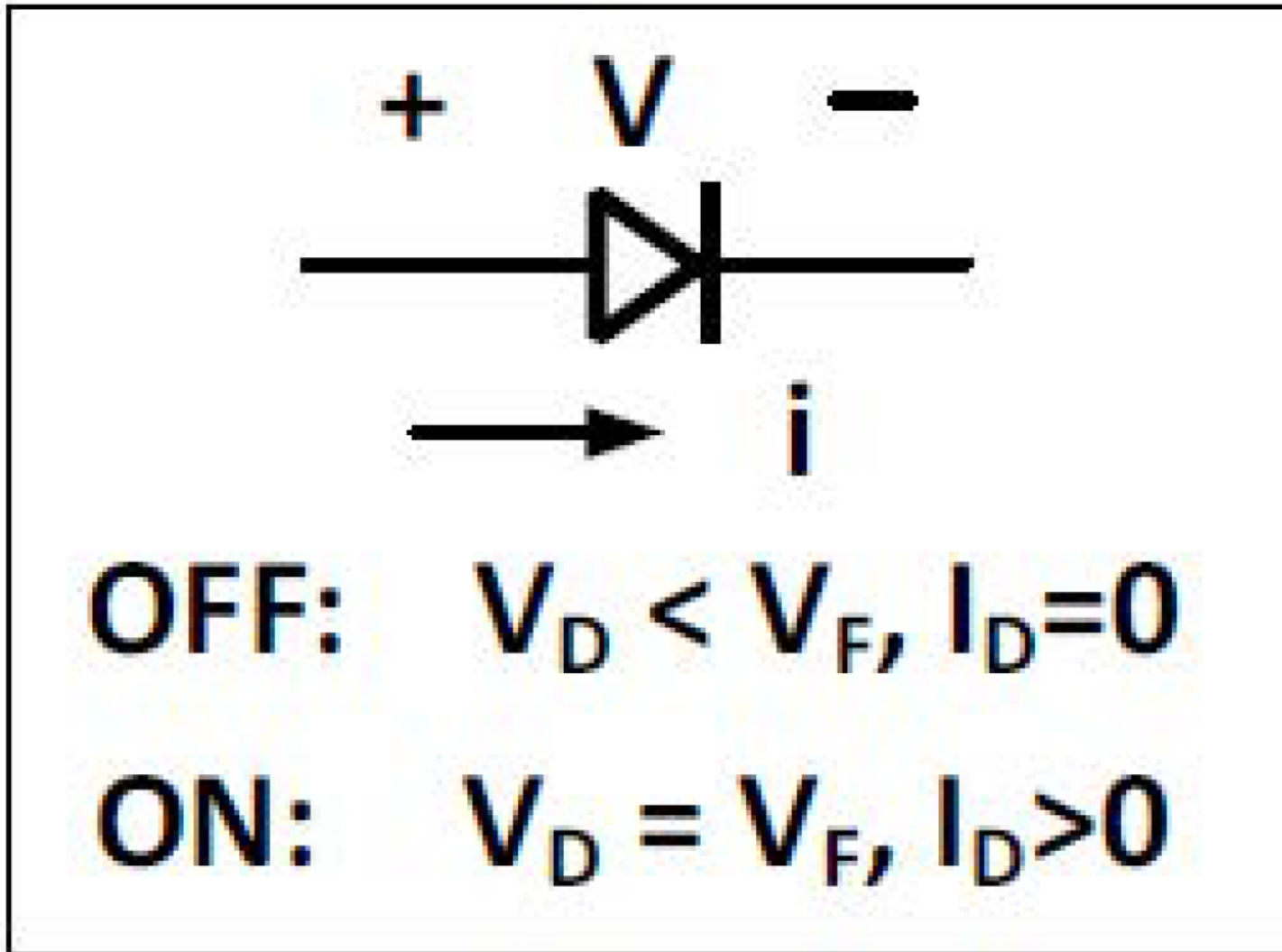



- Help sheet

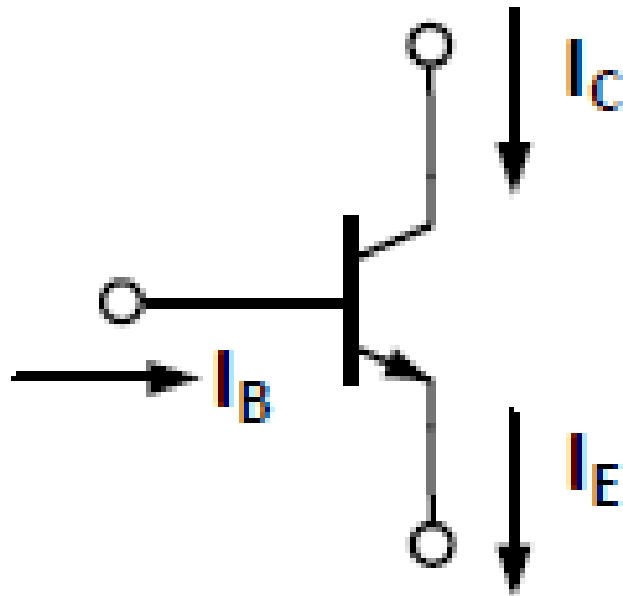


**OFF:**  $V_{BE} < V_{BE}(\text{on})$ ,  $I_B = I_C = I_E = 0$

**FA:**  $V_{BE} = V_{BE}(\text{on})$ ,  $I_C = \beta I_B$

**SAT:**  $V_{BE} = V_{BE}(\text{on})$ ,  $V_{CE} = V_{CE}(\text{sat})$

- Help sheet

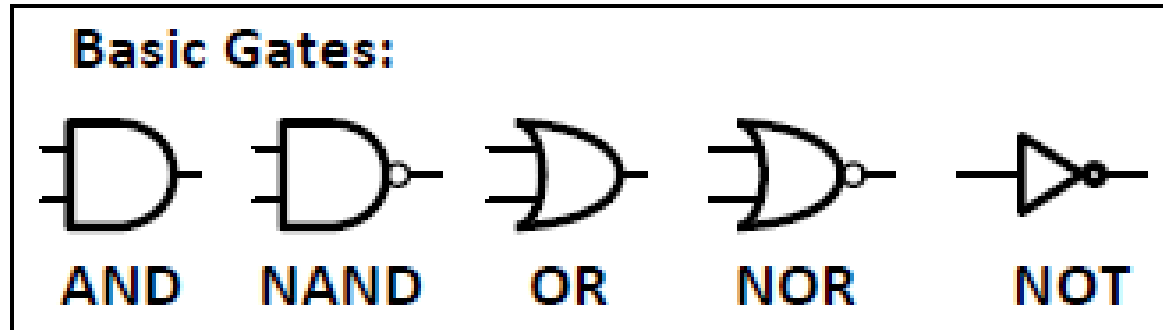

**Selected rules of boolean algebra:**

$$(a.b).c = a.(b.c); (a + b) + c = a + (b + c)$$

$$a.b = b.a ; a + b = b + a$$


$$a.(b + c) = a.b + a.c$$

$$\text{NOT}(\text{NOT}(a)) = a$$

$$a + \bar{a}.b = a + b ; a + a.b = a$$

De Morgan Theorem  $\overline{A + B} = \bar{A} \bar{B} \quad \overline{A B} = \bar{A} + \bar{B}$

- Help sheet

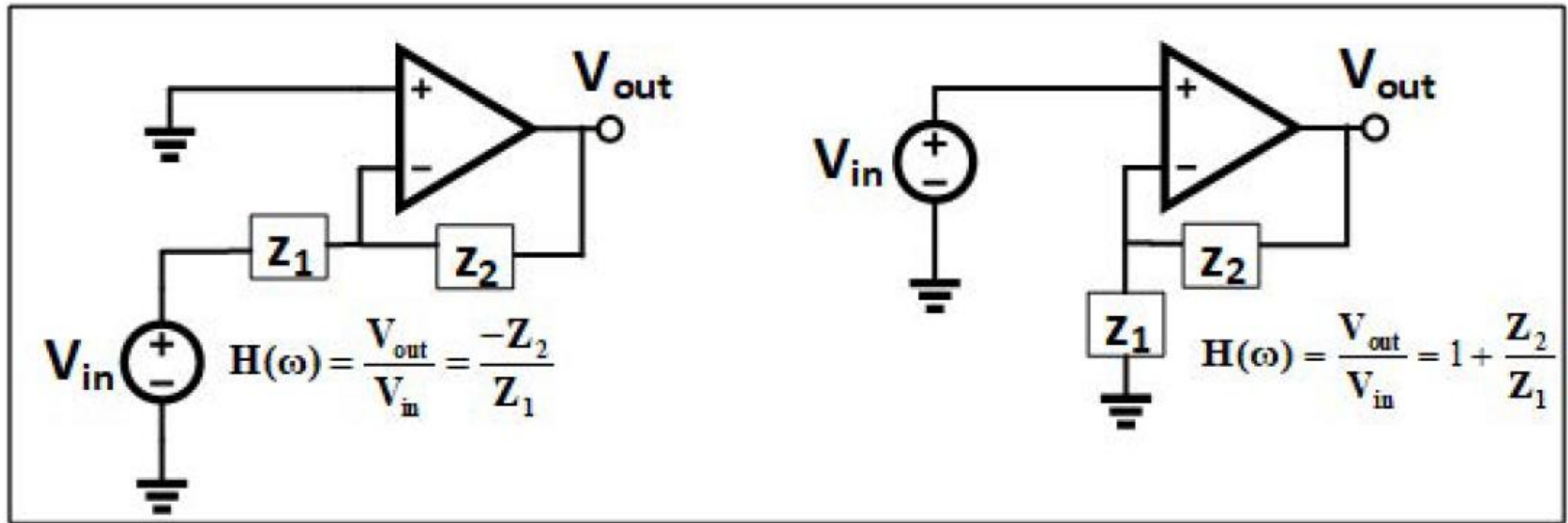

**You have plenty of time for the test. Verify your answers by plugging results back into the equations before pushing the “Grade” button.**

**Make sure you read the questions carefully (at least three times). Many of the mistakes you make are due to the fact that you solve a different problem than asked.**

**As last technical comments, let's revisit a few examples**


## BJT wired as a diode

$$-V_1 + R_1 I_1 + V_{BE} = 0$$

$$I_1 = \frac{V_1 - V_{BE}}{R_1}$$

As long as  $V_1 > V_{BE}(\text{on})$ , the BJT is in Forward-Active mode.

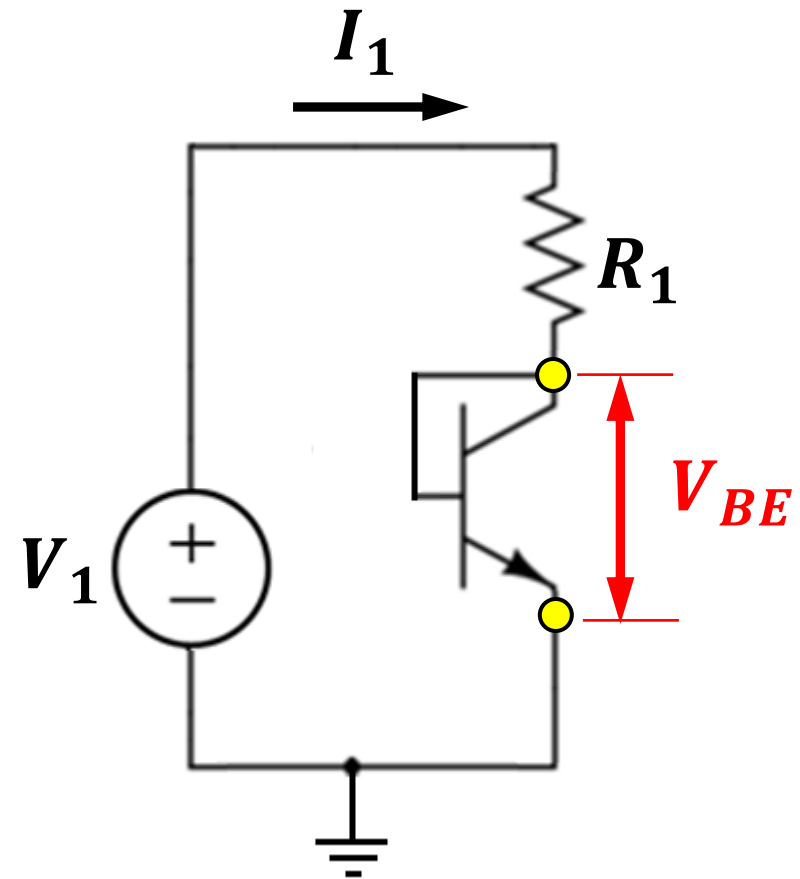
BJT's wired as in the diagram, are often adopted in integrated circuits, to obtain ultra-low leakage diodes and for design of circuits which are temperature compensating.



$$\beta = 100$$

$$V_{BE}(on) = 0.7V$$

$$V_{CE}(sat) = 0.2V$$

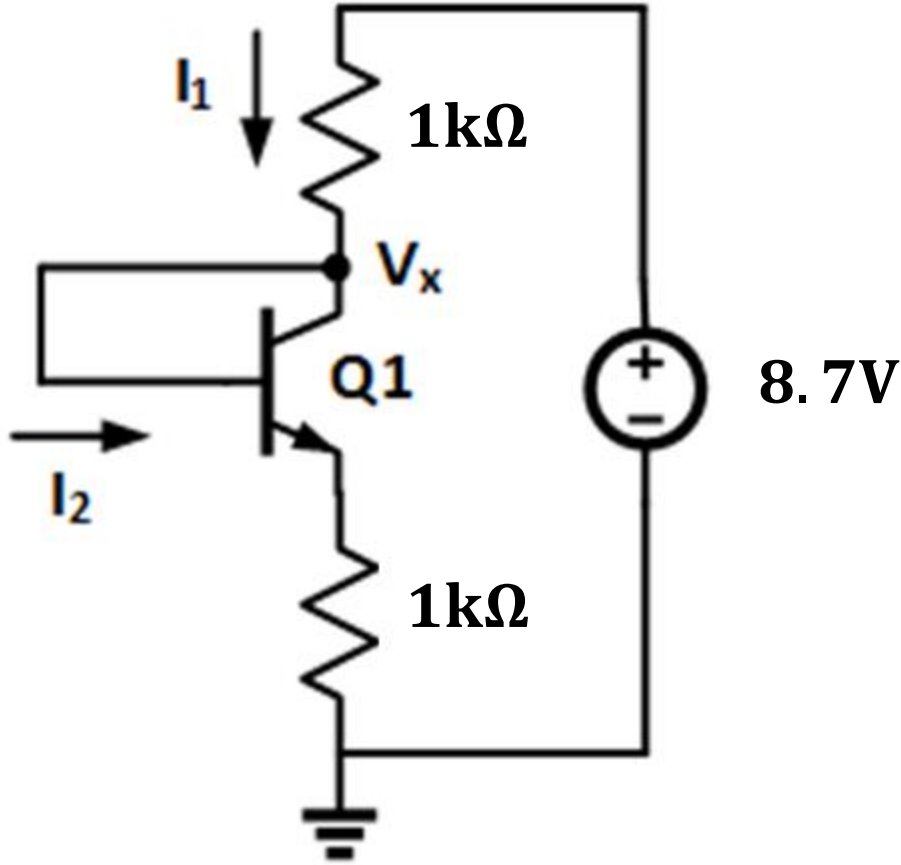


$$\beta = 100$$

$$V_{BE}(on) = 0.7V$$

$$V_{CE}(sat) = 0.2V$$

Assume: BJT ON

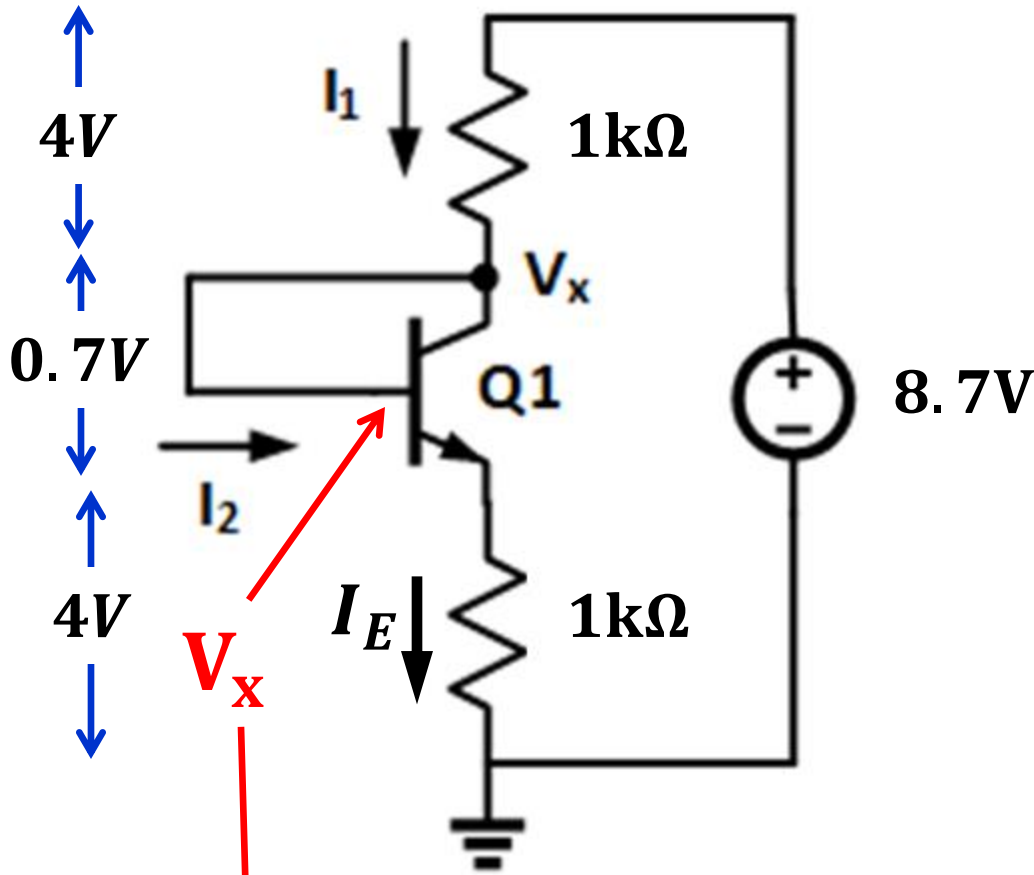

$$V_{BE} = V_{CE} = 0.7V$$


$$V_x = V_{CE} + 4V = 4.7V$$



$$\beta = 100$$

$$V_{BE}(on) = 0.7V$$

$$V_{CE}(sat) = 0.2V$$

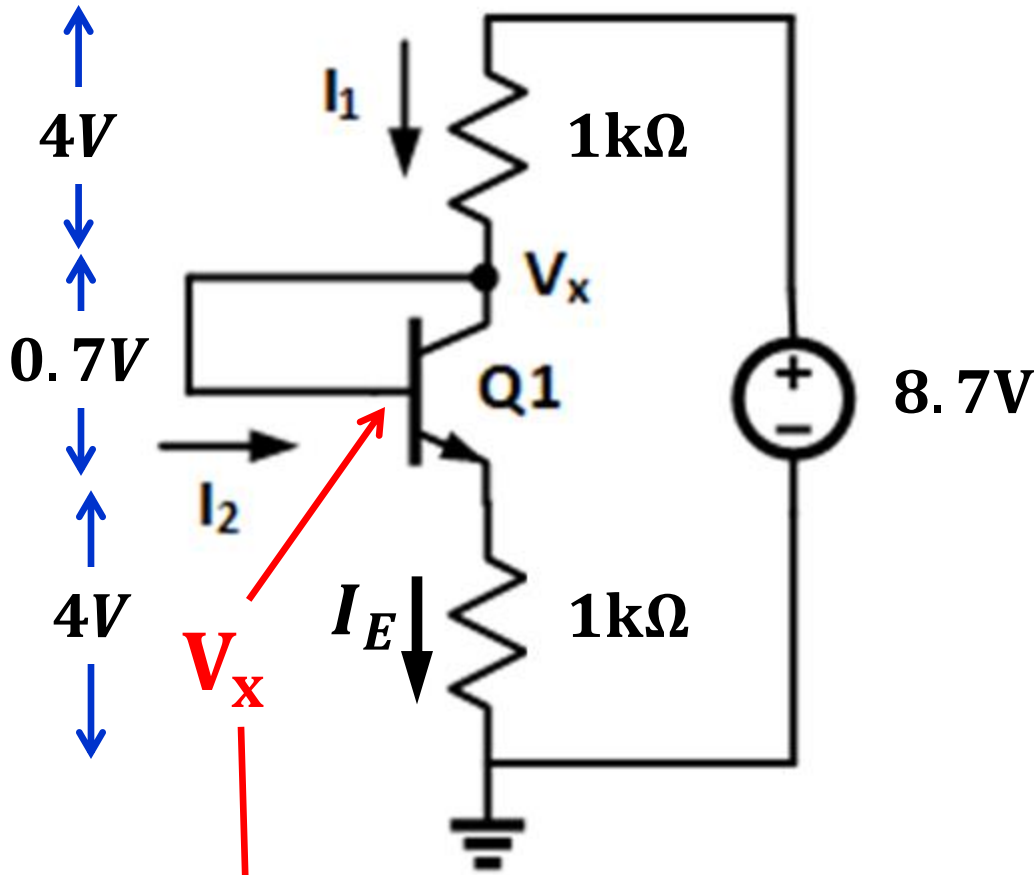

Assume: BJT ON

$$\begin{aligned} I_1 &= I_C + I_2 \\ &= I_C + I_B \end{aligned}$$


$$I_1 = I_E$$

$$\begin{aligned} I_1 &= 1k\Omega \times 4V \\ &= 4mA \end{aligned}$$

$$\begin{aligned} I_E &= 1k\Omega \times 4V \\ &= 4mA \end{aligned}$$

$$V_{BE} = V_{CE} = 0.7V$$

$$V_x = V_{CE} + 4V = 4.7V$$

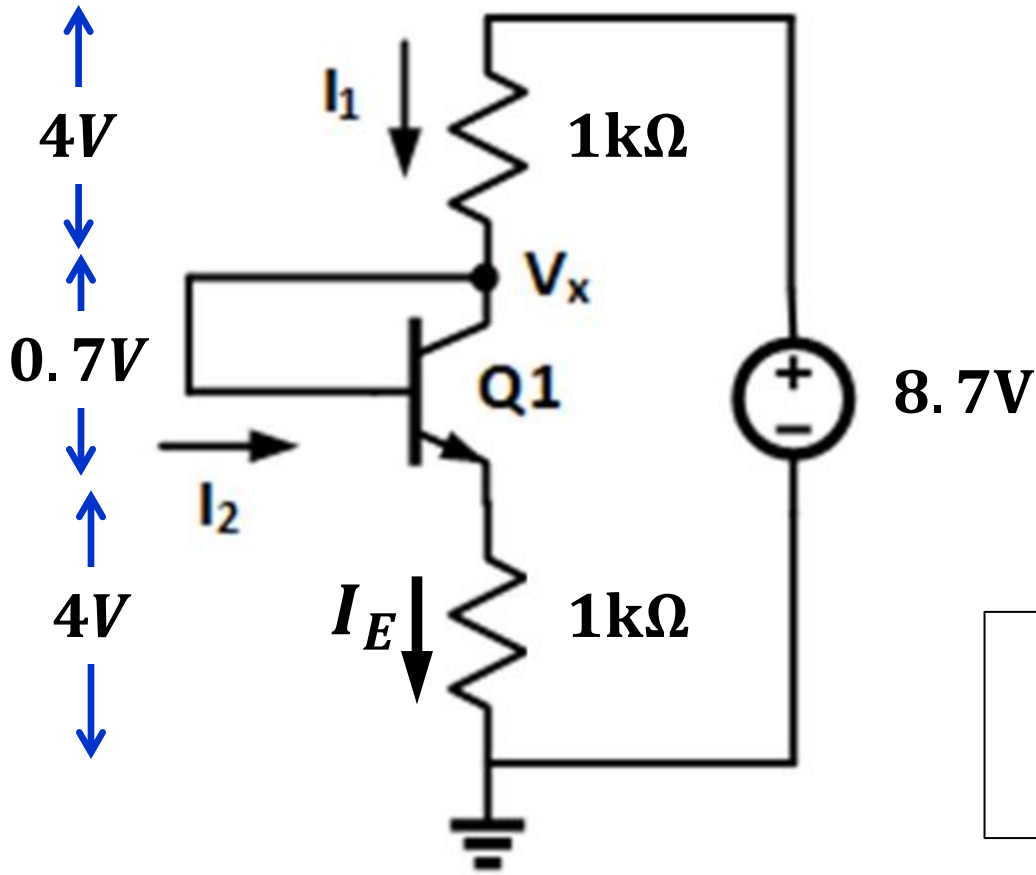

$$\beta = 100$$

$$V_{BE}(on) = 0.7V$$

$$V_{CE}(sat) = 0.2V$$

$$I_1 = I_E = 4mA$$

$$V_{CE} = 0.7V$$

What are  $I_B$  and  $I_C$ ?

$V_{CE} > V_{CE}(sat)$   
Forward-Active Mode


$$I_E = I_B + I_C = I_B + \beta I_B = 101I_B$$

$$I_B = 4m/101 = 39.6\mu A$$

$$I_C = 100I_B = 3.96mA$$


# OP AMP Current Source

$$V_+ = V_- = 0$$

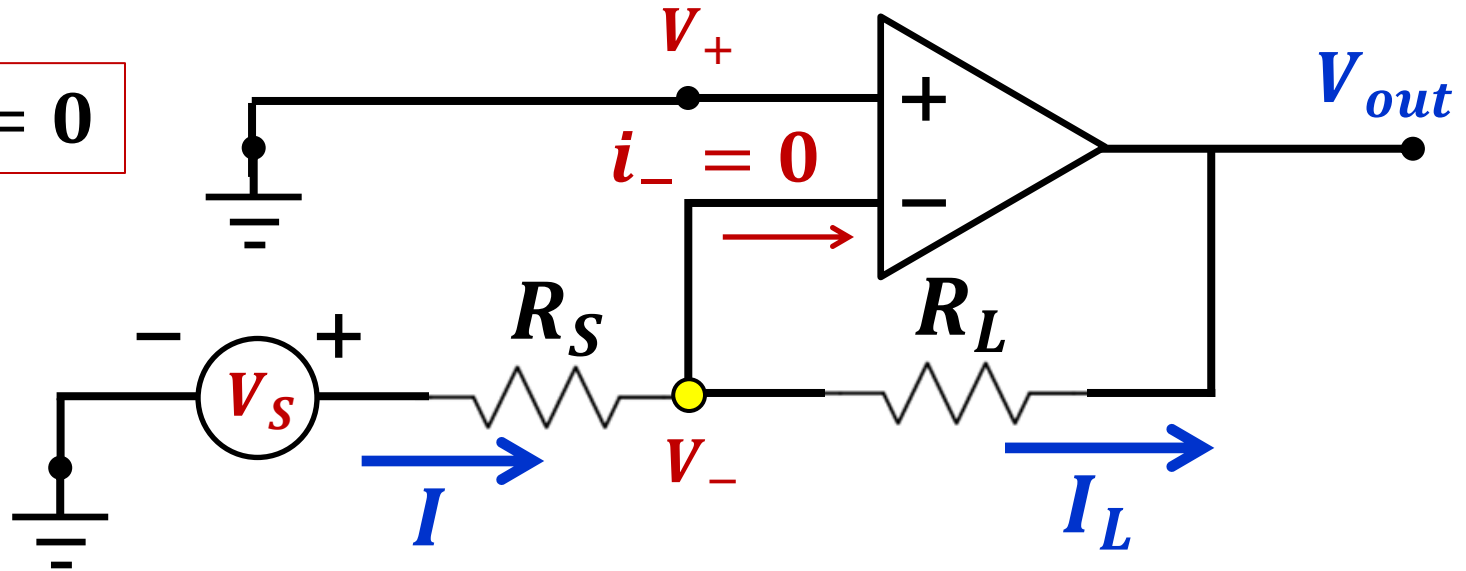

# OP AMP Current Source

$$V_+ = V_- = 0$$

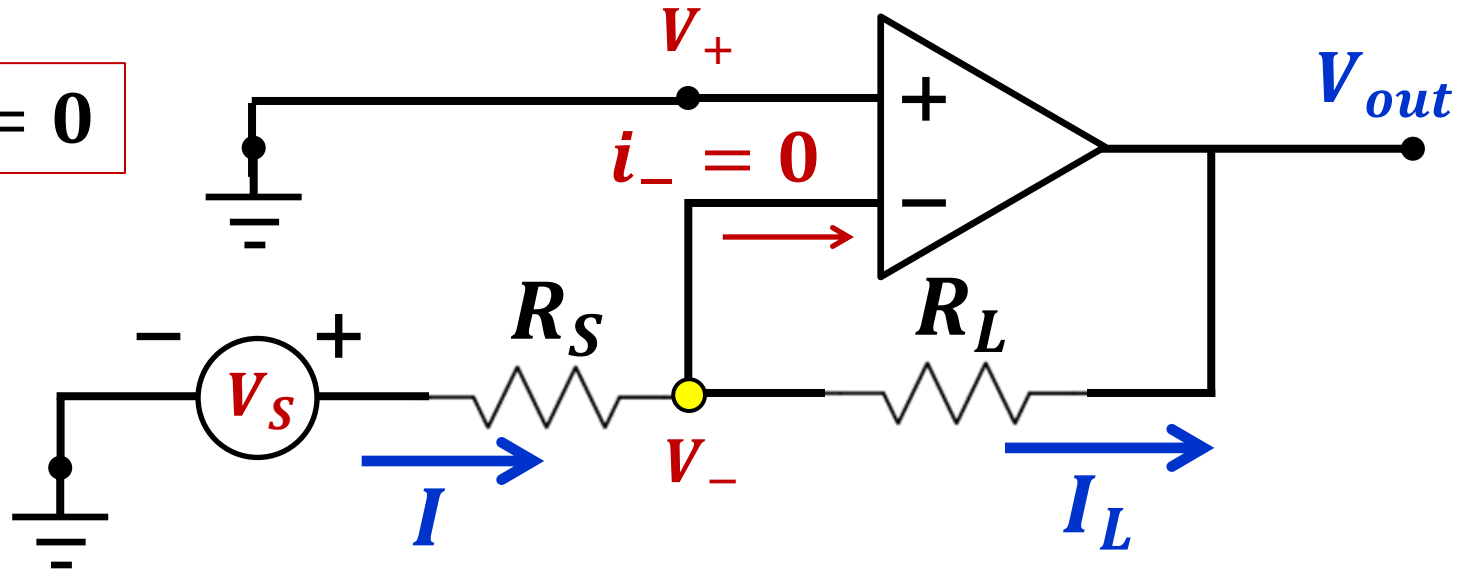


$$I = \overset{=0}{i_-} + I_L = I_L$$

$$I_L = \frac{V_S - V_-}{R_S} = \frac{V_S}{R_S}$$

# OP AMP Current Source

$$V_+ = V_- = 0$$

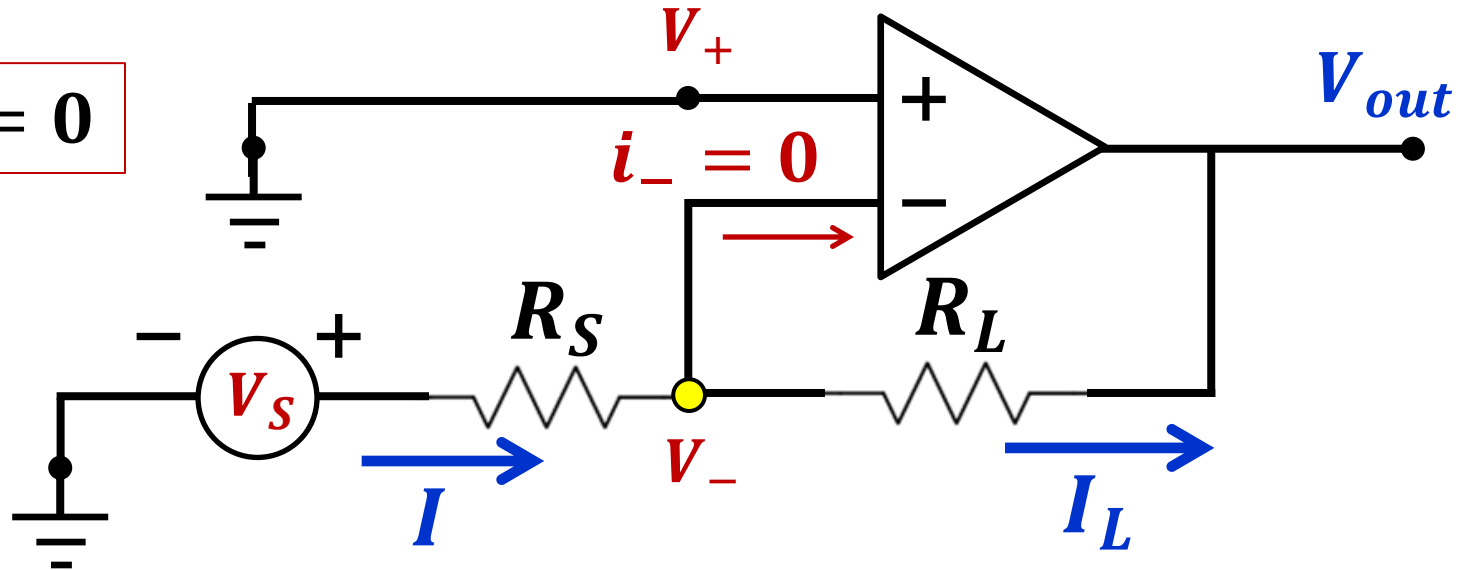

$$I = \overset{=0}{i_-} + I_L = I_L$$

$$I_L = \frac{V_S - V_-}{R_S} = \frac{V_S}{R_S}$$

Example:  $V_S = 1\text{V}$ ;  $R_S = 1\text{k}\Omega$



$$I_L = \frac{1 - 0}{1\text{k}\Omega} = 1\text{mA}$$

Independent of  $R_L$


# Example – Four equal resistors in input

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

$$R = 1\text{k}\Omega$$

$$V_i \Big|_{\text{max}} = 1\text{V}$$

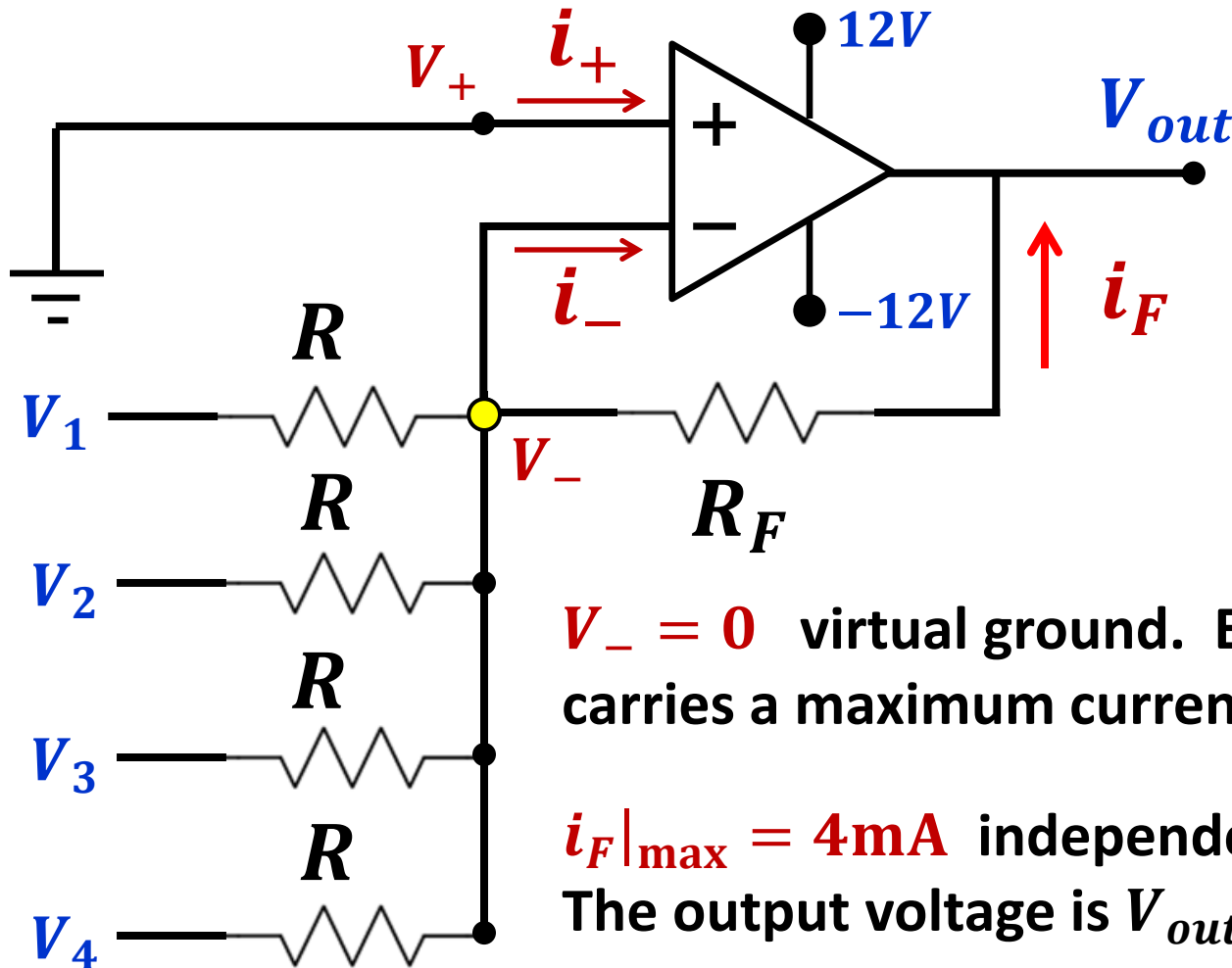

$V_- = 0$  virtual ground. Each input resistor carries a maximum current  $i_k \Big|_{\text{max}} = 1\text{mA}$

$i_F \Big|_{\text{max}} = 4\text{mA}$  independent of  $R_F$ .

The output voltage is  $V_{out} = R_F \times i_F \Big|_{\text{max}}$


# Example – Equal input resistors

$$V_+ = V_- = 0$$

$$i_+ = i_- = 0$$

$$R = 1\text{k}\Omega$$

$$V_i \Big|_{\text{max}} = 1\text{V}$$

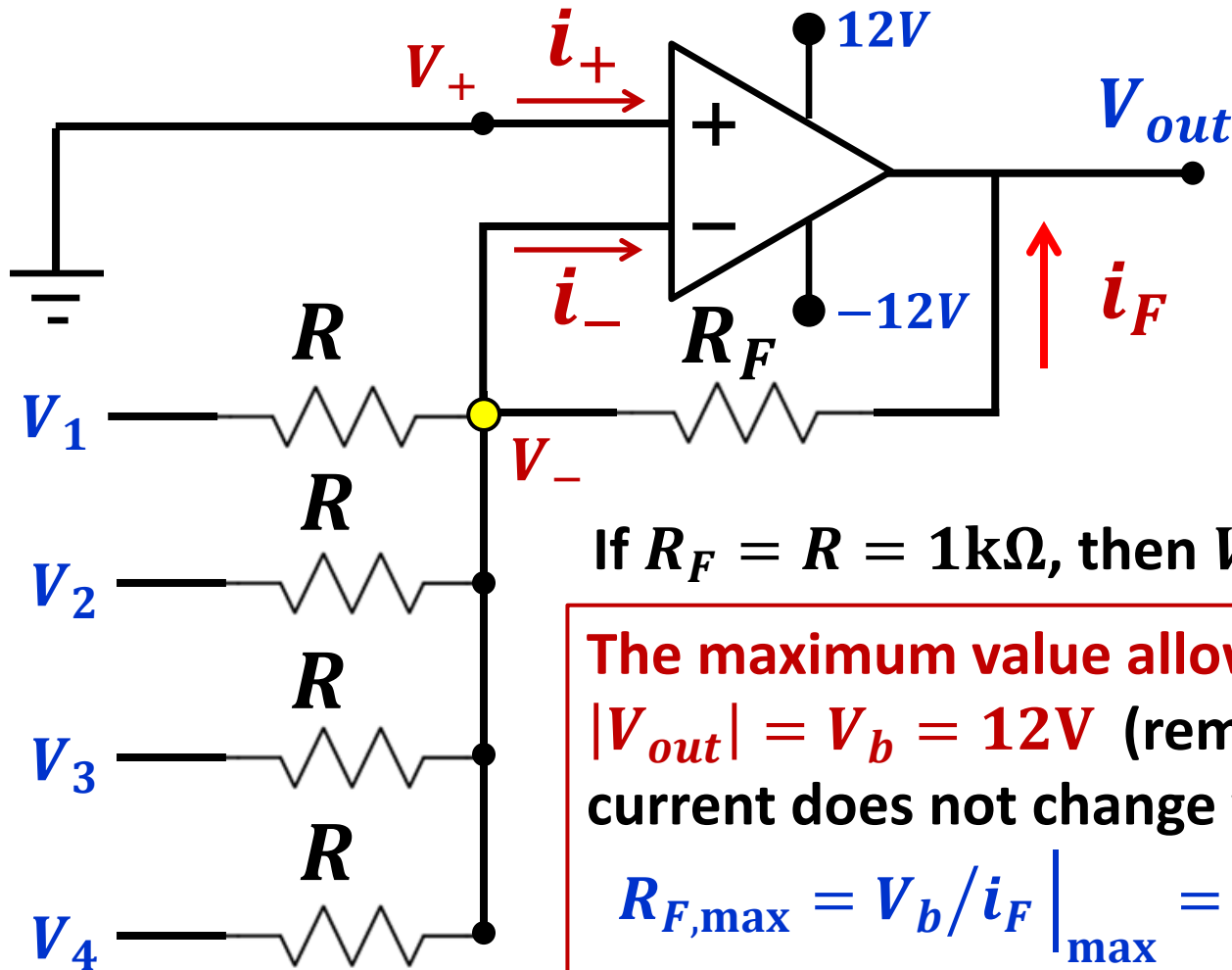

If  $R_F = R = 1\text{k}\Omega$ , then  $V_{out} = 4\text{V}$  at most.

The maximum value allowed for  $R_F$  is when  $|V_{out}| = V_b = 12\text{V}$  (remember, the input current does not change with  $R_F$ )

$$R_{F,\text{max}} = V_b / i_F \Big|_{\text{max}} = 12\text{V} / 4\text{mA} = 3\text{k}\Omega$$

# ICES Survey Online

There is still time to complete the course evaluation

**[go.illinois.edu/ices-online](https://go.illinois.edu/ices-online)**

or you can use the link sent to you by email.

The survey closes soon.



# QUESTIONS